

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 1

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $36.0\Omega + j \cdot 42.6\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.30\text{dB}$.
 - If the power applied at the input port is 7.9 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 66Ω resistor series with a 0.637 nH inductor, at 6.8 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 515 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 23.7\text{dB}$ and noise factor $F_1 = 3.90\text{dB}$), A2 ($G_2 = 24.8\text{dB}$, $F_2 = 4.23\text{dB}$) and A3 ($G_3 = 21.1\text{dB}$, $F_3 = 5.65\text{dB}$). The order in which you must connect the amplifiers is A2, A1, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.2

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $56.1\Omega - j \cdot 61.4\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.80\text{dB}$.
 - If the power applied at the input port is 7.0 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 72Ω resistor series with a 1.615 nH inductor, at 7.3 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 315 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 18.8\text{dB}$ and noise factor $F_1 = 3.17\text{dB}$), A2 ($G_2 = 22.7\text{dB}$, $F_2 = 4.12\text{dB}$) and A3 ($G_3 = 23.4\text{dB}$, $F_3 = 5.18\text{dB}$). The order in which you must connect the amplifiers is A2, A3, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A2, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 3

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $45.6\Omega - j \cdot 36.0\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 4.10\text{dB}$.
 - If the power applied at the input port is 4.8 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 60Ω resistor series with a 1.220 nH inductor, at 8.8 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 560 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 23.4\text{dB}$ and noise factor $F_1 = 3.81\text{dB}$), A2 ($G_2 = 24.8\text{dB}$, $F_2 = 4.83\text{dB}$) and A3 ($G_3 = 19.1\text{dB}$, $F_3 = 5.30\text{dB}$). The order in which you must connect the amplifiers is A3, A1, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A3, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 4

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $32.5\Omega + j \cdot 33.1\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.60\text{dB}$.
 - If the power applied at the input port is 5.9 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 73Ω resistor paralel with a 0.544 pF capacitor, at 7.0 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 575 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 19.5\text{dB}$ and noise factor $F_1 = 3.88\text{dB}$), A2 ($G_2 = 19.7\text{dB}$, $F_2 = 4.25\text{dB}$) and A3 ($G_3 = 24.6\text{dB}$, $F_3 = 5.46\text{dB}$). The order in which you must connect the amplifiers is A2, A1, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.5

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $60.9\Omega + j \cdot 54.2\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 4.70\text{dB}$.
 - If the power applied at the input port is 8.7 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 25Ω resistor series with a 0.474 nH inductor, at 9.9 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 325 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 24.0\text{dB}$ and noise factor $F_1 = 3.01\text{dB}$), A2 ($G_2 = 15.9\text{dB}$, $F_2 = 4.20\text{dB}$) and A3 ($G_3 = 21.8\text{dB}$, $F_3 = 5.64\text{dB}$). The order in which you must connect the amplifiers is A2, A3, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A2, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 6

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $52.4\Omega + j \cdot 57.7\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.75\text{dB}$.
 - If the power applied at the input port is 5.3 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 55Ω resistor paralel with a 1.133 nH inductor, at 9.6 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 455 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 17.0\text{dB}$ and noise factor $F_1 = 3.63\text{dB}$), A2 ($G_2 = 18.6\text{dB}$, $F_2 = 4.37\text{dB}$) and A3 ($G_3 = 23.6\text{dB}$, $F_3 = 5.31\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A3, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.7

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $42.4\Omega + j \cdot 55.7\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 8.05\text{dB}$.
 - If the power applied at the input port is 2.4 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 63Ω resistor series with a 0.302 pF capacitor, at 7.8 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 535 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 23.4\text{dB}$ and noise factor $F_1 = 3.55\text{dB}$), A2 ($G_2 = 15.3\text{dB}$, $F_2 = 4.83\text{dB}$) and A3 ($G_3 = 16.4\text{dB}$, $F_3 = 5.13\text{dB}$). The order in which you must connect the amplifiers is A3, A1, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 8

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $48.1\Omega - j\cdot 45.6\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.75\text{dB}$.
 - If the power applied at the input port is 2.6 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 25Ω resistor paralel with a 0.428 pF capacitor, at 6.7 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 530 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 18.4\text{dB}$ and noise factor $F_1 = 3.24\text{dB}$), A2 ($G_2 = 18.6\text{dB}$, $F_2 = 4.62\text{dB}$) and A3 ($G_3 = 20.7\text{dB}$, $F_3 = 5.59\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 9

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $33.6\Omega - j \cdot 58.3\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 6.75\text{dB}$.
 - If the power applied at the input port is 5.5 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 74Ω resistor series with a 0.828 pF capacitor, at 6.7 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 400 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 20.7\text{dB}$ and noise factor $F_1 = 3.52\text{dB}$), A2 ($G_2 = 19.9\text{dB}$, $F_2 = 4.29\text{dB}$) and A3 ($G_3 = 21.0\text{dB}$, $F_3 = 5.86\text{dB}$). The order in which you must connect the amplifiers is A1, A3, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 10

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $37.8\Omega + j \cdot 44.1\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.60\text{dB}$.
 - If the power applied at the input port is 9.5 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 57Ω resistor paralel with a 0.412 pF capacitor, at 8.3 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 370 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 20.8\text{dB}$ and noise factor $F_1 = 3.35\text{dB}$), A2 ($G_2 = 19.2\text{dB}$, $F_2 = 4.34\text{dB}$) and A3 ($G_3 = 16.8\text{dB}$, $F_3 = 5.20\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 11

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $49.2\Omega - j \cdot 35.9\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.20\text{dB}$.
 - If the power applied at the input port is 8.3 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 50Ω resistor series with a 0.643 nH inductor, at 7.2 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 585 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 18.8\text{dB}$ and noise factor $F_1 = 3.19\text{dB}$), A2 ($G_2 = 15.4\text{dB}$, $F_2 = 4.57\text{dB}$) and A3 ($G_3 = 17.9\text{dB}$, $F_3 = 5.09\text{dB}$). The order in which you must connect the amplifiers is A1, A3, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 12

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $42.5\Omega - j \cdot 55.8\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 6.45\text{dB}$.
 - If the power applied at the input port is 8.1 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 58Ω resistor series with a 0.843 pF capacitor, at 6.8 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 300 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 16.2\text{dB}$ and noise factor $F_1 = 3.16\text{dB}$), A2 ($G_2 = 23.1\text{dB}$, $F_2 = 4.46\text{dB}$) and A3 ($G_3 = 22.0\text{dB}$, $F_3 = 5.80\text{dB}$). The order in which you must connect the amplifiers is A2, A1, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A2, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 13

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $63.3\Omega - j \cdot 52.3\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 6.55\text{dB}$.
 - If the power applied at the input port is 7.3 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 33Ω resistor paralel with a 0.342 pF capacitor, at 9.1 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 585 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 15.2\text{dB}$ and noise factor $F_1 = 3.52\text{dB}$), A2 ($G_2 = 23.3\text{dB}$, $F_2 = 4.37\text{dB}$) and A3 ($G_3 = 23.1\text{dB}$, $F_3 = 5.49\text{dB}$). The order in which you must connect the amplifiers is A1, A3, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 14

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $61.1\Omega - j\cdot 60.9\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.60\text{dB}$.
 - If the power applied at the input port is 7.0 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 57Ω resistor paralel with a 0.618 nH inductor, at 8.8 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 580 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 15.4\text{dB}$ and noise factor $F_1 = 3.44\text{dB}$), A2 ($G_2 = 21.5\text{dB}$, $F_2 = 4.13\text{dB}$) and A3 ($G_3 = 21.3\text{dB}$, $F_3 = 5.60\text{dB}$). The order in which you must connect the amplifiers is A3, A1, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A2, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 15

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $58.5\Omega - j \cdot 51.8\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.25\text{dB}$.
 - If the power applied at the input port is 7.6 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 27Ω resistor series with a 0.536 pF capacitor, at 8.3 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 305 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 24.2\text{dB}$ and noise factor $F_1 = 3.58\text{dB}$), A2 ($G_2 = 19.7\text{dB}$, $F_2 = 4.54\text{dB}$) and A3 ($G_3 = 21.0\text{dB}$, $F_3 = 5.82\text{dB}$). The order in which you must connect the amplifiers is A2, A3, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A2, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 16

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $31.5\Omega + j \cdot 41.3\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.55\text{dB}$.
 - If the power applied at the input port is 9.5 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 54Ω resistor paralel with a 0.557 nH inductor, at 8.3 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 500 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 18.3\text{dB}$ and noise factor $F_1 = 3.73\text{dB}$), A2 ($G_2 = 18.7\text{dB}$, $F_2 = 4.31\text{dB}$) and A3 ($G_3 = 24.2\text{dB}$, $F_3 = 5.33\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A3, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.17

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $63.9\Omega + j\cdot 40.8\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.45\text{dB}$.
 - If the power applied at the input port is 4.4 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 41Ω resistor paralel with a 0.349 pF capacitor, at 7.2 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 595 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 24.3\text{dB}$ and noise factor $F_1 = 3.33\text{dB}$), A2 ($G_2 = 20.5\text{dB}$, $F_2 = 4.39\text{dB}$) and A3 ($G_3 = 20.0\text{dB}$, $F_3 = 5.90\text{dB}$). The order in which you must connect the amplifiers is A2, A3, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A1, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 18

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $64.6\Omega + j \cdot 35.5\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.00\text{dB}$.
 - If the power applied at the input port is 4.1 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 36Ω resistor paralel with a 0.972 nH inductor, at 9.9 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 345 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 21.4\text{dB}$ and noise factor $F_1 = 3.46\text{dB}$), A2 ($G_2 = 19.1\text{dB}$, $F_2 = 4.07\text{dB}$) and A3 ($G_3 = 21.6\text{dB}$, $F_3 = 5.39\text{dB}$). The order in which you must connect the amplifiers is A1, A3, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A1, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 19

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $38.2\Omega - j \cdot 33.8\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 4.25\text{dB}$.
 - If the power applied at the input port is 6.3 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 74Ω resistor paralel with a 0.264 pF capacitor, at 9.0 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 565 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 20.7\text{dB}$ and noise factor $F_1 = 3.59\text{dB}$), A2 ($G_2 = 24.1\text{dB}$, $F_2 = 4.41\text{dB}$) and A3 ($G_3 = 18.5\text{dB}$, $F_3 = 5.57\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A1, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.20

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $52.1\Omega + j \cdot 56.6\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 4.05\text{dB}$.
 - If the power applied at the input port is 4.2 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 70Ω resistor paralel with a 1.343 nH inductor, at 8.9 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 595 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 16.8\text{dB}$ and noise factor $F_1 = 3.79\text{dB}$), A2 ($G_2 = 22.2\text{dB}$, $F_2 = 4.56\text{dB}$) and A3 ($G_3 = 19.5\text{dB}$, $F_3 = 5.44\text{dB}$). The order in which you must connect the amplifiers is A3, A1, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.21

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $46.9\Omega + j \cdot 49.8\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 4.00\text{dB}$.
 - If the power applied at the input port is 7.7 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 28Ω resistor paralel with a 0.562 pF capacitor, at 9.6 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 575 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 20.9\text{dB}$ and noise factor $F_1 = 3.68\text{dB}$), A2 ($G_2 = 18.7\text{dB}$, $F_2 = 4.24\text{dB}$) and A3 ($G_3 = 19.8\text{dB}$, $F_3 = 5.98\text{dB}$). The order in which you must connect the amplifiers is A2, A3, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A1, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.22

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $48.4\Omega + j \cdot 35.1\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.95\text{dB}$.
 - If the power applied at the input port is 1.7 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 31Ω resistor series with a 0.325 pF capacitor, at 6.7 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 500 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 24.9\text{dB}$ and noise factor $F_1 = 3.97\text{dB}$), A2 ($G_2 = 15.7\text{dB}$, $F_2 = 4.95\text{dB}$) and A3 ($G_3 = 16.8\text{dB}$, $F_3 = 5.84\text{dB}$). The order in which you must connect the amplifiers is A2, A1, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A1, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.23

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $33.4\Omega + j \cdot 31.0\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.35\text{dB}$.
 - If the power applied at the input port is 9.8 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 69Ω resistor series with a 0.569 nH inductor, at 8.7 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 335 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 19.2\text{dB}$ and noise factor $F_1 = 3.32\text{dB}$), A2 ($G_2 = 19.2\text{dB}$, $F_2 = 4.63\text{dB}$) and A3 ($G_3 = 21.3\text{dB}$, $F_3 = 5.94\text{dB}$). The order in which you must connect the amplifiers is A2, A1, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.24

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $36.1\Omega - j\cdot 64.3\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.40\text{dB}$.
 - If the power applied at the input port is 7.5 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 32Ω resistor paralel with a 1.180 nH inductor, at 10.0 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 315 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 21.3\text{dB}$ and noise factor $F_1 = 3.68\text{dB}$), A2 ($G_2 = 18.1\text{dB}$, $F_2 = 4.64\text{dB}$) and A3 ($G_3 = 22.2\text{dB}$, $F_3 = 5.93\text{dB}$). The order in which you must connect the amplifiers is A3, A1, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A3, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.25

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $37.7\Omega - j.39.9\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 6.10\text{dB}$.
 - If the power applied at the input port is 9.7 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 66Ω resistor series with a 0.981 nH inductor, at 7.3 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 380 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 24.7\text{dB}$ and noise factor $F_1 = 3.79\text{dB}$), A2 ($G_2 = 17.1\text{dB}$, $F_2 = 4.89\text{dB}$) and A3 ($G_3 = 20.2\text{dB}$, $F_3 = 5.23\text{dB}$). The order in which you must connect the amplifiers is A2, A1, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A1, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.26

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $61.2\Omega + j \cdot 49.5\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.55\text{dB}$.
 - If the power applied at the input port is 3.3 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 58Ω resistor series with a 0.324 pF capacitor, at 9.3 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 315 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 20.0\text{dB}$ and noise factor $F_1 = 3.55\text{dB}$), A2 ($G_2 = 15.9\text{dB}$, $F_2 = 4.97\text{dB}$) and A3 ($G_3 = 15.4\text{dB}$, $F_3 = 5.43\text{dB}$). The order in which you must connect the amplifiers is A2, A1, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A2, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.27

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $51.4\Omega + j \cdot 31.3\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.70\text{dB}$.
 - If the power applied at the input port is 8.0 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 65Ω resistor paralel with a 0.681 nH inductor, at 8.1 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 520 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 17.8\text{dB}$ and noise factor $F_1 = 3.22\text{dB}$), A2 ($G_2 = 23.7\text{dB}$, $F_2 = 4.64\text{dB}$) and A3 ($G_3 = 20.7\text{dB}$, $F_3 = 5.59\text{dB}$). The order in which you must connect the amplifiers is A2, A3, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A1, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.28

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $54.6\Omega + j \cdot 50.8\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 4.85\text{dB}$.
 - If the power applied at the input port is 4.8 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 30Ω resistor series with a 1.292 nH inductor, at 8.0 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 330 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 17.0\text{dB}$ and noise factor $F_1 = 3.95\text{dB}$), A2 ($G_2 = 21.9\text{dB}$, $F_2 = 4.10\text{dB}$) and A3 ($G_3 = 15.2\text{dB}$, $F_3 = 5.64\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A3, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.29

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $56.5\Omega - j \cdot 59.6\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 6.65\text{dB}$.
 - If the power applied at the input port is 5.6 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 31Ω resistor paralel with a 1.231 nH inductor, at 7.8 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 560 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 17.0\text{dB}$ and noise factor $F_1 = 3.10\text{dB}$), A2 ($G_2 = 18.6\text{dB}$, $F_2 = 4.83\text{dB}$) and A3 ($G_3 = 15.7\text{dB}$, $F_3 = 5.24\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A1, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.30

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $60.9\Omega + j \cdot 63.7\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 4.70\text{dB}$.
 - If the power applied at the input port is 6.4 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 61Ω resistor paralel with a 0.483 nH inductor, at 9.5 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 590 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 20.9\text{dB}$ and noise factor $F_1 = 3.90\text{dB}$), A2 ($G_2 = 23.8\text{dB}$, $F_2 = 4.84\text{dB}$) and A3 ($G_3 = 19.7\text{dB}$, $F_3 = 5.16\text{dB}$). The order in which you must connect the amplifiers is A1, A3, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A2, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.31

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $36.1\Omega + j \cdot 63.8\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.25\text{dB}$.
 - If the power applied at the input port is 7.9 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 62Ω resistor series with a 1.493 nH inductor, at 7.2 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 380 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 18.4\text{dB}$ and noise factor $F_1 = 3.42\text{dB}$), A2 ($G_2 = 20.1\text{dB}$, $F_2 = 4.10\text{dB}$) and A3 ($G_3 = 16.6\text{dB}$, $F_3 = 5.53\text{dB}$). The order in which you must connect the amplifiers is A3, A2, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A2, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.32

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $45.1\Omega - j\cdot 60.5\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.15\text{dB}$.
 - If the power applied at the input port is 8.6 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 47Ω resistor paralel with a 0.383 pF capacitor, at 8.7 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 320 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 18.9\text{dB}$ and noise factor $F_1 = 3.81\text{dB}$), A2 ($G_2 = 19.7\text{dB}$, $F_2 = 4.09\text{dB}$) and A3 ($G_3 = 15.2\text{dB}$, $F_3 = 5.40\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.33

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $52.8\Omega - j \cdot 49.4\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.90\text{dB}$.
 - If the power applied at the input port is 3.0 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 39Ω resistor paralel with a 0.551 nH inductor, at 8.3 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 330 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 21.6\text{dB}$ and noise factor $F_1 = 3.80\text{dB}$), A2 ($G_2 = 22.1\text{dB}$, $F_2 = 4.99\text{dB}$) and A3 ($G_3 = 21.2\text{dB}$, $F_3 = 5.59\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A1, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.34

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $43.2\Omega + j \cdot 62.3\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 8.45\text{dB}$.
 - If the power applied at the input port is 5.8 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 31Ω resistor series with a 0.234 pF capacitor, at 9.7 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 505 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 24.5\text{dB}$ and noise factor $F_1 = 3.09\text{dB}$), A2 ($G_2 = 24.4\text{dB}$, $F_2 = 4.11\text{dB}$) and A3 ($G_3 = 20.2\text{dB}$, $F_3 = 5.47\text{dB}$). The order in which you must connect the amplifiers is A3, A1, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A3, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.35

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $36.0\Omega - j\cdot 36.8\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.05\text{dB}$.
 - If the power applied at the input port is 4.7 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 60Ω resistor paralel with a 1.682 nH inductor, at 6.5 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 475 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 24.4\text{dB}$ and noise factor $F_1 = 3.44\text{dB}$), A2 ($G_2 = 22.1\text{dB}$, $F_2 = 4.12\text{dB}$) and A3 ($G_3 = 21.3\text{dB}$, $F_3 = 5.50\text{dB}$). The order in which you must connect the amplifiers is A3, A2, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A1, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.36

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $61.2\Omega - j \cdot 51.4\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.75\text{dB}$.
 - If the power applied at the input port is 6.5 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 44Ω resistor series with a 1.201 nH inductor, at 8.5 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 370 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 16.6\text{dB}$ and noise factor $F_1 = 3.38\text{dB}$), A2 ($G_2 = 20.3\text{dB}$, $F_2 = 4.60\text{dB}$) and A3 ($G_3 = 16.4\text{dB}$, $F_3 = 5.10\text{dB}$). The order in which you must connect the amplifiers is A1, A3, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A1, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.37

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $34.8\Omega - j \cdot 50.8\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.55\text{dB}$.
 - If the power applied at the input port is 9.4 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 61Ω resistor series with a 0.431 pF capacitor, at 7.5 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 460 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 24.0\text{dB}$ and noise factor $F_1 = 3.08\text{dB}$), A2 ($G_2 = 20.4\text{dB}$, $F_2 = 4.28\text{dB}$) and A3 ($G_3 = 18.4\text{dB}$, $F_3 = 5.26\text{dB}$). The order in which you must connect the amplifiers is A3, A2, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A3, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.38

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $68.8\Omega - j\cdot 48.6\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.60\text{dB}$.
 - If the power applied at the input port is 9.0 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 26Ω resistor paralel with a 0.283 pF capacitor, at 8.4 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 515 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 17.3\text{dB}$ and noise factor $F_1 = 3.77\text{dB}$), A2 ($G_2 = 19.4\text{dB}$, $F_2 = 4.78\text{dB}$) and A3 ($G_3 = 19.0\text{dB}$, $F_3 = 5.56\text{dB}$). The order in which you must connect the amplifiers is A3, A1, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A2, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.39

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $46.1\Omega - j\cdot 32.3\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 6.55\text{dB}$.
 - If the power applied at the input port is 8.0 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 27Ω resistor series with a 0.328 pF capacitor, at 6.7 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 370 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 21.0\text{dB}$ and noise factor $F_1 = 3.70\text{dB}$), A2 ($G_2 = 19.1\text{dB}$, $F_2 = 4.55\text{dB}$) and A3 ($G_3 = 19.0\text{dB}$, $F_3 = 5.51\text{dB}$). The order in which you must connect the amplifiers is A2, A3, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A2, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 40

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $64.9\Omega + j \cdot 54.7\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.35\text{dB}$.
 - If the power applied at the input port is 3.9 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 37Ω resistor paralel with a 0.484 pF capacitor, at 8.6 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 540 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 22.4\text{dB}$ and noise factor $F_1 = 3.18\text{dB}$), A2 ($G_2 = 16.4\text{dB}$, $F_2 = 4.47\text{dB}$) and A3 ($G_3 = 19.9\text{dB}$, $F_3 = 5.09\text{dB}$). The order in which you must connect the amplifiers is A1, A3, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A1, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 41

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $50.1\Omega + j \cdot 64.9\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.55\text{dB}$.
 - If the power applied at the input port is 7.1 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 56Ω resistor series with a 0.323 pF capacitor, at 6.9 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 495 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 15.9\text{dB}$ and noise factor $F_1 = 3.86\text{dB}$), A2 ($G_2 = 18.3\text{dB}$, $F_2 = 4.59\text{dB}$) and A3 ($G_3 = 15.1\text{dB}$, $F_3 = 5.52\text{dB}$). The order in which you must connect the amplifiers is A2, A3, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A2, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 42

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $32.3\Omega + j \cdot 68.4\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.85\text{dB}$.
 - If the power applied at the input port is 1.1 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 61Ω resistor series with a 1.168 nH inductor, at 6.7 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 330 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 17.7\text{dB}$ and noise factor $F_1 = 3.93\text{dB}$), A2 ($G_2 = 17.9\text{dB}$, $F_2 = 4.72\text{dB}$) and A3 ($G_3 = 19.1\text{dB}$, $F_3 = 5.74\text{dB}$). The order in which you must connect the amplifiers is A2, A3, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A1, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 43

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $50.9\Omega + j \cdot 41.4\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 4.20\text{dB}$.
 - If the power applied at the input port is 3.4 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 32Ω resistor paralel with a 0.897 nH inductor, at 8.5 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 530 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 20.8\text{dB}$ and noise factor $F_1 = 3.06\text{dB}$), A2 ($G_2 = 23.3\text{dB}$, $F_2 = 4.76\text{dB}$) and A3 ($G_3 = 24.8\text{dB}$, $F_3 = 5.96\text{dB}$). The order in which you must connect the amplifiers is A2, A3, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A1, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 44

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $53.2\Omega + j \cdot 68.3\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 4.90\text{dB}$.
 - If the power applied at the input port is 7.3 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 35Ω resistor series with a 0.731 pF capacitor, at 6.8 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 410 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 19.3\text{dB}$ and noise factor $F_1 = 3.53\text{dB}$), A2 ($G_2 = 18.3\text{dB}$, $F_2 = 4.47\text{dB}$) and A3 ($G_3 = 20.0\text{dB}$, $F_3 = 5.91\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 45

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $61.0\Omega + j \cdot 64.9\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 6.25\text{dB}$.
 - If the power applied at the input port is 8.1 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 47Ω resistor series with a 0.362 pF capacitor, at 8.0 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 395 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 21.5\text{dB}$ and noise factor $F_1 = 3.63\text{dB}$), A2 ($G_2 = 18.2\text{dB}$, $F_2 = 4.41\text{dB}$) and A3 ($G_3 = 22.8\text{dB}$, $F_3 = 5.97\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A1, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 46

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $53.7\Omega - j\cdot 35.3\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.40\text{dB}$.
 - If the power applied at the input port is 6.6 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 67Ω resistor series with a 1.460 nH inductor, at 8.2 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 405 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 24.5\text{dB}$ and noise factor $F_1 = 3.28\text{dB}$), A2 ($G_2 = 24.6\text{dB}$, $F_2 = 4.64\text{dB}$) and A3 ($G_3 = 23.1\text{dB}$, $F_3 = 5.25\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A1, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 47

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $52.8\Omega + j \cdot 56.0\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 6.25\text{dB}$.
 - If the power applied at the input port is 2.2 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 28Ω resistor series with a 1.204 nH inductor, at 8.9 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 450 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 21.8\text{dB}$ and noise factor $F_1 = 3.27\text{dB}$), A2 ($G_2 = 15.3\text{dB}$, $F_2 = 4.49\text{dB}$) and A3 ($G_3 = 18.1\text{dB}$, $F_3 = 5.87\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A1, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 48

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $49.6\Omega + j \cdot 68.3\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.70\text{dB}$.
 - If the power applied at the input port is 8.1 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 71Ω resistor paralel with a 0.318 pF capacitor, at 9.7 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 335 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 17.8\text{dB}$ and noise factor $F_1 = 3.03\text{dB}$), A2 ($G_2 = 16.8\text{dB}$, $F_2 = 4.22\text{dB}$) and A3 ($G_3 = 20.4\text{dB}$, $F_3 = 5.76\text{dB}$). The order in which you must connect the amplifiers is A2, A3, A1.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A2, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No. 49

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $57.2\Omega - j \cdot 62.1\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.40\text{dB}$.
 - If the power applied at the input port is 1.0 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 73Ω resistor paralel with a 0.280 pF capacitor, at 9.6 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 365 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 21.8\text{dB}$ and noise factor $F_1 = 3.20\text{dB}$), A2 ($G_2 = 15.3\text{dB}$, $F_2 = 4.02\text{dB}$) and A3 ($G_3 = 15.3\text{dB}$, $F_3 = 5.96\text{dB}$). The order in which you must connect the amplifiers is A1, A3, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.50

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $30.8\Omega + j \cdot 63.5\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.10\text{dB}$.
 - If the power applied at the input port is 4.4 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 69Ω resistor series with a 0.326 pF capacitor, at 9.6 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 515 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 19.4\text{dB}$ and noise factor $F_1 = 3.88\text{dB}$), A2 ($G_2 = 24.9\text{dB}$, $F_2 = 4.68\text{dB}$) and A3 ($G_3 = 20.6\text{dB}$, $F_3 = 5.59\text{dB}$). The order in which you must connect the amplifiers is A3, A1, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.51

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $68.3\Omega + j \cdot 52.0\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 6.20\text{dB}$.
 - If the power applied at the input port is 3.0 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 73Ω resistor series with a 1.155 nH inductor, at 7.5 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 440 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 23.8\text{dB}$ and noise factor $F_1 = 3.50\text{dB}$), A2 ($G_2 = 21.4\text{dB}$, $F_2 = 4.00\text{dB}$) and A3 ($G_3 = 24.5\text{dB}$, $F_3 = 5.07\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.52

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $69.4\Omega - j \cdot 64.6\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 4.40\text{dB}$.
 - If the power applied at the input port is 2.7 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 43Ω resistor paralel with a 0.410 pF capacitor, at 7.1 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 500 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 22.8\text{dB}$ and noise factor $F_1 = 3.49\text{dB}$), A2 ($G_2 = 21.3\text{dB}$, $F_2 = 4.36\text{dB}$) and A3 ($G_3 = 23.5\text{dB}$, $F_3 = 5.42\text{dB}$). The order in which you must connect the amplifiers is A2, A1, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.53

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $53.4\Omega - j \cdot 67.9\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 6.90\text{dB}$.
 - If the power applied at the input port is 8.2 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 70Ω resistor paralel with a 1.342 nH inductor, at 8.3 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 315 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 23.5\text{dB}$ and noise factor $F_1 = 3.81\text{dB}$), A2 ($G_2 = 16.2\text{dB}$, $F_2 = 4.65\text{dB}$) and A3 ($G_3 = 16.9\text{dB}$, $F_3 = 5.29\text{dB}$). The order in which you must connect the amplifiers is A2, A1, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A2, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.54

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $62.8\Omega + j \cdot 47.4\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.05\text{dB}$.
 - If the power applied at the input port is 3.0 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 59Ω resistor series with a 0.267 pF capacitor, at 8.0 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 595 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 15.0\text{dB}$ and noise factor $F_1 = 3.06\text{dB}$), A2 ($G_2 = 18.2\text{dB}$, $F_2 = 4.84\text{dB}$) and A3 ($G_3 = 16.9\text{dB}$, $F_3 = 5.83\text{dB}$). The order in which you must connect the amplifiers is A3, A1, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A1, A3? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.55

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $43.7\Omega + j\cdot 30.0\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.80\text{dB}$.
 - If the power applied at the input port is 6.2 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 60Ω resistor series with a 1.179 nH inductor, at 9.3 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 540 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 23.8\text{dB}$ and noise factor $F_1 = 3.47\text{dB}$), A2 ($G_2 = 24.9\text{dB}$, $F_2 = 4.11\text{dB}$) and A3 ($G_3 = 20.4\text{dB}$, $F_3 = 5.23\text{dB}$). The order in which you must connect the amplifiers is A1, A3, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.56

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $58.1\Omega + j \cdot 38.9\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 8.00\text{dB}$.
 - If the power applied at the input port is 6.2 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 63Ω resistor paralel with a 0.930 pF capacitor, at 6.8 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 405 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 24.1\text{dB}$ and noise factor $F_1 = 3.81\text{dB}$), A2 ($G_2 = 20.2\text{dB}$, $F_2 = 4.84\text{dB}$) and A3 ($G_3 = 15.2\text{dB}$, $F_3 = 5.92\text{dB}$). The order in which you must connect the amplifiers is A1, A3, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.57

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $45.7\Omega + j \cdot 60.6\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 7.80\text{dB}$.
 - If the power applied at the input port is 5.3 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 32Ω resistor paralel with a 0.581 nH inductor, at 7.5 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (0.5dB) high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 395 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 18.1\text{dB}$ and noise factor $F_1 = 3.80\text{dB}$), A2 ($G_2 = 15.2\text{dB}$, $F_2 = 4.42\text{dB}$) and A3 ($G_3 = 21.9\text{dB}$, $F_3 = 5.52\text{dB}$). The order in which you must connect the amplifiers is A2, A1, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A3, A1? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.58

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $48.2\Omega - j\cdot 43.0\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 4.45\text{dB}$.
 - If the power applied at the input port is 5.3 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 71Ω resistor paralel with a 0.326 pF capacitor, at 8.1 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, equal ripple (3dB) low-pass filter (LPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 445 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 24.8\text{dB}$ and noise factor $F_1 = 3.12\text{dB}$), A2 ($G_2 = 18.9\text{dB}$, $F_2 = 4.36\text{dB}$) and A3 ($G_3 = 16.9\text{dB}$, $F_3 = 5.17\text{dB}$). The order in which you must connect the amplifiers is A1, A2, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A1, A3, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.59

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $37.9\Omega + j \cdot 33.6\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 5.50\text{dB}$.
 - If the power applied at the input port is 4.4 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 60Ω resistor paralel with a 0.546 pF capacitor, at 7.0 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 315 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 19.3\text{dB}$ and noise factor $F_1 = 3.19\text{dB}$), A2 ($G_2 = 19.2\text{dB}$, $F_2 = 4.02\text{dB}$) and A3 ($G_3 = 16.5\text{dB}$, $F_3 = 5.91\text{dB}$). The order in which you must connect the amplifiers is A2, A1, A3.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A3, A1, A2? (**1.5p**)

UNIVERSITATEA TEHNICĂ "GHEORGHE ASACHI" DIN IAȘI

Faculty / Department: Electronics, Telecommunications and Information Technology

Domain: Telecommunication Technologies and Systems

Course : MDCR - EDID407

Enrollment Year: ___4___, Examination Session _____ June _____ / ___2024

SUBJECT No.60

Time allowed: 2 hours; All materials/equipment authorized

Instructor: Assoc. Prof. Radu Damian Student: _____ Group _____

Note. Except where otherwise specified, assume 50Ω reference impedance.

Note. Any CAD solution (Matlab, Mathcad, ADS) must contain relevant intermediate results for maximum points.

- For a impedance equal to $63.0\Omega - j \cdot 59.6\Omega$ compute the normalized admittance (**1p**) and then plot on a Smith Chart (external circle and complex plane axes) the corresponding point (**1p**)
- An ideal lossless quadrature coupler (matched on all ports with infinite isolation) has coupling factor $C = 4.75\text{dB}$.
 - If the power applied at the input port is 2.4 dBm compute the power at the coupled port (**in dBm**). (**0.5p**)
 - In the same situation compute the power at the through port (**in dBm and mW**). (**1.5p**)
 - Design the coupler. (**1p**)
- For a load composed from a 69Ω resistor paralel with a 0.457 pF capacitor, at 6.8 GHz :
 - Compute the corresponding reflection coefficient. (**1p**)
 - Plot on a Smith Chart (external circle and complex plane axes) the corresponding point. (**0.5p**)
 - Design the match for this load to a 50Ω source with stubs (shunt stub, at least one solution) (**2p**)
 - Draw the match schematic. (**0.5p**)
- Design a 5th order, maximally flat high-pass filter (HPF) using reactive lumped elements (L/C). The filter must be designed with a cutoff frequency 575 MHz and with 50Ω both source and load.
 - Compute all the filter elements. (**1.5p**)
 - Draw the filter schematic. (**0.5p**)
 - Draw an estimate filter output (attenuation vs. frequency). (**1p**)
- You must cascade three amplifiers, A1 (having gain $G_1 = 16.5\text{dB}$ and noise factor $F_1 = 3.42\text{dB}$), A2 ($G_2 = 24.4\text{dB}$, $F_2 = 4.13\text{dB}$) and A3 ($G_3 = 23.7\text{dB}$, $F_3 = 5.94\text{dB}$). The order in which you must connect the amplifiers is A1, A3, A2.
 - Compute the overall gain (**in linear scale**). (**0.5p**)
 - Compute the overall noise factor (**in dB**). (**1p**)
 - What are the changes you expect if you connect the amplifiers in this wrong order: A2, A1, A3? (**1.5p**)