

Laboratory 1 (w3-4)



2021/2022

# Microwave Devices and Circuits

# Online results submission

- many numerical values

	Z1	Z2	Z3	Z4	Z5	Z6	Z7
	148.33	155.88	202.12	164.35	180.91	30.29	185.19
	25.97	153.5	34.64	35.79	55.56	26.212	10.693
	0	0	0	0	0	0	0
	50	50	50	50	50	50	50

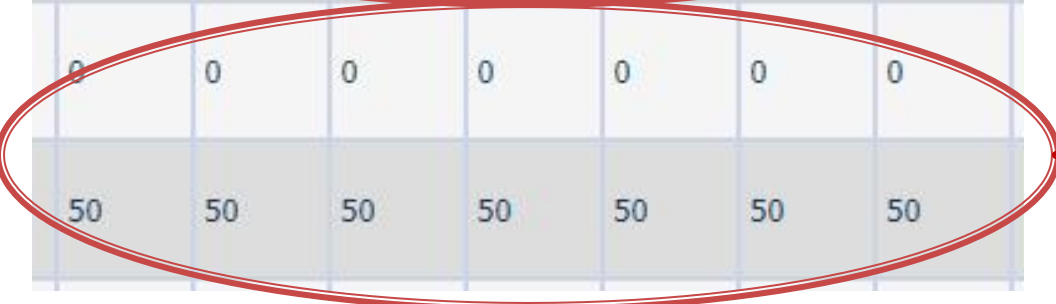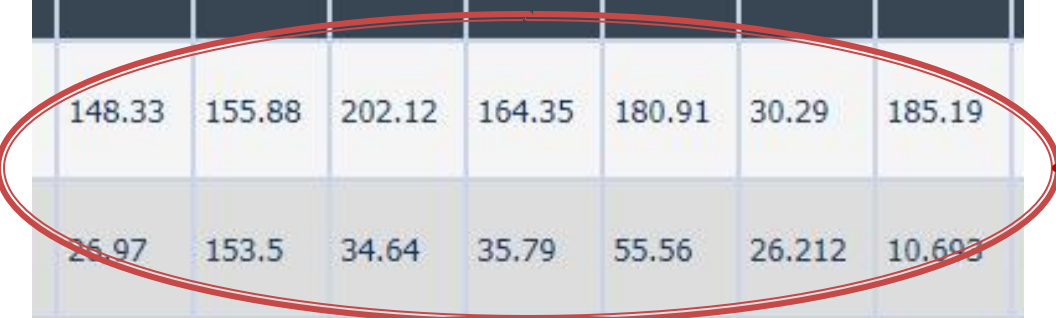

# Online results submission

---

Grade = Quality of the work +  
+ Quality of the submission


# Short theory

# Impedance matching

- Impedance matching is required when we have an abrupt change of the impedance or characteristic impedance (transmission lines)
- The quality of the match is denoted by the value of the reflection coefficient ( $\Gamma$ )
  - $|\Gamma|=0$  perfect match
  - $|\Gamma|\approx 0, |\Gamma|<\Gamma_{\max}$  “good enough” match
- in ADS:  $|\Gamma|=|S_{11}|$
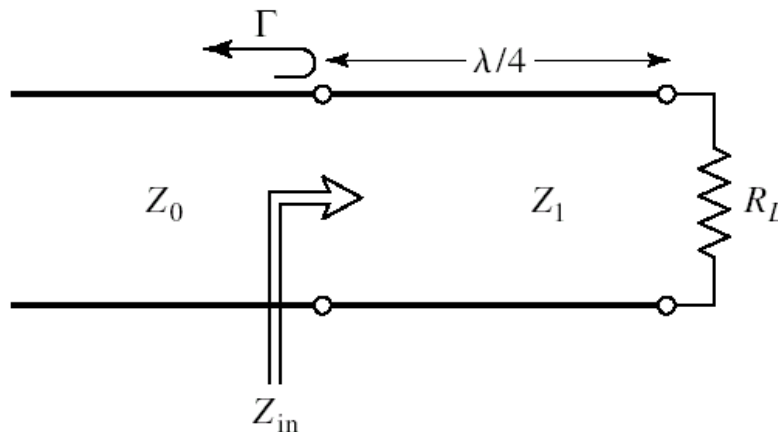
# The quarter-wave transformer


- Feed line – input line with characteristic impedance  $Z_0$
- (**Real!**) load impedance  $R_L$
- We desire matching the load to the fider with a second line with the length  $\lambda/4$  and characteristic impedance  $Z_1$



$$\Gamma_{in} = 0 \Rightarrow Z_1 = \sqrt{Z_0 R_L}$$

$$Z_{in} = Z_1 \frac{R_L + jZ_1 \tan(\beta l)}{Z_1 + jR_L \tan(\beta l)}$$

# The quarter-wave transformer

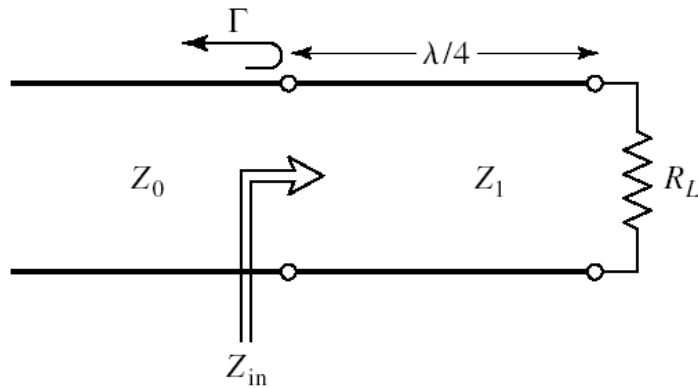

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$\beta \cdot l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}$$



$$Z_{in} = \frac{Z_1^2}{R_L}$$

$$\Gamma_{in} = \frac{Z_1^2 - Z_0 \cdot R_L}{Z_1^2 + Z_0 \cdot R_L}$$

$$\Gamma_{in} = 0 \Rightarrow Z_1 = \sqrt{Z_0 R_L}$$

- In the feed line ( $Z_0$ ) we have only progressive wave
- In the quarter-wave line ( $Z_1$ ) we have standing waves

# The quarter-wave transformer

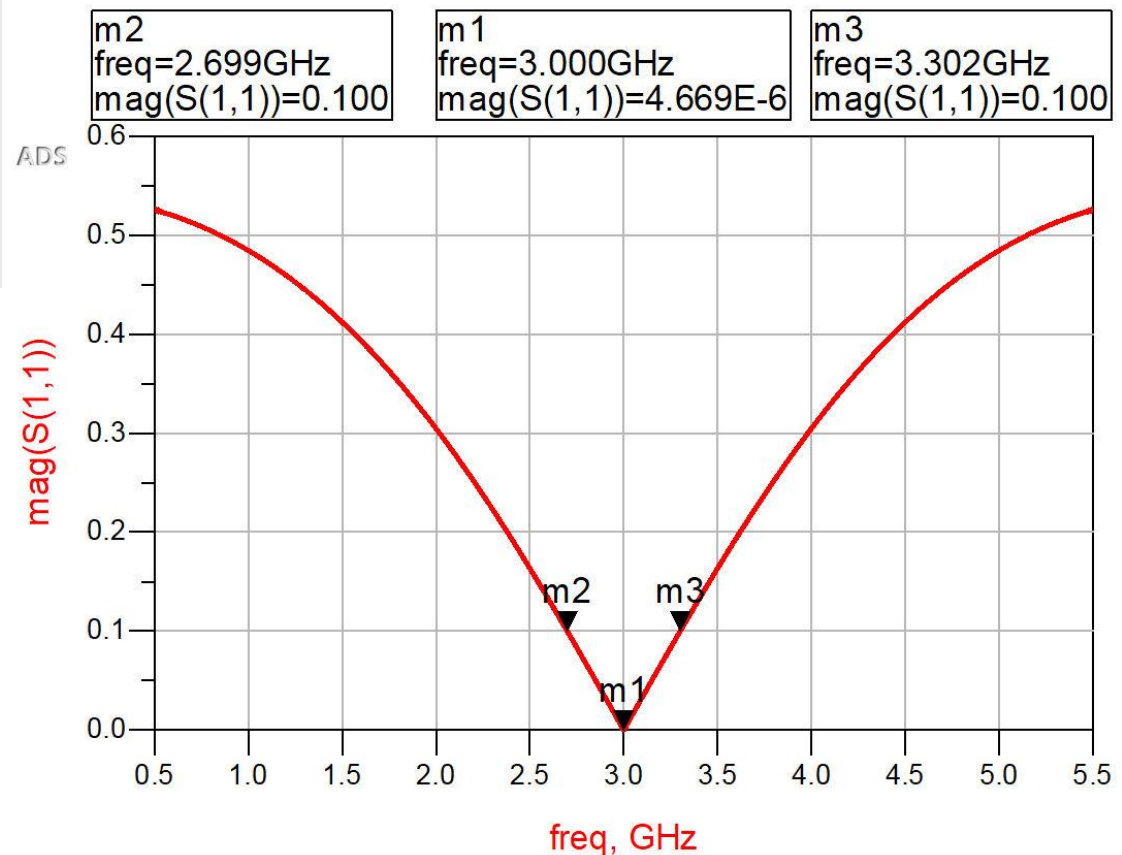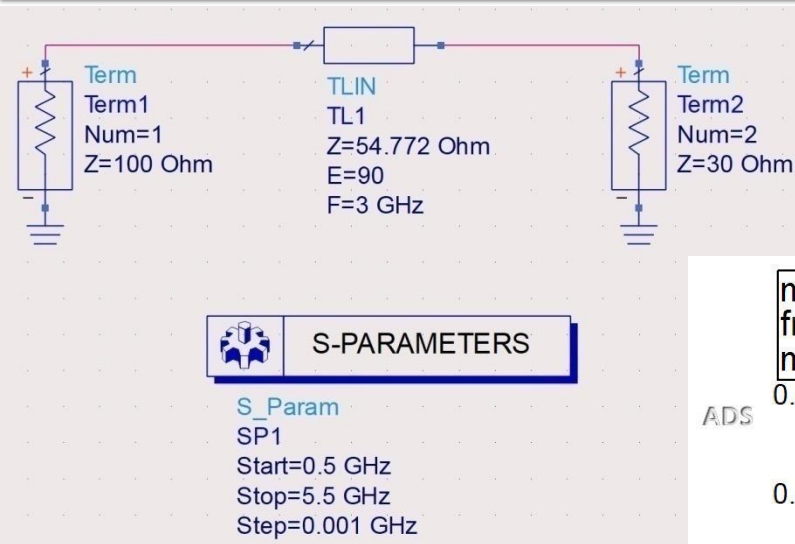




# Multisection Impedance Transformer

- The quarter-wave transformer can match any real load to any feed line impedance
- If a greater bandwidth for the match is required we must use multiple sections of transmission lines transformers:
  - binomial
  - Chebyshev

# Multisection Impedance Transformers

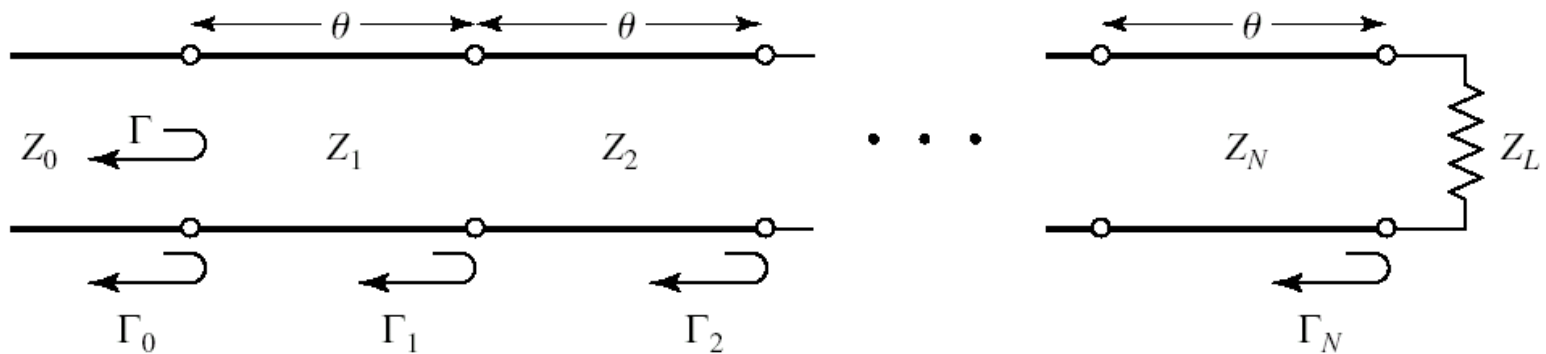

- We assume that all impedances **increase or decrease monotonically** across the transformer
- This implies that all reflection coefficients will be real and of the same sign
- Previously, 1 section  $\Gamma \cong \Gamma_1 + \Gamma_3 \cdot e^{-2j\theta} \Rightarrow$

$$\Gamma(\theta) = \Gamma_0 + \Gamma_1 \cdot e^{-2j\theta} + \Gamma_2 \cdot e^{-4j\theta} + \dots + \Gamma_N \cdot e^{-2jN\theta}$$

$$\Gamma_1 = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$


$$\Gamma_n = \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n}$$

$n = \overline{1, N-1}$


$$\Gamma_N = \frac{Z_L - Z_N}{Z_L + Z_N}$$

# Binomial




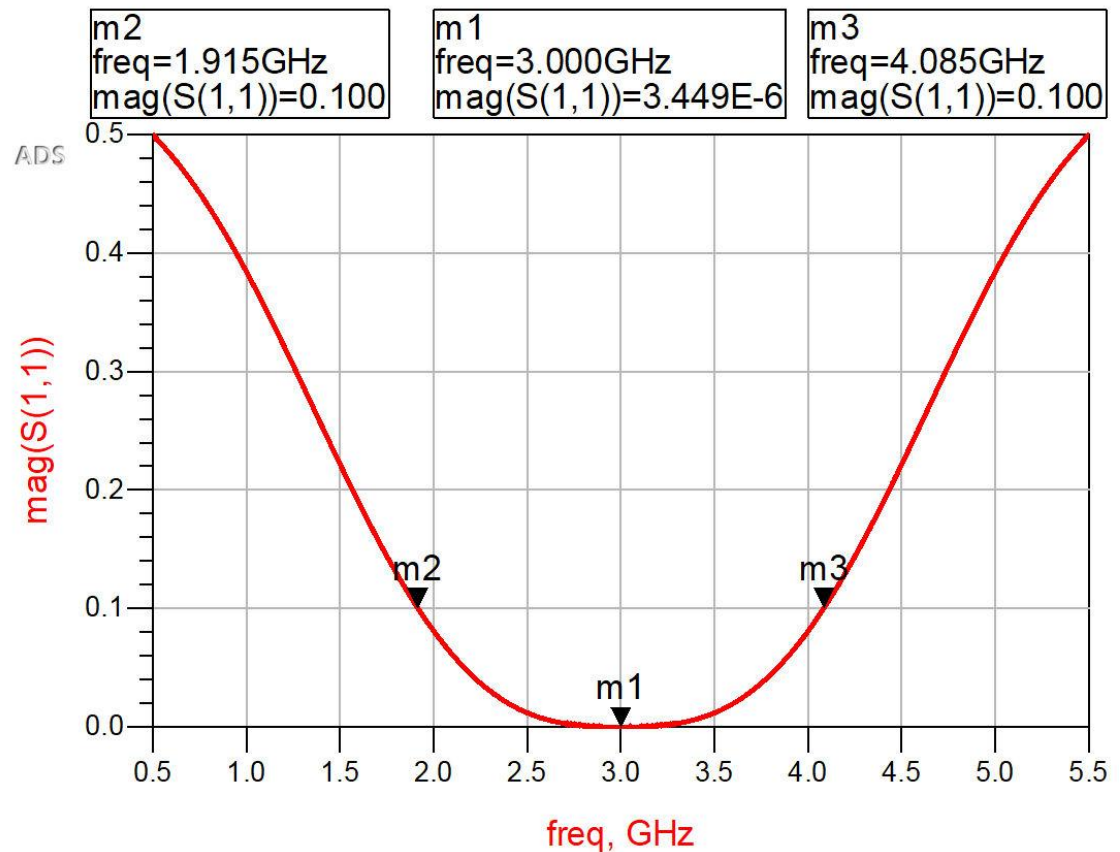
 **S-PARAMETERS**

S\_Param  
SP1  
Start=0.5 GHz  
Stop=5.5 GHz  
Step=0.001 GHz




# Chebyshev

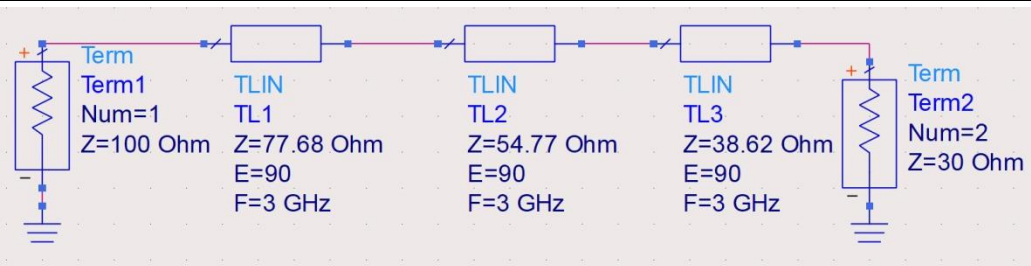

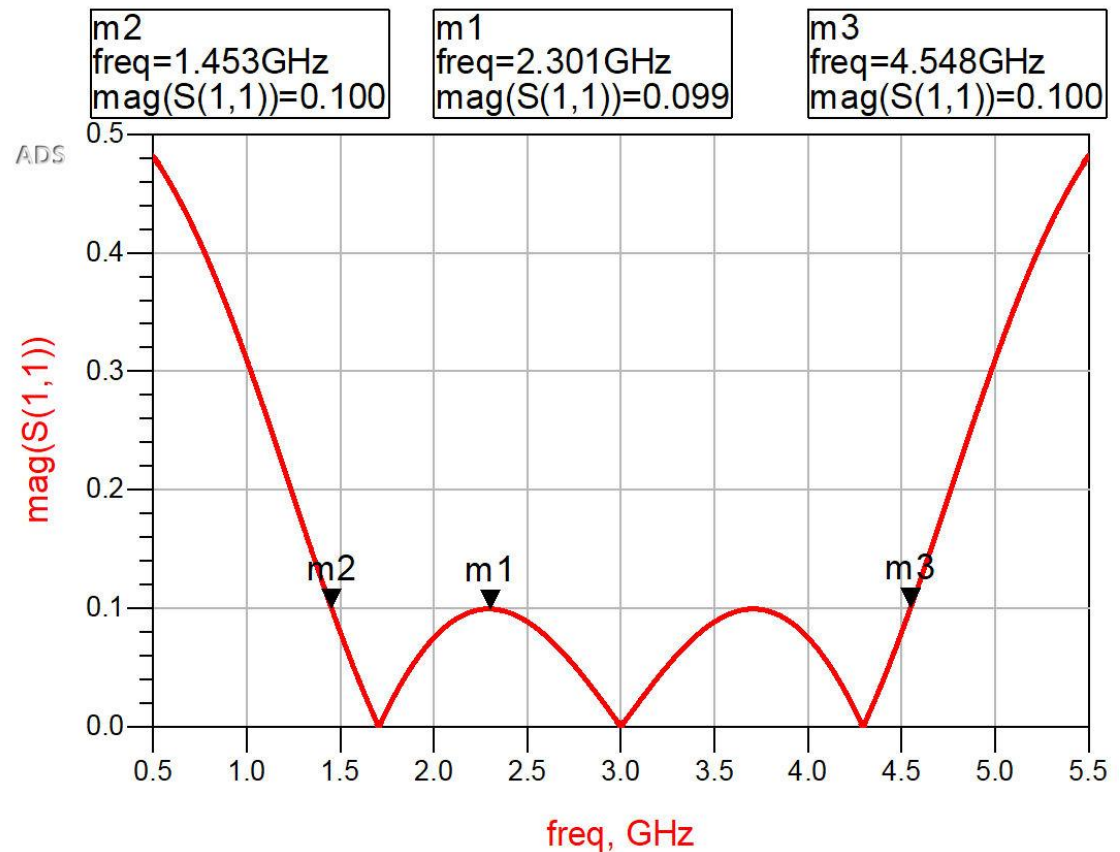
 **S-PARAMETERS**

S\_Param  
SP1  
Start=0.5 GHz  
Stop=5.5 GHz  
Step=0.001 GHz


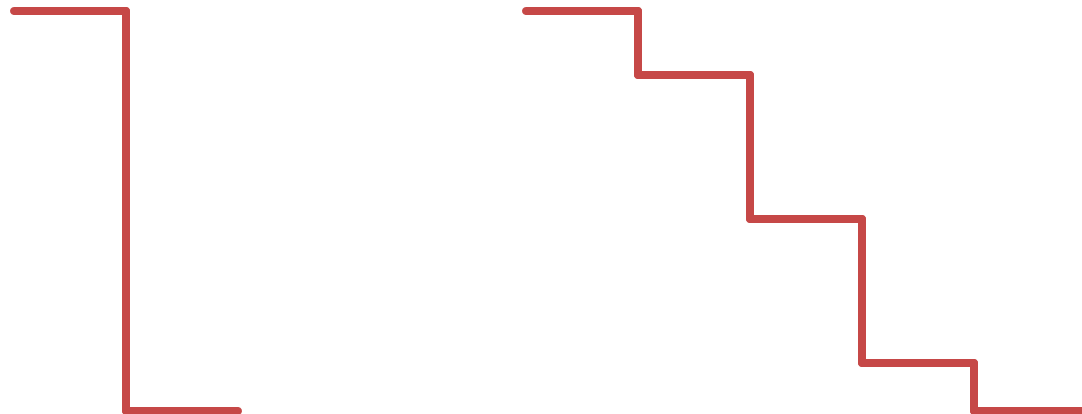
# Impedance matching

- In principle we replace an **abrupt change** of the impedance value with a **step by step change** of the impedance value, with smaller steps
- The increase/decrease steps must be carefully designed for good results



# Practical Procedure

# Step 0

- Write by hand on a sheet of paper 100 times:
- I solemnly promise to read the text  
AND NOT to jump from picture to  
picture
- 😊

# Step 1

- Identify which one of the received impedance values will be  $Z_o$  and which one will be  $Z_L$  in formulas (in order to use the design tables)
- Use as  $Z_o$  **the smaller value** of the two values you received (source or load), and as  $Z_L$  **use the larger value**



# Step 2

- Using the proper table (binomial) **compute**  $Z_1, Z_2, Z_3$
- **!!** If at step 1 you switched  $Z_0$  and  $Z_L$  (meaning your individual subject has  $Z_L > Z_0$ ) switch also the order of the impedances you computed (eg.  $Z_1 \leftrightarrow Z_3$ )


$Z_L/Z_0$	$N = 2$		$N = 3$			$N = 4$			
	$Z_1/Z_0$	$Z_2/Z_0$	$Z_1/Z_0$	$Z_2/Z_0$	$Z_3/Z_0$	$Z_1/Z_0$	$Z_2/Z_0$	$Z_3/Z_0$	$Z_4/Z_0$
1.0	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000
1.5	1.1067	1.3554	1.0520	1.2247	1.4259	1.0257	1.1351	1.3215	1.4624
2.0	1.1892	1.6818	1.0907	1.4142	1.8337	1.0444	1.2421	1.6102	1.9150
3.0	1.3161	2.2795	1.1479	1.7321	2.6135	1.0718	1.4105	2.1269	2.7990
4.0	1.4142	2.8285	1.1907	2.0000	3.3594	1.0919	1.5442	2.5903	3.6633
6.0	1.5651	3.8336	1.2544	2.4495	4.7832	1.1215	1.7553	3.4182	5.3500
8.0	1.6818	4.7568	1.3022	2.8284	6.1434	1.1436	1.9232	4.1597	6.9955
10.0	1.7783	5.6233	1.3409	3.1623	7.4577	1.1613	2.0651	4.8424	8.6110

$Z_L/Z_0$	$N = 5$					$N = 6$					
	$Z_1/Z_0$	$Z_2/Z_0$	$Z_3/Z_0$	$Z_4/Z_0$	$Z_5/Z_0$	$Z_1/Z_0$	$Z_2/Z_0$	$Z_3/Z_0$	$Z_4/Z_0$	$Z_5/Z_0$	$Z_6/Z_0$
1.0	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000
1.5	1.0128	1.0790	1.2247	1.3902	1.4810	1.0064	1.0454	1.1496	1.3048	1.4349	1.4905
2.0	1.0220	1.1391	1.4142	1.7558	1.9569	1.0110	1.0790	1.2693	1.5757	1.8536	1.9782
3.0	1.0354	1.2300	1.7321	2.4390	2.8974	1.0176	1.1288	1.4599	2.0549	2.6577	2.9481
4.0	1.0452	1.2995	2.0000	3.0781	3.8270	1.0225	1.1661	1.6129	2.4800	3.4302	3.9120
6.0	1.0596	1.4055	2.4495	4.2689	5.6625	1.0296	1.2219	1.8573	3.2305	4.9104	5.8275
8.0	1.0703	1.4870	2.8284	5.3800	7.4745	1.0349	1.2640	2.0539	3.8950	6.3291	7.7302
10.0	1.0789	1.5541	3.1623	6.4346	9.2687	1.0392	1.2982	2.2215	4.5015	7.7030	9.6228

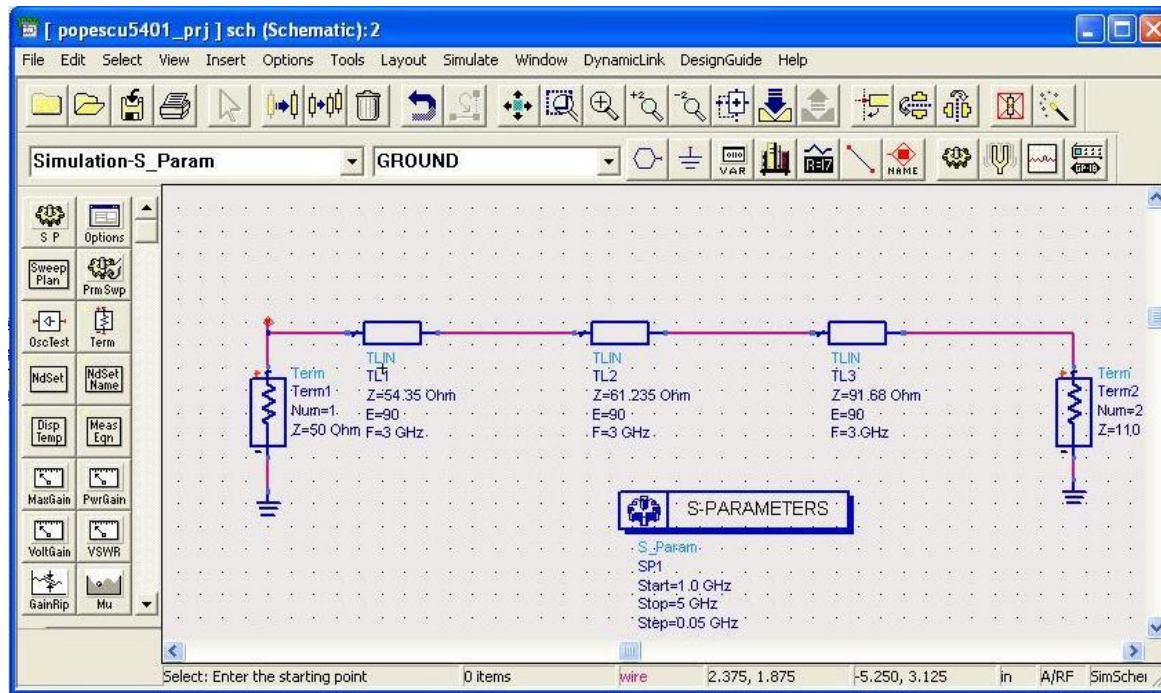
# Step 3

- Draw the schematic as instructed in the lab manual
- **Save it** with whatever name (~~untitled~~)



# Step 4


- Start the simulation

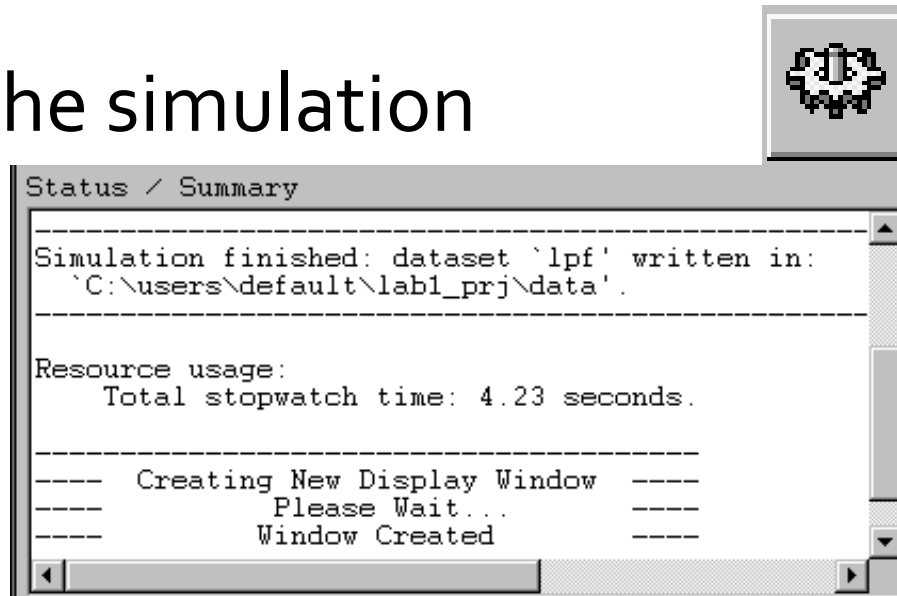

- Successful simulation will open a new window, for results report
  - the window will have the same file name (but a different extension) as the name you used when you saved the schematic


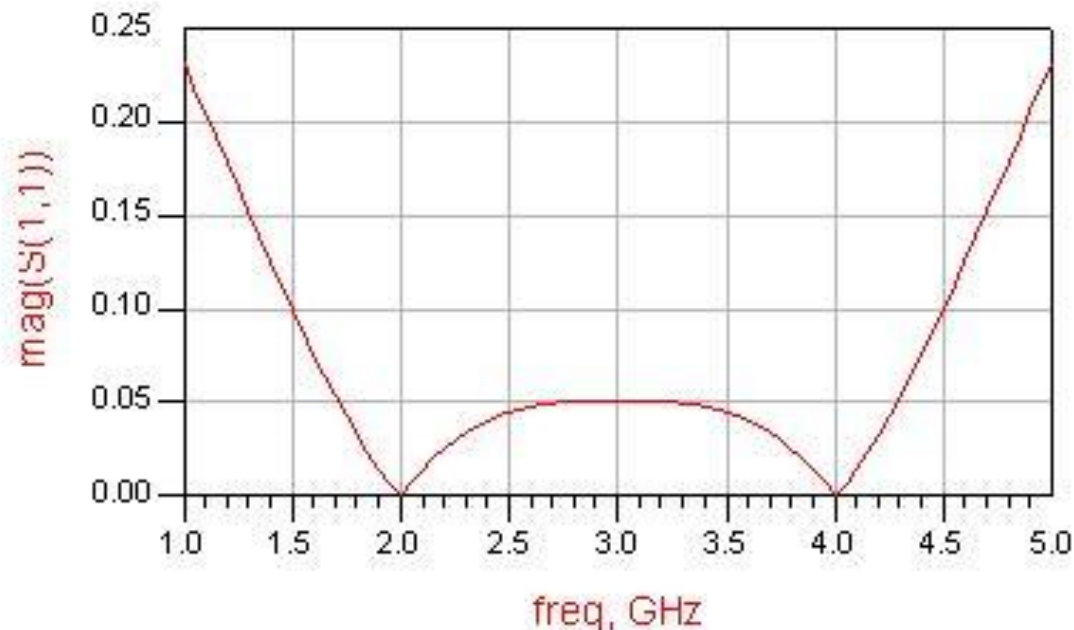
# Step 5

- Insert the rectangular graph to plot the results
- Most likely you won't get the perfect results but they represent an intermediary step



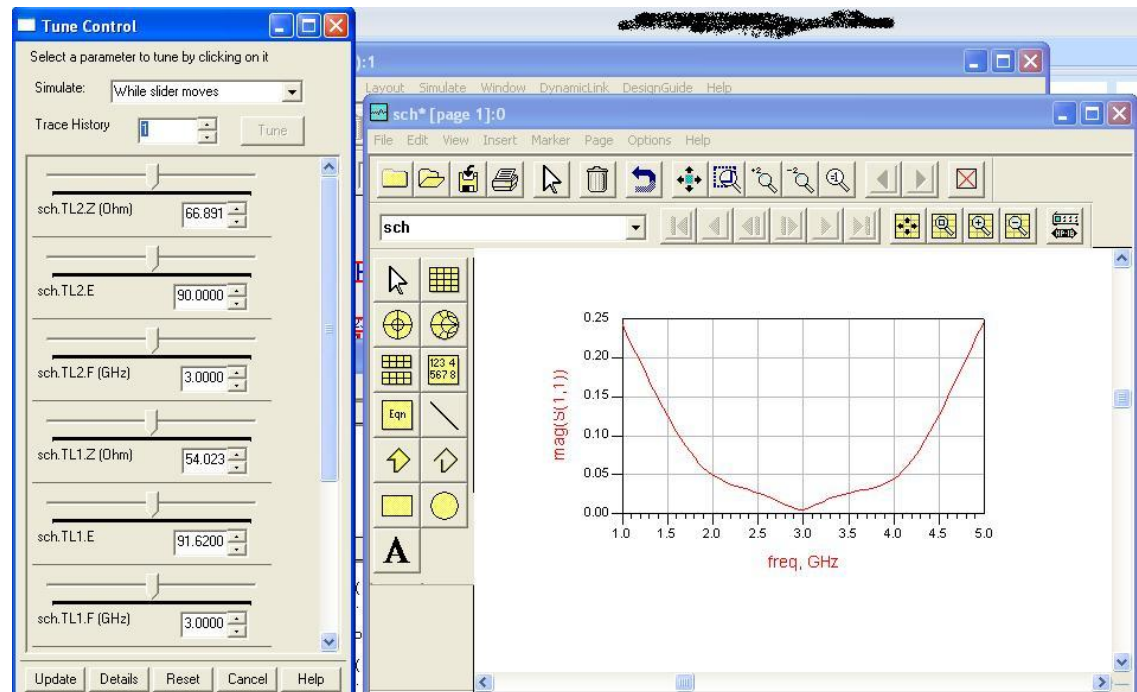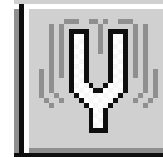
# Step 6

- Start the **tune** tool
- Position the windows on the screen appropriately in order to see **in real time** the tune effect



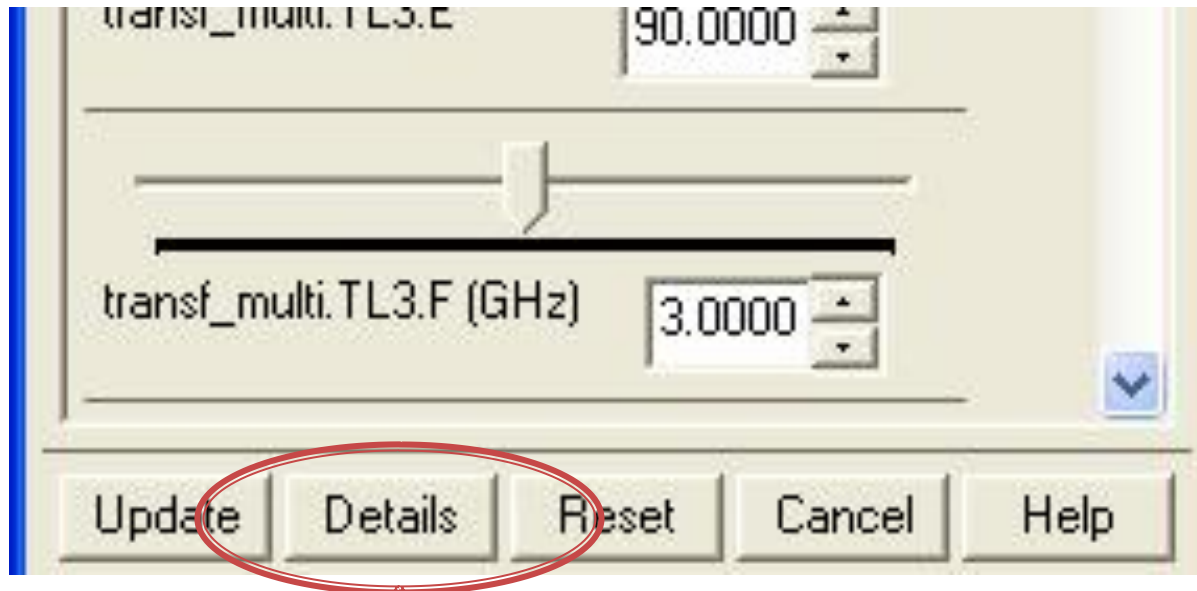
# Step 7a

- If needed (most likely scenario) press “Details” on Tune Control and change the step size



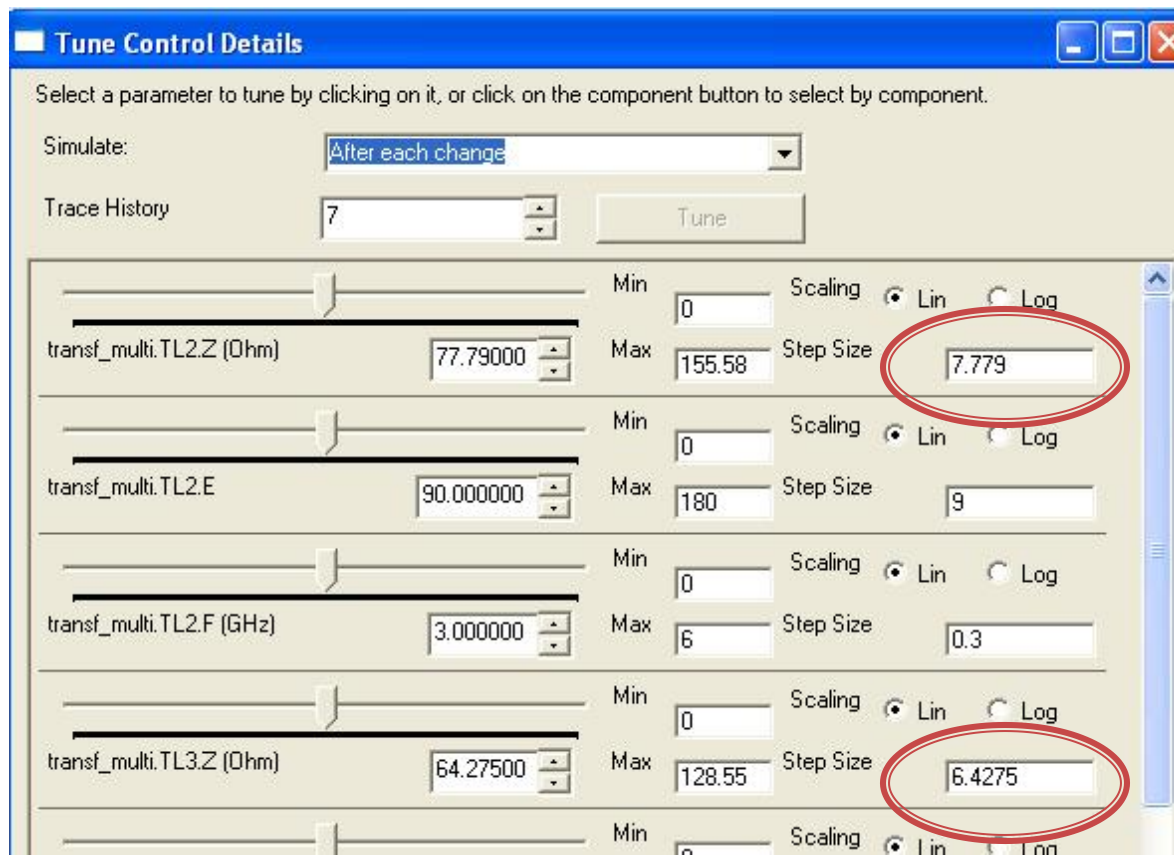
# Step 7b

- Change the “Step Size” (! only for impedances)
  - 1, then 0.1, then 0.01 ..... (as required)


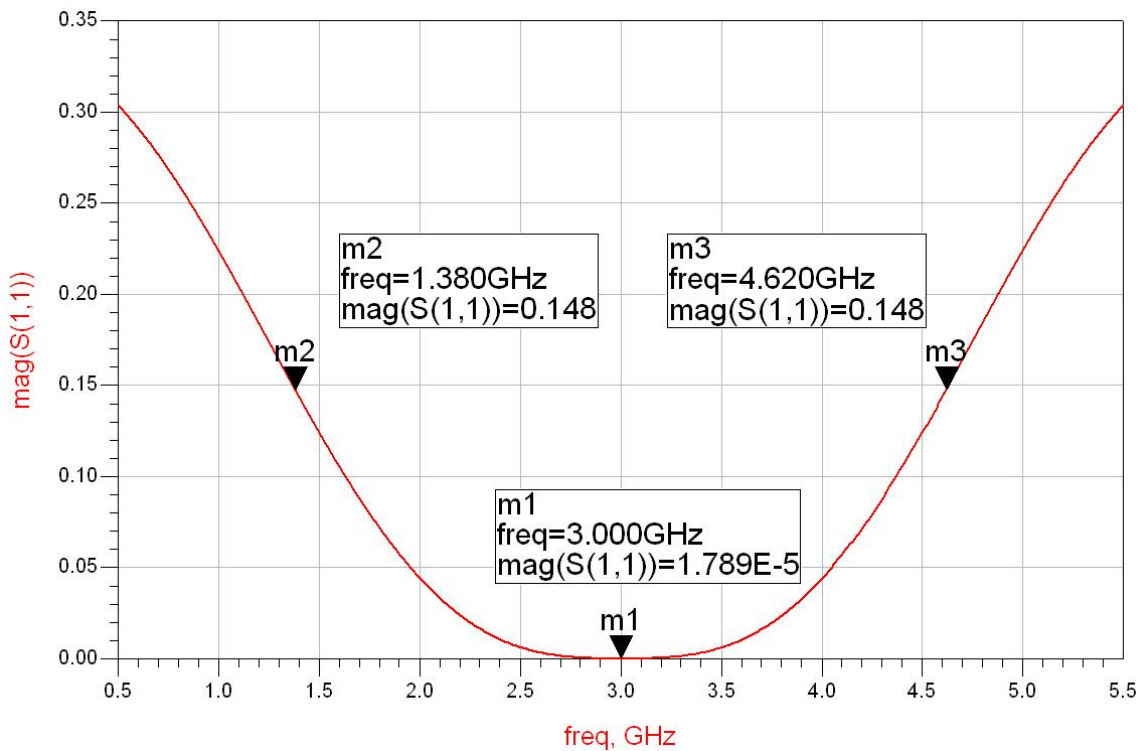
# Step 8

- Finish the tune using smaller and smaller step size ( $1 > 0.1 > 0.01 \dots$ ) watching as the result approaches the desired one





# Step 9

- When you are satisfied with the results press **“Update”** in Tune Control to send the tuned values to the schematic. **Save** the schematic again
- **Carefully write down**  $Z_1$ ,  $Z_2$ ,  $Z_3$  and the bandwidth as  $f_1$  and  $f_2$  (the limits of the bandwidth can be found using 1-2 markers in the points where  $|S_{11}|$  equals  $\Gamma_{\max}$  for your individual subject)

# Step 10

- Save the schematic with a different name (**Save As**)
  - the schematic for Chebyshev transformer is the same, except the numerical values of the impedances, which will have to be replaced


# Steps 11 - 19

- **Repeat** steps 2-10 but using the table for Chebyshev transformer and targeting an **equiripple** result by **tuning**

$Z_L/Z_0$	$N = 2$				$N = 3$					
	$\Gamma_m = 0.05$		$\Gamma_m = 0.20$		$\Gamma_m = 0.05$			$\Gamma_m = 0.20$		
	$Z_1/Z_0$	$Z_2/Z_0$	$Z_1/Z_0$	$Z_2/Z_0$	$Z_1/Z_0$	$Z_2/Z_0$	$Z_3/Z_0$	$Z_1/Z_0$	$Z_2/Z_0$	$Z_3/Z_0$
1.0	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000
1.5	1.1347	1.3219	1.2247	1.2247	1.1029	1.2247	1.3601	1.2247	1.2247	1.2247
2.0	1.2193	1.6402	1.3161	1.5197	1.1475	1.4142	1.7429	1.2855	1.4142	1.5558
3.0	1.3494	2.2232	1.4565	2.0598	1.2171	1.7321	2.4649	1.3743	1.7321	2.1829
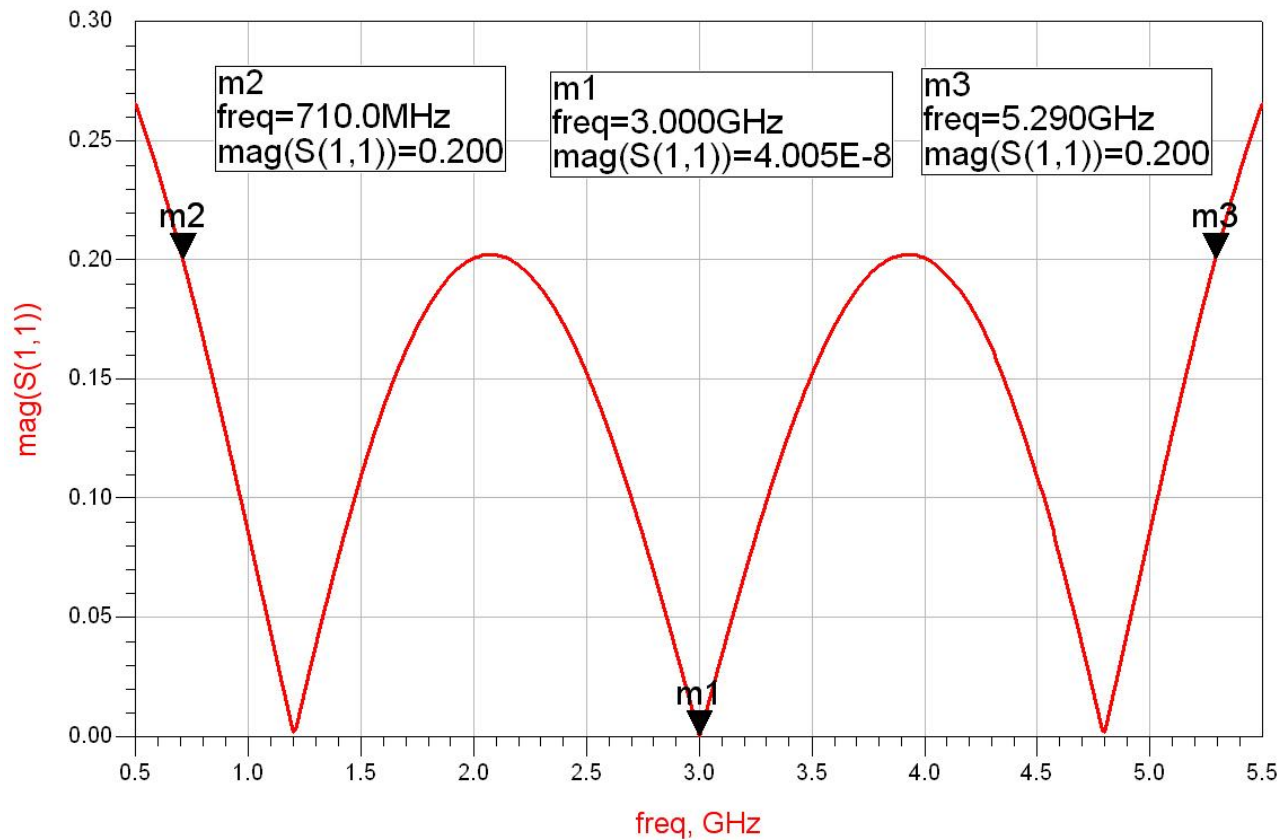
# Pas 20

- When satisfied with the results press Update, save the second schematic write down a second set of values  $Z_1$ ,  $Z_2$ ,  $Z_3$  and  $f_1, f_2$



# Pas 21

- **Carefully** fill in the input boxes in the on-line “exam” Laboratory 1 on the rf-opto server with the exact values you got (the **final tuned** ones not the initial computed ones)

# Online results submission


---

Grade = Quality of the work +  
+ Quality of the submission

# Frequent mistakes
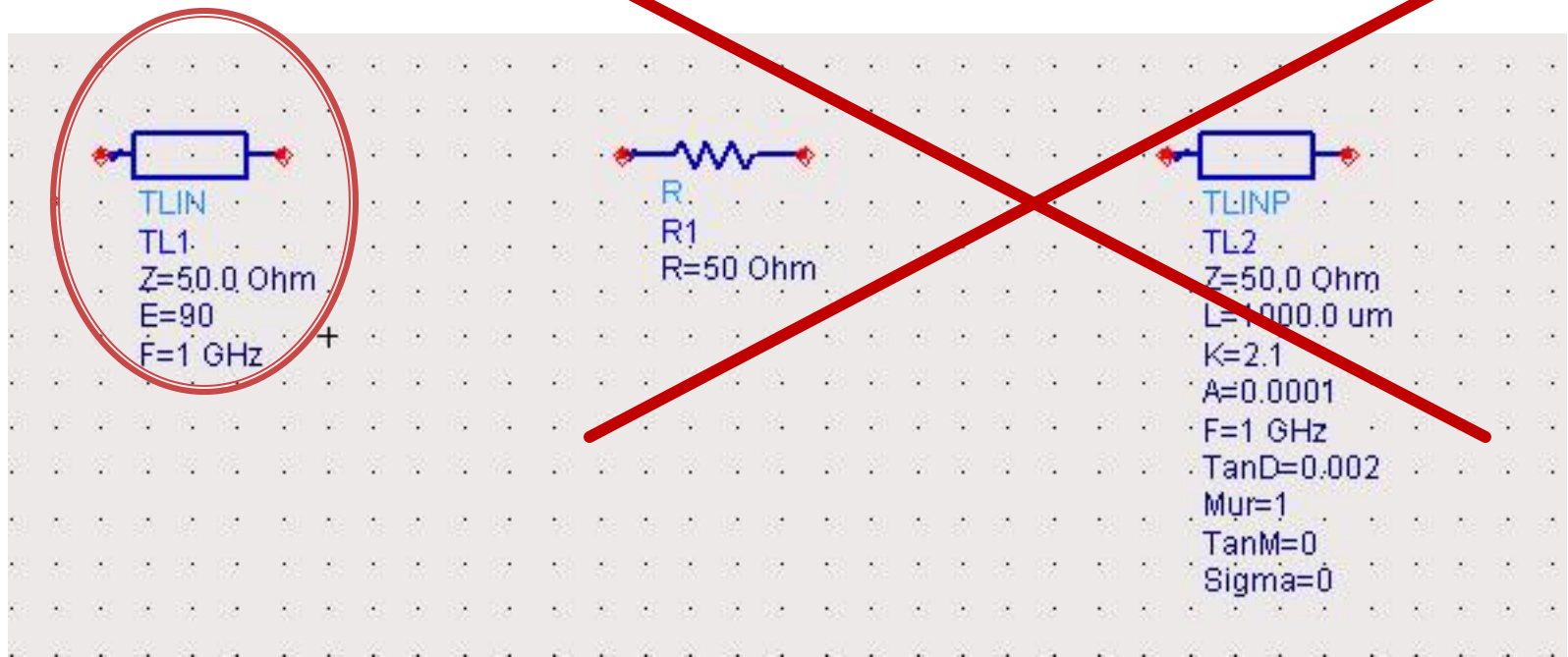
# Mistakes 1

- Putting in the schematic instead of the ideal transmission lines (**TLIN**) resistors or other parts (microstrip, physical etc.)





# Mistakes 2

- Putting in the schematic instead of terminators/ports (**TERM –Simulation S-param palette**) R\_model or even R (Lumped Components palette)




# Mistakes 3

- **Forgetting** to change to the numerical values (from the individual subject) for terminators/ports/source/load (**TERM<sub>1</sub>** and **TERM<sub>2</sub>**)
- Forgetting to change the frequency to the one from the individual subject (**TLIN<sub>1</sub>**, **TLIN<sub>2</sub>**, **TLIN<sub>3</sub>**)
- Wrong order of the impedances (! **frequent**)
  - as a quick check (including during tune), all impedances **must increase or decrease monotonically** across the transformer (including source/load)
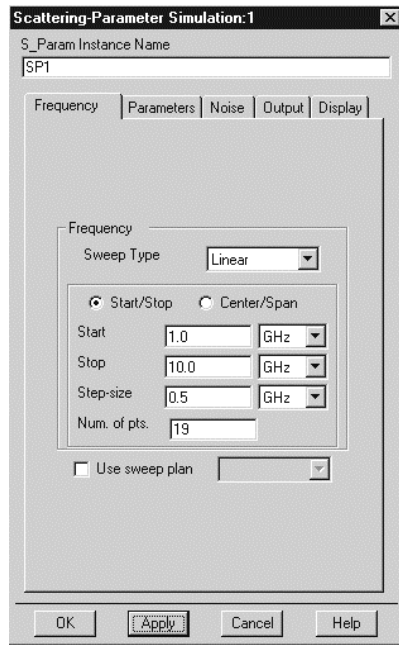
# Mistakes 4


- Forgetting to change the parameters for the simulation
  - often **Start/Stop/Step size** stays at:  
**1GHz/10GHz/1GHz** (undesirable)



- **Start/Stop/Step size**: should be changed to  
 **$f_0 - \Delta f / f_0 + \Delta f / (0.05\text{GHz or } 0.01\text{GHz})$**
- where  $\Delta f$  is applied symmetrically around the imposed  $f_0$  such as the matching bandwidth can be observed; if results show  $\Delta f$  was chosen too small, increase it and repeat simulation
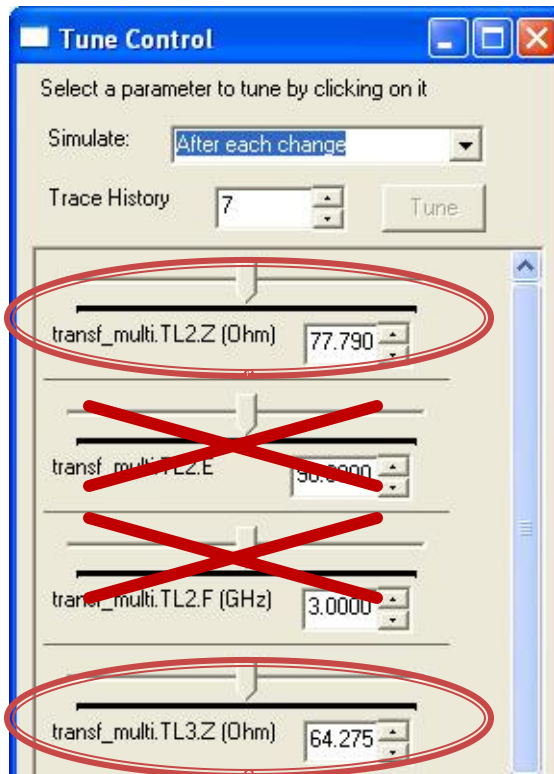
# Mistakes 5


- During tune, due to frustration or haste, for the lines, the **frequencies** or **electrical lengths** are modified



- Always check (**permanently**) that the frequencies (**F**) electrical lengths (**E**) remain the correct ones ( $f_0$  and  $g_0$ ) and only the impedance (**Z**) is tuned
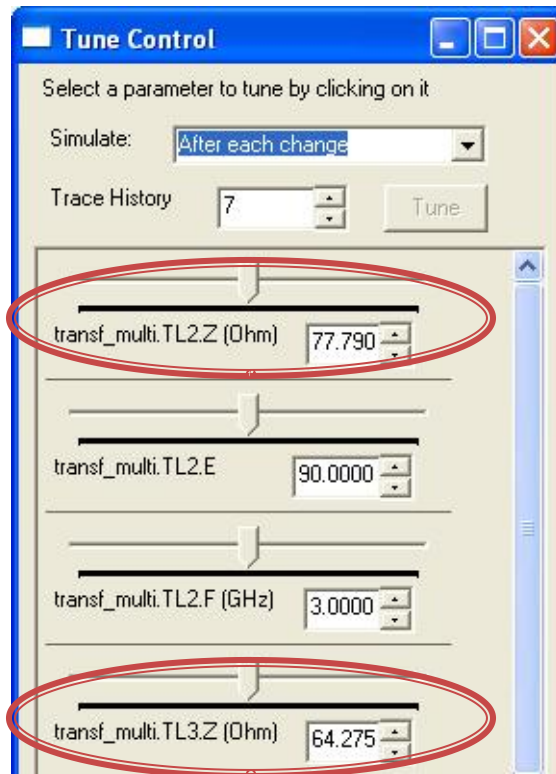
# Mistakes 6


- During tune, the impedances are modified until the monotony rule is breached  $Z_S > Z_1 > Z_2 > Z_3 > Z_L$  **or**  $Z_S < Z_1 < Z_2 < Z_3 < Z_L$



- **Permanently check** that the 5 impedance values are either increasing or decreasing. The 3 transmission line values you tune must be in the **correct order and inside the interval** imposed by  $Z_S$  and  $Z_L$
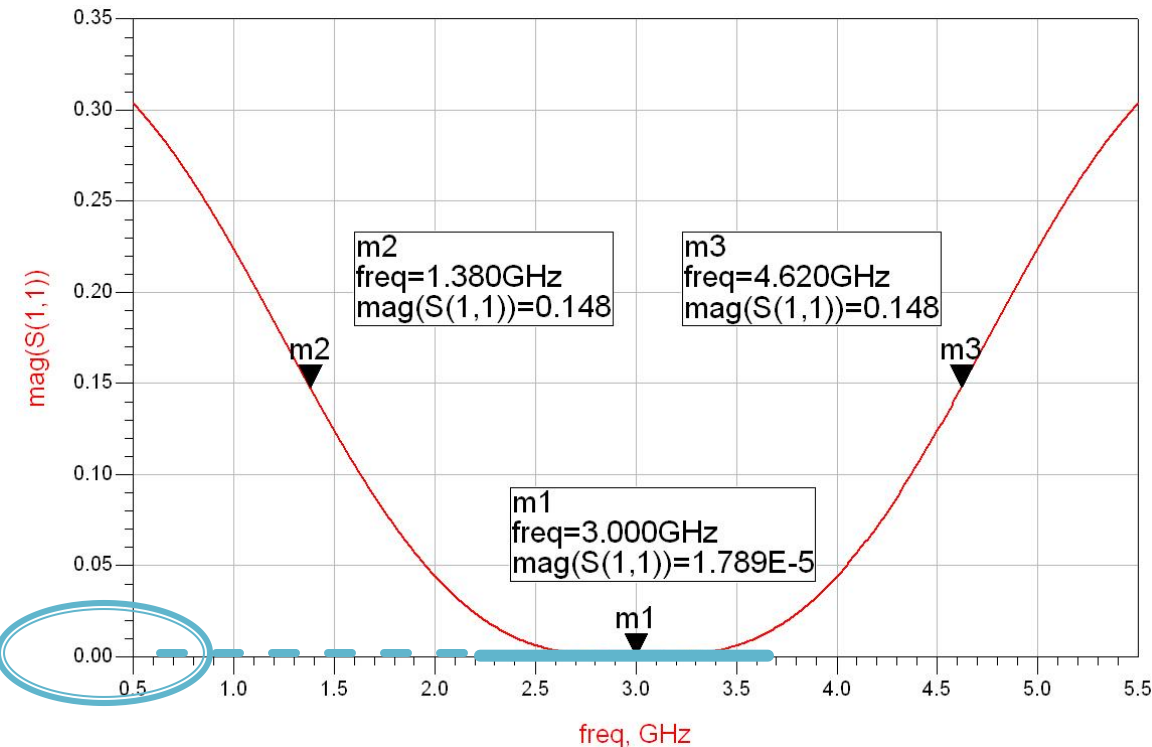
# Mistakes 7


- You don't check the vertical axis against which the reflection coefficient is plotted.



- for the binomial transformer the graph **must not** be pointed/angled in fo but the tangent must be horizontal and reach **0.0** (or at least 0.00X)
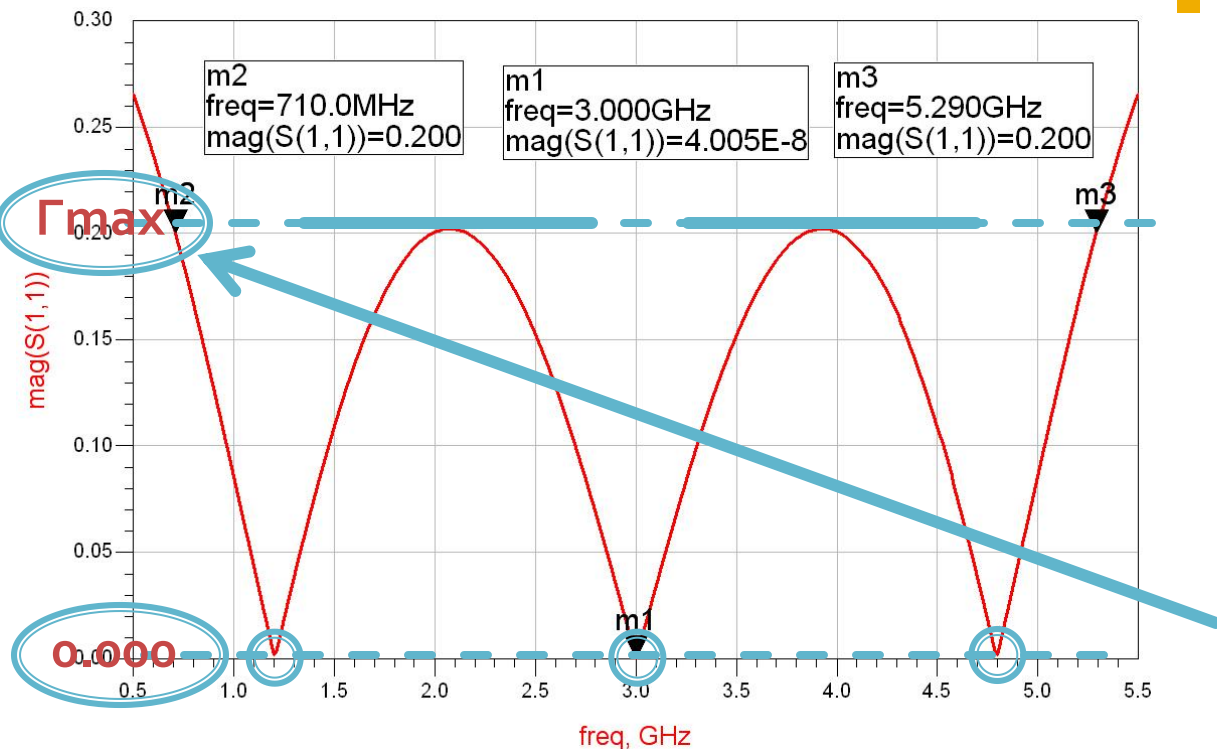
# Mistakes 8

- You don't check the vertical axis against which the reflection coefficient is plotted.



- for the Chebyshev transformer the graph **is** pointed and reaches **0.0** (or at least 0.00X) at **fo and at least two other frequencies** and the ripple inside the bandwidth reaches  **$\Gamma_{\text{max}}$**  (from your individual subject)

# Contact

---

- Laboratorul de microunde si optoelectronica
- <http://rf-opto.etti.tuiasi.ro>
- [rdamian@etti.tuiasi.ro](mailto:rdamian@etti.tuiasi.ro)