**Lecture 10** 2020/2021

# Microwave Devices and Circuits for Radiocommunications

#### 2020/2021

- 2C/1L, MDCR
- Attendance at minimum 7 sessions (course + laboratory)
- Lectures- associate professor Radu Damian
  - Wednesday 15-17, Online, Microsoft Teams
  - E 50% final grade
  - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
    - 3p=+0.5p
  - all materials/equipments authorized

#### **Materials**

- RF-OPTO
  - http://rf-opto.etti.tuiasi.ro
- David Pozar, "Microwave Engineering",
   Wiley; 4th edition, 2011
  - 1 exam problem Pozar
- Photos
  - sent by email/online exam
  - used at lectures/laboratory

# Profile photo

Profile photo – online "exam"

Examene online: 2020/2021

Disciplina: MDC (Microwave Devices and Circuits (Engleza))

#### Pas 3


Nr.	Titlu	Start	Stop	Text
1	Profile photos	03/03/2021; 10:00	08/04/2021; 08:00	Online "exam" created f
2	Mini Test 1 (lecture 2)	03/03/2021; 15:35	03/03/2021; 15:50	The current test consis

### Online

access to online exams requires the password


received by email



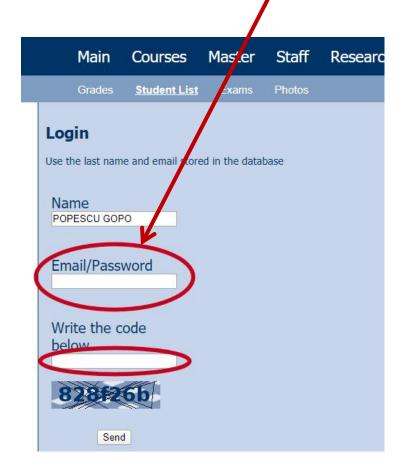

### Online results submission

many numerical values

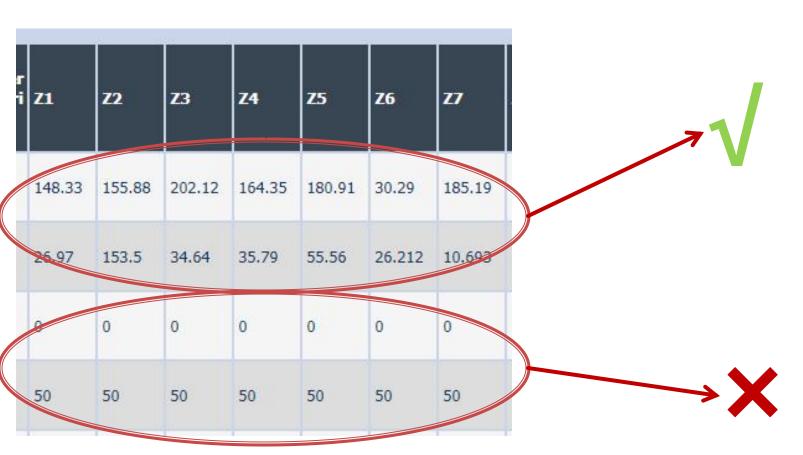


### Online results submission

Grade = Quality of the work + + Quality of the submission


# Important
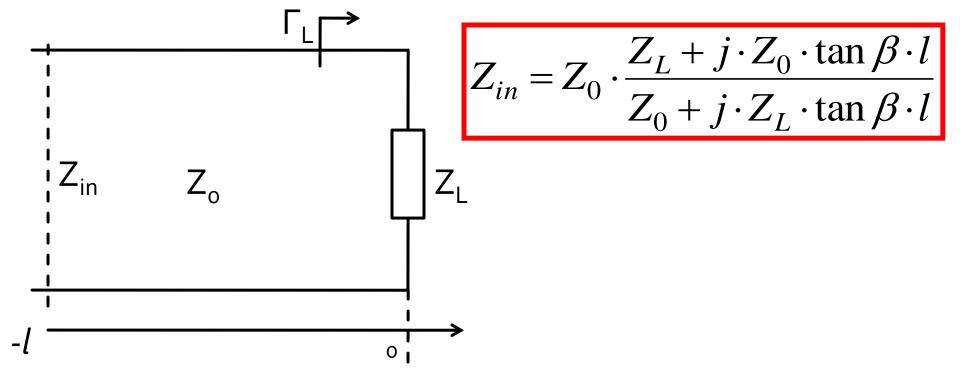
#### The lossless line

• input impedance of a length  $\boldsymbol{l}$  of transmission line with characteristic impedance  $\boldsymbol{Z_o}$ , loaded with an arbitrary impedance  $\boldsymbol{Z_L}$ 



#### The lossless line

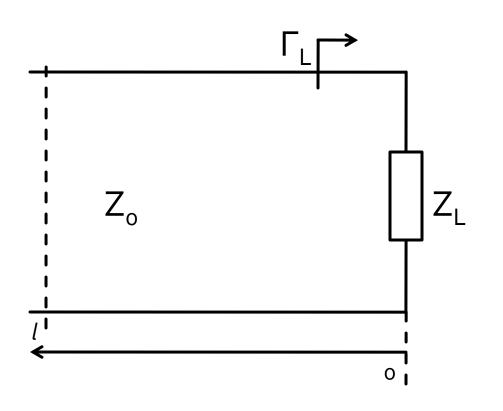

$$V(z) = V_0^+ e^{-j \cdot \beta \cdot z} + V_0^- e^{j \cdot \beta \cdot z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j \cdot \beta \cdot z} - \frac{V_0^-}{Z_0} e^{j \cdot \beta \cdot z}$$

$$Z_L = \frac{V(0)}{I(0)} \qquad Z_L = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \cdot Z_0$$

voltage reflection coefficient

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

-  $Z_o$  real

#### The lossless line

$$V(z) = V_0^+ \cdot \left( e^{-j \cdot \beta \cdot z} + \Gamma \cdot e^{j \cdot \beta \cdot z} \right) \qquad I(z) = \frac{V_0^+}{Z_0} \cdot \left( e^{-j \cdot \beta \cdot z} - \Gamma \cdot e^{j \cdot \beta \cdot z} \right)$$

time-average Power flow along the line


$$P_{avg} = \frac{1}{2} \cdot \text{Re} \left\{ V(z) \cdot I(z)^* \right\} = \frac{1}{2} \cdot \frac{\left| V_0^+ \right|^2}{Z_0} \cdot \text{Re} \left\{ 1 - \Gamma^* \cdot e^{-2j \cdot \beta \cdot z} + \Gamma \cdot e^{2j \cdot \beta \cdot z} - \left| \Gamma \right|^2 \right\}$$

$$P_{avg} = \frac{1}{2} \cdot \frac{\left| V_0^+ \right|^2}{Z_0} \cdot \left( 1 - \left| \Gamma \right|^2 \right)$$

$$(z - z^*) = \text{Im}$$

- Total power delivered to the load = Incident power – "Reflected" power
- Return "Loss" [dB]  $RL = -20 \cdot \log |\Gamma|$  [dB]

## Reflection and power / Model

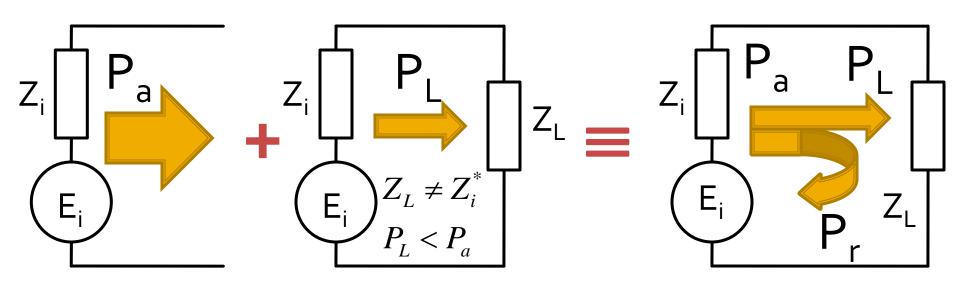

- The source has the ability to sent to the load a certain maximum power (available power) P<sub>a</sub>
- For a particular load the power sent to the load is less than the maximum (mismatch) P<sub>L</sub> < P<sub>a</sub>
- The phenomenon is "as if" (model) some of the power is reflected  $P_r = P_a P_l$
- The power is a scalar!

# Matching, from the point of view of power transmission


$$Z_L = Z_i^*$$

If we choose a real Zo


$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

$$\Gamma_L = \Gamma_i^*$$

- complex numbers
- in the complex plane

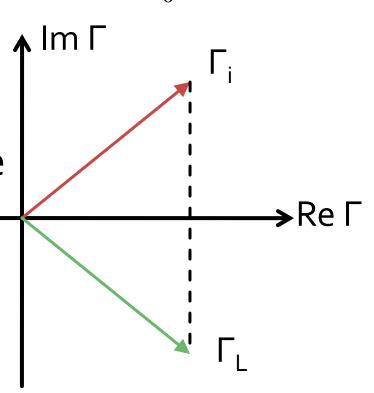

# Scattering matrix – S

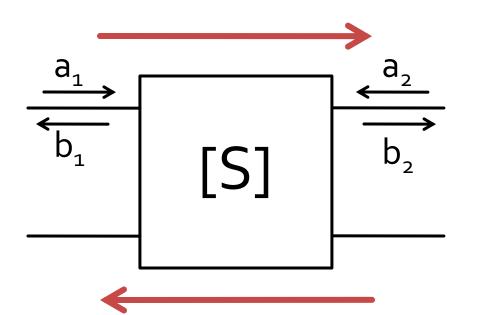


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$


$$|S_{21}|^2 = \frac{Power in Z_0 load}{Power from Z_0 source}$$

- a,b
  - information about signal power AND signal phase
- S<sub>ij</sub>
  - network effect (gain) over signal power including phase information


# Impedance matching

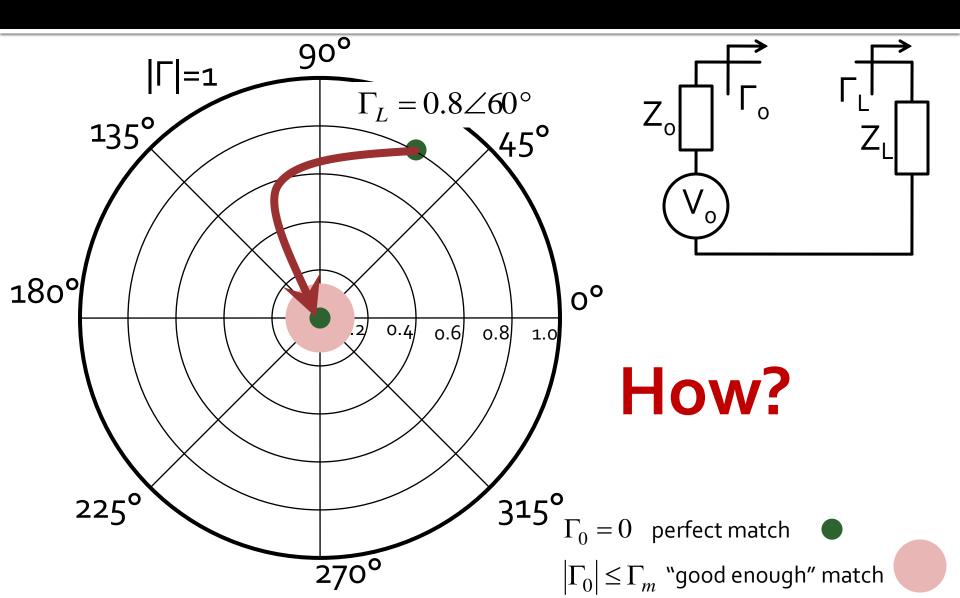

# The Smith Chart

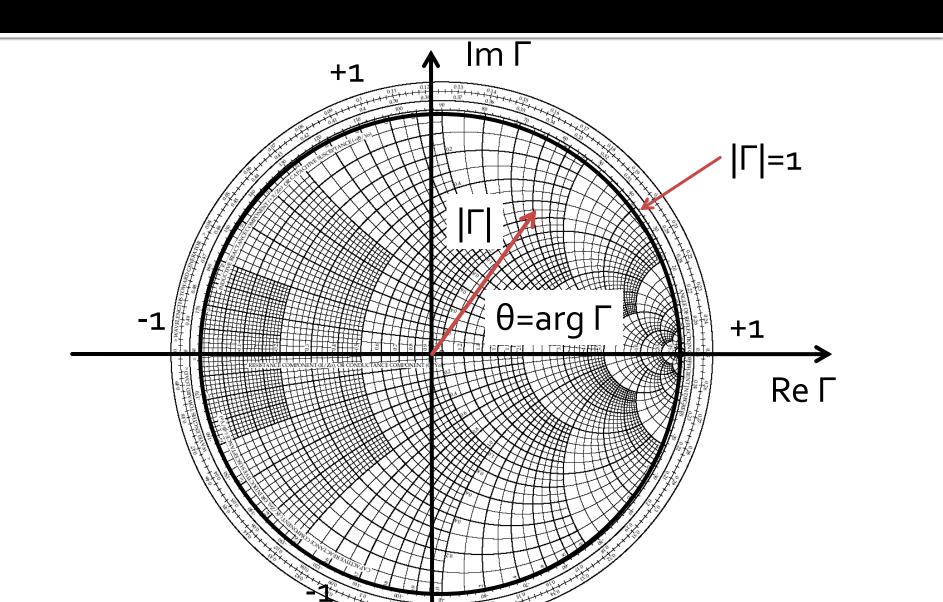


# The Smith Chart

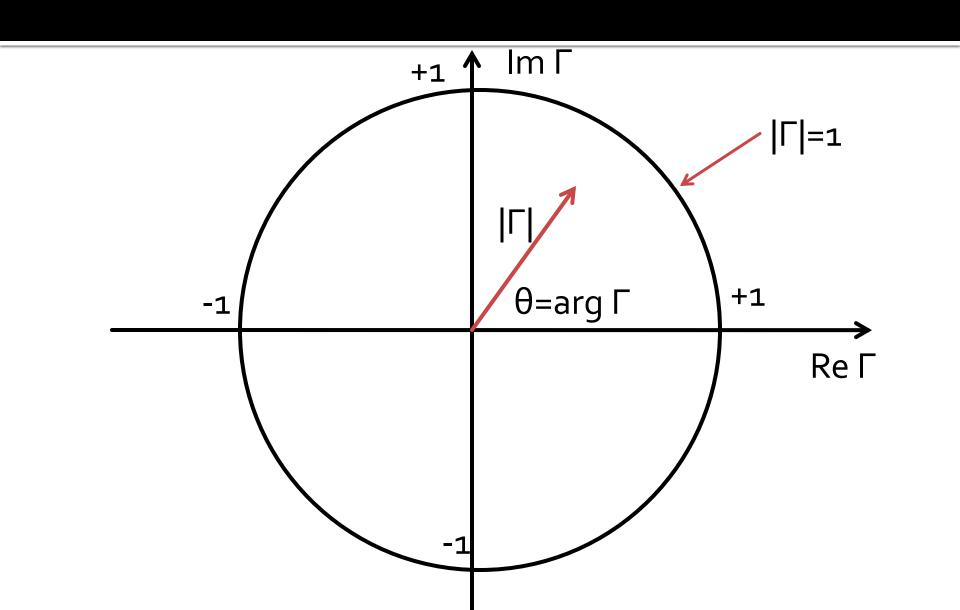


Impedance Matching


# Impedance Matching with Stubs


# Smith chart, r=1 and g=1

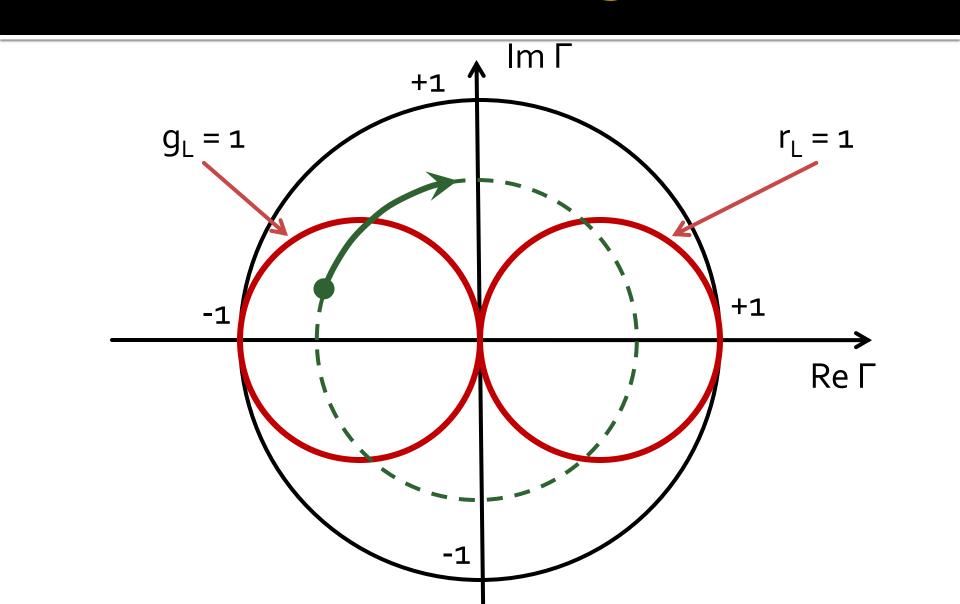



# Impedance Matching with Stubs

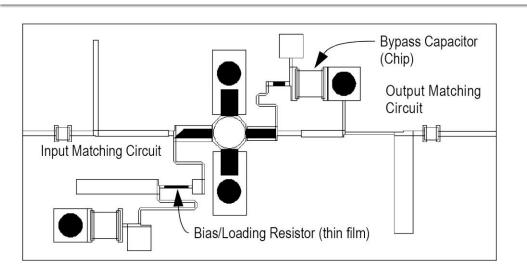

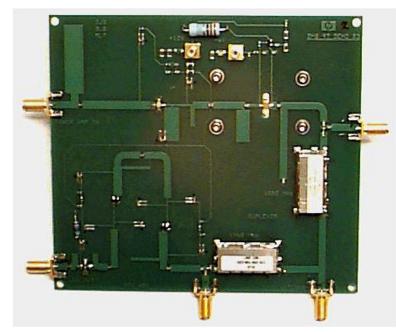

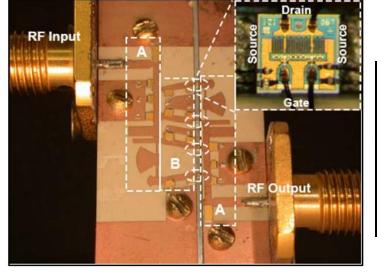

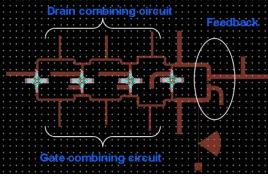

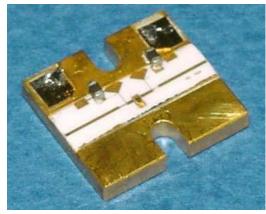


# **Analytical solutions**

Exam / Project

# Case 1, Shunt Stub

#### Shunt Stub

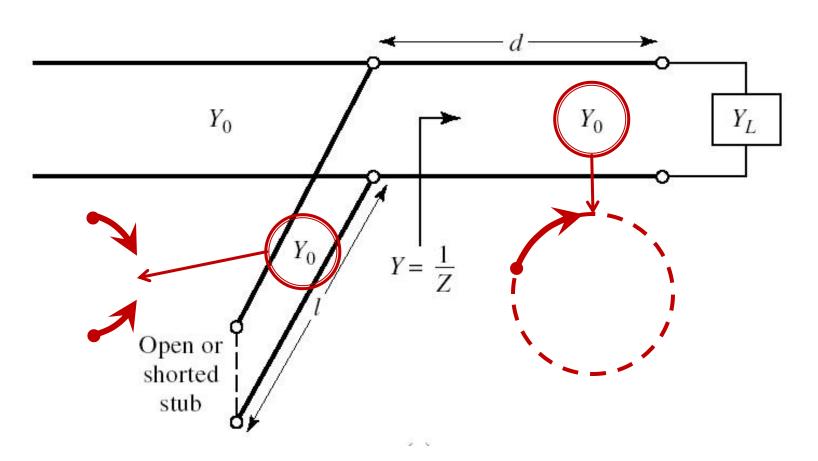

# Analytical solution, usage

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_{\rm s} = 0.593 \angle 46.85^{\circ}$$

$$|\Gamma_{\rm s}| = 0.593; \quad \varphi = 46.85^{\circ}$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.593; \quad \varphi = 46.85^{\circ} \quad \cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^{\circ}$$

The sign (+/-) chosen for the series line equation imposes the sign used for the shunt stub equation


\*\*\* solution (46.85° + 2\theta) = +126.35° 
$$\theta$$
 = +39.7°  $\text{Im } y_S = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.472$ 

$$\theta_{sp} = \tan^{-1}(\text{Im } y_S) = -55.8^{\circ}(+180^{\circ}) \rightarrow \theta_{sp} = 124.2^{\circ}$$

\*-" solution (46.85° + 2
$$\theta$$
) = -126.35°  $\theta$  = -86.6°(+180°)  $\rightarrow \theta$  = 93.4° Im  $y_s = \frac{+2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}}$  = +1.472  $\theta_{sp} = \tan^{-1}(\operatorname{Im} y_s) = 55.8$ °
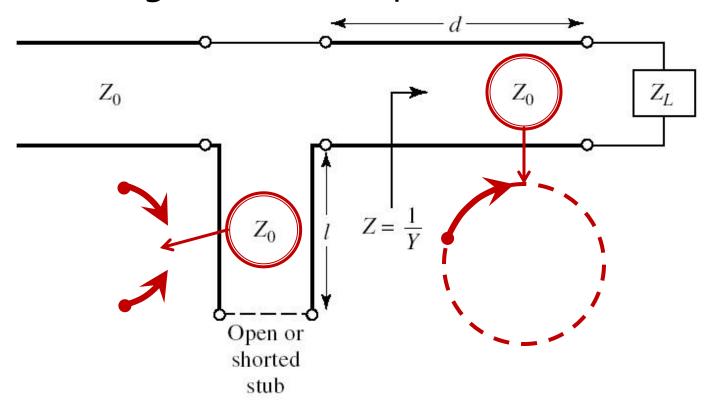
# Case 2, Series Stub

- Series Stub
- difficult to realize in single conductor line technologies (microstrip)



# Analytical solution, usage

$$\cos(\varphi + 2\theta) = |\Gamma_S|$$

$$\theta_{ss} = \beta \cdot l = \cot^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.555 \angle -29.92^{\circ}$$

$$|\Gamma_S| = 0.555; \quad \varphi = -29.92^{\circ} \quad \cos(\varphi + 2\theta) = 0.555 \Rightarrow (\varphi + 2\theta) = \pm 56.28^{\circ}$$

- The sign (+/-) chosen for the series line equation imposes the sign used for the series stub equation
  - \*\*-" solution (-29.92°+2 $\theta$ )=+56.28°  $\theta$ =43.1° Im  $z_S = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1-|\Gamma_S|^2}} = +1.335$  $\theta_{ss} = -\cot^{-1}(\operatorname{Im} z_S) = -36.8$ °(+180°)  $\rightarrow \theta_{ss} = 143.2$ °


\*-" solution  

$$(-29.92^{\circ} + 2\theta) = -56.28^{\circ}$$
  $\theta = -13.2^{\circ}(+180^{\circ}) \rightarrow \theta = 166.8^{\circ}$   
 $\operatorname{Im} z_{s} = \frac{-2 \cdot |\Gamma_{s}|}{\sqrt{1 - |\Gamma_{s}|^{2}}} = -1.335$   $\theta_{ss} = -\cot^{-1}(\operatorname{Im} z_{s}) = 36.8^{\circ}$ 


# Microwave Amplifiers
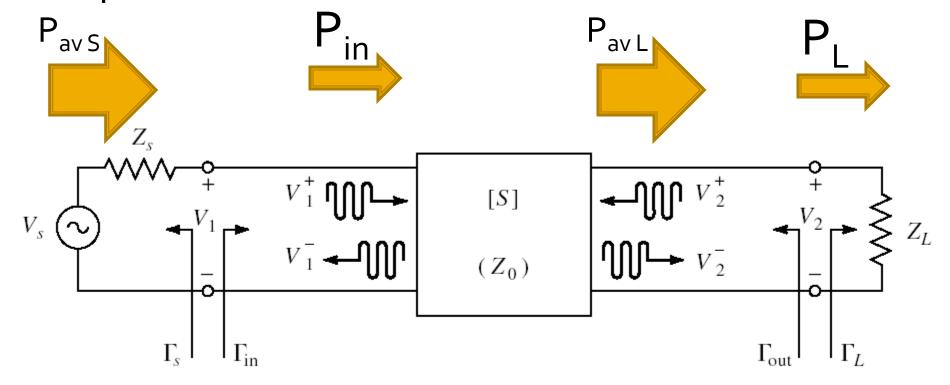
# **Amplifier Power / Matching**

 Two ports in which matching influences the power transfer




# Amplifier as two-port

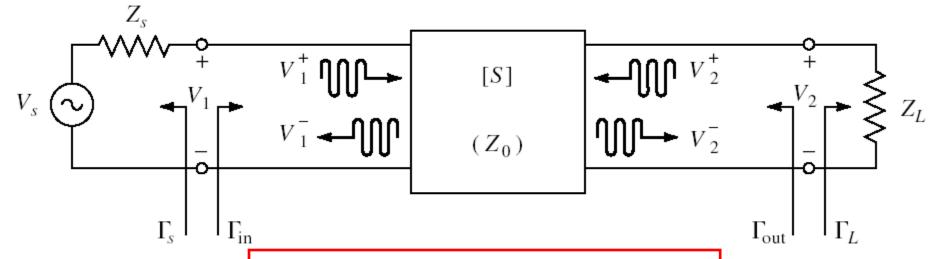

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$


$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

# Input matching circuit

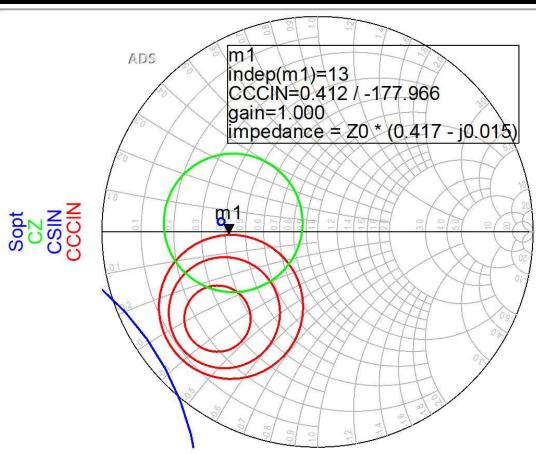


- If we can afford a 1.2dB decrease of the input gain for better NF,Q (Gs = 1 dB), position m1 above is better
- We obtain better (smaller) NF

# Output matching circuit

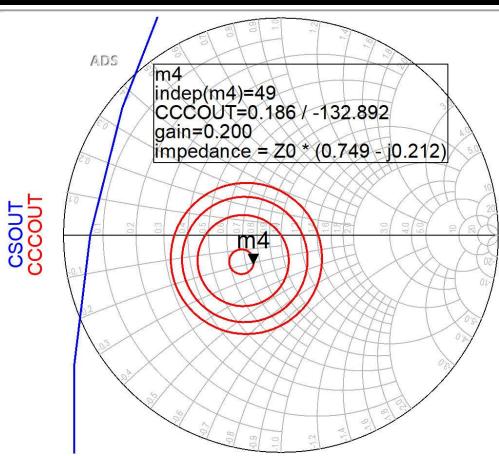


- output constant gain circles CCCOUT: -0.4dB, -0.2dB, odB, +0.2dB
- the lack of noise restrictions allows optimization for better gain (close to maximum – position m4)

# The Smith Chart

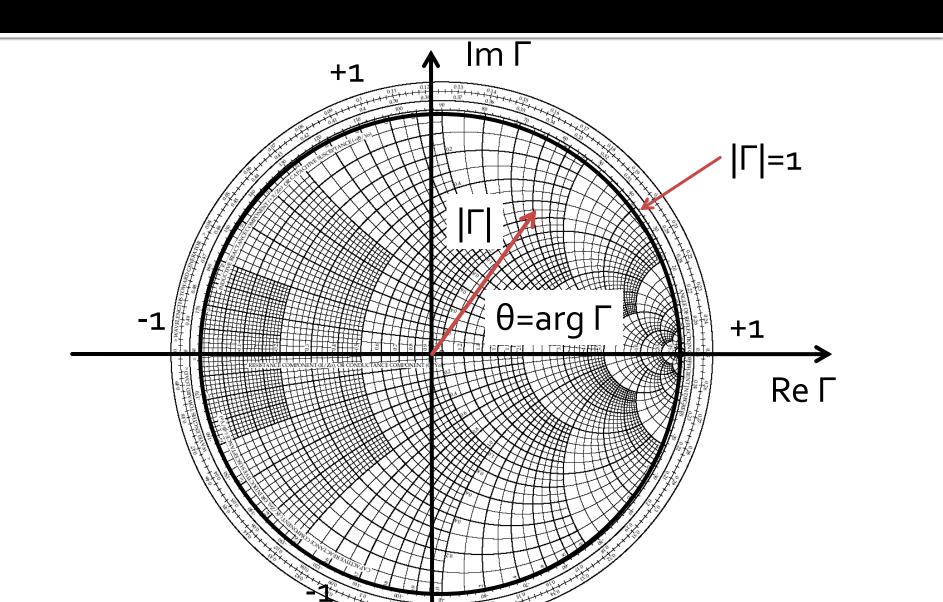

# The Smith Chart

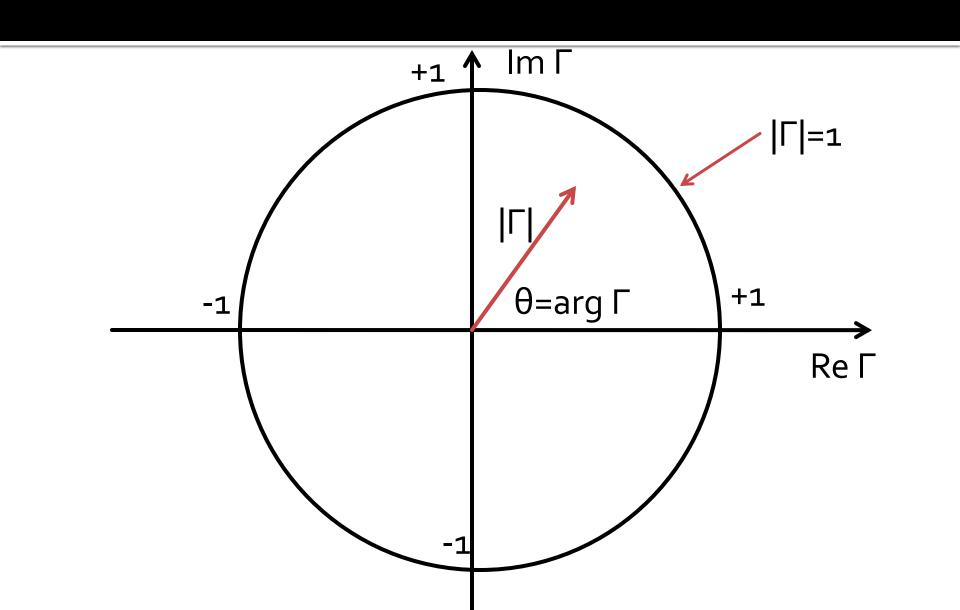


Microwave Amplifiers

# **Broadband amplifiers**

# Broadband/Wideband amplifiers

- Achieved by some design techniques (only at the expense of gain, complexity)
  - Compensated matching networks
  - 2. Resistive matching networks
  - 3. Negative feedback
  - 4. Balanced amplifiers
  - 5. Distributed amplifiers
  - 6. Differential amplifiers

# **Balanced amplifiers**

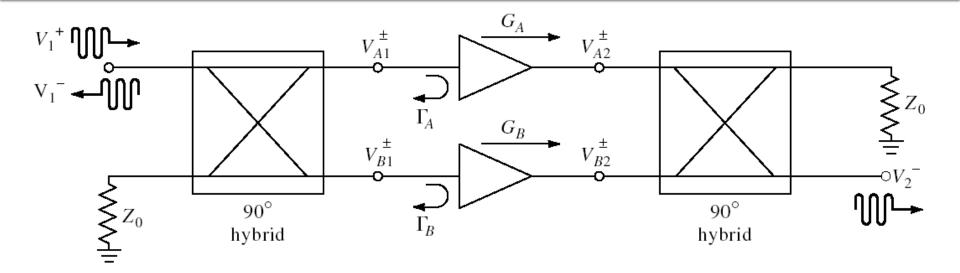

two identical amplifiers with two hybrid couplers
 3 dB / 90° to cancel input and output reflections


$$S_{21} = \frac{-j}{2} \cdot (G_A + G_B)$$

$$F = \frac{1}{2} \cdot (F_A + F_B)$$


$$S_{11} = \frac{1}{2} \cdot (\Gamma_A - \Gamma_B)$$

$$S_{11}|_{A=B} = 0$$

# **Balanced amplifiers**

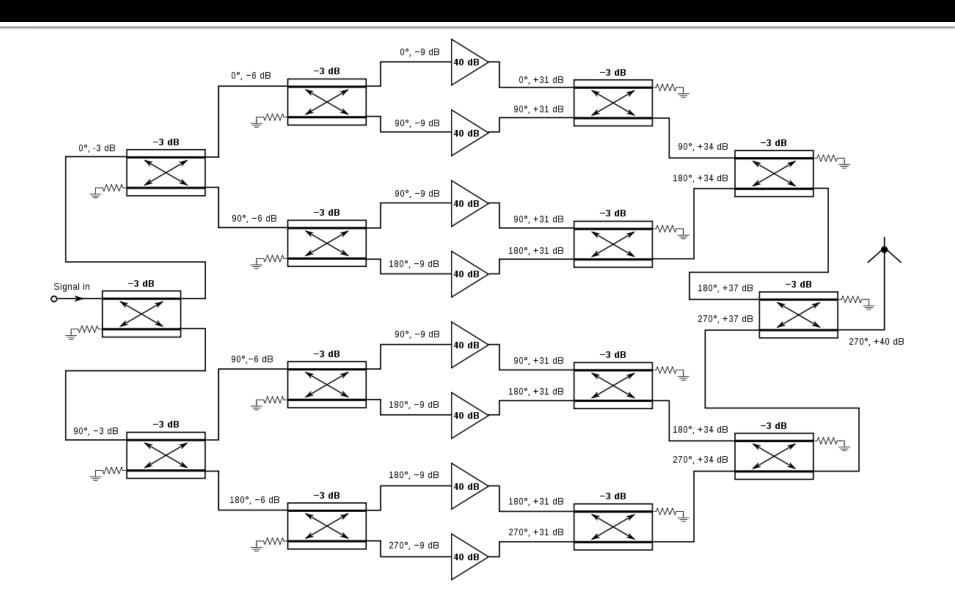

#### Distributed amplifiers

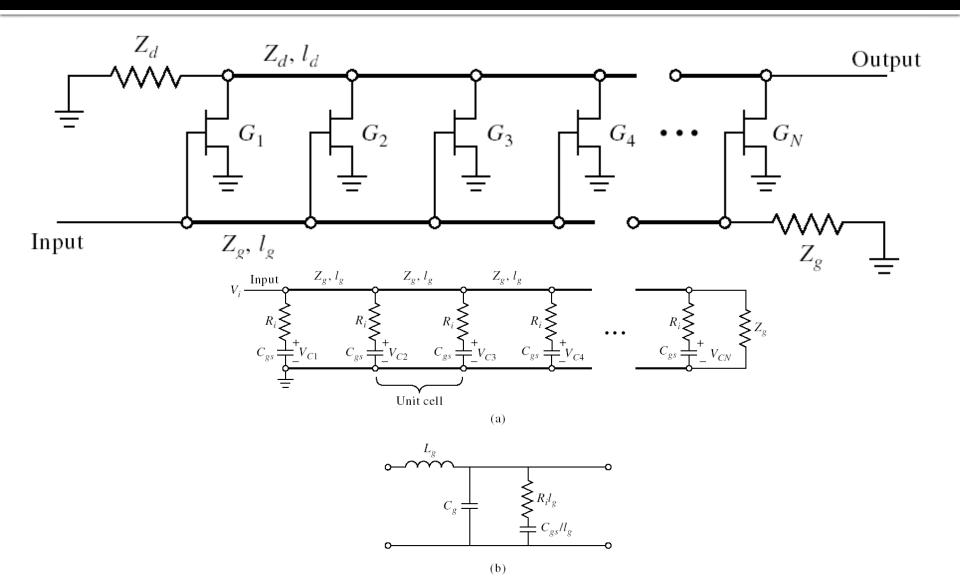

#### Distributed amplifiers

 the phase delays on the gate (input) and drain (output) lines are synchronized

$$\gamma_g = \alpha_g + j \cdot \beta_g$$
  $\gamma_d = \alpha_d + j \cdot \beta_d$   $\beta_g \cdot l_g = \beta_d \cdot l_d$ 


Power gain

$$G = \frac{g_m^2 \cdot Z_d \cdot Z_g}{4} \cdot \frac{\left(e^{-N \cdot \alpha_g \cdot l_g} - e^{-N \cdot \alpha_d \cdot l_d}\right)^2}{\left(e^{-\alpha_g \cdot l_g} - e^{-\alpha_d \cdot l_d}\right)^2}$$

Lossless power gain

$$G = \frac{g_m^2 \cdot Z_d \cdot Z_g \cdot N^2}{4}$$


#### Distributed amplifiers

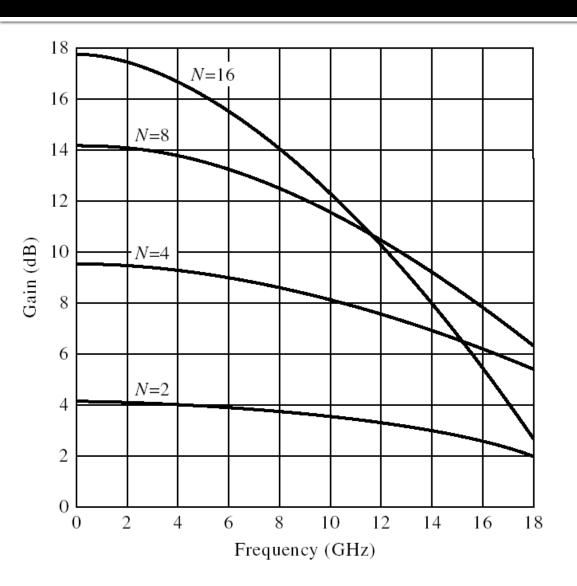


$$N_{opt} = \frac{\ln(\alpha_g \cdot l_g) - \ln(\alpha_d \cdot l_d)}{\alpha_g \cdot l_g - \alpha_d \cdot l_d}$$
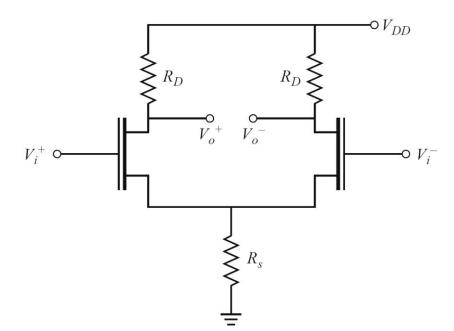
#### Differential amplifiers


- In differential mode the input capacitances of the two transistors are connected in series
- Unity gain frequency is doubled



#### Differential amplifiers

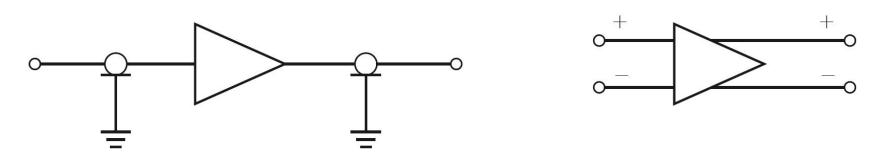


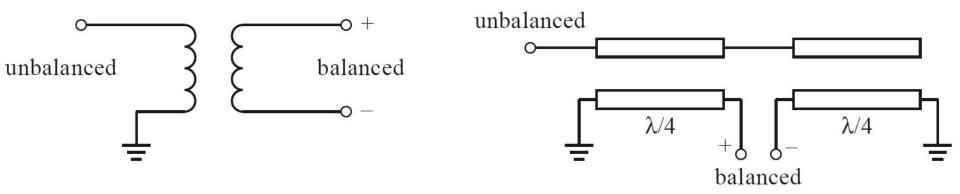- We use circuits to transition from an unbalanced signal to a balanced signal (or vice versa)
  - hybrid couplers 3dB / 180°
  - "balun" (balanced unbalanced)


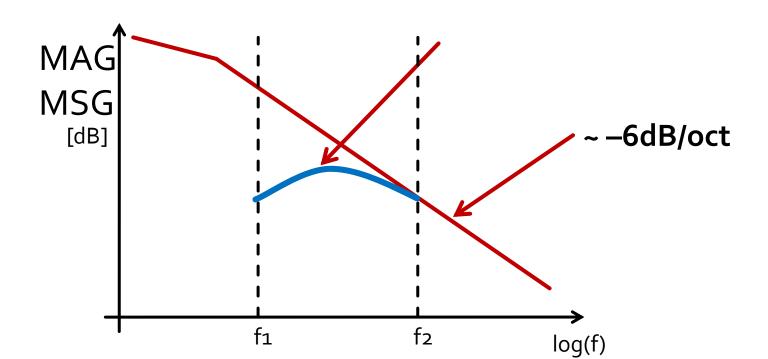
#### Compensated matching networks

 Control the design of the matching networks at more (at least 2) frequencies and impose the same gain




Microwave Amplifiers

# Multistage Amplifier Design

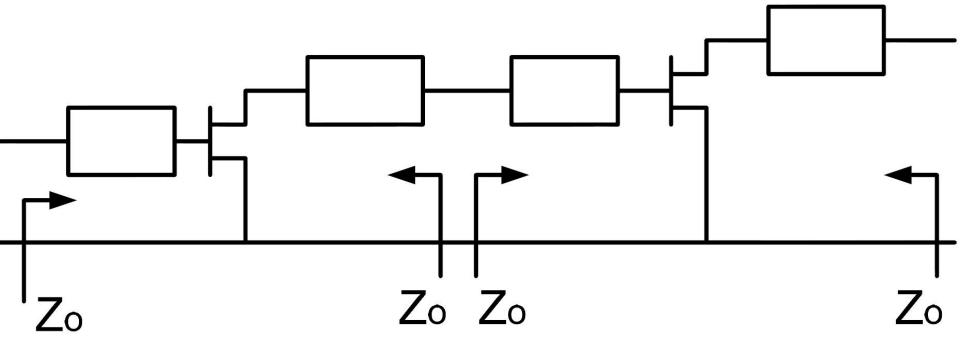
## Multistage amplifiers

- Interstage matching can be designed in two modes:
  - Each stage is matched to a virtual  $\Gamma = 0$


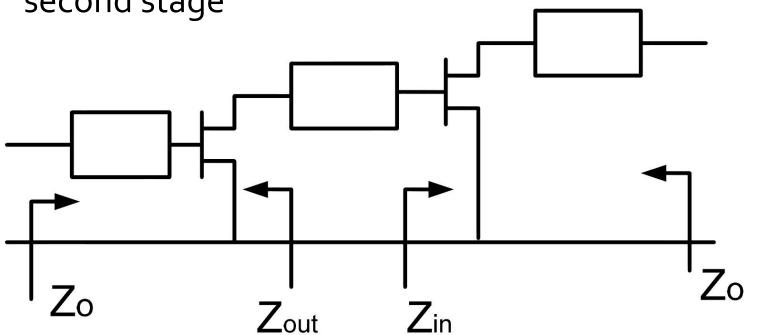
## Multistage amplifiers

- Interstage matching can be designed in two modes:
  - One stage is matched to offer necessary Γ for the second stage




#### Example multistage LNA

- Similar to the project assignment
- LNA using ATF-34143 providing:
  - G = 20dB
  - F = 1dB
  - @f = 5GHz
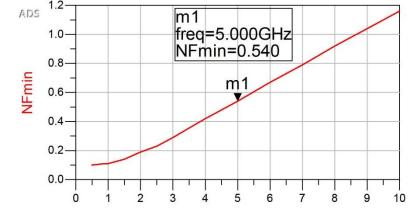
#### Example

- ATF-34143 at Vds=3V Id=20mA.
- @5GHz
  - S11 =  $0.64\angle 139^{\circ}$
  - $S12 = 0.119 \angle -21^{\circ}$
  - S21 =  $3.165 \angle 16^{\circ}$
  - $S22 = 0.22 \angle 146^{\circ}$
  - Fmin = 0.54 (typically[dB]!)
  - $\Gamma_{\text{opt}} = 0.45 \angle 174^{\circ}$
  - $r_n = 0.03$





#### Example, LNA @ 5 GHz

- ATF-34143 at Vds=3V Id=20mA.
- @5GHz
  - $S11 = 0.64 \angle 139^{\circ}$
  - $S12 = 0.119 \angle -21^{\circ}$
  - S21 =  $3.165 \angle 16^{\circ}$
  - $S22 = 0.22 \angle 146^{\circ}$
  - Fmin = 0.54 (tipic [dB]
  - $\Gamma_{\text{opt}} = 0.45 \angle 174^{\circ}$
  - $r_n = 0.03$

```
!ATF-34143
!S-PARAMETERS at Vds=3V Id=20mA. LAST UPDATED 01-29-99
# ghz s ma r 50
2.0 0.75 -126 6.306 90 0.088 23 0.26 -120
2.5 0.72 -145 5.438 75 0.095 15 0.25 -140
3.0 0.69 -162 4.762 62 0.102 7 0.23 -156
4.0 0.65 166 3.806 38 0.111 -8 0.22 174
5.0 0.64 139 3.165 16 0.119 -21 0.22 146
6.0 0.65 114 2.706 -5 0.125 -35 0.23 118
7.0 0.66 89 2.326 -27 0.129 -49 0.25 91
8.0 0.69 67 2.017 -47 0.133 -62 0.29 67
9.0 0.72 48 1.758 -66 0.135 -75 0.34 46
!FREQ Fopt GAMMA OPT
                            RN/Zo
!GHZ dB MAG ANG -
2.0 0.19 0.71 66 0.09
2.5 0.23 0.65 83 0.07
3.0 0.29 0.59 102 0.06
4.0 0.42 0.51 138 0.03
5.0 0.54 0.45 174 0.03
6.0 0.67 0.42 -151 0.05
7.0 0.79 0.42 -118 0.10
8.0 0.92 0.45 -88 0.18
```

9.0 1.04 0.51 -63 0.30 10.0 1.16 0.61 -43 0.46

#### Multistage amplifiers

- If we need more power gain than only one transistor can supply
  - design target 2odB
  - MAG @5GHz = 14.248 dB < 20dB</p>
- We use Friis formula to separate the target:
  - Power gain
  - Noise
- on two amplifier stages

$$F_{cas} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 \cdot G_2} + \frac{F_4 - 1}{G_1 \cdot G_2 \cdot G_3} + \cdots$$

- Effects of Friis Formula:
  - it's essential that the first stage is as noiseless as possible even if that means sacrificing power
  - the second stage can be optimized for power gain
- Friis Formula must be used in linear scale!
- Avago/Broadcom AppCAD
  - AppCAD Free Design Assistant Tool for Microsoft Windows → Google

$$G_{cas} = G_1 \cdot G_2$$
  $F_{cas} = F_1 + \frac{1}{G_1} (F_2 - 1)$ 

- Friis formula
  - first stage: low noise factor, probably resulting in a smaller gain
  - second stage: high gain, probably resulting in higher noise factor
- It's essential to introduce a design margin (reserve:  $\Delta F$ ,  $\Delta G$ )
  - $G = G_{design} + \Delta G$
  - $F = F_{design} \Delta F$
- Interpretation of the design target
  - G > G<sub>design</sub>, better, but it's not required to sacrifice other parameters to maximize the gain
  - F < F<sub>design</sub>, better, the smaller the better, we must target the smallest possible noise factor as long as the other design parameters are met

- Friis formula
  - first stage: low noise factor, probably resulting in a smaller gain
  - second stage: high gain, probably resulting in higher noise factor
- Separation of the design parameters on the 2 amplification stages (Estimated!)
  - input stage: F1 = 0.7 dB, G1 = 9 dB
  - output stage: F2 = 1.2 dB, G2 = 13 dB
- To verify the result apply Friis formula
- First transform to linear scale!

$$F_{1} = 10^{\frac{F_{1}[dB]}{10}} = 10^{0.07} = 1.175$$

$$F_{2} = 10^{\frac{G_{1}[dB]}{10}} = 10^{0.12} = 1.318$$

$$F_{2} = 10^{-10} = 10^{0.12} = 1.318$$

$$G_{1} = 10^{\frac{G_{1}[dB]}{10}} = 10^{0.9} = 7.943$$

$$G_{2} = 10^{-10} = 10^{1.3} = 19.953$$


$$F_{cas} = F_{1} + \frac{1}{G_{1}}(F_{2} - 1) = 1.215$$

$$G_{cas} = G_{1} \cdot G_{2} = 158.49$$

$$F_{cas} = 10 \cdot \log(1.215) = 0.846 \ dB$$

$$G_{cas} = 10 \cdot \log(158.49) = 22 \ dB$$


#### Avago/Broadcom AppCAD

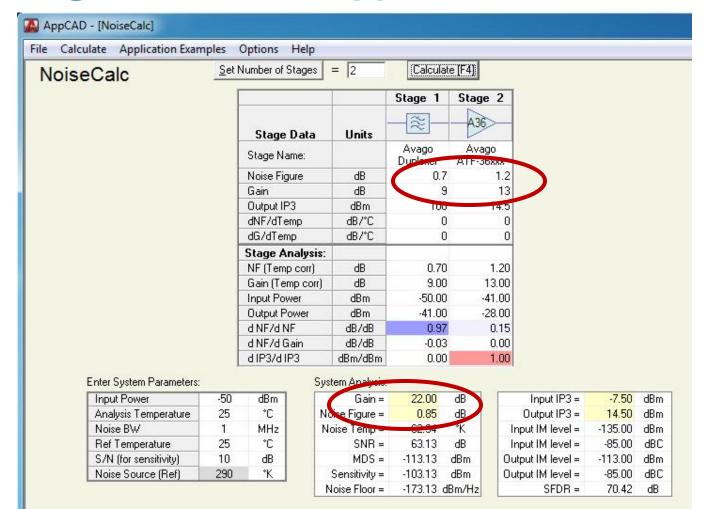


#### Multistage amplifier design

- Separation of the design parameters on the 2 amplification stages (Estimated!)
  - input stage: F1 = 0.7 dB, G1 = 9 dB
  - output stage: F2 = 1.2 dB, G2 = 13 dB
  - total: F = 0.85 dB, G = 22 dB
- Meets design specifications (with design margin)
- We can reuse some of the results in the single stage LNA design (Lecture 8)
  - input matching can be used for the input of the first stage very low noise, good enough power gain
  - output matching was designed for maximum gain, can be used for the output of the second stage
  - input and output matching were designed for  $50\Omega$  source and load, similar to current conditions


#### Multistage amplifier design

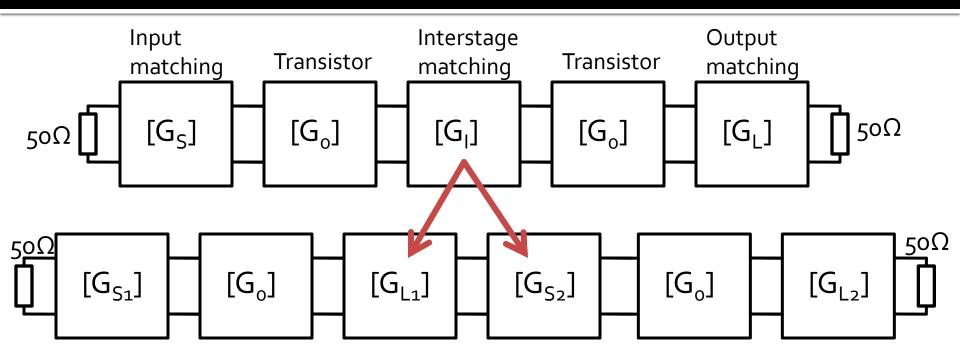

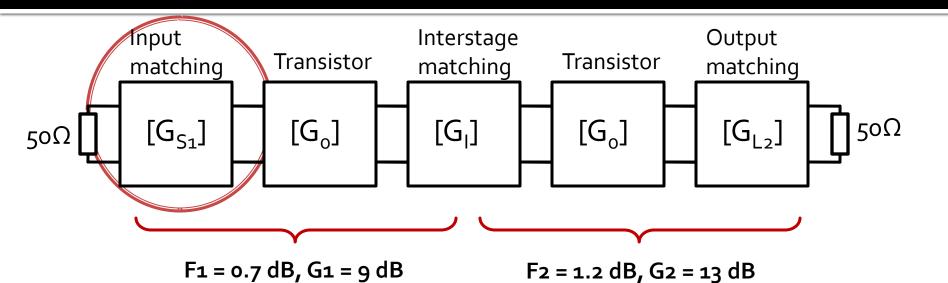
- Gain computation
  - Interstage matching can supplement the gain for both amplifier stages
  - The design for input and output matching must be achieved on a single transistor schematic (recommended: easier)



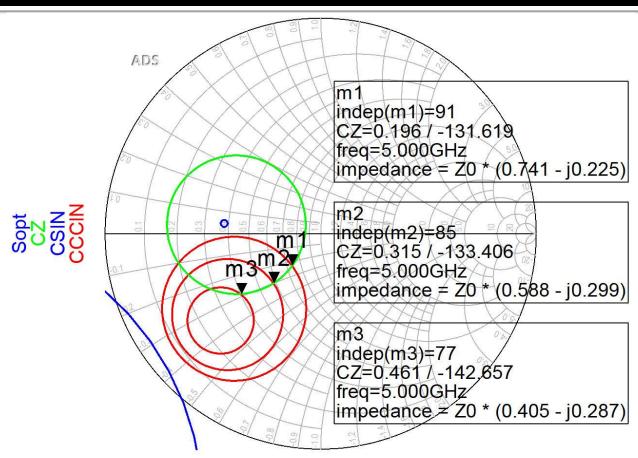- We favor optimization for noise (low/minimum)
- Also considered
  - Power gain (can be lower, but not too much)
  - Bandwidth (through Q, quality factor)
  - Stability



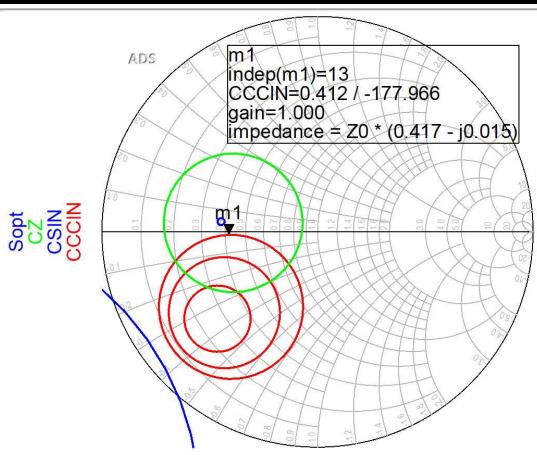- For the input matching circuit
  - noise circle CZ: 0.75dB
  - input constant gain circles CCCIN: 1dB, 1.5dB, 2 dB
- We choose (small Q → wide bandwidth) position m1



- If we can afford a 1.2dB decrease of the input gain for better NF,Q (Gs = 1 dB), position m1 above is better
- We favor better (smaller) NF

G<sub>S1</sub>: Position m1 in complex plane, 1dB

$$\Gamma_{S} = 0.412 \angle -178^{\circ} \qquad |\Gamma_{S}| = 0.412; \quad \varphi = -178^{\circ}$$


$$\cos(\varphi + 2\theta) = -|\Gamma_{S}| \qquad \operatorname{Im}[y_{S}(\theta)] = \frac{\mp 2 \cdot |\Gamma_{S}|}{\sqrt{1 - |\Gamma_{S}|^{2}}}$$

$$\cos(\varphi + 2\theta) = -0.412 \Rightarrow \qquad (\varphi + 2\theta) = \pm 114.33^{\circ}$$

$$\theta_{sp} = \tan^{-1}(\operatorname{Im}[y_{S}(\theta)]) = \tan^{-1}\left(\frac{\mp 2 \cdot |\Gamma_{S}|}{\sqrt{1 - |\Gamma_{S}|^{2}}}\right)$$

$$(\varphi + 2\theta) = \begin{cases} +114.33^{\circ} \\ -114.33^{\circ} \end{cases} \theta = \begin{cases} 146.2^{\circ} \\ 31.8^{\circ} \end{cases} \operatorname{Im}[y_{S}(\theta)] = \begin{cases} -0.904 \\ +0.904 \end{cases} \theta_{sp} = \begin{cases} 137.9^{\circ} \\ 42.1^{\circ} \end{cases}$$

## Output matching stage 2 (L2)

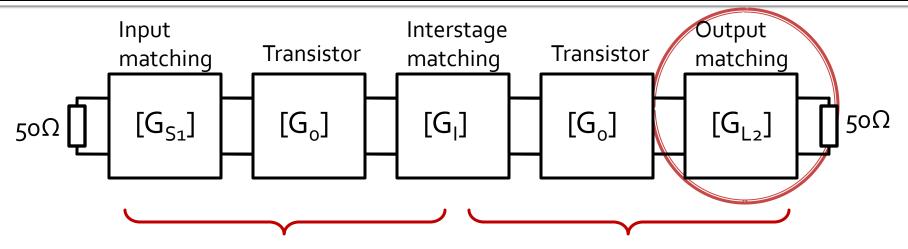


F1 = 0.7 dB, G1 = 9 dB

 $F_2 = 1.2 \text{ dB}, G_2 = 13 \text{ dB}$ 

- We favor optimization for gain (high/maximum)
- Also considered
  - Bandwidth (through Q, quality factor)
  - Stability
- noise is not an issue, output matching doesn't influence noise factor

## Output matching stage 2 (L2)

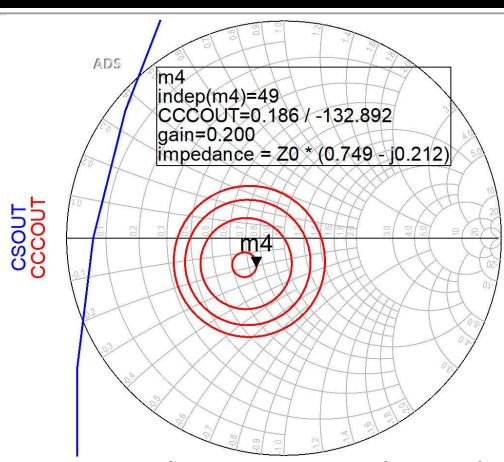

- output constant gain circles CCCOUT: -0.4dB, -0.2dB, odB, +0.2dB
- The lack of noise restrictions allows optimization for better gain (close to maximum – position m4)

## Output matching stage 2 (L2)

G<sub>L2</sub>: Position m<sub>4</sub> in complex plane, o.2dB


$$\Gamma_{L} = 0.186 \angle -132.9^{\circ} \qquad |\Gamma_{L}| = 0.186; \quad \varphi = -132.9^{\circ}$$

$$\cos(\varphi + 2\theta) = -|\Gamma_{L}| \qquad \operatorname{Im}[y_{L}(\theta)] = \frac{-2 \cdot |\Gamma_{L}|}{\sqrt{1 - |\Gamma_{L}|^{2}}} = -0.379$$

$$\cos(\varphi + 2\theta) = -0.186 \implies (\varphi + 2\theta) = \pm 100.72^{\circ}$$

$$\theta_{sp} = \tan^{-1}(\operatorname{Im}[y_{L}(\theta)]) = \tan^{-1}\left(\frac{\mp 2 \cdot |\Gamma_{L}|}{\sqrt{1 - |\Gamma_{L}|^{2}}}\right)$$
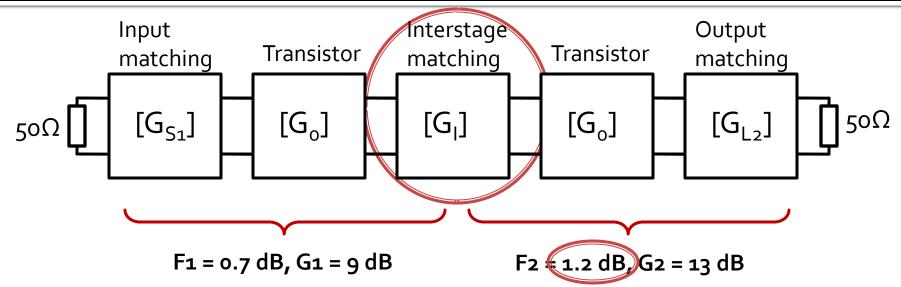
$$(\varphi + 2\theta) = \begin{cases} +100.72^{\circ} \\ -100.72^{\circ} \end{cases} \theta = \begin{cases} 116.8^{\circ} \\ 16.1^{\circ} \end{cases} \operatorname{Im}[y_{L}(\theta)] = \begin{cases} -0.379 \\ +0.379 \end{cases} \theta_{sp} = \begin{cases} 159.3^{\circ} \\ 20.7^{\circ} \end{cases}$$



- We take into account gain (high) but also noise
- Also considered
  - Bandwidth (through Q, quality factor)
  - Stability
- We influence the noise factor of the second stage, the noise must be considered but with less restrictive conditions (Friis shows that higher noise is acceptable).

#### Multistage amplifier

Power gain


$$G_{T}[dB] = G_{S1}[dB] + G_{0}[dB] + G_{I}[dB] + G_{0}[dB] + G_{I}[dB]$$

$$G_{0} = |S_{21}|^{2} = 10.017 = 10.007 dB$$


$$G_{T}[dB] = 1 dB + 10 dB + G_{I}[dB] + 10 dB + 0.2 dB$$

$$G_{T}[dB] = 21.2 dB + G_{I}[dB]$$

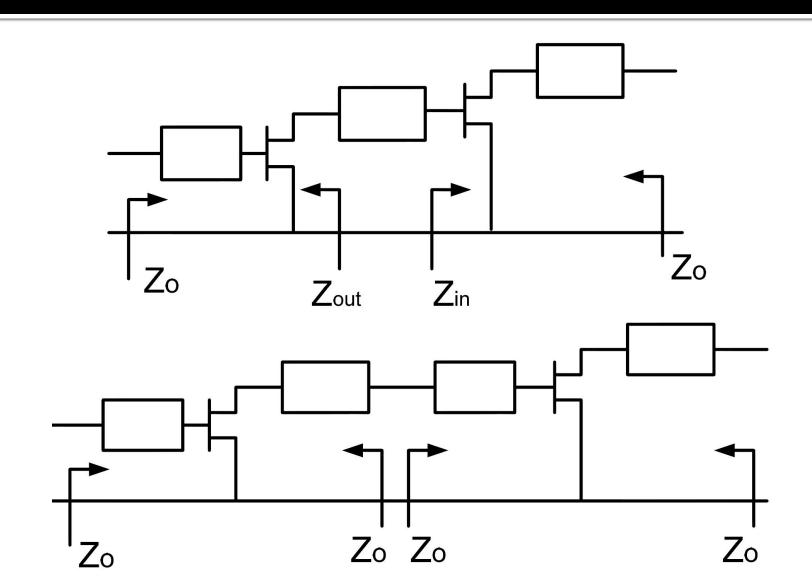Interstage match design must provide at least o.8dB gain to meet specifications, by better match for the output of the first transistor and for the input of the second transistor




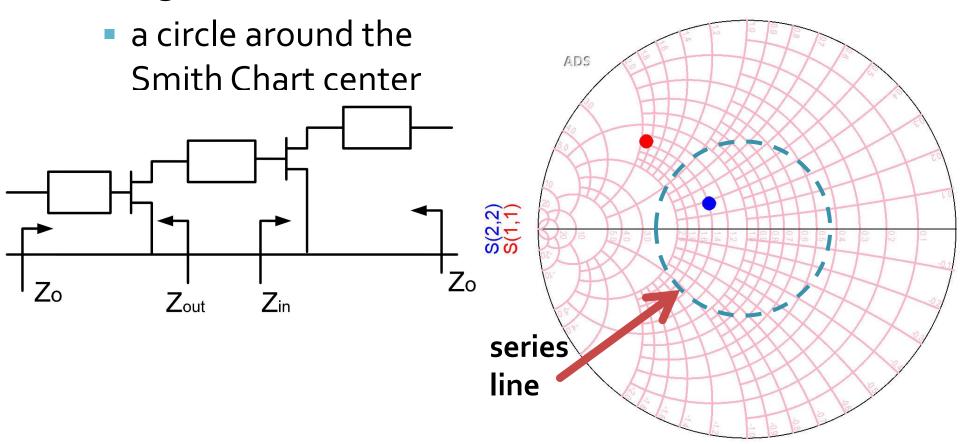
 A single transmission line keeps constant the magnitude of the reflection coefficient



- Can be designed in two ways:
  - starting from the output of the first stage (reflection coefficient S22\*) towards the circles (drawn for the second stage):
    - stability
    - gain
    - noise
  - starting from the input of the second stage (reflection coefficient S11\*) towards the circles (drawn for the first stage):
    - stability
    - gain
- First design direction has the advantage to offer control over the noise introduced by the second stage

Starting point – complex conjugate

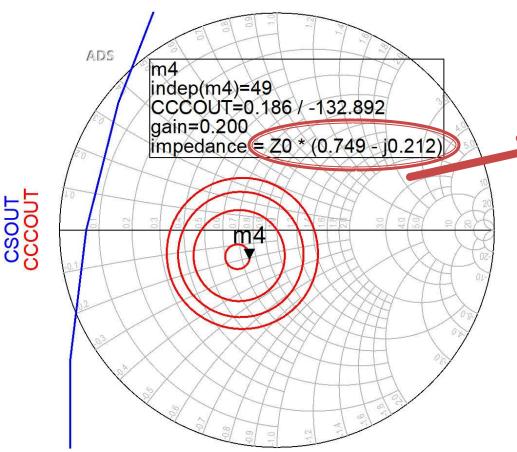

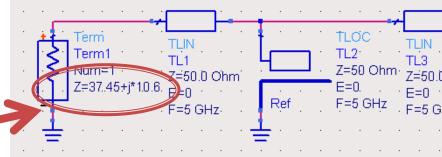


$$Z = 50\Omega \cdot (0.749 - j \cdot 0.212)$$


$$Z = 37.45\Omega - j \cdot 10.6\Omega$$


$$Z^* = 37.45\Omega + j \cdot 10.6\Omega$$

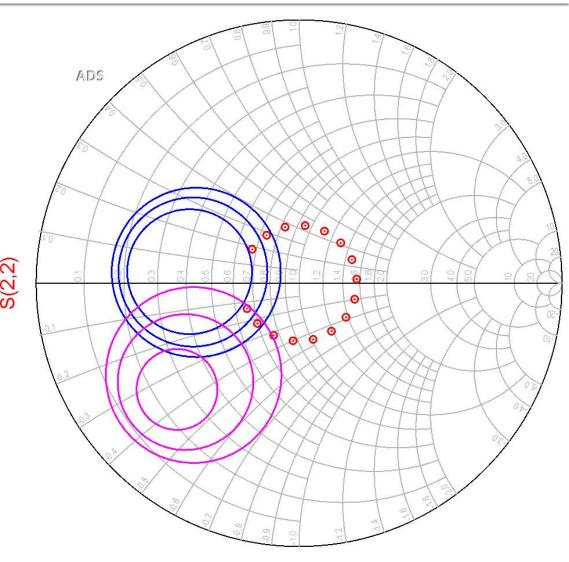- A single transmission line allows reaching a point that cannot be optimized
  - $G_{L_1} = 0.2dB$
  - $G_{S_2} = 1 dB$
  - $F_2 = 0.7 \, dB$
- Only one parameter is available for wide band performance tuning





#### **ADS**

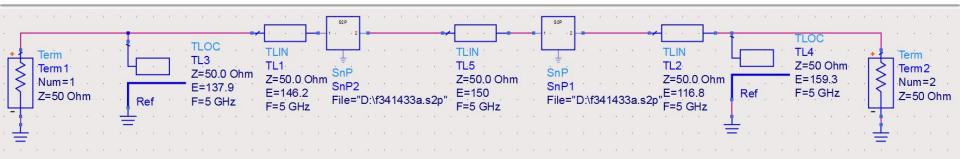

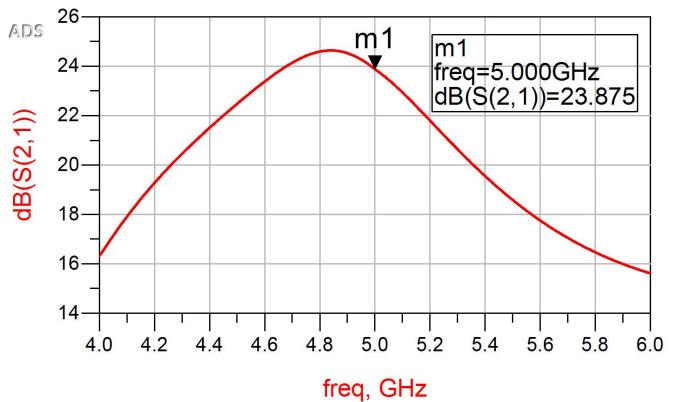



#### **ADS**

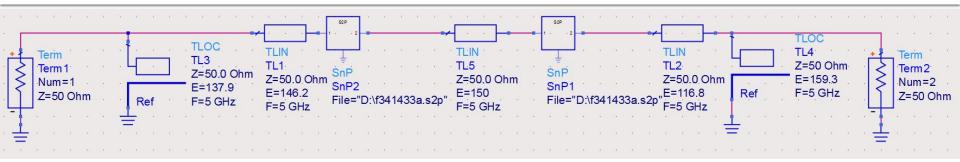

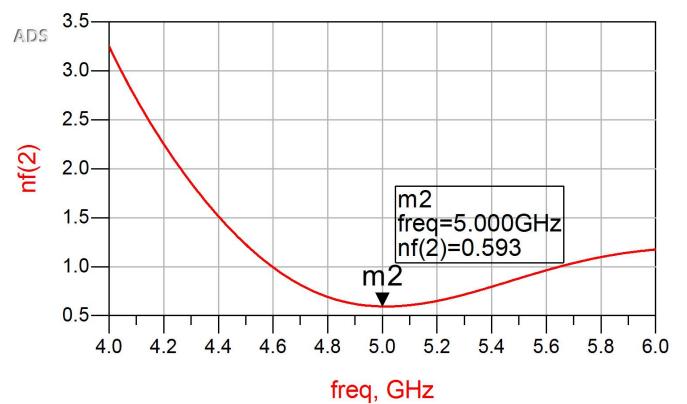

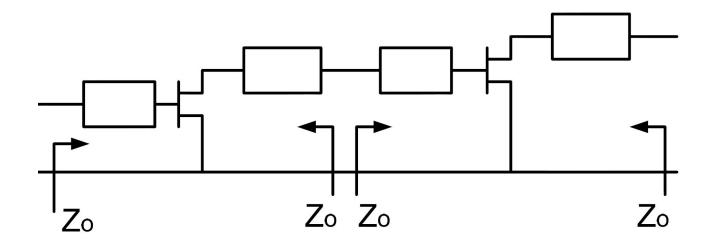 Using multiple transmission lines for matching each stage to a intermediate Γ=ο (virtual) allows detailed control over final reflection coefficient (and thus gain/noise)



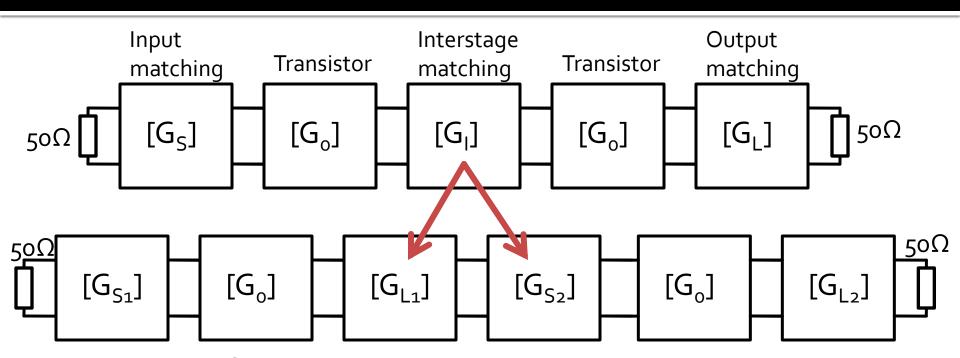

- Instead of a single match design we have to design two matching networks
- However both matching networks are anchored to a fixed point ( $50\Omega$ ,  $\Gamma$ =0) so we can use design **formulas** (Impedance Matching with Stubs)
- Also, due to the presence of multiple networks, we can target precise positions (reflection coefficients) on both stages

### Multistage amplifier

Power gain


$$G_{T}[dB] = G_{S1}[dB] + G_{0}[dB] + G_{L1}[dB] + G_{S2}[dB] + G_{0}[dB] + G_{L2}[dB]$$

$$G_{T}[dB] = 1 dB + 10 dB + G_{L1}[dB] + G_{S2}[dB] + 10 dB + 0.2 dB$$


$$G_{T}[dB] = 21.2 dB + G_{L1}[dB] + G_{S2}[dB]$$

 Interstage match design must provide at least o.8dB in total gain to meet specifications, by separately better matching the output of the first transistor and for the input of the second transistor

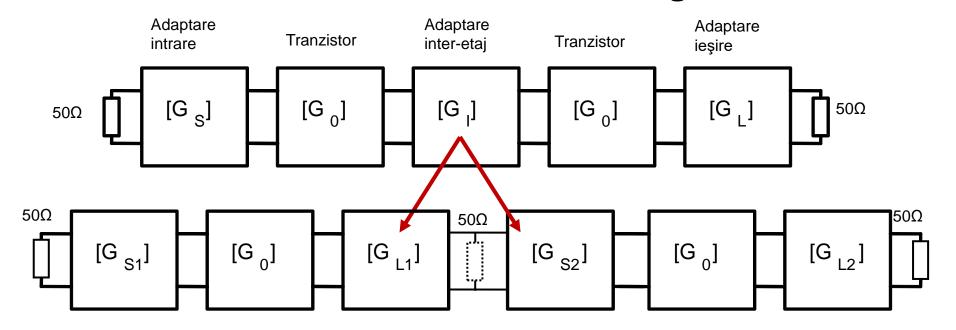
 Using multiple transmission lines for matching each stage to a intermediate Γ=ο (virtual) allows detailed control over reflection coefficient on both stages



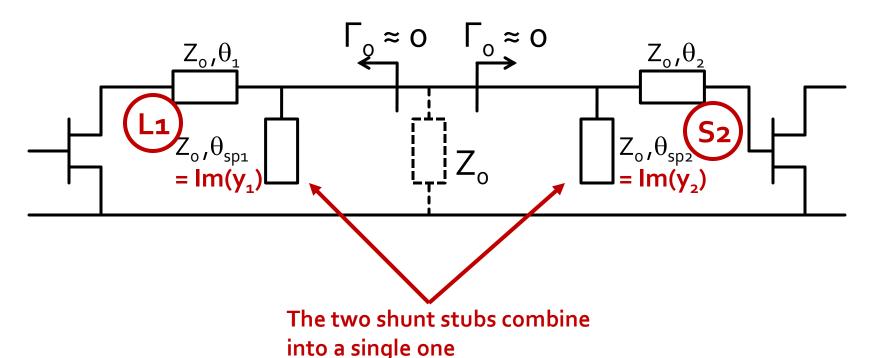 One of the stages creates through its matching network a reflection coefficient Γ=0 towards which the other stage is matched




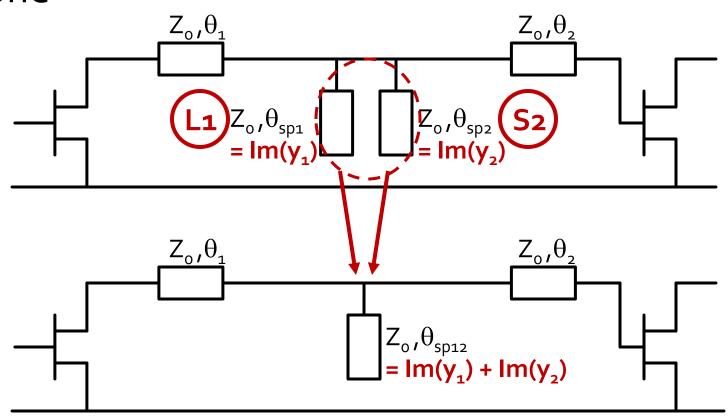The two shunt stubs combine into a single one




stub

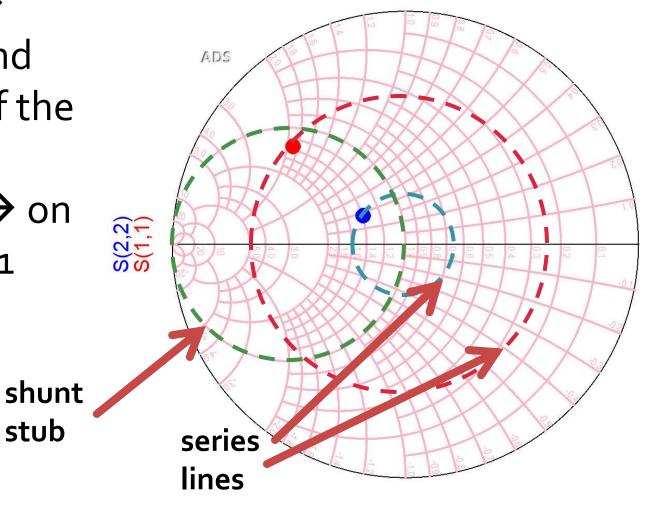- series line → moves around the center of the SC
- shunt stub → on the circle g=1



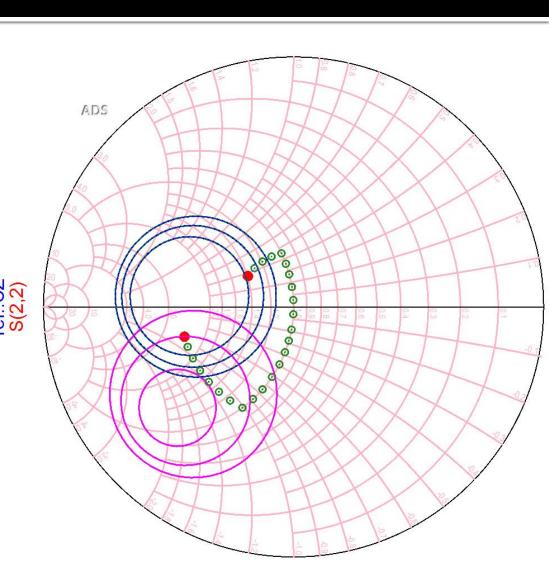- For every stage we use a series line and a shunt stub
  - the series line moves the reflection coefficient from the desired starting point on the unity conductance circle g=1
  - the shunt stub moves the point to the center of the Smith Chart (Zo match)
- The two shunt stubs will then combine into one



## Output matching stage 1 (L1)

G<sub>L1</sub> (we use the same point <- output L2), o.2dB</li>

$$\begin{split} & \Gamma_{L} = 0.186 \angle -132.9^{\circ} & |\Gamma_{L}| = 0.186; \quad \varphi = -132.9^{\circ} \\ & \cos(\varphi + 2\theta) = -|\Gamma_{L}| & \operatorname{Im}[y_{L}(\theta)] = \frac{-2 \cdot |\Gamma_{L}|}{\sqrt{1 - |\Gamma_{L}|^{2}}} = -0.379 \\ & \cos(\varphi + 2\theta) = -0.186 \Rightarrow \quad (\varphi + 2\theta) = \pm 100.72^{\circ} \end{split}$$


- the length of the shunt stub  $\theta_{sp}$  is not calculated because it is **not** needed

$$(\varphi + 2\theta) = \begin{cases} +100.72^{\circ} \\ -100.72^{\circ} \end{cases} \theta = \begin{cases} 116.8^{\circ} \\ 16.1^{\circ} \end{cases} \operatorname{Im}[y_{L}(\theta)] = \begin{cases} -0.379 \\ +0.379 \end{cases}$$

## Output matching stage 1 (L1)


Equation	Solution L1A	Solution L1B
Φ+2θ	+100.72°	-100.72°
θ	116.8°	16.1°
$Im[y(\theta)]$	-0.379	+0.379

## Verify stage 1

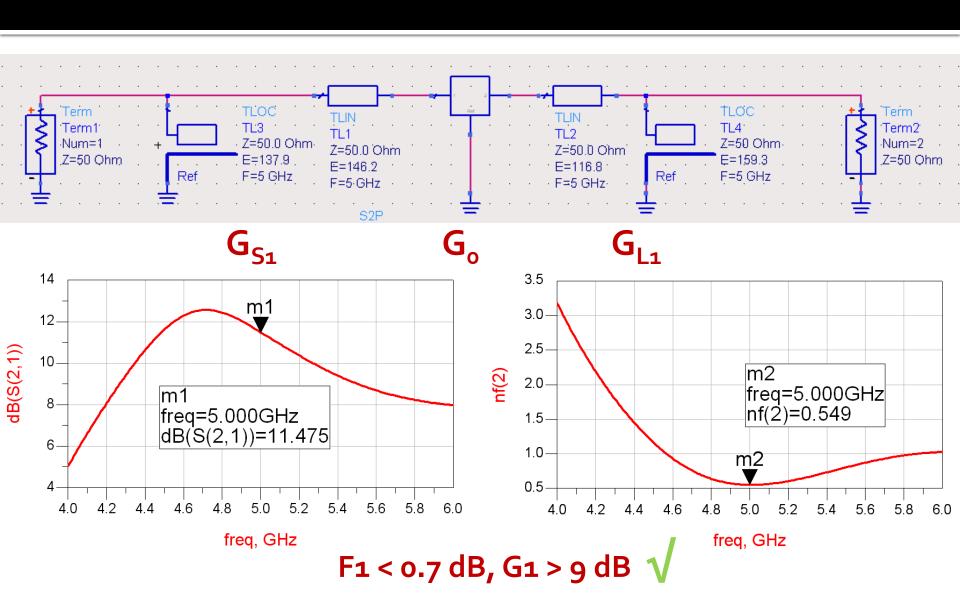
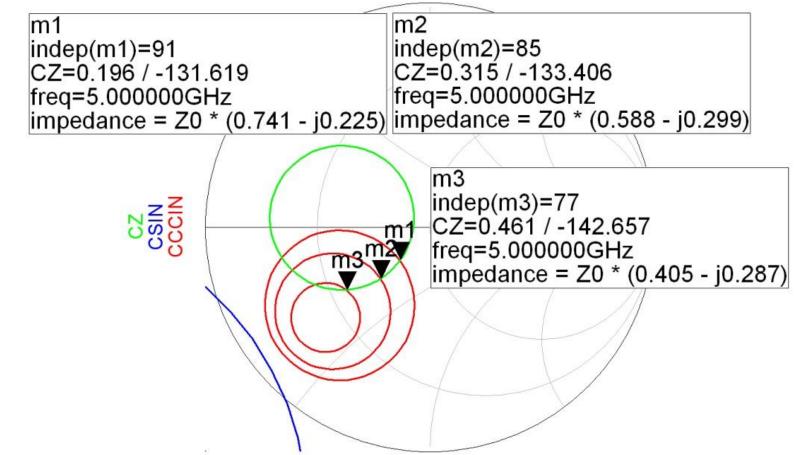
### Input matching stage 2 (S2)

•  $G_{S_2}$  (moving from  $\Gamma_{S_2}$  we choose towards complex plane origin –  $m_3$  – gain 2dB)



## Input matching stage 2 (S2)

G<sub>S2</sub> (going from m<sub>3</sub> towards origin), 2dB

$$\Gamma_{S2} = 0.461 \angle -142.66^{\circ} \qquad |\Gamma_{S2}| = 0.461; \quad \varphi = -142.66^{\circ}$$

$$\cos(\varphi + 2\theta) = -|\Gamma_{S2}| \qquad \operatorname{Im}[y_{S2}(\theta)] = \frac{\mp 2 \cdot |\Gamma_{S2}|}{\sqrt{1 - |\Gamma_{S2}|^2}}$$

$$\cos(\varphi + 2\theta) = -0.461 \Rightarrow \qquad (\varphi + 2\theta) = \pm 117.45^{\circ}$$


- the length of the shunt stub  $\theta_{sp}$  is not calculated because it is **not** needed

$$(\varphi + 2\theta) = \begin{cases} +117.45^{\circ} \\ -117.45^{\circ} \end{cases} \theta = \begin{cases} 130.1^{\circ} \\ 12.6^{\circ} \end{cases} \operatorname{Im}[y_{s2}(\theta)] = \begin{cases} -1.039 \\ +1.039 \end{cases}$$

## Input matching stage 2 (S2)

Equation	Solution S2A	Solution S2B
Φ+2θ	+117.45°	-117.45°
θ	130.1°	12.6°
$Im[y(\theta)]$	-1.039	+1.039


## Verify stage 2

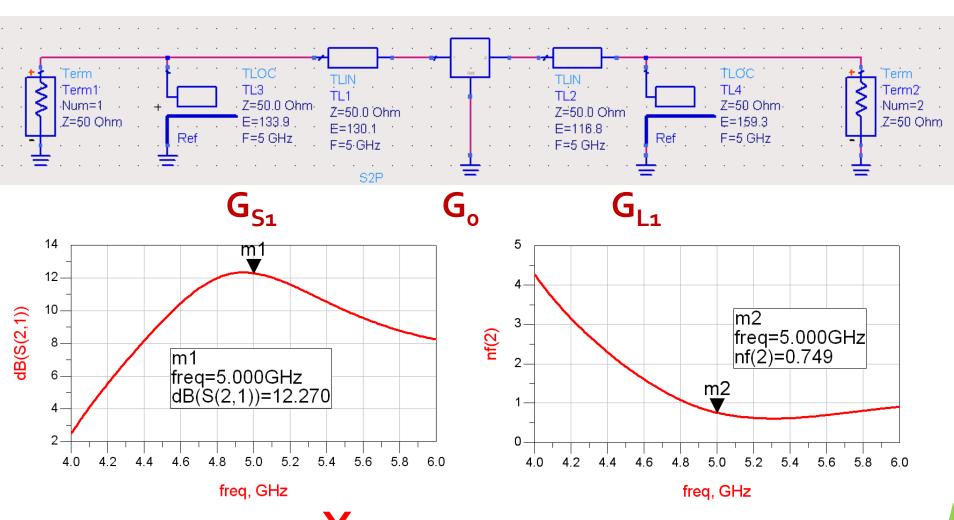

 $F_2 < 1.2 \text{ dB, } G_2 < 13 \text{ dB } X$   $G_1 = 11.5 \text{dB, } G_2 = 12.3 \text{dB, } G_1 + G_2 > 22 \text{dB}$ 
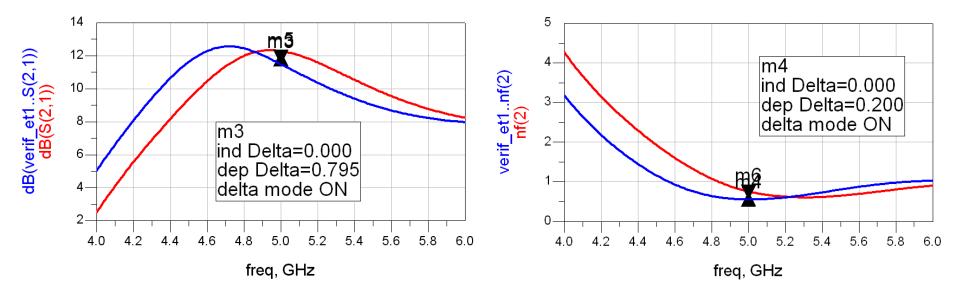
### Stage 1/2

 According to the conclusions of the Friis formula, the second stage obtains a higher gain because a higher noise is acceptable.




### Merging the two shunt stubs

- The two shunt stubs merge into a single one
- There are 4 possible combinations depending on how we chose the electrical length for the two series lines
  - for each chosen electric length (θ) the corresponding Im[y(θ)] must be used
- Ex:


$$\theta_{L1} = 116.8^{\circ}$$
  $\theta_{S2} = 130.1^{\circ}$   $\text{Im}[y_{sp}] = \text{Im}[y_{L1}(\theta)] + \text{Im}[y_{S2}(\theta)] = -1.418$   
 $\theta_{sp} = \tan^{-1}(\text{Im}[y_{sp}])$   $\theta_{sp} = 125.2^{\circ}$ 
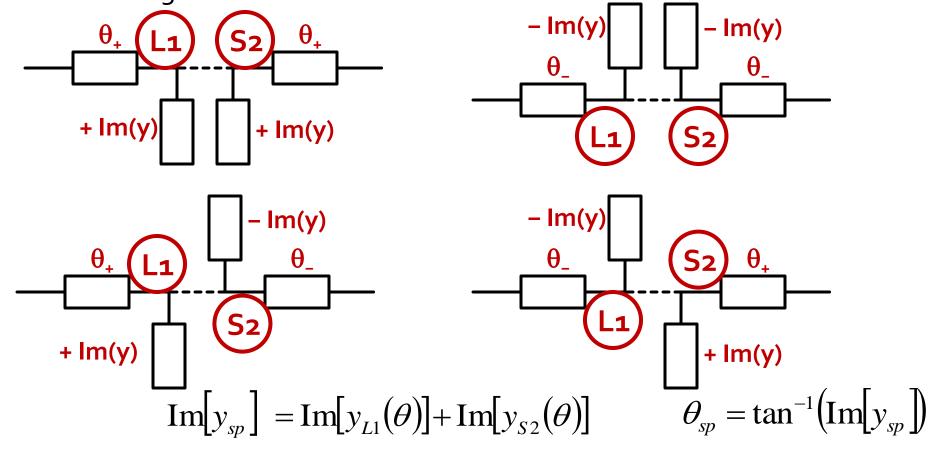
### Merging the two shunt stubs

- 4 possible combinations
  - the admittances are in parallel and add up, not the electrical lengths




#### Merging the two shunt stubs

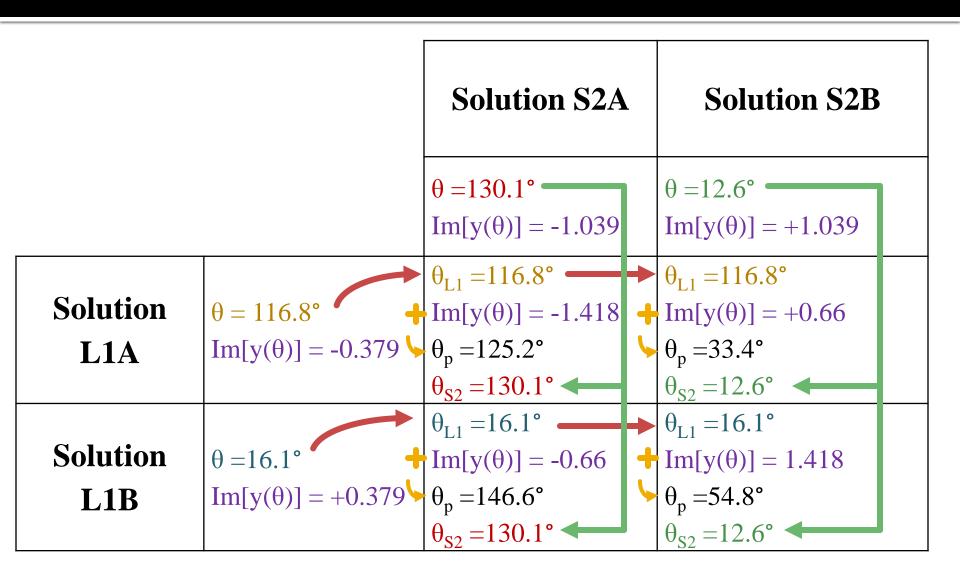


#### **Smith Chart**

- series line → moves around the center of the SC
- shunt stub → on the circle g=1


stub

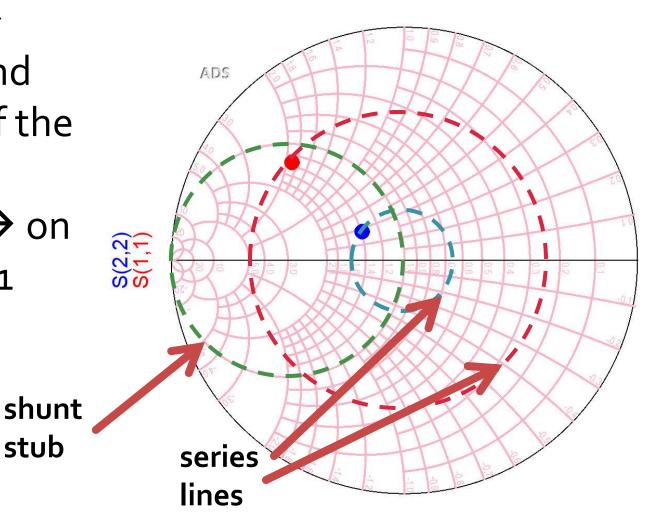


## Merge 1, Smith Chart

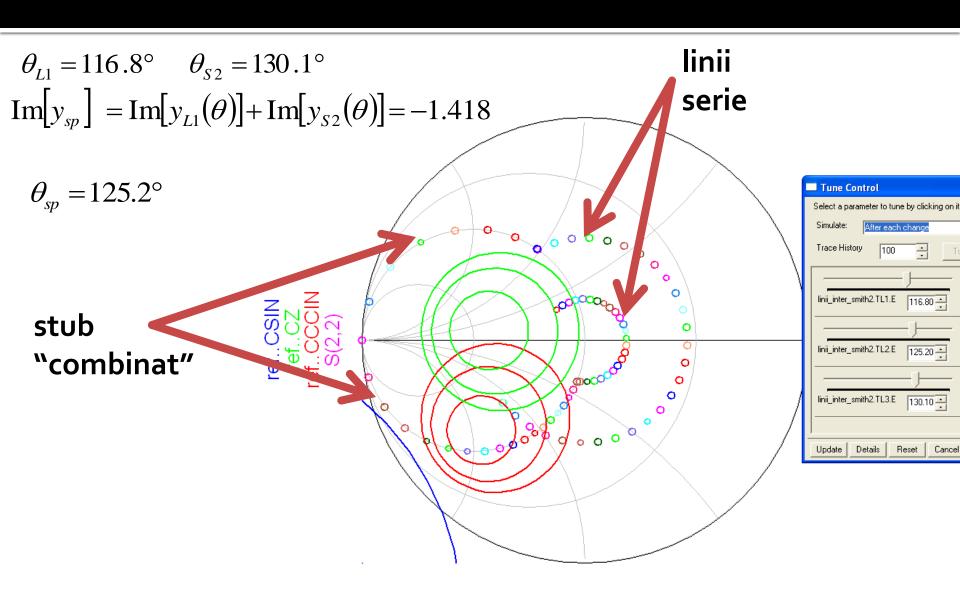


#### Merge 1, ADS

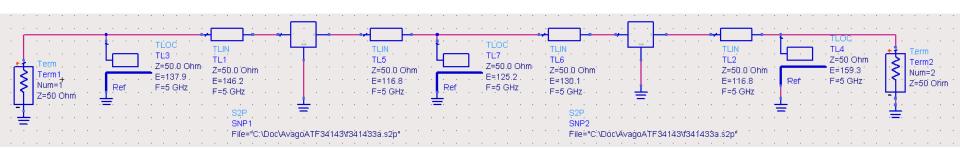


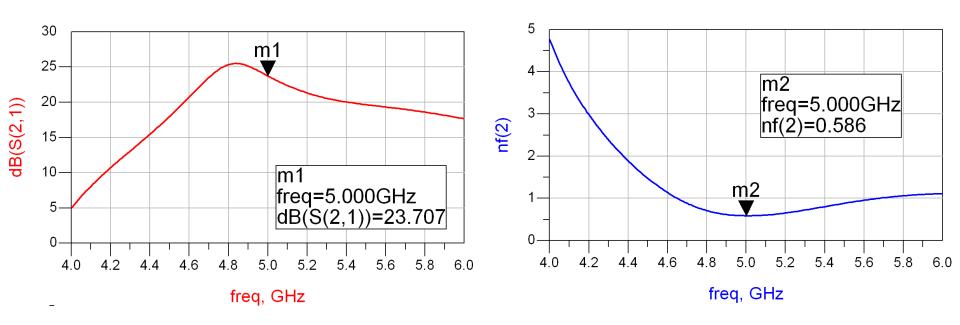


### Merge 2, Smith Chart

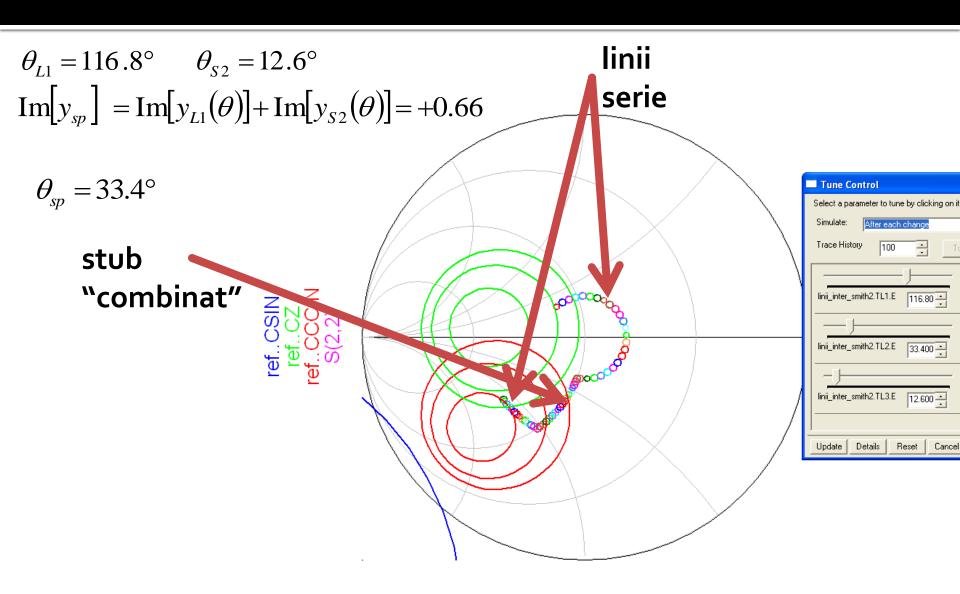


#### Merge 2, ADS

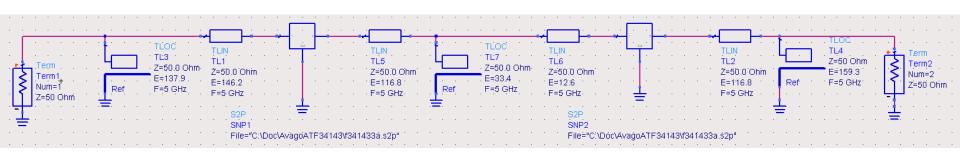


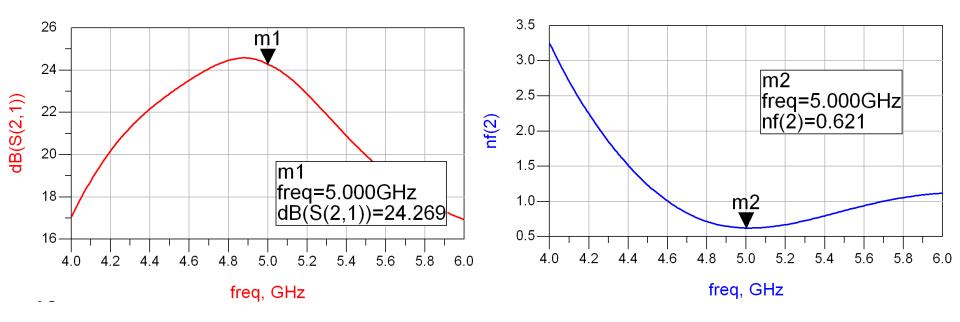


## Merge 3, Smith Chart

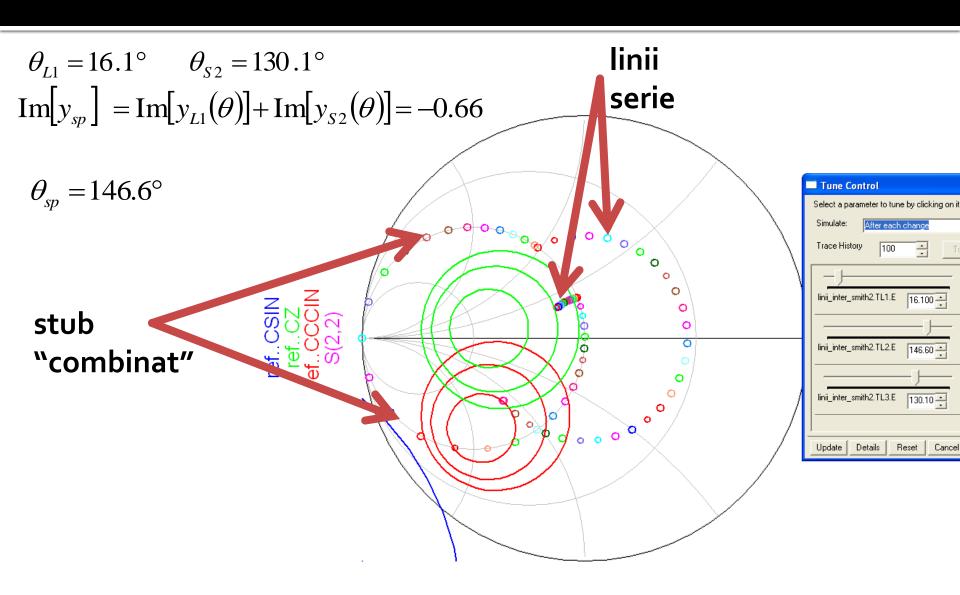


#### Merge 3, ADS

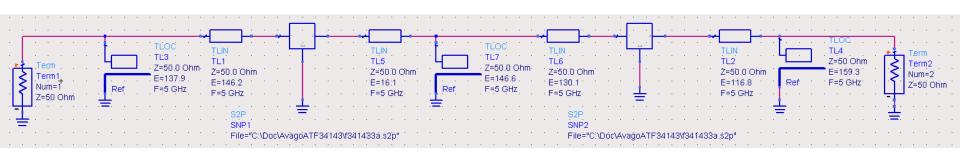


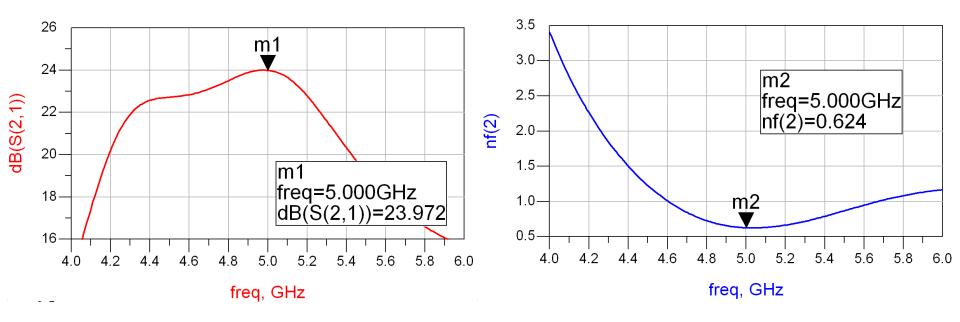


## Merge 4, Smith Chart

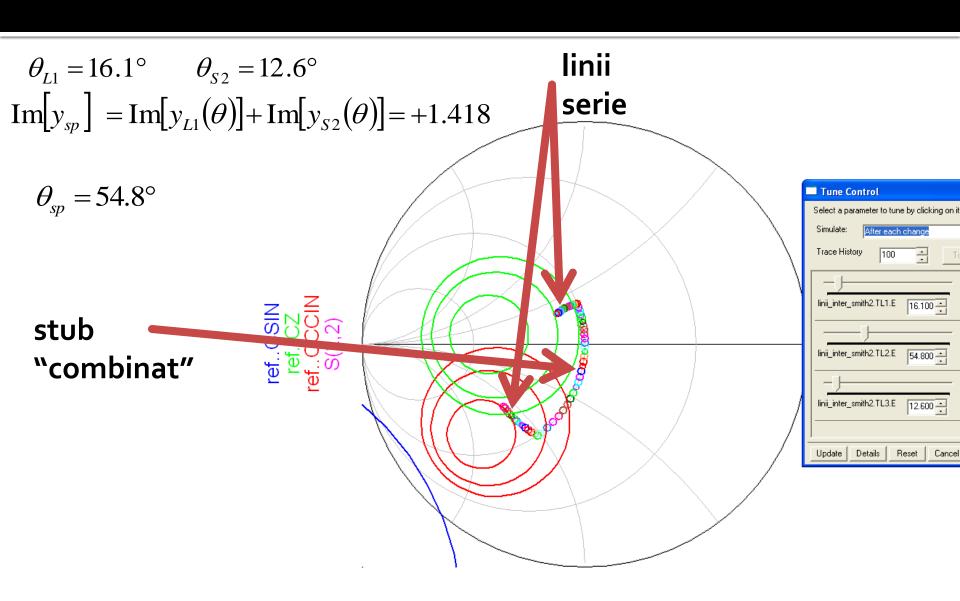

#### Merge 4, ADS

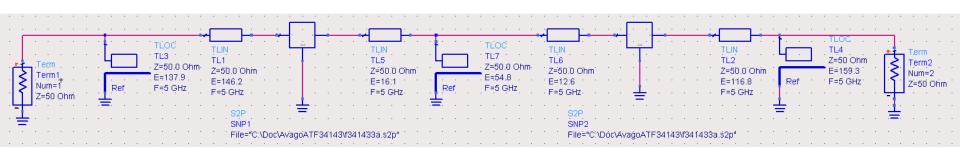


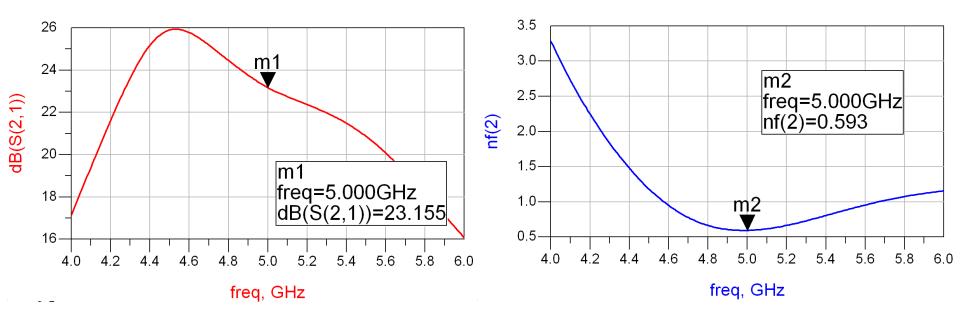

- All the combinations obtained meet the target conditions for gain and noise
- Choose a convenient one depending on:
  - the physical dimensions of the lines  $l = \frac{\theta}{360^{\circ}} \cdot \lambda$
  - frequency bandwidth/flatness
  - stability
  - performance (noise/gain)
  - input and output reflection
  - etc.
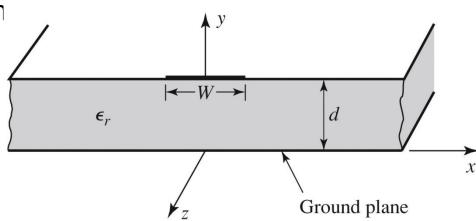
## Supplement Mini Project

- microstrip lines
  - dielectric layer
  - plane metallization (ground plane)
  - traces which will control:
    - characteristic impedance
    - physical/electrical length



quasi TEM line


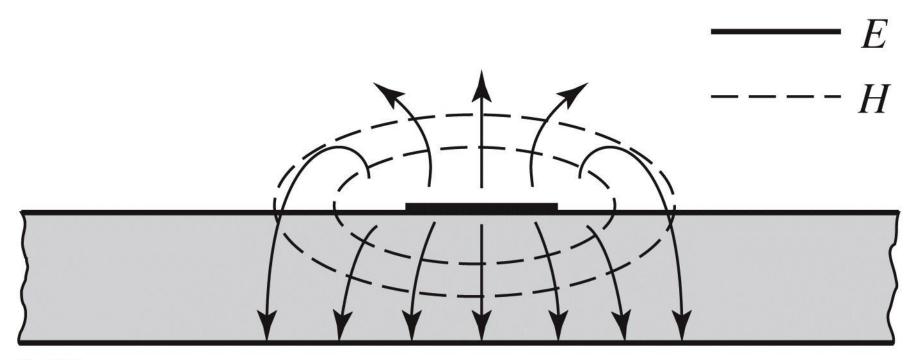



Figure 3.25b

© John Wiley & Sons, Inc. All rights reserved.


quasi TEM line, EmPro

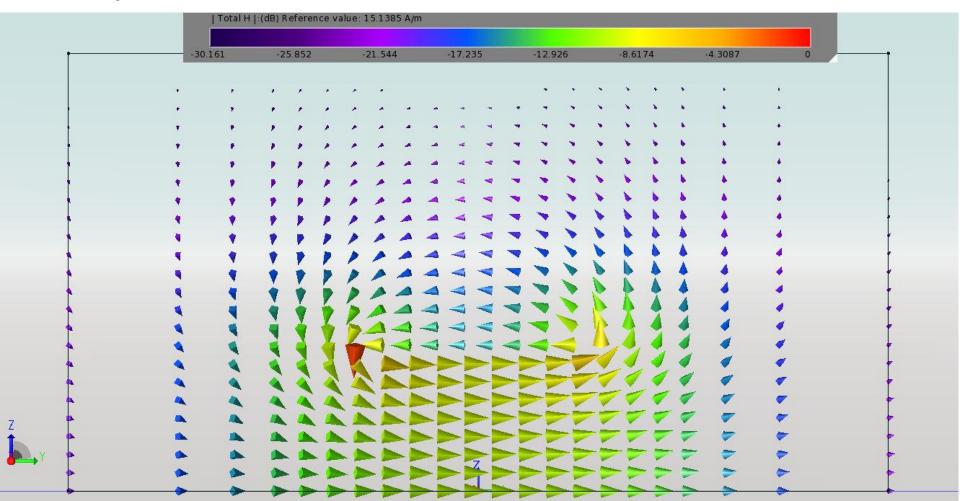


quasi TEM line, EmPro

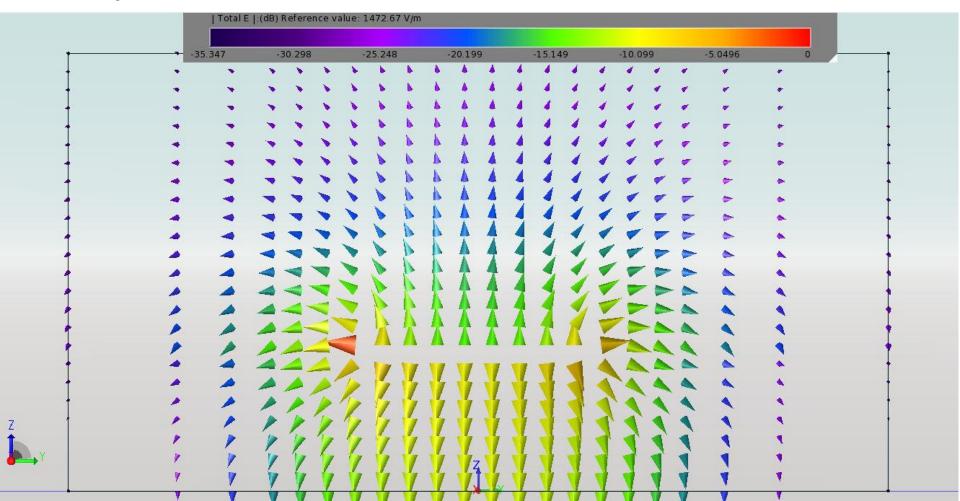


quasi TEM line, EmPro

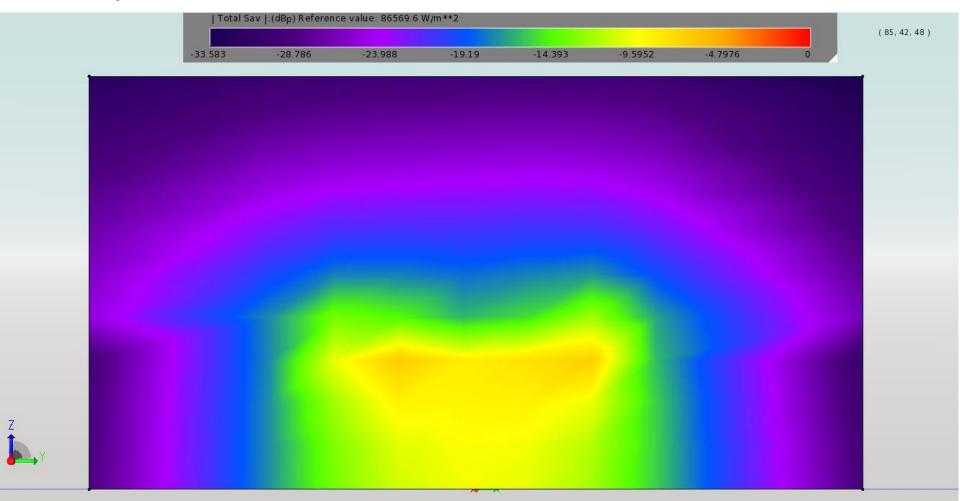


~ Aproximativ TEM

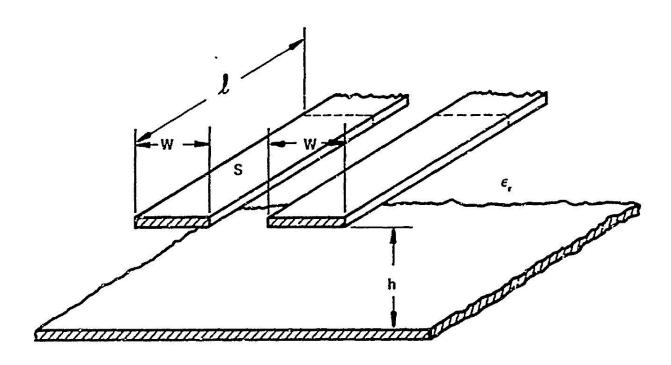

~ AproximativTEM

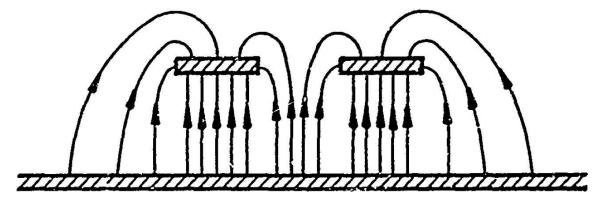

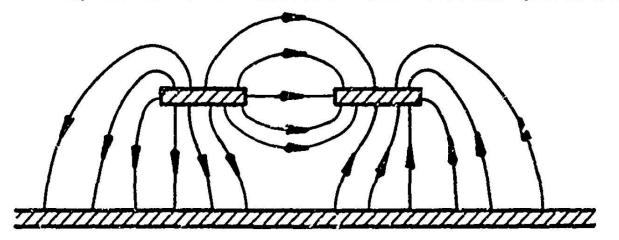b) EVEN MODE ELECTRIC FIELD PATTERN (SCHEMATIC)



c) ODD MODE ELECTRIC FIELD PATTERN (SCHEMATIC)

 Equivalent geometry of a quasi-TEM microstrip line with effective dielectric constant homogeneous medium


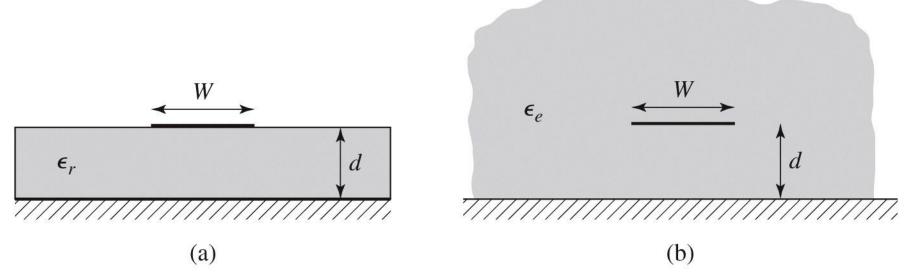


Figure 3.26 © John Wiley & Sons, Inc. All rights reserved.
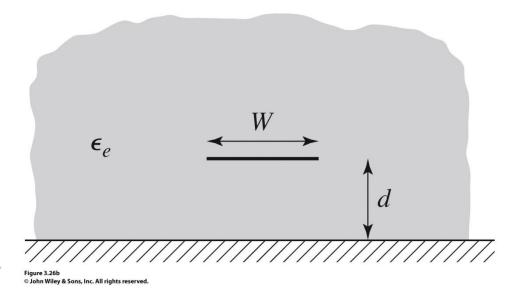
#### Empirical formulas

$$v_p = \frac{c}{\sqrt{\epsilon_e}},$$
$$\beta = k_0 \sqrt{\epsilon_e},$$

$$\epsilon_e = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \frac{1}{\sqrt{1 + 12d/W}}.$$



$$\int \frac{60}{\sqrt{\epsilon_e}} \ln \left( \frac{8d}{W} + \frac{W}{4d} \right)$$

for 
$$W/d \le 1$$


$$Z_{0} = \begin{cases} \frac{60}{\sqrt{\epsilon_{e}}} \ln \left( \frac{8d}{W} + \frac{W}{4d} \right) \\ \frac{120\pi}{\sqrt{\epsilon_{e}} \left[ W/d + 1.393 + 0.667 \ln \left( W/d + 1.444 \right) \right]} \end{cases}$$

for 
$$W/d \ge 1$$
.

### Design
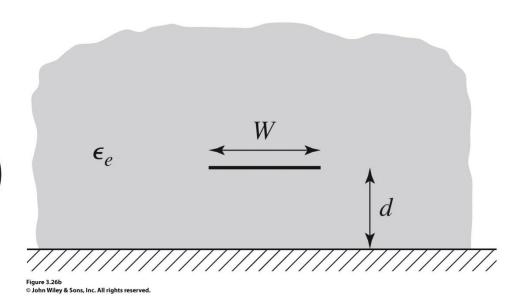
#### Empirical formulas


$$A = \frac{Z_0}{60} \sqrt{\frac{\epsilon_r + 1}{2}} + \frac{\epsilon_r - 1}{\epsilon_r + 1} \left( 0.23 + \frac{0.11}{\epsilon_r} \right)$$
$$B = \frac{377\pi}{2Z_0 \sqrt{\epsilon_r}}.$$



$$\frac{W}{d} = \begin{cases} \frac{8e^A}{e^{2A} - 2} & \text{for } W/d < 2\\ \frac{2}{\pi} \left[ B - 1 - \ln(2B - 1) + \frac{\epsilon_r - 1}{2\epsilon_r} \left\{ \ln(B - 1) + 0.39 - \frac{0.61}{\epsilon_r} \right\} \right] & \text{for } W/d > 2, \end{cases}$$
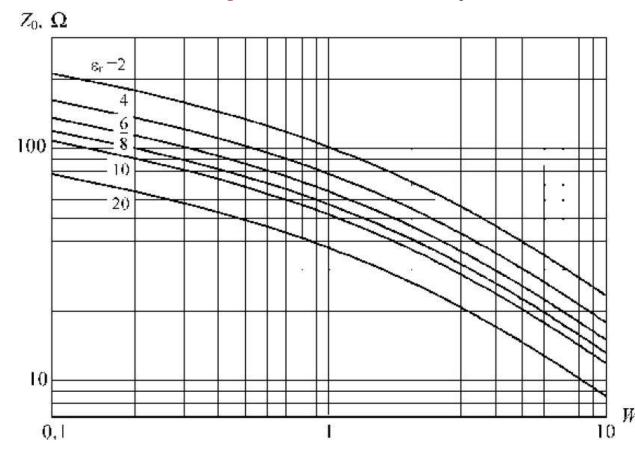
# Characteristic impedance

- Large impedances require narrow traces
- Small impedances require wide traces



$$k_0 = \frac{2\pi f}{c}$$
$$\beta \ell = \sqrt{\epsilon_e k_0} \ell,$$

# Microstrip standardization

- Standardization
  - dimensions in mil
  - 1 mil = 10<sup>-3</sup> inch
  - 1 inch = 2.54 cm
- Trace thickness
  - based on the weight of the deposited copper
  - oz/ft²
  - 10z=28.35g and 1ft=30.48cm

Greutatea cuprului depus		Grosimea stratului	
oz/ft²	g/ft²	inch	mm
0.5	14.175	0.0007	0.0178
1.0	28.35	0.0014	0.0356
2.0	56.7	0.0028	0.0712

## Microstrip standardization

 Typically the height of the dielectric layers is also standardized in mil

```
Standard Thickness
```

#### RO4003C:


```
0.008" (0.203mm), 0.012 (0.305mm), 0.016" (0.406mm), 0.020" (0.508mm)
```

0.032" (0.813mm), 0.060" (1.524mm)
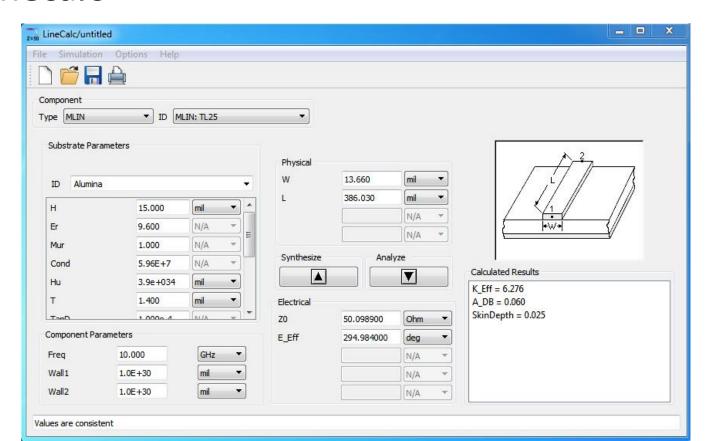
#### RO4350B:


```
*0.004" (0.101mm), 0.0066" (0.168mm) 0.010" (0.254mm), 0.0133 (0.338mm), 0.0166 (0.422mm), 0.020" (0.508mm) 0.030" (0.762mm), 0.060" (1.524mm)
```

- In schematics: >Tools>LineCalc>Start
- for Microstrip lines >Tools>LineCalc>Send to Linecalc





- 1. Define substrate (receive from schematic)
- 2. Insert frequency
- 3. Insert input data
  - Analyze: W,L → Zo,E or Ze,Zo,E / at f [GHz]

Synthesis: Zo,E → W,L / at f [GHz]

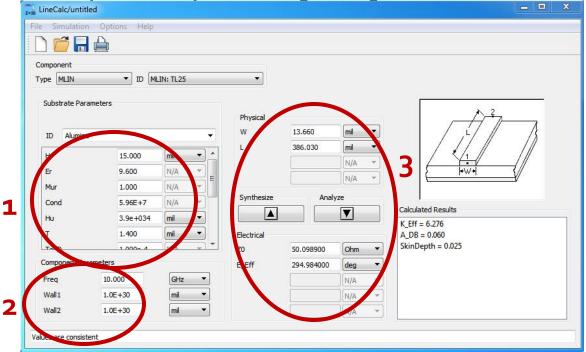

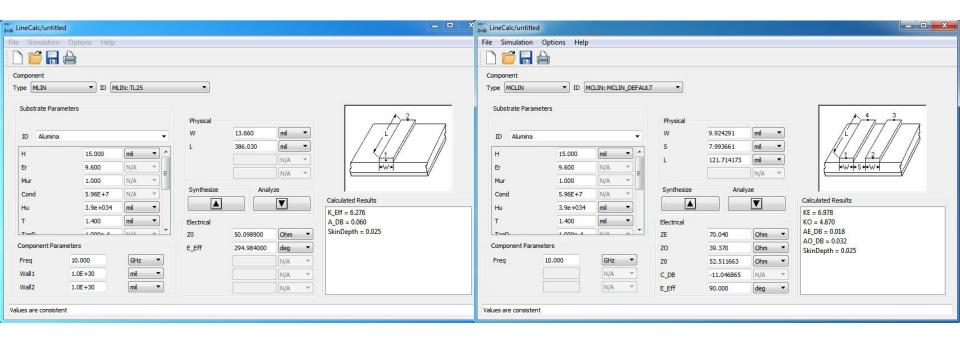
- Can be used for:
  - microstrip lines MLIN: W,L ⇔ Zo,E
  - microstrip coupled lines MCLIN: W,L,S ⇔ Ze,Zo,E



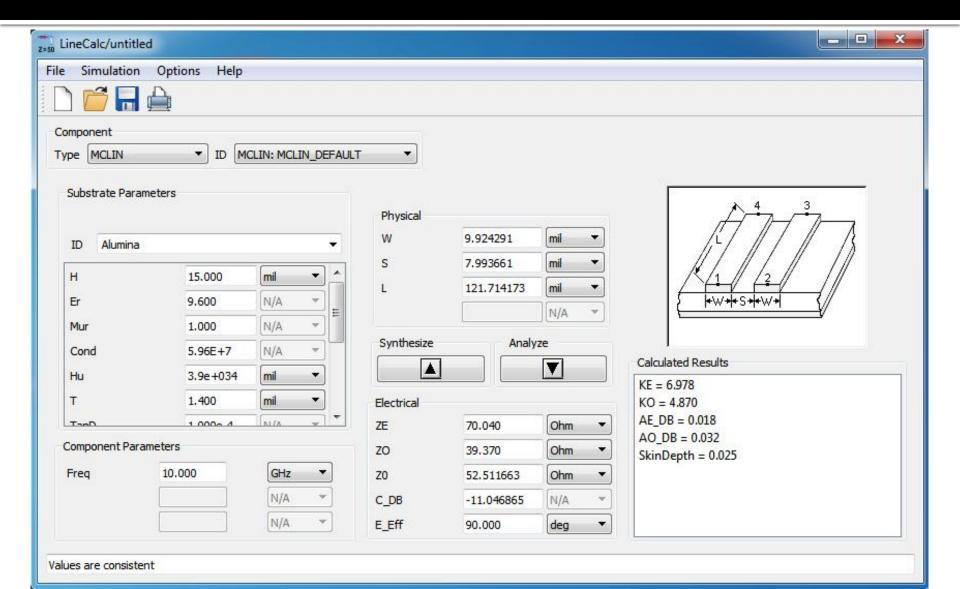

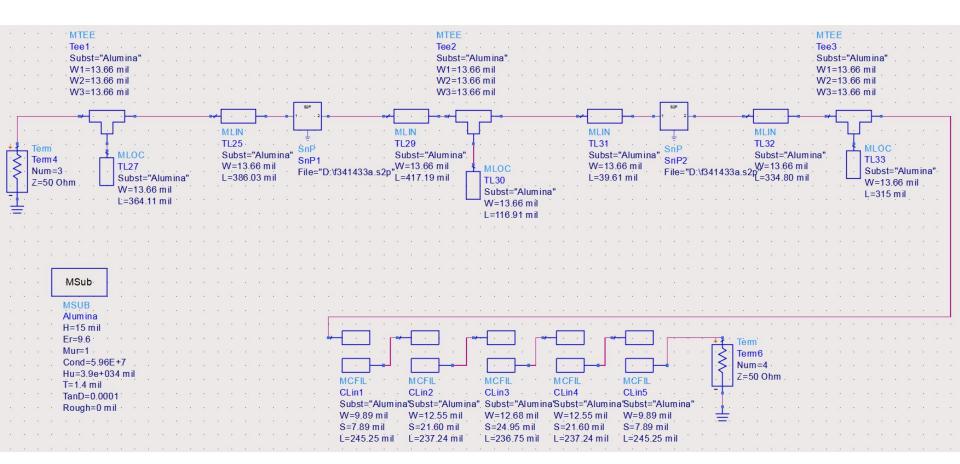
### **Transmission lines**

- http://rf-opto.etti.tuiasi.ro
- Transmission lines / Rogers
  - more precise formulas including
    - t, trace thickness
    - f, frequency
  - formulas for
    - microstrip
    - strip
    - coupled lines




On all schematics you must have an substrate model/component

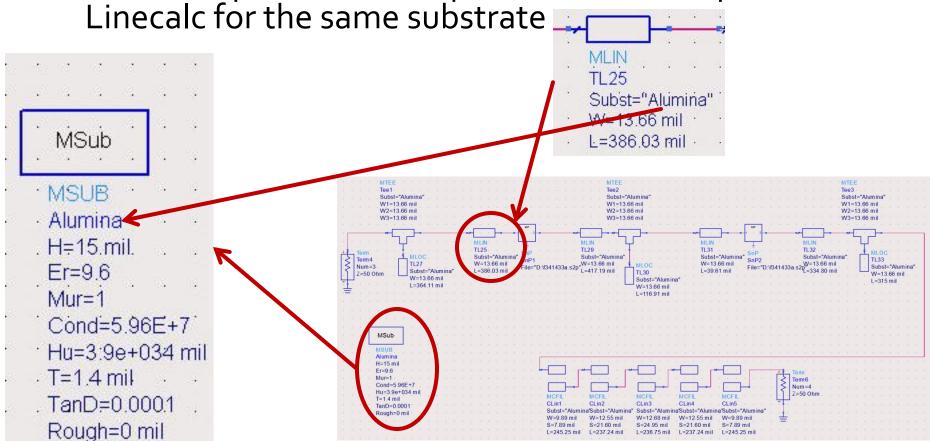
Miscrostrip lines and coupled lines are computed in




- We use components from the "Transmission Lines – Microstrip" pallete
  - MSUB substrate
  - MLIN series line
  - MLOC open-circuit shunt stub
  - MTEE modeling of T junction (shunt stub connection to main line)
  - MCFIL coupled line filter section (more accurate model than MCLIN – takes into account that two adjacent sections are physically close)

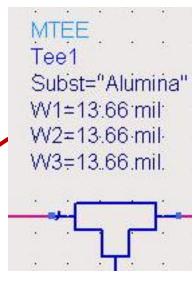 Attention is required when inserting parameters for MTEE and MCFIL by checking in the schematic the width of the lines connected to each port.



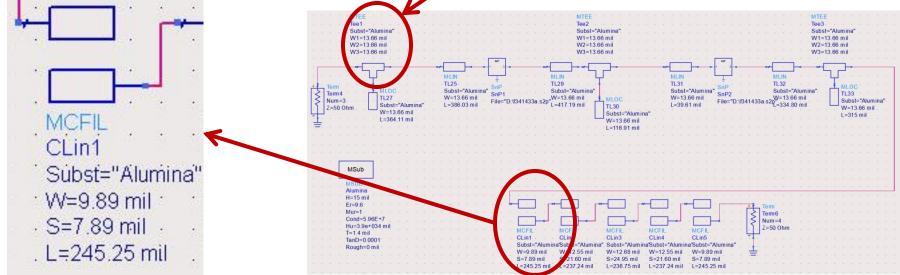

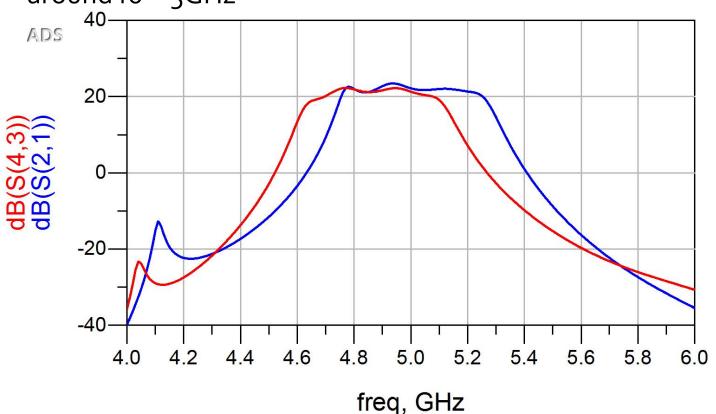
- Usually there is a shift of the transfer function (red) towards lower frequencies compared to the ideal model (blue)
  - due to the MCFIL/MCLIN difference
- Tune the length of filter elements to move the filter bandwidth around fo = 5GHz




#### **DC Bias**


- http://rf-opto.etti.tuiasi.ro
- Agilent Application Notes
  - decoupling signal from DC Bias circuitry
  - DC Bias circuits for microwave transistors
- Appcad has tools for designing DC Bias circuits

### **DC Bias**

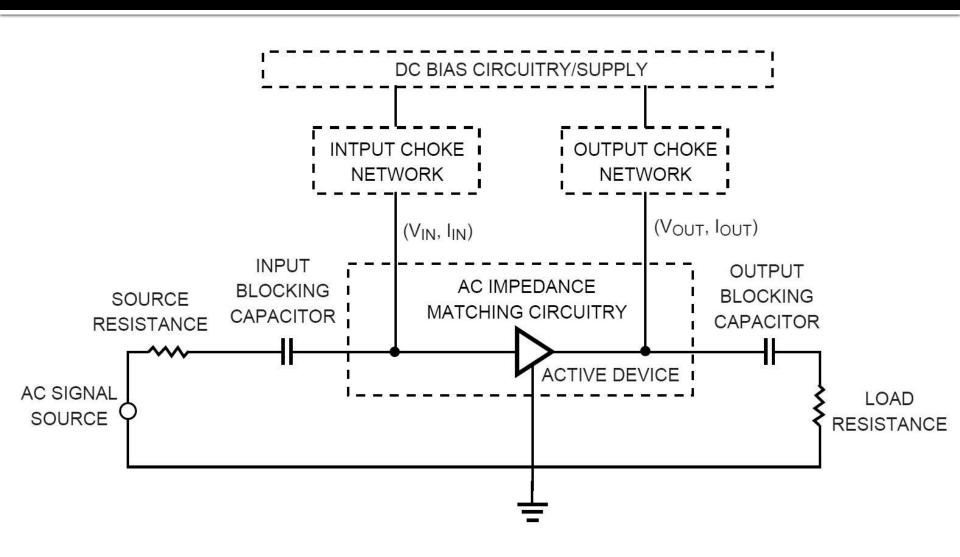



# DC Bias, typical choke

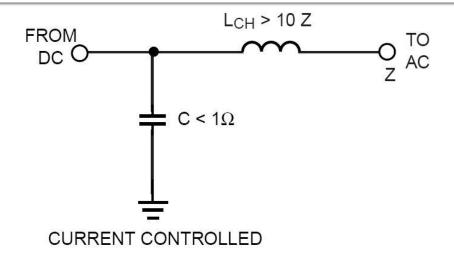

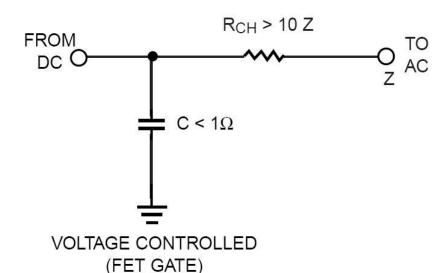


### DC Bias, typical schematics/values

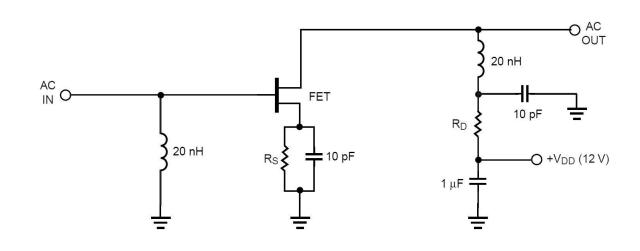

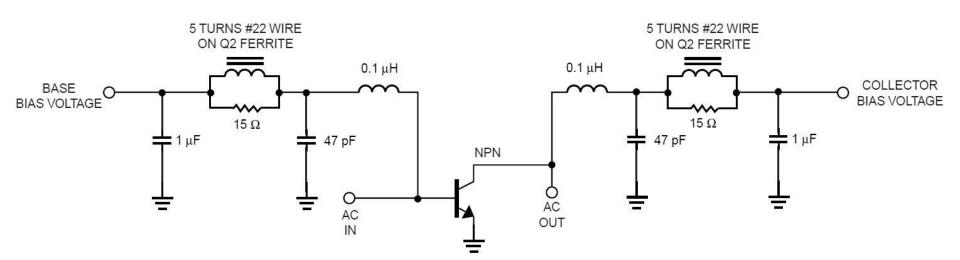


# DC Bias, elements in E/S

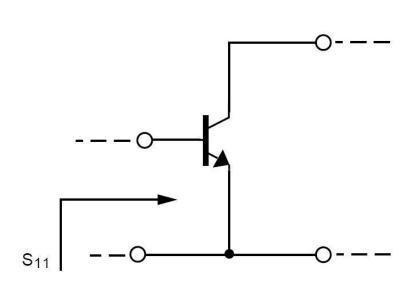

 $S_{11}$  (AT 4 GHz) =  $0.52 \angle 154^{\circ}$ 

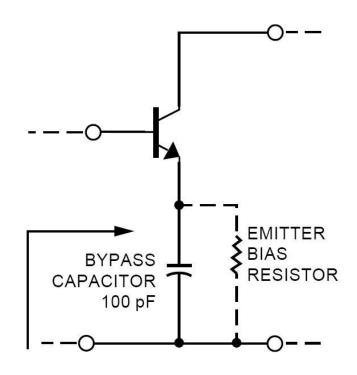
 $S_{11}$  (AT 0.1 GHz) = 0.901  $\angle -14.9^{\circ}$ 



 $S'_{11}$  (AT 4 GHz) =  $0.52 \angle 154^{\circ}$  UNCHANGED AT 4 GHz


 $S'_{11}$  (AT 0.1 GHz) = 1.066  $\angle$  -8.5°  $|S_{11}|$ >1 AT 0.1GHz

# DC Bias, bipolar transistors

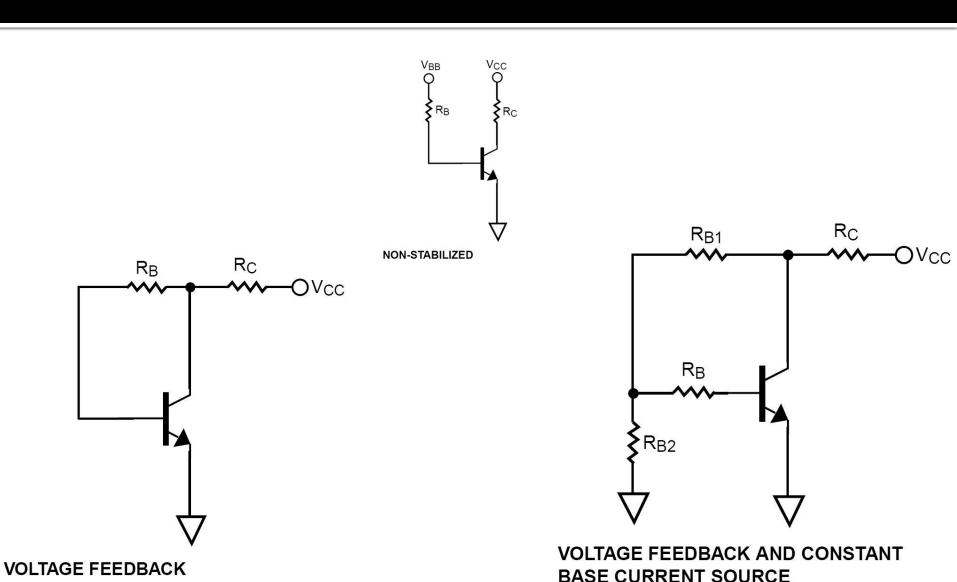

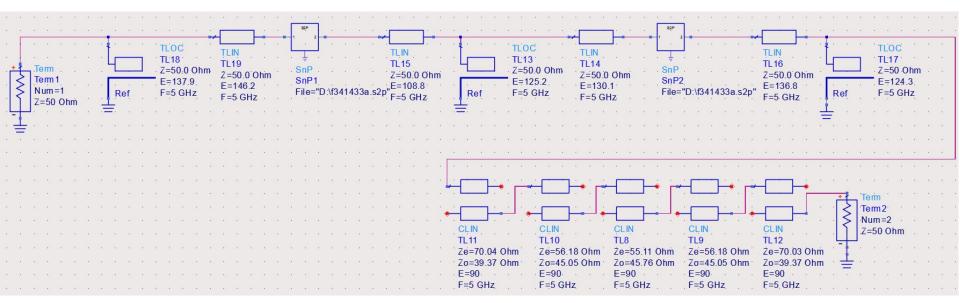
# Example project


- Unify the two schematics
  - L8 amplifier
  - L9 filter




# Result (unbalanced)

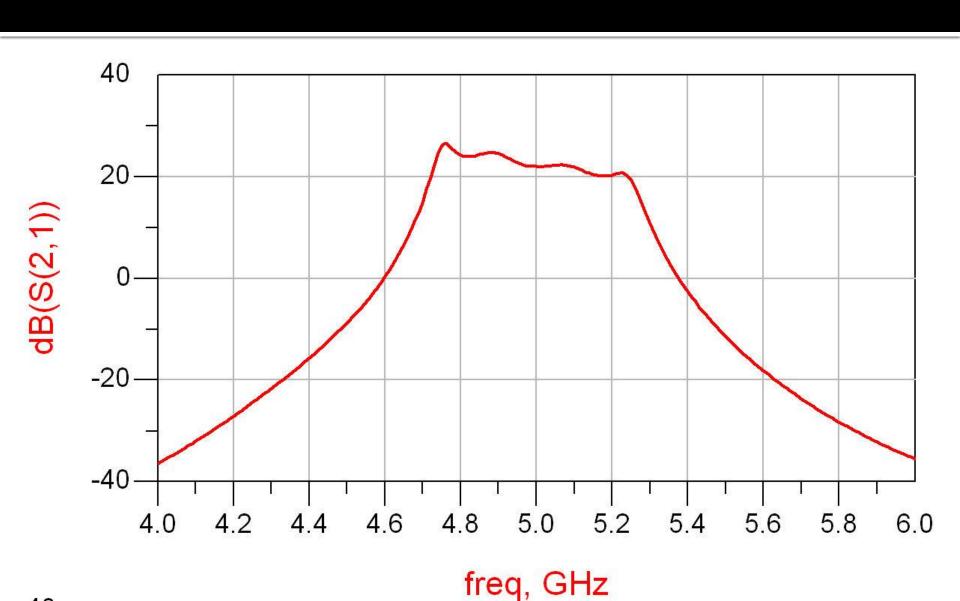

# Result (unbalanced)

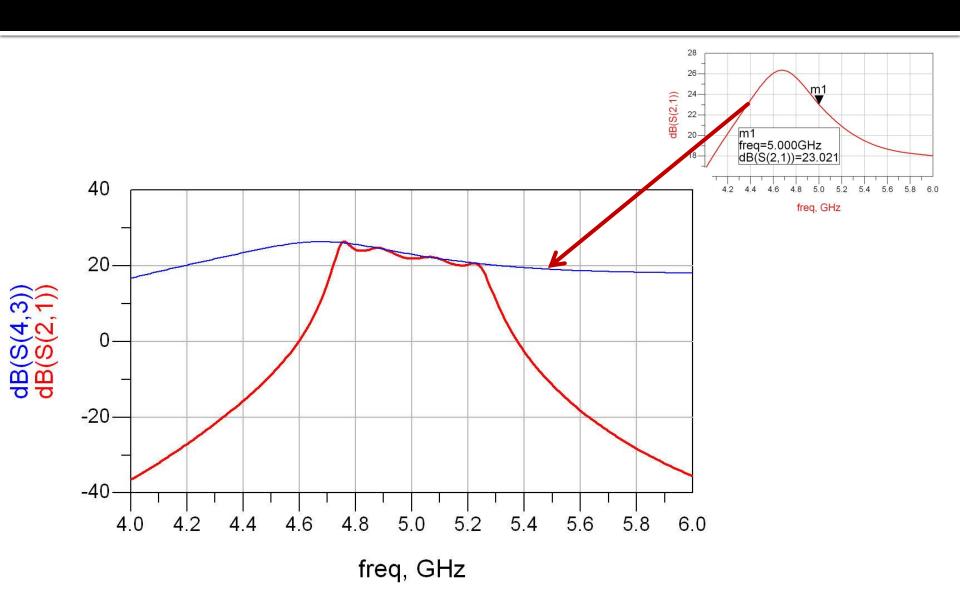


# Result (~periodic in frequency)

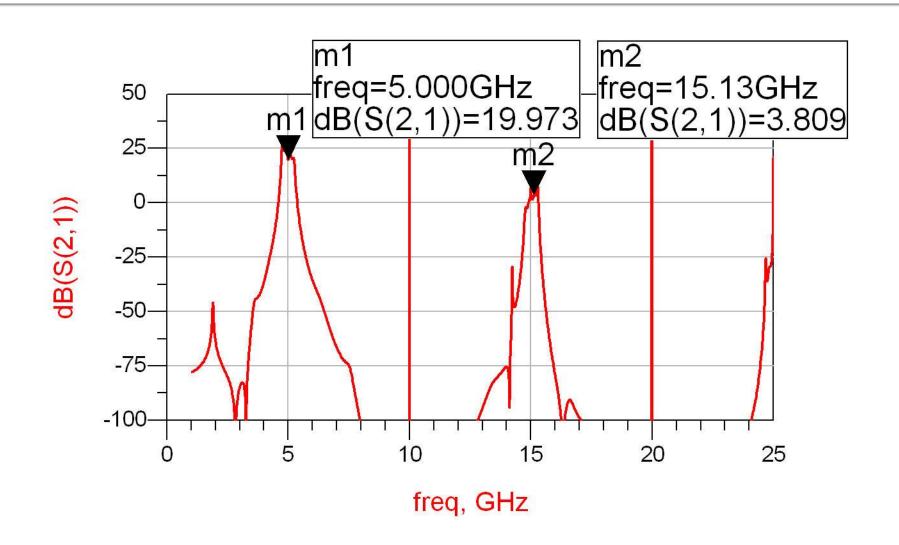
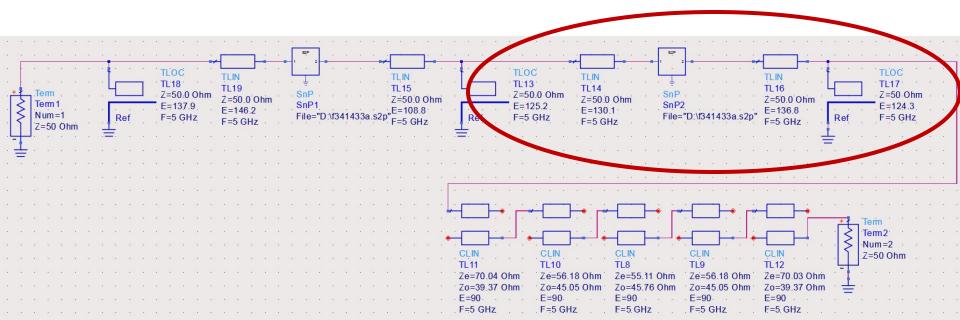
#### Tune -> balance

- purpose: balance the gain characteristic of the amplifier (maximum at design frequency)
  - favor tuning lines at the end of the amplifier
    - eliminate/minimize effect of the tune on noise



### Tune -> balance, result




# Amplifier, Filter, Total



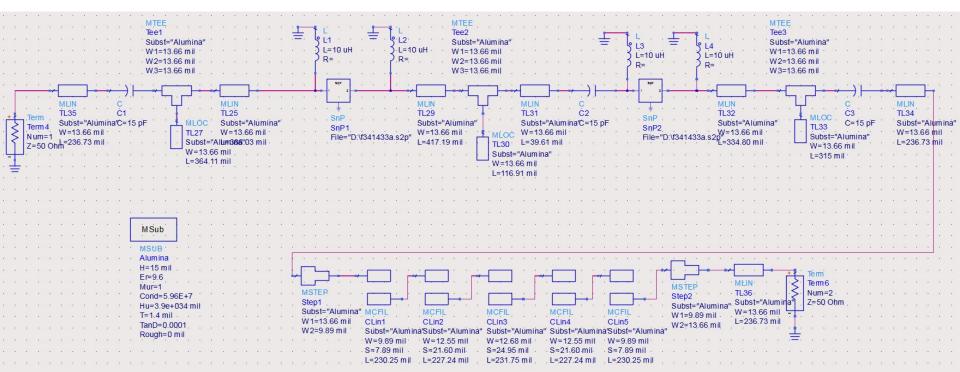
#### DC Bias elements in ADS schematic


- Insert L (RF chokes) and C (decoupling)
- additional  $50\Omega$  connection lines
  - source
  - load
  - between blocks




# Gain -> Tune/Optimization

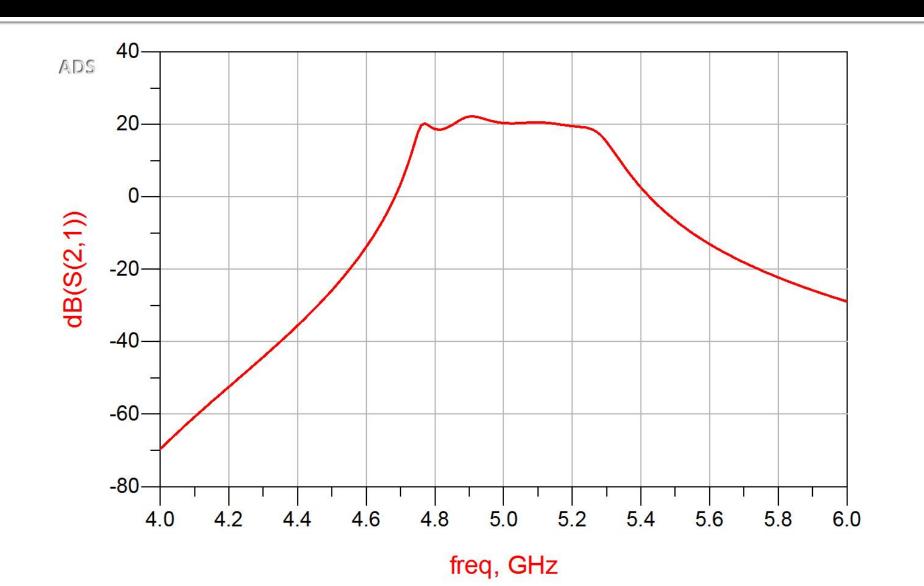

# Final result (Gain)

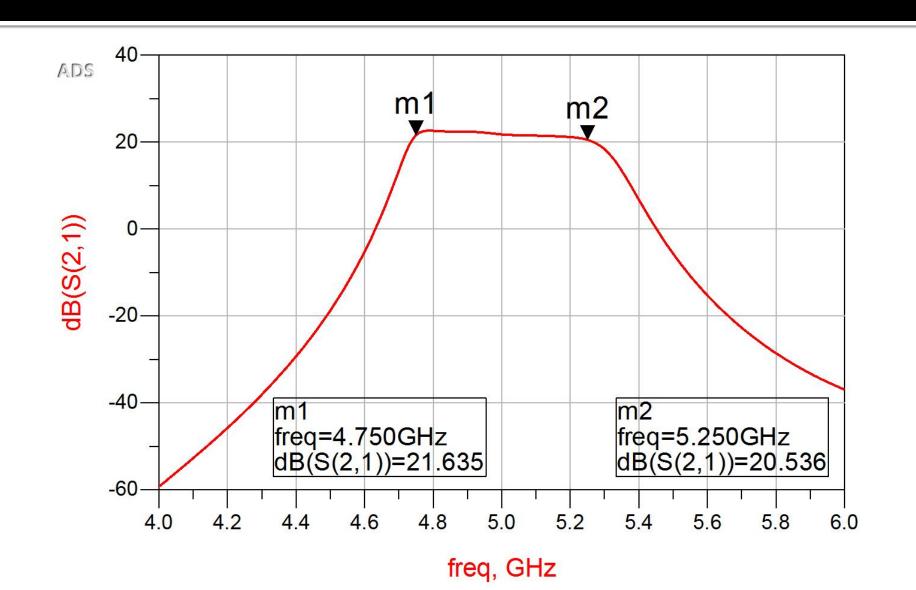


# Final result (Noise)

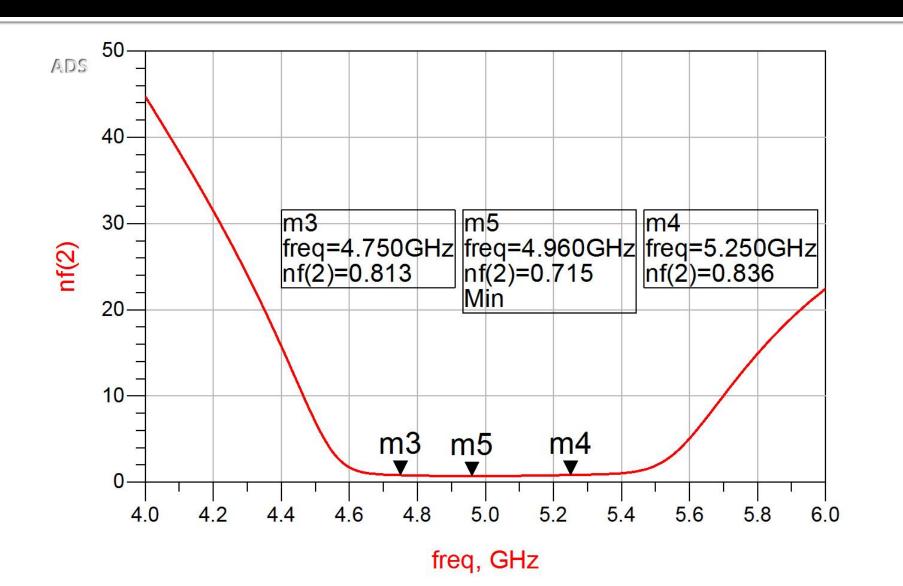

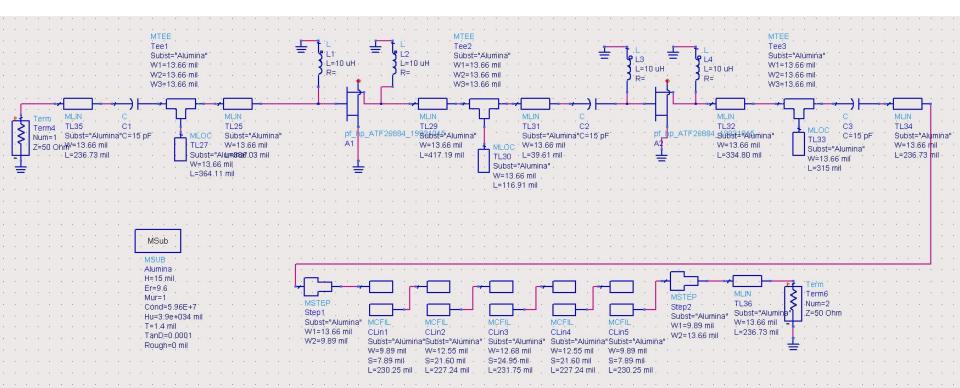
### Layout (Example)

 Temporary replacement of the transistors and lumped elements (LC) with elements for which ADS has case information



# Layout (Example)

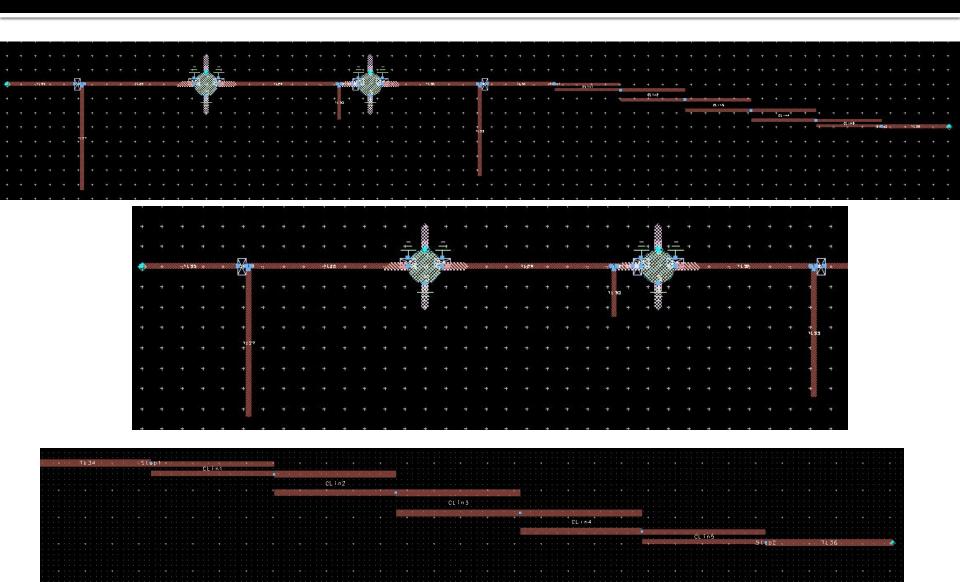

#### Contact

- Microwave and Optoelectronics Laboratory
- http://rf-opto.etti.tuiasi.ro
- rdamian@etti.tuiasi.ro