

Lecture 10

2023/2024

Microwave Devices and Circuits for Radiocommunications

2023/2024

- 2C/1L, **MDCR**
- **Attendance at minimum 7 sessions (course or laboratory)**
- Lectures- **associate professor Radu Damian**
 - Tuesday 16-18, ~~Online~~, P8
 - E – 50% final grade
 - **problems** + (2p atten. lect.) + (3 tests) + (bonus activity)
 - first test L1: 20-27.02.2024 (t2 and t3 not announced, lecture)
 - 3att.=+0.5p
 - **all materials/equipments authorized**

2023/2024

- Laboratory – **associate professor Radu Damian**
 - Tuesday 08-12, 11.13 / (08:10)
 - L – 25% final grade
 - ADS, 4 sessions
 - Attendance + **personal results**
 - P – 25% final grade
 - ADS, 3 sessions (-1? 20.02.2024)
 - personal homework

Materials

■ <http://rf-opto.etti.tuiasi.ro>

The screenshot shows a web browser window with the URL http://rf-opto.etti.tuiasi.ro/microwave_cd.php?chg_lang=0. The page features a dark blue navigation bar with links for Main, Courses, Master, Staff, Research, Students, and Admin. Below this is a secondary navigation bar with links for Microwave CD, Optical Communications, Optoelectronics, Internet, Antennas, Practica, Networks, and Educational software. The main content area is titled "Microwave Devices and Circuits for Radiocommunications (English)" and includes the following information:

- Course: MDCR (2017-2018)**
- Course Coordinator:** Assoc.P. Dr. Radu-Florin Damian
- Code:** EDOS412T
- Discipline Type:** DOS; Alternative, Specialty
- Credits:** 4
- Enrollment Year:** 4, Sem. 7

Activities

Course: Instructor: Assoc.P. Dr. Radu-Florin Damian, 2 Hours/Week, Specialization Section, Timetable:
Laboratory: Instructor: Assoc.P. Dr. Radu-Florin Damian, 1 Hours/Week, Group, Timetable:

Evaluation

Type: Examen

A: 50%, (Test/Colloquium)
B: 25%, (Seminary/Laboratory/Project Activity)
D: 25%, (Homework/Specialty papers)

Grades

[Aggregate Results](#)

Attendance

[Course](#)
[Laboratory](#)

Lists

[Bonus-uri acumulate \(final\)](#)
[Studenti care nu pot intra in examen](#)

Materials

Course Slides

[MDCR Lecture 1](#) (pdf, 5.43 MB, en, [↗](#))
[MDCR Lecture 2](#) (pdf, 3.67 MB, en, [↗](#))
[MDCR Lecture 3](#) (pdf, 4.76 MB, en, [↗](#))
[MDCR Lecture 4](#) (pdf, 5.58 MB, en, [↗](#))

On the right side of the screenshot, there is a banner for "RF-OPTO" with the ETTI logo and the University of Technical Sciences (UTS) logo. The banner includes language selection options: "English" (highlighted with a red circle) and "Romana". Below the banner is another navigation bar with links for Main, Courses, Master, Staff, Research, Grades, Student List, Exams, and Photos. The page also features a section for "Online Exams" with the text: "In order to participate at online exams you must get ready following..."

Site



Microwave and Optoelectronics Laboratory



We are enlisted in the Telecommunications Department of the Electronics, Telecommunication and Information Technology Faculty (ETTI) from the "Gh. Asachi" Technical University (TUIASI) in Iasi, Romania

We currently cover inside ETTI the fields related to:

- Microwave Circuits and Devices
- Optoelectronics
- Information Technology

Courses

Nr.	Course	Shortcut	Code	Type	Semester	Credits	Weekly	Examination	Link
1	Microwave Devices and Circuits for Radiocommunications	DCMR	DOS412T	DOS	7	4	0P,1L,0S,2C	Exam	details
2	Monolithic Microwave Integrated Circuits	CIMM	RD.IA.207	DOMS	11	6	1.5L,0S,2C,0P	Exam	details
3	Advanced Techniques in the Design of the Radio-communications Systems	TAPSR	RD.IA.103	DIMS	9	6	1.5P,0L,0S,2C	Exam	details
4	Optical Communications	CO	DOS409T	DOS	7	5	0P,1L,0S,3C	Colloquium	details
5	Optical Communications	OC	EDOS409T	DOS	7	5	0P,1L,0S,3C	Exam	details
6	Satellite Communications	CS	RC.IA.104	DIMS	9	6	0L,0S,2C,1.5P	Exam	details
7	Applied Informatics 1	IA1	DOF135	DOF	1	4	0P,1L,0S,2C	Verification	details
8	Applied Informatics 1	AI1	EDOF135	DOF	1	4	0P,1L,0S,2C	Verification	details
9	Databases, Web Programming and Interfacing	DWPI	ITT.IA.601	DIS	11	5	1P,1L,0.25S,1C	Verification	details
10	Web Applications Design	PAW	RC.IA.108	DIMS	10	5	1L,0S,1.5C,1P	Exam	details
11	Optoelectronics	OPTO	DID405M	DID	8	4	0P,1L,0S,2C	Colloquium	details
12	Microwave Devices and Circuits for Radiocommunications (English)	MDCR	EDOS412T	DOS	8	4	0P,1L,0S,2C	Exam	details



Materials

- RF-OPTO
 - <http://rf-opto.etti.tuiasi.ro>
- **David Pozar, “Microwave Engineering”,**
Wiley; 4th edition , 2011
 - 1 exam problem ← Pozar
- Photos
 - sent by email/**online exam > Week4-Week6**
 - used at lectures/laboratory

Online – Registration no.

- access to **online exams** requires the **password** received by email

The password is communicated during the lectures. It is necessary to

Password

Registration no.

Name of the student

Proposed email 1

Proposed email 2

Write the code below

 **RF-OPTO** 

English | Romana |

[Main](#) [Courses](#) [Master](#) [Staff](#) [Research](#) [Students](#)

[Login](#) [Tutoring](#)

Login

Use the Registration no. and your email or the password received by email

Registration no.

Email/Password

Write the code below

Password

■ received by email

Important message from RF-OPTO Inbox x

 **Radu-Florin Damian**
to me, POPESCU ▾

🗣 Romanian ▾ > English ▾ [Translate message](#)



Laboratorul de Microunde si Optoelectronica
Facultatea de Electronica, Telecomunicatii si Tehnologia Informatiei
Universitatea Tehnica "Gh. Asachi" Iasi

In atentie: POPESCU GOPO ION

Parola pentru a accesa examenele pe server-ul **rf-opto** este
Parola: [REDACTED]

Identificati-va pe [server](#), cu parola, cat mai rapid, pentru confirmare.

Memorati acest mesaj intr-un loc sigur, pentru utilizare ulterioara

Attention: POPESCU GOPO ION

The password to access the exams on the **rf-opto** server is
Password: [REDACTED]

Login to the [server](#), with this password, as soon as possible, for confirmation.

Save this message in a safe place for later use

[Reply](#) [Reply all](#) [Forward](#)

Subject	Correspondents
Important message from RF-OPTO	POPESCU GOPO ION
Validation of MD/CR exam from 02/05/2020	[REDACTED]
[REDACTED]	[REDACTED]

From: Me <rdamian@etti.tuiasi.ro> ★
Subject: Important message from RF-OPTO
To: [REDACTED]
Cc: Me <rdamian@etti.tuiasi.ro> ★



Laboratorul de Microunde si Optoelectronica
Facultatea de Electronica, Telecomunicatii si Tehnologia Informatiei
Universitatea Tehnica "Gh. Asachi" Iasi

In atentie: POPESCU GOPO ION

Parola pentru a accesa examenele pe server-ul **rf-opto** este
Parola: [REDACTED]

Identificati-va pe [server](#), cu parola, cat mai rapid, pentru confirmare.

Memorati acest mesaj intr-un loc sigur, pentru utilizare ulterioara

Attention: POPESCU GOPO ION

The password to access the exams on the **rf-opto** server is
Password: [REDACTED]

Login to the [server](#), with this password, as soon as possible, for confirmation.

Save this message in a safe place for later use

Online exam manual

- The online exam app used for:
 - ~~lectures (attendance)~~
 - laboratory
 - project
 - ~~examinations~~

Materials

Other data

[Manual examen on-line](#) (pdf, 2.65 MB, ro, 🇷🇴)

[Simulare Examen](#) (video) (mp4, 65.12 MB, ro, 🇷🇴)

Microwave Devices and Circuits (Englis

Examen online

- always against a **timetable**
 - long period (lecture attendance/laboratory results)
 - ~~short period (tests: 15min, exam: 2h)~~

Announcement 23:59 (10/05/2020)	Support material 00:05 (11/05/2020)	Exam Topics 00:07 (11/05/2020)	Results 00:10 (11/05/2020)	End 00:20 (15/05/2020)	Confirmation 00:20 (16/05/2020)	Next timeframe in: 05 m 43 s Refresh now
---	---	--	--------------------------------------	----------------------------------	---	--

Announcement

This is a "fake" exam, introduced to familiarize you with the server interface and to perform the necessary actions during an exam: thesis scan, selfie, use email for co

Server Time

All exams are based on the server's time zone (it may be different from local time). For reference time on the server is now:

10/05/2020 23:59:16

Online results submission

- many numerical values/files

Schema finala	Rezultate - castig	Rezultate - zgomot	Fisier justificare calcul (factor andrei)	Fisier zap (optional)	T1, fisier parametri S	T2, fisier parametri S	Z1	Z2	Z3	Z4	Z5	Z6	Z7	Ze1	Zo1	Ze2	Zo2	Ze3	Zo3	Ze4	Zo4	Ze5	Zo5	Ze6
86 - 5428 - 259 ...	86 - 5428 - 260 ...	86 - 5428 - 261 ...	86 - 5428 - 316 ...	-	86 - 5428 - 314 ...	86 - 5428 - 315 ...	148.33	155.88	202.12	164.35	180.91	30.29	185.19	79.9	37	68.89	45.14	61.83	45.05	57.97	46.02	61.85	45.05	68.8
86 - 5622 - 259 ...	86 - 5622 - 260 ...	86 - 5622 - 261 ...	86 - 5622 - 316 ...	86 - 5622 - 262 ...	86 - 5622 - 314 ...	86 - 5622 - 315 ...	26.97	153.5	34.64	35.79	55.56	26.212	10.693	0	0	0	0	0	0	0	0	0	0	0
86 - 5488 - 259 ...	86 - 5488 - 260 ...	86 - 5488 - 261 ...	86 - 5488 - 316 ...	86 - 5488 - 262 ...	86 - 5488 - 314 ...	86 - 5488 - 315 ...	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
86 - 5391 - 259 ...	86 - 5391 - 260 ...	86 - 5391 - 261 ...	86 - 5391 - 316 ...	-	-	-	50	50	50	50	50	50	50	70.14	40.39	61.85	44.59	55.7	45.2	54.89	45.38	58.65	45.8	70.0
86 - 5664 - 259 ...	86 - 5664 - 260 ...	86 - 5664 - 261 ...	86 - 5664 - 316 ...	-	86 - 5664 - 314 ...	86 - 5664 - 315 ...	168.02	150.5	178.28	133.75	92.12	121.67	144.48	94.36	36.19	70.77	42.56	65.69	42.05	55.17	42.29	65.59	42.05	70.7
86 - 5665 - 259 ...	86 - 5665 - 260 ...	86 - 5665 - 261 ...	86 - 5665 - 316 ...	-	86 - 5665 - 314 ...	86 - 5665 - 315 ...	162.2	80.8	209.2	140.85	135.1	183.7	167.6	94.58	36.15	78.16	39.77	65.57	45.05	65.57	45.05	78.16	39.77	94.5
86 - 5433 - 259 ...	86 - 5433 - 260 ...	86 - 5433 - 261 ...	86 - 5433 - 316 ...	-	86 - 5433 - 314 ...	86 - 5433 - 315 ...	165.138	106.228	226.157	130.134	72.71	180.177	164.616	101.36	36.11	77.22	42.49	68.02	45.62	60	45.42	68.02	45.62	77.2
86 - 5608 - 259 ...	86 - 5608 - 260 ...	86 - 5608 - 261 ...	86 - 5608 - 316 ...	-	86 - 5608 - 314 ...	86 - 5608 - 315 ...	150.84	152.5	30.94	32.37	54.36	19.837	29.85	64.14	40.145	54.32	46.32	53.8	46.7	53.8	46.7	54.32	46.32	54.9
86 - 5555 - 259 ...	86 - 5555 - 260 ...	86 - 5555 - 261 ...	86 - 5555 - 316 ...	-	86 - 5555 - 314 ...	86 - 5555 - 315 ...	168.001	150.288	178.399	133.115	92.491	121.257	144.126	97.05	36.16	71.13	43.09	65.45	42.12	55.66	42.18	65.45	42.12	71.1

Online results submission

- many numerical values

	Z1	Z2	Z3	Z4	Z5	Z6	Z7
	148.33	155.88	202.12	164.35	180.91	30.29	185.19
	25.97	153.5	34.64	35.79	55.56	26.212	10.692
	0	0	0	0	0	0	0
	50	50	50	50	50	50	50



Online results submission


**Grade = Quality of the work +
+ Quality of the submission**

TEM transmission lines

Course Topics

- **Transmission lines**
- Impedance matching and tuning
- Directional couplers
- Power dividers
- Microwave amplifier design
- Microwave filters
- ~~Oscillators and mixers?~~

The lossless line

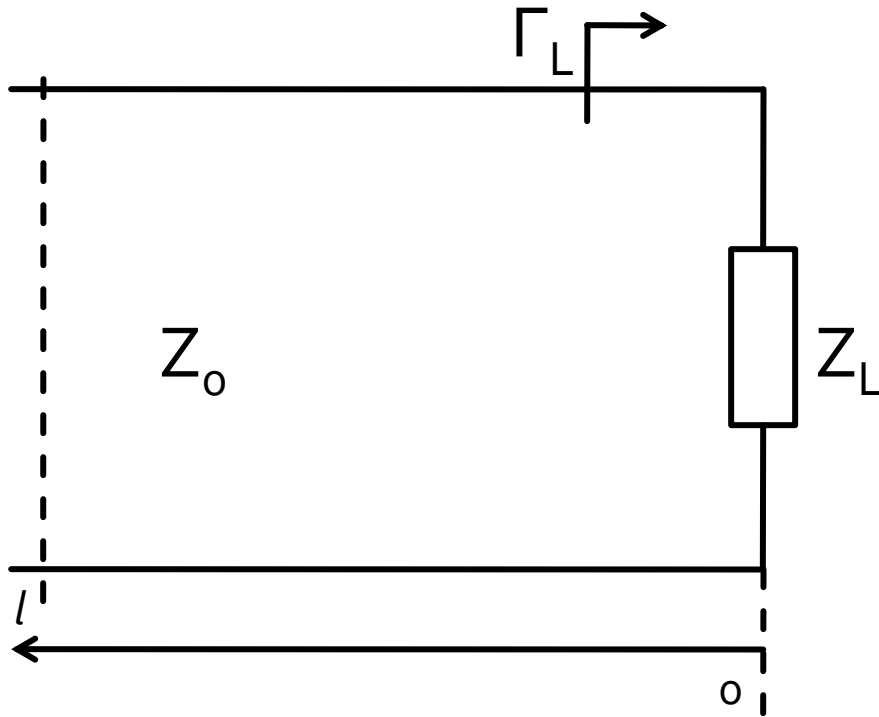

$$V(z) = V_0^+ e^{-j\beta \cdot z} + V_0^- e^{j\beta \cdot z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta \cdot z} - \frac{V_0^-}{Z_0} e^{j\beta \cdot z}$$

$$Z_L = \frac{V(0)}{I(0)} \quad Z_L = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \cdot Z_0$$

- voltage reflection coefficient

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

- Z_0 real

The lossless line

$$V(z) = V_0^+ \cdot (e^{-j\beta \cdot z} + \Gamma \cdot e^{j\beta \cdot z})$$

$$I(z) = \frac{V_0^+}{Z_0} \cdot (e^{-j\beta \cdot z} - \Gamma \cdot e^{j\beta \cdot z})$$

- time-average Power flow along the line

$$P_{avg} = \frac{1}{2} \cdot \text{Re}\{V(z) \cdot I(z)^*\} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot \text{Re}\{1 - \Gamma^* \cdot e^{-2j\beta \cdot z} + \Gamma \cdot e^{2j\beta \cdot z} - |\Gamma|^2\}$$

$$P_{avg} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot (1 - |\Gamma|^2)$$

$$(z - z^*) = \text{Im}$$


- Total power delivered to the load = Incident power – “Reflected” power

- Return “Loss” [dB]

$$RL = -20 \cdot \log|\Gamma| \quad [\text{dB}]$$

The lossless line

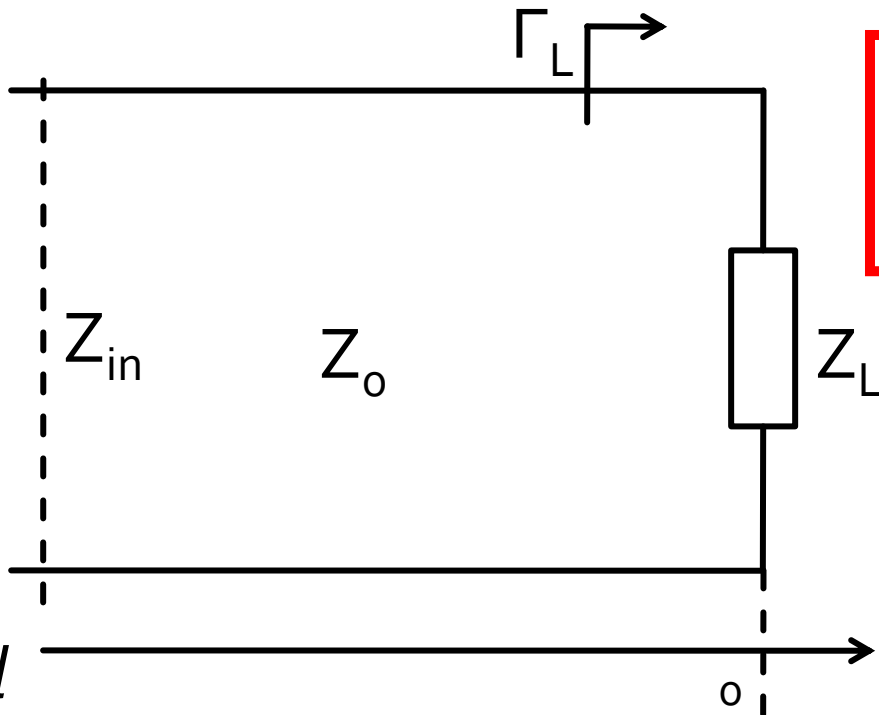- input impedance of a length l of transmission line with characteristic impedance Z_0 , loaded with an arbitrary impedance Z_L




$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

General theory

Microwave Network Analysis

Scattering matrix – S

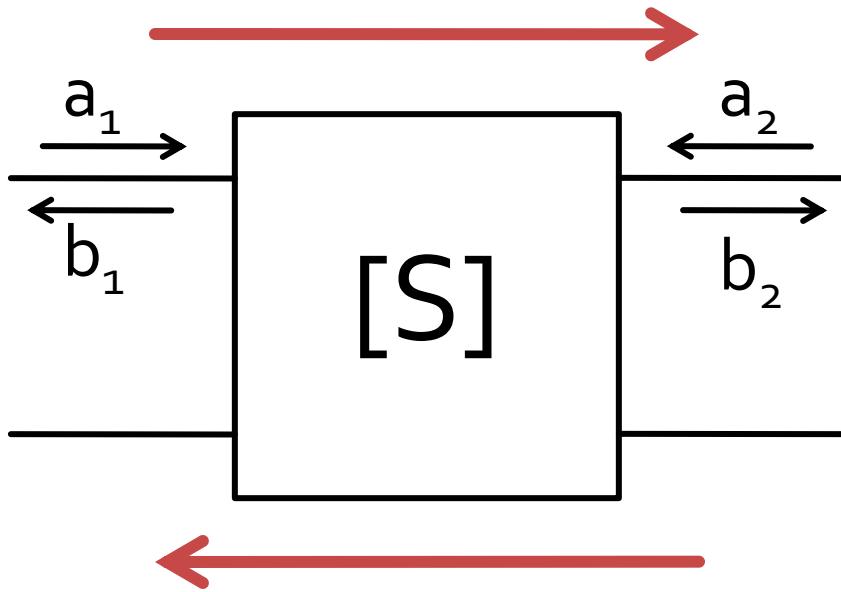

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$


$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- a, b
 - information about signal power **AND** signal phase
- S_{ij}
 - network effect (gain) over signal power **including** phase information


Impedance Matching

The Smith Chart

The Smith Chart

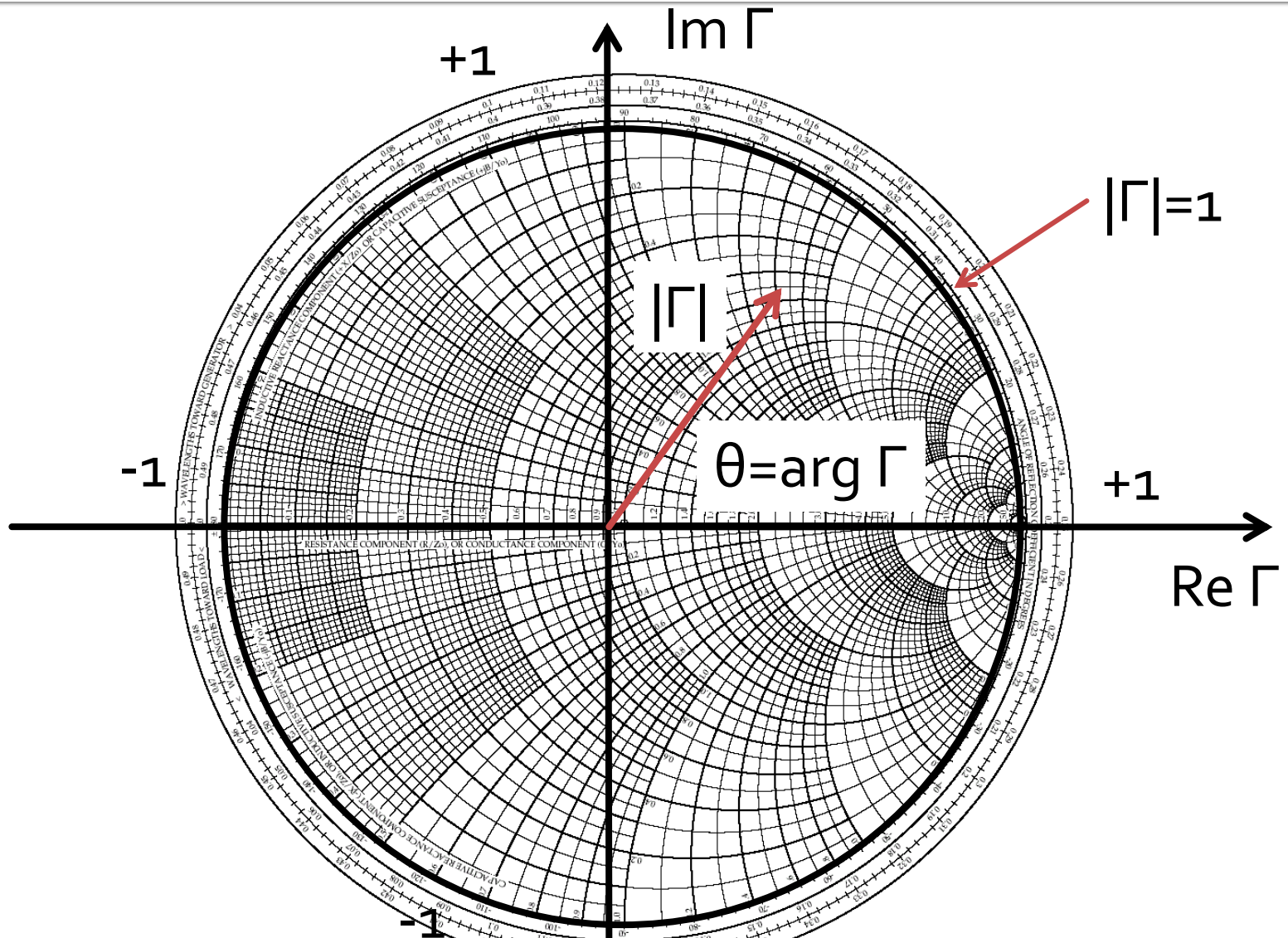


The Smith Chart

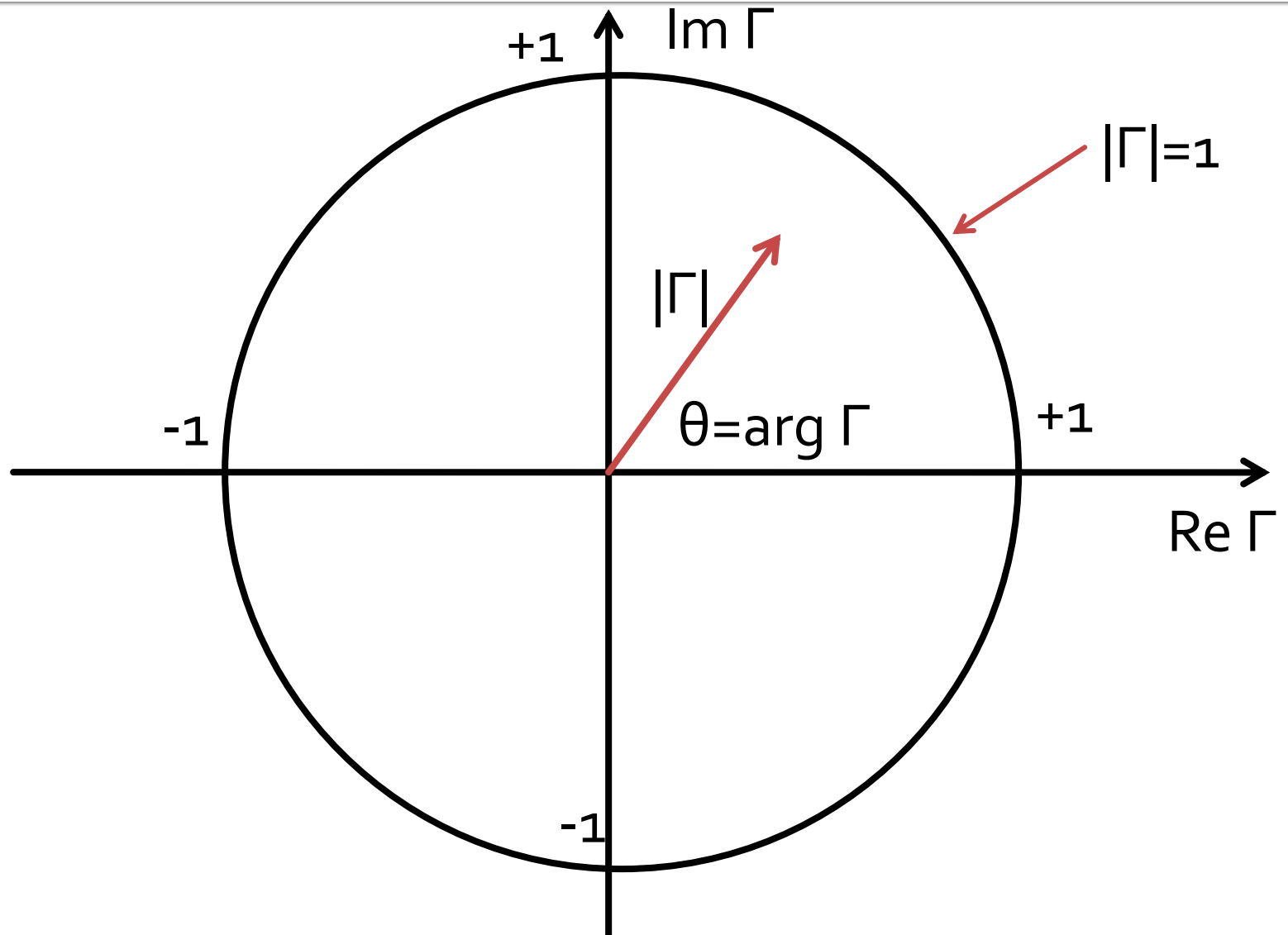

Impedance Matching

Impedance Matching with Stubs

Smith chart, $r=1$ and $g=1$

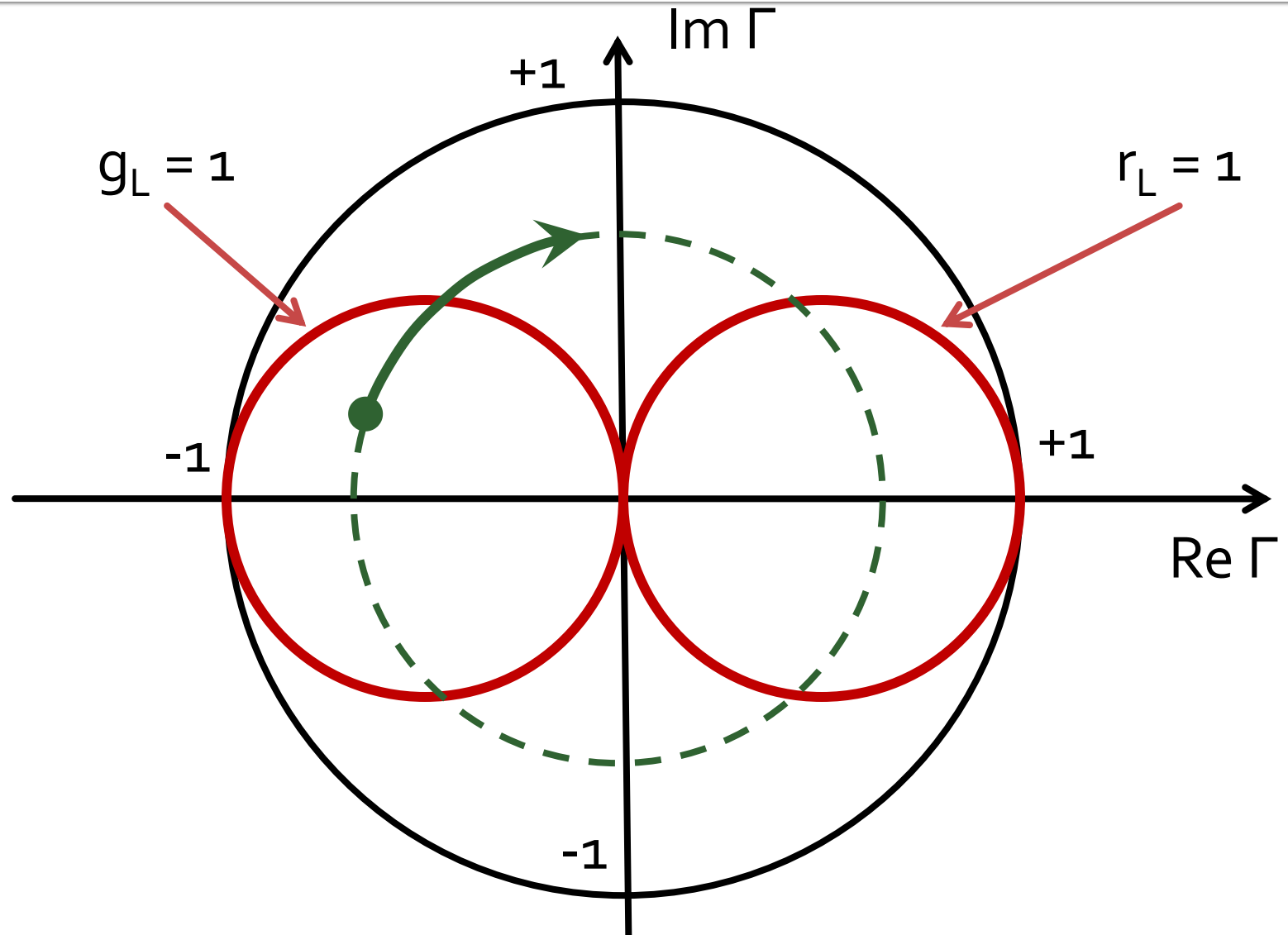


Analytical solutions


Exam / Project

Case 1, Shunt Stub

- Shunt Stub

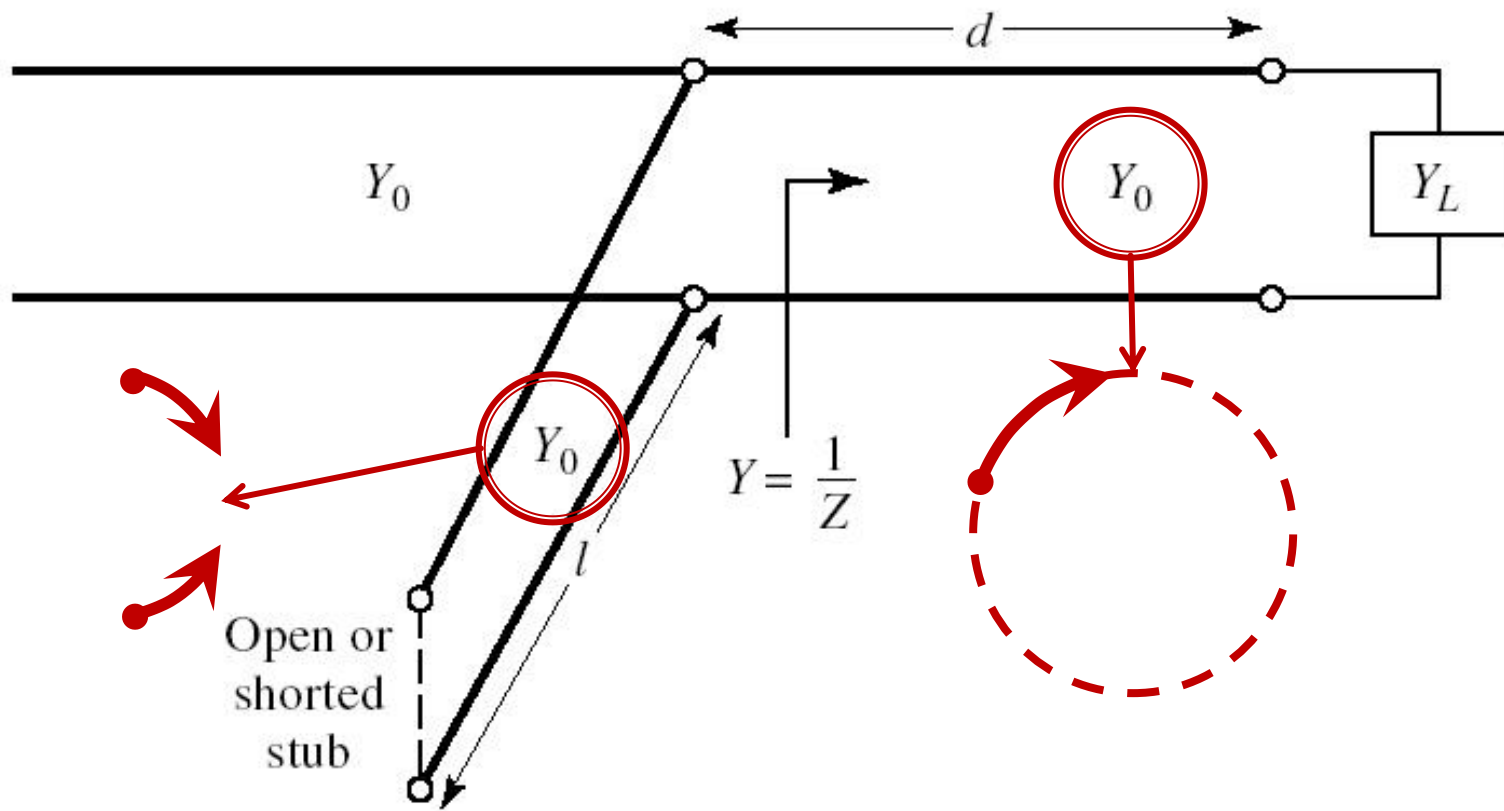

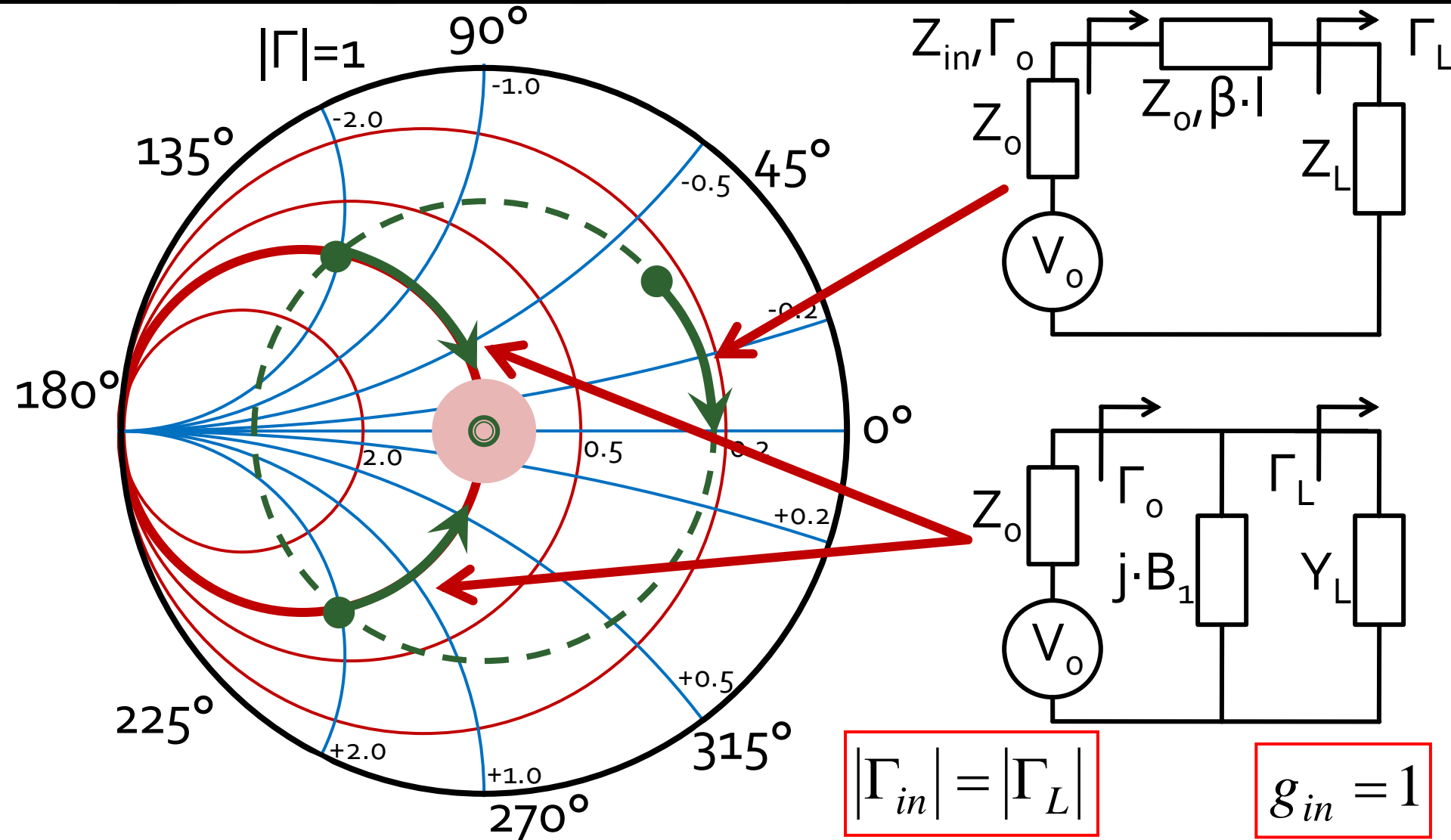Matching, series line + shunt susceptance



Analytical solution, usage

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = 0.593 \angle 46.85^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ \quad \cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **“+” solution** ↓

$$(46.85^\circ + 2\theta) = +126.35^\circ \quad \theta = +39.7^\circ \quad \text{Im } y_S = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.472$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_S) = -55.8^\circ (+180^\circ) \rightarrow \theta_{sp} = 124.2^\circ$$

- **“-” solution** ↓

$$(46.85^\circ + 2\theta) = -126.35^\circ \quad \theta = -86.6^\circ (+180^\circ) \rightarrow \theta = 93.4^\circ$$

$$\text{Im } y_S = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +1.472 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_S) = 55.8^\circ$$

Analytical solution, usage

$$(\varphi + 2\theta) = \begin{cases} +126.35^\circ \\ -126.35^\circ \end{cases} \quad \theta = \begin{cases} 39.7^\circ \\ 93.4^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -1.472 \\ +1.472 \end{cases} \quad \theta_{sp} = \begin{cases} -55.8^\circ + 180^\circ = 124.2^\circ \\ +55.8^\circ \end{cases}$$



- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

$$l_1 = \frac{39.7^\circ}{360^\circ} \cdot \lambda = 0.110 \cdot \lambda$$

$$l_2 = \frac{124.2^\circ}{360^\circ} \cdot \lambda = 0.345 \cdot \lambda$$


$$l_1 = \frac{93.4^\circ}{360^\circ} \cdot \lambda = 0.259 \cdot \lambda$$
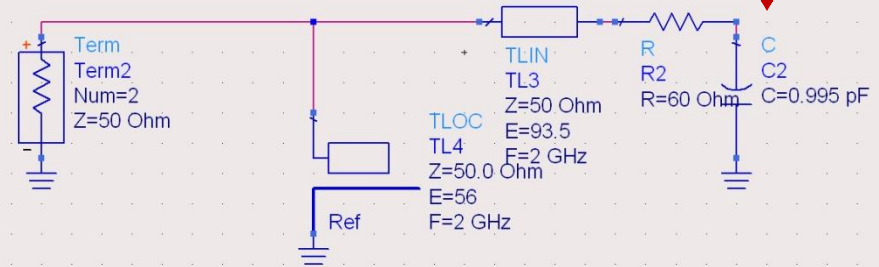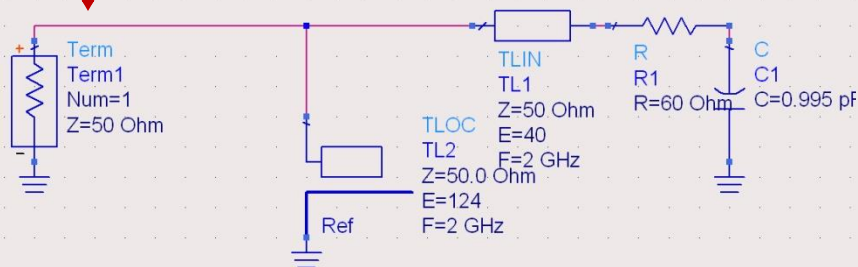
$$l_2 = \frac{55.8^\circ}{360^\circ} \cdot \lambda = 0.155 \cdot \lambda$$






Case 2, Series Stub

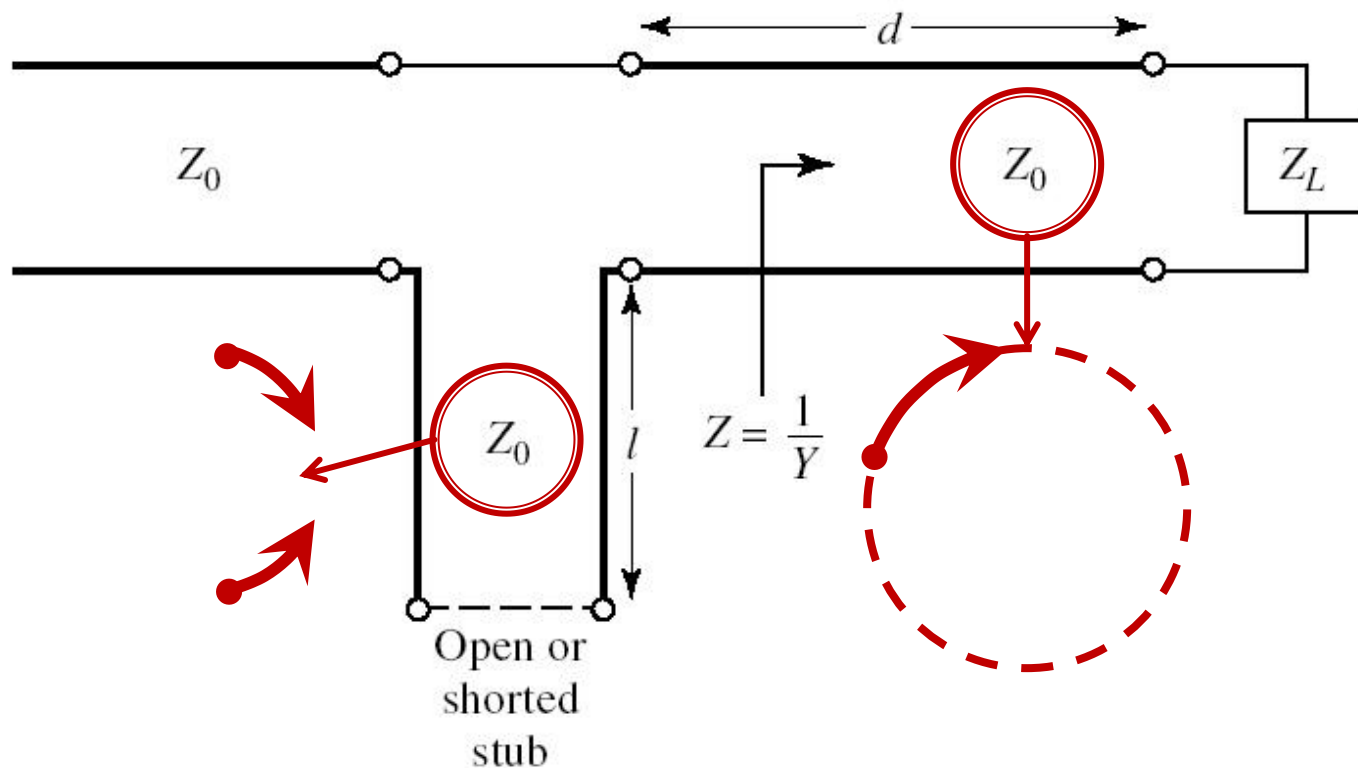- Series Stub
- difficult to realize in single conductor line technologies (microstrip)



Matching, series line + series reactance

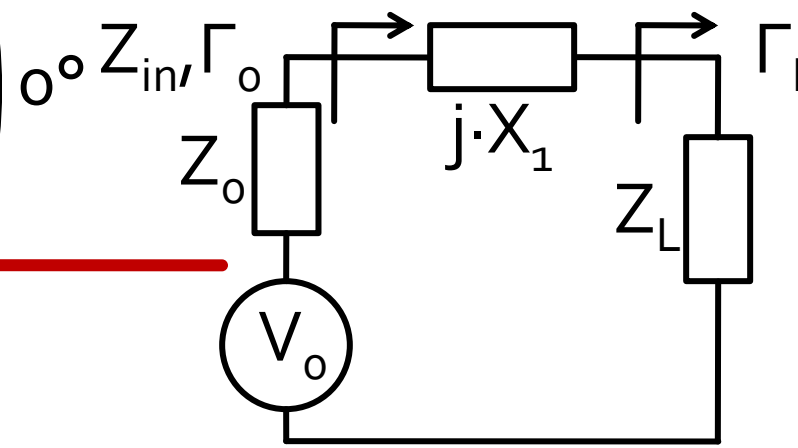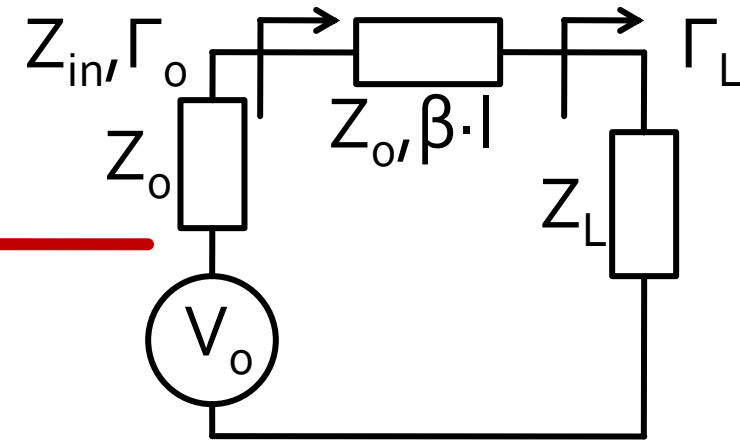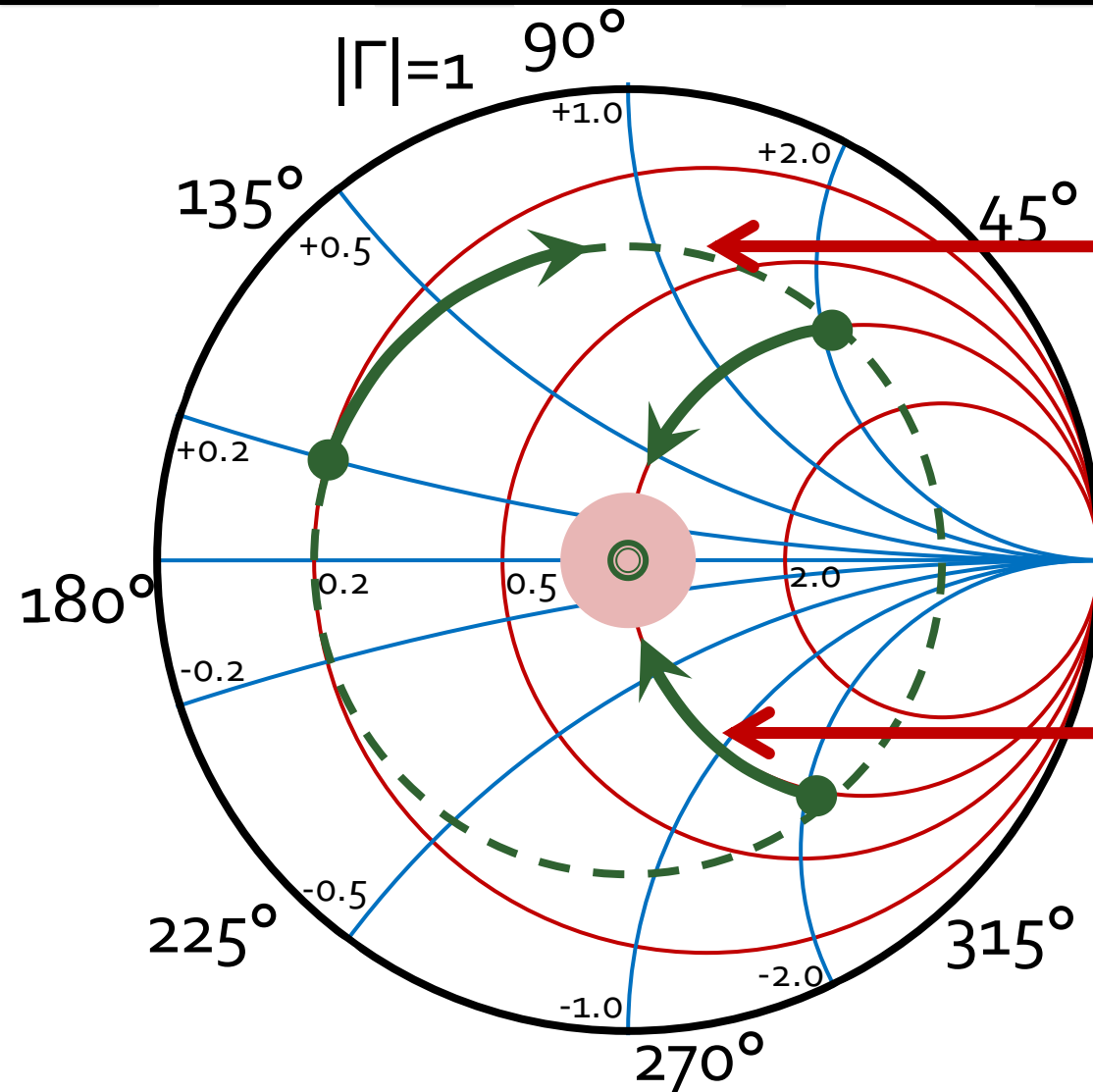

$$|\Gamma_{in}| = |\Gamma_L|$$

$$r_{in} = 1$$

Analytical solution, usage

$$\cos(\varphi + 2\theta) = |\Gamma_s|$$

$$\theta_{ss} = \beta \cdot l = \cot^{-1} \frac{\mp 2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}}$$

$$\Gamma_s = 0.555 \angle -29.92^\circ$$

$$|\Gamma_s| = 0.555; \quad \varphi = -29.92^\circ \quad \cos(\varphi + 2\theta) = 0.555 \Rightarrow (\varphi + 2\theta) = \pm 56.28^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

- **"+" solution** ↓

$$(-29.92^\circ + 2\theta) = +56.28^\circ \quad \theta = 43.1^\circ \quad \text{Im } z_s = \frac{+2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} = +1.335$$

$$\theta_{ss} = -\cot^{-1}(\text{Im } z_s) = -36.8^\circ (+180^\circ) \rightarrow \theta_{ss} = 143.2^\circ$$

- **"-" solution** ↓

$$(-29.92^\circ + 2\theta) = -56.28^\circ \quad \theta = -13.2^\circ (+180^\circ) \rightarrow \theta = 166.8^\circ$$

$$\text{Im } z_s = \frac{-2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} = -1.335 \quad \theta_{ss} = -\cot^{-1}(\text{Im } z_s) = 36.8^\circ$$

Analytical solution, usage

$$(\varphi + 2\theta) = \begin{cases} +56.28^\circ \\ -56.28^\circ \end{cases} \quad \theta = \begin{cases} 43.1^\circ \\ 166.8^\circ \end{cases} \quad \text{Im}[z_s(\theta)] = \begin{cases} +1.335 \\ -1.335 \end{cases} \quad \theta_{ss} = \begin{cases} -36.8^\circ + 180^\circ = 143.2^\circ \\ +36.8^\circ \end{cases}$$

- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

$$l_1 = \frac{43.1^\circ}{360^\circ} \cdot \lambda = 0.120 \cdot \lambda$$

$$l_2 = \frac{143.2^\circ}{360^\circ} \cdot \lambda = 0.398 \cdot \lambda$$

$$l_1 = \frac{166.8^\circ}{360^\circ} \cdot \lambda = 0.463 \cdot \lambda$$

$$l_2 = \frac{36.8^\circ}{360^\circ} \cdot \lambda = 0.102 \cdot \lambda$$



Stub, observations

- adding or subtracting **180°** ($\lambda/2$) doesn't change the result (full rotation around the Smith Chart)

$$E = \beta \cdot l = \pi = 180^\circ \quad l = k \cdot \frac{\lambda}{2}, \forall k \in \mathbf{N}$$


- if the lines/stubs result with **negative** "length"/ "electrical length" we add $\lambda/2 / 180^\circ$ to obtain physically realizable lines
- adding or subtracting **90°** ($\lambda/4$) change the stub impedance:

$$Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l \quad \Leftrightarrow \quad Z_{in,g} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$

- for the stub we can add or subtract 90° ($\lambda/4$) while in the same time changing **open-circuit** \Leftrightarrow **short-circuit**

Microwave Amplifiers

Amplifier as two-port

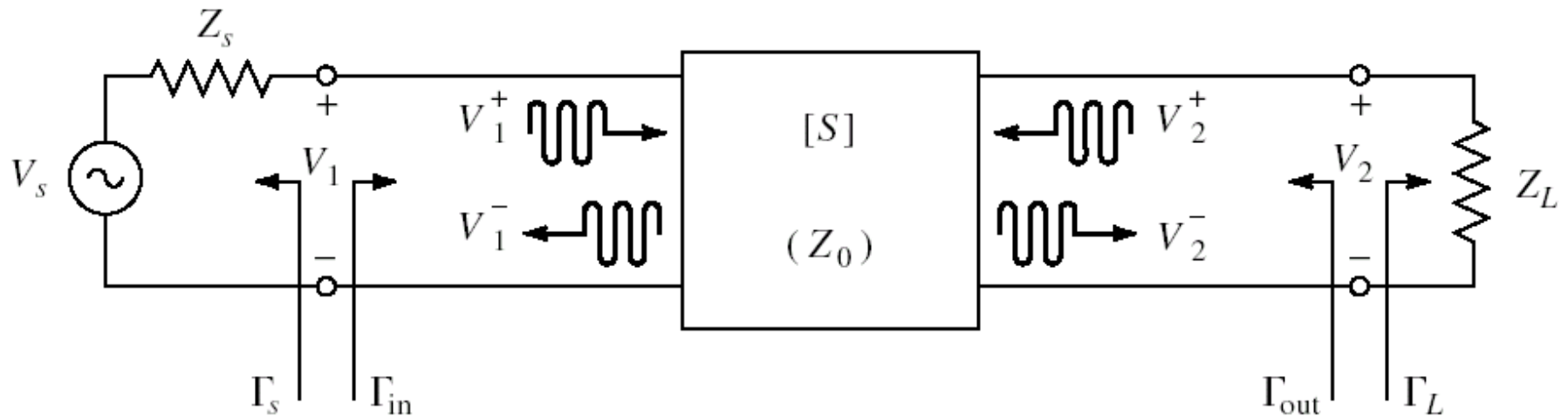


- Charaterized with S parameters
- normalized at Z_0 (implicit 50Ω)
- Datasheets: S parameters for specific bias conditions

S2P - Touchstone

- Touchstone file format (*.s2p)

```
! SIEMENS Small Signal Semiconductors
! VDS = 3.5 V   ID = 15 mA
# GHz S MA R 50
! f      S11      S21      S12      S22
! GHz   MAG ANG   MAG ANG   MAG ANG   MAG ANG
1.000 0.9800 -18.0 2.230 157.0 0.0240 74.0 0.6900 -15.0
2.000 0.9500 -39.0 2.220 136.0 0.0450 57.0 0.6600 -30.0
3.000 0.8900 -64.0 2.210 110.0 0.0680 40.0 0.6100 -45.0
4.000 0.8200 -89.0 2.230 86.0 0.0850 23.0 0.5600 -62.0
5.000 0.7400 -115.0 2.190 61.0 0.0990 7.0 0.4900 -80.0
6.000 0.6500 -142.0 2.110 36.0 0.1070 -10.0 0.4100 -98.0
!
! f      Fmin  Gammaopt  rn/50
! GHz   dB   MAG ANG   -
2.000   1.00 0.72 27 0.84
4.000   1.40 0.64 61 0.58
```

Amplifier as two-port

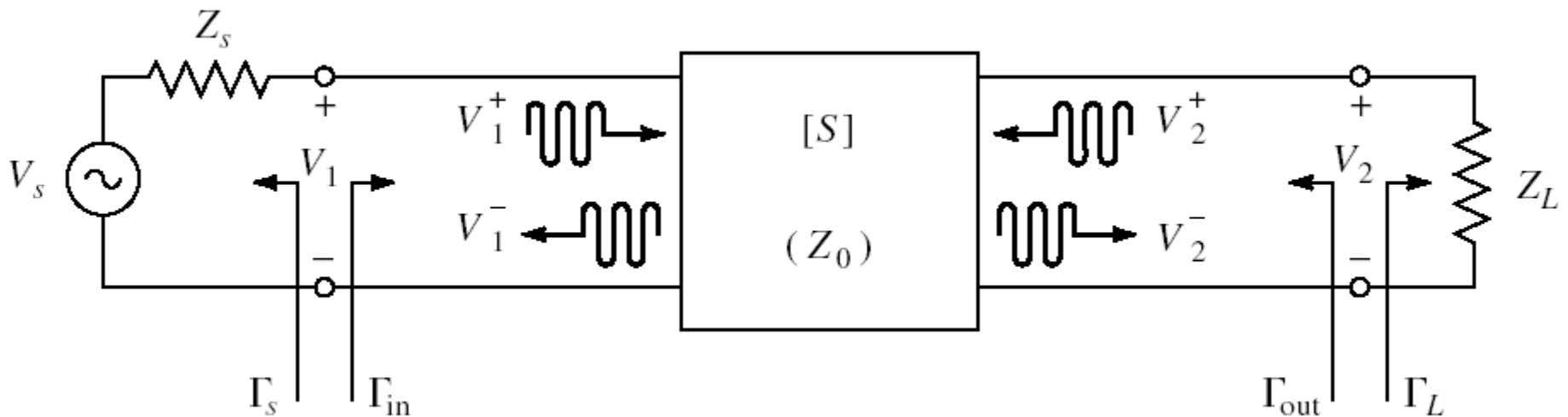


$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_s}{1 - S_{11} \cdot \Gamma_s}$$

Power / Matching

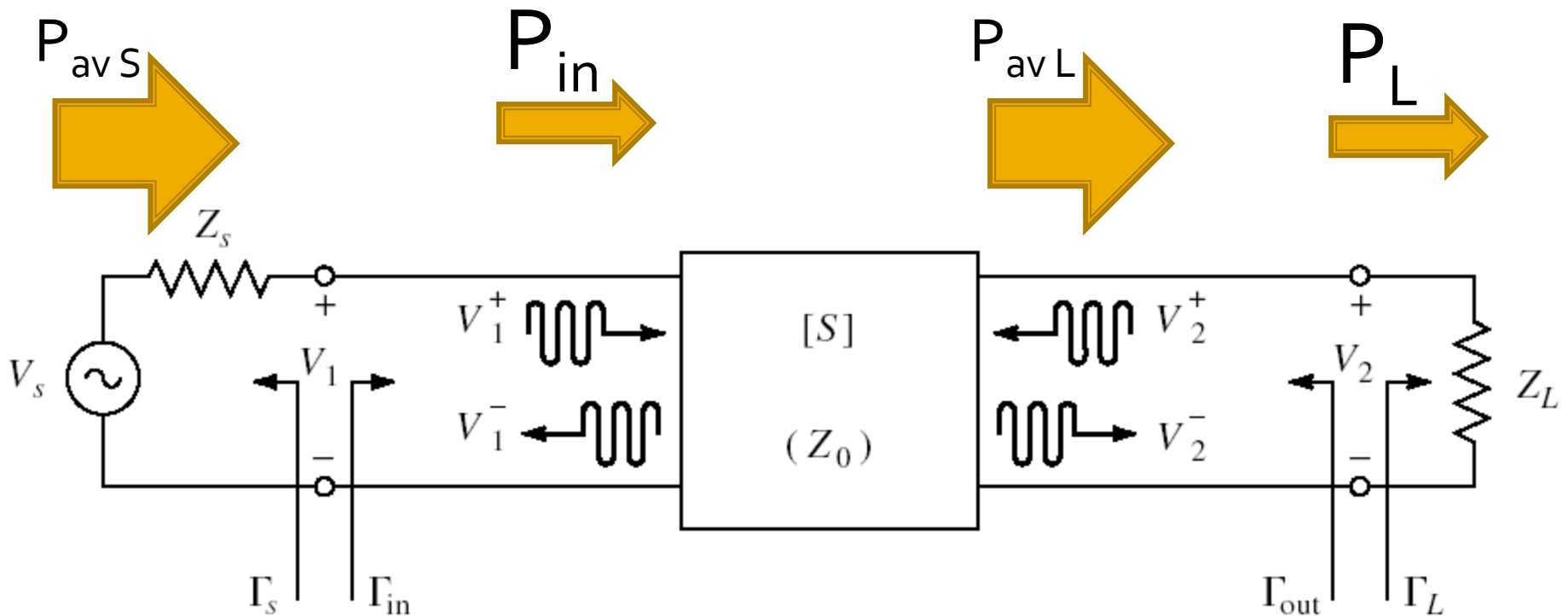- Two ports in which matching influences the power transfer



Two-Port Power Gains

- **Available** power gain

$$G_A = \frac{P_{av L}}{P_{av S}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2)}{|1 - S_{22} \cdot \Gamma_L|^2 \cdot (1 - |\Gamma_{out}|^2)}$$

- **Transducer** power gain

$$G_T = \frac{P_L}{P_{av S}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2}$$

$$\Gamma_{in} = \Gamma_{in}(\Gamma_L)$$

- **Unilateral transducer** power gain

$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$S_{12} \cong 0$$


$$\Gamma_{in} = S_{11}$$

Input and output can be treated independently

Microwave Amplifiers

Stability

Amplifier as two-port

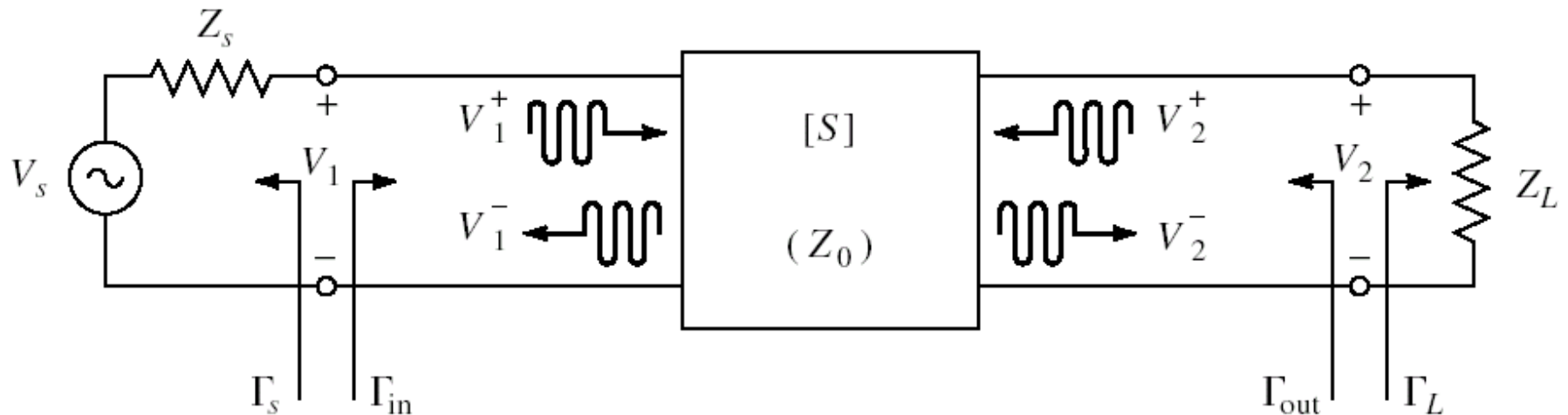

- For an amplifier two-port we are interested in:
 - **stability**
 - power gain
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)

Stability

- L7 $\Gamma = \Gamma_r + j \cdot \Gamma_i$ $r_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$
 Z_{in} $\Gamma_{in} = \Gamma_r + j \cdot \Gamma_i$
- instability
 $\text{Re}\{Z_{in}\} < 0 \iff 1 - \Gamma_r^2 - \Gamma_i^2 < 0 \quad \Gamma_r^2 + \Gamma_i^2 > 1 \quad |\Gamma_{in}| > 1$
- stability, Z_{in}
 - conditions to be met by Γ_L to achieve (input) stability
 $|\Gamma_{in}| < 1 \quad \left| S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \right| < 1$
- similarly Z_{out}
 - conditions to be met by Γ_S to achieve (output) stability

Output stability circle (CSOUT)

$$\left| \Gamma_L - \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12} \cdot S_{21}}{|S_{22}|^2 - |\Delta|^2} \right| \quad |\Gamma_L - C_L| = R_L$$


- We obtain the equation of a circle in the complex plane, which represents the locus of Γ_L for the **limit between stability and instability** ($|\Gamma_{in}| = 1$)
- This circle is the **output stability circle** (Γ_L)

$$C_L = \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \quad R_L = \frac{|S_{12} \cdot S_{21}|}{\left| |S_{22}|^2 - |\Delta|^2 \right|}$$


3D representation of $|\Gamma_{in}|$, $|\Gamma_{out}|$, $|\Gamma|=1$

- $|\Gamma| = 1 \rightarrow \log_{10}|\Gamma| = 0$, the intersection with the plane $z = 0$ is a circle

$\log(\Gamma_{in}(\Gamma_L))$

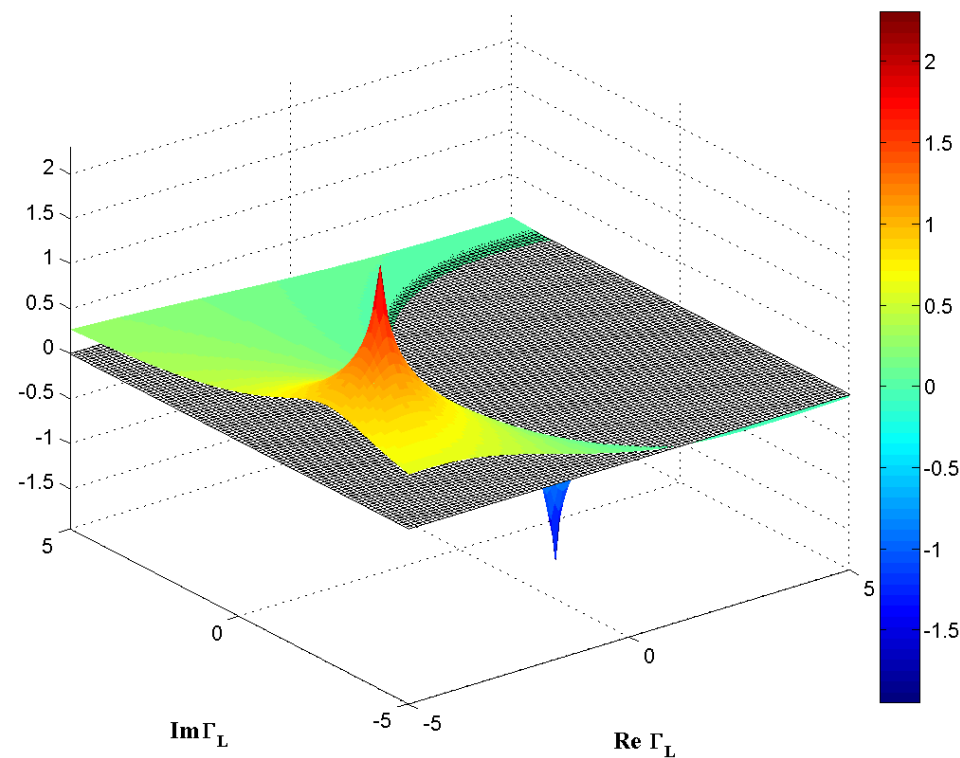


$\log(\Gamma_{out}(\Gamma_S))$


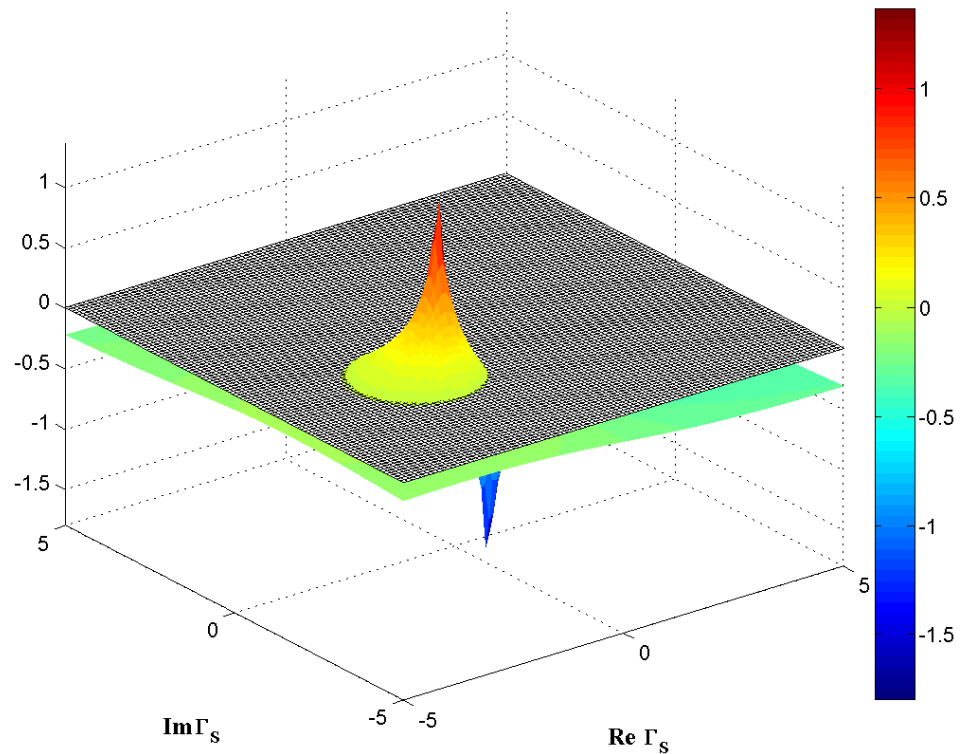


Contour map/lines

contoured peak
(side view)



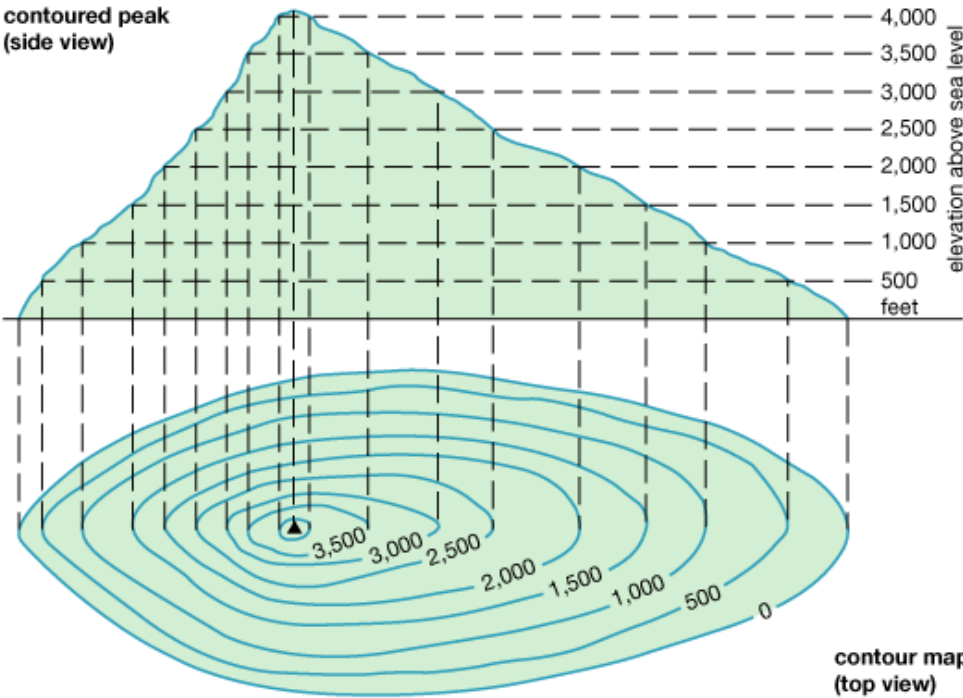


© 2011 Encyclopædia Britannica, Inc.

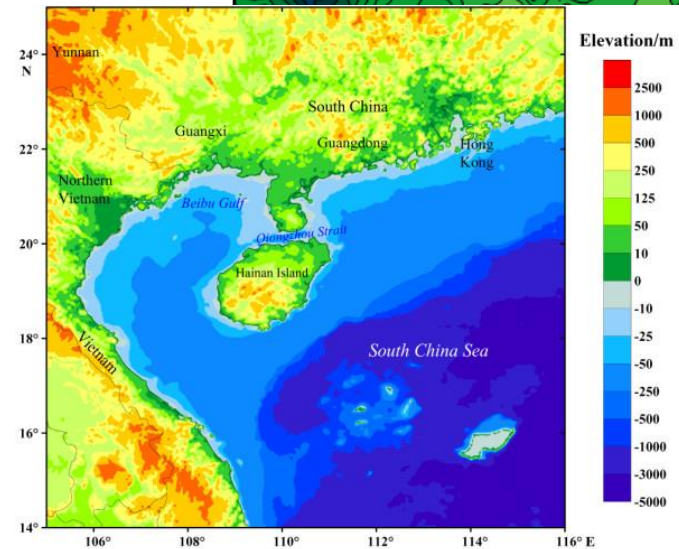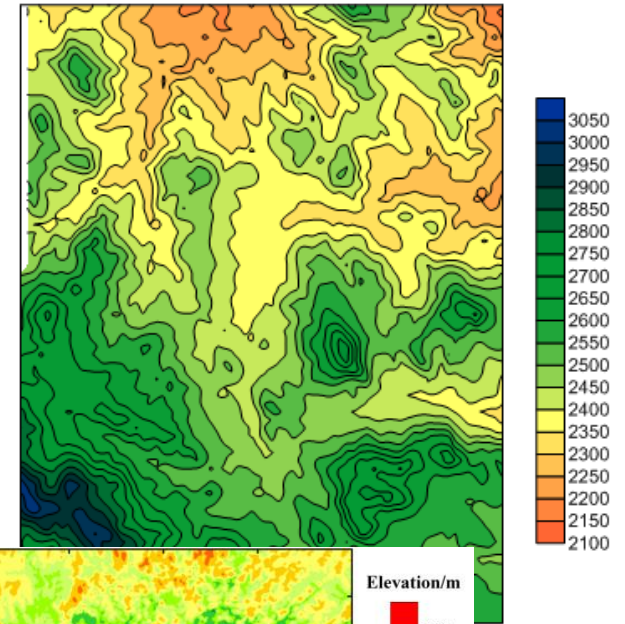


CSIN, CSOUT


CSOUT
CSIN

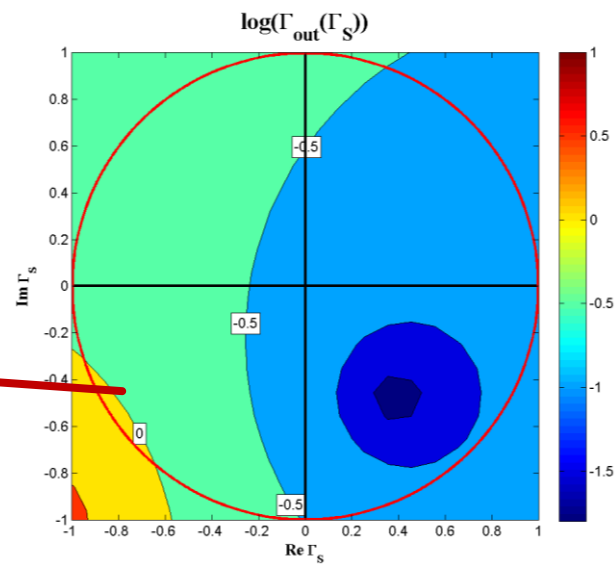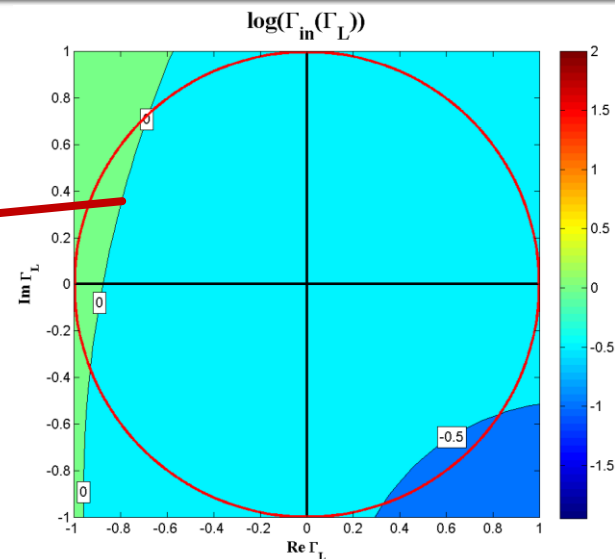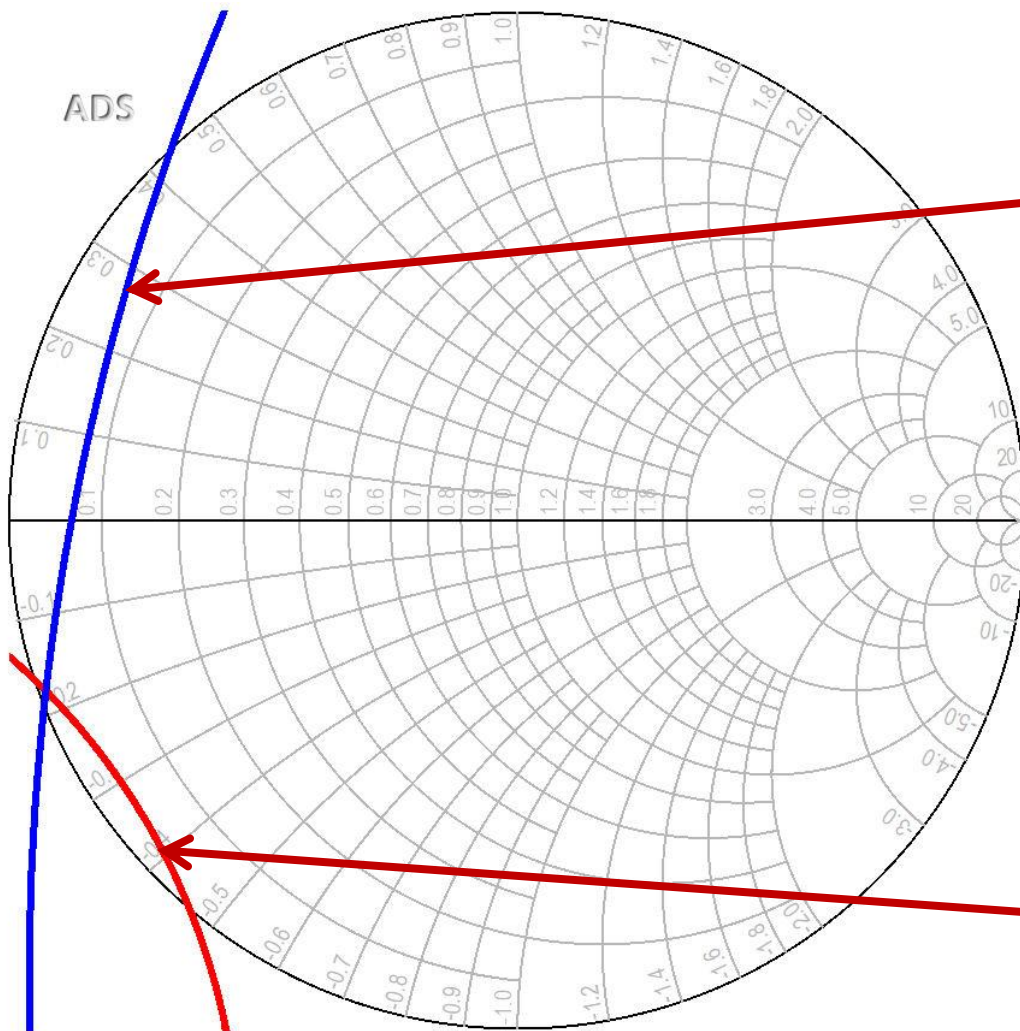


Several possible positioning

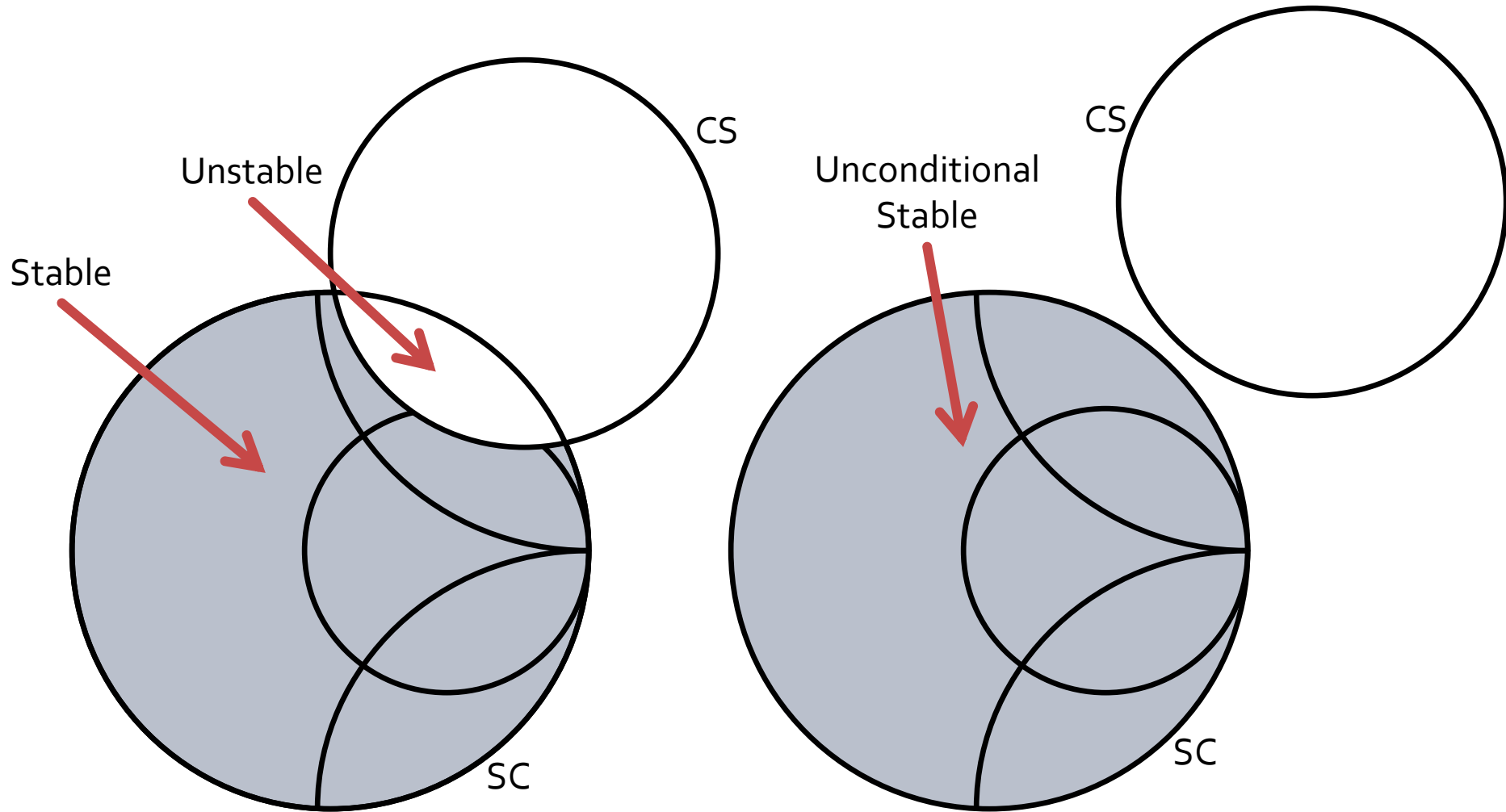

Several possible positioning

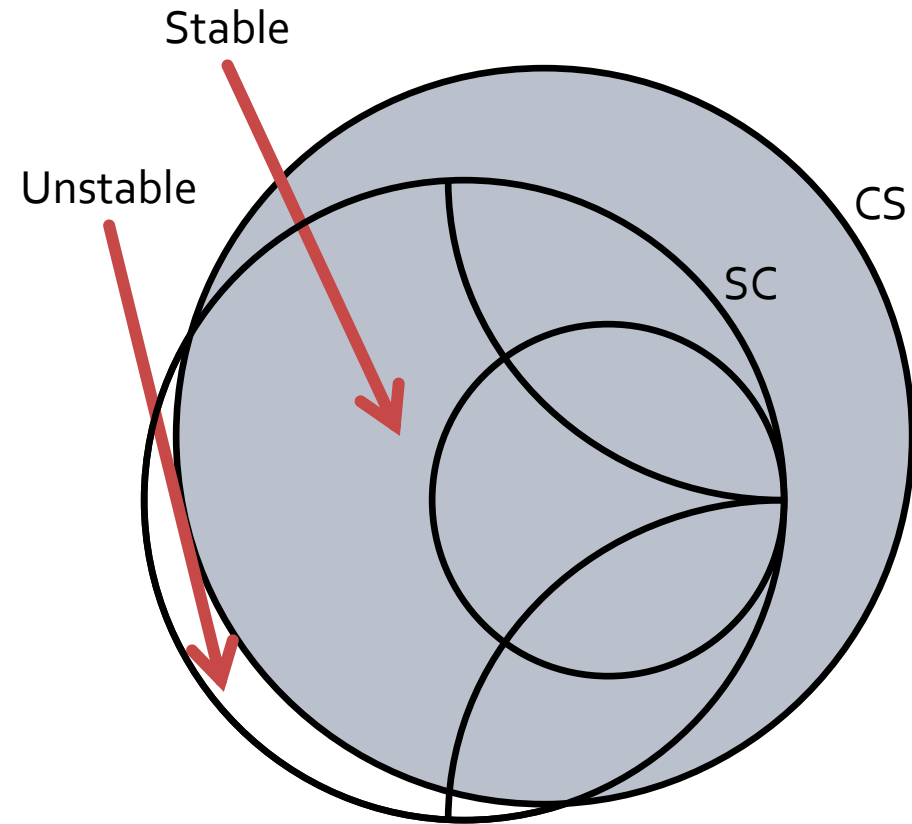

Unconditional
Stable

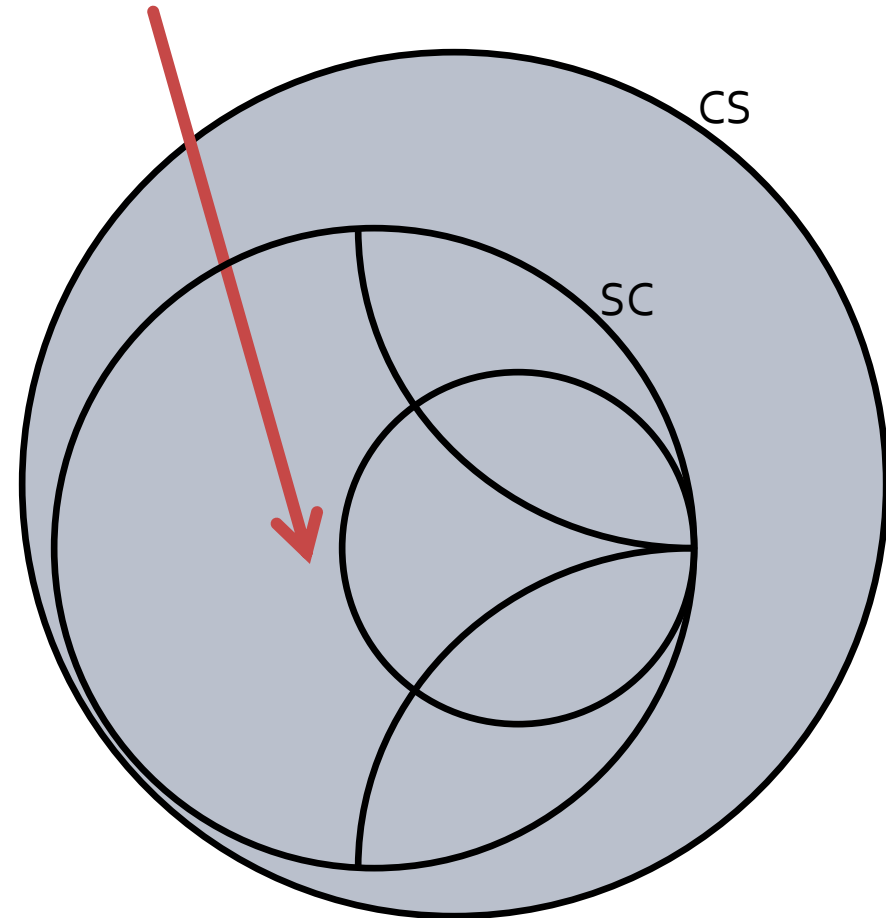


Stability


- **Unconditional stability:** the circuit is unconditionally stable if $|\Gamma_{in}| < 1$ and $|\Gamma_{out}| < 1$ for **any** passive impedance of the load/source
- **Conditional stability:** the circuit is conditionally stable if $|\Gamma_{in}| < 1$ and $|\Gamma_{out}| < 1$ only for **some** passive impedance of the load/source
 - passive impedance of the load/source \leftrightarrow interior of the Smith Chart (radius 1 circle in the complex plane)

Circles in wide frequency range

CSIN

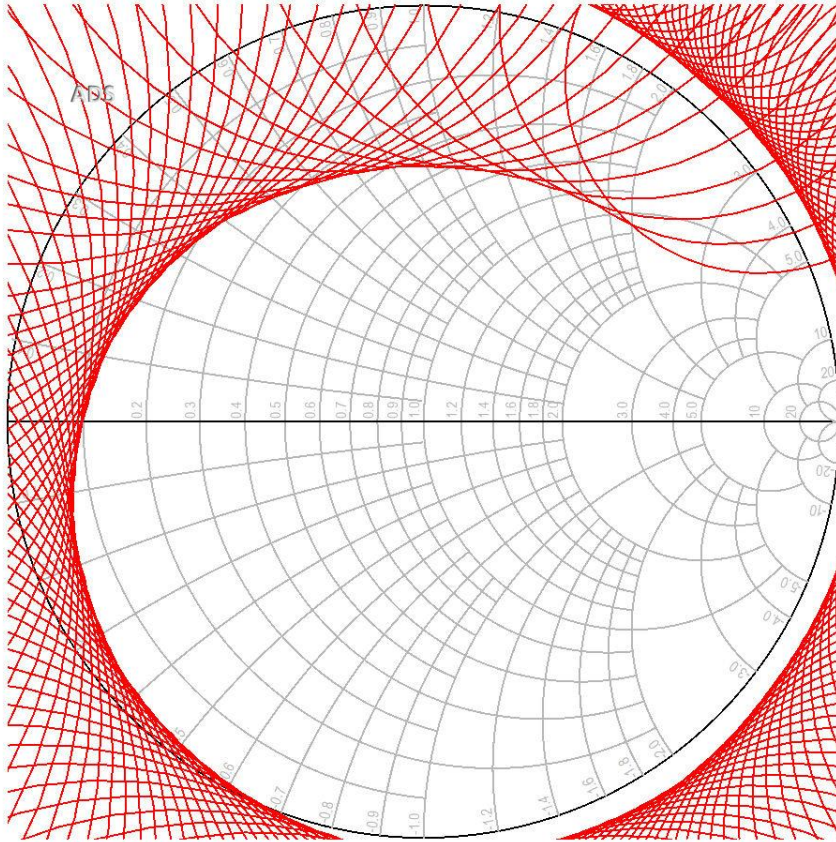

CSOUT

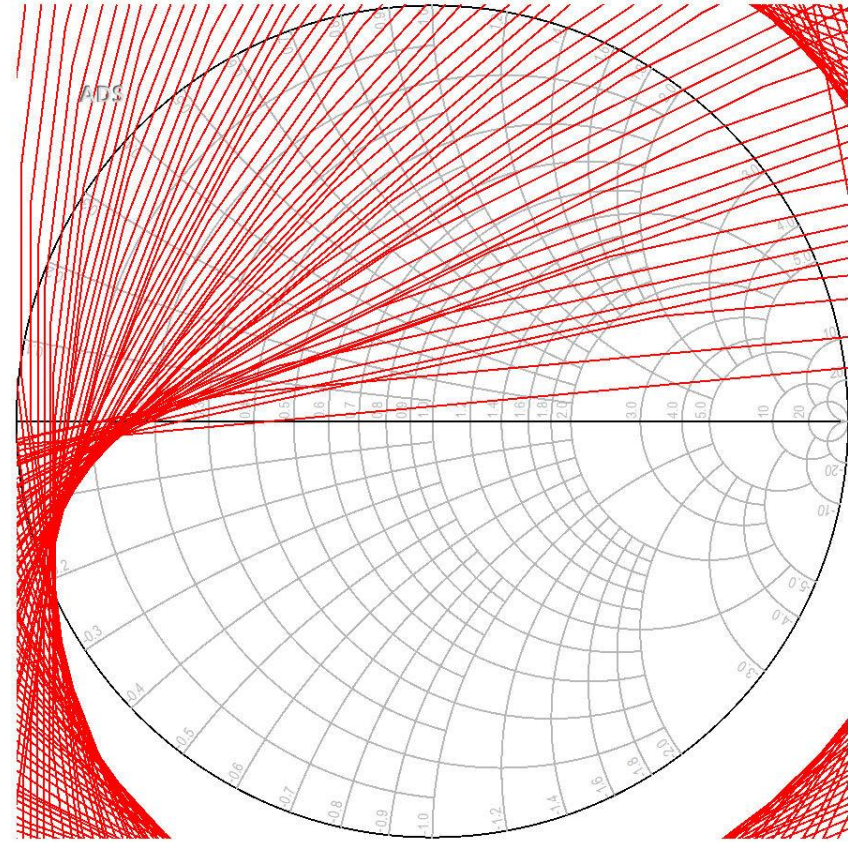

Rollet's condition

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 \cdot |S_{12} \cdot S_{21}|}$$

$$\Delta = S_{11} \cdot S_{22} - S_{12} \cdot S_{21}$$



- The two-port is **unconditionally stable** if:
- two conditions are simultaneously satisfied:
 - $K > 1$
 - $|\Delta| < 1$
- together with the implicit conditions:
 - $|S_{11}| < 1$
 - $|S_{22}| < 1$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 \cdot |S_{12} \cdot S_{21}|} > 1$$


$$|\Delta| = |S_{11} \cdot S_{22} - S_{12} \cdot S_{21}| < 1$$

Stability

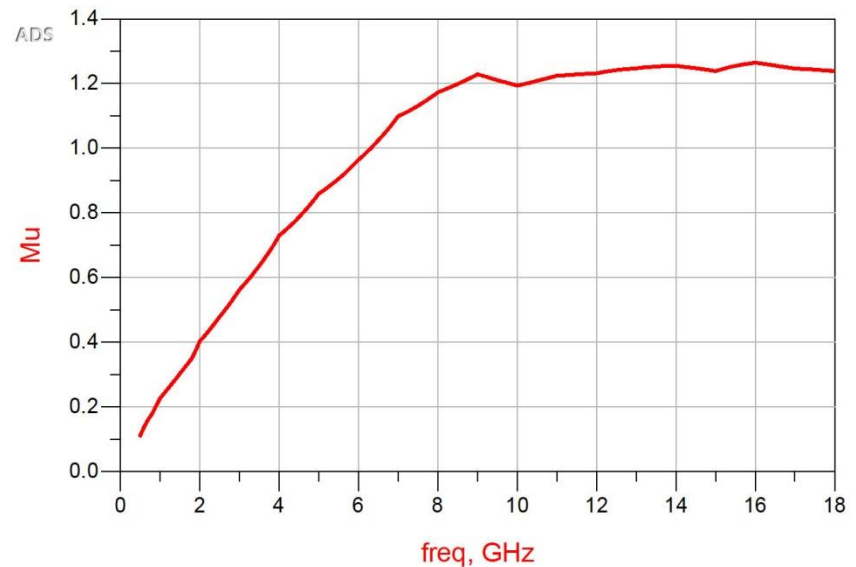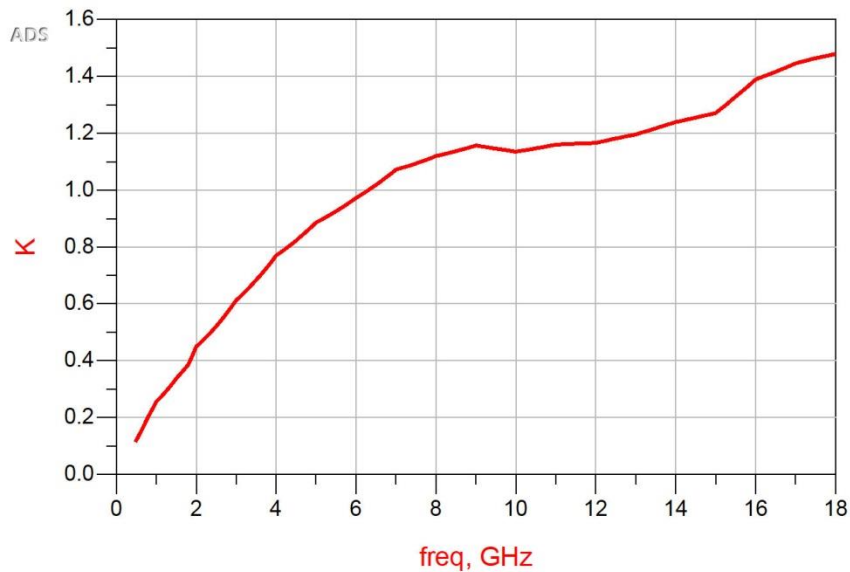
- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz
- unconditionally stable for $f > 6.31GHz$




ADS, $R_s = 2\Omega$

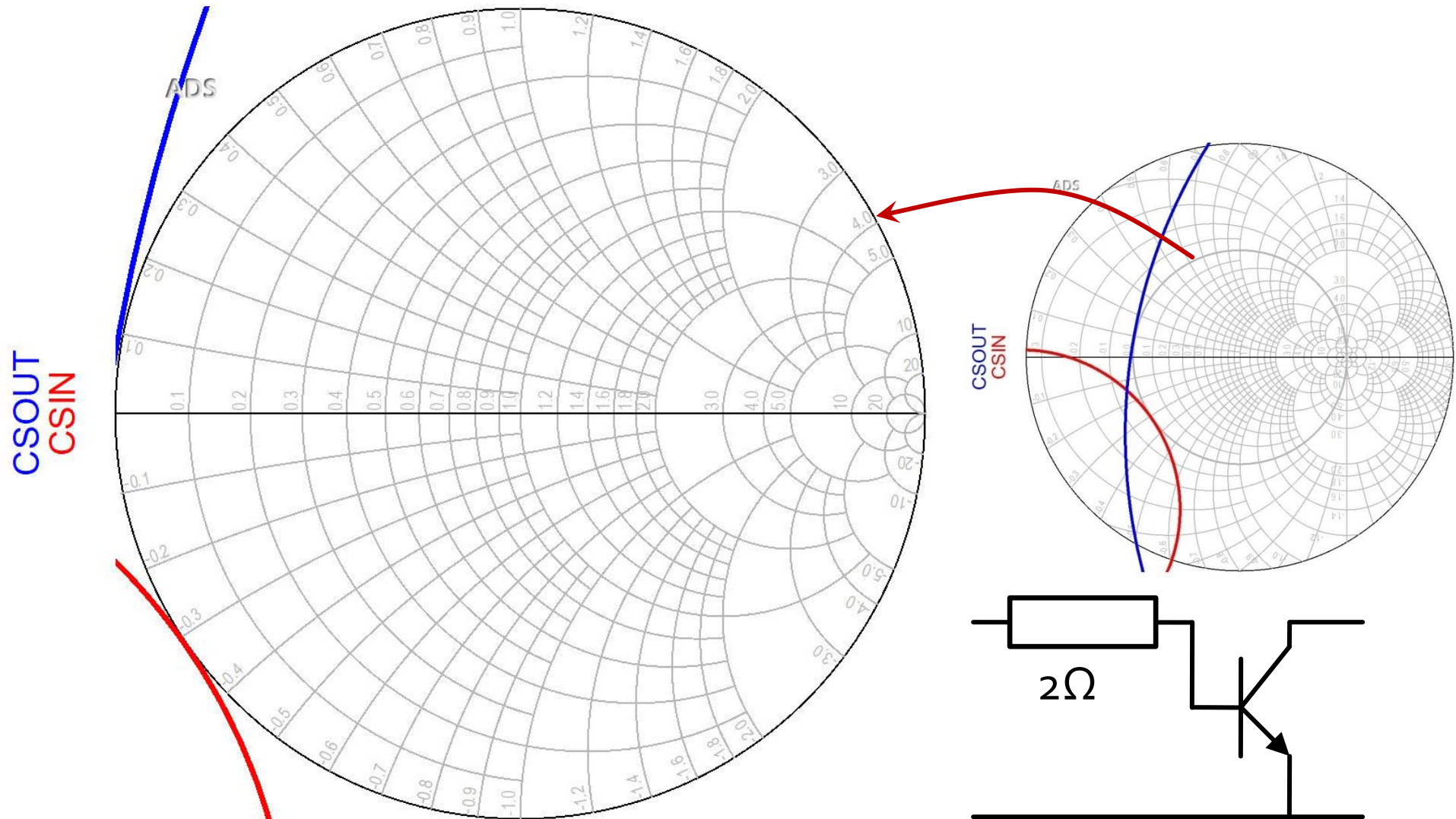


Stabilization of two-port

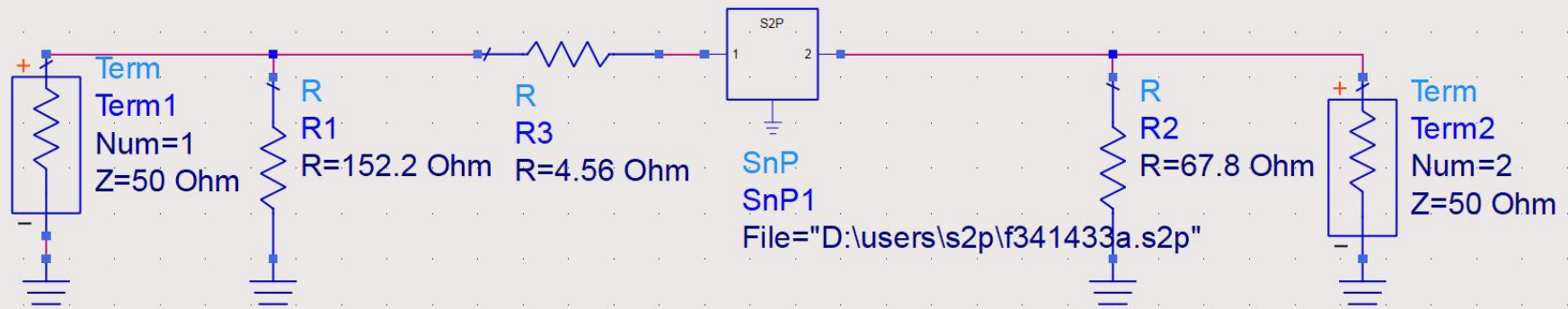


 S-PARAMETERS


S_Param
SP1
Start=0.5 GHz
Stop=10.0 GHz
Step=0.1 GHz

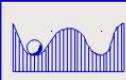 StabFact

StabFact
K
K=stab_fact(S)



 MaxGain

MaxGain
MAG
MAG=max_gain(S)

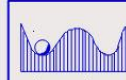
 Mu

Mu
Mu1
Mu=mu(S)

Stabilization of two-port

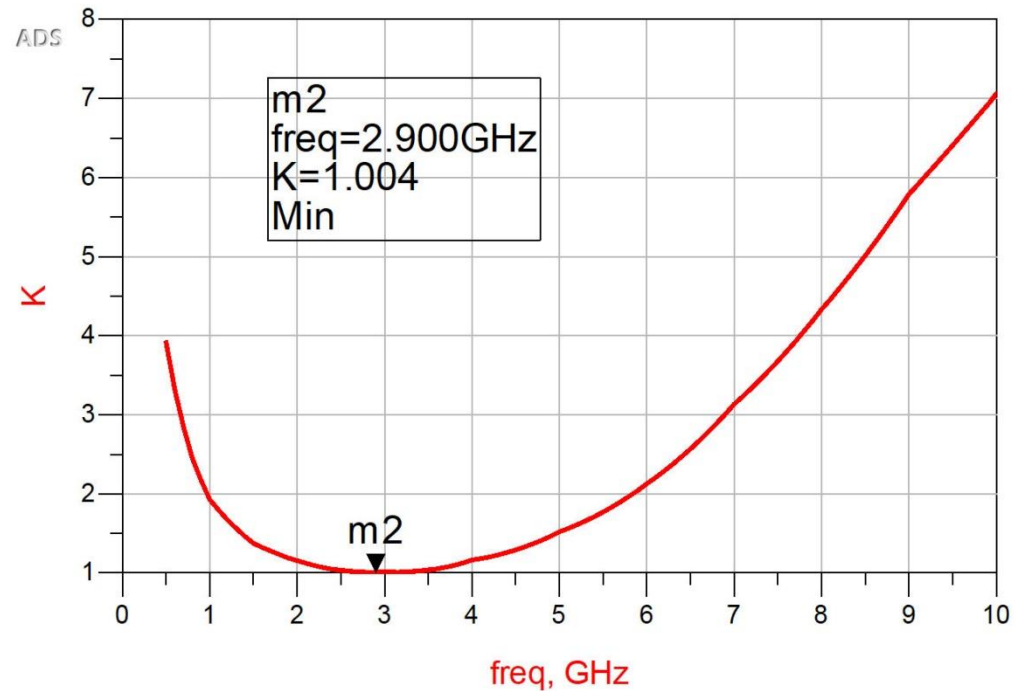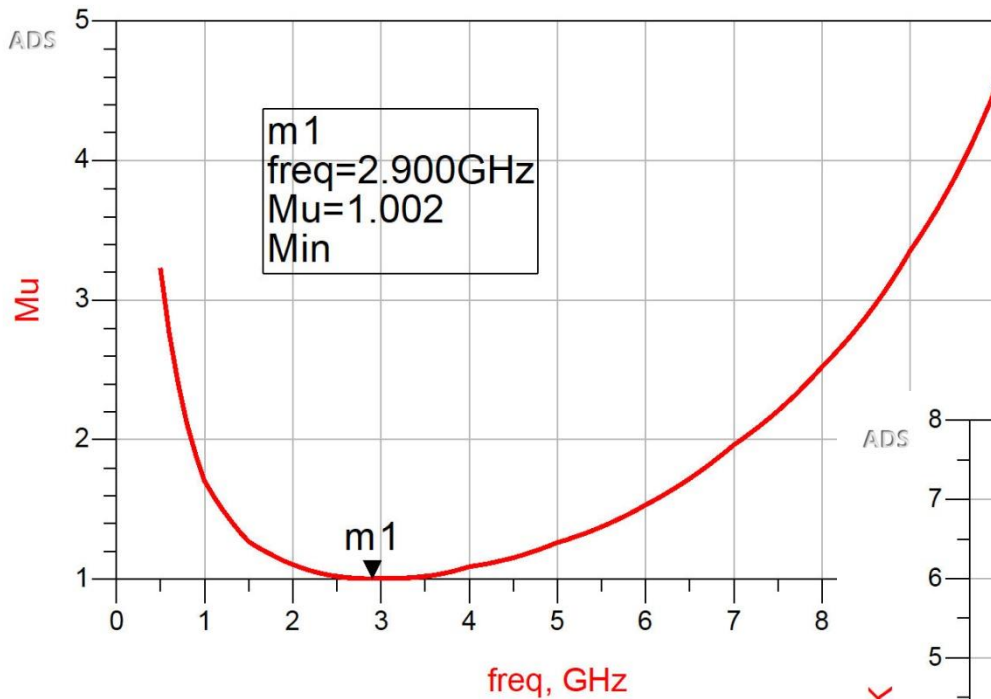

Stabilization of two-port

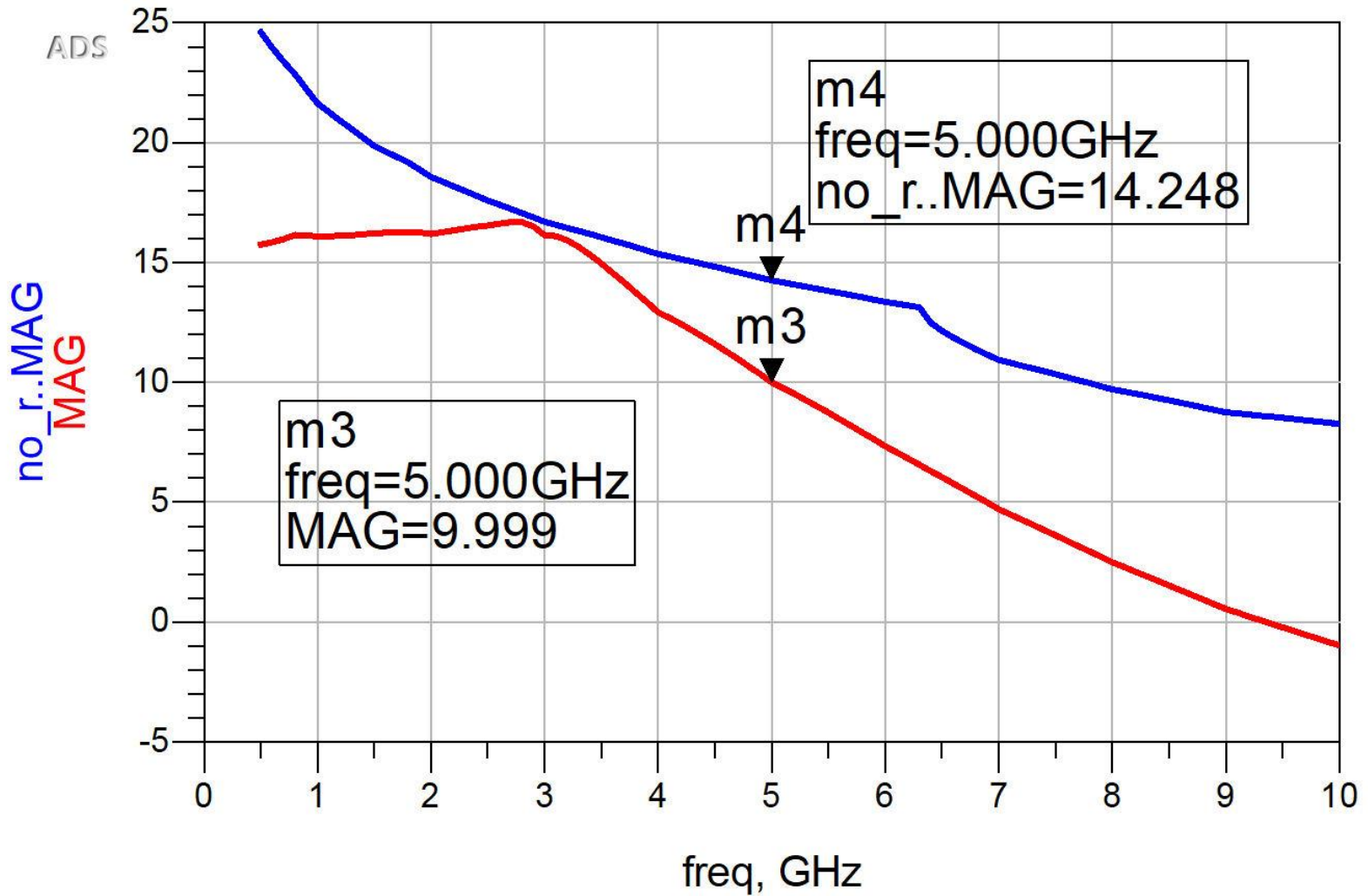


Continue

Microwave Amplifiers

Power Gain of Microwave Amplifiers


Amplifier as two-port

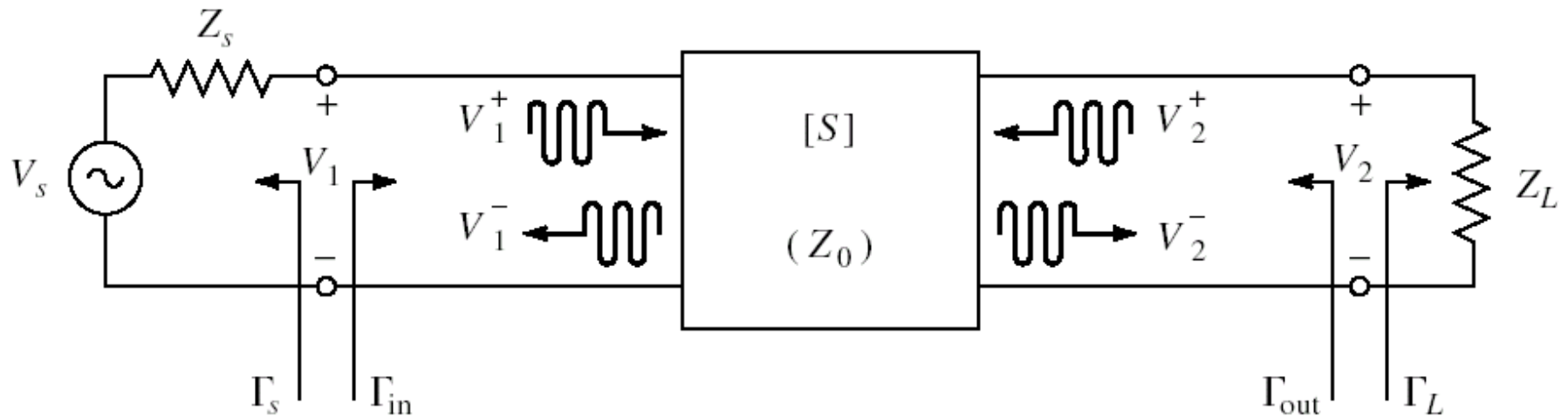


- For an amplifier two-port we are interested in:
 - stability
 - **power gain**
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)

Power / Matching

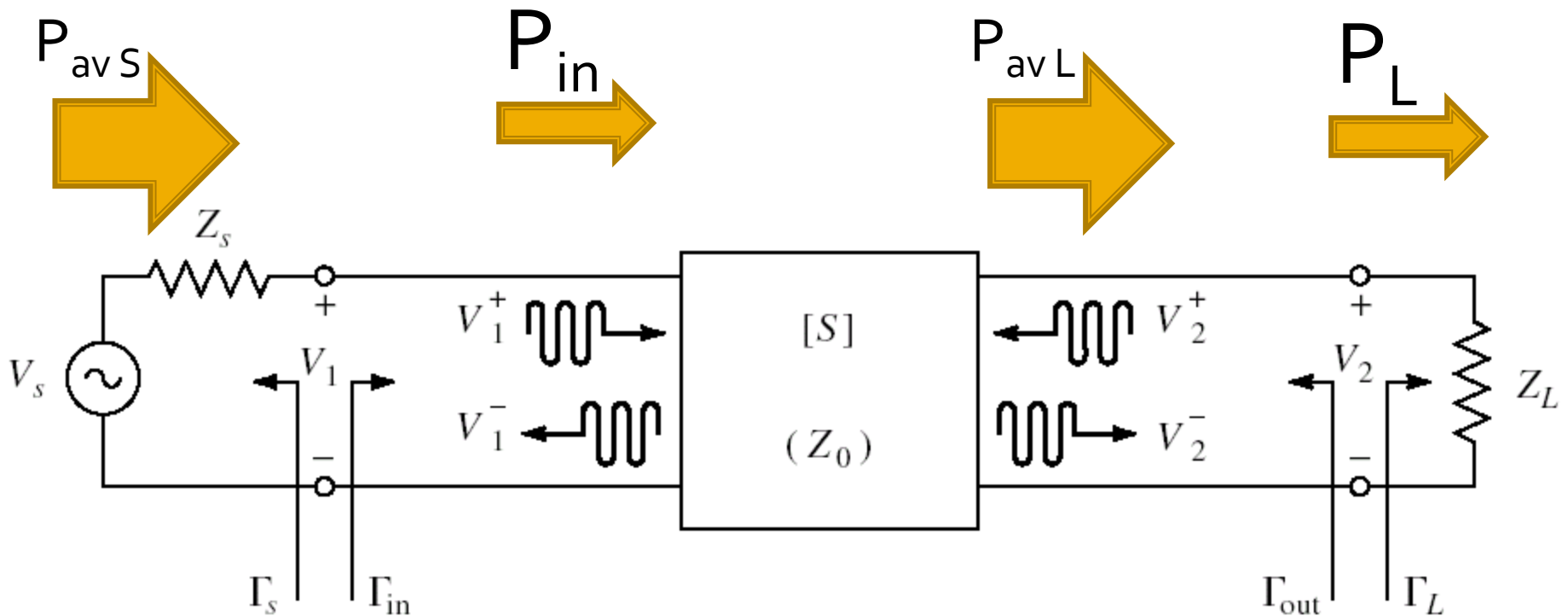- Two ports in which matching influences the power transfer



Design for Maximum Gain

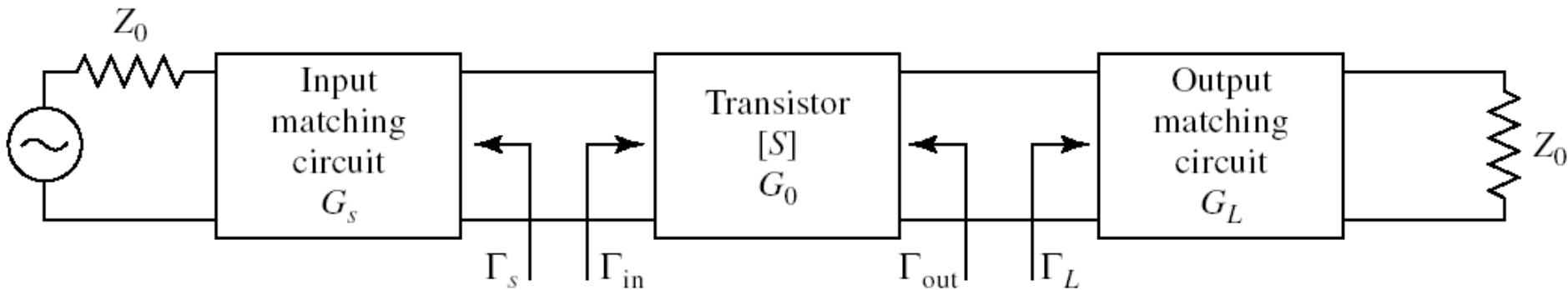

- Maximum power gain (complex conjugate matching):

$$\Gamma_{in} = \Gamma_S^* \quad \Gamma_{out} = \Gamma_L^*$$



- For lossless matching sections

$$G_{T \max} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2} \quad G_{T \max} = \frac{1}{1 - |\Gamma_S|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

- For the general case of the bilateral transistor ($S_{12} \neq 0$)

Γ_{in} and Γ_{out} depend on each other so the input and output sections must be matched simultaneously

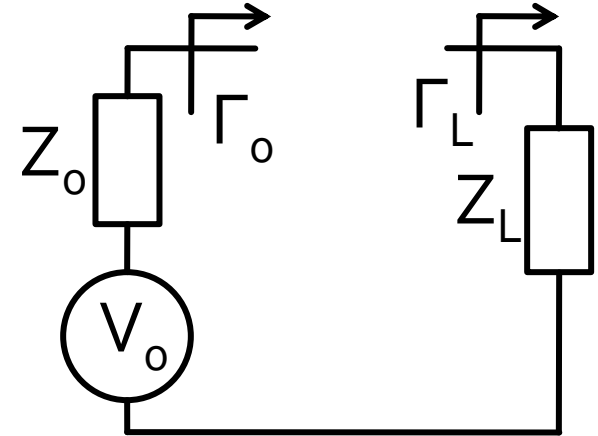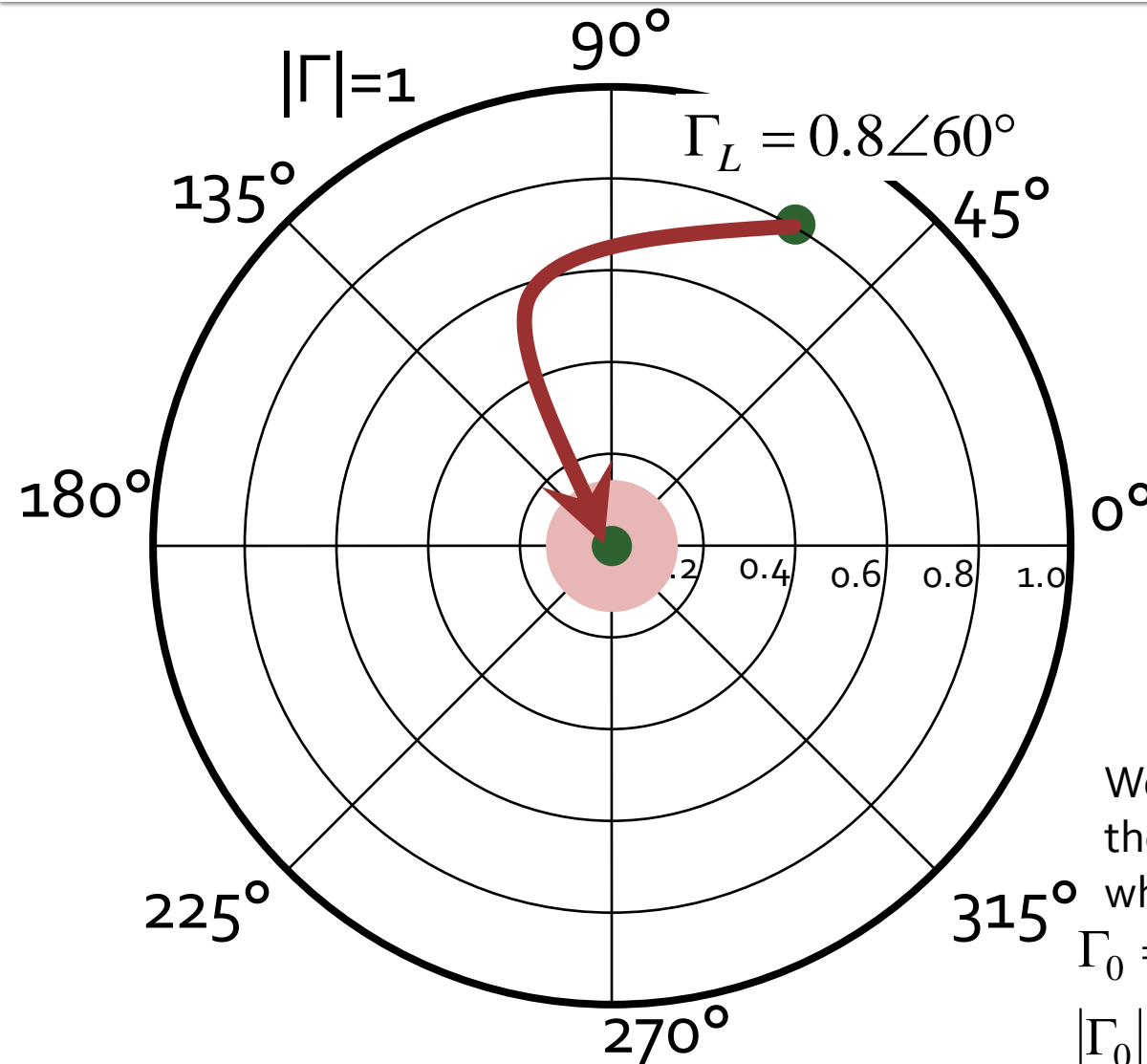The Smith Chart, matching, $Z_L \neq Z_o$



Matching Z_L load to Z_o source.
We normalize Z_L over Z_o

$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

$$z_L = 0.429 + j \cdot 1.65$$



$$\Gamma_L = 0.8 \angle 60^\circ$$

We must move the point denoting the reflection coefficient in the area where with a Z_o source we have:

$$\Gamma_0 = 0 \text{ perfect match } \bullet$$

$$|\Gamma_0| \leq \Gamma_m \text{ "good enough" match } \circ$$

The Smith Chart, matching, $Z_L = Z_o$

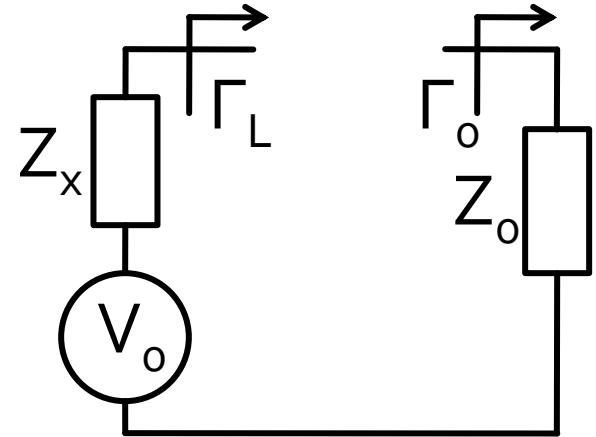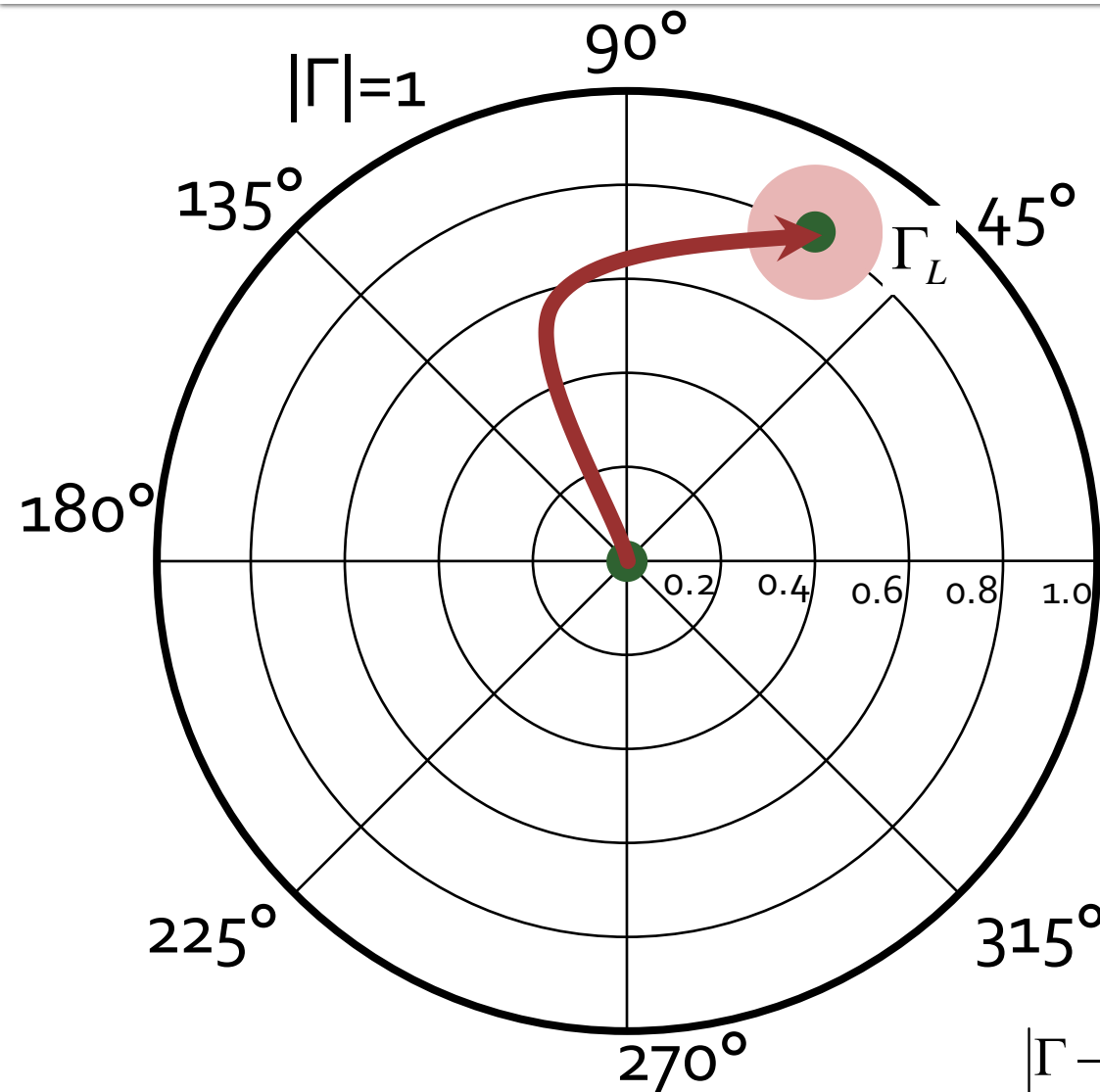

The source (eg. the transistor) having Z_x needs to see a certain reflection coefficient Γ_L towards the load Z_o


The matching circuit must move the point denoting the reflection coefficient in the area where for a Z_o load ($\Gamma_o=0$) we see towards it:

$\Gamma = \Gamma_L$ perfect match ●

$|\Gamma - \Gamma_L| \leq \Gamma_m$ "good enough" match ●

The Smith Chart, matching ,

$$Z_L \neq Z_o, Z_L = Z_o$$

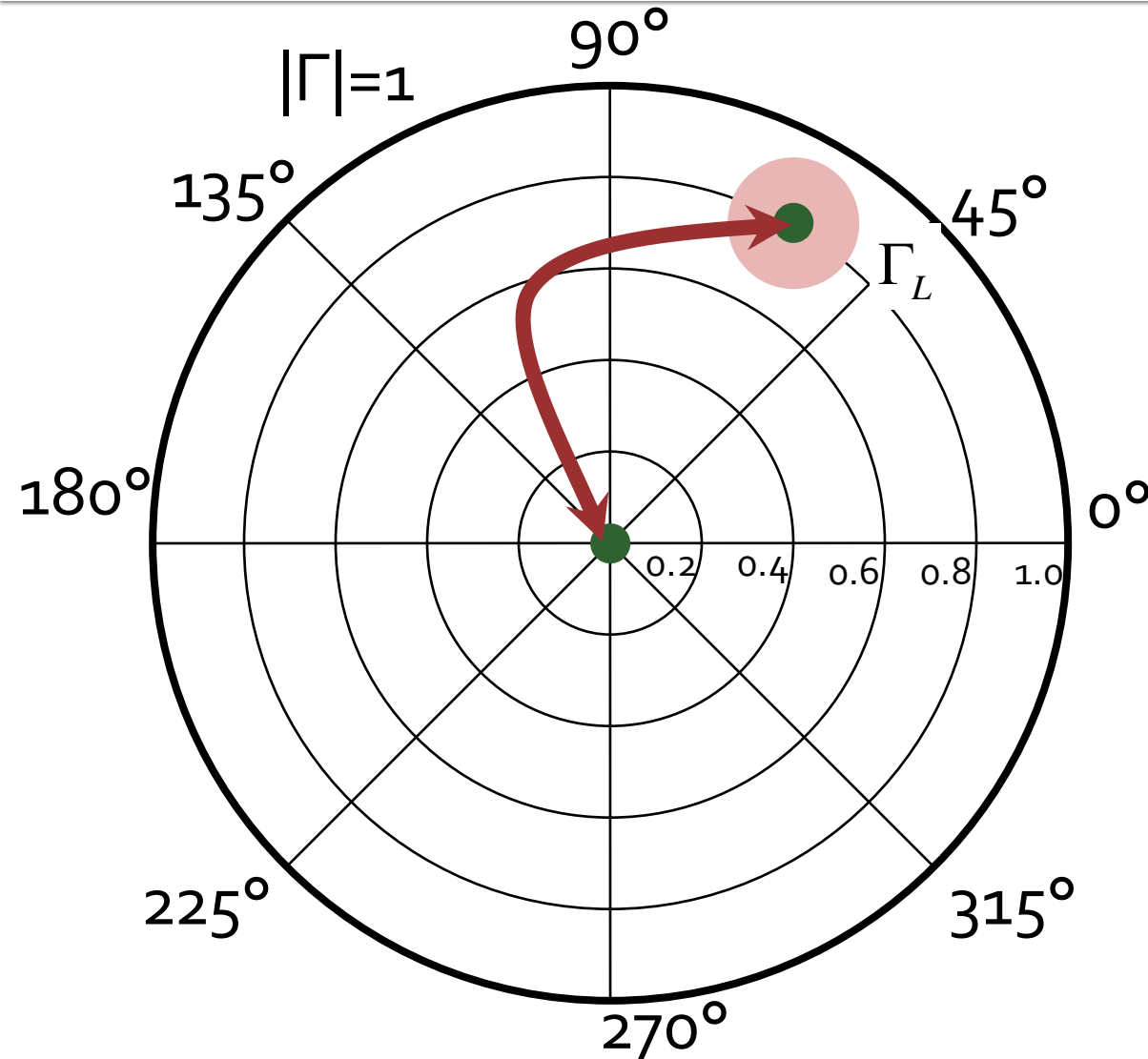

- The matching sections needed to move
 - Γ_L in Γ_o
 - Γ_o in Γ_L
- are **identical**. They differ only by the **order** in which the elements are introduced into the matching circuit
- As a result, we can use in match design the same:
 - **methods**
 - **formulae**

Simultaneous matching

$$\rightarrow \Gamma_{in} = \Gamma_S^*$$

$$\Gamma_{in} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_S^* = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\rightarrow \Gamma_{out} = \Gamma_L^*$$

$$\Gamma_{out} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

$$\Gamma_L^* = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

- We find Γ_S

$$\Gamma_S = S_{11}^* + \frac{S_{12}^* \cdot S_{21}^*}{1/\Gamma_L^* - S_{22}^*}$$

$$\Gamma_L^* = \frac{S_{22} - \Delta \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

$$\Gamma_S \cdot (1 - |S_{22}|^2) + \Gamma_S^2 \cdot (\Delta \cdot S_{22}^* - S_{11}) = \Gamma_S \cdot (\Delta \cdot S_{11}^* \cdot S_{22}^* - |S_{22}|^2 - \Delta \cdot S_{12}^* \cdot S_{21}^*) + S_{11}^* \cdot (1 - |S_{22}|^2) + S_{12}^* \cdot S_{21}^* \cdot S_{22}$$

Simultaneous matching

$$\Delta \cdot (S_{11}^* \cdot S_{22}^* - S_{12}^* \cdot S_{21}^*) = |\Delta|^2$$

$$\Gamma_S^2 \cdot \underbrace{(S_{11} - \Delta \cdot S_{22}^*)}_C + \Gamma_S \cdot \underbrace{(|\Delta|^2 - |S_{11}|^2 + |S_{22}|^2 - 1)}_{-B} + \underbrace{(S_{11}^* - \Delta^* \cdot S_{22})}_{C^*} = 0$$

- A quadratic equation

$$\Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

- Similarly

$$\Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

- With variables defined as:

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases} \quad \begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

Simultaneous matching

- Simultaneous matching is possible if:

$$B_1^2 - 4 \cdot |C_1|^2 > 0 \quad B_2^2 - 4 \cdot |C_2|^2 > 0$$

$$\Delta \cdot (S_{11}^* \cdot S_{22}^* - S_{12}^* \cdot S_{21}^*) = |\Delta|^2$$

$$|C_1|^2 = |S_{11} - \Delta \cdot S_{22}^*|^2 = |S_{12}|^2 \cdot |S_{21}|^2 + (1 - |S_{22}|^2) \cdot (|S_{11}|^2 - |\Delta|^2)$$

$$B_1^2 - 4 \cdot |C_1|^2 = (1 + |S_{11}|^2)^2 + (|S_{22}|^2 + |\Delta|^2)^2 - 2 \cdot (1 + |S_{11}|^2) \cdot (|S_{22}|^2 + |\Delta|^2) - 4 \cdot |S_{12} \cdot S_{21}|^2 - 4 \cdot (1 - |S_{22}|^2) \cdot (|S_{22}|^2 - |\Delta|^2)$$

$$B_1^2 - 4 \cdot |C_1|^2 = (1 + |S_{11}|^2)^2 + (|S_{22}|^2 + |\Delta|^2)^2 - 4 \cdot |S_{11}|^2 - 4 \cdot |S_{22}|^2 \cdot |\Delta|^2 - 2 \cdot (1 - |S_{11}|^2) \cdot (|S_{22}|^2 - |\Delta|^2) - 4 \cdot |S_{12} \cdot S_{21}|^2$$

Simultaneous matching

$$B_1^2 - 4 \cdot |C_1|^2 = \left(1 + |S_{11}|^2\right)^2 + \left(|S_{22}|^2 + |\Delta|^2\right)^2 - 4 \cdot |S_{11}|^2 - 4 \cdot |S_{22}|^2 \cdot |\Delta|^2 - 2 \cdot \left(1 - |S_{11}|^2\right) \cdot \left(|S_{22}|^2 - |\Delta|^2\right) - 4 \cdot |S_{12} \cdot S_{21}|^2$$

$$B_1^2 - 4 \cdot |C_1|^2 = \left(1 - |S_{11}|^2\right)^2 + \left(|S_{22}|^2 - |\Delta|^2\right)^2 - 2 \cdot \left(1 - |S_{11}|^2\right) \cdot \left(|S_{22}|^2 - |\Delta|^2\right) - 4 \cdot |S_{12} \cdot S_{21}|^2$$

$$B_1^2 - 4 \cdot |C_1|^2 = \left(1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2\right)^2 - 4 \cdot |S_{12} \cdot S_{21}|^2$$

$$B_1^2 - 4 \cdot |C_1|^2 = \left(K \cdot 2 \cdot |S_{12} \cdot S_{21}|\right)^2 - 4 \cdot |S_{12} \cdot S_{21}|^2$$

$$B_1^2 - 4 \cdot |C_1|^2 = 4 \cdot |S_{12}|^2 \cdot |S_{21}|^2 \cdot (K^2 - 1)$$

■ Similarly

$$B_2^2 - 4 \cdot |C_2|^2 = 4 \cdot |S_{12}|^2 \cdot |S_{21}|^2 \cdot (K^2 - 1)$$

Simultaneous matching

$$\Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1} \quad \Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

- Solutions must ensure stability:

$$|\Gamma_S| < 1 \quad |\Gamma_L| < 1$$

$$|\Delta| = |S_{11} \cdot S_{22} - S_{12} \cdot S_{21}| < 1$$

$$\begin{cases} B_1 > 0 \\ B_2 > 0 \end{cases}$$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 \cdot |S_{12} \cdot S_{21}|} > 1$$

$$\begin{cases} B_1^2 - 4 \cdot |C_1|^2 = 4 \cdot |S_{12}|^2 \cdot |S_{21}|^2 \cdot (K^2 - 1) > 0 \\ B_2^2 - 4 \cdot |C_2|^2 = 4 \cdot |S_{12}|^2 \cdot |S_{21}|^2 \cdot (K^2 - 1) > 0 \end{cases}$$

Simultaneous matching

- Simultaneous matching can be achieved **if and only if** the amplifier is **unconditionally stable** at the operating frequency, and $|\Gamma| < 1$ solutions are those with “-” sign of quadratic solutions

$$\Gamma_S = \frac{B_1 - \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases}$$

$$\Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

$$\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

Simultaneous matching

- In the case of the simultaneous matching the amplifier achieves the maximum transducer power gain for the bilateral transistor


$$G_{T \max} = \frac{|S_{21}|}{|S_{12}|} \cdot \left(K - \sqrt{K^2 - 1} \right)$$

- If the device is **not unconditionally stable** at a certain frequency we can use MSG (Maximum Stable Gain) as an indicator of the capability to obtain a power gain in stable conditions

$$G_{MSG} = \frac{|S_{21}|}{|S_{12}|}$$


Maximum Available Gain

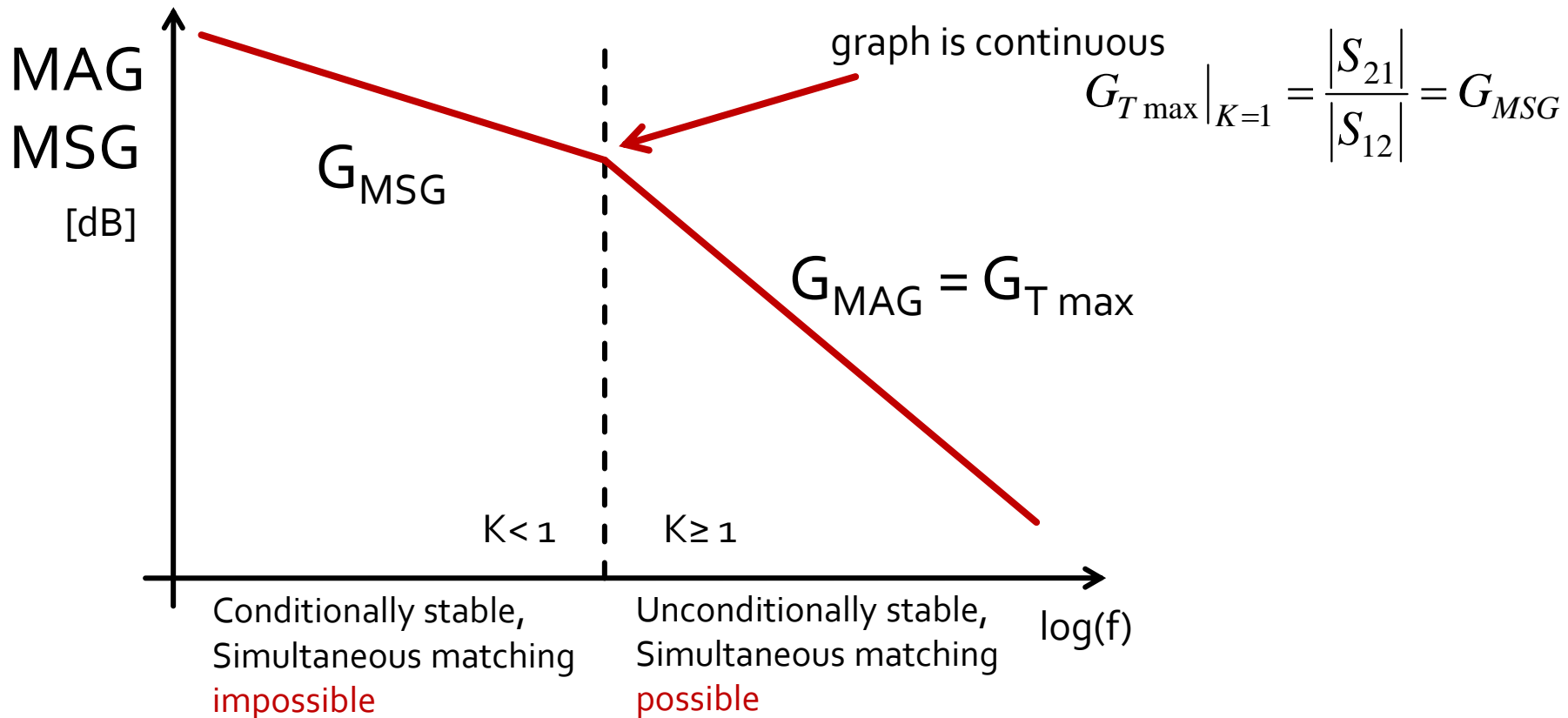- Indicator across full frequency range of the capability to obtain a power gain




Stability

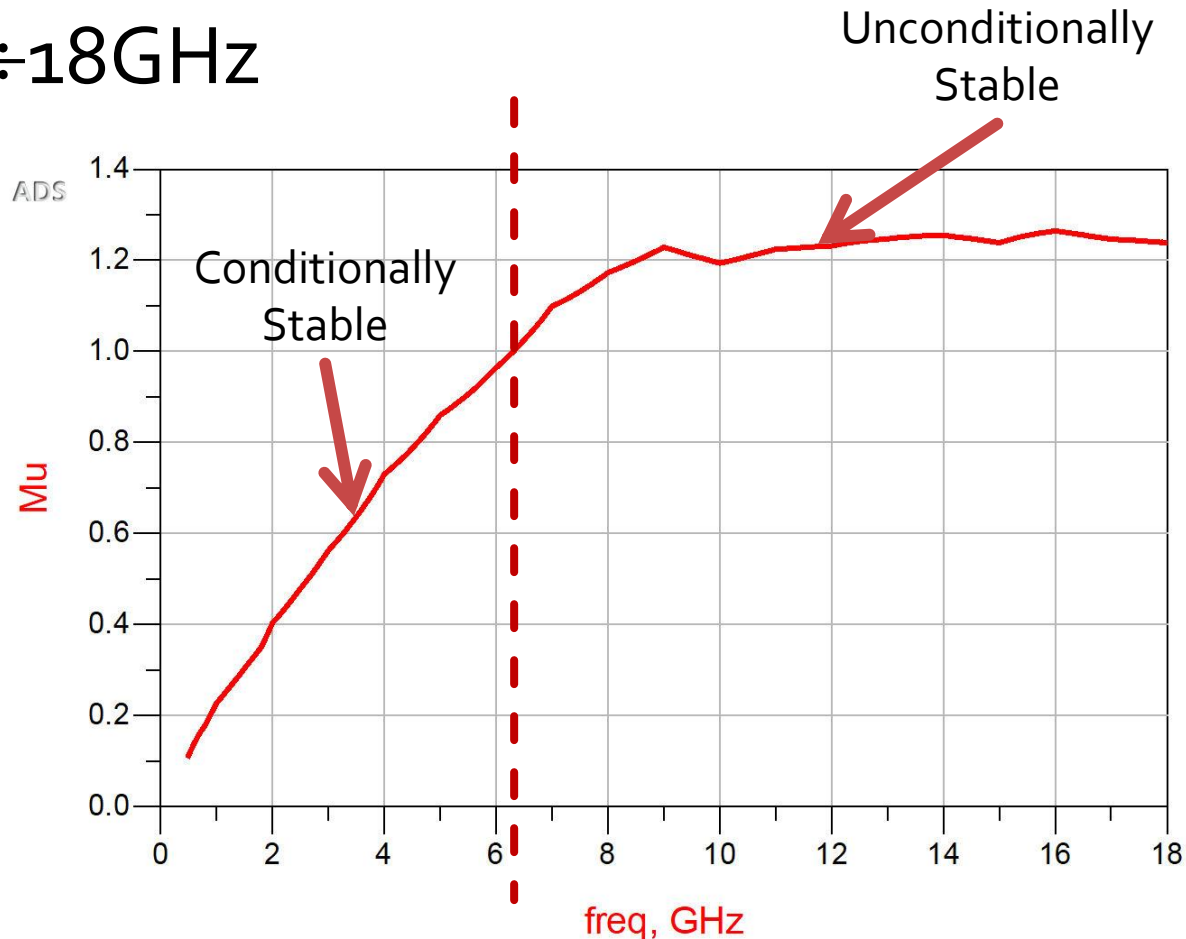- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz




MAG/MSG

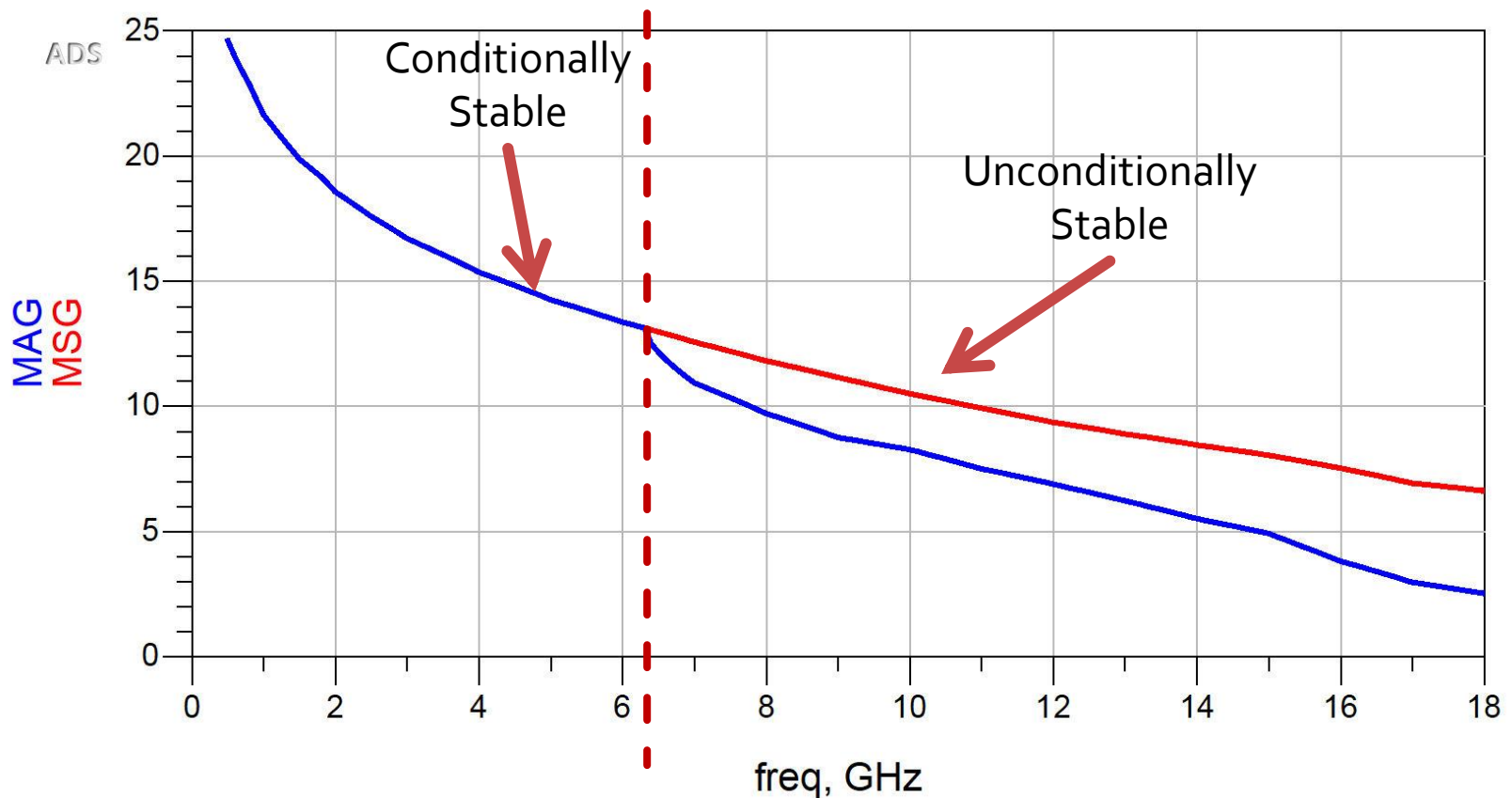- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz



Simultaneous matching, unilateral transistor

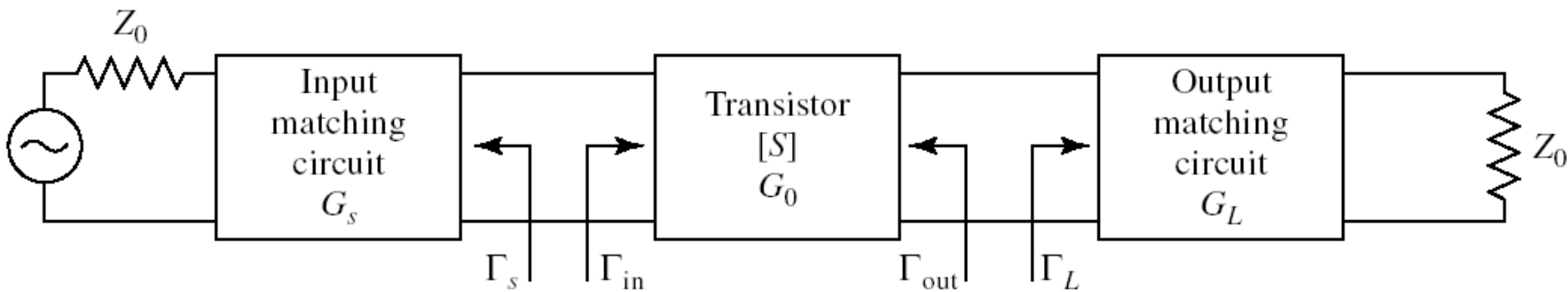- In the case of **unilateral** amplifier/transistor ($S_{12} = 0$) simultaneous matching implies:



$$\Gamma_{in} = S_{11}$$

$$\Gamma_{out} = S_{22}$$

$$\Gamma_S = S_{11}^*$$

$$\Gamma_L = S_{22}^*$$

$$G_{T \max} = \frac{1}{1 - |\Gamma_S|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$G_{TU \max} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2}$$

Example

- ATF-34143 **at $V_{ds}=3V$ $I_d=20mA$.**
 - without stabilization $K = 0.886$, $MAG = 14.248dB$ @ 5GHz
 - cannot be used with this bias conditions
- ATF-34143 **at $V_{ds}=4V$ $I_d=40mA$**
 - without stabilization $K = 1.031$, $MAG = 12.9dB$ @ 5GHz
 - we use this bias conditions for simultaneous matching

Example

- ATF-34143 at $V_{ds}=4V$ $I_d=40mA$.
- @5GHz
 - $S_{11} = 0.64 \angle 111^\circ$
 - $S_{12} = 0.117 \angle -27^\circ$
 - $S_{21} = 2.923 \angle -6^\circ$
 - $S_{22} = 0.21 \angle 111^\circ$

Computations

■ Complex S Parameters

- $S_{11} = -0.229 + 0.597 \cdot j$
 - $S_{12} = 0.104 - 0.053 \cdot j$
 - $S_{21} = 2.907 - 0.306 \cdot j$
 - $S_{22} = -0.075 + 0.196 \cdot j$
- $$\begin{cases} S_{11} = 0.64 \angle 111^\circ \\ S_{11} = 0.64 \cdot \cos 111^\circ + j \cdot 0.64 \cdot \sin 111^\circ \end{cases}$$

$$G_{T \max} = \frac{|S_{21}|}{|S_{12}|} \cdot \left(K - \sqrt{K^2 - 1} \right) = 19.497 = 12.9 \text{ dB}$$

$$G_{TU \max} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2} = 15.139 = 11.8 \text{ dB}$$

Computations

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases}$$

$$\begin{cases} B_1 = ? \\ C_1 = ? \end{cases}$$

$$\Gamma_S = \frac{B_1 - \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

$$\Gamma_S = ?$$

$$\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

$$\begin{cases} B_2 = ? \\ C_2 = ? \end{cases}$$

$$\Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

$$\Gamma_L = ?$$

Computations

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases}$$

$$\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

$$\begin{cases} B_1 = 1.207 \\ C_1 = -0.277 + j \cdot 0.529 \end{cases}$$

$$\begin{cases} B_2 = 0.476 \\ C_2 = -0.222 - j \cdot 0.013 \end{cases}$$

$$\Gamma_S = \frac{B_1 - \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

$$\Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

$$\Gamma_S = -0.403 - j \cdot 0.768$$

$$\Gamma_L = -0.685 + j \cdot 0.04$$


$$|\Gamma_S| = 0.867 < 1$$

$$|\Gamma_L| = 0.686 < 1$$

$$\Gamma_S = 0.867 \angle -117.7^\circ$$

$$\Gamma_L = 0.686 \angle 176.7^\circ$$

Shunt stub matching, L8

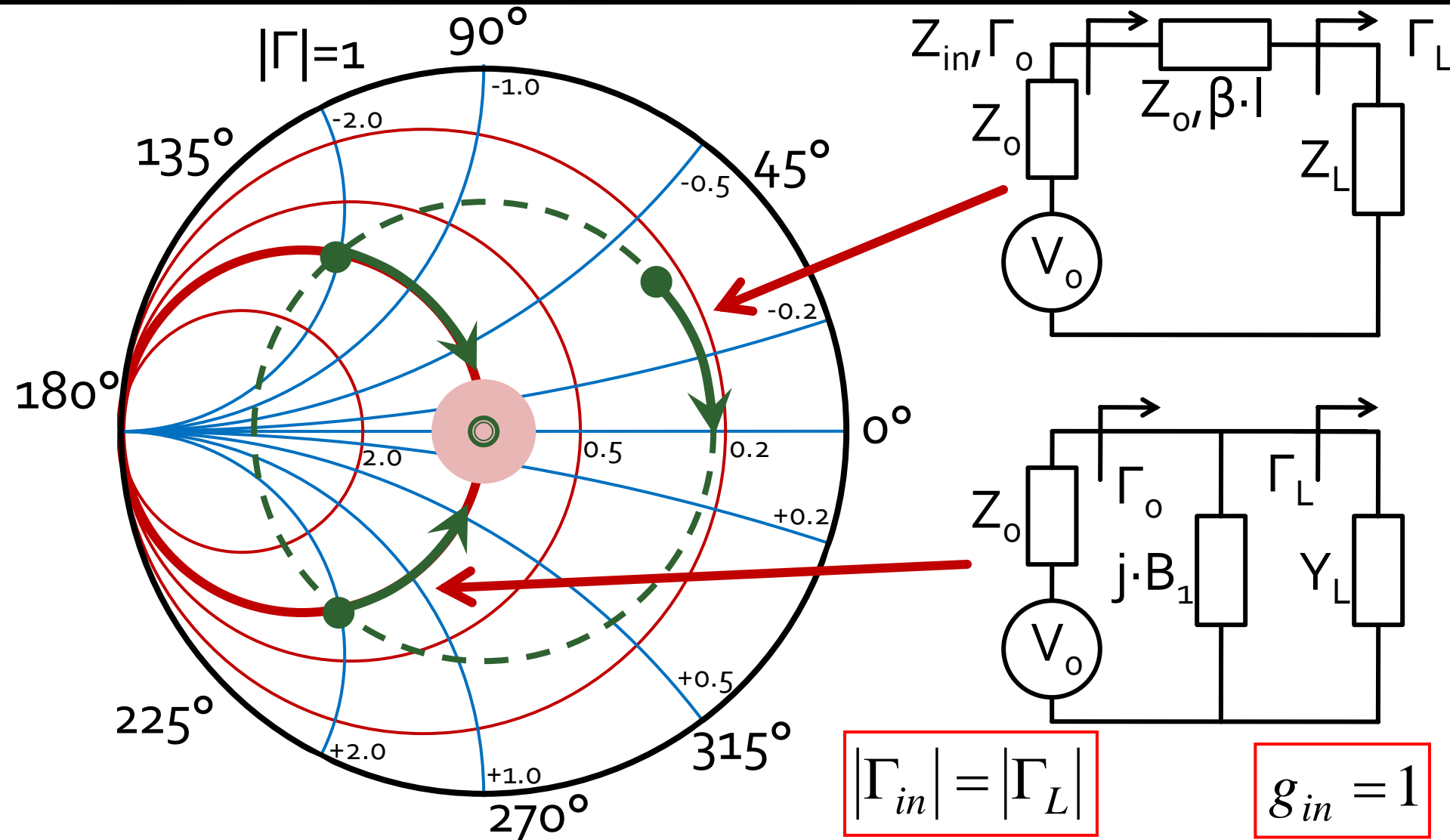

Analytical solution (Γ_S)

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = 0.867 \angle -117.7^\circ$$

$$|\Gamma_S| = 0.867; \quad \varphi = -117.7^\circ \quad \cos(\varphi + 2\theta) = -0.867 \Rightarrow (\varphi + 2\theta) = \pm 150.1^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **“+” solution**

$$(-117.7^\circ + 2\theta) = +150.1^\circ \quad \theta = 133.9^\circ \quad \text{Im } y_s = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -3.477$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_s) = -74^\circ (+180^\circ) \rightarrow \theta_{sp} = 106^\circ$$

- **“-” solution**

$$(-117.7^\circ + 2\theta) = -150.1^\circ \quad \theta = -16.2^\circ (+180^\circ) \rightarrow \theta = 163.8^\circ$$

$$\text{Im } y_s = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +3.477 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_s) = 74^\circ$$

Analytical solution (Γ_L)

$$\cos(\varphi + 2\theta) = -|\Gamma_L|$$

$$\Gamma_L = 0.686 \angle 176.7^\circ$$

$$|\Gamma_L| = 0.686; \quad \varphi = 176.7^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}}$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation
 - **“+” solution**
 - **“-” solution**

Analytical solution (Γ_L)

$$\cos(\varphi + 2\theta) = -|\Gamma_L|$$

$$\Gamma_L = 0.686 \angle 176.7^\circ$$

$$|\Gamma_L| = 0.686; \quad \varphi = 176.7^\circ \quad \cos(\varphi + 2\theta) = -0.686 \Rightarrow (\varphi + 2\theta) = \pm 133.3^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}}$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- "+" solution 

$$(176.7^\circ + 2\theta) = +133.3^\circ \quad \theta = -21.7^\circ (+180^\circ) \rightarrow \theta = 158.3^\circ$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_L) = -62.1^\circ (+180^\circ) \rightarrow \theta_{sp} = 117.9^\circ \quad \text{Im } y_L = \frac{-2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}} = -1.885$$

- "-" solution 

$$(176.7^\circ + 2\theta) = -133.3^\circ \quad \theta = -155^\circ (+180^\circ) \rightarrow \theta = 25^\circ$$

$$\text{Im } y_L = \frac{+2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}} = +1.885 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_L) = 62.1^\circ$$

Complete analytical solution

- We choose **one** of the two possible solutions for the input matching


$$(\varphi + 2\theta) = \begin{cases} +150.1^\circ \\ -150.1^\circ \end{cases} \quad \theta = \begin{cases} 133.9^\circ \\ 163.8^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -3.477 \\ +3.477 \end{cases} \quad \theta_{sp} = \begin{cases} -74^\circ + 180^\circ = 106^\circ \\ +74^\circ \end{cases}$$

- Similarly for the output matching

$$(\varphi + 2\theta) = \begin{cases} +133.3^\circ \\ -133.3^\circ \end{cases} \quad \theta = \begin{cases} 158.3^\circ \\ 25.0^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -1.885 \\ +1.885 \end{cases} \quad \theta_{sp} = \begin{cases} 117.9^\circ \\ 62.1^\circ \end{cases}$$


- In total there are **4** possible solutions input/output

ADS

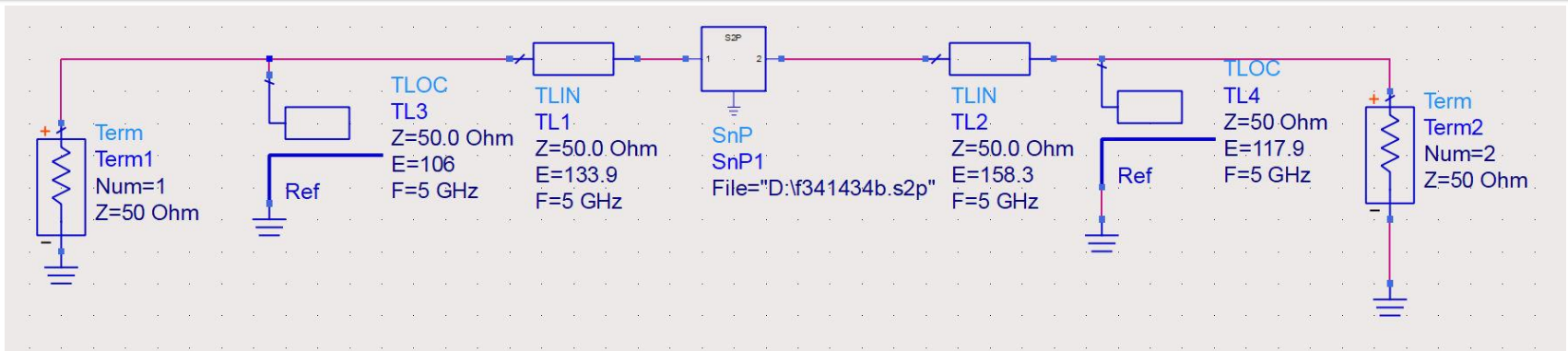



$$\text{Eqn GT} = 10 * \log(\text{mag}(S(2,1))^{**2})$$

freq	S(2,1)	GT	S(1,1)	S(2,2)
5.000 GHz	4.415 / 157.353	12.900	0.004 / 86.088	0.004 / 37.766

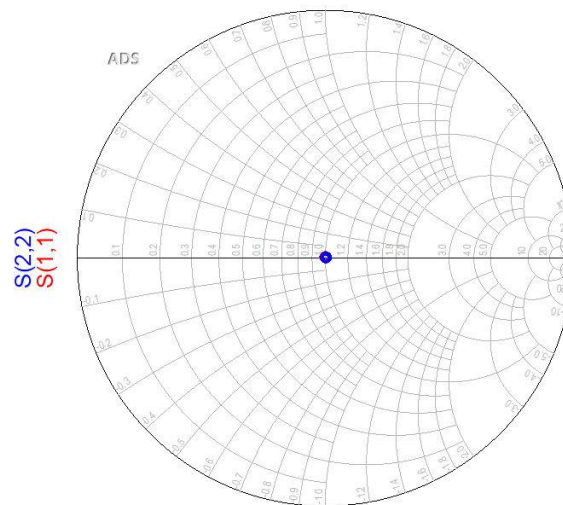

freq (5.000GHz to 5.000GHz)


ADS

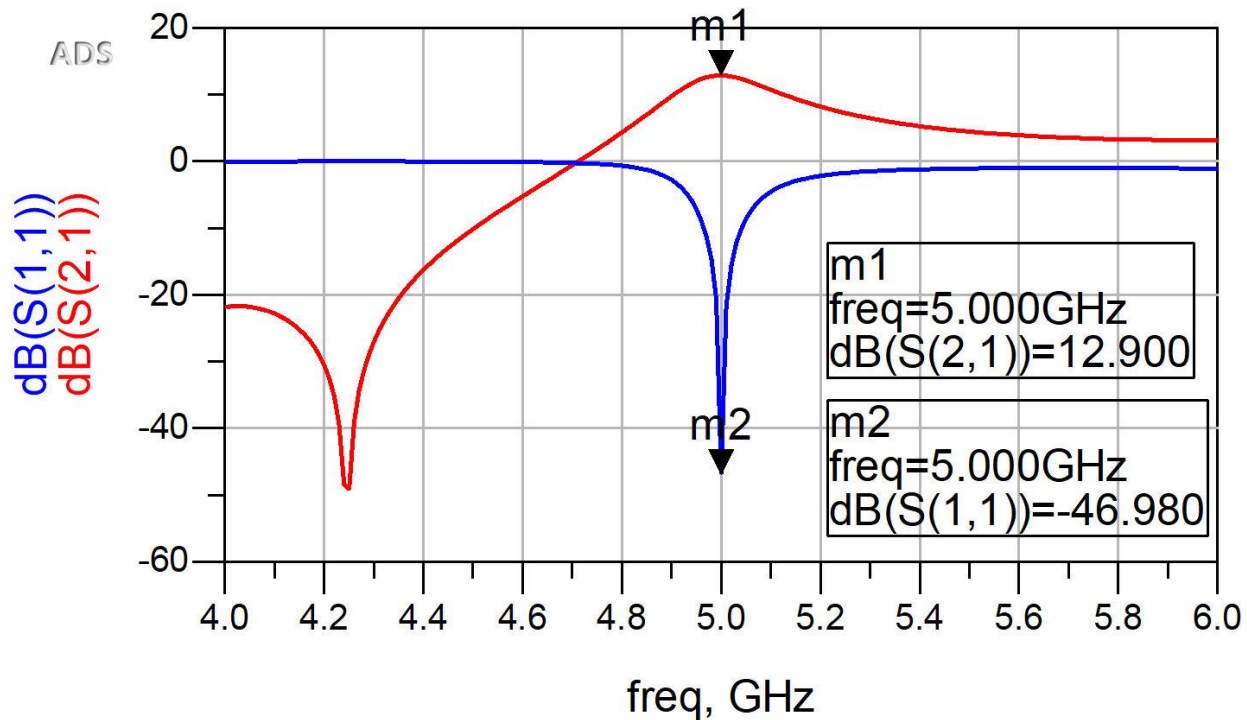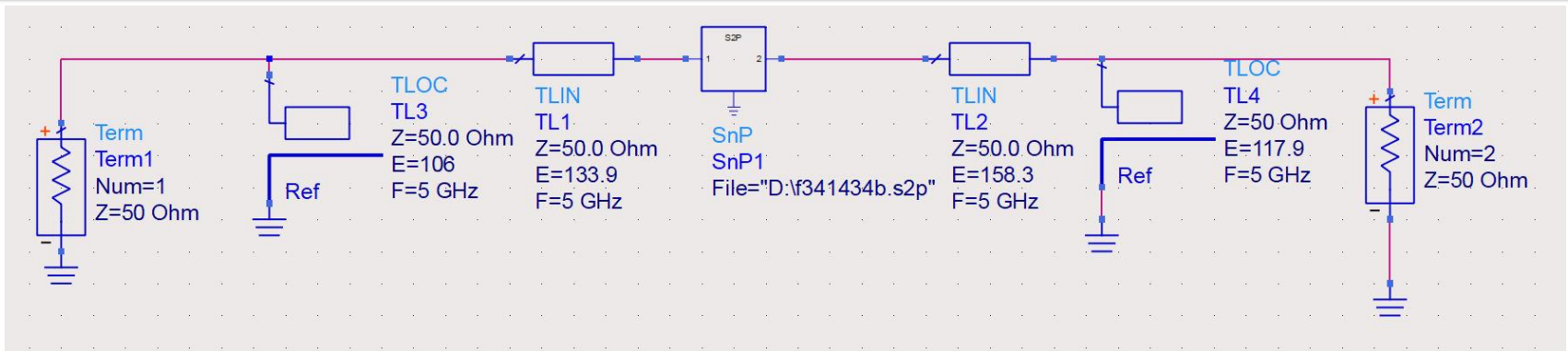

Microwave Amplifiers

Design for Specified Gain

Amplifier as two-port

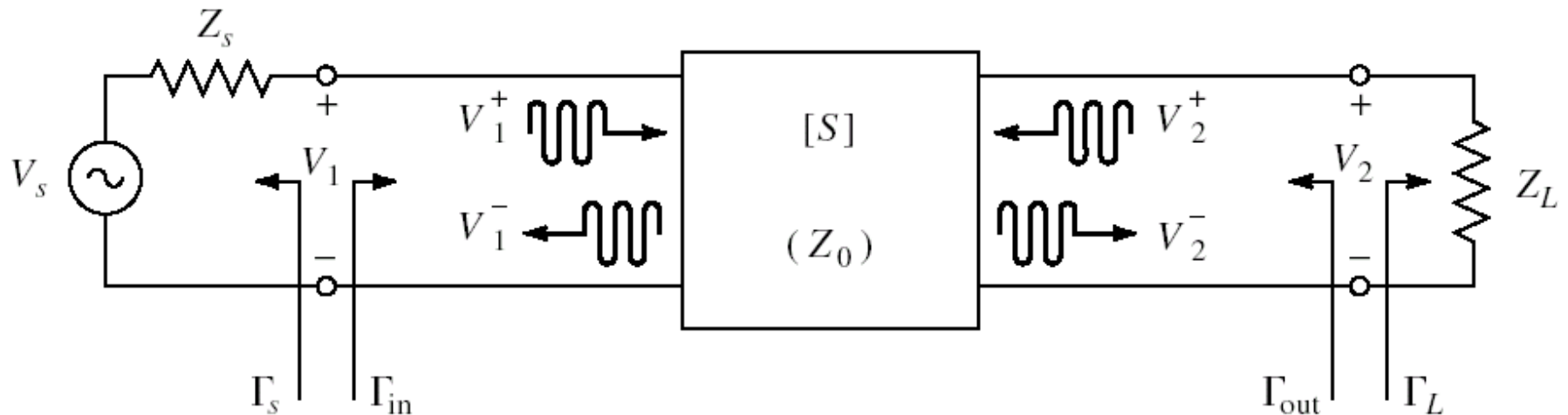

- For an amplifier two-port we are interested in:
 - stability
 - **power gain**
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)


Design for Specified Gain

- In many cases we need an approach other than “brute force” when we prefer to design for **less than the maximum obtainable gain**, in order to:
 - improve noise behavior (Lab 3 + Lect. 10 next)
 - improve stability
 - improve VSWR
 - control performance at multiple frequencies
 - improve amplifier’s bandwidth

Constant VSWR circles

- Certain applications may require a certain ratio between maximum / minimum line voltage
- $VSWR = \text{const} \rightarrow \Gamma = \text{const}$



$$VSWR = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

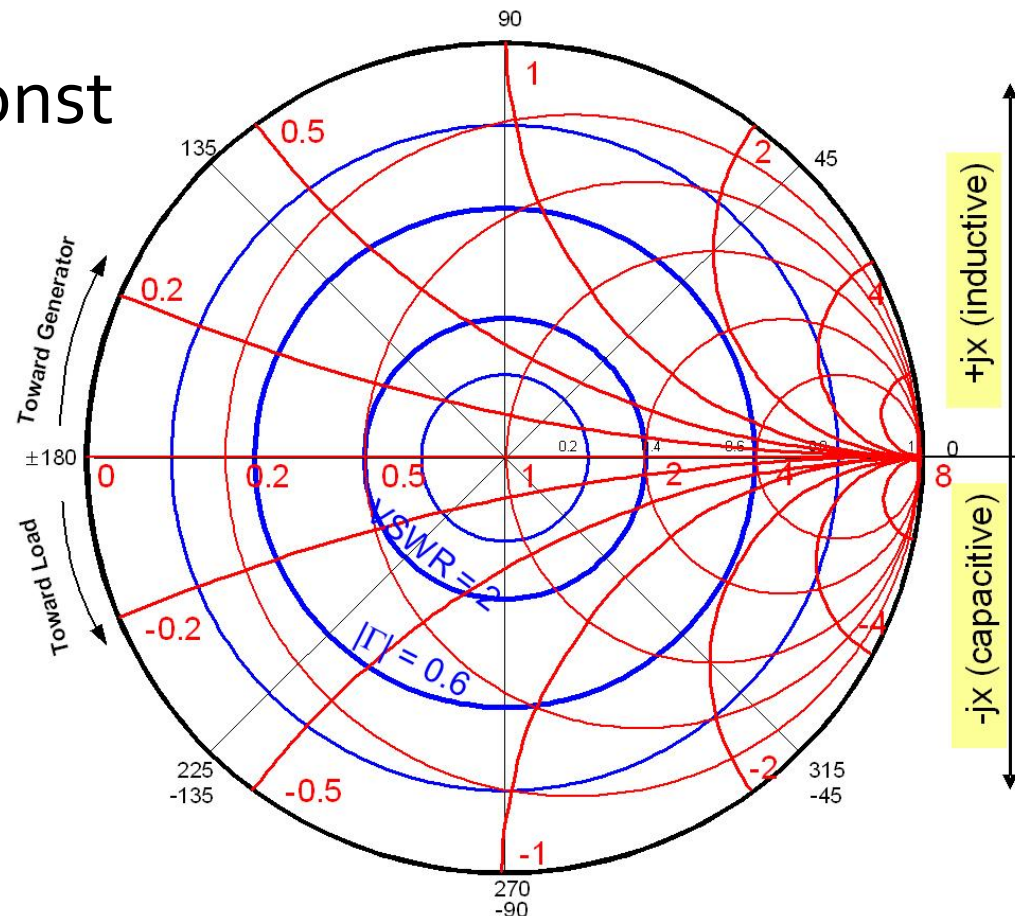

Constant Q circles


- Quality factor Q
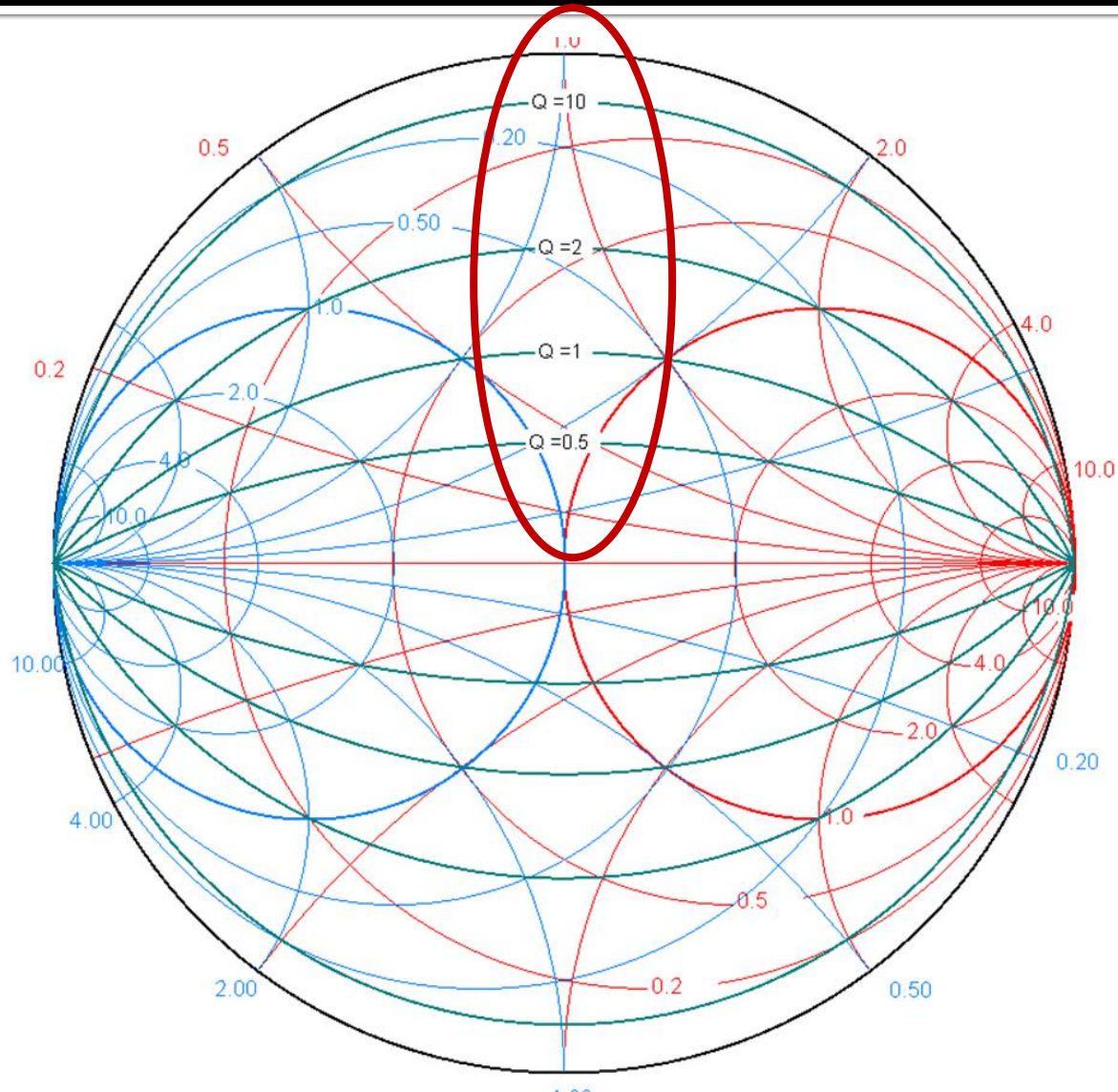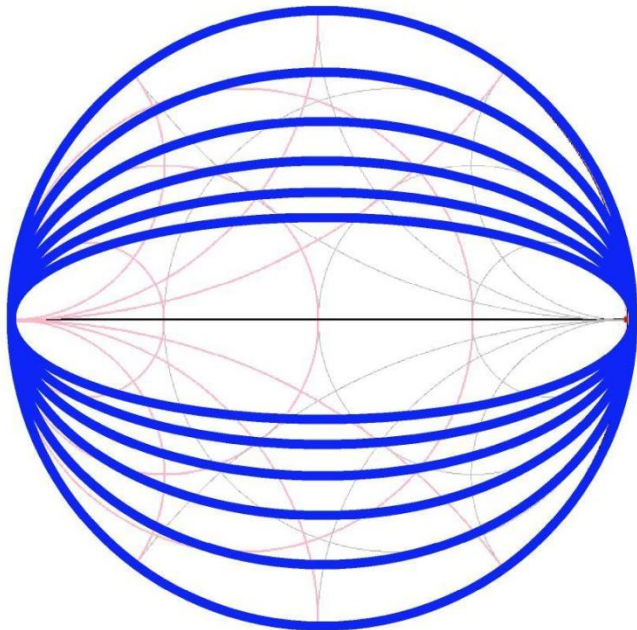
$$Q = \frac{X}{R} = \frac{G}{B} = \text{const}$$




Quality factor - bandwidth

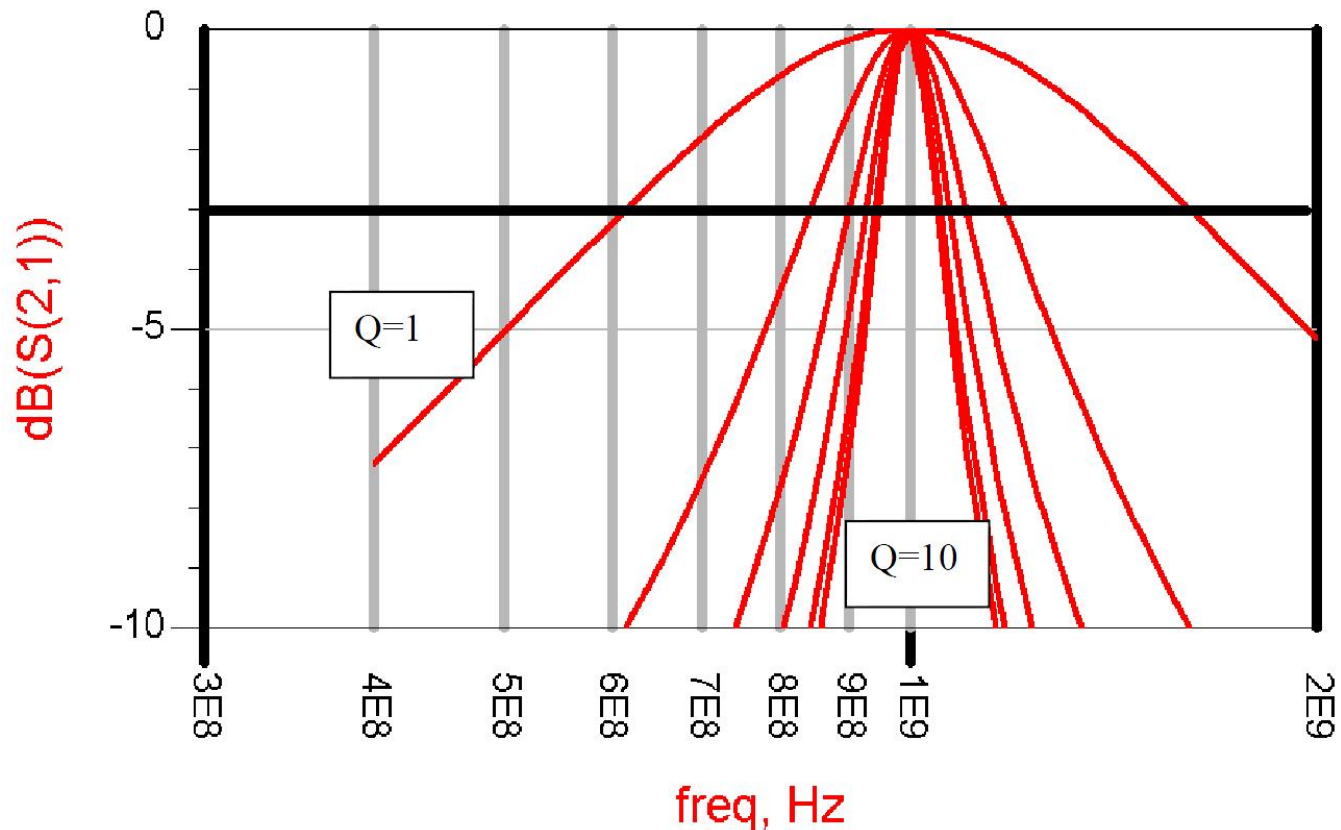- High quality factor is equivalent with narrow bandwidth




Wide bandwidth amplifier

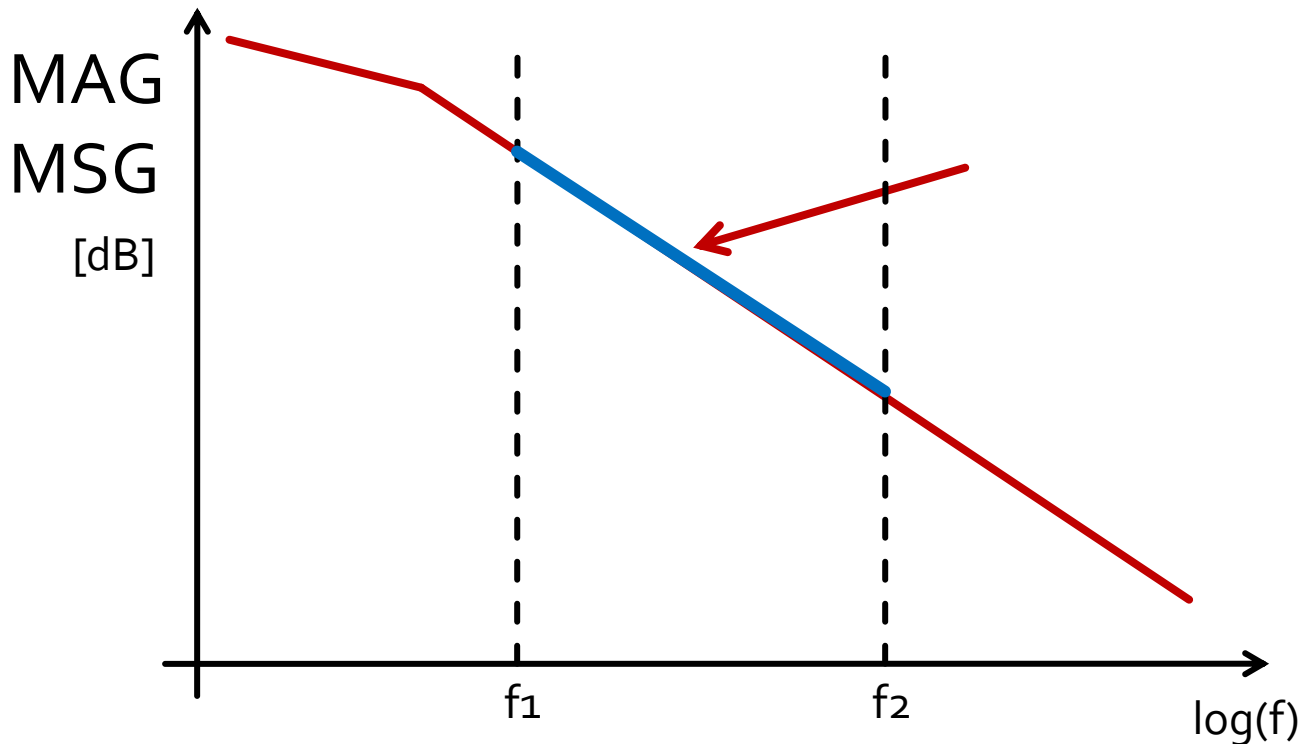- Design for maximum gain at two different frequencies creates an frequency unbalanced amplifier



Wide bandwidth amplifier

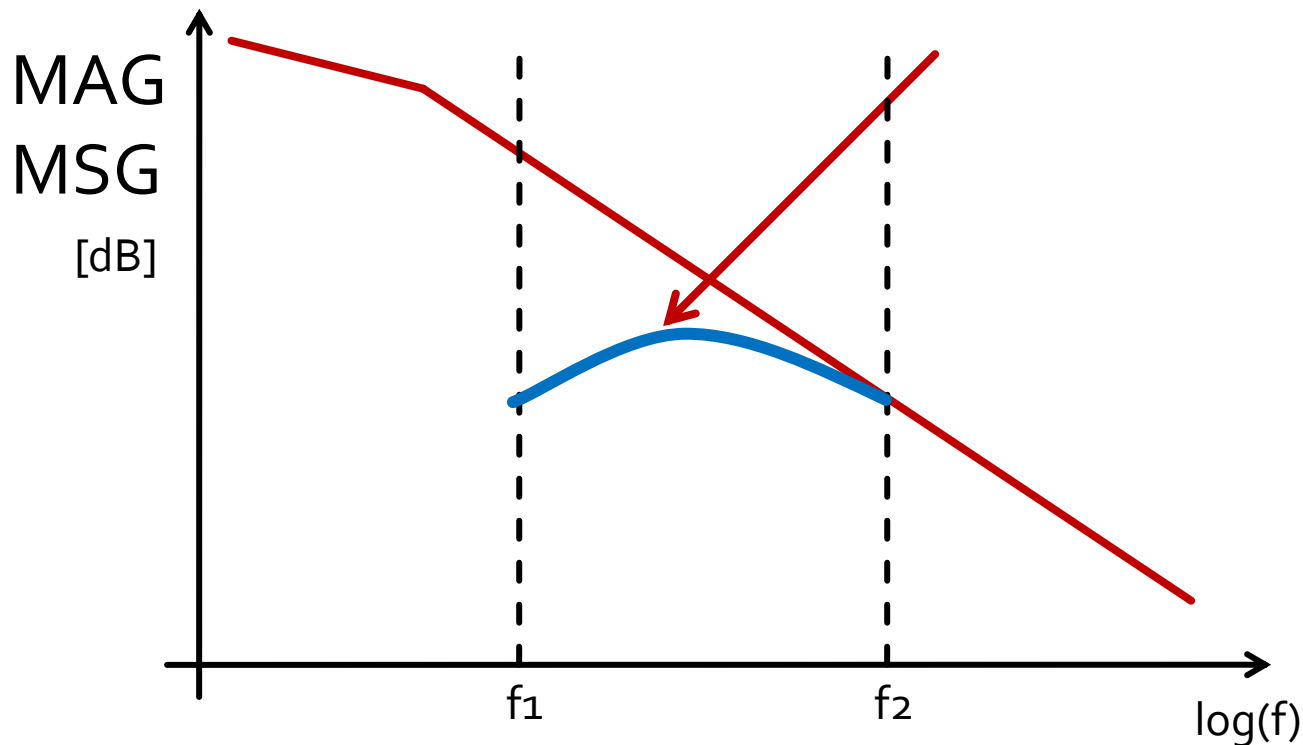- Design for maximum gain at highest frequency
- Controlled mismatch at lower frequency
 - eventually at more frequencies inside the bandwidth



Design for Specified Gain

- Assumes the amplifier device **unilateral**

Input and output can be treated independently

$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$S_{12} \cong 0$$

$$\Gamma_{in} = S_{11}$$

- Maximum power gain

$$\Gamma_S = S_{11}^*$$

$$\Gamma_L = S_{22}^*$$

$$G_{TU \max} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2}$$

Unilateral figure of merit

- Allows estimation of the error introduced by the unilateral assumption

$$\frac{1}{(1+U)^2} < \frac{G_T}{G_{TU}} < \frac{1}{(1-U)^2} \quad U = \frac{|S_{12}| \cdot |S_{21}| \cdot |S_{11}| \cdot |S_{22}|}{(1-|S_{11}|^2) \cdot (1-|S_{22}|^2)}$$

- We compute U then the maximum and minimum deviation of G_{TU} from G_T
 - this deviation must be accounted in the design as a reserve gain against the target gain

$$-20 \cdot \log(1+U) < G_T [dB] - G_{TU} [dB] < -20 \cdot \log(1-U)$$

Example

- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @5GHz


- $S_{11} = 0.64 \angle 139^\circ$
- $S_{12} = 0.119 \angle -21^\circ$
- $S_{21} = 3.165 \angle 16^\circ$
- $S_{22} = 0.22 \angle 146^\circ$

$$U = \frac{|S_{12}| \cdot |S_{21}| \cdot |S_{11}| \cdot |S_{22}|}{(1 - |S_{11}|^2) \cdot (1 - |S_{22}|^2)} = 0.094$$

$$-0.783 \text{ dB} < G_T [\text{dB}] - G_{TU} [\text{dB}] < 0.861 \text{ dB}$$

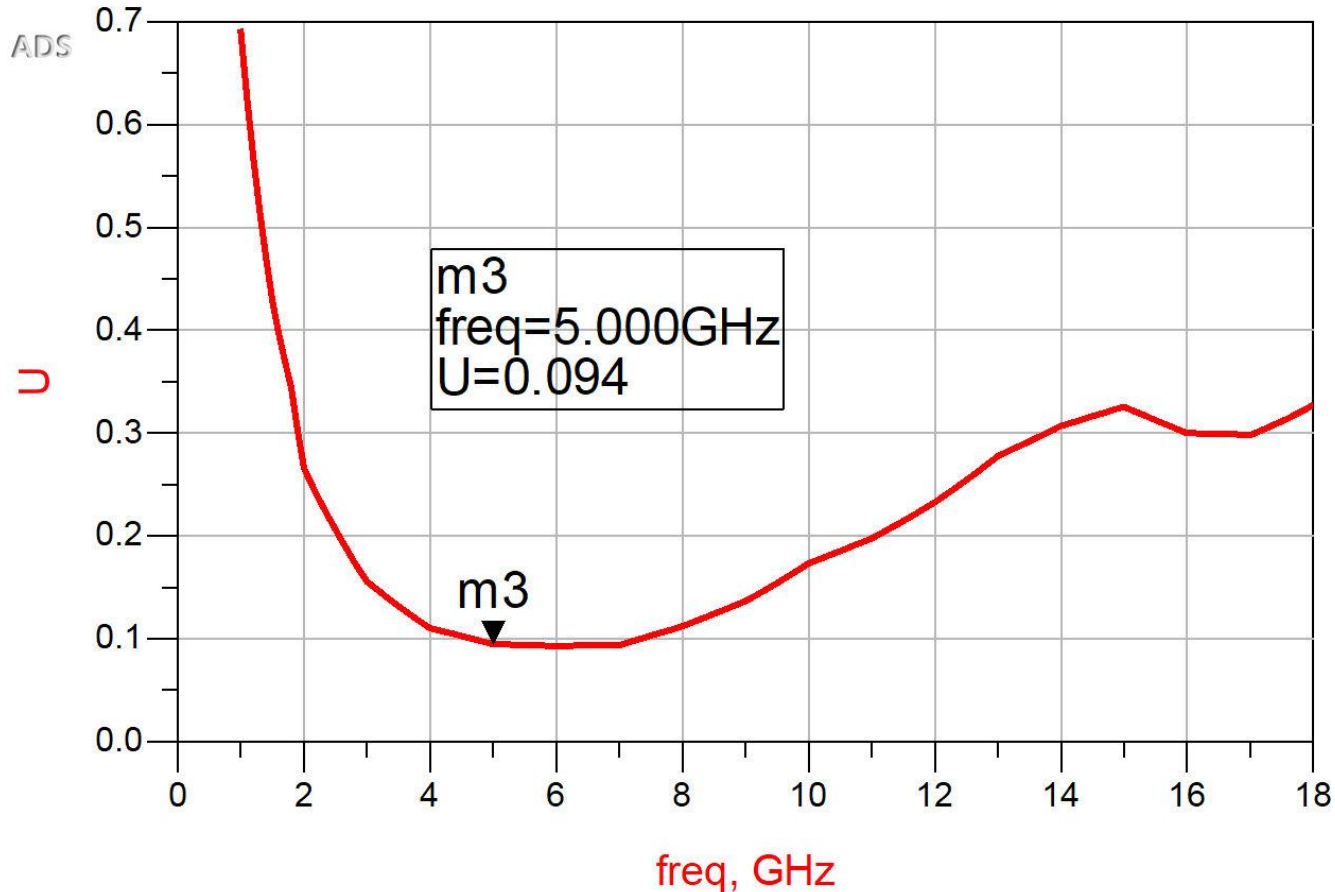
Example

- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @5GHz




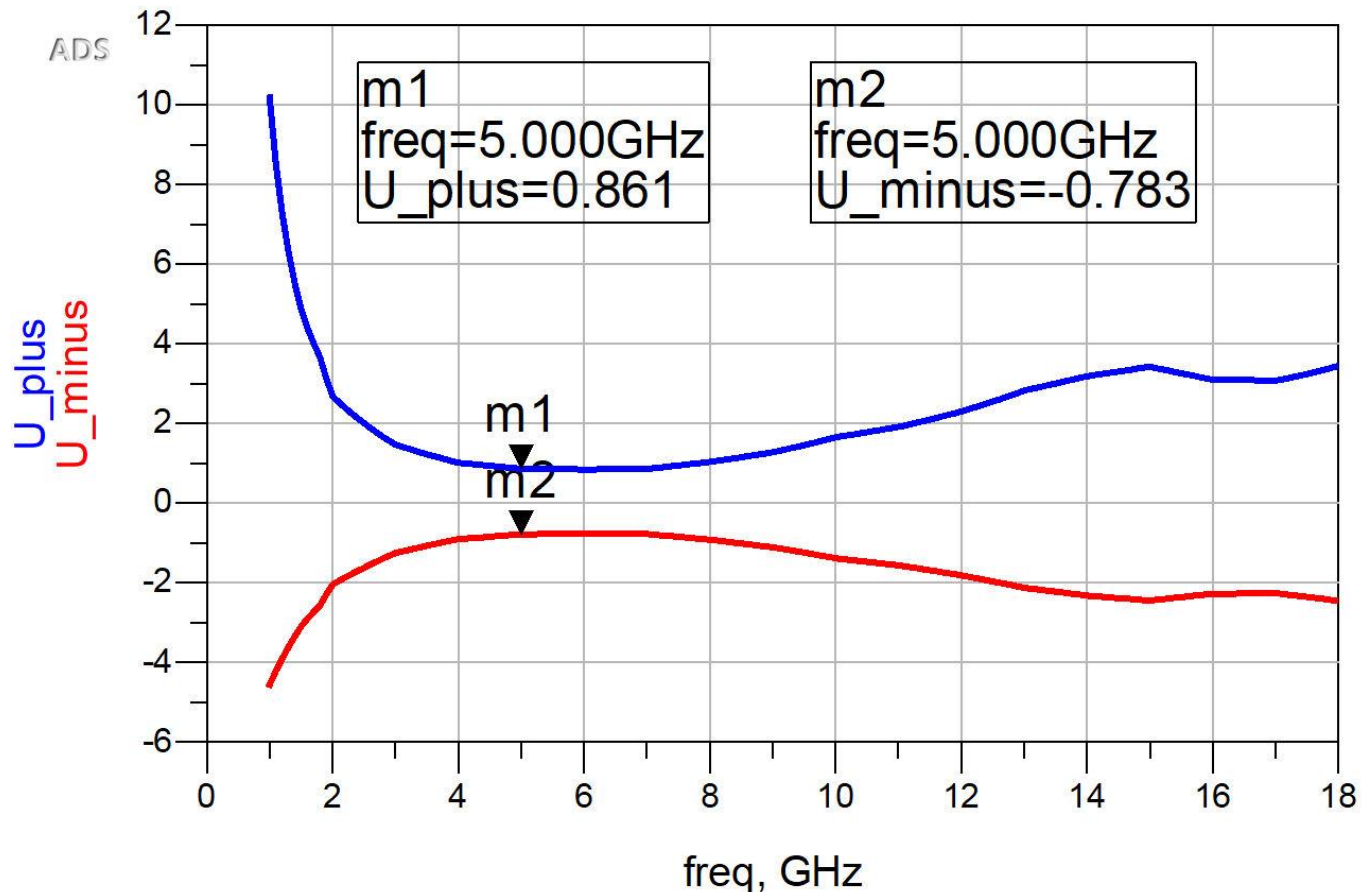Example

- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @5GHz, maximum and minimum deviation [dB]



Design for Specified Gain

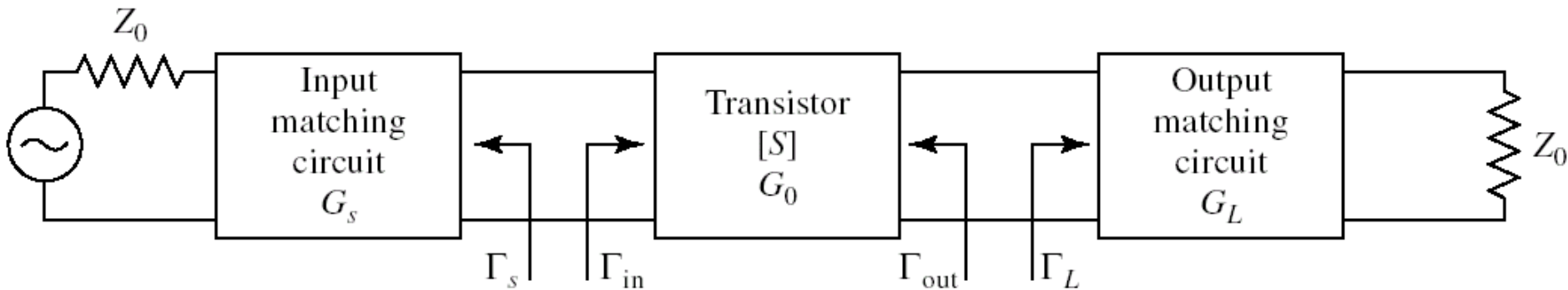

- In the unilateral assumption:

$$G_{TU} = \frac{1 - |\Gamma_s|^2}{|1 - S_{11} \cdot \Gamma_s|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$G_s = \frac{1 - |\Gamma_s|^2}{|1 - S_{11} \cdot \Gamma_s|^2}$$


$$G_s = G_s(\Gamma_s)$$

$$G_0 = |S_{21}|^2$$

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$G_L = G_L(\Gamma_L)$$

Design for Specified Gain

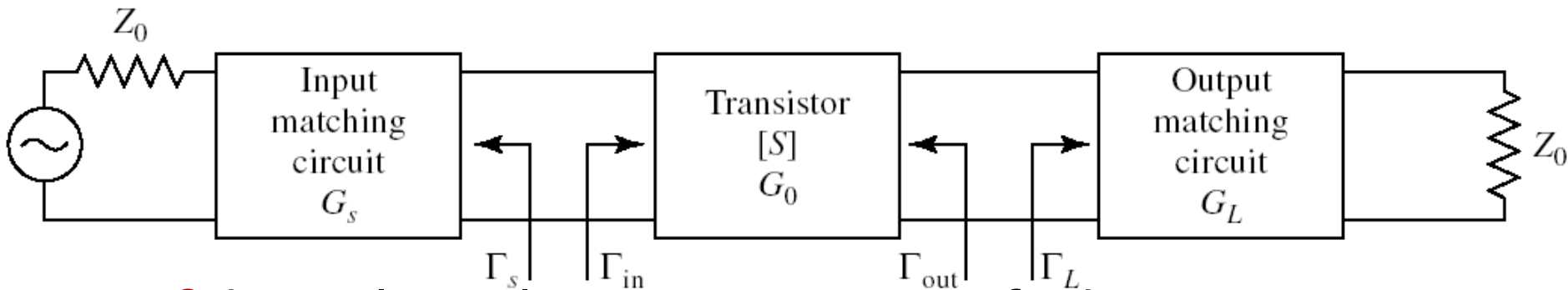


- **If** the unilateral assumption is justified :
 - power gain added by the input matching circuit **is not** influenced by the output matching circuit $G_S = G_S(\Gamma_S)$
 - power gain added by the output matching circuit **is not** influenced by the input matching circuit $G_L = G_L(\Gamma_L)$
- Output /Input match can be designed **independently**
 - We can impose different demands for input/output
 - Total gain is:

$$G_T = G_S \cdot G_0 \cdot G_L$$

$$G_T [dB] = G_S [dB] + G_0 [dB] + G_L [dB]$$

Input matching circuit

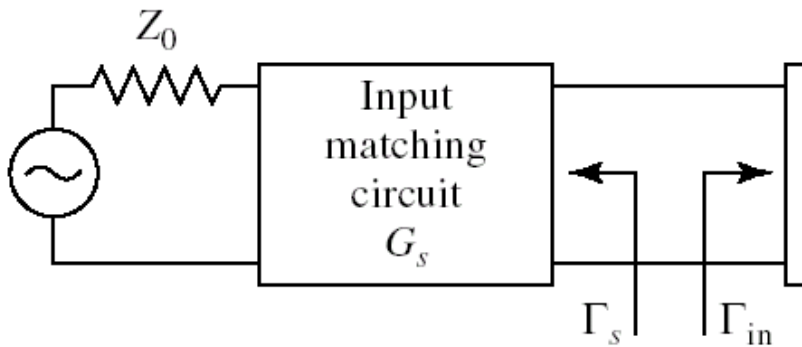

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2}$$

- Maximum gain in the case of complex conjugate match

$$\Gamma_S = S_{11}^* \Rightarrow G_{S \max} = \frac{1}{1 - |S_{11}|^2}$$

- For any other input matching circuit:

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} < G_{S \max} = \frac{1}{1 - |S_{11}|^2}$$

Example

- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @5GHz

- $S_{11} = 0.64 \angle 139^\circ$
- $S_{12} = 0.119 \angle -21^\circ$
- $S_{21} = 3.165 \angle 16^\circ$
- $S_{22} = 0.22 \angle 146^\circ$

$$U = \frac{|S_{12}| \cdot |S_{21}| \cdot |S_{11}| \cdot |S_{22}|}{(1 - |S_{11}|^2) \cdot (1 - |S_{22}|^2)} = 0.094$$


$$-0.783 \text{ dB} < G_T [\text{dB}] - G_{TU} [\text{dB}] < 0.861 \text{ dB}$$

$$G_{TU \text{ max}} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2} = 17.83$$

$$G_{TU \text{ max}} [\text{dB}] = 12.511 \text{ dB}$$


$$G_{S \text{ max}} = \frac{1}{1 - |S_{11}|^2} = 1.694 = 2.289 \text{ dB}$$

$G_S(\Gamma_S)$

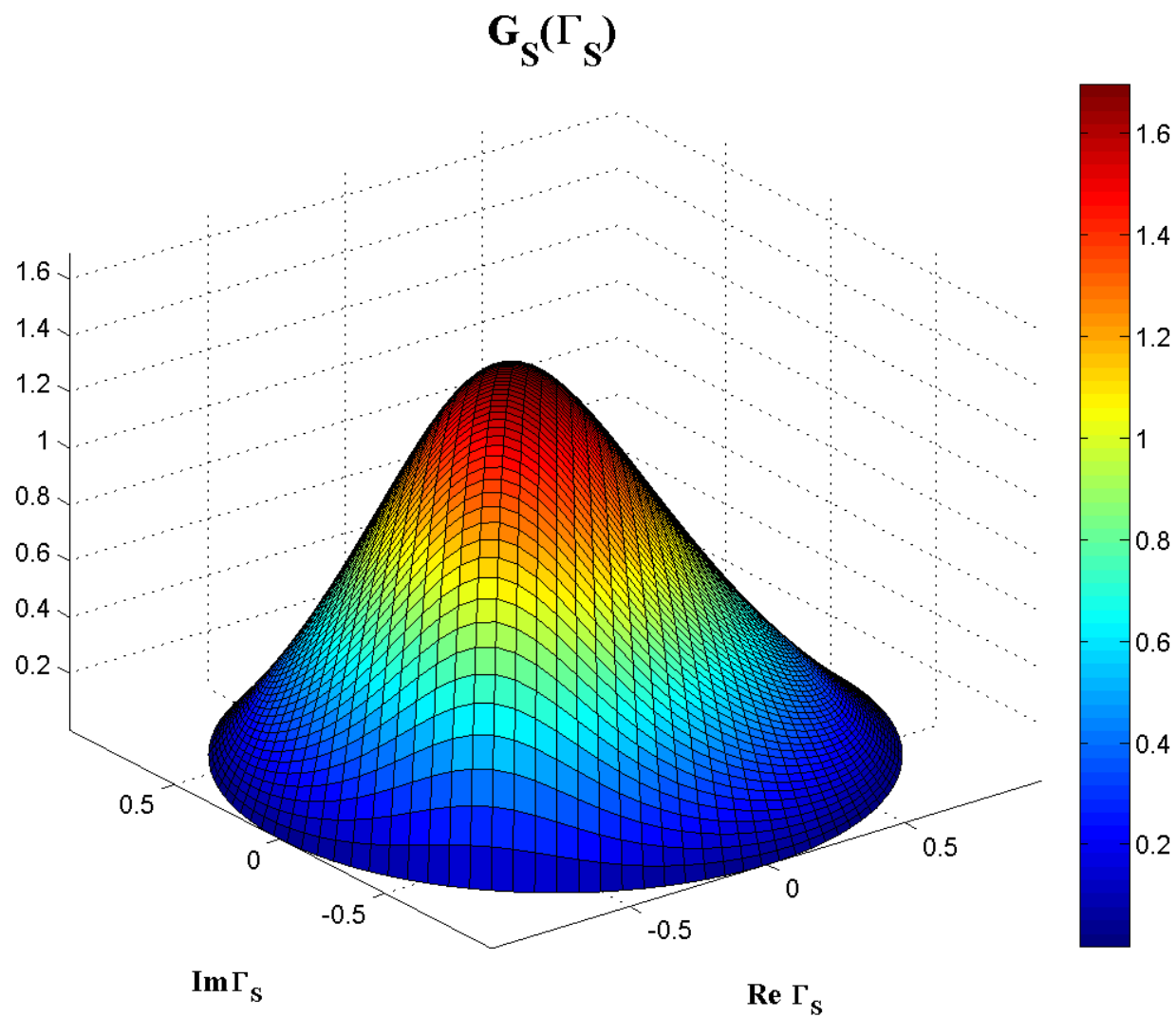


$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2}$$


$G_S(\Gamma_S)$, constant value contours

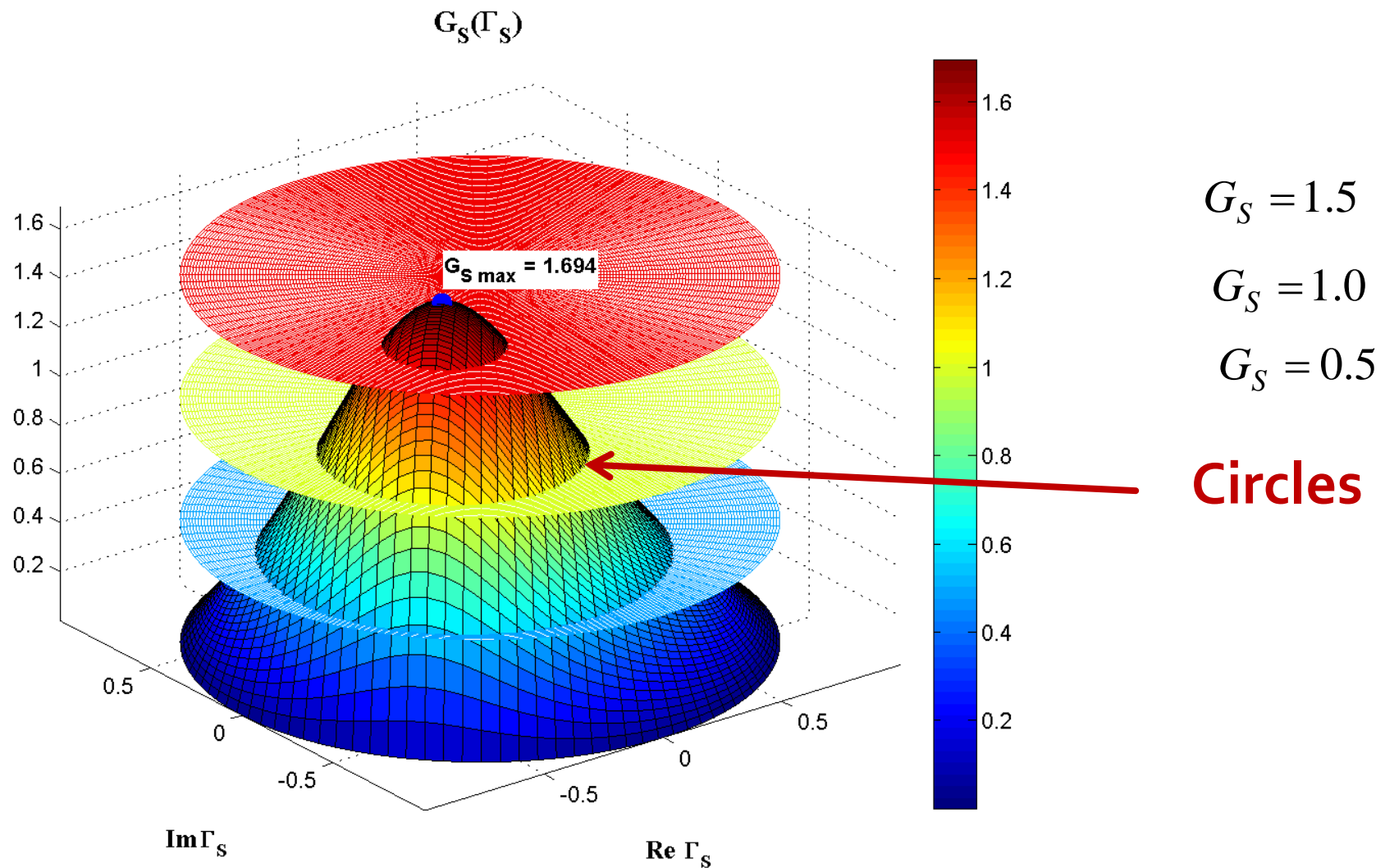


Contour map/lines

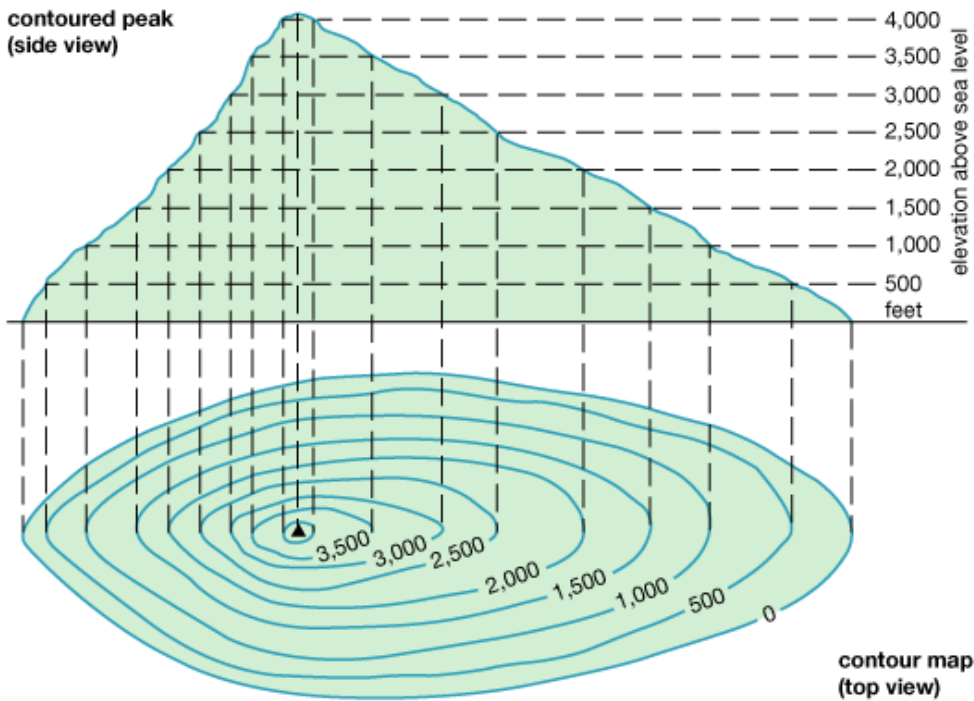

© 2011 Encyclopædia Britannica, Inc.

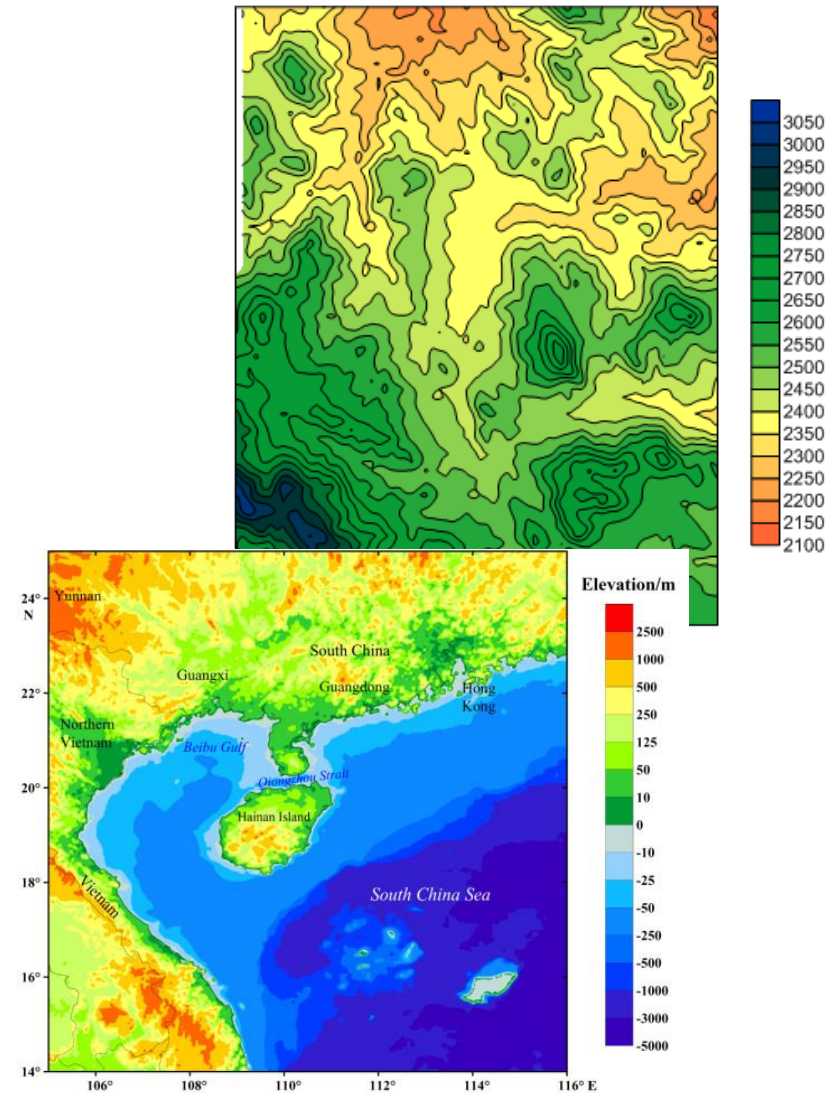


$G_S(\Gamma_S)$, constant value contours

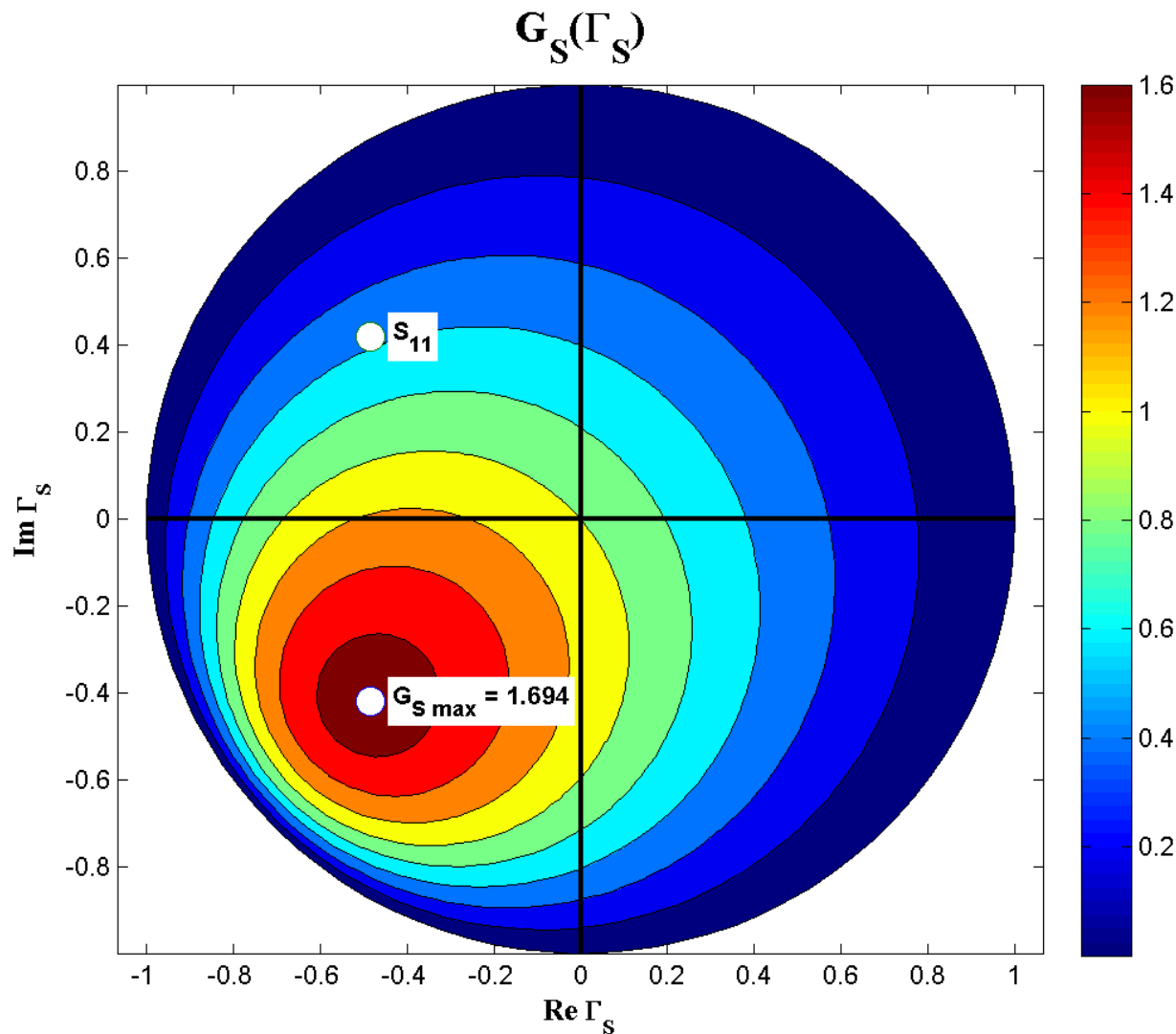

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2}$$

$$G_{S \max} = G_S \Big|_{\Gamma_S = S_{11}^*}$$

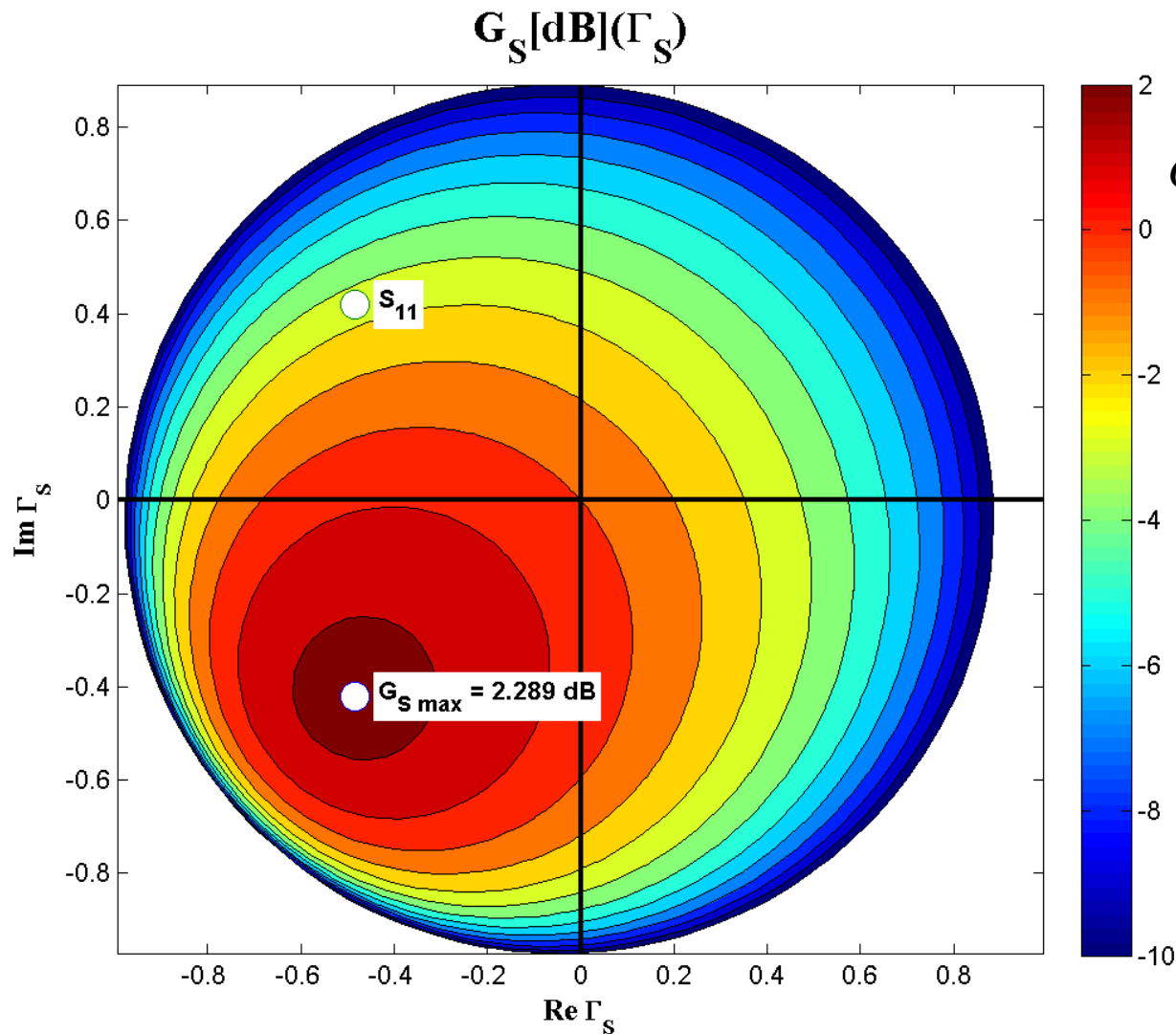$G_S[dB](\Gamma_S)$, constant value contours



$$G_S[dB] = 10 \cdot \log \left(\frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \right)$$

$$G_{S \max} = G_S \Big|_{\Gamma_S = S_{11}^*}$$

Input section constant gain circles

- The normalized gain factor (**linear scale!**)

$$g_S = \frac{G_S}{G_{S \max}} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot (1 - |S_{11}|^2) < 1$$

- Locus of the points with fixed values $g_S < 1$

$$g_S \cdot |1 - S_{11} \cdot \Gamma_S|^2 = (1 - |\Gamma_S|^2) \cdot (1 - |S_{11}|^2)$$

$$(g_S \cdot |S_{11}|^2 + 1 - |S_{11}|^2) \cdot |\Gamma_S|^2 - g_S \cdot (S_{11} \cdot \Gamma_S + S_{11}^* \cdot \Gamma_S^*) = 1 - |S_{11}|^2 - g_S$$

$$\Gamma_S \cdot \Gamma_S^* - \frac{g_S \cdot (S_{11} \cdot \Gamma_S + S_{11}^* \cdot \Gamma_S^*)}{1 - (1 - g_S) \cdot |S_{11}|^2} = \frac{1 - |S_{11}|^2 - g_S}{1 - (1 - g_S) \cdot |S_{11}|^2} + \frac{g_S^2 \cdot |S_{11}|^2}{[1 - (1 - g_S) \cdot |S_{11}|^2]^2}$$

$$|a + b|^2 = (a + b) \cdot (a + b)^* = (a + b) \cdot (a^* + b^*) = \underbrace{|a|^2} + \underbrace{|b|^2} + \underbrace{a^* \cdot b + a \cdot b^*}$$

Input section constant gain circles

$$\left| \Gamma_S - \frac{g_S \cdot S_{11}^*}{1 - (1 - g_S) \cdot |S_{11}|^2} \right| = \frac{\sqrt{1 - g_S} \cdot (1 - |S_{11}|^2)}{1 - (1 - g_S) \cdot |S_{11}|^2} \quad |\Gamma_S - C_S| = R_S$$

$$C_S = \frac{g_S \cdot S_{11}^*}{1 - (1 - g_S) \cdot |S_{11}|^2} \quad R_S = \frac{\sqrt{1 - g_S} \cdot (1 - |S_{11}|^2)}{1 - (1 - g_S) \cdot |S_{11}|^2}$$


- Equation of a circle in the complex plane where Γ_S is plotted
- **Interpretation:** Any reflection coefficient Γ_S which plotted in the complex plane lies **on** the circle drawn for $g_{\text{circle}} = G_{\text{circle}}/G_{S_{\text{max}}}$ will lead to a gain $G_S = G_{\text{circle}}$
 - Any reflection coefficient Γ_S plotted **outside** this circle will lead to a gain $G_S < G_{\text{circle}}$
 - Any reflection coefficient Γ_S plotted **inside** this circle will lead to a gain $G_S > G_{\text{circle}}$

Input section constant gain circles

$$C_S = \frac{g_S \cdot S_{11}^*}{1 - (1 - g_S) \cdot |S_{11}|^2} \quad R_S = \frac{\sqrt{1 - g_S} \cdot (1 - |S_{11}|^2)}{1 - (1 - g_S) \cdot |S_{11}|^2}$$

- The centers of each family of circles lie along straight lines given by the angle of $\Gamma_{S_{\max}} = S_{11}^*$
- Circles are plotted (traditionally, CAD) in **logarithmic scale** ([dB])
 - formulas are in **linear scale!**
- The circle for $G_S = 0$ dB will always pass through the origin of the complex plane (center of the Smith chart)

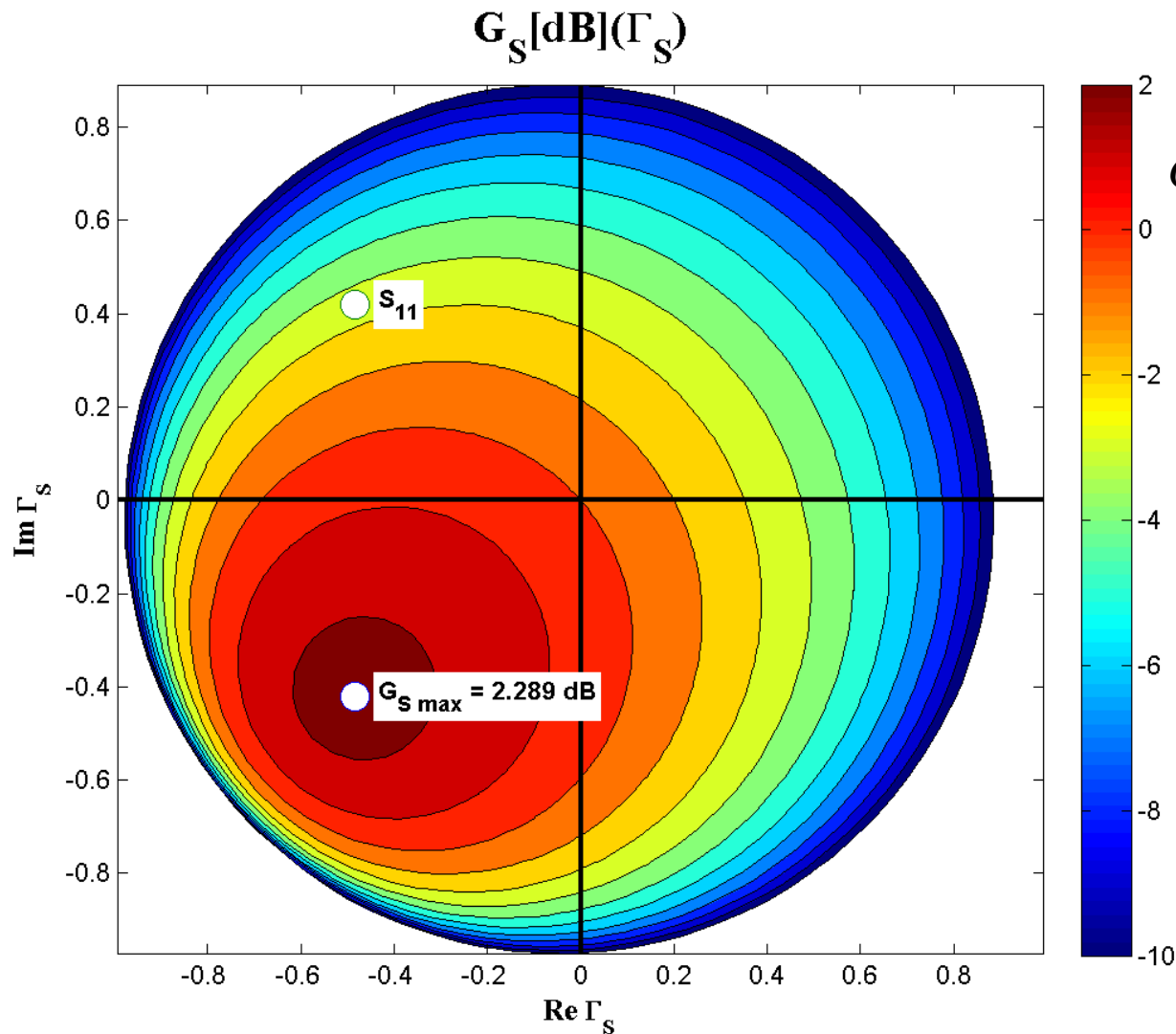
$G_S[dB](\Gamma_S)$, constant value contours



$$G_S[dB] = 10 \cdot \log \left(\frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \right)$$

$$G_{S \max} = G_S \Big|_{\Gamma_S = S_{11}^*}$$

Output section constant gain circles

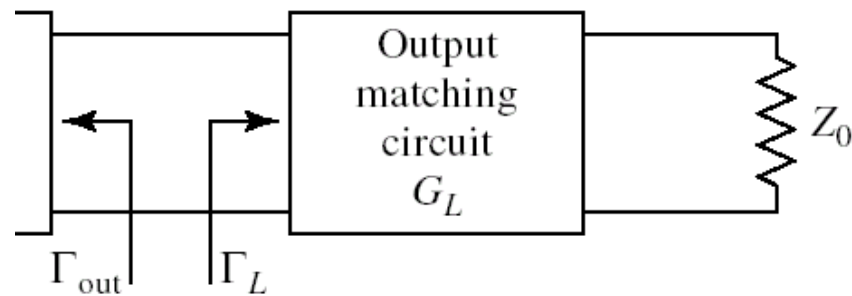

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

- Maximum gain for $\Gamma_L = S_{22}^* \Rightarrow G_{Lmax} = \frac{1}{1 - |S_{22}|^2}$

$$g_L = \frac{G_L}{G_{Lmax}} = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2} \cdot (1 - |S_{22}|^2) < 1$$

- Similar computations


$$C_L = \frac{g_L \cdot S_{22}^*}{1 - (1 - g_L) \cdot |S_{22}|^2}$$

$$R_L = \frac{\sqrt{1 - g_L} \cdot (1 - |S_{22}|^2)}{1 - (1 - g_L) \cdot |S_{22}|^2}$$

- Example


$$G_{Lmax} = \frac{1}{1 - |S_{22}|^2} = 1.051 = 0.215 \text{ dB}$$

$G_L(\Gamma_L)$

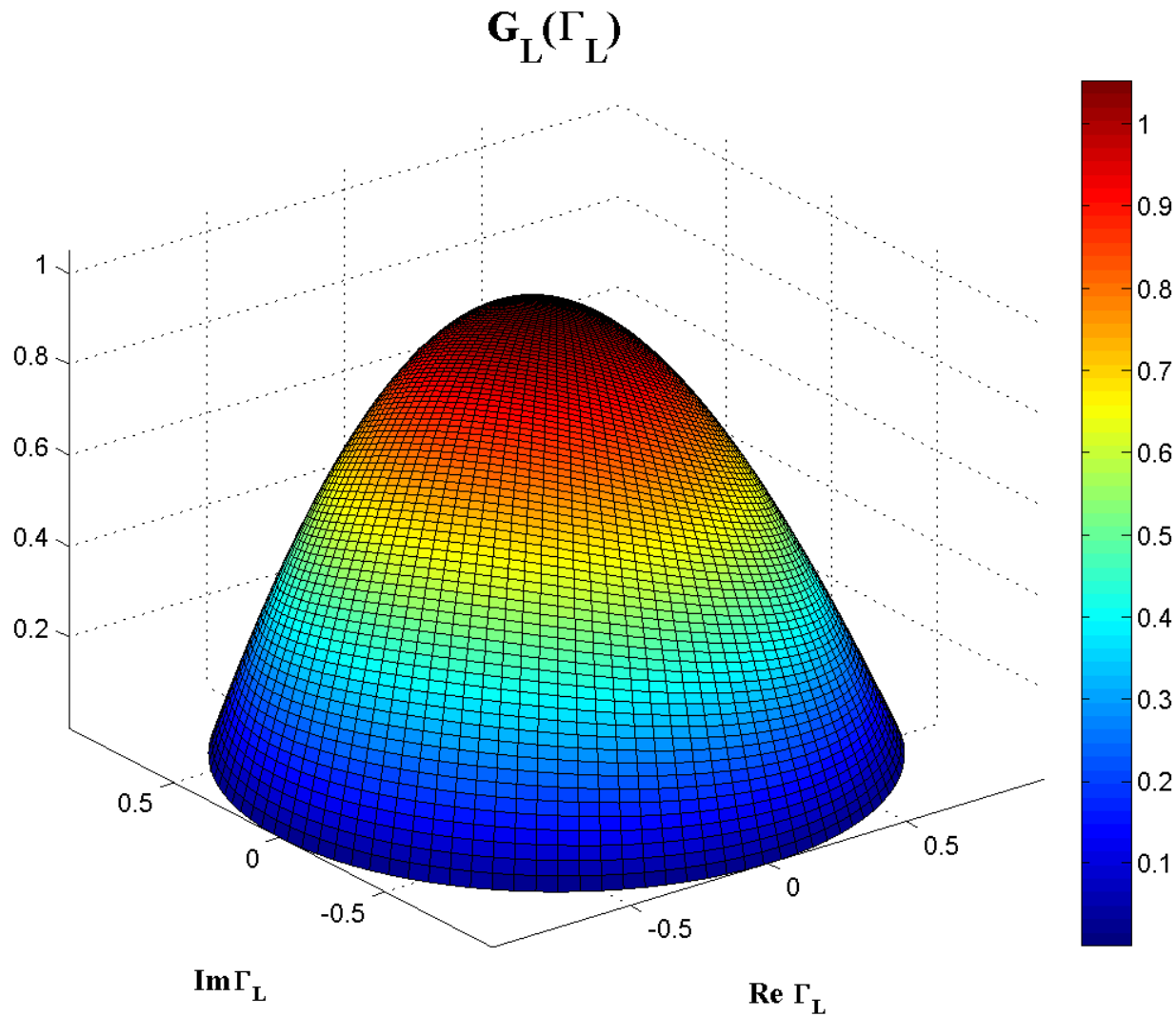

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$


$G_L(\Gamma_L)$, constant value contours

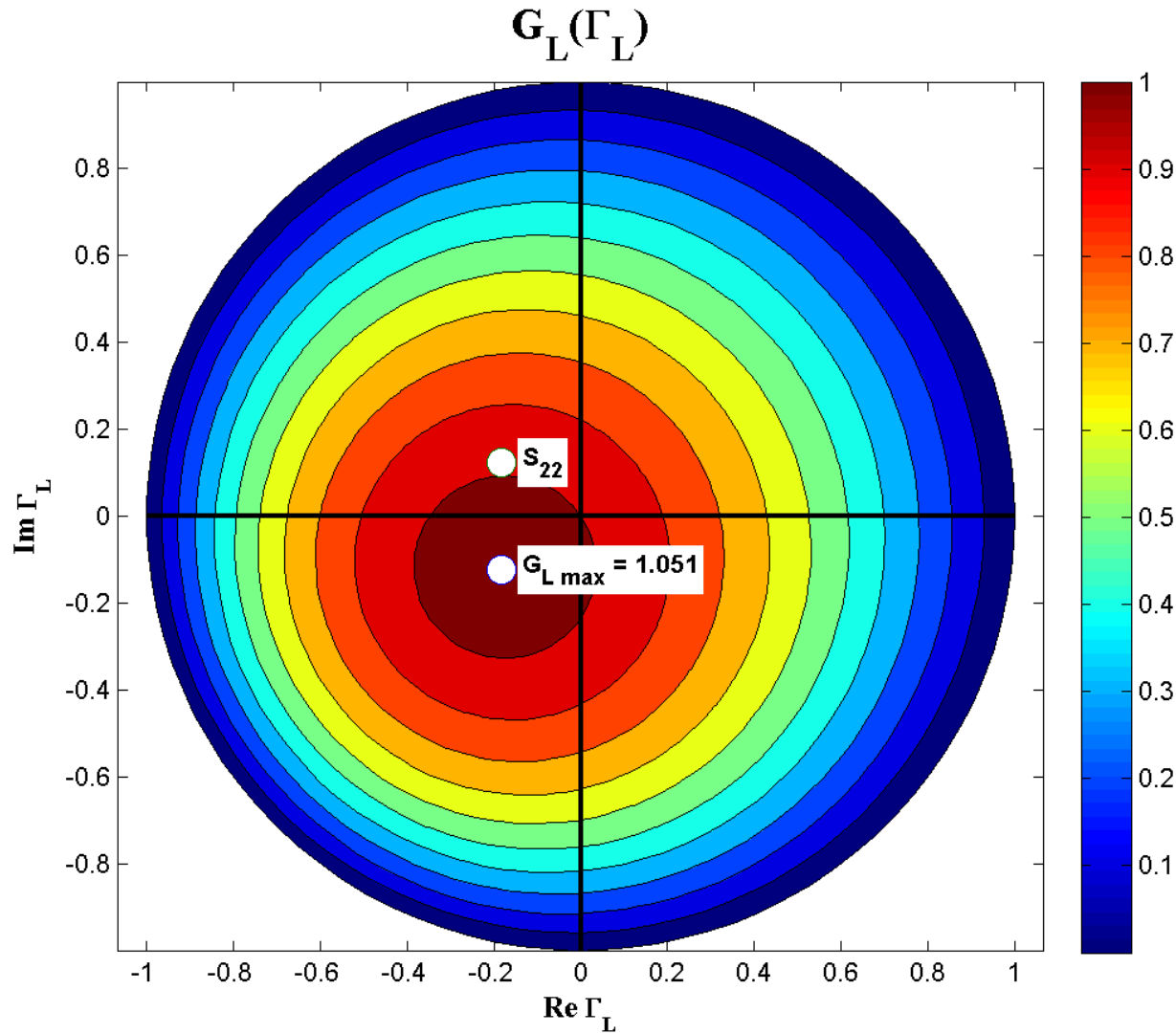

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$G_{L \max} = G_L \Big|_{\Gamma_L = S_{22}^*}$$


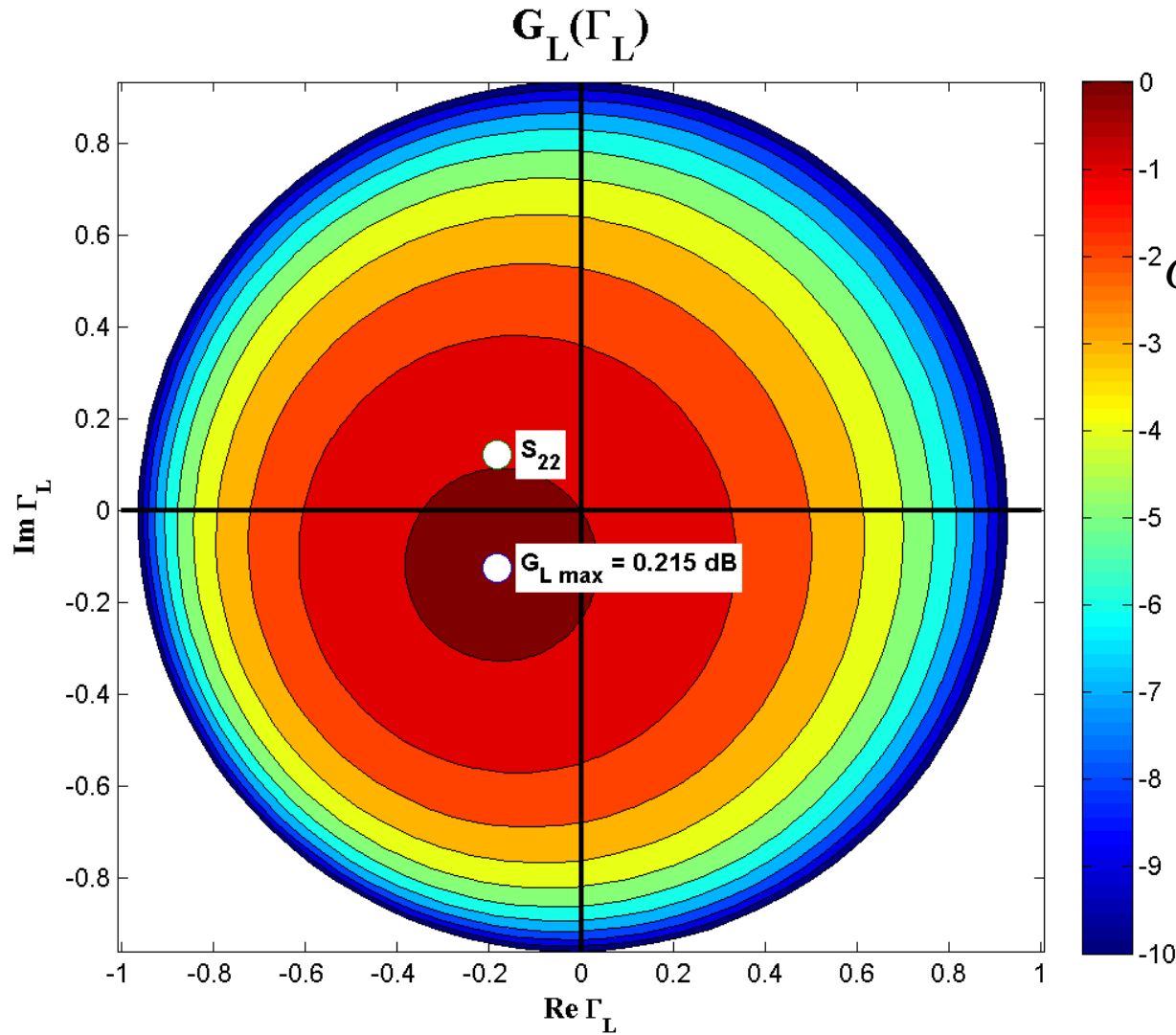
$G_L[\text{dB}](\Gamma_L)$, constant value contours



$$G_L[\text{dB}] = 10 \cdot \log \left(\frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2} \right)$$

$$G_{L \text{ max}} = G_L \Big|_{\Gamma_L = S_{22}^*}$$


ADS

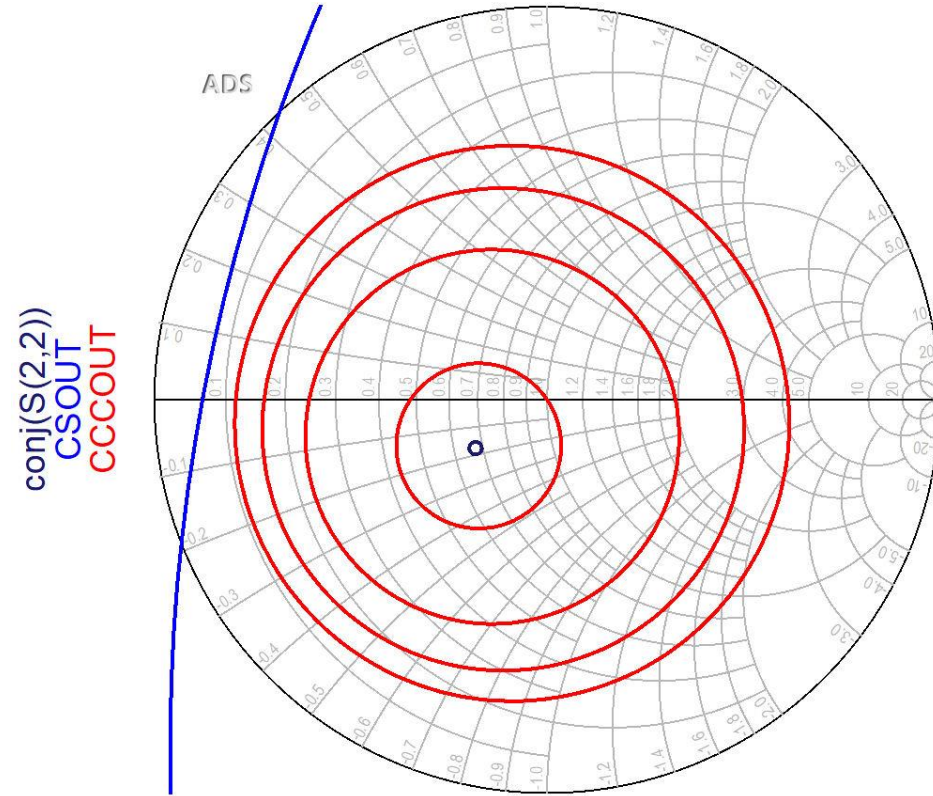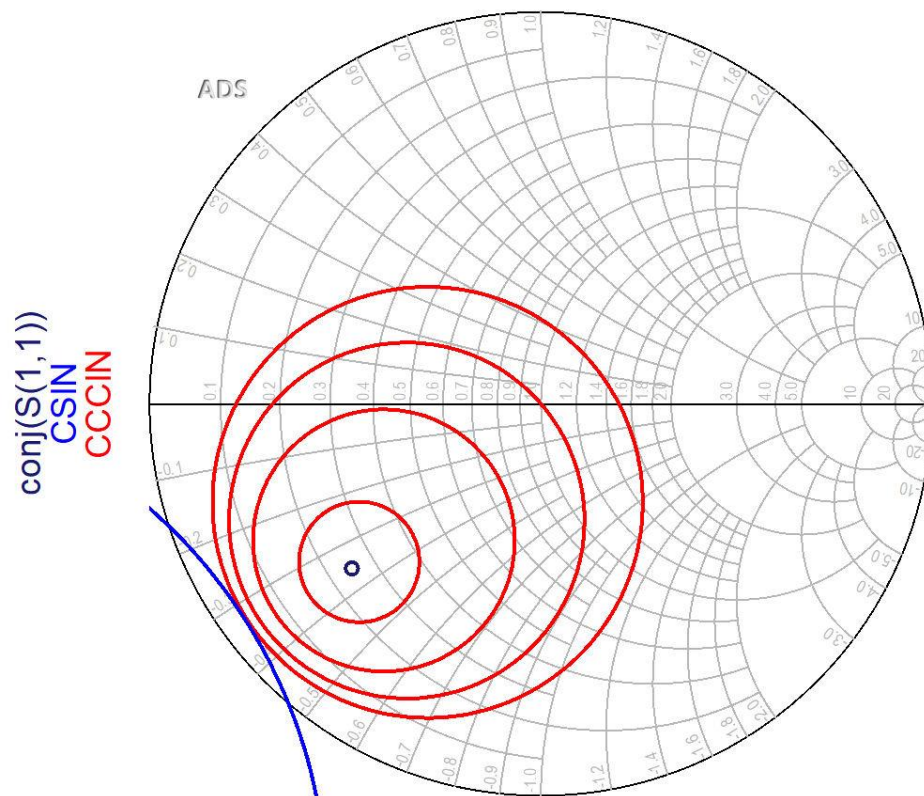

- Circles are plotted for requested values (**in dB!**)
- It is useful to compute $G_{S_{\max}}$ and $G_{L_{\max}}$ before
 - in order to request relevant circles

Schematic 1 – Lab 3

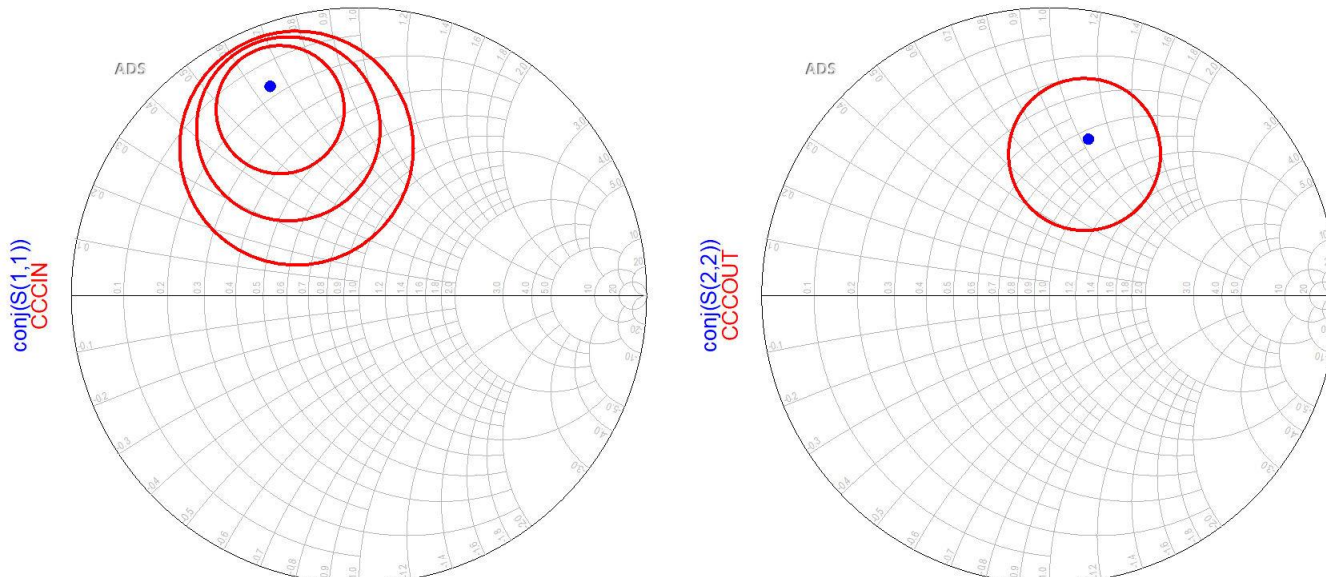- **multiple circles (families)** are plotted and some required values are computed



Eqn $\gamma_{opt} = S_{opt}$

Eqn $G_0 = 10 \cdot \log(\text{mag}(S(2,1))^2)$

Eqn $G_{Smax} = 10 \cdot \log(1/(1 - \text{mag}(S(1,1))^2))$

Eqn $G_{Lmax} = 10 \cdot \log(1/(1 - \text{mag}(S(2,2))^2))$

freq	K	MAG	NFmin	Sopt	Rn	G0	GLmax	GSmax
5.000 GHz	0.533	15.296	0.700	0.660 / 106...	19.500	8.974	1.634	4.249

Design for Specified Gain

- We compute G_o , $G_{S_{max}}$, $G_{L_{max}}$
- To obtain the design gain we **choose** supplemental gain needed (supplemental to constant G_o)
 - we account for the deviation that might arise from the unilateral assumption (using unilateral figure of merit U)


$$G_{design} [dB] = G_{S_design} [dB] + G_o [dB] + G_{L_design} [dB]$$

- We plot the circles for design (chosen) values G_{S_design} , G_{L_design}
- We design input and output matching circuits which move the reflection coefficient **on** or **inside** the design circles (depending on specific application requirements)

Microwave Amplifiers

Low-Noise Amplifier Design


Amplifier as two-port

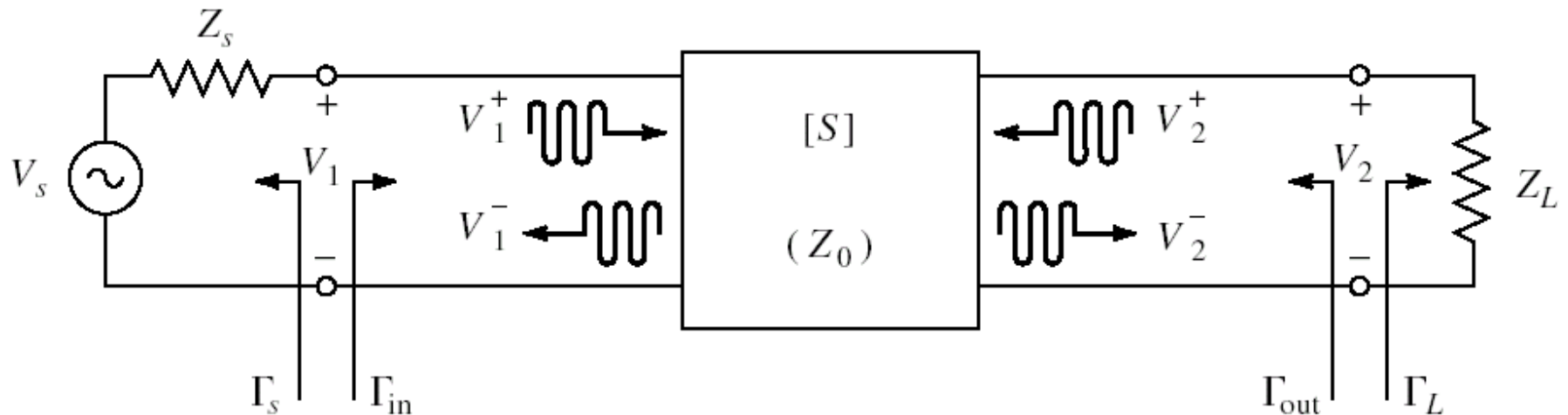

- For an amplifier two-port we are interested in:
 - stability
 - power gain
 - **noise** (sometimes – **small signals**)
 - linearity (sometimes – large signals)

Noise

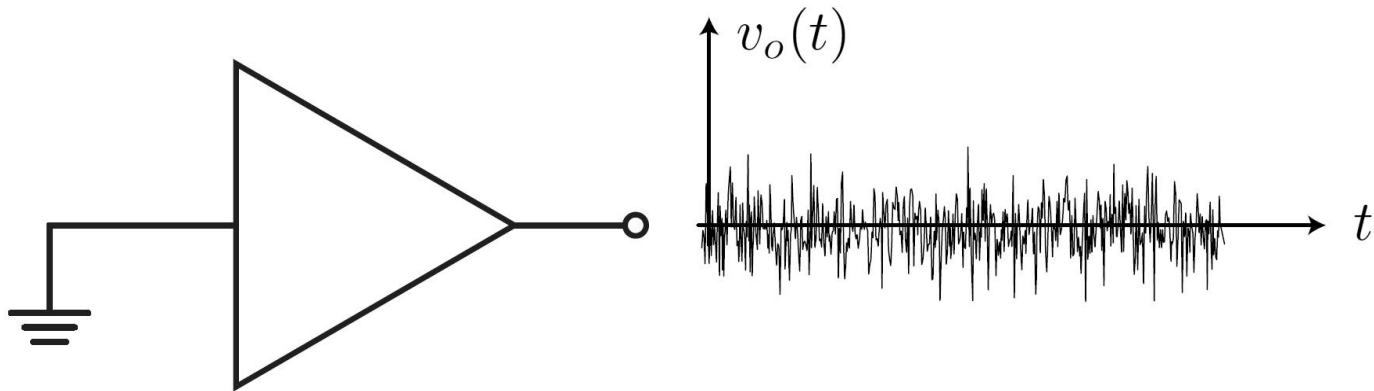- Noise: random fluctuations of the signal




$$\overline{v_n(t)} = \langle v_n(t) \rangle = \frac{1}{T} \int_0^T v_n(t) dt = 0$$

$$\overline{v_n^2(t)} = \langle v_n^2(t) \rangle = \frac{1}{T} \int_0^T v_n^2(t) dt \neq 0$$

$$V_{n(e\text{f})} = \sqrt{\overline{v_n^2(t)}}$$

Noise

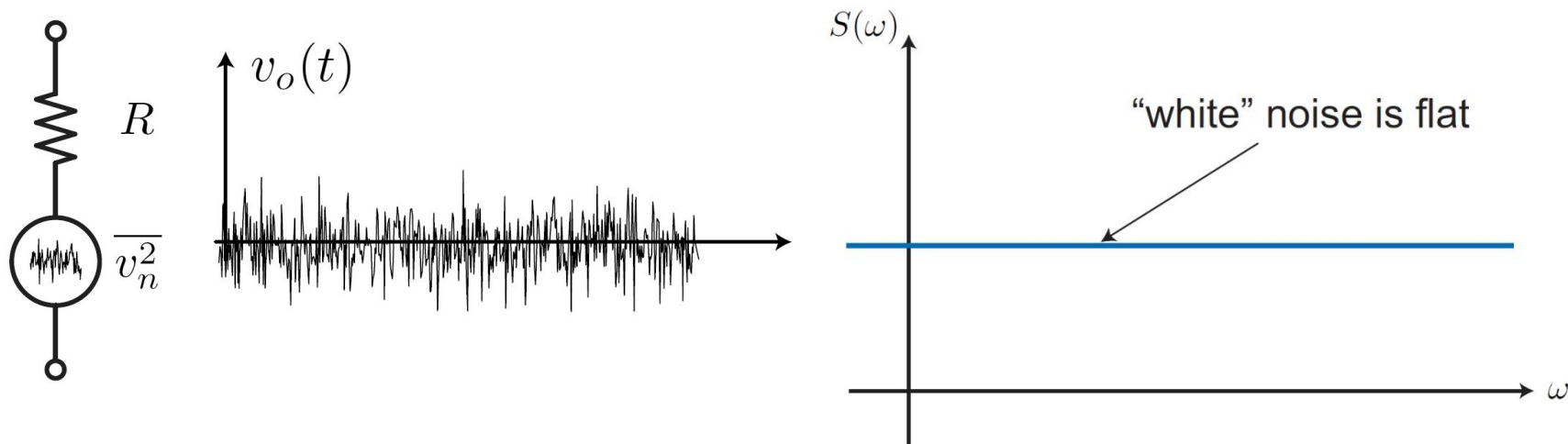


- effective noise voltage

$$V_{n(ef)} = \sqrt{4kTBR}$$

- noise power available (for maximum power transfer with impedance/resistance matching)

$$P_n = kTB$$

Noise Figure F

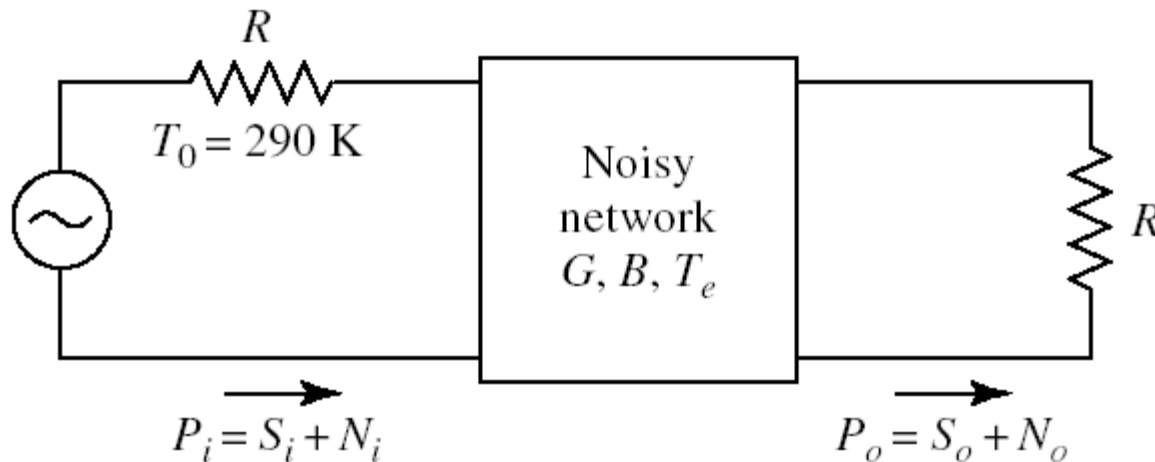


- The noise figure F , is a measure of the reduction in signal-to-noise ratio between the input and output of a device, when (by definition) the input noise power is assumed to be the noise power resulting from a matched resistor at $T_0 = 290\text{ K}$ (reference noise conditions)

$$F = \left. \frac{S_i/N_i}{S_o/N_o} \right|_{T_0=290K}$$

$$V_{n(e\text{f})} = \sqrt{4kTB R}$$

$$P_n = kTB$$


Noise Figure F

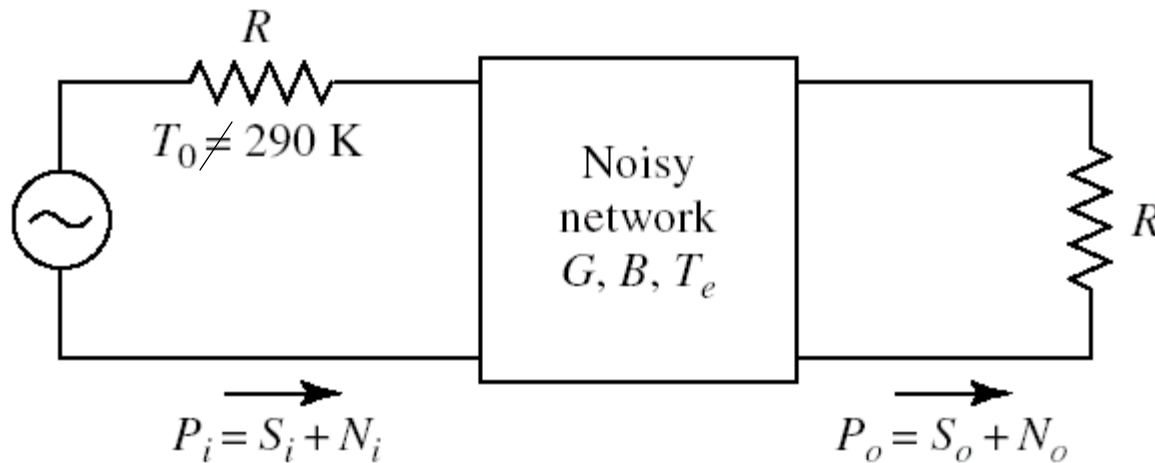

- The noise figure F , **is not** directly a measure of the reduction in signal-to-noise ratio between the input and output of a device, when the input noise power is different from that of the reference noise conditions


$$F \neq \left. \frac{S_i/N_i}{S_o/N_o} \right|_{T_0 \neq 290 \text{ K}}$$

Noise Figure F

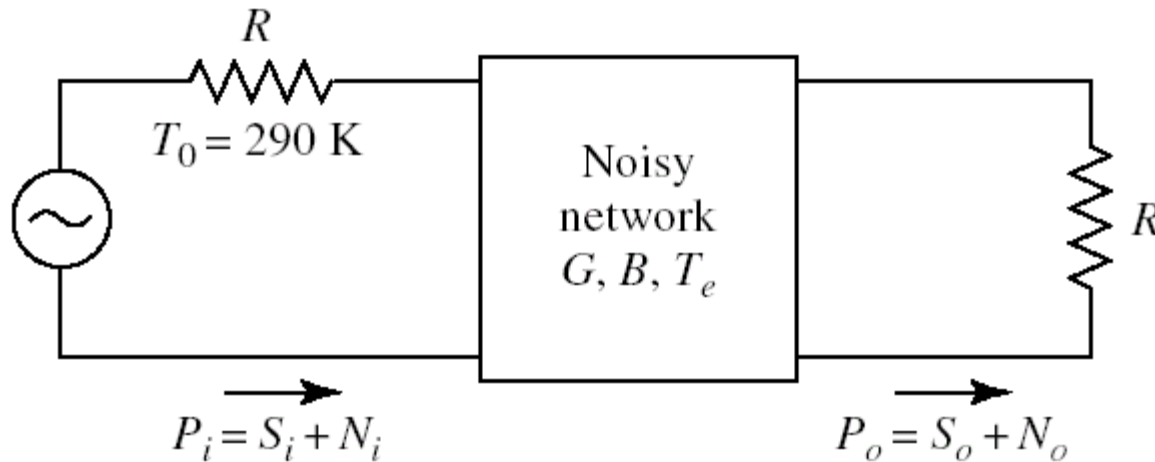

- In general, the output noise power consists of two elements:
 - the input noise power amplified or attenuated by the device (for example amplified with the power gain G applied also to the desired signal)
 - a noise power generated internally by the network if the network is noisy (this power **does not** depend on the input noise power)

Noise Figure F

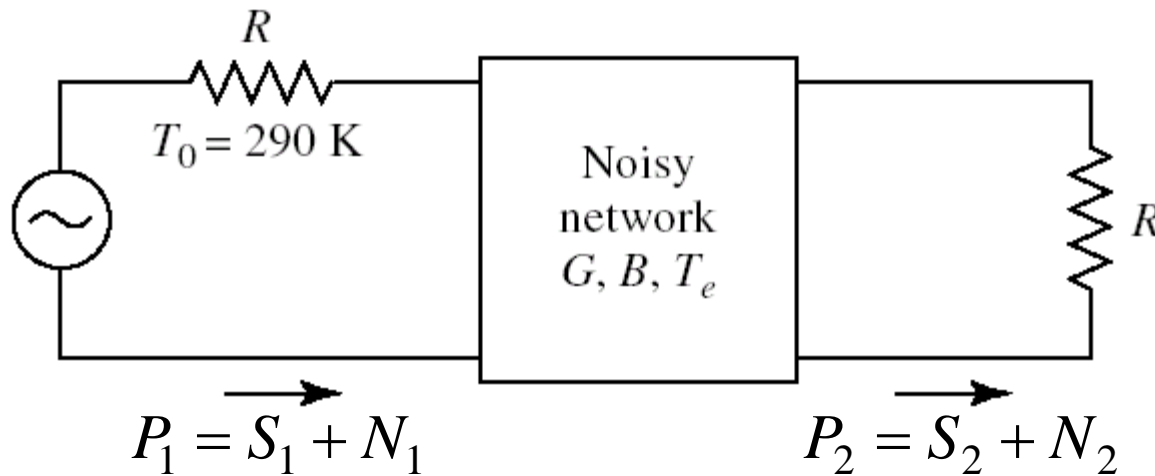


- Estimation of the internally generated noise power can be done using the Noise Figure F definition:

$$F = \left. \frac{S_1/N_1}{S_2/N_2} \right|_{T_0=290\text{K}, N_1=N_0}$$

$$N_2 = F \cdot N_0 \cdot \frac{S_2}{S_1} = F \cdot N_0 \cdot G$$

$$N_2 = N_0 \cdot G + (F - 1) \cdot N_0 \cdot G$$

Noise Figure F


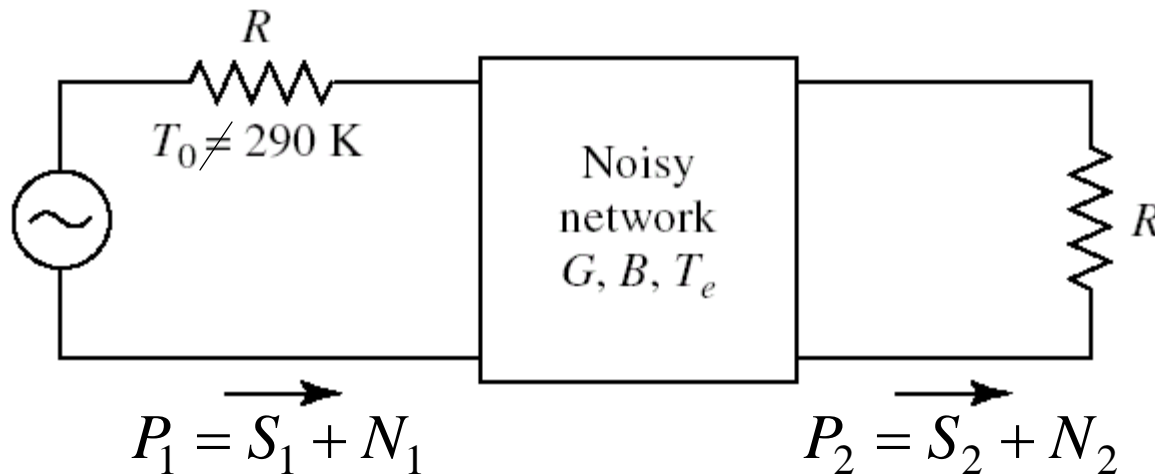


- We identify the two terms:
 - amplified input noise
 - internally generated noise
- When the input noise does not correspond to reference noise conditions ($N_1 \neq N_0$)
 - the internally generated noise does not change

$$N_2 = N_0 \cdot G + (F - 1) \cdot N_0 \cdot G$$

$$N_2 = N_1 \cdot G + (F - 1) \cdot N_0 \cdot G$$

Noise figure of a cascaded system

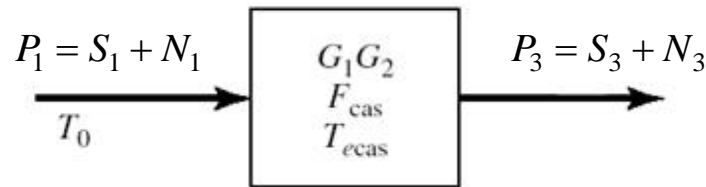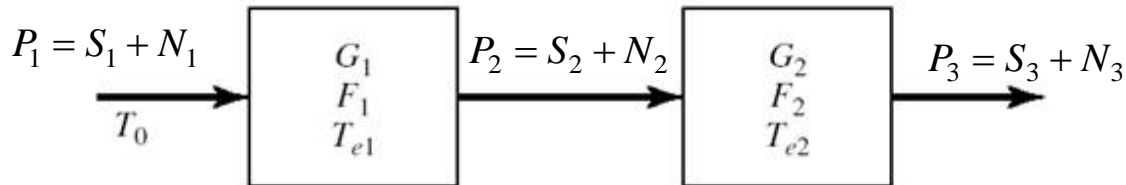

$$N_2 = N_1 \cdot G_1 + (F_1 - 1) \cdot N_0 \cdot G_1$$

$$G_{cas} = G_1 \cdot G_2$$

$$N_3 = N_2 \cdot G_2 + (F_2 - 1) \cdot N_0 \cdot G_2$$



$$N_3 = N_1 \cdot G_{cas} + (F_{cas} - 1) \cdot N_0 \cdot G_{cas}$$



$$N_3 = [N_1 \cdot G_1 + (F_1 - 1) \cdot N_0 \cdot G_1] \cdot G_2 + (F_2 - 1) \cdot N_0 \cdot G_2$$

$$N_3 = N_1 \cdot G_1 \cdot G_2 + (F_1 - 1) \cdot N_0 \cdot G_1 \cdot G_2 + (F_2 - 1) \cdot N_0 \cdot G_2$$

Noise figure of a cascaded system

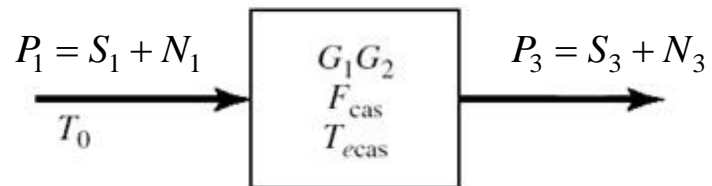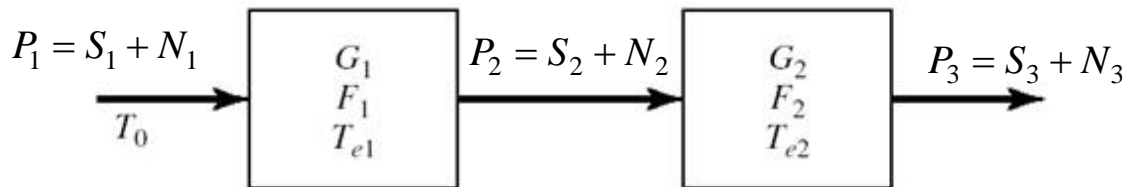


$$N_3 = N_1 \cdot G_1 \cdot G_2 + (F_1 - 1) \cdot N_0 \cdot G_1 \cdot G_2 + (F_2 - 1) \cdot N_0 \cdot G_2$$

$$G_{cas} = G_1 \cdot G_2 \quad N_3 = N_1 \cdot G_{cas} + (F_{cas} - 1) \cdot N_0 \cdot G_{cas}$$


$$(F_1 - 1) \cdot N_0 \cdot G_1 \cdot G_2 + (F_2 - 1) \cdot N_0 \cdot G_2 = (F_{cas} - 1) \cdot N_0 \cdot G_1 \cdot G_2$$

$$F_{cas} = F_1 + \frac{1}{G_1} (F_2 - 1)$$

Noise figure of a cascaded system

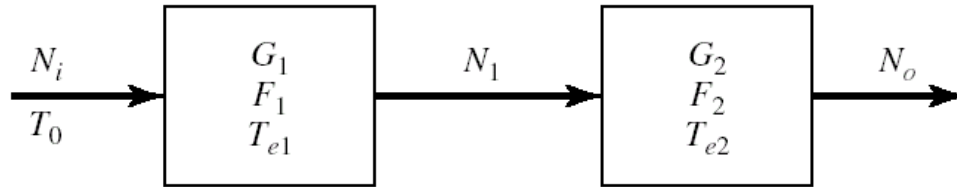

(a)

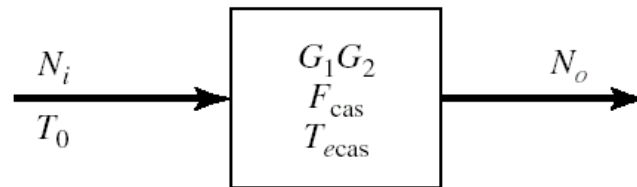

(b)

$$G_{cas} = G_1 \cdot G_2 \qquad F_{cas} = F_1 + \frac{1}{G_1} (F_2 - 1)$$

- Friis Formula (!linear scale)

$$F_{cas} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 \cdot G_2} + \frac{F_4 - 1}{G_1 \cdot G_2 \cdot G_3} + \dots$$

Friis Formula (noise)

$$F_{cas} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 \cdot G_2} + \frac{F_4 - 1}{G_1 \cdot G_2 \cdot G_3} + \dots$$

- Friis Formula shows that:
 - the overall noise figure of a cascaded system is largely determined by the noise characteristics of the first stage
 - the noise introduced by the following stages is reduced:
 - -1
 - division by G (usually $G > 1$)

Friis Formula (noise)

$$F_{cas} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 \cdot G_2} + \frac{F_4 - 1}{G_1 \cdot G_2 \cdot G_3} + \dots$$


- Effects of Friis Formula:
- in multi stage amplifiers:
 - it's essential that the first stage is as noiseless as possible even if that means sacrificing power gain
 - the following stages can be optimized for power gain
- in single stage amplifiers:
 - in the input matching circuit it's important to have noiseless elements (pure reactance, lossless lines)
 - output matching circuit has less influence on the noise (noise generated at this level appears when the desired signal has already been amplified by the transistor)

$$V_{n(ef)} = \sqrt{4kTBR}$$

$$P_n = kTB$$

Noise Figure of a Mismatched Amplifier

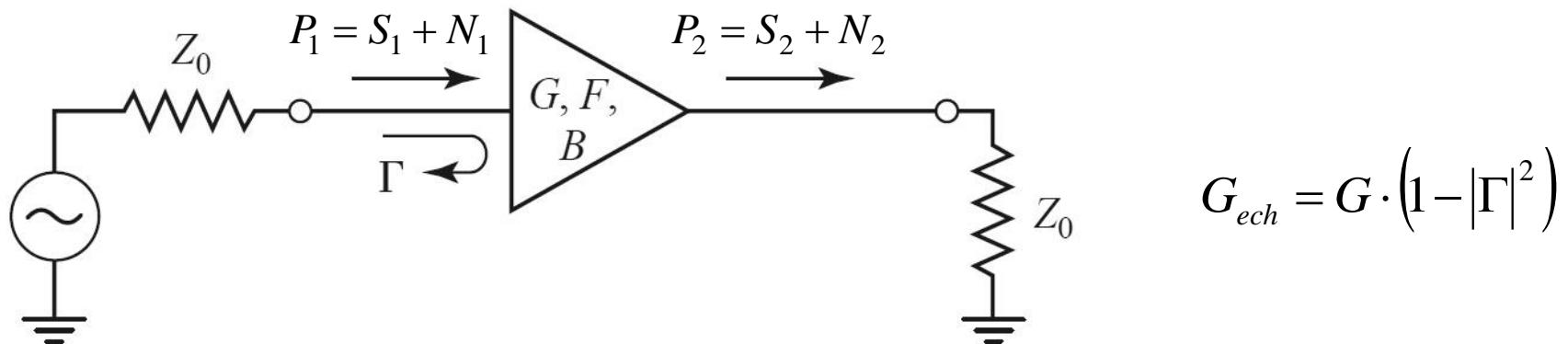- An input mismatched amplifier ($\Gamma \neq 0$)



$$N_2 = N_1 \cdot G \cdot (1 - |\Gamma|^2) + (F - 1) \cdot N_0 \cdot G = N_1 \cdot G \cdot (1 - |\Gamma|^2) + \frac{F - 1}{1 - |\Gamma|^2} \cdot N_0 \cdot G \cdot (1 - |\Gamma|^2)$$

$$N_2 = N_1 \cdot G_{ech} + (F_{ech} - 1) \cdot N_0 \cdot G_{ech} \qquad F_{ech} = 1 + \frac{F - 1}{1 - |\Gamma|^2} \geq F$$

- Good noise figure **requires** good impedance matching

Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.etti.tuiasi.ro>
- rdamian@etti.tuiasi.ro