

Lecture 11

2022/2023

Microwave Devices and Circuits for Radiocommunications

2022/2023

- 2C/1L, **MDCR**
- Attendance at minimum 7 sessions (course or laboratory)
- Lectures- **associate professor Radu Damian**
 - Tuesday 12-14, ~~Online~~, P8
 - E – 50% final grade
 - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
 - first test L1: 21-28.02.2023 (t2 and t3 not announced, lecture)
 - 3att.=+0.5p
 - all materials/equipments authorized

2022/2023

- Laboratory – **associate professor Radu Damian**
 - Tuesday 08-12, II.13 / (08:10)
 - L – 25% final grade
 - ADS, 4 sessions
 - Attendance + **personal results**
 - P – 25% final grade
 - ADS, 3 sessions (-1? 21.02.2022)
 - personal homework

Materials

■ <http://rf-opto.etti.tuiasi.ro>

Laboratorul de Microunde si Opti

Not secure | rf-opto.etti.tuiasi.ro/microwave_cd.php?chg_lang=0

☆

Main

Courses

Master

Staff

Research

Students

Admin

Microwave CD

Optical Communications

Optoelectronics

Internet

Antennas

Practica

Networks

Educational software

Microwave Devices and Circuits for Radiocommunications (English)

Course: MDCR (2017-2018)

Course Coordinator: Assoc.P. Dr. Radu-Florin Damian
Code: EDOS412T
Discipline Type: DOS; Alternative, Specialty
Credits: 4
Enrollment Year: 4, Sem. 7

Activities

Course: Instructor: Assoc.P. Dr. Radu-Florin Damian, 2 Hours/Week, Specialization Section, Timetable:
Laboratory: Instructor: Assoc.P. Dr. Radu-Florin Damian, 1 Hours/Week, Group, Timetable:

Evaluation

Type: **Examen**

A: 50%, (Test/Colloquium)
B: 25%, (Seminary/Laboratory/Project Activity)
D: 25%, (Homework/Specialty papers)

Grades

[Aggregate Results](#)

Attendance

[Course](#)
[Laboratory](#)

Lists

[Bonus-uri acumulate \(final\)](#)
[Studenti care nu pot intra in examen](#)

Materials

Course Slides

[MDCR Lecture 1](#) (pdf, 5.43 MB, en, [99](#))
[MDCR Lecture 2](#) (pdf, 3.67 MB, en, [99](#))
[MDCR Lecture 3](#) (pdf, 4.76 MB, en, [99](#))
[MDCR Lecture 4](#) (pdf, 5.58 MB, en, [99](#))



 **English** |  Romana |

Main

Courses

Master

Staff

Rese

Grades

Student List

Exams

Photos

Online Exams

In order to participate at online exams you must get ready following

1. On the main menu, choose the language you are comfortable

Materials

- RF-OPTO
 - <http://rf-opto.etti.tuiasi.ro>
- **David Pozar, “Microwave Engineering”,**
Wiley; 4th edition , 2011
 - 1 exam problem ← Pozar
- Photos
 - sent by **email**/online exam
 - used at lectures/laboratory

Access

■ Not customized



A screenshot of a student profile page. On the left is a small, pixelated portrait of a man. To the right of the portrait is a table with student details. Below the table is a link 'Acceseaza ca acest student' circled in red. At the bottom is a table of grades.

Date:

Grupa	5304 (2015/2016)
Specializarea	Tehnologii si sisteme de telecomunicatii
Marca	5184

[Acceseaza ca acest student](#)

Note obtinute

Disciplina	Tip	Data	Descriere	Nota	Puncte	Obs.
TW	Tehnologii Web					
	N	17/01/2014	Nota finala	10	-	
	A	17/01/2014	Colocviu Tehnologii Web 2013/2014	10	7.55	
	B	17/01/2014	Laborator Tehnologii Web 2013/2014	9	-	
	D	17/01/2014	Tema Tehnologii Web 2013/2014	9	-	



A screenshot of a login form. It contains fields for 'Nume', 'Email', and 'Cod de verificare'. The 'Email' and 'Cod de verificare' fields are circled in red. Below the 'Cod de verificare' field is a blue box with the text '344bd9f' and a red 'X' over it. At the bottom is a 'Trimite' button.

Nume
IACOBSCU

Email

Cod de verificare

344bd9f

Trimite

Online

- access to **online exams** requires the **password** received by email

English | Romana |

Main Courses Master Staff Research **Student**

Grades Student List Exams Photos

POPESCU GOPO ION



Fotografia nu exista

Date:	
Grupa	5700 (2019/2020)
Specializarea	Inginerie electronica si telecomunicatii
Marca	7000000

[Access the site as this student](#) | [request access to software](#)

Grades

Inca nu a fost notat.

Main Courses Master Staff Research

Grades **Student List** Exams Photos

Login

Use the last name and email stored in the database

Name
POPESCU GOPO

Email/Password

Write the code below

828f26b

Send

Online

- access email/password

Main Courses Master Staff Research

Grades Student List Exams Photos

POPESCU GOPO ION



**Fotografia
nu exista**

Date:


Grupa	5700 (2019/2020)
Specializarea	Inginerie electronica si telec
Marca	7000000

You access the site as **this student!**

Main Courses Master Staff Research

Grades Student List Exams Photos

POPESCU GOPO ION



**Fotografia
nu exista**

Date:

Grupa	5700 (2019/2020)
Specializarea	Inginerie electronica si telec
Marca	7000000

You access the site as **this student (including exams)!**

Password

■ received by email

Important message from RF-OPTO

Inbox x



Radu-Florin Damian

to me, POPESCU



Romanian

> English

[Translate message](#)



Laboratorul de Microunde si Optoelectronica
Facultatea de Electronica, Telecomunicatii si Tehnologia Informatiei
Universitatea Tehnica "Gh. Asachi" Iasi

In atentie: POPESCU GOPO ION

Parola pentru a accesa examenele pe server-ul **rf-opto** este

Parola: [REDACTED]

Identificati-va pe [server](#), cu parola, cat mai rapid, pentru confirmare.

Memorati acest mesaj intr-un loc sigur, pentru utilizare ulterioara

Attention: POPESCU GOPO ION

The password to access the exams on the **rf-opto** server is

Password: [REDACTED]

Login to the [server](#), with this password, as soon as possible, for confirmation.

Save this message in a safe place for later use

Reply

Reply all

Forward

Subject	Correspondents
Important message from RF-OPTO	POPESCU GOPO ION
Validation of MDCK exam from 02/05/2020	[REDACTED]
[REDACTED]	[REDACTED]

From: Me <rdamian@etti.tuiasi.ro>

Subject: Important message from RF-OPTO

To: [REDACTED]

Cc: Me <rdamian@etti.tuiasi.ro>



Laboratorul de Microunde si Optoelectronica
Facultatea de Electronica, Telecomunicatii si Tehnologia Informatiei
Universitatea Tehnica "Gh. Asachi" Iasi

In atentie: POPESCU GOPO ION

Parola pentru a accesa examenele pe server-ul **rf-opto** este

Parola: [REDACTED]

Identificati-va pe [server](#), cu parola, cat mai rapid, pentru confirmare.

Memorati acest mesaj intr-un loc sigur, pentru utilizare ulterioara

Attention: POPESCU GOPO ION

The password to access the exams on the **rf-opto** server is

Password: [REDACTED]

Login to the [server](#), with this password, as soon as possible, for confirmation.


Save this message in a safe place for later use


Online exam manual

- The online exam app used for:
 - ~~lectures (attendance)~~
 - laboratory
 - project
 - ~~examinations~~

Materials

Other data

[Manual examen on-line](#) (pdf, 2.65 MB, ro, )

[Simulare Examen](#) (video) (mp4, 65.12 MB, ro, )

Microwave Devices and Circuits (Englis

Examen online

- always against a **timetable**
 - long period (lecture attendance/laboratory results)
 - ~~short period (tests: 15min, exam: 2h)~~

Announcement 23:59 (10/05/2020)	Support material 00:05 (11/05/2020)	Exam Topics 00:07 (11/05/2020)	Results 00:10 (11/05/2020)	End 00:20 (15/05/2020)	Confirmation 00:20 (16/05/2020)	Next timeframe in: 05 m 43 s Refresh now
---	---	--	--------------------------------------	----------------------------------	---	--

Announcement

This is a "fake" exam, introduced to familiarize you with the server interface and to perform the necessary actions during an exam: thesis scan, selfie, use email for co

Server Time

All exams are based on the server's time zone (it may be different from local time). For reference time on the server is now:

10/05/2020 23:59:16

Online results submission



- many numerical values/files

Schema finala	Rezultate - castig	Rezultate - zgomot	Fisier justificare calcul (factor andrei)	Fisier zap (optional)	T1, fisier parmetri S	T2, fisier parmetri S	Z1	Z2	Z3	Z4	Z5	Z6	Z7	Ze1	Zo1	Ze2	Zo2	Ze3	Zo3	Ze4	Zo4	Ze5	Zo5	Ze6
86 - 5428 - 259 ...	86 - 5428 - 260 ...	86 - 5428 - 261 ...	86 - 5428 - 316 ...	-	86 - 5428 - 314 ...	86 - 5428 - 315 ...	148.33	155.88	202.12	164.35	180.91	30.29	185.19	79.9	37	68.89	45.14	61.83	45.05	57.97	46.02	61.85	45.05	68.8
86 - 5622 - 259 ...	86 - 5622 - 260 ...	86 - 5622 - 261 ...	86 - 5622 - 316 ...	86 - 5622 - 262 ...	86 - 5622 - 314 ...	86 - 5622 - 315 ...	26.97	153.5	34.64	35.79	55.56	26.212	10.693	0	0	0	0	0	0	0	0	0	0	0
86 - 5488 - 259 ...	86 - 5488 - 260 ...	86 - 5488 - 261 ...	86 - 5488 - 316 ...	86 - 5488 - 262 ...	86 - 5488 - 314 ...	86 - 5488 - 315 ...	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
86 - 5391 - 259 ...	86 - 5391 - 260 ...	86 - 5391 - 261 ...	86 - 5391 - 316 ...	-	-	-	50	50	50	50	50	50	50	70.14	40.39	61.85	44.59	55.7	45.2	54.89	45.38	58.65	45.8	70.0
86 - 5664 - 259 ...	86 - 5664 - 260 ...	86 - 5664 - 261 ...	86 - 5664 - 316 ...	-	86 - 5664 - 314 ...	86 - 5664 - 315 ...	168.02	150.5	178.28	133.75	92.12	121.67	144.48	94.36	36.19	70.77	42.56	65.69	42.05	55.17	42.29	65.59	42.05	70.7
86 - 5665 - 259 ...	86 - 5665 - 260 ...	86 - 5665 - 261 ...	86 - 5665 - 316 ...	-	86 - 5665 - 314 ...	86 - 5665 - 315 ...	162.2	80.8	209.2	140.85	135.1	183.7	167.6	94.58	36.15	78.16	39.77	65.57	45.05	65.57	45.05	78.16	39.77	94.5
86 - 5433 - 259 ...	86 - 5433 - 260 ...	86 - 5433 - 261 ...	86 - 5433 - 316 ...	-	86 - 5433 - 314 ...	86 - 5433 - 315 ...	165.138	106.228	226.157	130.134	72.71	180.177	164.616	101.36	36.11	77.22	42.49	68.02	45.62	60	45.42	68.02	45.62	77.2
86 - 5608 - 259 ...	86 - 5608 - 260 ...	86 - 5608 - 261 ...	86 - 5608 - 316 ...	-	86 - 5608 - 314 ...	86 - 5608 - 315 ...	150.84	152.5	30.94	32.37	54.36	19.837	29.85	64.14	40.145	54.32	46.32	53.8	46.7	53.8	46.7	54.32	46.32	54.9
86 - 5555 - 259 ...	86 - 5555 - 260 ...	86 - 5555 - 261 ...	86 - 5555 - 316 ...	-	86 - 5555 - 314 ...	86 - 5555 - 315 ...	168.001	150.288	178.399	133.115	92.491	121.257	144.126	97.05	36.16	71.13	43.09	65.45	42.12	55.66	42.18	65.45	42.12	71.1

Online results submission

- many numerical values

	Z1	Z2	Z3	Z4	Z5	Z6	Z7
	148.33	155.88	202.12	164.35	180.91	30.29	185.19
	25.97	153.5	34.64	35.79	55.56	26.212	10.693
	0	0	0	0	0	0	0
	50	50	50	50	50	50	50

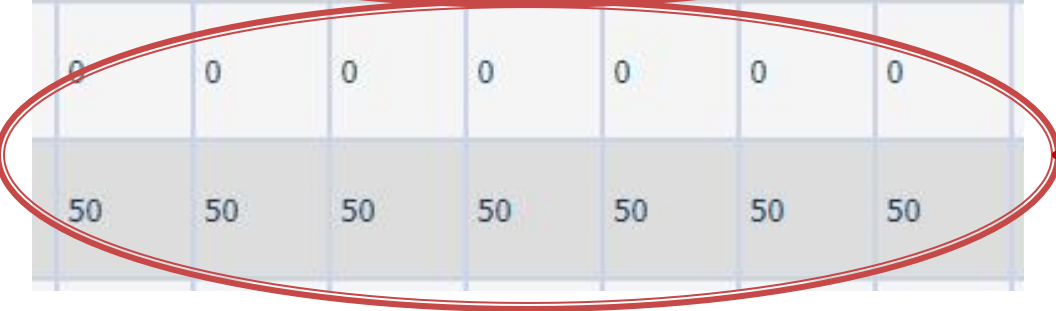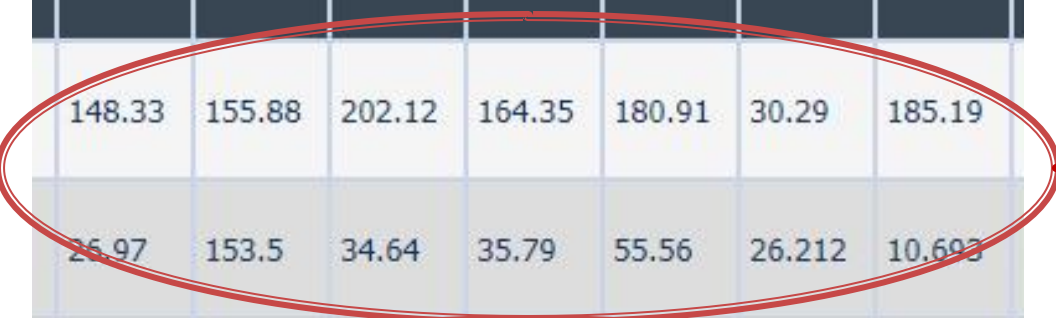

Online results submission


Grade = Quality of the work +
+ Quality of the submission

Recap

General theory

Microwave Network Analysis

Scattering matrix – S

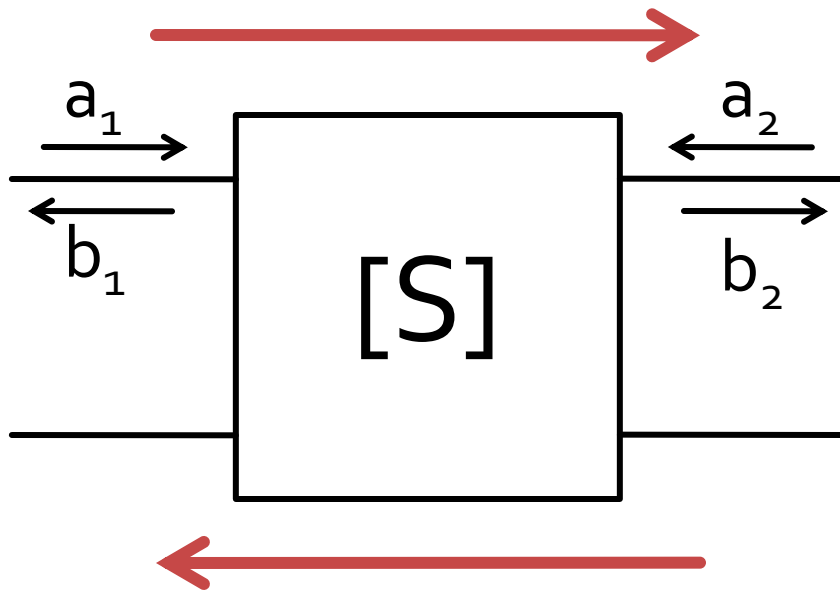

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$


$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- a, b
 - information about signal power **AND** signal phase
- S_{ij}
 - network effect (gain) over signal power **including** phase information

Impedance Matching

The Smith Chart

The Smith Chart

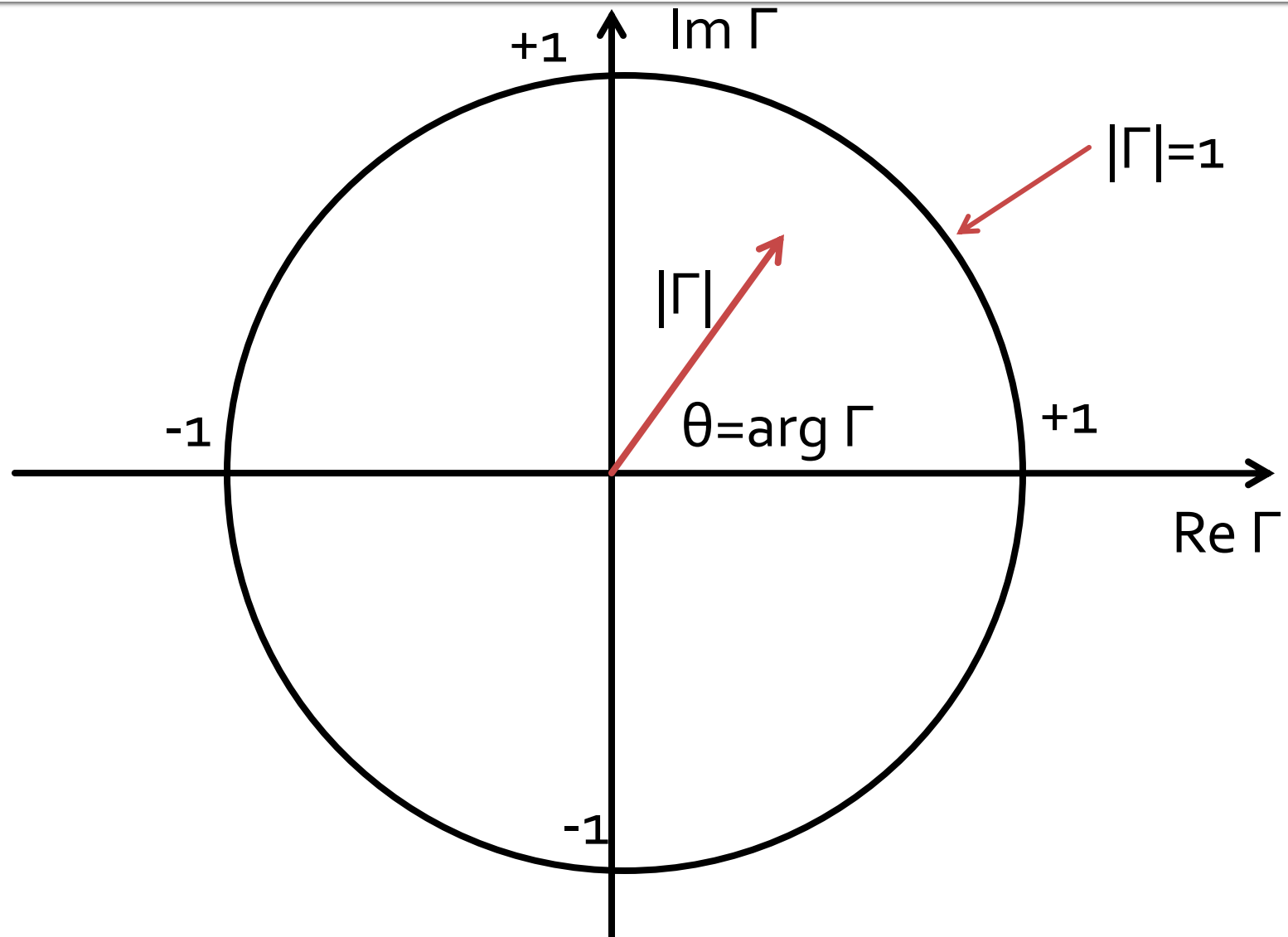



Impedance matching

Impedance Matching with lumped elements (L Networks)

Course Topics

- Transmission lines
- Impedance matching and tuning
- Directional couplers
- Power dividers
- Microwave amplifier design
- Microwave filters
- ~~Oscillators and mixers?~~

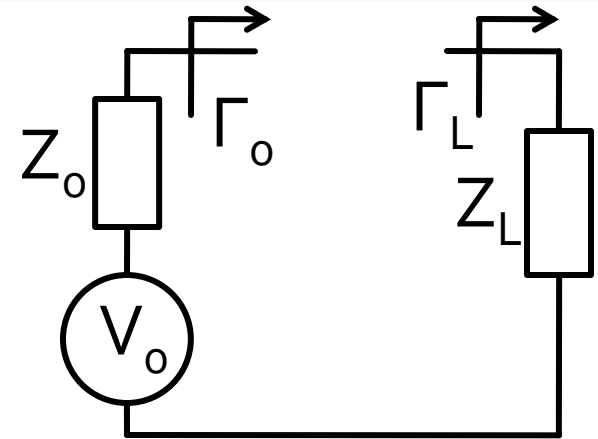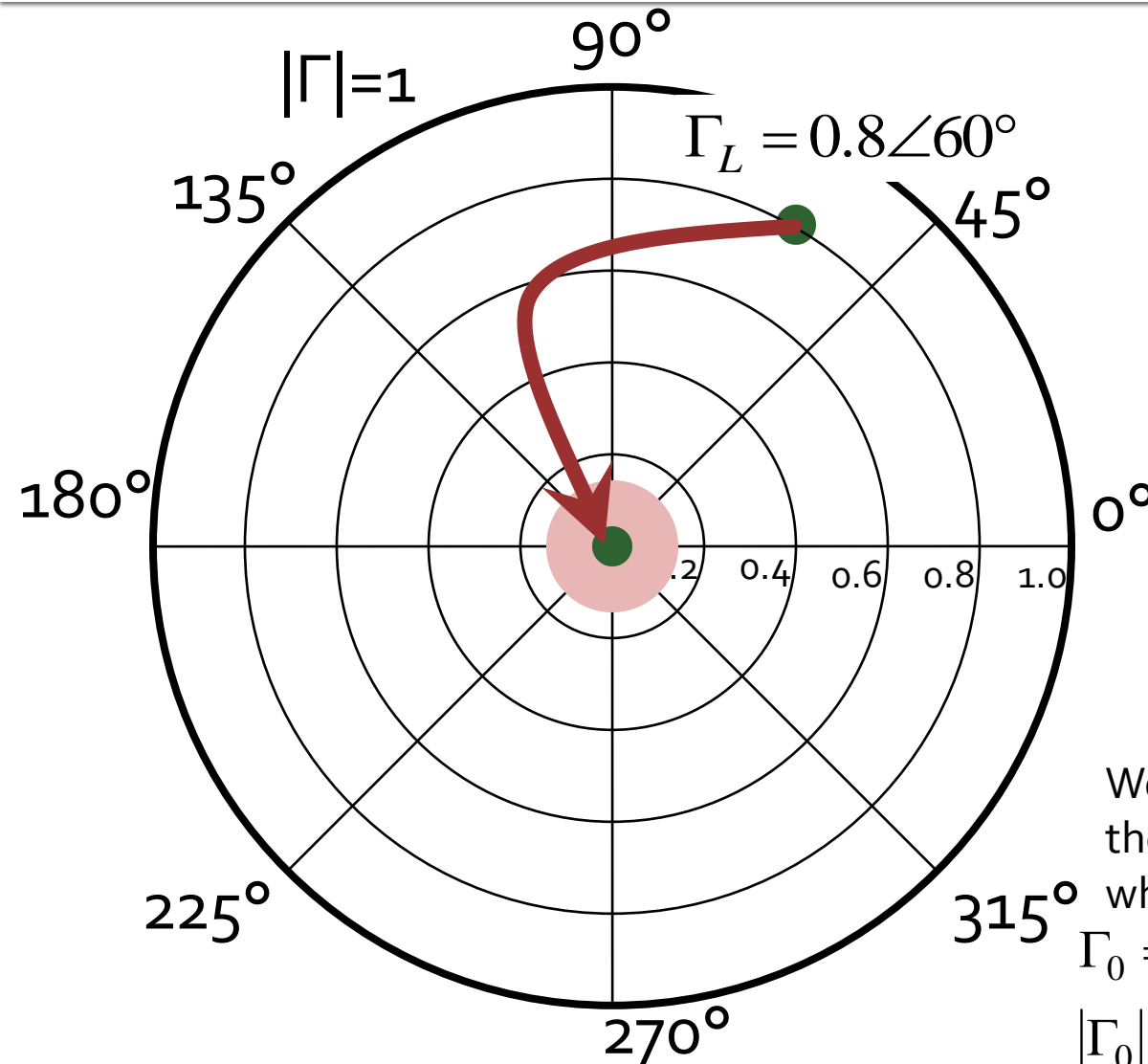The Smith Chart, reflection coefficient, impedance matching



Matching Z_L load to Z_o source.
We normalize Z_L over Z_o

$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

$$z_L = 0.429 + j \cdot 1.65$$



$$\Gamma_L = 0.8\angle 60^\circ$$

We must move the point denoting the reflection coefficient in the area where with a Z_o source we have:

$$\Gamma_o = 0 \quad \text{perfect match}$$

$$|\Gamma_o| \leq \Gamma_m \quad \text{"good enough" match}$$

The Smith Chart, matching, $Z_L = Z_o$

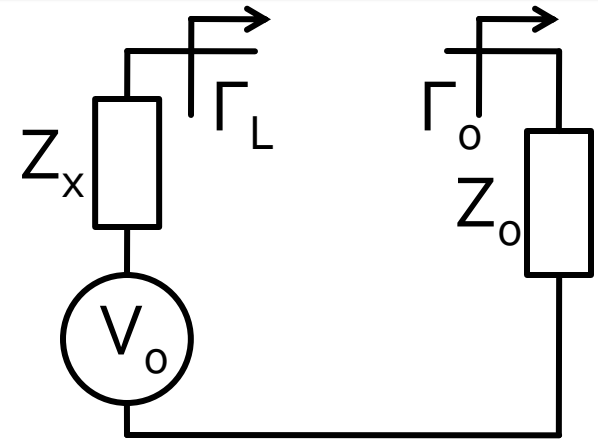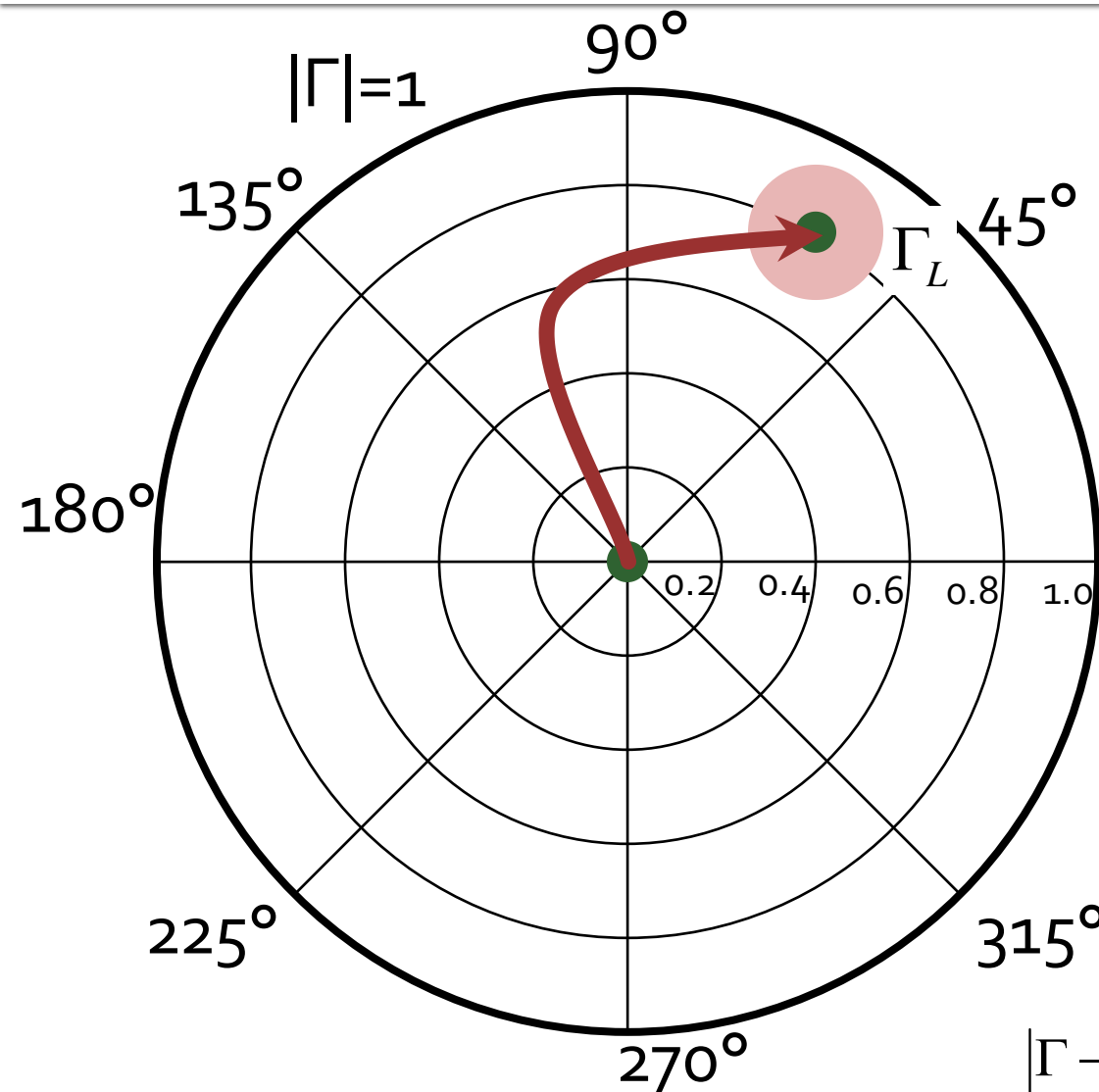

0° The source (eg. the transistor) having Z_x needs to see a certain reflection coefficient Γ_L towards the load Z_o

The matching circuit must move the point denoting the reflection coefficient in the area where for a Z_o load ($\Gamma_o=0$) we see towards it:


$\Gamma = \Gamma_L$ perfect match

$|\Gamma - \Gamma_L| \leq \Gamma_m$ "good enough" match



The Smith Chart, matching ,

$Z_L \neq Z_o, Z_L = Z_o$

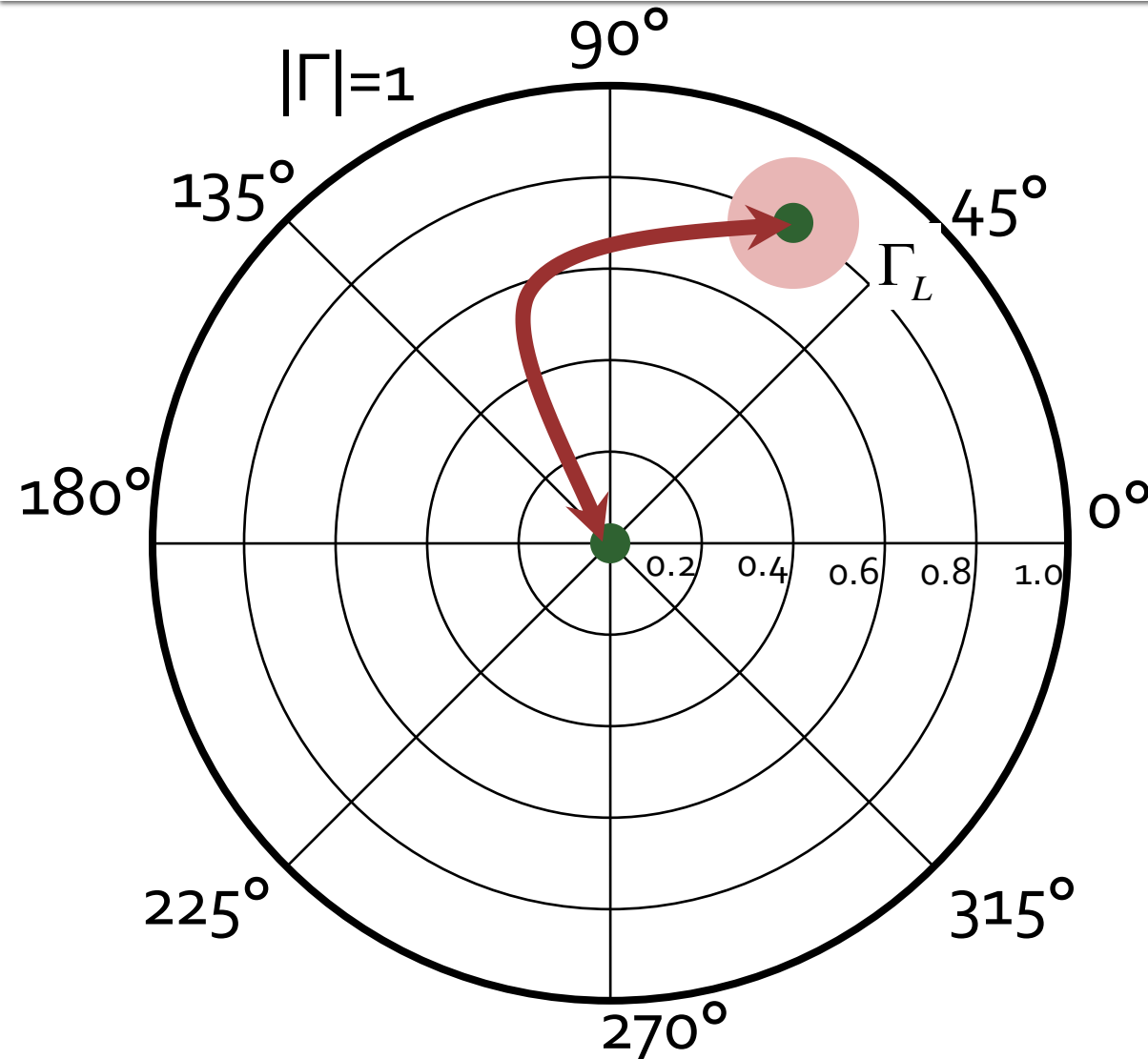


- The matching sections needed to move
 - Γ_L in Γ_o
 - Γ_o in Γ_L
- are **identical**. They differ only by the **order** in which the elements are introduced into the matching circuit
- As a result, we can use in match design the same:
 - **methods**
 - **formulae**

Impedance Matching


Impedance Matching with Stubs

Smith chart, $r=1$ and $g=1$

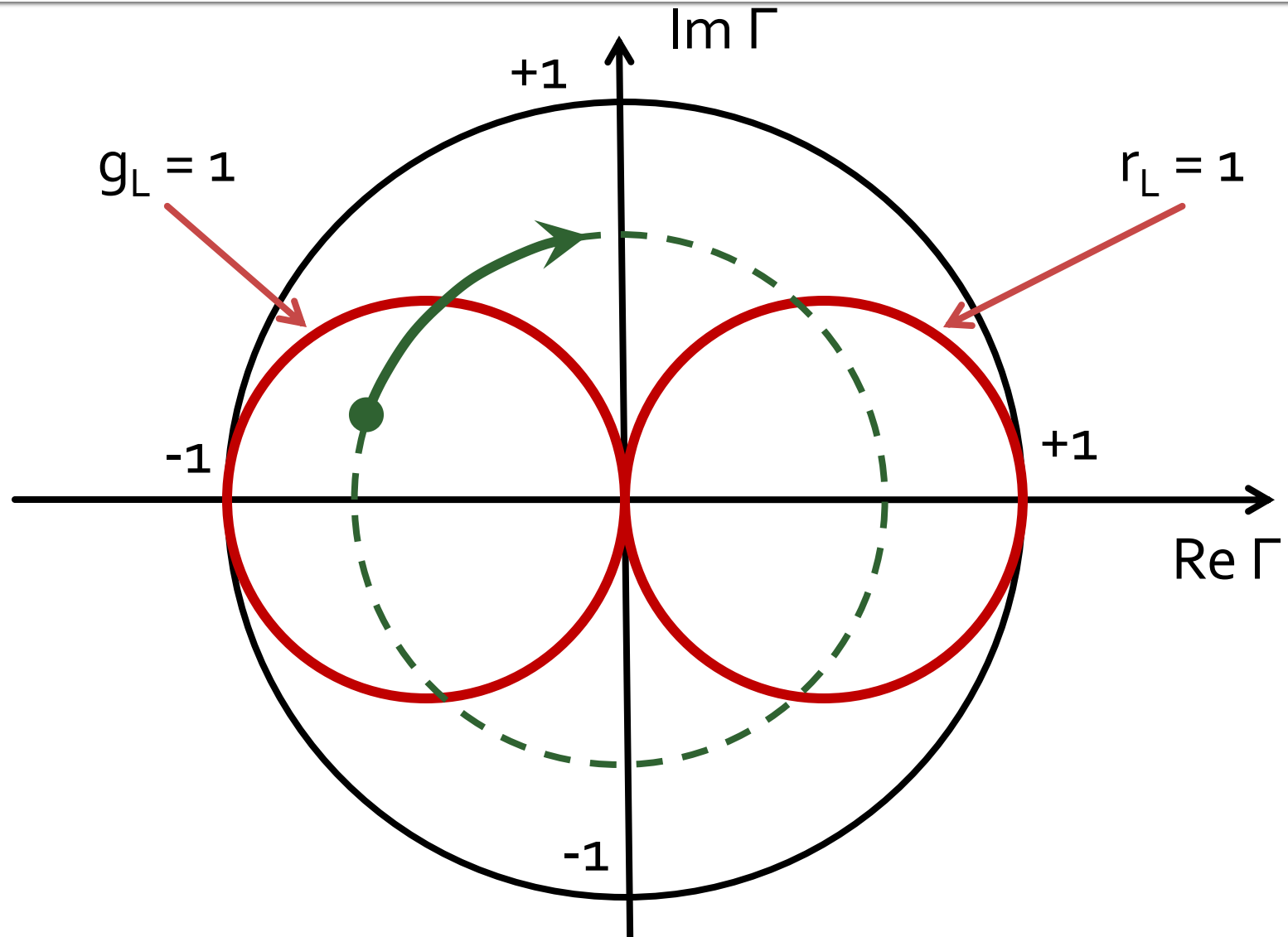

Case 1, Shunt Stub

- Shunt Stub

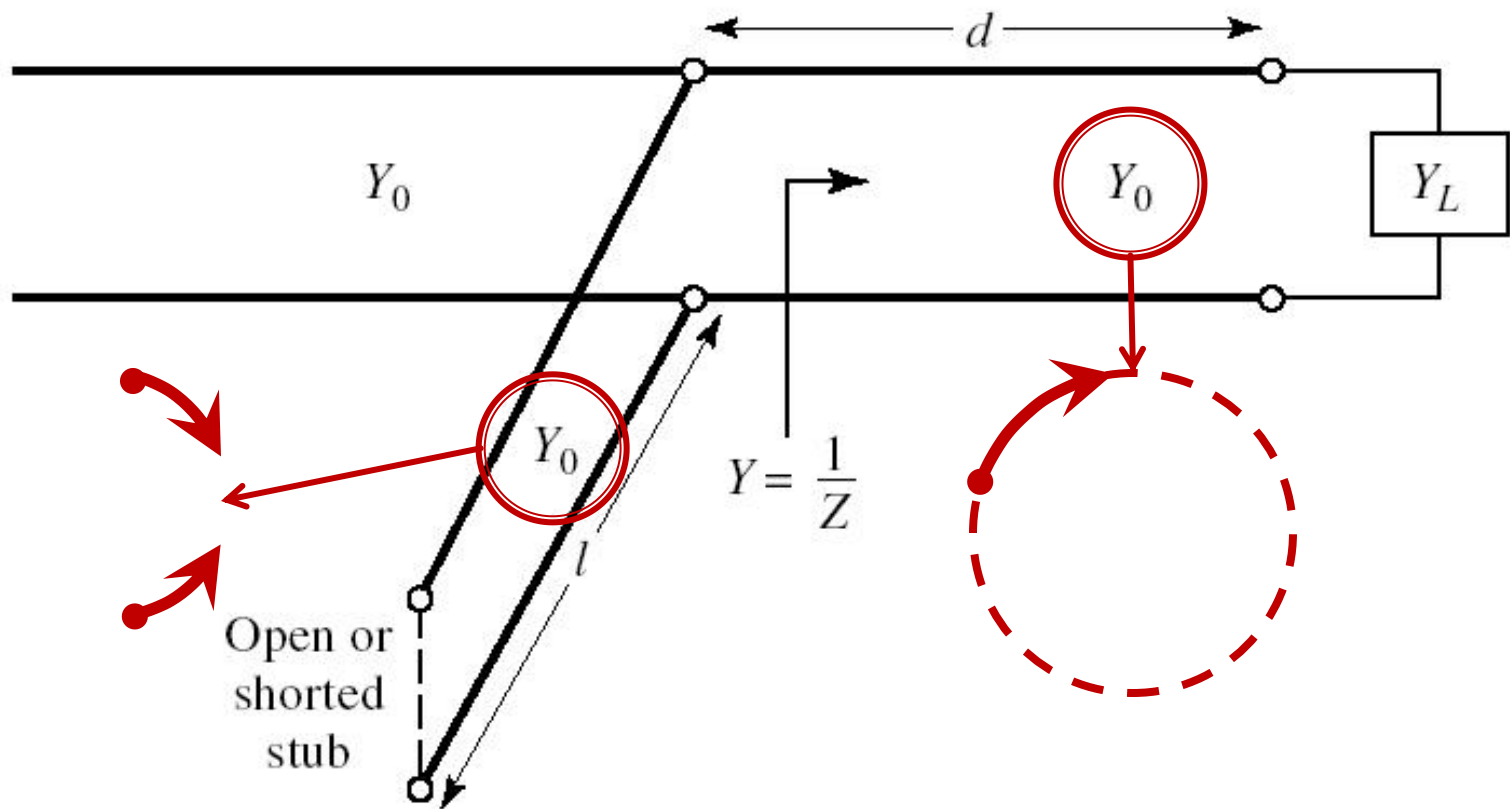

Analytical solution, usage

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = 0.593 \angle 46.85^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ \quad \cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **"+" solution** 

$$(46.85^\circ + 2\theta) = +126.35^\circ \quad \theta = +39.7^\circ \quad \text{Im } y_s = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.472$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_s) = -55.8^\circ (+180^\circ) \rightarrow \theta_{sp} = 124.2^\circ$$

- **"-" solution** 


$$(46.85^\circ + 2\theta) = -126.35^\circ \quad \theta = -86.6^\circ (+180^\circ) \rightarrow \theta = 93.4^\circ$$

$$\text{Im } y_s = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +1.472 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_s) = 55.8^\circ$$

Microwave Amplifiers

Power / Matching

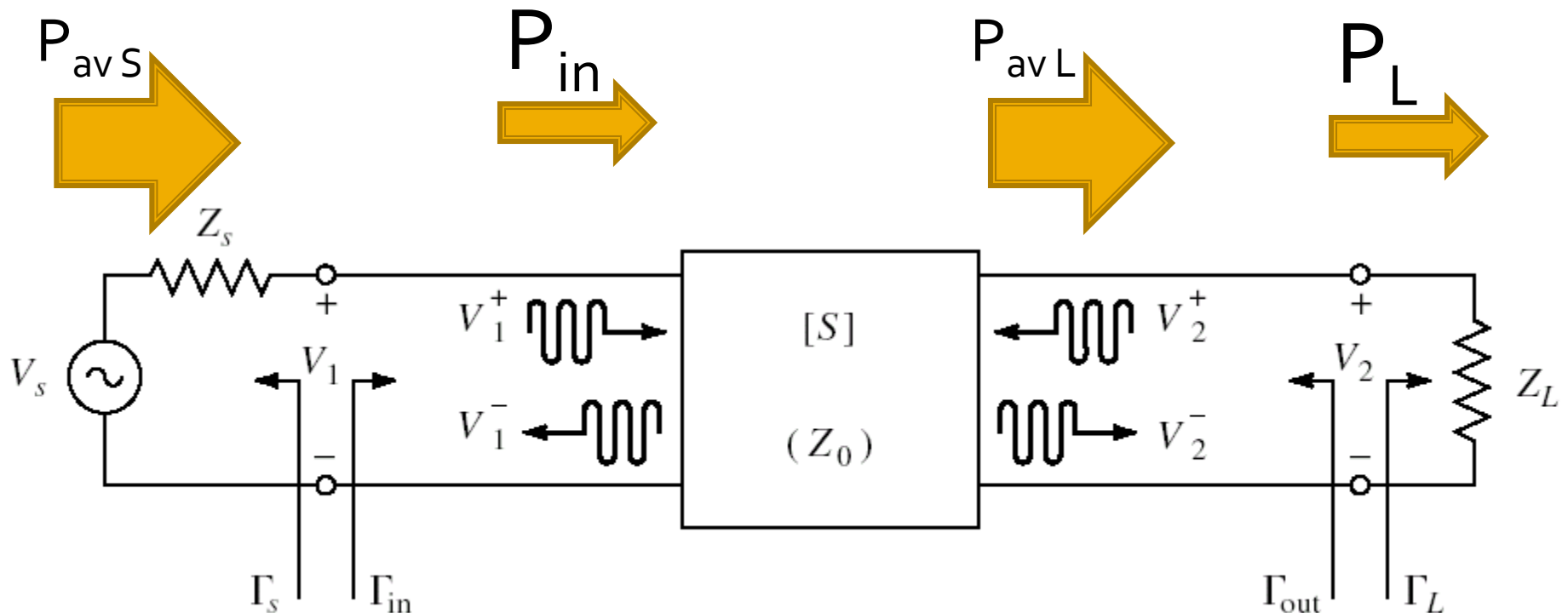
- Two ports in which matching influences the power transfer



Microwave Filters

Assignment

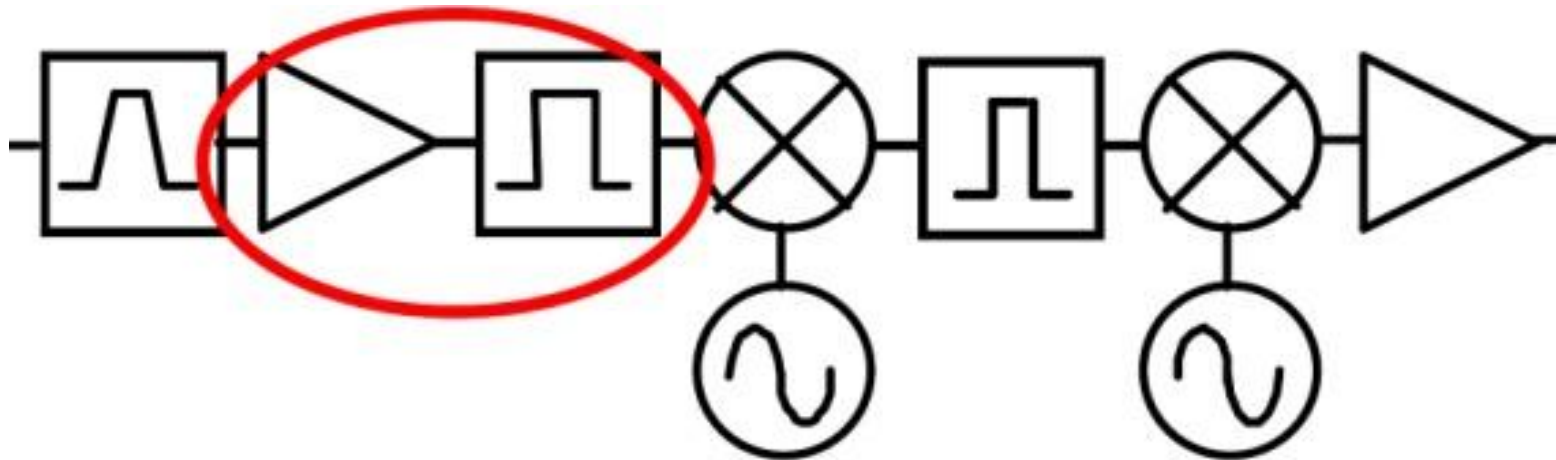- this structure is frequently encountered in radiocommunication systems



Insertion loss method

$$P_{LR} = \frac{P_S}{P_L} = \frac{1}{1 - |\Gamma(\omega)|^2}$$

- $|\Gamma(\omega)|^2$ is an even function of ω

$$|\Gamma(\omega)|^2 = \frac{M(\omega^2)}{M(\omega^2) + N(\omega^2)}$$

$$P_{LR} = 1 + \frac{M(\omega^2)}{N(\omega^2)}$$

- Choosing M and N polynomials appropriately leads to a filter with a completely specified frequency response

Insertion loss method

- We control the power loss ratio/attenuation introduced by the filter:
 - in the passband (pass all frequencies)
 - in the stopband (reject all frequencies)


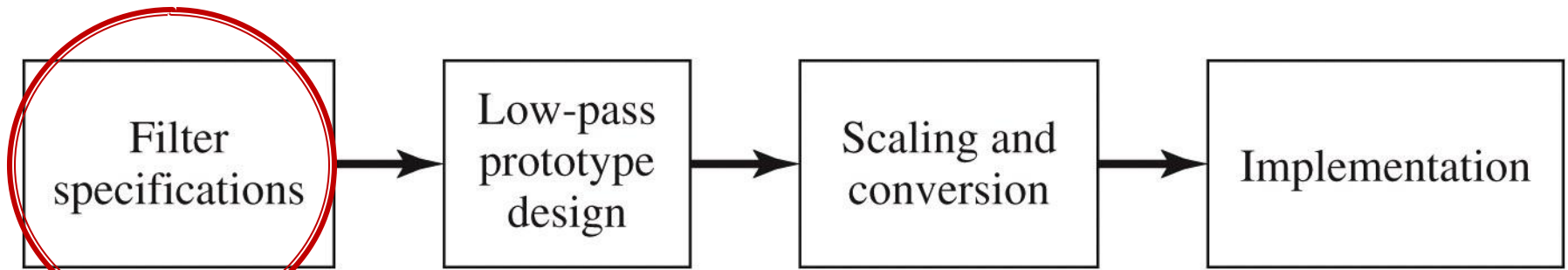


Figure 8.23

© John Wiley & Sons, Inc. All rights reserved.

Filter specifications

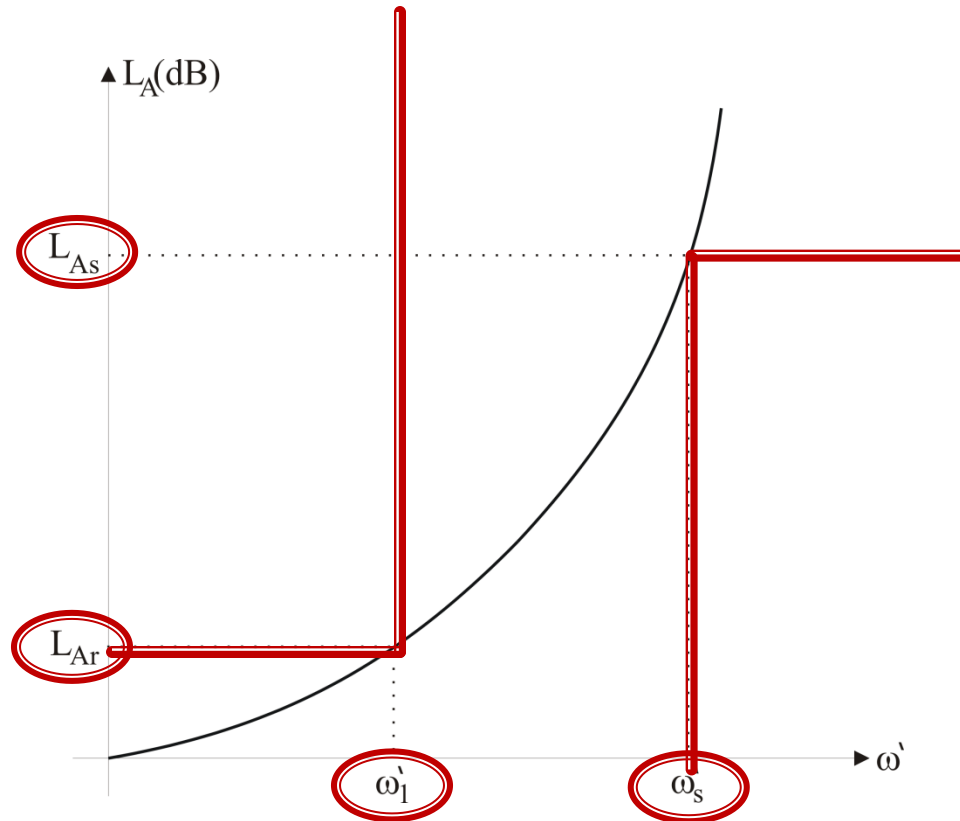- Attenuation
 - in passband
 - in stopband
 - most often in **dB**
- Frequency range
 - passband
 - stopband
 - cutoff frequency ω_1'
usually normalized
(= **1**)



Insertion loss method

- We choose the right polynomials to design an **low-pass** filter (prototype)
- The low-pass prototype are then converted to the desired other types of filters
 - low-pass, high-pass, bandpass, or bandstop

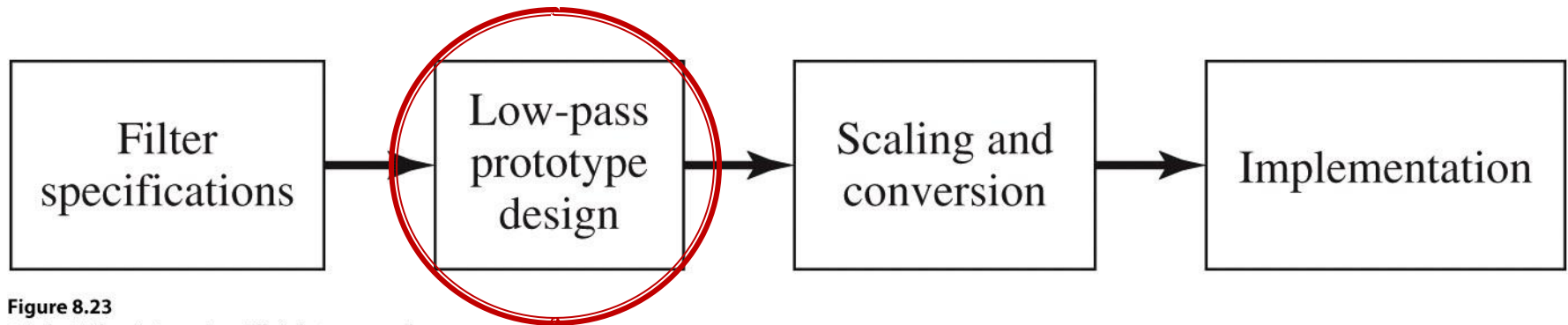


Figure 8.23
© John Wiley & Sons, Inc. All rights reserved.

Maximally Flat/Equal ripple LPF Prototype


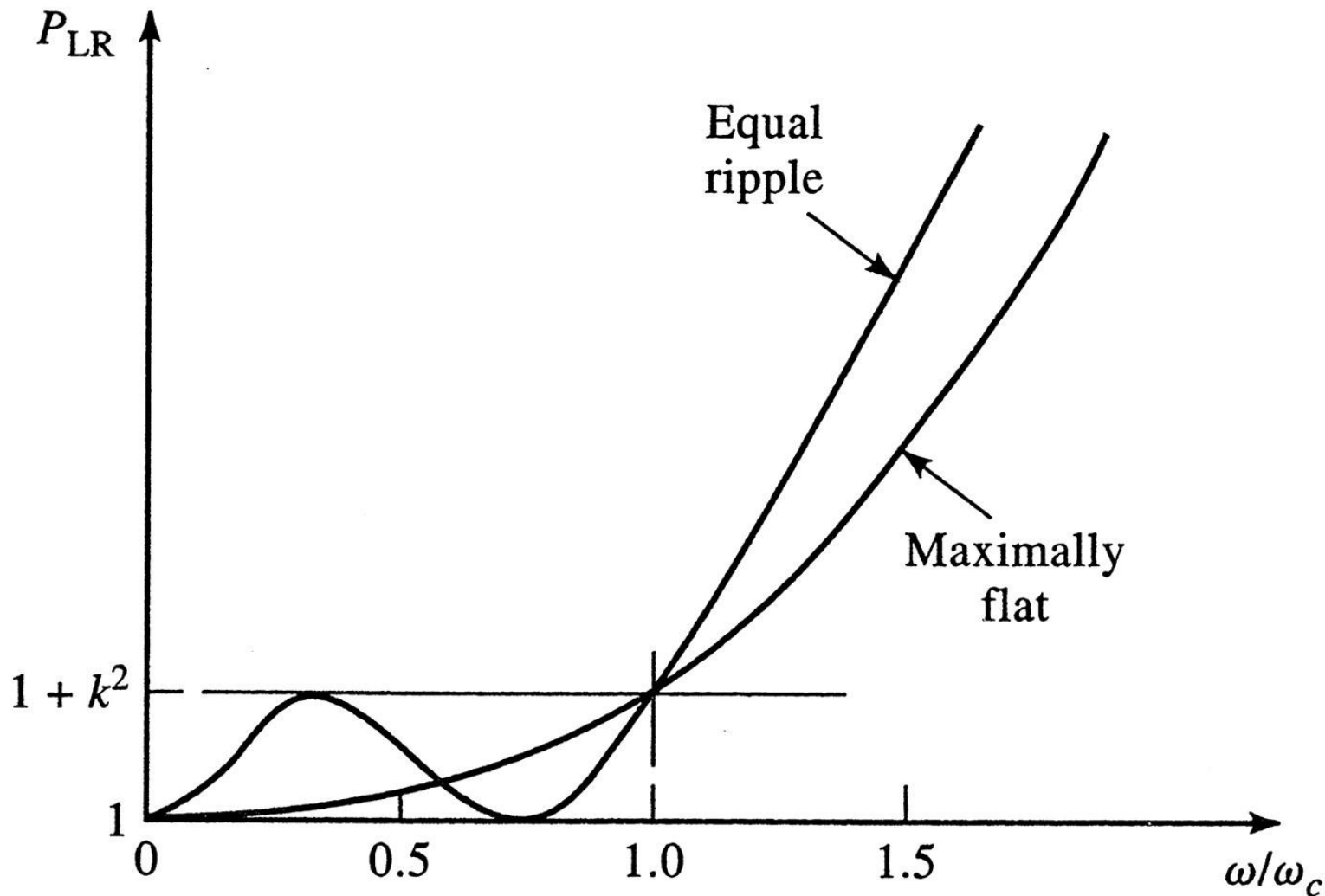



Figure 8.21

Maximally flat filter prototypes

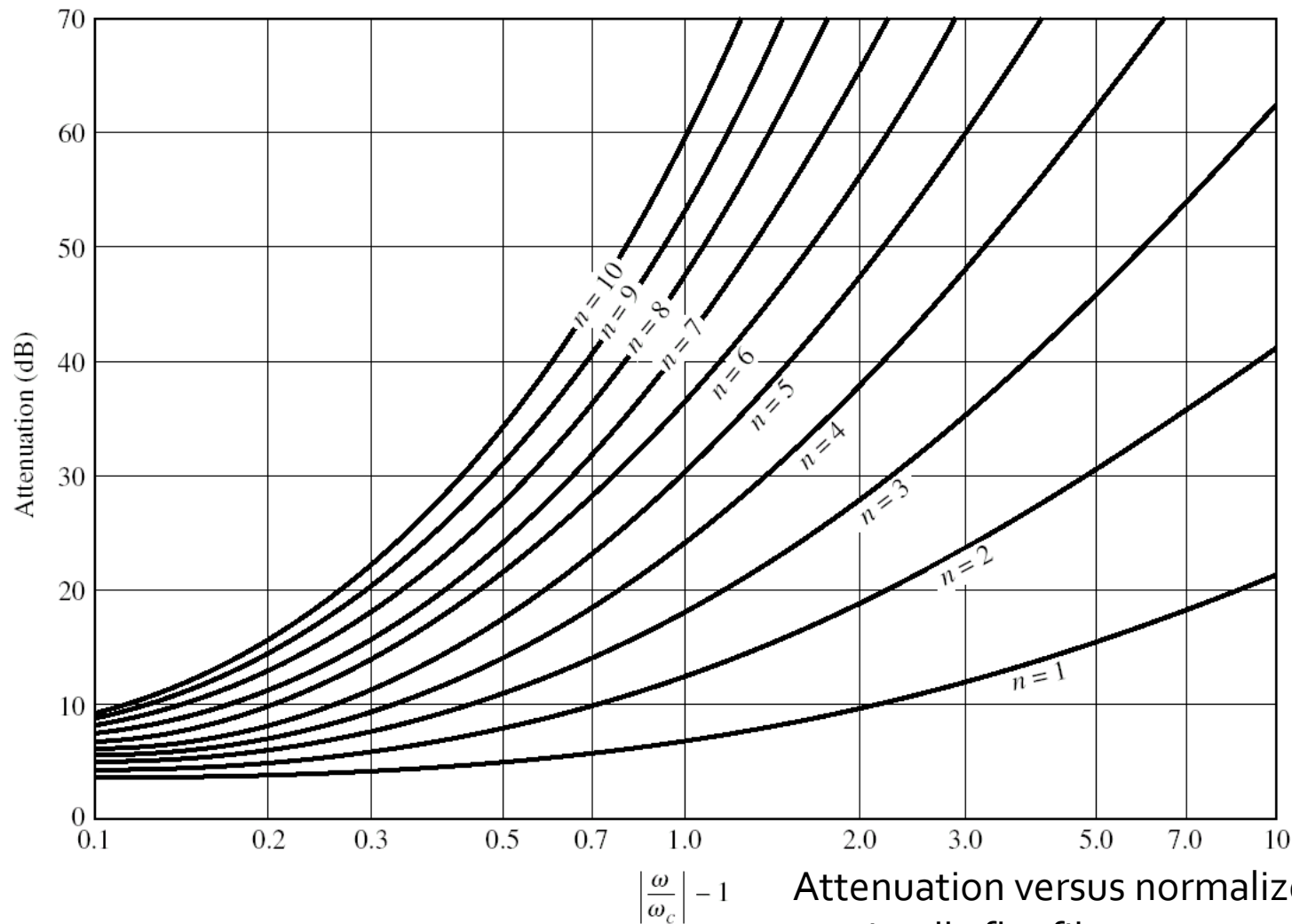


Attenuation versus normalized frequency for maximally flat filter prototypes

Prototype Filters

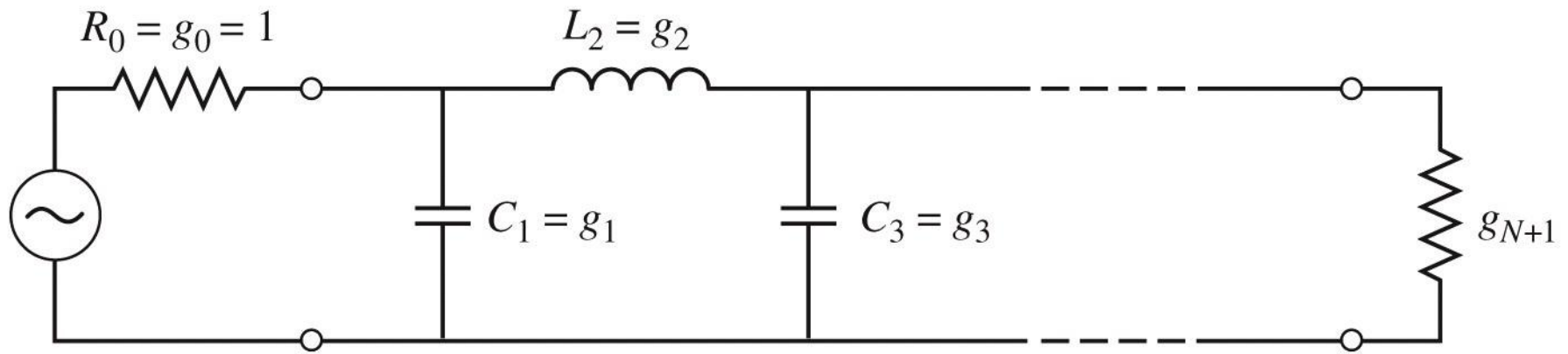

(a)

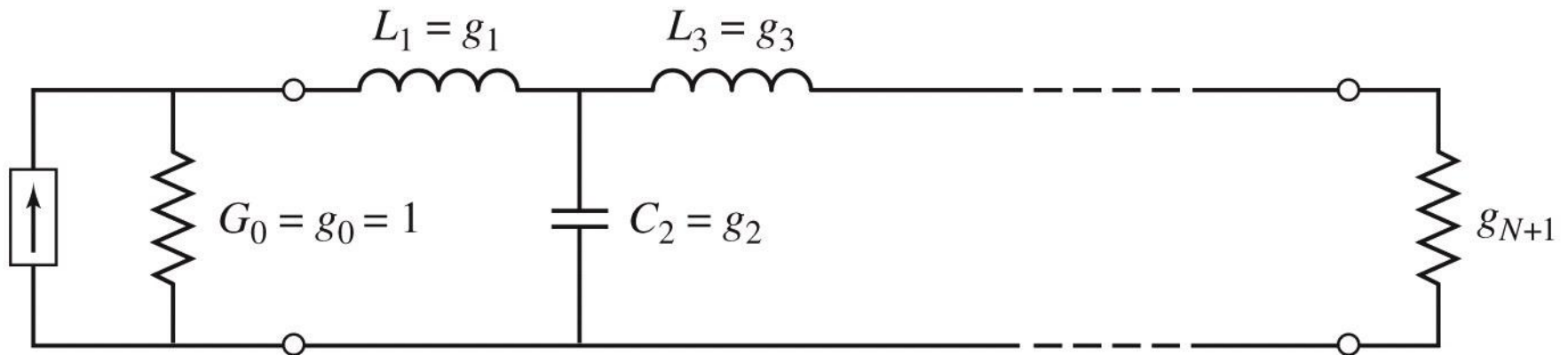

(b)

Prototype Filters

- Prototype filters are:
 - Low-Pass Filters (LPF)
 - cutoff frequency $\omega_o = 1 \text{ rad/s}$ ($f_o = 0.159 \text{ Hz}$)
 - connected to a source with $R = 1\Omega$
- The number of reactive elements (L/C) is the order of the filter (N)
- Reactive elements are alternated: series L / shunt C
- There two prototypes with the same response, a prototype beginning with a shunt C element, and a prototype beginning with a series L element

Maximally Flat LPF Prototype

TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ($g_0 = 1$, $\omega_c = 1$, $N = 1$ to 10)

N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

Example

- Design a **3rd order** bandpass filter with **0.5 dB ripples** in passband. The center frequency of the filter should be 1 GHz. The fractional bandwidth of the passband should be 10%, and the impedance 50Ω.

LPF Prototype


- 0.5dB equal-ripple table or design formulas:

- $g_1 = 1.5963 = L_1/C_3,$

- $g_2 = 1.0967 = C_2/L_4,$



- $g_3 = 1.5963 = L_3/C_5,$

- $g_4 = 1.000 = R_L$

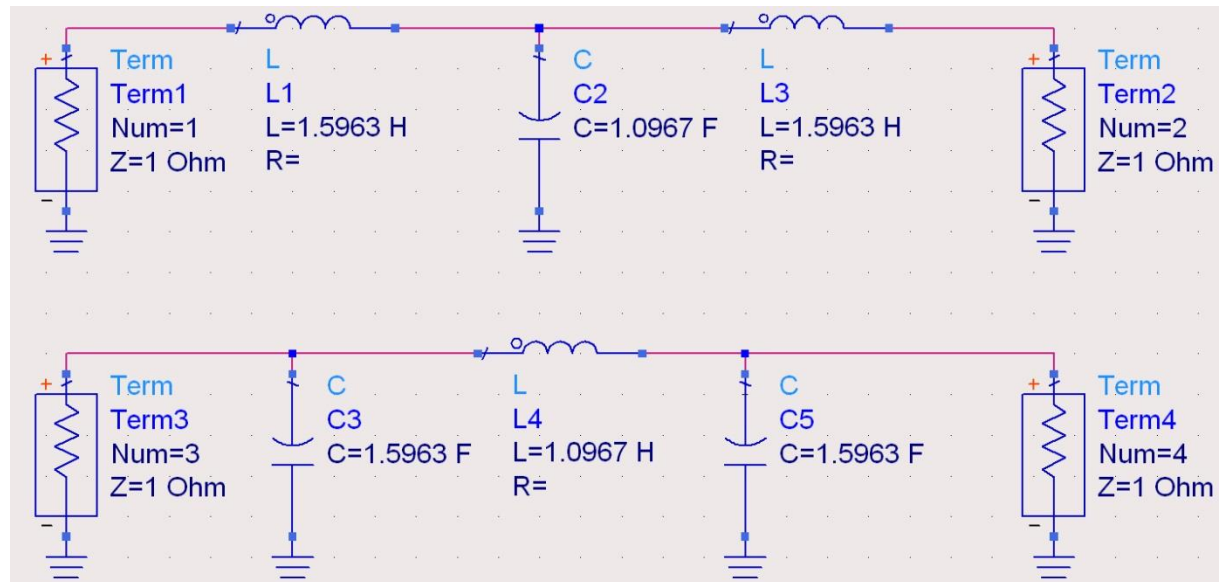

LPF Prototype

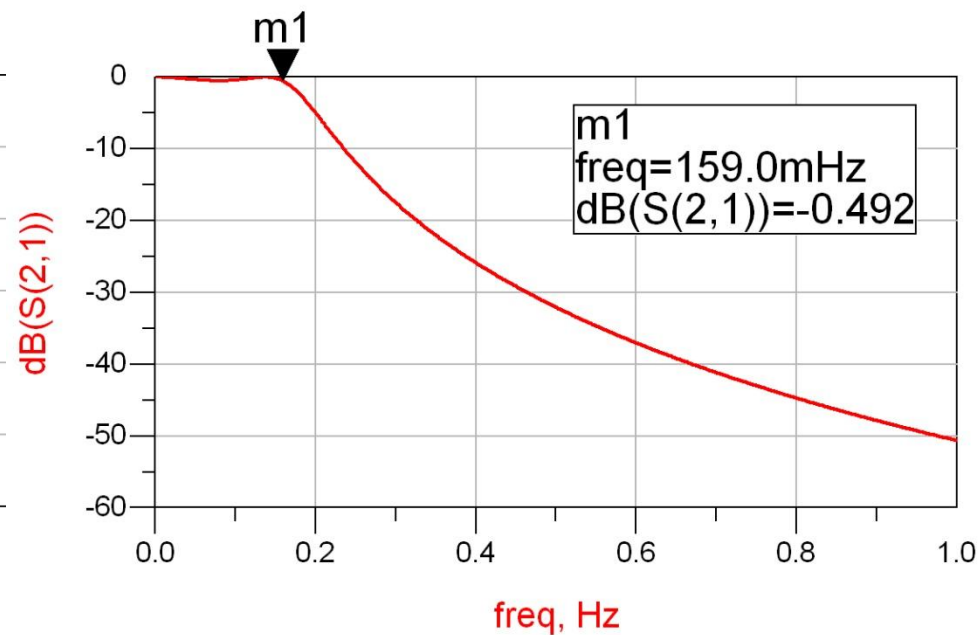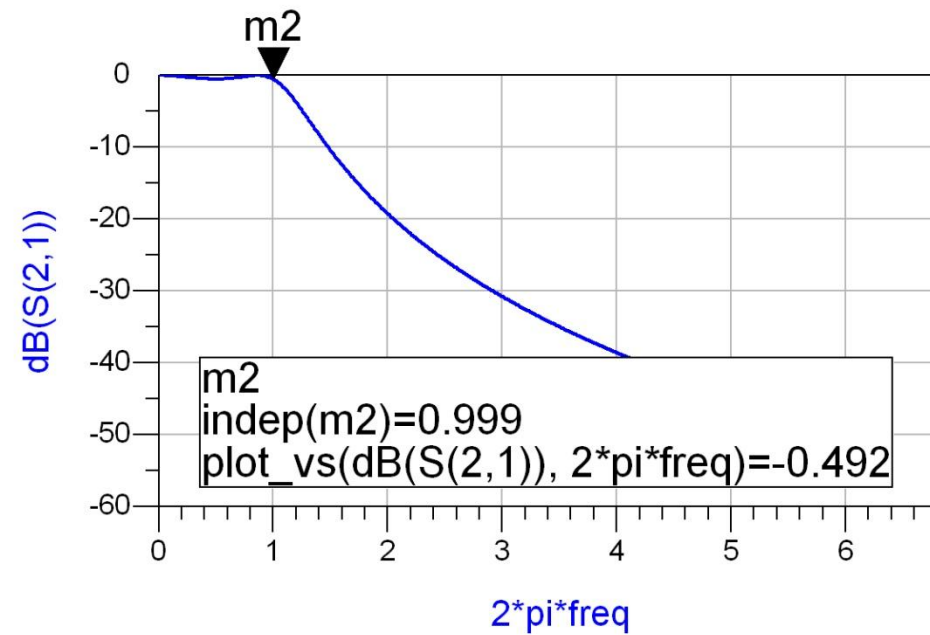- $\omega_o = 1 \text{ rad/s}$ ($f_o = \omega_o / 2\pi = 0.159 \text{ Hz}$)



Continue

Impedance and Frequency Scaling

- After computing prototype filter's elements:
 - Low-Pass Filters (LPF)
 - cutoff frequency $\omega_o = 1 \text{ rad/s}$ ($f_o = 0.159 \text{ Hz}$)
 - connected to a source with $R = 1\Omega$
- component values can be scaled in terms of impedance and frequency

Impedance and Frequency Scaling

- LPF Prototype is only used as an intermediate step
 - Low-Pass Filter (LPF)
 - cutoff frequency $\omega_o = 1 \text{ rad/s}$ ($f_o = 0.159 \text{ Hz}$)
 - connected to a source with $R = 1\Omega$

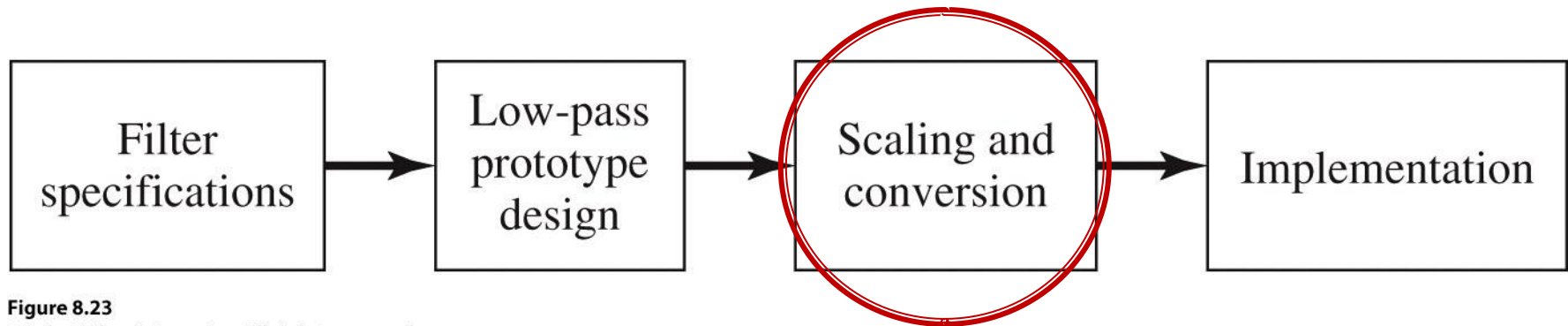


Figure 8.23

Impedance Scaling

- To design a filter which will work with a source resistance of R_0 we multiply all the impedances of the prototype design by R_0 (" $'$ " denotes scaled values)

$$R'_s = R_0 \cdot (R_s = 1)$$


$$R'_L = R_0 \cdot R_L$$

$$L' = R_0 \cdot L$$

$$C' = \frac{C}{R_0}$$

Frequency Scaling

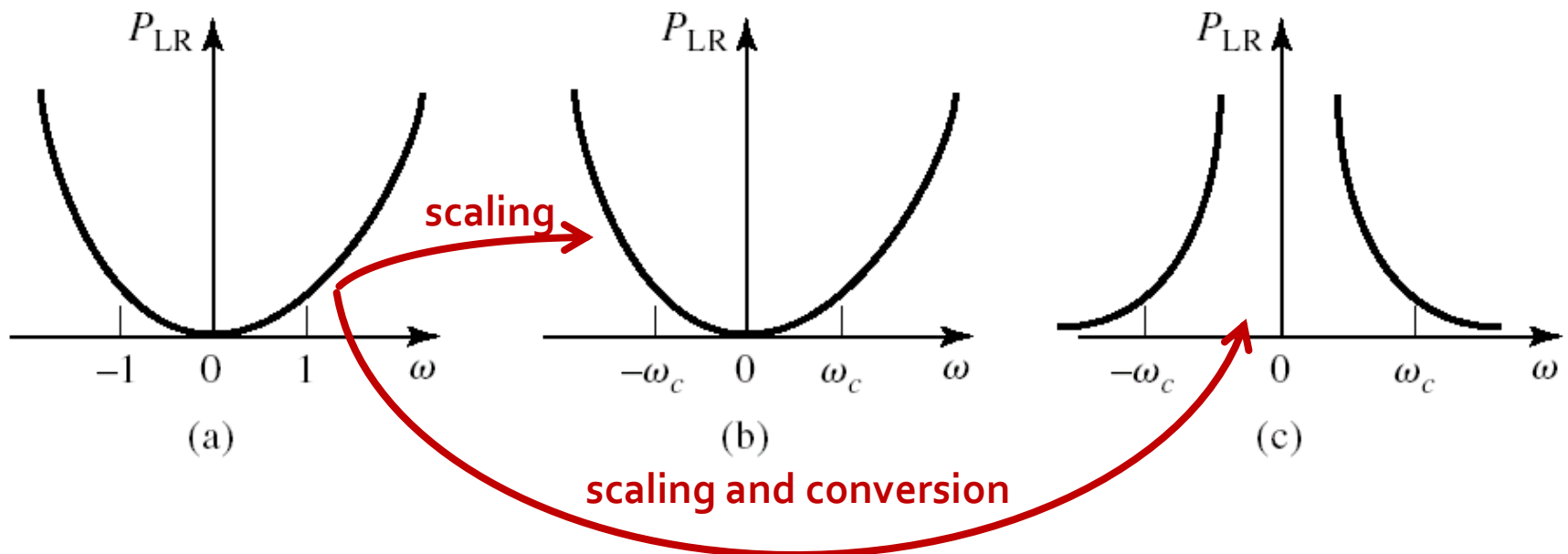
- changing the cutoff frequency – (fig. b)
- changing the type (for example LPF \rightarrow HPF – fig. c) requires also conversion



Frequency Scaling

- To change the cutoff frequency of a low-pass prototype from unity to ω_c we apply a variable substitution
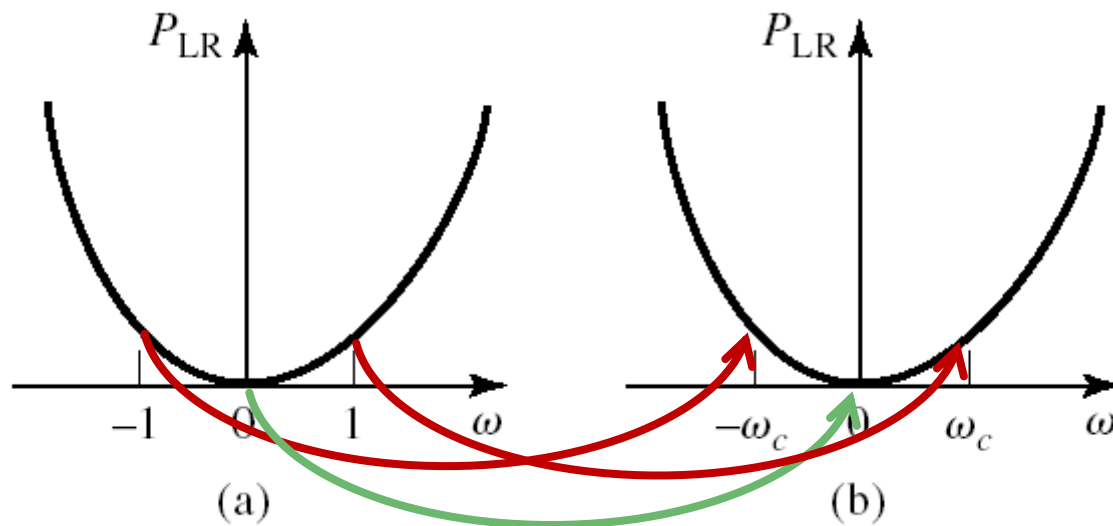
$$\omega \leftarrow \frac{\omega}{\omega_c}$$



Frequency Scaling

- To change the cutoff frequency of a low-pass prototype we apply a variable substitution:

$$\omega \leftarrow \frac{\omega}{\omega_c}$$

- Equivalent to the widening of the power loss filter response

$$P'_{LR}(\omega) = P_{LR}\left(\frac{\omega}{\omega_c}\right)$$

$$j \cdot X_k = j \cdot \frac{\omega}{\omega_c} \cdot L_k = j \cdot \omega \cdot L'_k$$

$$j \cdot B_k = j \cdot \frac{\omega}{\omega_c} \cdot C_k = j \cdot \omega \cdot C'_k$$

Frequency Scaling LPF \rightarrow LPF

- New element values for frequency scaling:

$$L'_k = \frac{L_k}{\omega_c} \quad C'_k = \frac{C_k}{\omega_c}$$


- When both impedance and frequency scaling are required:

$$L'_k = \frac{R_0 \cdot L_k}{\omega_c} \quad C'_k = \frac{C_k}{R_0 \cdot \omega_c}$$

Low-pass to high-pass transformation LPF \rightarrow HPF

- Variable substitution for LPF \rightarrow HPF:
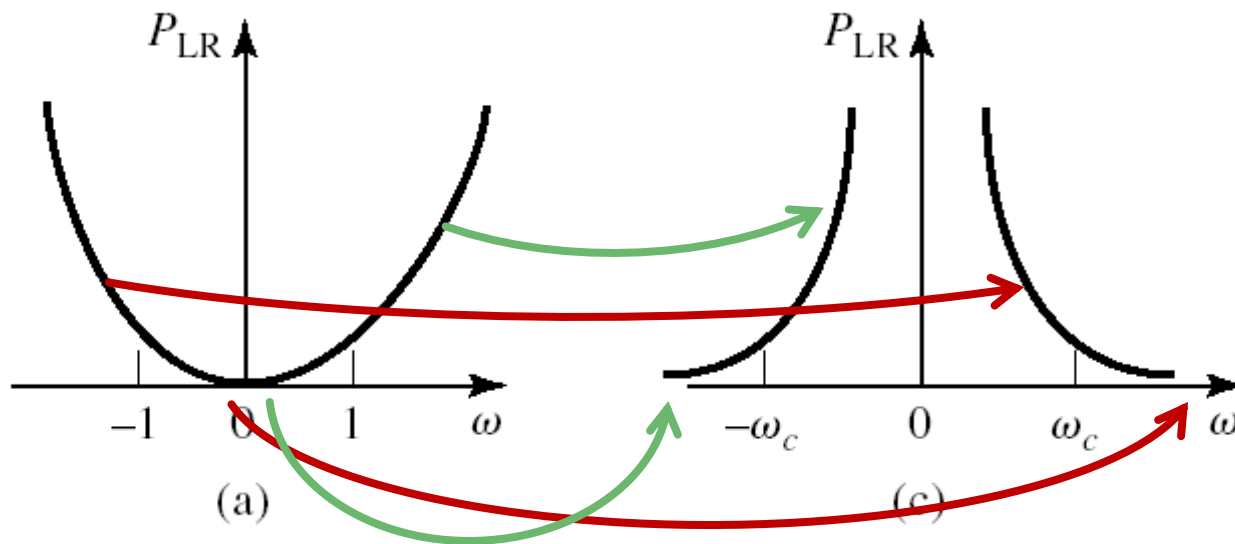
$$\omega \leftarrow -\frac{\omega_c}{\omega}$$



High-pass transformation LPF \rightarrow HPF

- Variable substitution for LPF \rightarrow HPF :

$$\omega \leftarrow -\frac{\omega_c}{\omega}$$
$$j \cdot X_k = -j \cdot \frac{\omega_c}{\omega} \cdot L_k = \frac{1}{j \cdot \omega \cdot C'_k} \quad j \cdot B_k = -j \cdot \frac{\omega_c}{\omega} \cdot C_k = \frac{1}{j \cdot \omega \cdot L'_k}$$

- Impedance scaling can be included

$$C'_k = \frac{1}{R_0 \cdot \omega_c \cdot L_k} \quad L'_k = \frac{R_0}{\omega_c \cdot C_k}$$

- In the schematic series **inductors** must be replaced with series **capacitors**, and shunt **capacitors** must be replaced with shunt **inductors**

Bandpass Transformation LPF \rightarrow BPF

- Variable substitution for LPF \rightarrow BPF:

$$\omega \leftarrow \frac{\omega_0}{\omega_2 - \omega_1} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)$$


- where we use the fractional bandwidth of the passband and the center frequency

$$\Delta = \frac{\omega_2 - \omega_1}{\omega_0}$$

$$\omega_0 = \sqrt{\omega_1 \cdot \omega_2}$$

Bandpass Transformation LPF \rightarrow BPF

$$\begin{aligned}\omega = \omega_0 &\rightarrow \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega_0}{\omega_0} - \frac{\omega_0}{\omega_0} \right) = 0 & \omega = -\omega_0 &\rightarrow \frac{1}{\Delta} \left(\frac{-\omega_0}{\omega_0} - \frac{\omega_0}{-\omega_0} \right) = 0 \\ \omega = \omega_1 &\rightarrow \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega_1^2 - \omega_0^2}{\omega_0 \cdot \omega_1} \right) = -1 \\ \omega = \omega_2 &\rightarrow \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega_2^2 - \omega_0^2}{\omega_0 \cdot \omega_2} \right) = 1\end{aligned}$$

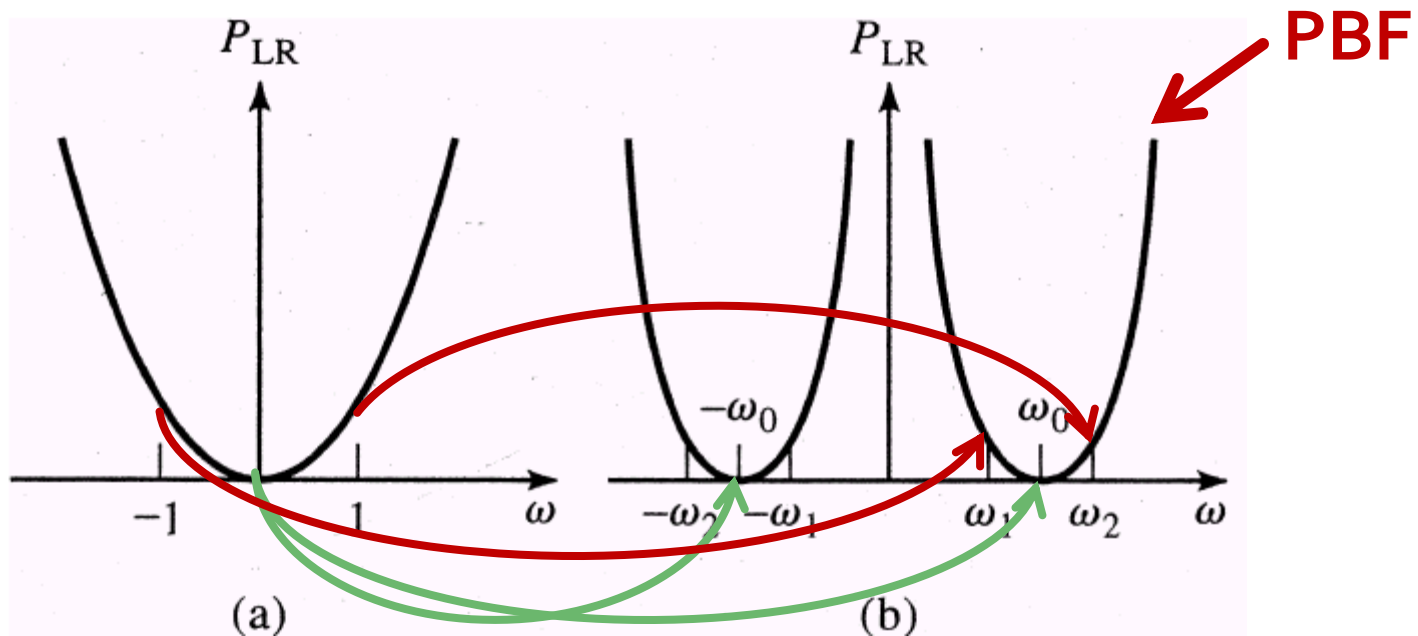

Bandpass Transformation LPF \rightarrow BPF

$$j \cdot X_k = \frac{j}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \cdot L_k = j \cdot \frac{\omega \cdot L_k}{\Delta \cdot \omega_0} - j \cdot \frac{\omega_0 \cdot L_k}{\Delta \cdot \omega} = j \cdot \omega \cdot L'_k - j \frac{1}{\omega \cdot C'_k}$$
$$j \cdot B_k = \frac{j}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \cdot C_k = j \cdot \frac{\omega \cdot C_k}{\Delta \cdot \omega_0} - j \cdot \frac{\omega_0 \cdot C_k}{\Delta \cdot \omega} = j \cdot \omega \cdot C'_k - j \frac{1}{\omega \cdot L'_k}$$

- A series **inductor** in the prototype filter is transformed to a **series LC** circuit **in series**



$$L'_k = \frac{L_k}{\Delta \cdot \omega_0} \quad C'_k = \frac{\Delta}{\omega_0 \cdot L_k}$$

- A shunt **capacitor** in the prototype filter is transformed to a **shunt LC** circuit **in parallel**

$$L'_k = \frac{\Delta}{C_k \cdot \omega_0} \quad C'_k = \frac{C_k}{\omega_0 \cdot \Delta}$$

Bandstop Transformation LPF \rightarrow BSF
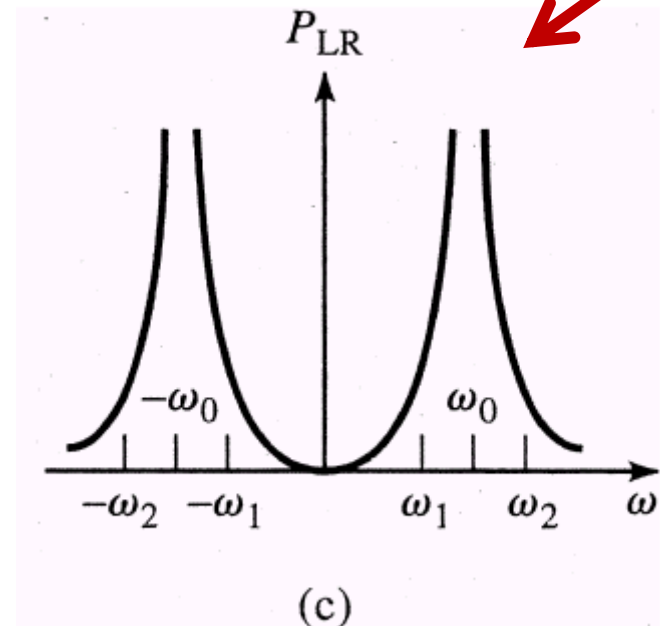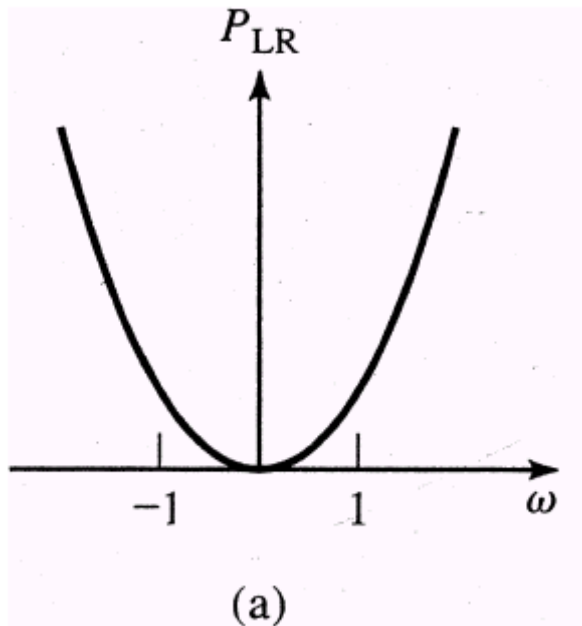
$$\omega \leftarrow -\Delta \cdot \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^{-1} \quad \omega = \omega_0 \rightarrow \frac{-\Delta}{\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)} = \frac{-\Delta}{\left(\frac{\omega_0}{\omega_0} - \frac{\omega_0}{\omega_0} \right)} \rightarrow \pm\infty$$



BSF

Bandstop Transformation LPF \rightarrow BSF

$$\omega \leftarrow -\Delta \cdot \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^{-1}$$

- A series **inductor** in the prototype filter is transformed to a **shunt LC** circuit **in series**

$$L'_k = \frac{\Delta \cdot L_k}{\omega_0} \quad C'_k = \frac{1}{\omega_0 \cdot \Delta \cdot L_k}$$

- A shunt **capacitor** in the prototype filter is transformed to a **series LC** circuit **in parallel**

$$L'_k = \frac{1}{\Delta \cdot \omega_0 \cdot C_k} \quad C'_k = \frac{\Delta \cdot C_k}{\omega_0}$$

Summary of Prototype Filter Transformations


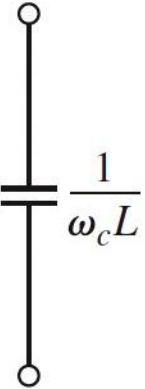
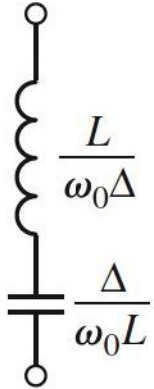
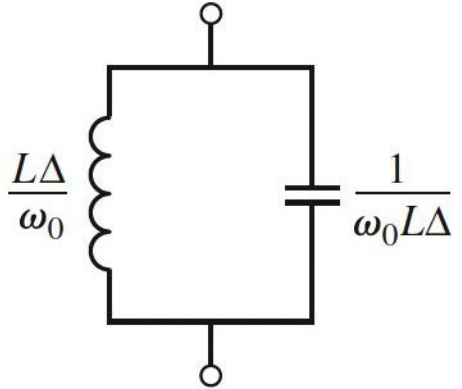
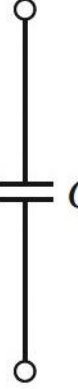
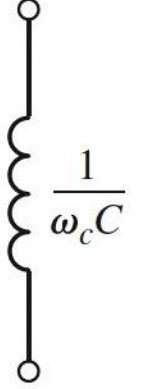
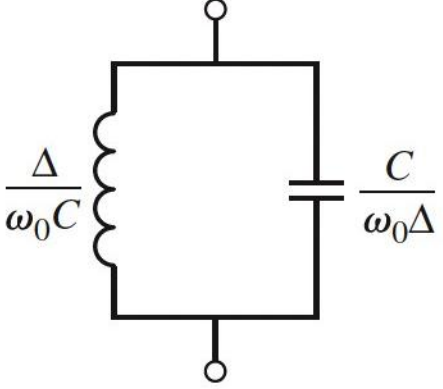
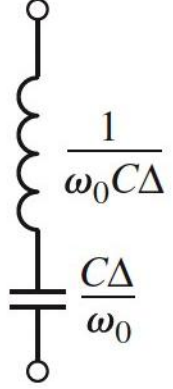
Low-pass	High-pass	Bandpass	Bandstop
			
			

Table 8.6

Example

- Design a 3rd order **bandpass** filter with 0.5 dB ripples in passband. The **center frequency** of the filter should be 1 GHz. The **fractional bandwidth** of the passband should be 10%, and the **impedance** 50Ω.

$$\omega_0 = 2 \cdot \pi \cdot 1 \text{ GHz} = 6.283 \cdot 10^9 \text{ rad / s}$$

$$\Delta = 0.1$$

LPF Prototype


- 0.5dB equal-ripple table or design formulas:

- $g_1 = 1.5963 = L_1/C_3,$

- $g_2 = 1.0967 = C_2/L_4,$



- $g_3 = 1.5963 = L_3/C_5,$

- $g_4 = 1.000 = R_L$

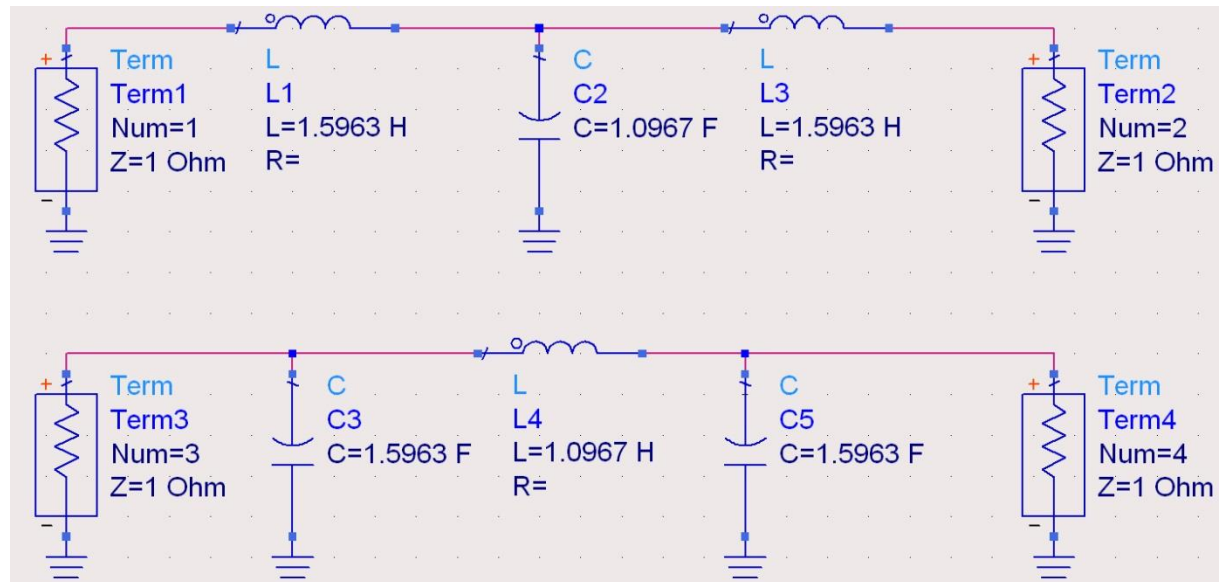

LPF Prototype

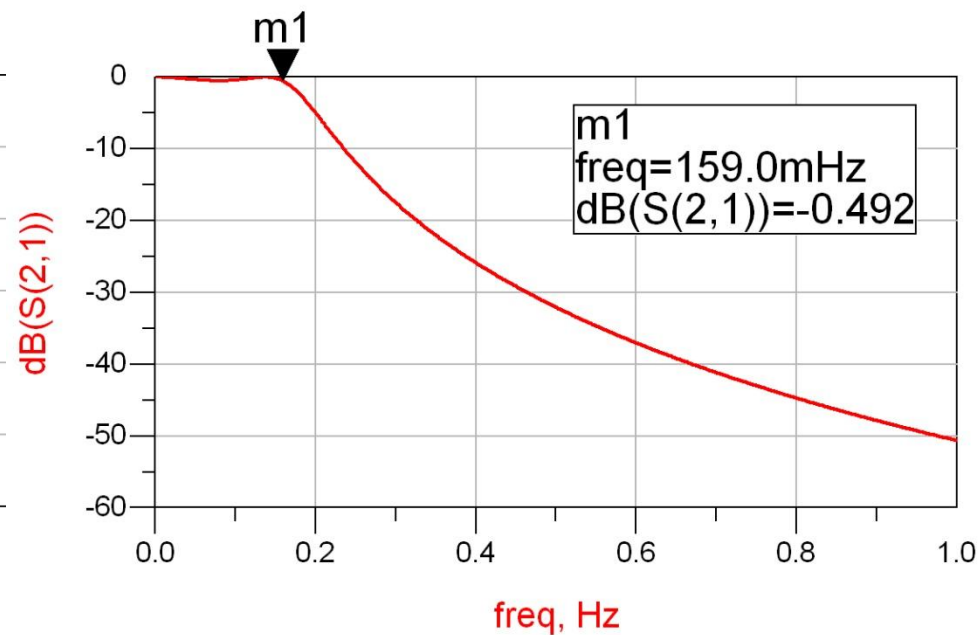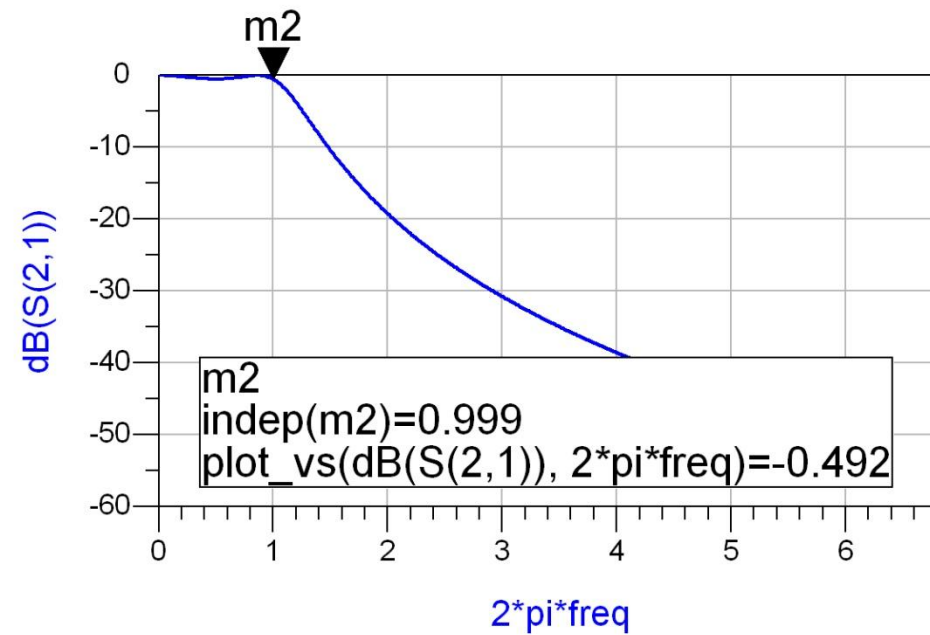- $\omega_o = 1 \text{ rad/s}$ ($f_o = \omega_o / 2\pi = 0.159 \text{ Hz}$)



Bandpass Transformation / BPF

$$\omega_0 = 2 \cdot \pi \cdot 1 \text{GHz} = 6.283 \cdot 10^9 \text{ rad / s} \quad \Delta = \frac{\Delta \omega}{\omega_0} = \frac{\Delta f}{f_0} = 0.1 \quad R_0 = 50 \Omega$$

$$g_1 = 1.5963 = L_1,$$

$$g_2 = 1.0967 = C_2,$$

$$g_3 = 1.5963 = L_3,$$

$$g_4 = 1.000 = R_L$$

$$L'_1 = \frac{L_1 \cdot R_0}{\Delta \cdot \omega_0} = 127.0 \text{ nH}$$

$$C'_1 = \frac{\Delta}{\omega_0 \cdot L_1 \cdot R_0} = 0.199 \text{ pF}$$



$$L'_2 = \frac{\Delta \cdot R_0}{\omega_0 \cdot C_2} = 0.726 \text{ nH}$$

$$C'_2 = \frac{C_2}{\Delta \cdot \omega_0 \cdot R_0} = 34.91 \text{ pF}$$

$$L'_3 = \frac{L_3 \cdot R_0}{\Delta \cdot \omega_0} = 127.0 \text{ nH}$$

$$C'_3 = \frac{\Delta}{\omega_0 \cdot L_3 \cdot R_0} = 0.199 \text{ pF}$$

ADS

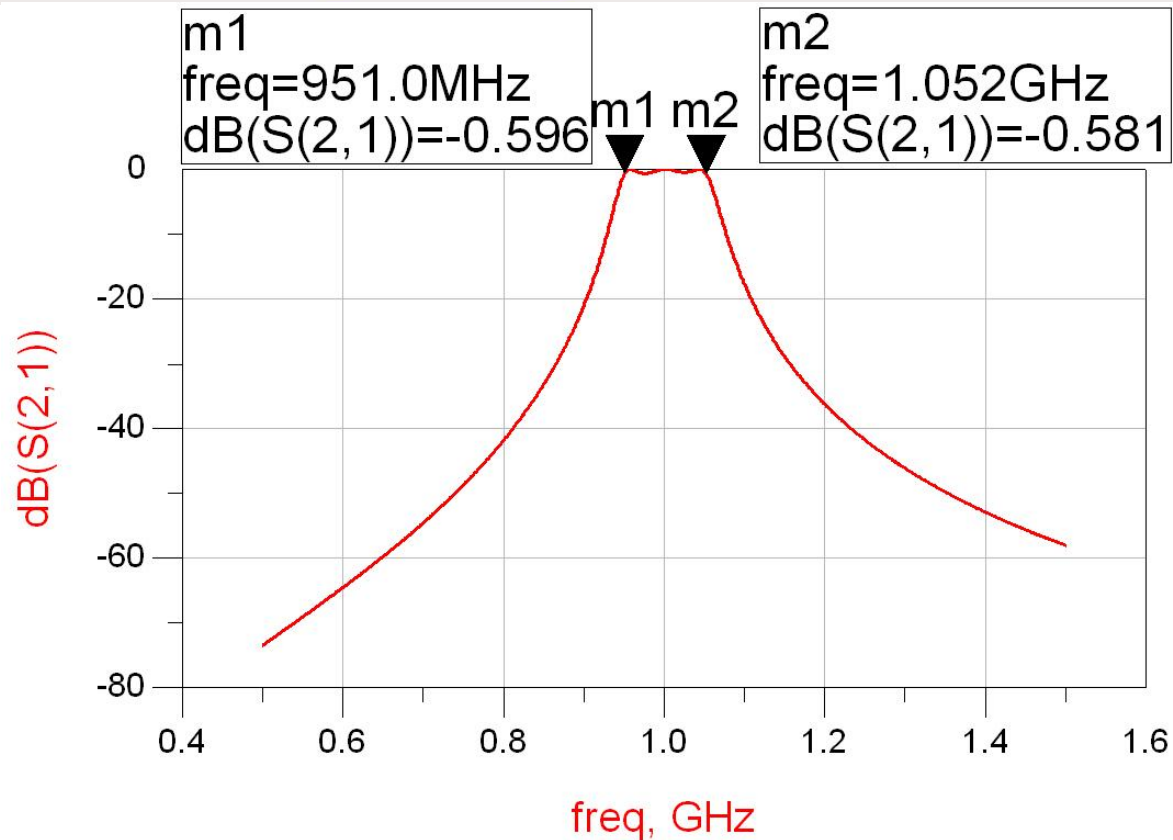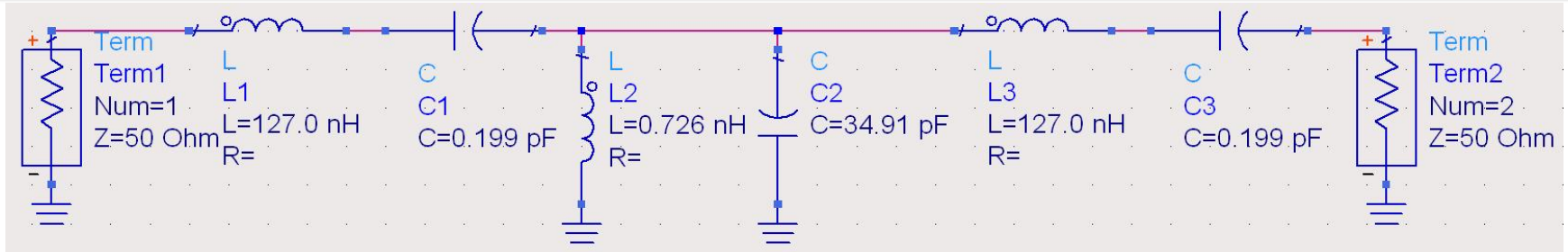

Microwave Filters Implementation

Microwave Filters Implementation

- The lumped-element (L, C) filter design generally works well **only** at low frequencies (RF):
 - lumped-element inductors and capacitors are generally available only for a limited range of values, and can be difficult to implement at microwave frequencies
 - difficulty to obtain the (very low) required tolerance for elements

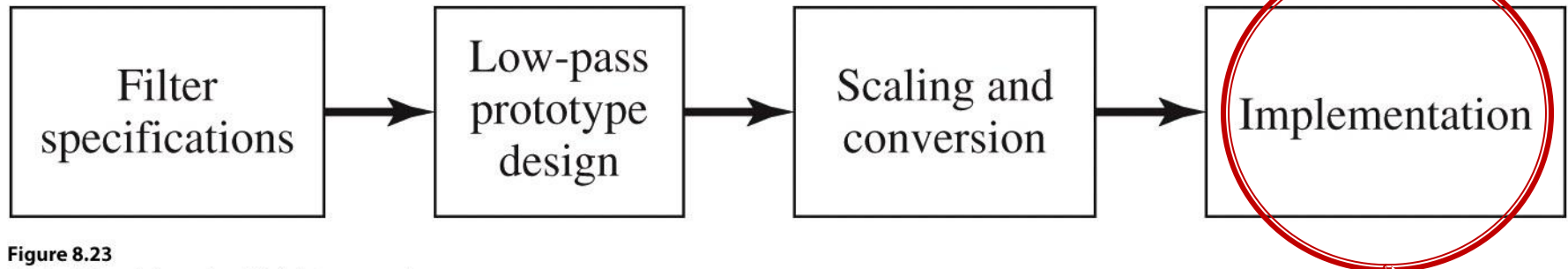


Figure 8.23

Richards' Transformation

- Impedance seen at the input of a line loaded with Z_L

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

- We prefer the load impedance to be:

- open circuit ($Z_L = \infty$) $Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l$

- short circuit ($Z_L = 0$) $Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l$

- Input impedance is:

- capacitive $Z_{in,oc} = j \cdot X_C = \frac{1}{j \cdot B_C}$ $Z_0 \leftrightarrow \frac{1}{C}$ $\tan \beta \cdot l \leftrightarrow \omega$

- inductive $Z_{in,sc} = j \cdot X_L$ $Z_0 \leftrightarrow L$ $\tan \beta \cdot l \leftrightarrow \omega$

Richards' Transformation

- Variable substitution

$$\Omega = \tan \beta \cdot l = \tan \left(\frac{\omega \cdot l}{v_p} \right)$$

- With this variable substitution we define:

- reactance of an inductor

$$j \cdot X_L = j \cdot \Omega \cdot L = j \cdot L \cdot \tan \beta \cdot l$$

- susceptance of a capacitor



$$j \cdot B_C = j \cdot \Omega \cdot C = j \cdot C \cdot \tan \beta \cdot l$$

- The equivalent filter in Ω has a cutoff frequency at:

$$\Omega = 1 = \tan \beta \cdot l \rightarrow \beta \cdot l = \frac{\pi}{4} \rightarrow l = \frac{\lambda}{8}$$

Richards' Transformation

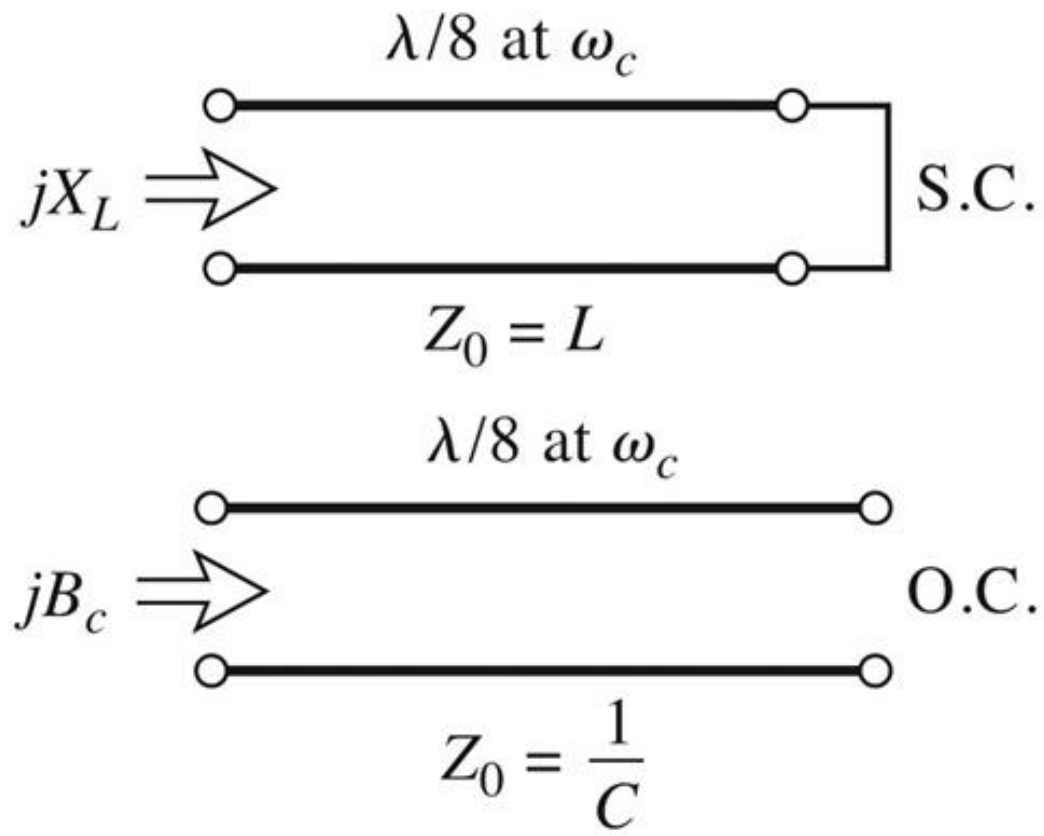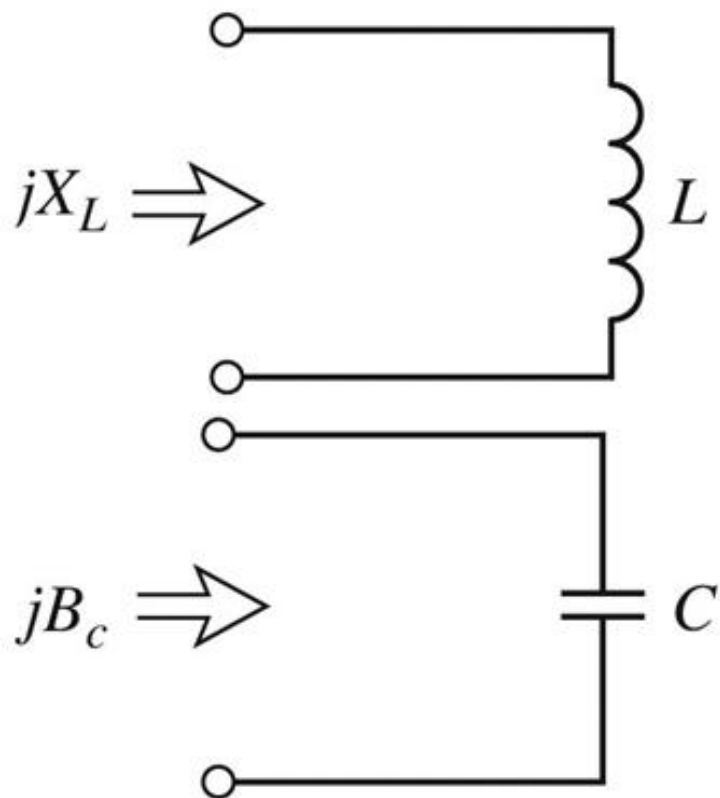- allows implementation of the inductors and capacitors with lines **after** the transformation of the LPF prototype to the required type (LPF/HPF/BPF/BSF)



Richards' Transformation

- By choosing the open-circuited or short-circuited lines to be $\lambda/8$ at the desired cutoff frequency (ω_c) and the corresponding characteristic impedances (L/C from LPF prototype) we will obtain at frequencies around ω_c a behavior similar to that of the prototype filter.
 - At frequencies far from ω_c the behavior of the filter will no longer be identical to that of the prototype (in specific situations the correct behavior must be **verified**)
 - Frequency scaling is simplified: choosing the appropriate physical length of the line to have the electrical length $\lambda/8$ at the desired cutoff frequency
- All lines will have equal electrical lengths ($\lambda/8$) and thus comparable physical lengths, so the lines are called **commensurate** lines

Richards' Transformation

- At the frequency $\omega = 2 \cdot \omega_c$ the lines will be $\lambda/4$ long

$$l = \frac{\lambda}{4} \Rightarrow \beta \cdot l = \frac{\pi}{2} \Rightarrow \tan \beta \cdot l \rightarrow \infty$$

- an supplemental attenuation pole will occur at $2 \cdot \omega_c$ (LPF):
 - inductances (usually in series) $Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l \rightarrow \infty$
 - capacitances (usually shunt) $Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l \rightarrow 0$

Richards' Transformation

- the periodicity of tan function implies the periodicity of the filter implemented with lines
 - the filter response will be repeated every $4 \cdot \omega_c$

$$\tan(\alpha + \pi) = \tan \alpha$$

$$\beta \cdot l \Big|_{\omega=\omega_c} = \frac{\pi}{4} \Rightarrow \frac{\omega_c \cdot l}{v_p} = \frac{\pi}{4} \Rightarrow \pi = \frac{(4 \cdot \omega_c) \cdot l}{v_p}$$


$$Z_{in}(\omega) = Z_{in}(\omega + 4 \cdot \omega_c) \Rightarrow P_{LR}(\omega) = P_{LR}(\omega + 4 \cdot \omega_c)$$

$$P_{LR}(4 \cdot \omega_c) = P_{LR}(0) \quad P_{LR}(3 \cdot \omega_c) = P_{LR}(-\omega_c) \quad P_{LR}(5 \cdot \omega_c) = P_{LR}(\omega_c)$$

Example

- Low-pass filter 4th order, 4 GHz cutoff frequency, maximally flat design (working with 50Ω source and load)
- maximally flat table or formulas:
 - $g_1 = 0.7654 = L_1$
 - $g_2 = 1.8478 = C_2$
 - $g_3 = 1.8478 = L_3$
 - $g_4 = 0.7654 = C_4$
 - $g_5 = 1$ (**does not** need supplemental impedance matching – required only for even order equal-ripple filters)

LPF Prototype

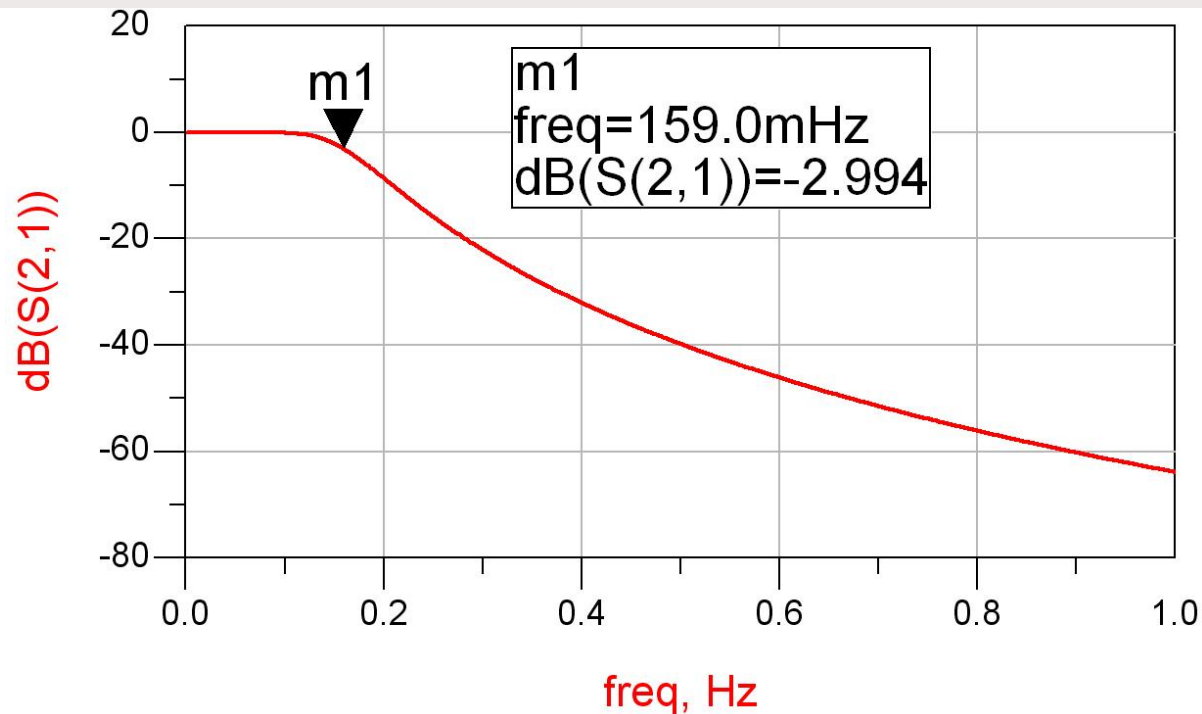

Lumped elements

$$\omega_c = 2 \cdot \pi \cdot 4 \text{GHz} = 2.5133 \cdot 10^{10} \text{rad} / \text{s}$$

$$g_1 = 0.7654 = L_1,$$

$$g_2 = 1.8478 = C_2,$$

$$g_3 = 1.8478 = L_3,$$

$$g_4 = 0.7654 = C_4,$$

$$g_5 = 1 = RL$$



$$L'_1 = \frac{R_0 \cdot L_1}{\omega_c} = 1.523 \text{ nH}$$

$$C'_2 = \frac{C_2}{R_0 \cdot \omega_c} = 1.470 \text{ pF}$$

$$L'_3 = \frac{R_0 \cdot L_3}{\omega_c} = 3.676 \text{ nH}$$

$$C'_4 = \frac{C_4}{R_0 \cdot \omega_c} = 0.609 \text{ pF}$$

Lumped elements – ADS

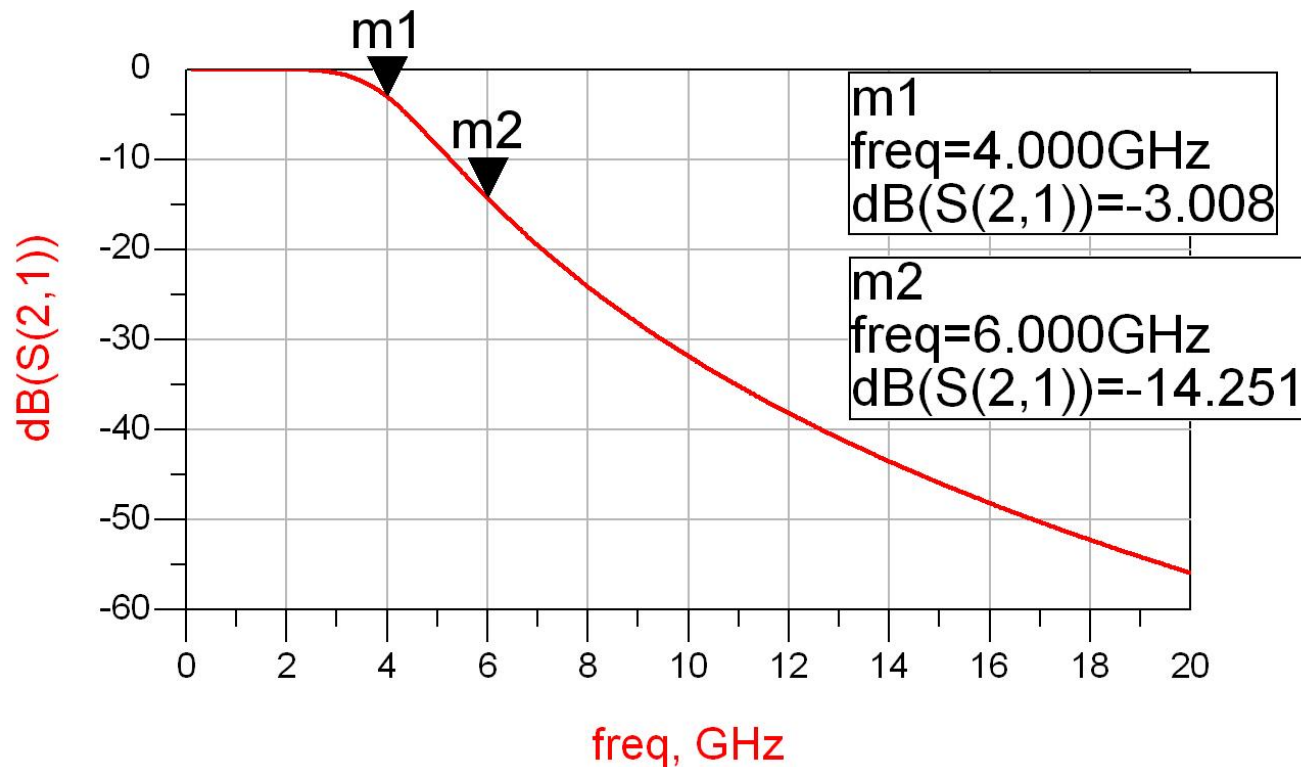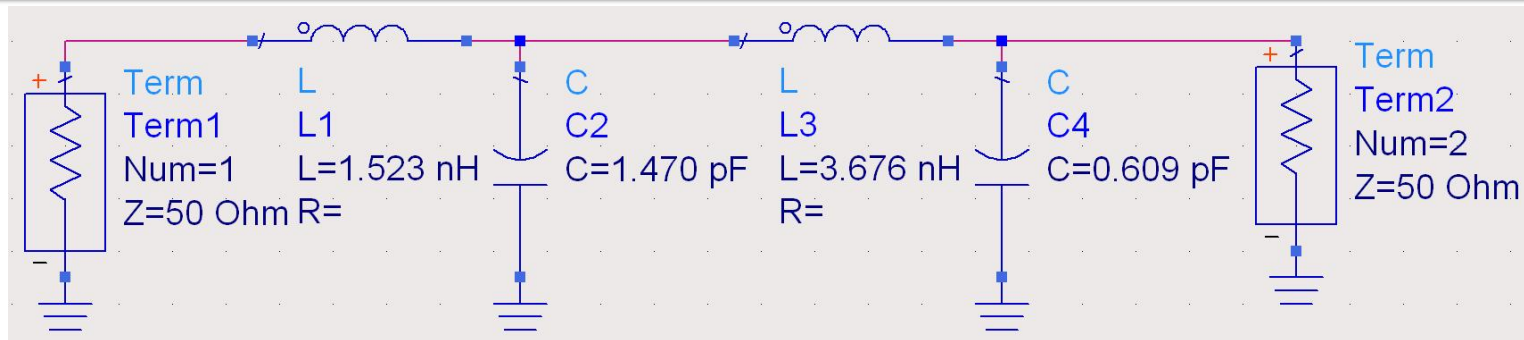



Richards' Transformation

- LPF Prototype parameters:
 - $g_1 = 0.7654 = L_1$
 - $g_2 = 1.8478 = C_2$
 - $g_3 = 1.8478 = L_3$
 - $g_4 = 0.7654 = C_4$
- Normalized line impedances
 - $z_1 = 0.7654 = \text{series / short circuit}$
 - $z_2 = 1 / 1.8478 = 0.5412 = \text{shunt / open circuit}$
 - $z_3 = 1.8478 = \text{series / short circuit}$
 - $z_4 = 1 / 0.7654 = 1.3065 = \text{shunt / open circuit}$
- Impedance scaling by multiplying with $Z_0 = 50\Omega$
- All lines must have the length equal to $\lambda/8$ (electrical length $E = 45^\circ$) at 4GHz

$$Z_0 \leftrightarrow \frac{1}{C}$$


$$Z_0 \leftrightarrow L$$

Richards' Transformation – ADS

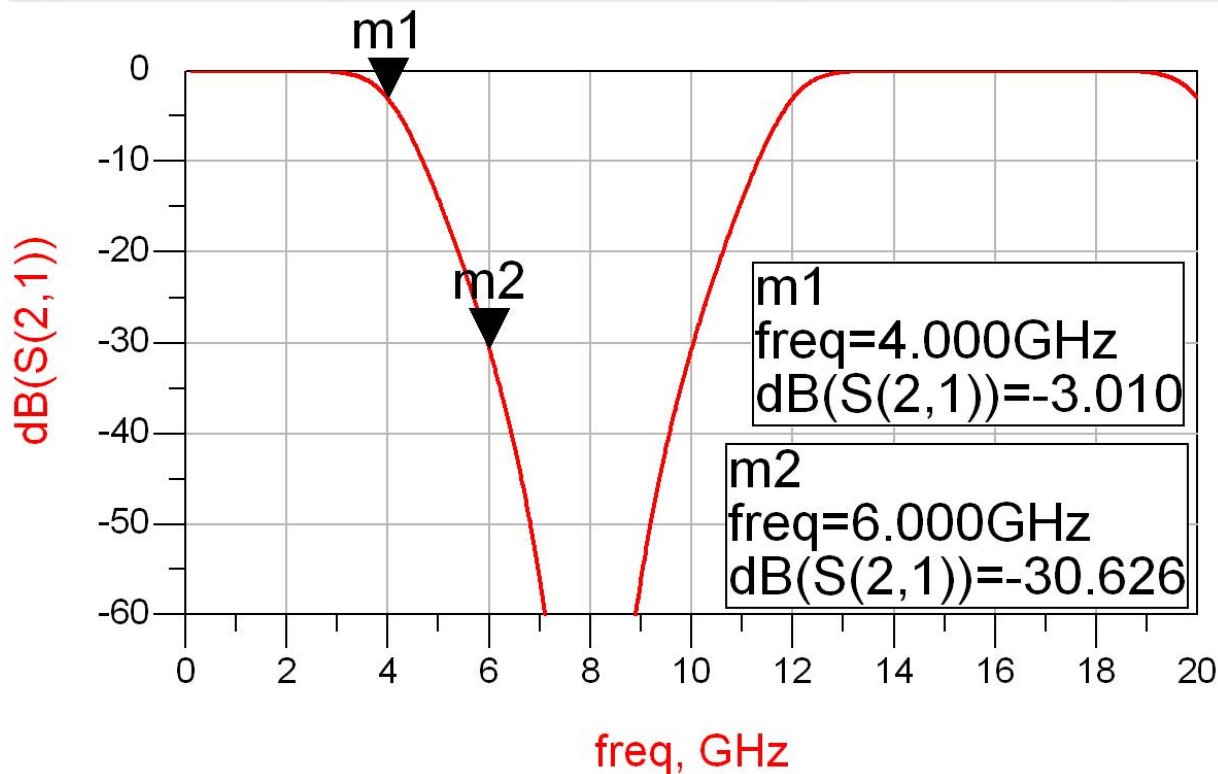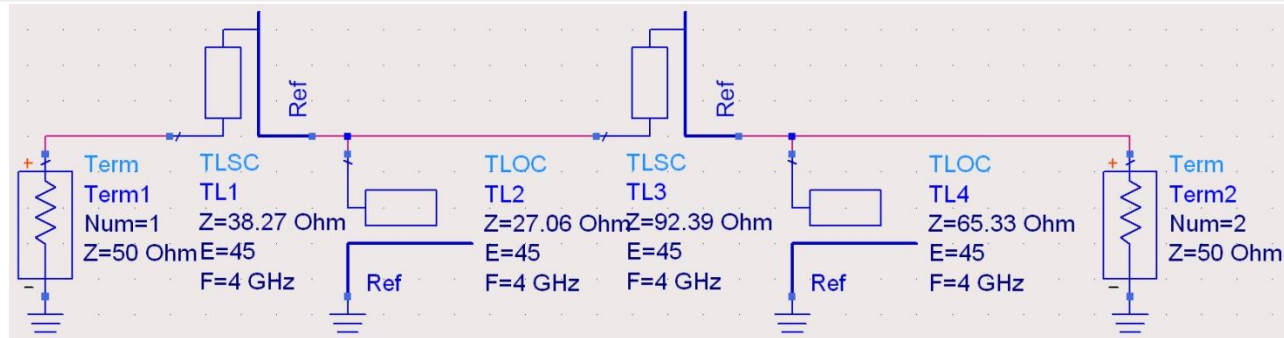

Richards' Transformation

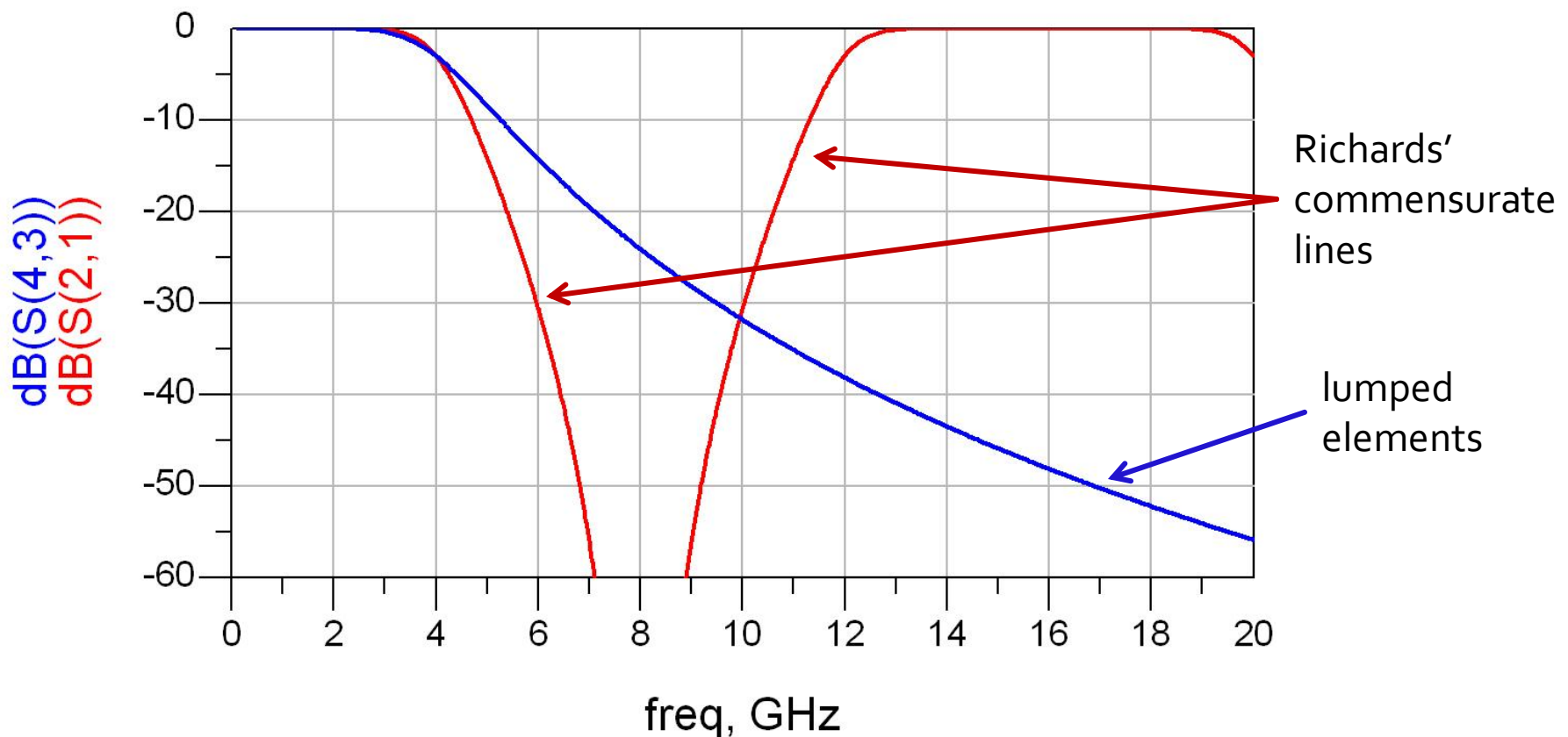- Filters implemented with Richards' Transformation
 - beneficiate from the supplemental pole at $2 \cdot \omega_c$
 - have the major disadvantage of frequency periodicity, a supplemental non-periodic LPF must be inserted if needed



Equal-ripple prototype



- For even N order of the filter ($N = 2, 4, 6, 8 \dots$) equal-ripple filters **must** closed by a non-standard load impedance **$g_{N+1} \neq 1$**
- If the application doesn't allow this, supplemental impedance matching is required (quarter-wave transformer, binomial ...) to **$g_L = 1$**

$$g_{N+1} \neq 1 \rightarrow R \neq R_0 \quad (50\Omega)$$

Observation: even order equal-ripple


- Same filter, 3dB equal-ripple
- 3dB equal-ripple tables or formulas:
 - $g_1 = 3.4389 = L_1$
 - $g_2 = 0.7483 = C_2$
 - $g_3 = 4.3471 = L_3$
 - $g_4 = 0.5920 = C_4$
 - $g_5 = 5.8095 = R_L$
- Line impedances
 - $Z_1 = 3.4389 \cdot 50\Omega = 171.945\Omega = \text{series / short circuit}$
 - $Z_2 = 50\Omega / 0.7483 = 66.818\Omega = \text{shunt / open circuit}$
 - $Z_3 = 4.3471 \cdot 50\Omega = 217.355\Omega = \text{series / short circuit}$
 - $Z_4 = 50\Omega / 0.5920 = 84.459\Omega = \text{shunt / open circuit}$
 - $R_L = 5.8095 \cdot 50\Omega = 295.475\Omega = \text{load}$

Even order equal-ripple – ADS

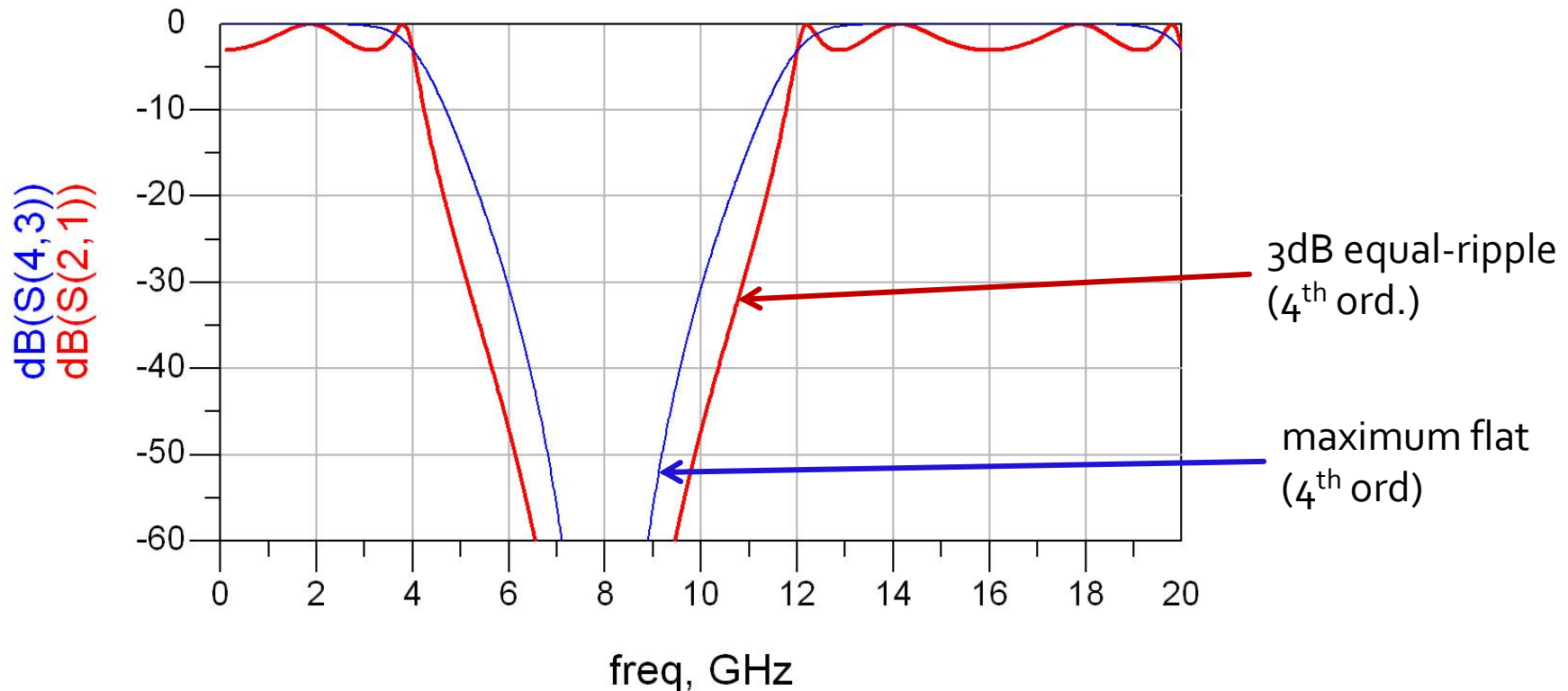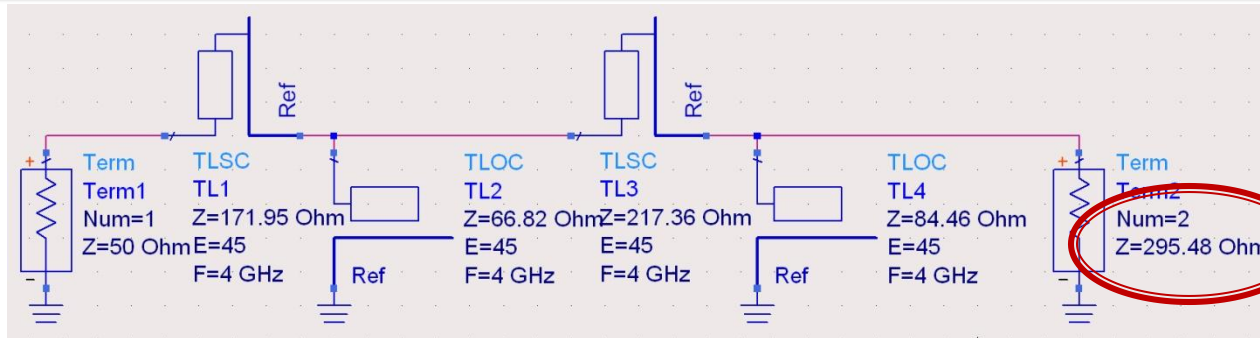


Observation: even order equal-ripple

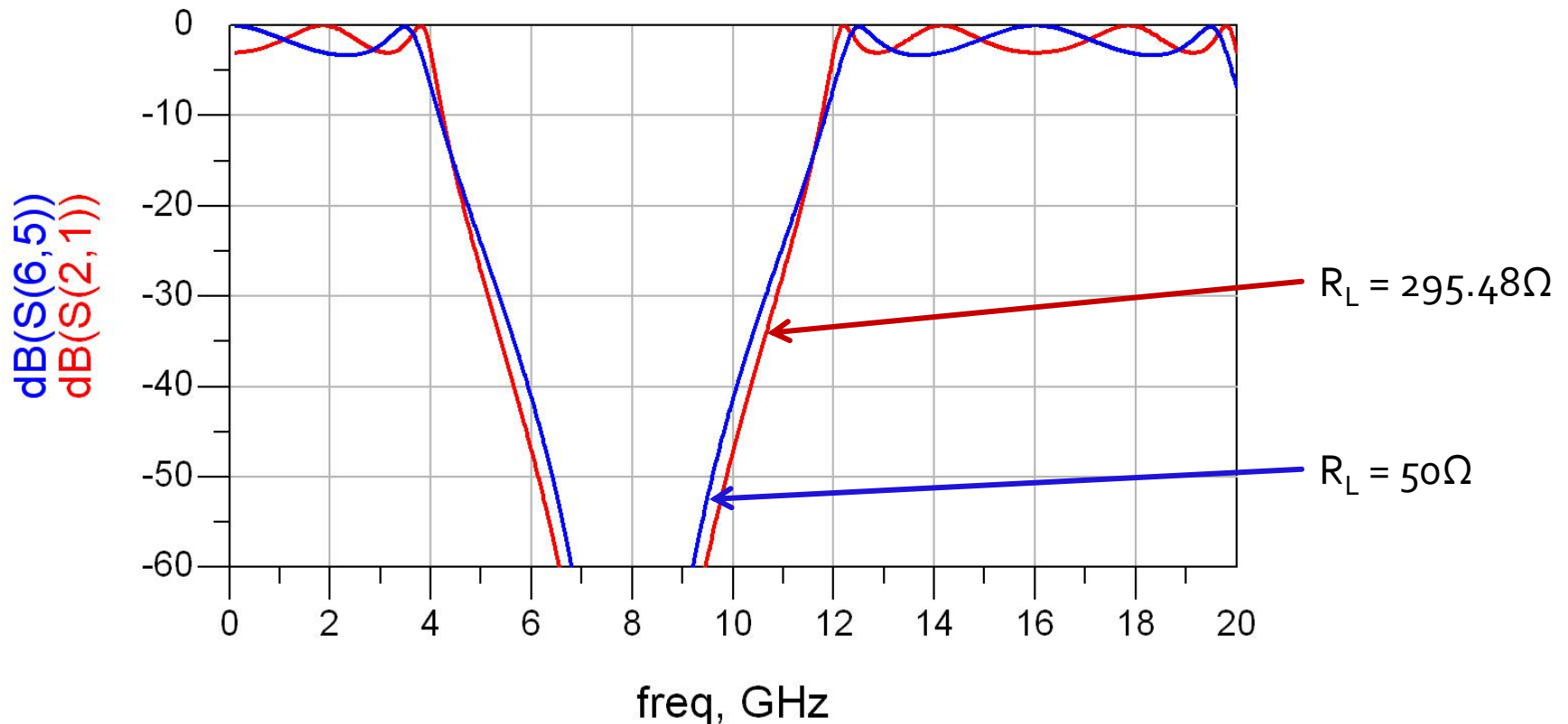- Even order equal-ripple filters need output matching towards 50Ω for precise results.
Example:




Kuroda's Identities

- Filters implemented with the Richards' transformation have certain disadvantages in terms of practical use
- Kuroda's Identities/Transformations can eliminate some of these disadvantages
- We use additional line sections to obtain systems that are easier to implement in practice
- The additional line sections are called unit elements and have lengths of $\lambda / 8$ at the desired cutoff frequency (ω_c) thus being commensurate with the stubs implementing the inductors and capacitors.

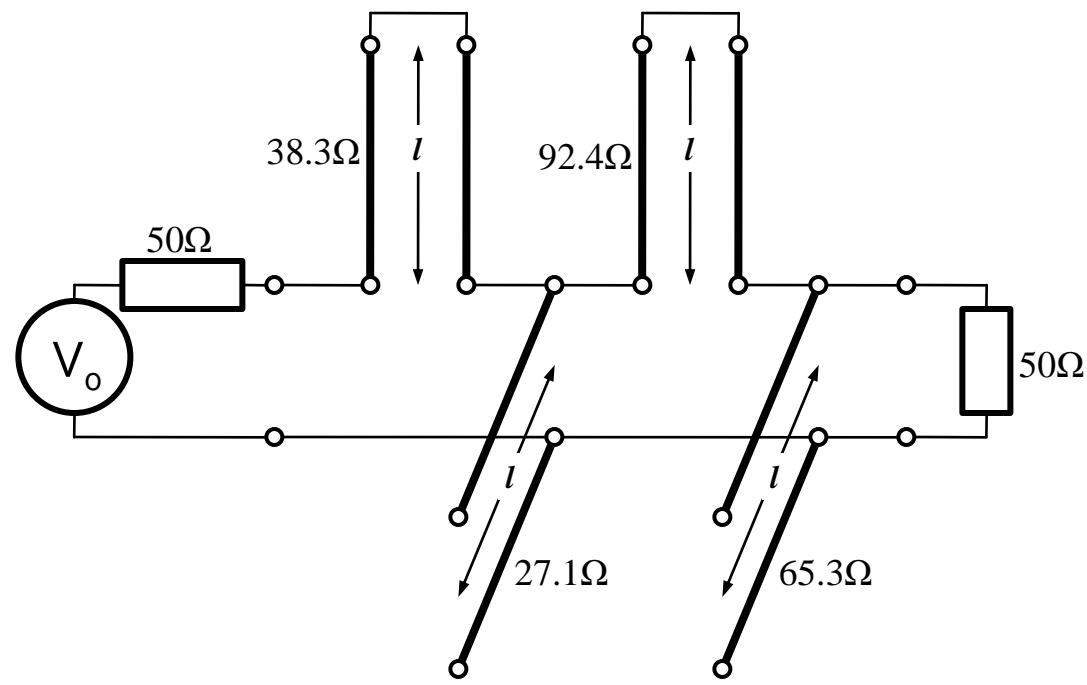



Kuroda's Identities

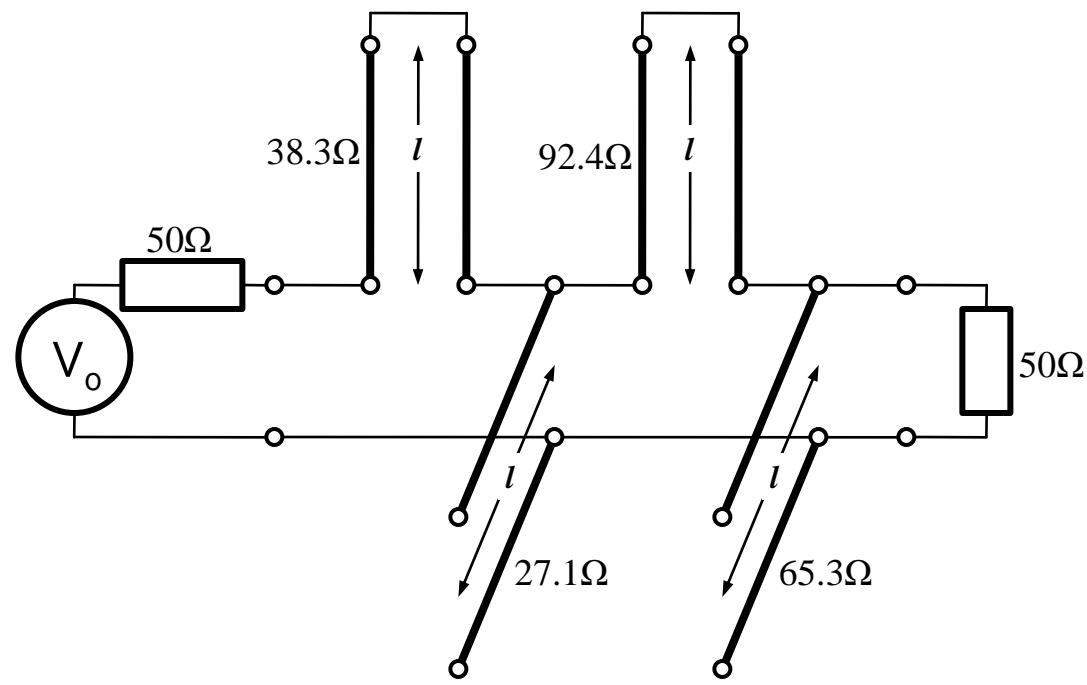- Kuroda's Identities perform any of the following operations:
 - Physically separate transmission line stubs
 - Transform series stubs into shunt stubs, or vice versa
 - Change impractical characteristic impedances into more realizable values ($\sim 50\Omega$)





Kuroda's Identities

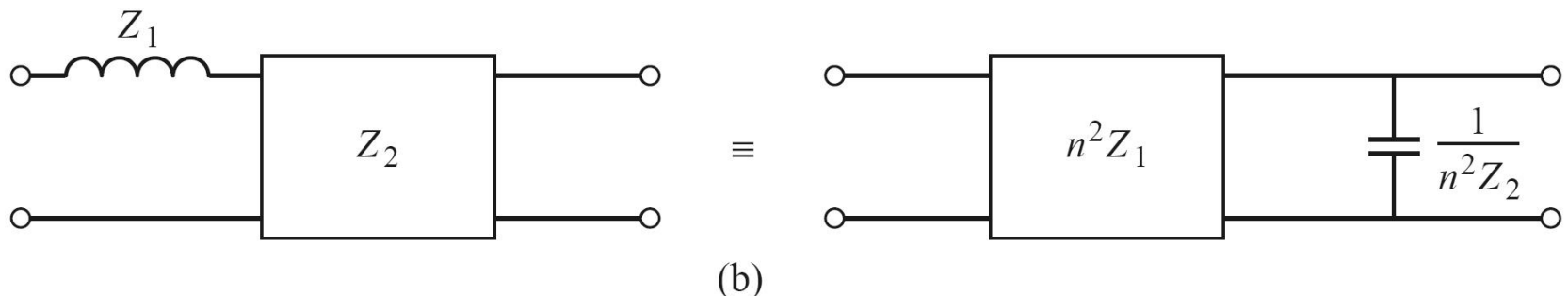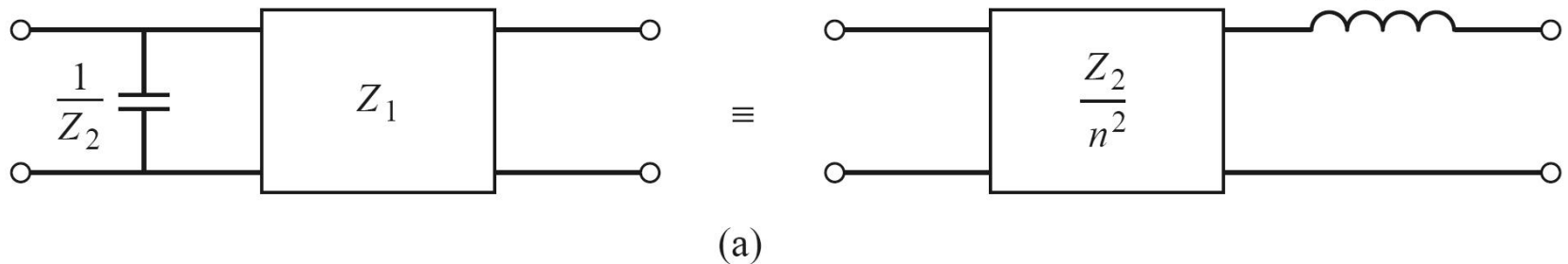- 4 circuit equivalents (a,b)
 - each box represents a unit element, or transmission line, of the indicated characteristic impedance and length ($\lambda/8$ at ω_c). The inductors and capacitors represent short-circuit and open-circuit stubs $\frac{Z_1}{n^2}$



Kuroda's Identities

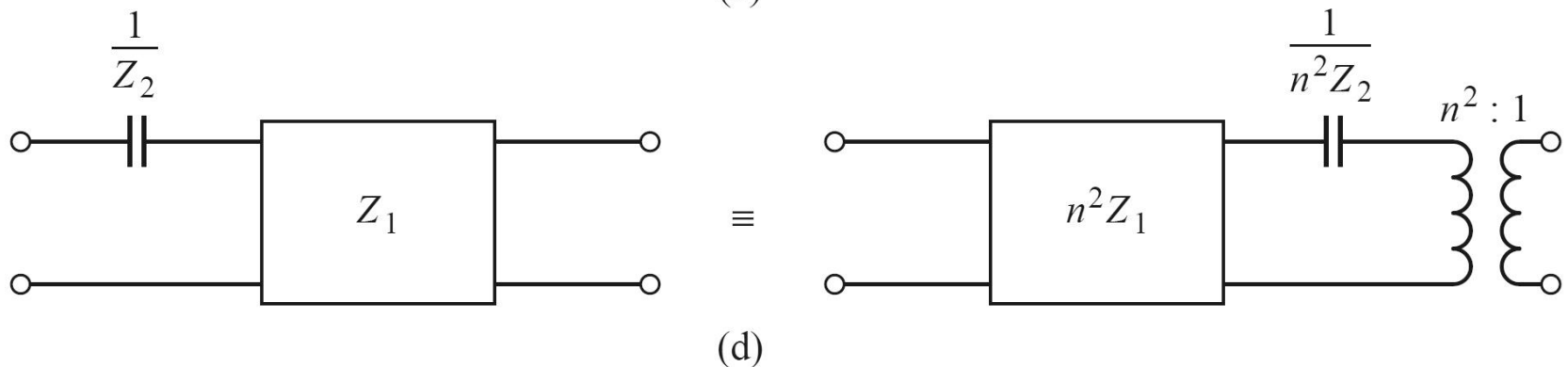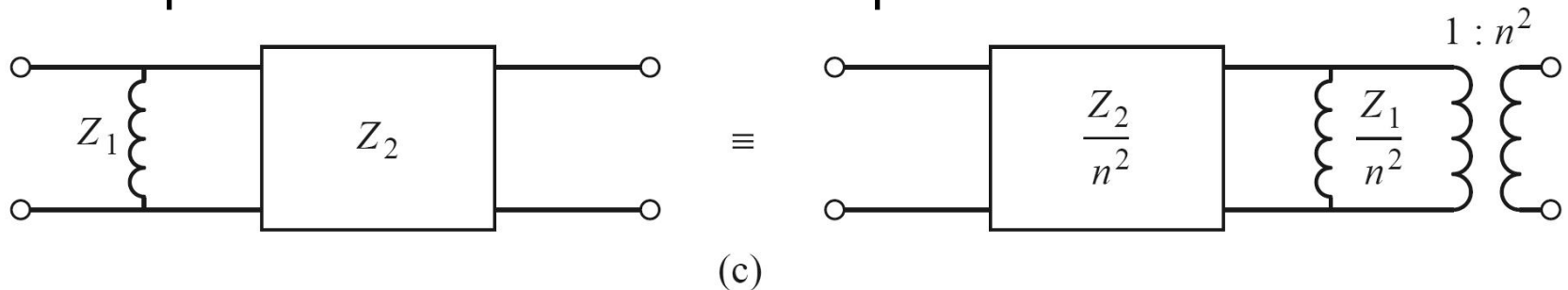- 4 circuit equivalents (c,d)
 - each box represents a unit element, or transmission line, of the indicated characteristic impedance and length ($\lambda/8$ at ω_c). The inductors and capacitors represent short-circuit and open-circuit stubs



Kuroda's Identities

- In all Kuroda's Identities:

- n:

$$n^2 = 1 + \frac{Z_2}{Z_1}$$

- The inductors and capacitors represent short-circuit and open-circuit stubs resulted from Richards' transformation ($\lambda/8$ at ω_c).
 - Each box represents a unit element, or transmission line, of the indicated characteristic impedance and length ($\lambda/8$ at ω_c).

First Kuroda's Identity

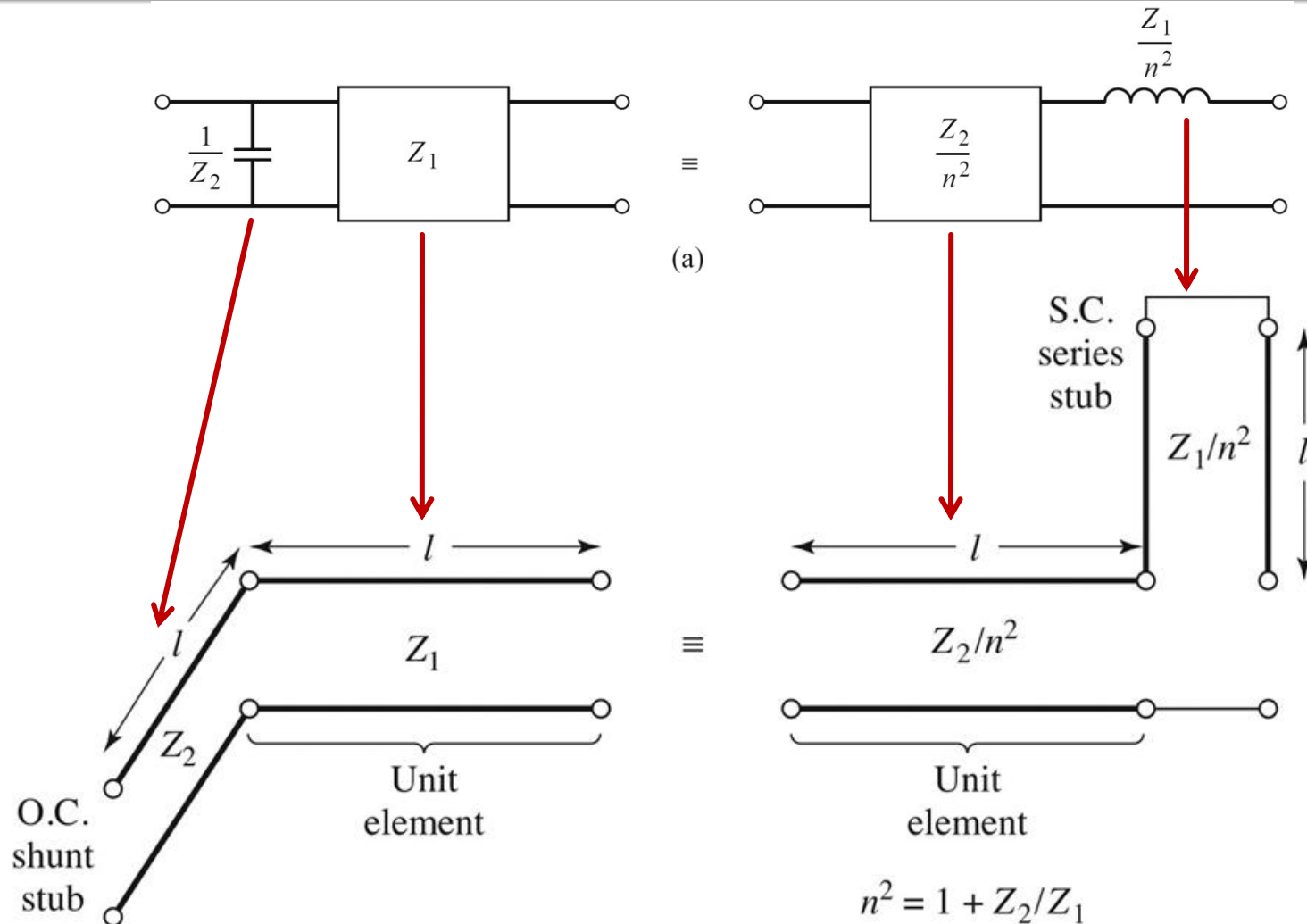


Figure 8.35
© John Wiley & Sons, Inc. All rights reserved.

First Kuroda's Identity – Proof



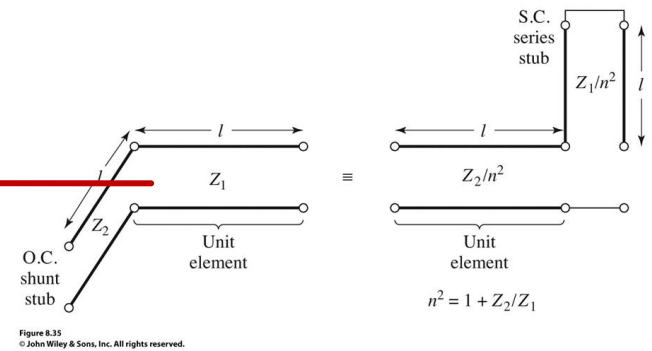
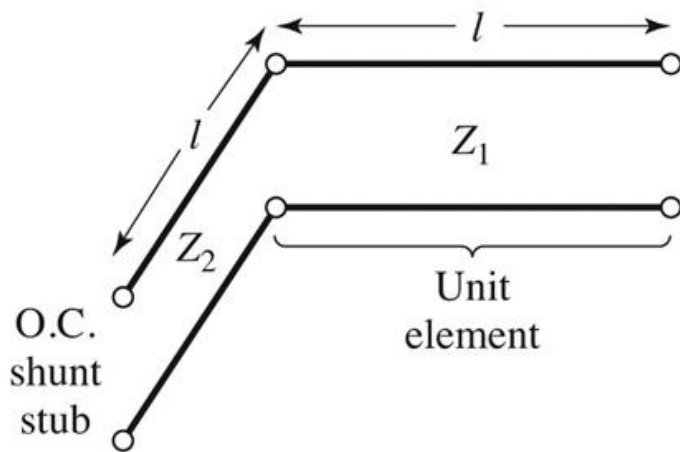


Figure 8.35
© John Wiley & Sons, Inc. All rights reserved.

■ ABCD matrices, L_4

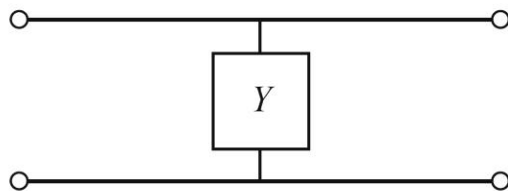


+

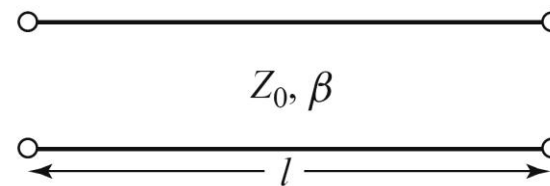

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \beta \cdot l & j \cdot Z_0 \cdot \sin \beta \cdot l \\ j \cdot Y_0 \cdot \sin \beta \cdot l & \cos \beta \cdot l \end{bmatrix}$$

First Kuroda's Identity – Proof

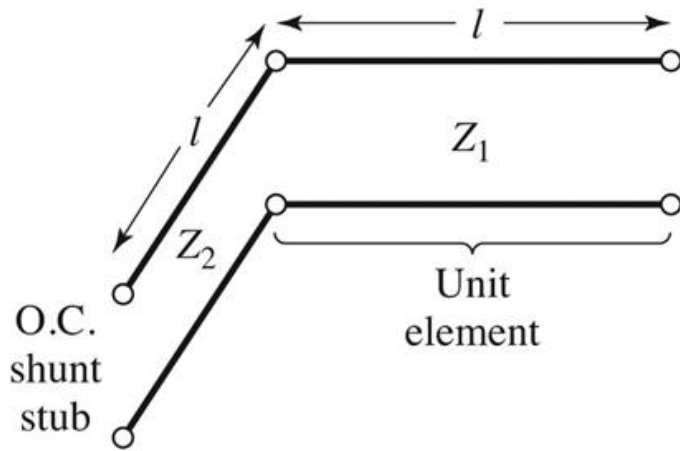

$$\Omega = \tan \beta \cdot l$$

$$\cos \beta \cdot l = \frac{1}{\sqrt{1 + \Omega^2}} \quad \sin \beta \cdot l = \frac{\Omega}{\sqrt{1 + \Omega^2}}$$

$$Z_{in,oc} = -j \cdot Z_2 \cdot \cot \beta \cdot l = -j \cdot \frac{Z_2}{\Omega}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{j \cdot \Omega}{Z_2} & 1 \end{bmatrix} \cdot \begin{bmatrix} \frac{1}{\sqrt{1 + \Omega^2}} & j \cdot Z_1 \cdot \frac{\Omega}{\sqrt{1 + \Omega^2}} \\ j \cdot \frac{1}{Z_1} \cdot \frac{\Omega}{\sqrt{1 + \Omega^2}} & \frac{1}{\sqrt{1 + \Omega^2}} \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{1}{\sqrt{1 + \Omega^2}} \cdot \begin{bmatrix} 1 & 0 \\ \frac{j \cdot \Omega}{Z_2} & 1 \end{bmatrix} \cdot \begin{bmatrix} 1 & j \cdot \Omega \cdot Z_1 \\ \frac{j \cdot \Omega}{Z_1} & 1 \end{bmatrix} = \frac{1}{\sqrt{1 + \Omega^2}} \cdot \begin{bmatrix} 1 & j \cdot \Omega \cdot Z_1 \\ j \cdot \Omega \cdot \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) & 1 - \Omega^2 \cdot \frac{Z_1}{Z_2} \end{bmatrix}$$

First Kuroda's Identity – Proof


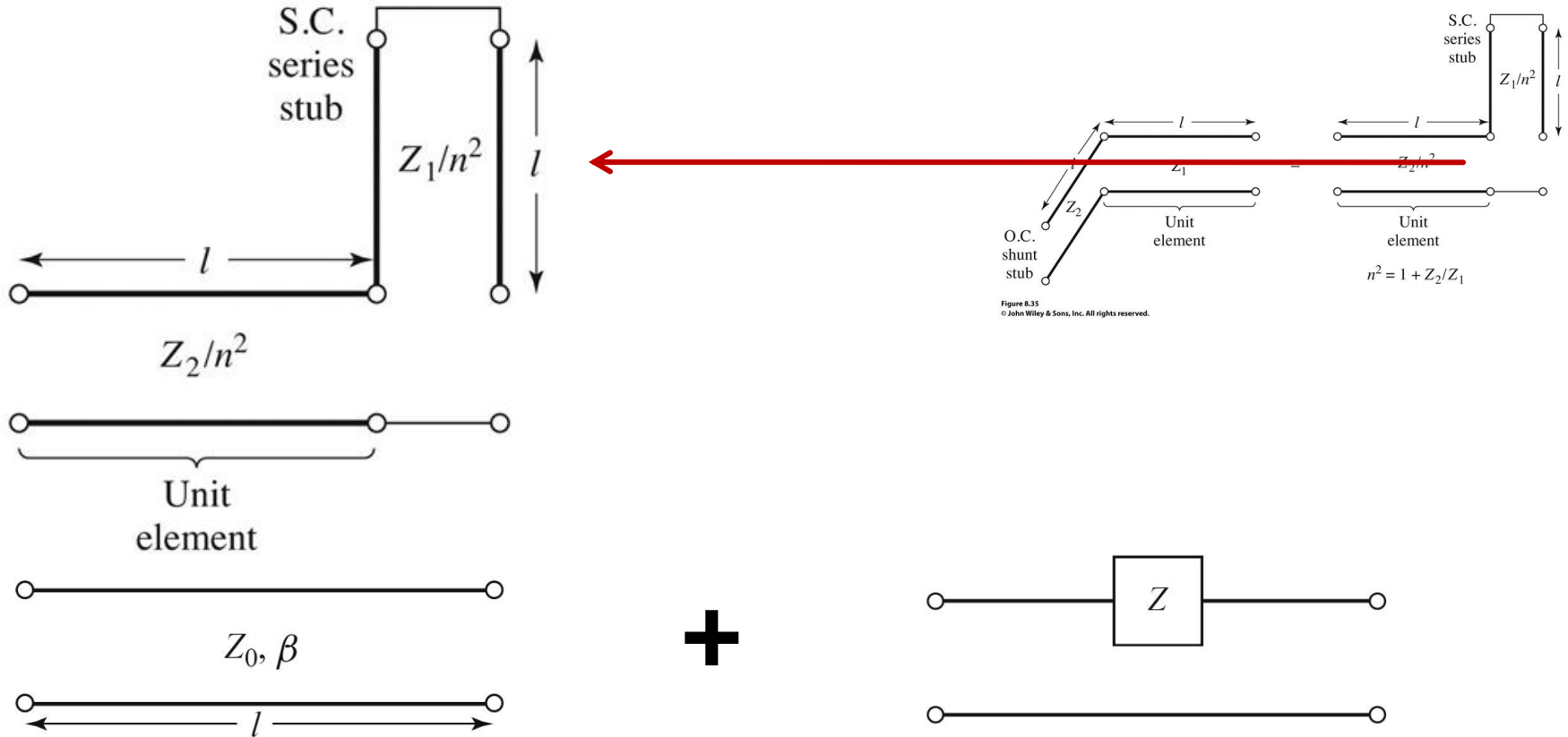


Figure 8.35
© John Wiley & Sons, Inc. All rights reserved.

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \beta \cdot l & j \cdot Z_0 \cdot \sin \beta \cdot l \\ j \cdot Y_0 \cdot \sin \beta \cdot l & \cos \beta \cdot l \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$

First Kuroda's Identity – Proof

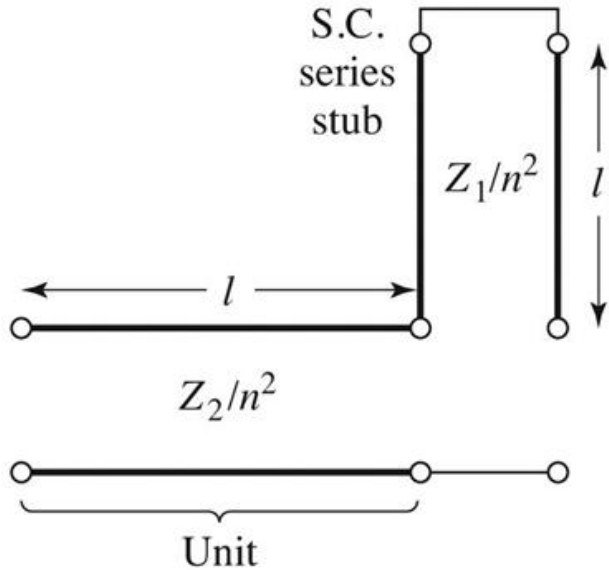

$$\Omega = \tan \beta \cdot l$$

$$\cos \beta \cdot l = \frac{1}{\sqrt{1 + \Omega^2}} \quad \sin \beta \cdot l = \frac{\Omega}{\sqrt{1 + \Omega^2}}$$

$$Z_{in,sc} = j \cdot \left(\frac{Z_1}{n^2} \right) \cdot \tan \beta \cdot l = \frac{j \cdot \Omega \cdot Z_1}{n^2}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & j \cdot \frac{Z_2}{n^2} \cdot \frac{\Omega}{\sqrt{1 + \Omega^2}} \\ j \cdot \frac{n^2}{Z_2} \cdot \frac{\Omega}{\sqrt{1 + \Omega^2}} & 1 \end{bmatrix} \cdot \begin{bmatrix} 1 & \frac{j \cdot \Omega \cdot Z_1}{n^2} \\ 0 & 1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{1}{\sqrt{1 + \Omega^2}} \cdot \begin{bmatrix} 1 & j \cdot \Omega \cdot \frac{Z_2}{n^2} \\ \frac{j \cdot \Omega \cdot n^2}{Z_2} & 1 \end{bmatrix} \cdot \begin{bmatrix} 1 & j \cdot \Omega \cdot \frac{Z_1}{n^2} \\ 0 & 1 \end{bmatrix} = \frac{1}{\sqrt{1 + \Omega^2}} \cdot \begin{bmatrix} 1 & j \cdot \frac{\Omega}{n^2} \cdot (Z_1 + Z_2) \\ \frac{j \cdot \Omega \cdot n^2}{Z_2} & 1 - \Omega^2 \cdot \frac{Z_1}{Z_2} \end{bmatrix}$$

First Kuroda's Identity – Proof

- First circuit

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{1}{\sqrt{1+\Omega^2}} \cdot \begin{bmatrix} 1 & j \cdot \Omega \cdot Z_1 \\ j \cdot \Omega \cdot \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) & 1 - \Omega^2 \cdot \frac{Z_1}{Z_2} \end{bmatrix}$$

- Second circuit

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{1}{\sqrt{1+\Omega^2}} \cdot \begin{bmatrix} 1 & j \cdot \frac{\Omega}{n^2} \cdot (Z_1 + Z_2) \\ \frac{j \cdot \Omega \cdot n^2}{Z_2} & 1 - \Omega^2 \cdot \frac{Z_1}{Z_2} \end{bmatrix}$$

- Results are identical if we choose

$$n^2 = 1 + \frac{Z_2}{Z_1}$$

- The other 3 identities can be proved in the same way

(Same) Example


- Low-pass filter 4th order, 4 GHz cutoff frequency, maximally flat design (working with 50Ω source and load)
- maximally flat table or formulas:
 - $g_1 = 0.7654 = L_1$
 - $g_2 = 1.8478 = C_2$
 - $g_3 = 1.8478 = L_3$
 - $g_4 = 0.7654 = C_4$
 - $g_5 = 1$ (**does not** need supplemental impedance matching – required only for even order equal-ripple filters)

Example

■ Apply Richards's transformation


■ Problems:

- the series stubs would be **very difficult** to implement in microstrip line form
- in microstrip technology it is preferable to have open-circuit stubs (short-circuit requires a **via-hole** to the ground plane)
- the 4 stubs are physically connected at the same point, an implementation that eliminates/reduces the **coupling** between these lines is impossible
- not the case here, but sometimes the normalized impedances are much different from 1. Most circuit technologies are designed for 50Ω lines

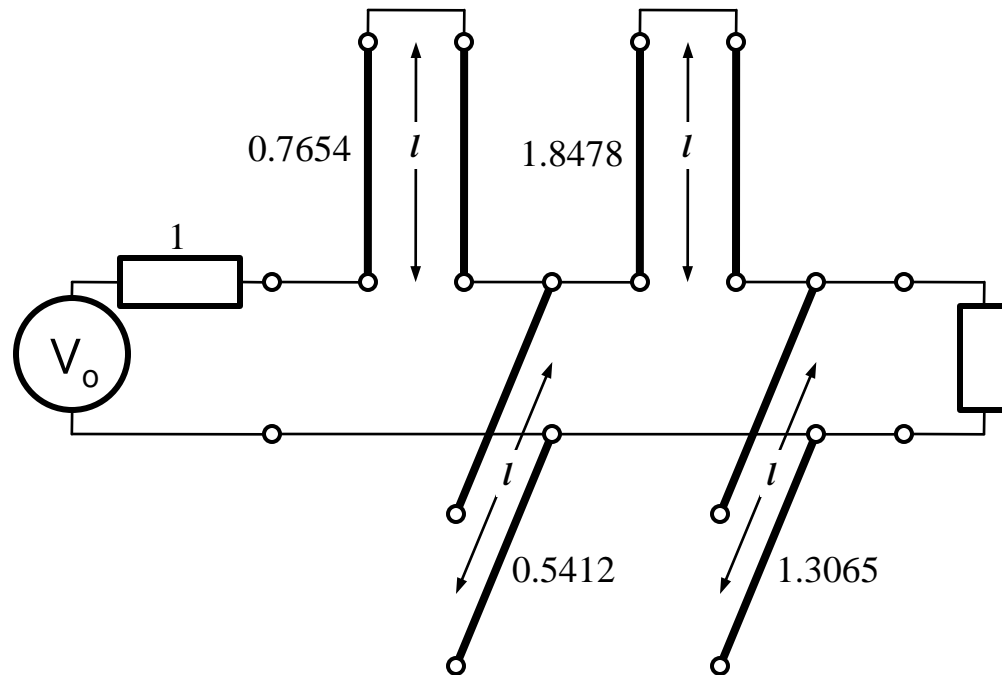

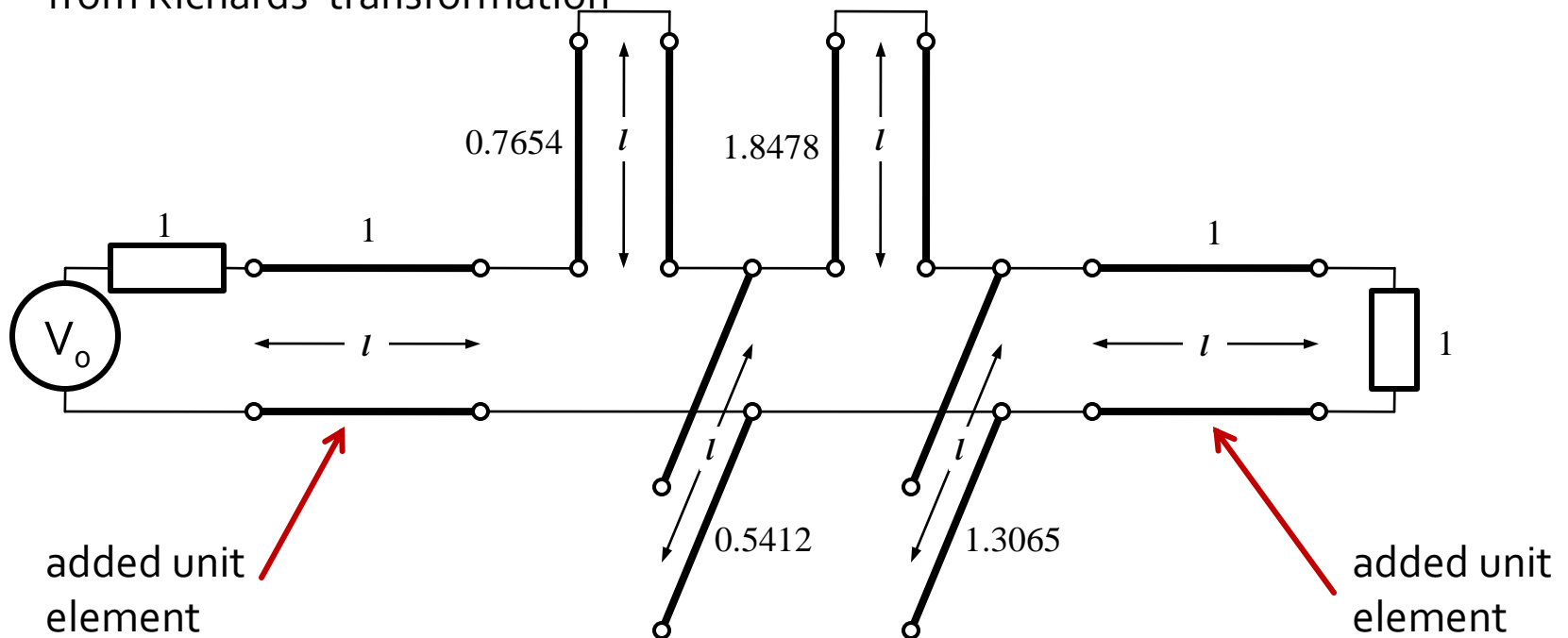
Example

- In all 4 Kuroda's Identities we **always** have a circuit with a series line section (not present in initial circuit):
 - we **add** unit elements ($z = 1, l = \lambda/8$) at the ends of the filter (these redundant elements do not affect filter performance since they are matched to $z = 1$, both source and load)
 - we **apply** one of the Kuroda's Identities at both ends and **continue** (add unit ...)
 - we can **stop** the procedure when we have a series line section between all the stubs from Richards' transformation



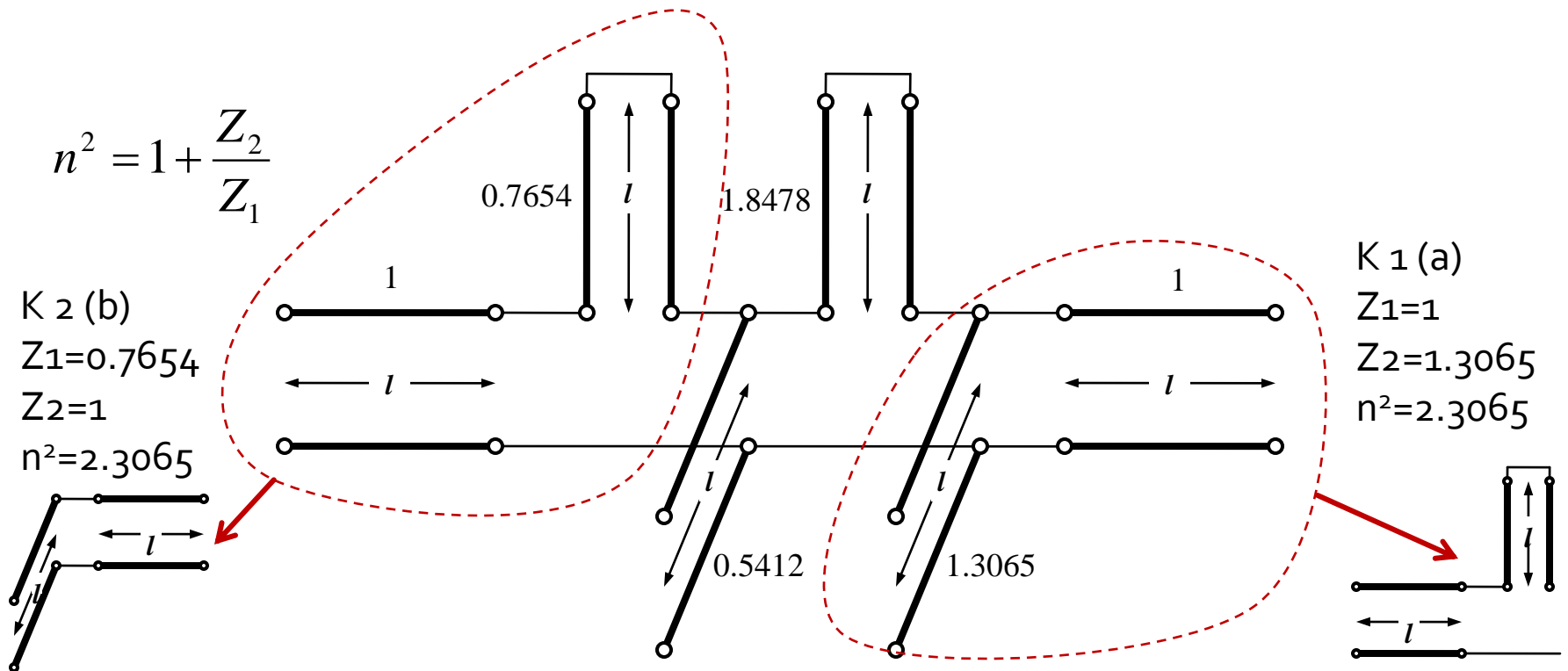Example


- Apply:
 - Kuroda 2 (L, Z known $\rightarrow C, Z$) on the left side
 - Kuroda 1 (C, Z known $\rightarrow L, Z$) on the right side




Example

- We add another unit element on the right side and apply Kuroda 2 twice


$$n^2 = 1 + \frac{Z_2}{Z_1}$$

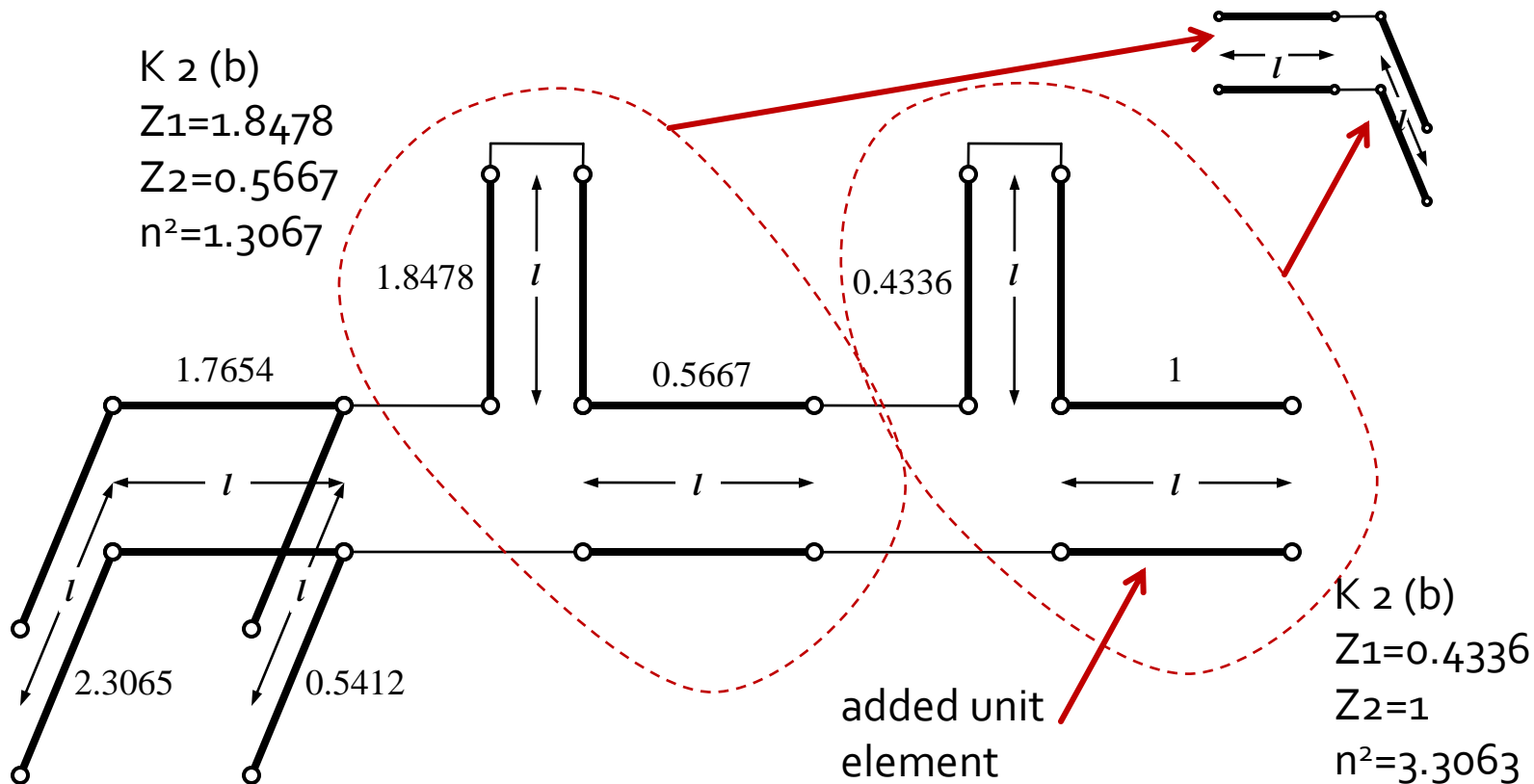



Example

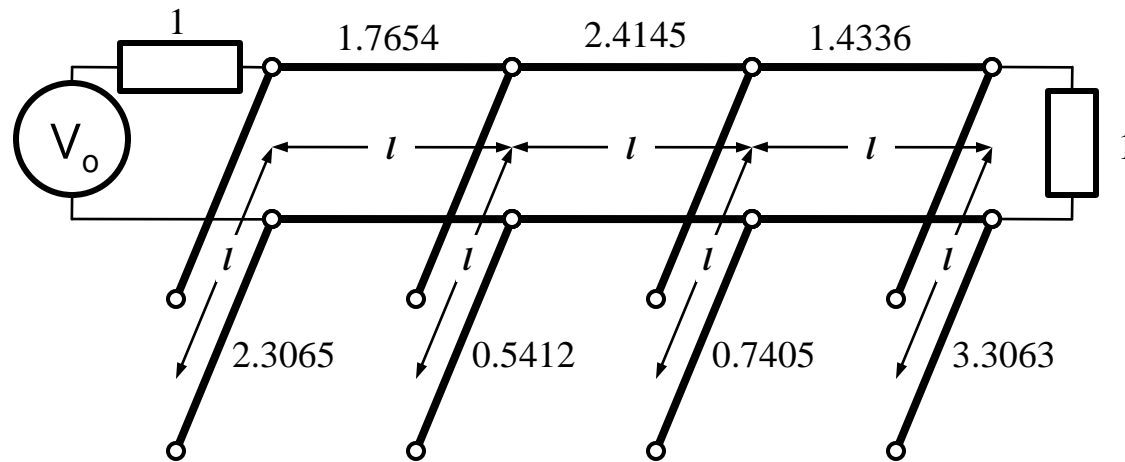

- Impedance scaling (multiply by 50Ω)

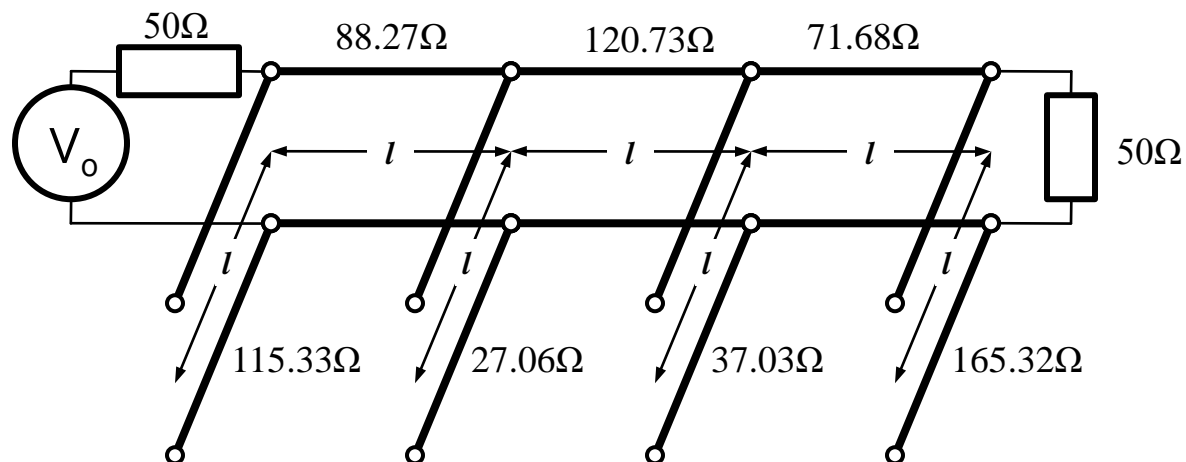

Kuroda's Identities – ADS

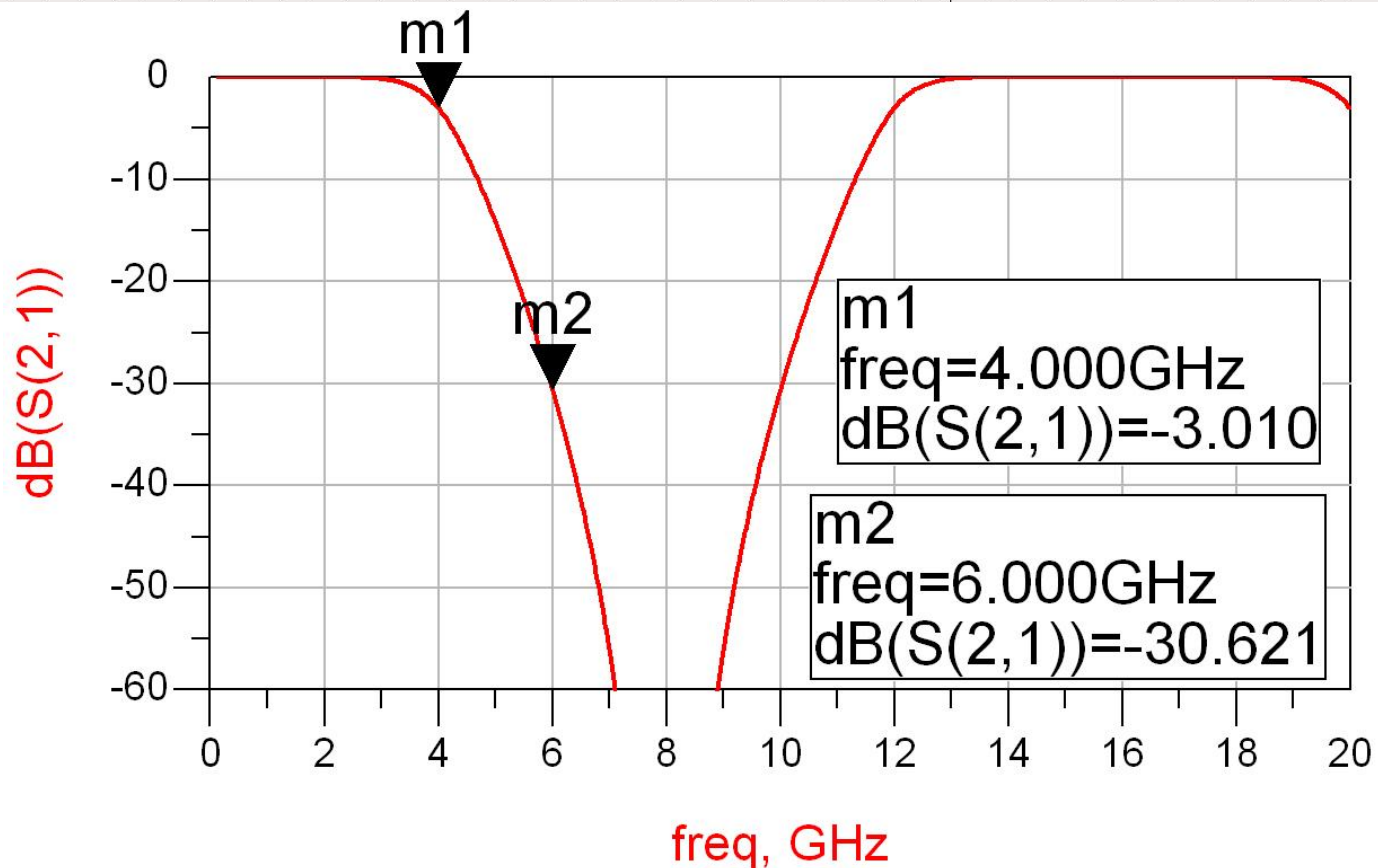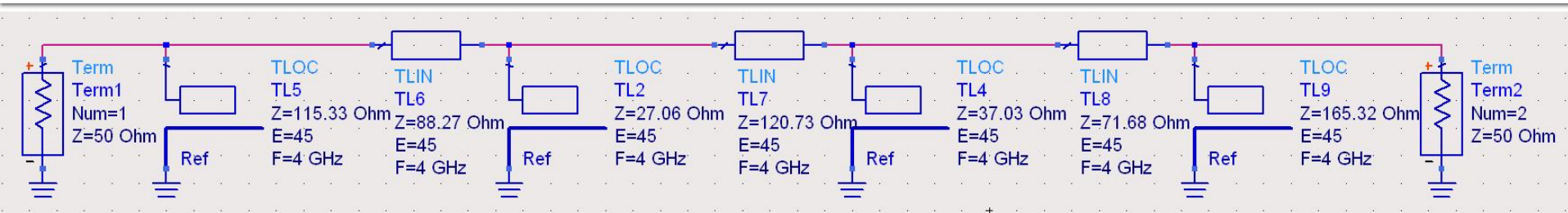

Examples

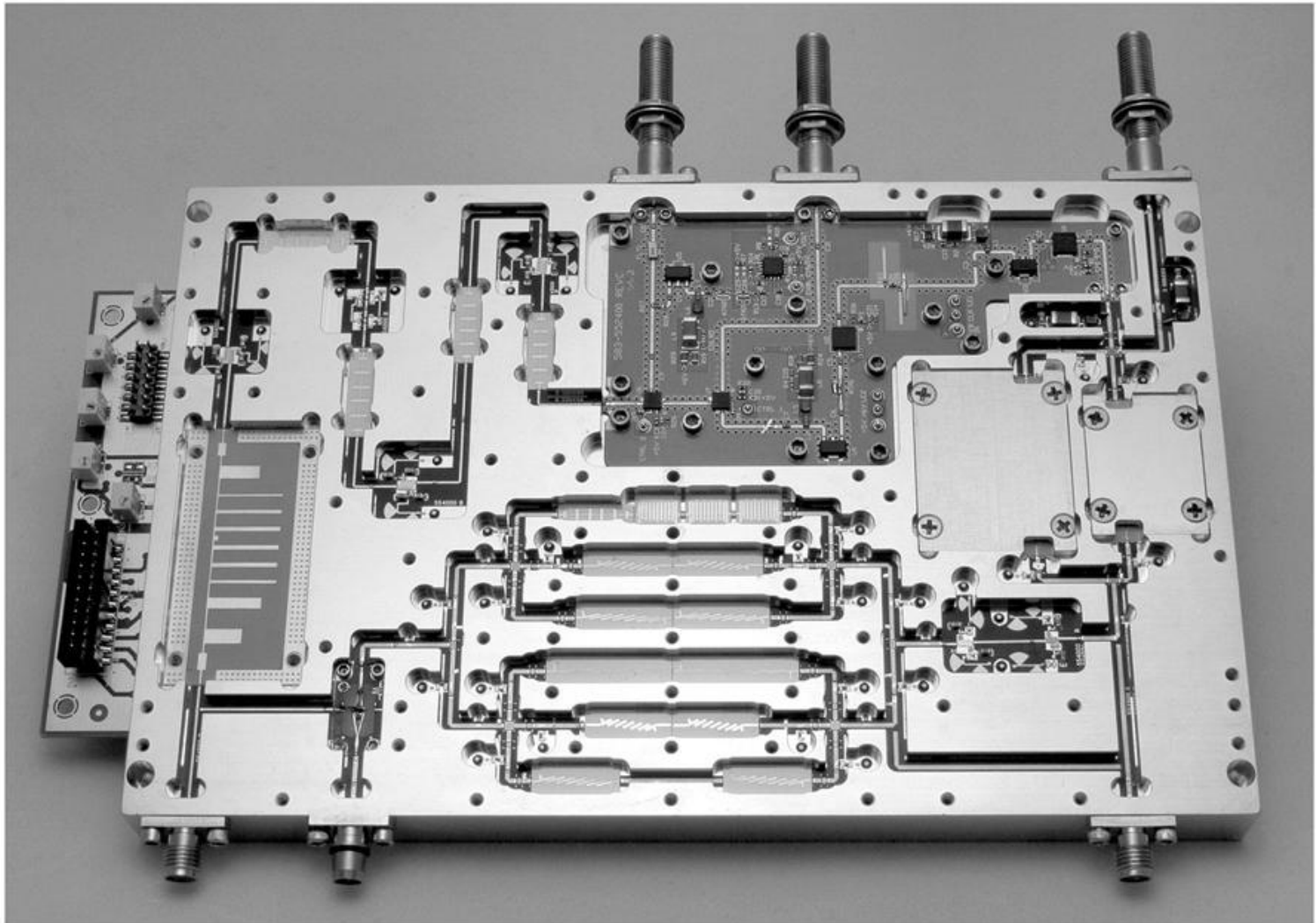


Figure 8.55
Courtesy of LNX Corporation, Salem, N.H.

Examples


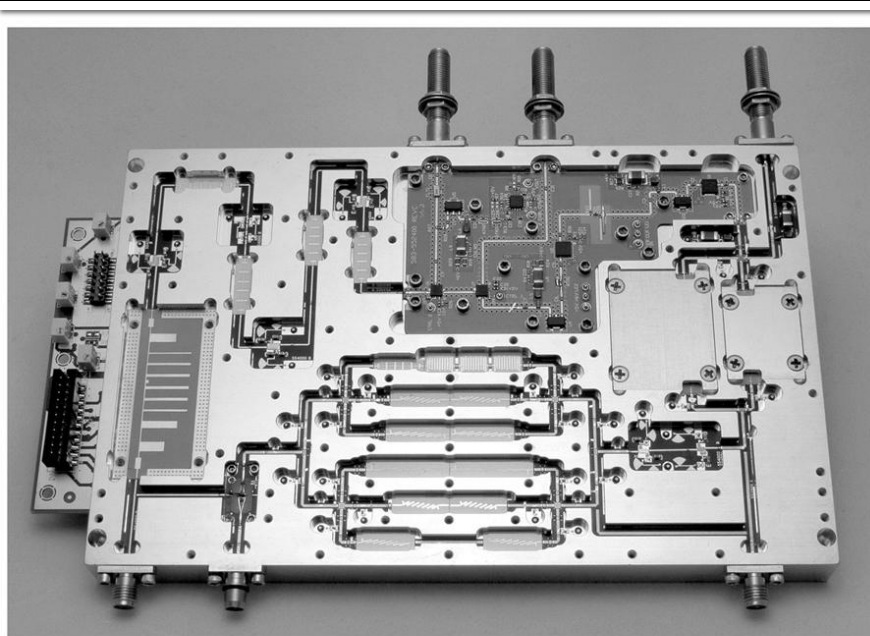
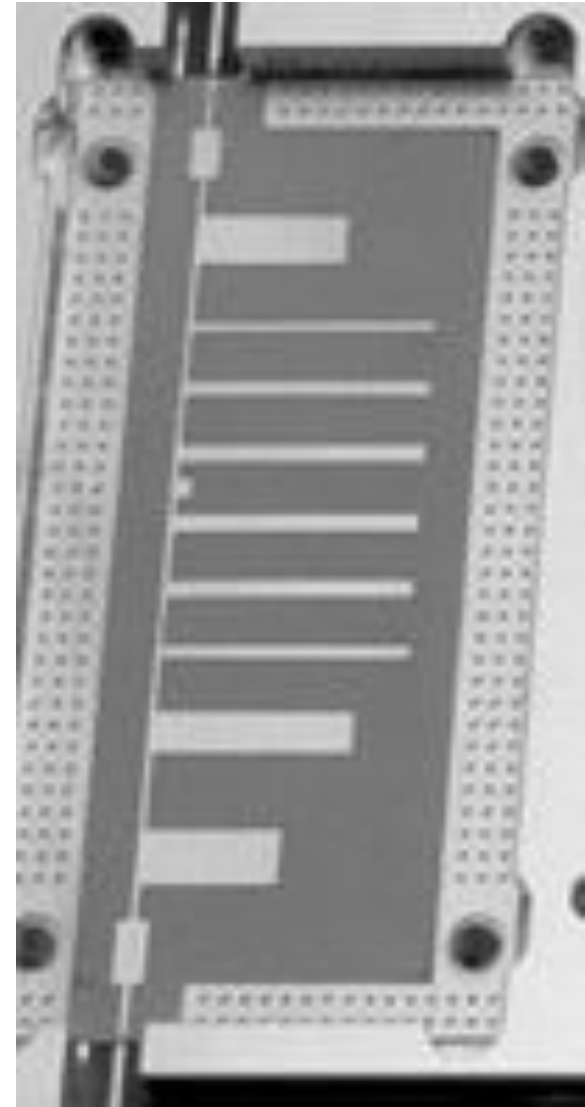
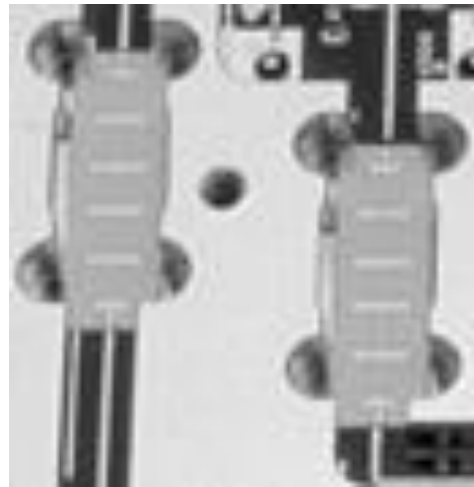


Figure 8.55
Courtesy of LNX Corporation, Salem, N.H.

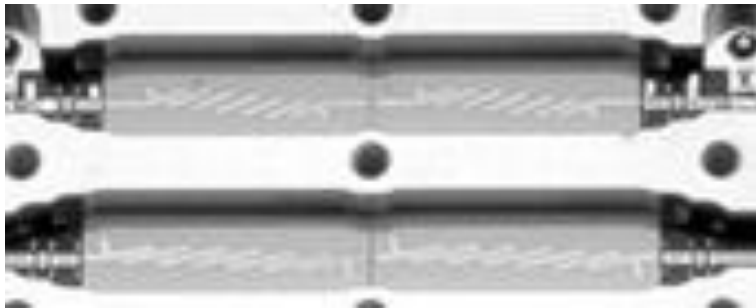

Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.etti.tuiasi.ro>
- rdamian@etti.tuiasi.ro