

Lecture 11

2023/2024

# Microwave Devices and Circuits for Radiocommunications

# 2023/2024

- 2C/1L, **MDCR**
- **Attendance at minimum 7 sessions (course or laboratory)**
- Lectures- **associate professor Radu Damian**
  - Tuesday 16-18, ~~Online~~, P8
  - E – 50% final grade
  - **problems** + (2p atten. lect.) + (3 tests) + (bonus activity)
    - first test L1: 20-27.02.2024 (t2 and t3 not announced, lecture)
    - 3att.=+0.5p
  - **all materials/equipments authorized**

# 2023/2024

- Laboratory – **associate professor Radu Damian**
  - Tuesday 08-12, 11.13 / (08:10)
  - L – 25% final grade
    - ADS, 4 sessions
    - Attendance + **personal results**
  - P – 25% final grade
    - ADS, 3 sessions (-1? 20.02.2024)
    - personal homework

# Materials

■ <http://rf-opto.etti.tuiasi.ro>

The screenshot shows a web browser window with the URL [http://rf-opto.etti.tuiasi.ro/microwave\\_cd.php?chg\\_lang=0](http://rf-opto.etti.tuiasi.ro/microwave_cd.php?chg_lang=0). The page features a dark blue navigation bar with links for Main, Courses, Master, Staff, Research, Students, and Admin. Below this is a secondary navigation bar with links for Microwave CD, Optical Communications, Optoelectronics, Internet, Antennas, Practica, Networks, and Educational software. The main content area is titled "Microwave Devices and Circuits for Radiocommunications (English)" and includes the following information:

- Course: MDCR (2017-2018)**
- Course Coordinator:** Assoc.P. Dr. Radu-Florin Damian
- Code:** EDOS412T
- Discipline Type:** DOS; Alternative, Specialty
- Credits:** 4
- Enrollment Year:** 4, Sem. 7

**Activities**

**Course:** Instructor: Assoc.P. Dr. Radu-Florin Damian, 2 Hours/Week, Specialization Section, Timetable:  
**Laboratory:** Instructor: Assoc.P. Dr. Radu-Florin Damian, 1 Hours/Week, Group, Timetable:

**Evaluation**

Type: **Examen**

**A:** 50%, (Test/Colloquium)  
**B:** 25%, (Seminary/Laboratory/Project Activity)  
**D:** 25%, (Homework/Specialty papers)

**Grades**

[Aggregate Results](#)

**Attendance**

[Course](#)  
[Laboratory](#)

**Lists**

[Bonus-uri acumulate \(final\)](#)  
[Studenti care nu pot intra in examen](#)

**Materials**

**Course Slides**

- [MDCR Lecture 1](#) (pdf, 5.43 MB, en, [↗](#))
- [MDCR Lecture 2](#) (pdf, 3.67 MB, en, [↗](#))
- [MDCR Lecture 3](#) (pdf, 4.76 MB, en, [↗](#))
- [MDCR Lecture 4](#) (pdf, 5.58 MB, en, [↗](#))

On the right side of the screenshot, there is a banner for "RF-OPTO" with the ETTI logo and the University of Technical Sciences (UTS) logo. The banner includes a language selection menu with "English" (circled in red) and "Romana". Below the banner is another navigation bar with links for Main, Courses, Master, Staff, Research, Grades, Student List, Exams, and Photos. The "Exams" link is underlined. Below this is a section titled "Online Exams" with the text "In order to participate at online exams you must get ready following" and a numbered list starting with "1. On the main menu, choose the language you are comfortable with".

# Site



[Main](#) [Courses](#) [Master](#) [Staff](#) [Research](#) [Students](#)

## Microwave and Optoelectronics Laboratory

We are enlisted in the Telecommunications Department of the Electronics, Telecommunication and Information Technology Faculty (ETTI) from the "Gh. Asachi" Technical University (TUIASI) in Iasi, Romania

We currently cover inside ETTI the fields related to:

- Microwave Circuits and Devices
- Optoelectronics
- Information Technology

### Courses

Nr.	Course	Shortcut	Code	Type	Semester	Credits	Weekly	Examination	Link
1	Microwave Devices and Circuits for Radiocommunications	DCMR	DOS412T	DOS	7	4	0P,1L,0S,2C	Exam	<a href="#">details</a>
2	Monolithic Microwave Integrated Circuits	CIMM	RD.IA.207	DOMS	11	6	1.5L,0S,2C,0P	Exam	<a href="#">details</a>
3	Advanced Techniques in the Design of the Radio-communications Systems	TAPSR	RD.IA.103	DIMS	9	6	1.5P,0L,0S,2C	Exam	<a href="#">details</a>
4	Optical Communications	CO	DOS409T	DOS	7	5	0P,1L,0S,3C	Colloquium	<a href="#">details</a>
5	Optical Communications	OC	EDOS409T	DOS	7	5	0P,1L,0S,3C	Exam	<a href="#">details</a>
6	Satellite Communications	CS	RC.IA.104	DIMS	9	6	0L,0S,2C,1.5P	Exam	<a href="#">details</a>
7	Applied Informatics 1	IA1	DOF135	DOF	1	4	0P,1L,0S,2C	Verification	<a href="#">details</a>
8	Applied Informatics 1	AI1	EDOF135	DOF	1	4	0P,1L,0S,2C	Verification	<a href="#">details</a>
9	Databases, Web Programming and Interfacing	DWPI	ITT.IA.601	DIS	11	5	1P,1L,0.25S,1C	Verification	<a href="#">details</a>
10	Web Applications Design	PAW	RC.IA.108	DIMS	10	5	1L,0S,1.5C,1P	Exam	<a href="#">details</a>
11	Optoelectronics	OPTO	DID405M	DID	8	4	0P,1L,0S,2C	Colloquium	<a href="#">details</a>
12	Microwave Devices and Circuits for Radiocommunications (English)	MDCR	EDOS412T	DOS	8	4	0P,1L,0S,2C	Exam	<a href="#">details</a>



# Materials

- RF-OPTO
  - <http://rf-opto.etti.tuiasi.ro>
- **David Pozar, “Microwave Engineering”,**  
Wiley; 4th edition , 2011
  - 1 exam problem ← Pozar
- Photos
  - sent by email/**online exam > Week4-Week6**
  - used at lectures/laboratory

# Online – Registration no.

- access to **online exams** requires the **password** received by email

The password is communicated during the lectures. It is necessary to

**Password**

**Registration no.**

**Name of the student**



**Proposed email 1**

**Proposed email 2**

**Write the code below**

6fb6953

Send

 **RF-OPTO** 

English | Romana |

Main Courses Master Staff Research **Students**

Login Tutoring

**Login**

Use the Registration no. and your email or the password received by email

**Registration no.**

**Email/Password**

**Write the code below**

5dd64f9

Send

# Password

## ■ received by email

Important message from RF-OPTO Inbox x

 **Radu-Florin Damian**  
to me, POPESCU ▾

🗣️ Romanian ▾ > English ▾ [Translate message](#)



Laboratorul de Microunde si Optoelectronica  
Facultatea de Electronica, Telecomunicatii si Tehnologia Informatiei  
Universitatea Tehnica "Gh. Asachi" Iasi

**In atentia: POPESCU GOPO ION**

Parola pentru a accesa examenele pe server-ul **rf-opto** este  
Parola: [REDACTED]

Identificati-va pe [server](#), cu parola, cat mai rapid, pentru confirmare.

**Memorati** acest mesaj intr-un loc sigur, pentru utilizare ulterioara

**Attention: POPESCU GOPO ION**

The password to access the exams on the **rf-opto** server is  
Password: [REDACTED]

Login to the [server](#), with this password, as soon as possible, for confirmation.

**Save** this message in a safe place for later use

[↩ Reply](#) [↩↩ Reply all](#) [➡ Forward](#)

Subject

Subject	Correspondents
Important message from RF-OPTO	POPESCU GOPO ION
Validation of MD/CR exam from 02/05/2020	[REDACTED]
[REDACTED]	[REDACTED]

From Me <rdamian@etti.tuiasi.ro> ★

Subject **Important message from RF-OPTO**

To [REDACTED]

Cc Me <rdamian@etti.tuiasi.ro> ★



Laboratorul de Microunde si Optoelectronica  
Facultatea de Electronica, Telecomunicatii si Tehnologia Informatiei  
Universitatea Tehnica "Gh. Asachi" Iasi

**In atentia: POPESCU GOPO ION**

Parola pentru a accesa examenele pe server-ul **rf-opto** este  
Parola: [REDACTED]

Identificati-va pe [server](#), cu parola, cat mai rapid, pentru confirmare.

**Memorati** acest mesaj intr-un loc sigur, pentru utilizare ulterioara

**Attention: POPESCU GOPO ION**

The password to access the exams on the **rf-opto** server is  
Password: [REDACTED]

Login to the [server](#), with this password, as soon as possible, for confirmation.

**Save** this message in a safe place for later use



# Online exam manual

- The online exam app used for:
  - ~~lectures (attendance)~~
  - laboratory
  - project
  - ~~examinations~~

## Materials

### Other data

[Manual examen on-line](#) (pdf, 2.65 MB, ro, 🇷🇴)

[Simulare Examen](#) (video) (mp4, 65.12 MB, ro, 🇷🇴)

## Microwave Devices and Circuits (Englis

# Examen online

- always against a **timetable**
  - long period (lecture attendance/laboratory results)
  - ~~short period (tests: 15min, exam: 2h)~~

<b>Announcement</b> 23:59 (10/05/2020)	<b>Support material</b> 00:05 (11/05/2020)	<b>Exam Topics</b> 00:07 (11/05/2020)	<b>Results</b> 00:10 (11/05/2020)	<b>End</b> 00:20 (15/05/2020)	<b>Confirmation</b> 00:20 (16/05/2020)	Next timeframe in: 05 m 43 s <a href="#">Refresh now</a>
---	---	--	--------------------------------------	----------------------------------	---	--

**Announcement**

This is a "fake" exam, introduced to familiarize you with the server interface and to perform the necessary actions during an exam: thesis scan, selfie, use email for co

**Server Time**

All exams are based on the server's time zone (it may be different from local time). For reference time on the server is now:

10/05/2020 23:59:16

# Online results submission

- many numerical values/files

Schema finala	Rezultate - castig	Rezultate - zgomot	Fisier justificare calcul (factor andrei)	Fisier zap (optional)	T1, fisier parametri S	T2, fisier parametri S	Z1	Z2	Z3	Z4	Z5	Z6	Z7	Ze1	Zo1	Ze2	Zo2	Ze3	Zo3	Ze4	Zo4	Ze5	Zo5	Ze6
86 - 5428 - 259 ...	86 - 5428 - 260 ...	86 - 5428 - 261 ...	86 - 5428 - 316 ...	-	86 - 5428 - 314 ...	86 - 5428 - 315 ...	148.33	155.88	202.12	164.35	180.91	30.29	185.19	79.9	37	68.89	45.14	61.83	45.05	57.97	46.02	61.85	45.05	68.8
86 - 5622 - 259 ...	86 - 5622 - 260 ...	86 - 5622 - 261 ...	86 - 5622 - 316 ...	86 - 5622 - 262 ...	86 - 5622 - 314 ...	86 - 5622 - 315 ...	26.97	153.5	34.64	35.79	55.56	26.212	10.693	0	0	0	0	0	0	0	0	0	0	0
86 - 5488 - 259 ...	86 - 5488 - 260 ...	86 - 5488 - 261 ...	86 - 5488 - 316 ...	86 - 5488 - 262 ...	86 - 5488 - 314 ...	86 - 5488 - 315 ...	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
86 - 5391 - 259 ...	86 - 5391 - 260 ...	86 - 5391 - 261 ...	86 - 5391 - 316 ...	-	-	-	50	50	50	50	50	50	50	70.14	40.39	61.85	44.59	55.7	45.2	54.89	45.38	58.65	45.8	70.0
86 - 5664 - 259 ...	86 - 5664 - 260 ...	86 - 5664 - 261 ...	86 - 5664 - 316 ...	-	86 - 5664 - 314 ...	86 - 5664 - 315 ...	168.02	150.5	178.28	133.75	92.12	121.67	144.48	94.36	36.19	70.77	42.56	65.69	42.05	55.17	42.29	65.59	42.05	70.7
86 - 5665 - 259 ...	86 - 5665 - 260 ...	86 - 5665 - 261 ...	86 - 5665 - 316 ...	-	86 - 5665 - 314 ...	86 - 5665 - 315 ...	162.2	80.8	209.2	140.85	135.1	183.7	167.6	94.58	36.15	78.16	39.77	65.57	45.05	65.57	45.05	78.16	39.77	94.5
86 - 5433 - 259 ...	86 - 5433 - 260 ...	86 - 5433 - 261 ...	86 - 5433 - 316 ...	-	86 - 5433 - 314 ...	86 - 5433 - 315 ...	165.138	106.228	226.157	130.134	72.71	180.177	164.616	101.36	36.11	77.22	42.49	68.02	45.62	60	45.42	68.02	45.62	77.2
86 - 5608 - 259 ...	86 - 5608 - 260 ...	86 - 5608 - 261 ...	86 - 5608 - 316 ...	-	86 - 5608 - 314 ...	86 - 5608 - 315 ...	150.84	152.5	30.94	32.37	54.36	19.837	29.85	64.14	40.145	54.32	46.32	53.8	46.7	53.8	46.7	54.32	46.32	54.9
86 - 5555 - 259 ...	86 - 5555 - 260 ...	86 - 5555 - 261 ...	86 - 5555 - 316 ...	-	86 - 5555 - 314 ...	86 - 5555 - 315 ...	168.001	150.288	178.399	133.115	92.491	121.257	144.126	97.05	36.16	71.13	43.09	65.45	42.12	55.66	42.18	65.45	42.12	71.1

# Online results submission

- many numerical values

	Z1	Z2	Z3	Z4	Z5	Z6	Z7
	148.33	155.88	202.12	164.35	180.91	30.29	185.19
	25.97	153.5	34.64	35.79	55.56	26.212	10.692
	0	0	0	0	0	0	0
	50	50	50	50	50	50	50




# Online results submission

**Grade = Quality of the work +  
+ Quality of the submission**

Impedance Matching

# Impedance Matching with Stubs

# Smith chart, $r=1$ and $g=1$

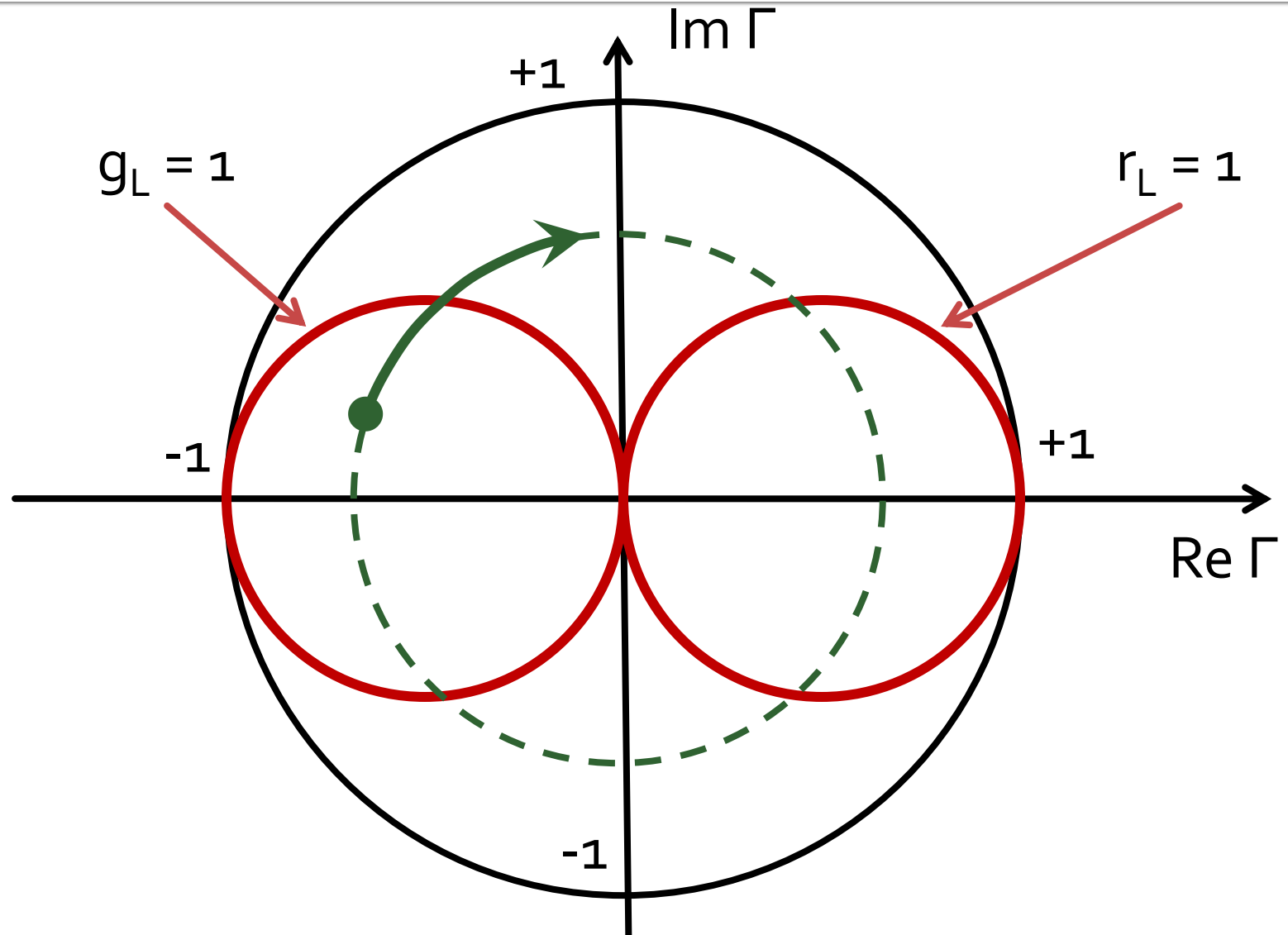

# Analytical solutions


Exam / Project

---




# Case 1, Shunt Stub

- Shunt Stub

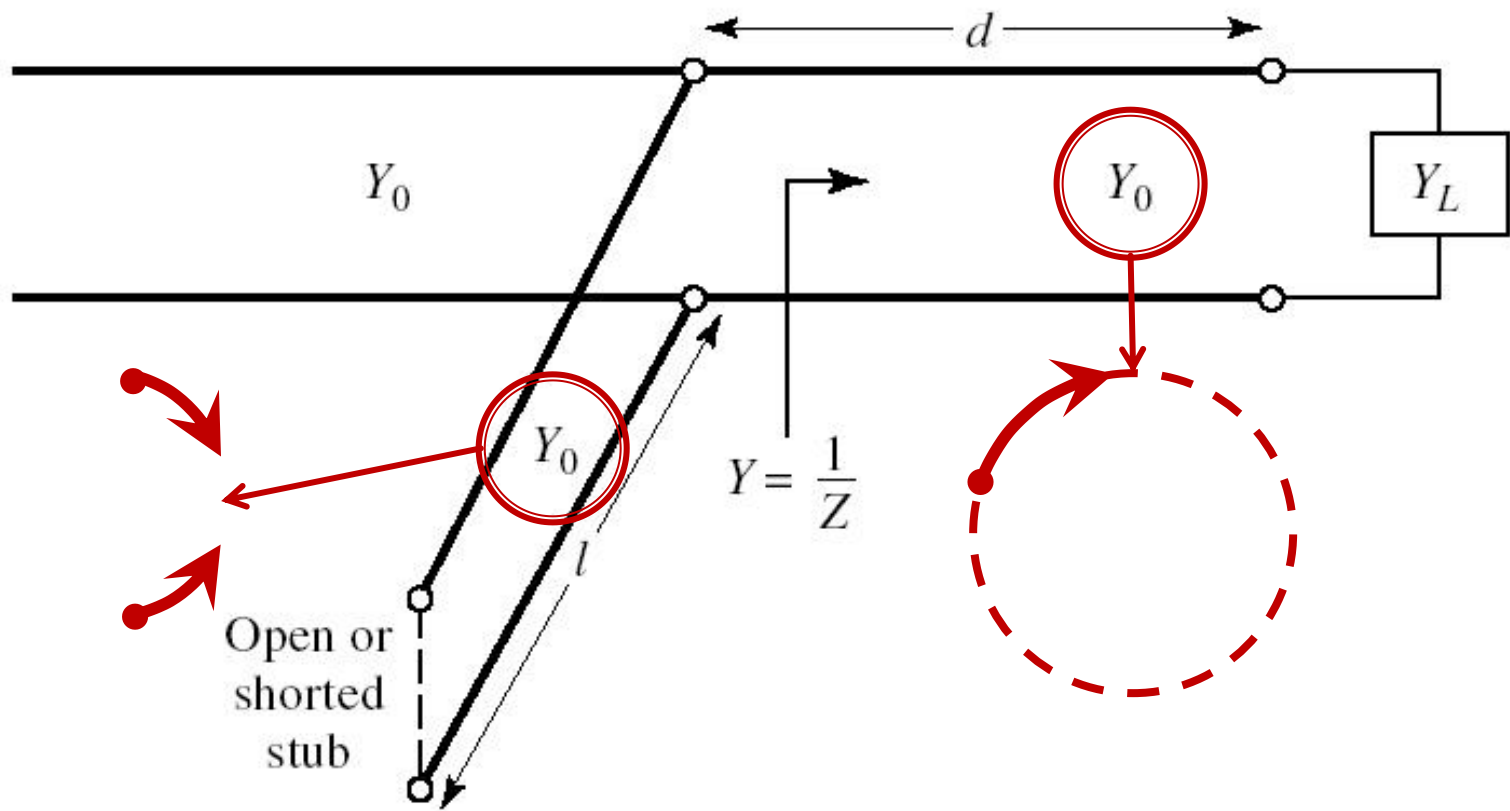
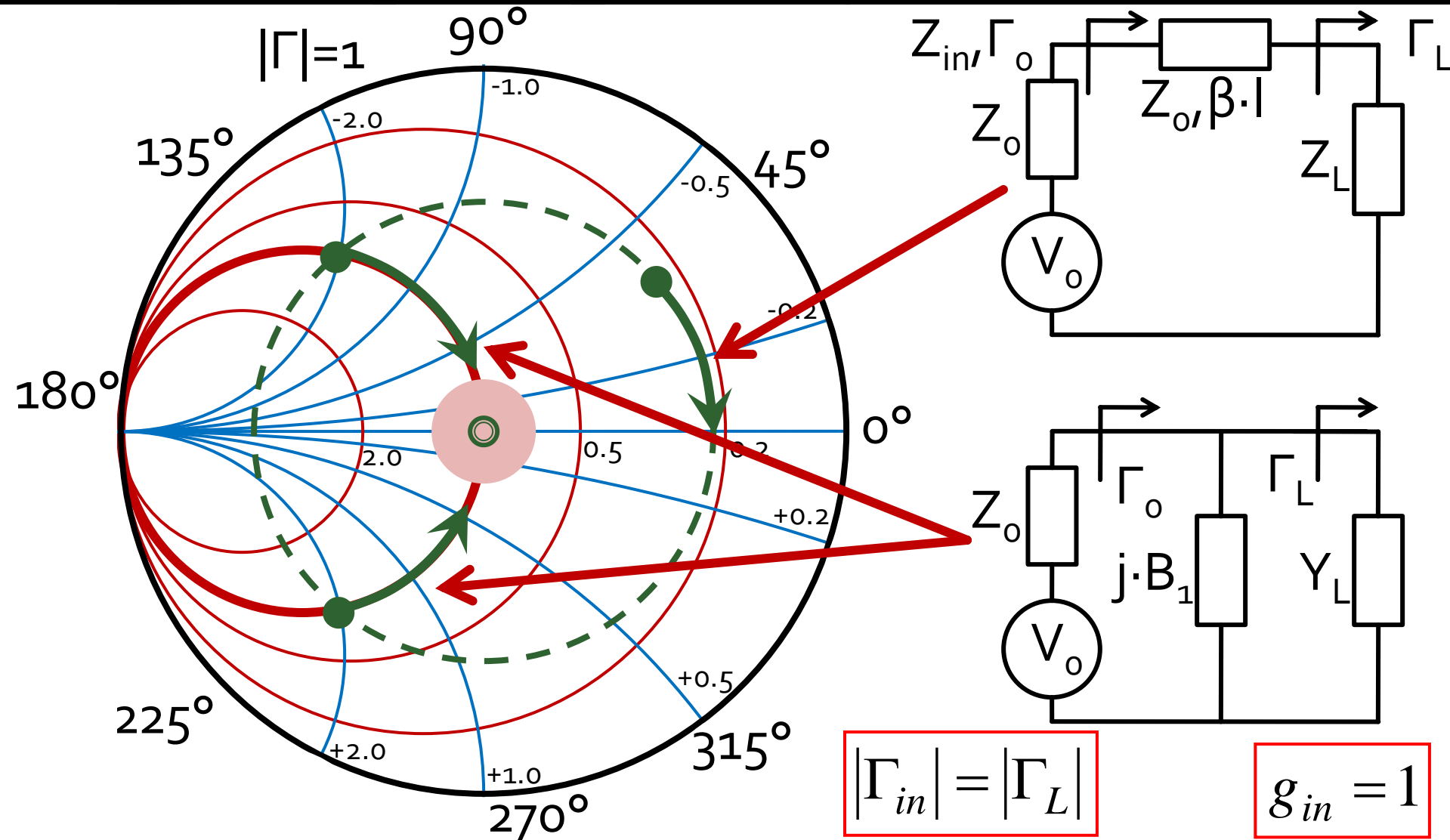
# Matching, series line + shunt susceptance



# Analytical solution, usage

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = 0.593 \angle 46.85^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ \quad \cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **"+" solution** ↓

$$(46.85^\circ + 2\theta) = +126.35^\circ \quad \theta = +39.7^\circ \quad \text{Im } y_S = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.472$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_S) = -55.8^\circ (+180^\circ) \rightarrow \theta_{sp} = 124.2^\circ$$

- **"-" solution** ↓

$$(46.85^\circ + 2\theta) = -126.35^\circ \quad \theta = -86.6^\circ (+180^\circ) \rightarrow \theta = 93.4^\circ$$

$$\text{Im } y_S = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +1.472 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_S) = 55.8^\circ$$

# Analytical solution, usage

$$(\varphi + 2\theta) = \begin{cases} +126.35^\circ \\ -126.35^\circ \end{cases} \quad \theta = \begin{cases} 39.7^\circ \\ 93.4^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -1.472 \\ +1.472 \end{cases} \quad \theta_{sp} = \begin{cases} -55.8^\circ + 180^\circ = 124.2^\circ \\ +55.8^\circ \end{cases}$$



- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

$$l_1 = \frac{39.7^\circ}{360^\circ} \cdot \lambda = 0.110 \cdot \lambda$$

$$l_2 = \frac{124.2^\circ}{360^\circ} \cdot \lambda = 0.345 \cdot \lambda$$


$$l_1 = \frac{93.4^\circ}{360^\circ} \cdot \lambda = 0.259 \cdot \lambda$$
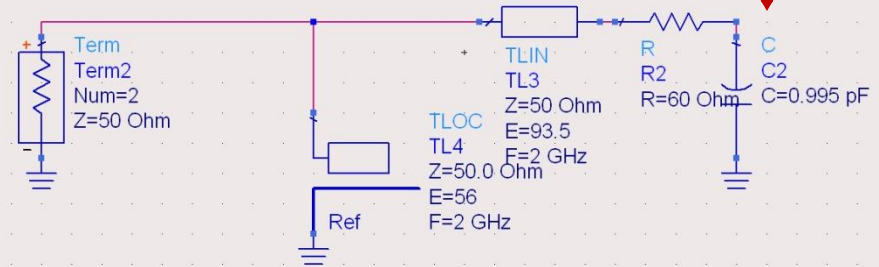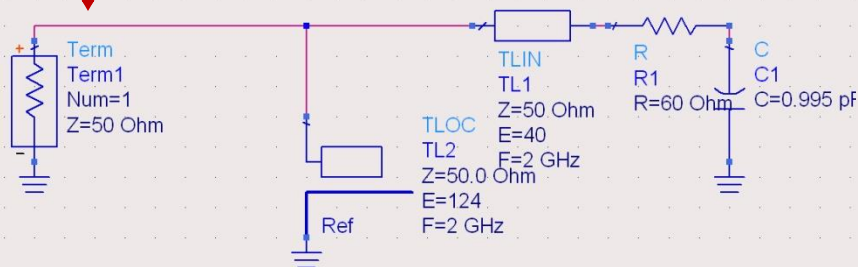
$$l_2 = \frac{55.8^\circ}{360^\circ} \cdot \lambda = 0.155 \cdot \lambda$$





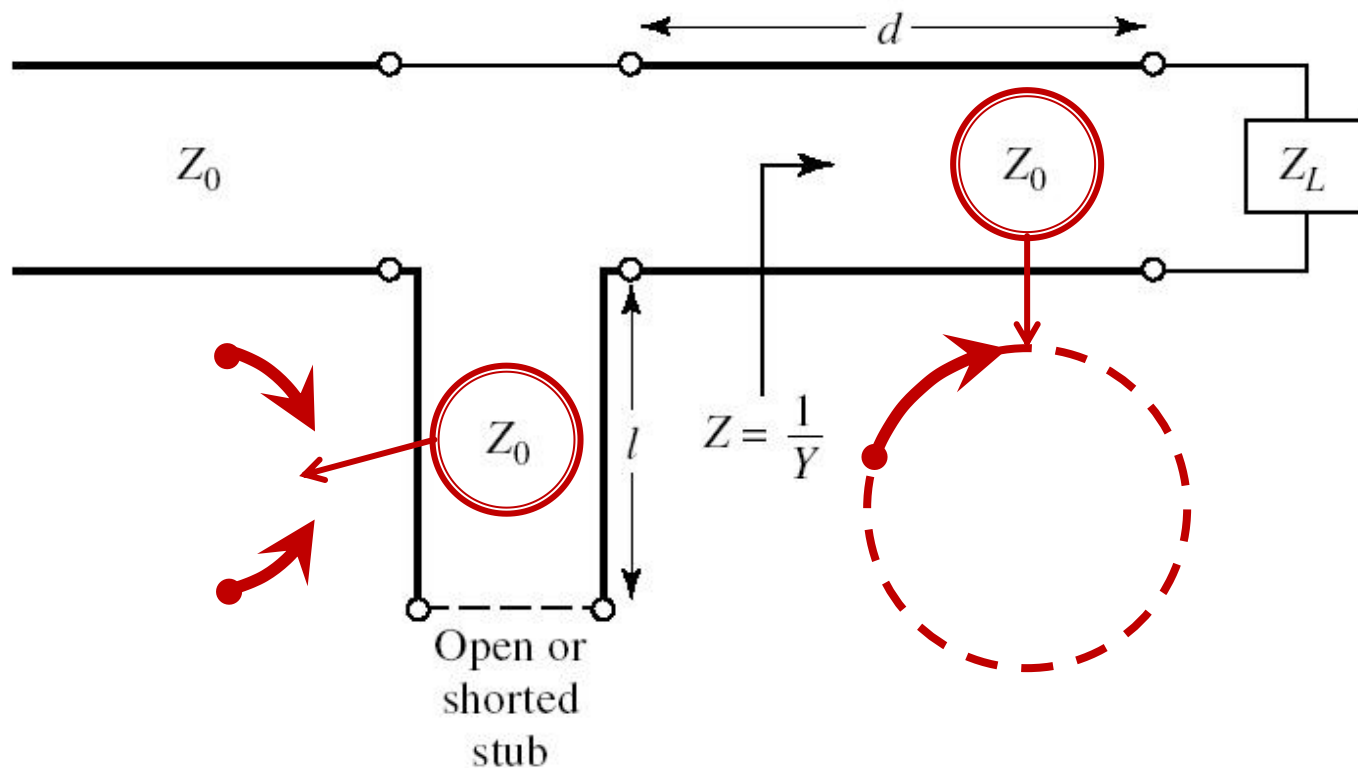
# Case 2, Series Stub

- Series Stub
- difficult to realize in single conductor line technologies (microstrip)


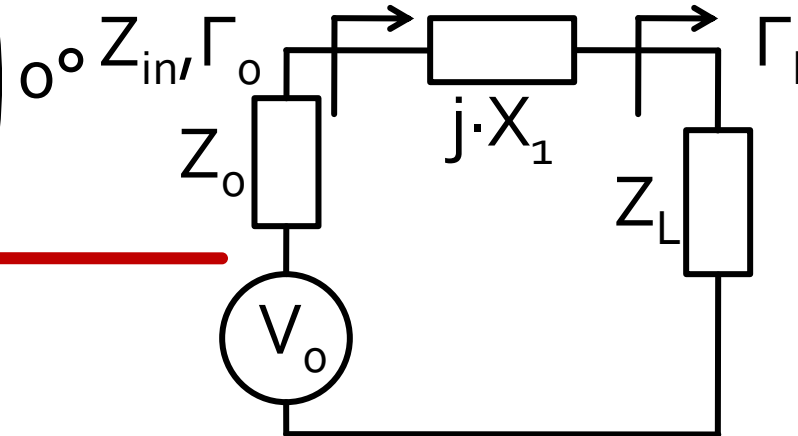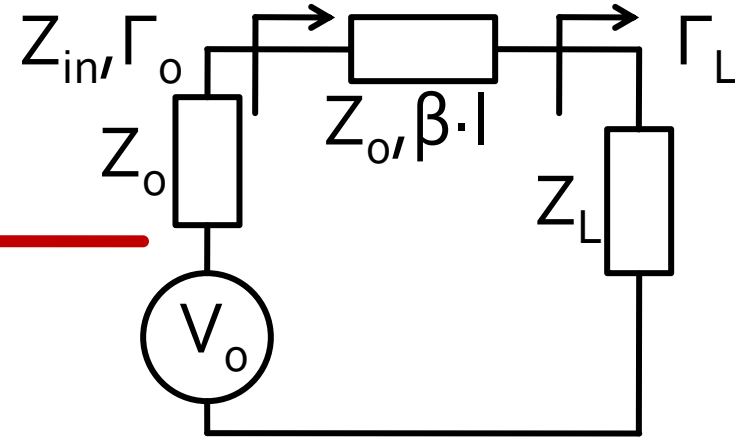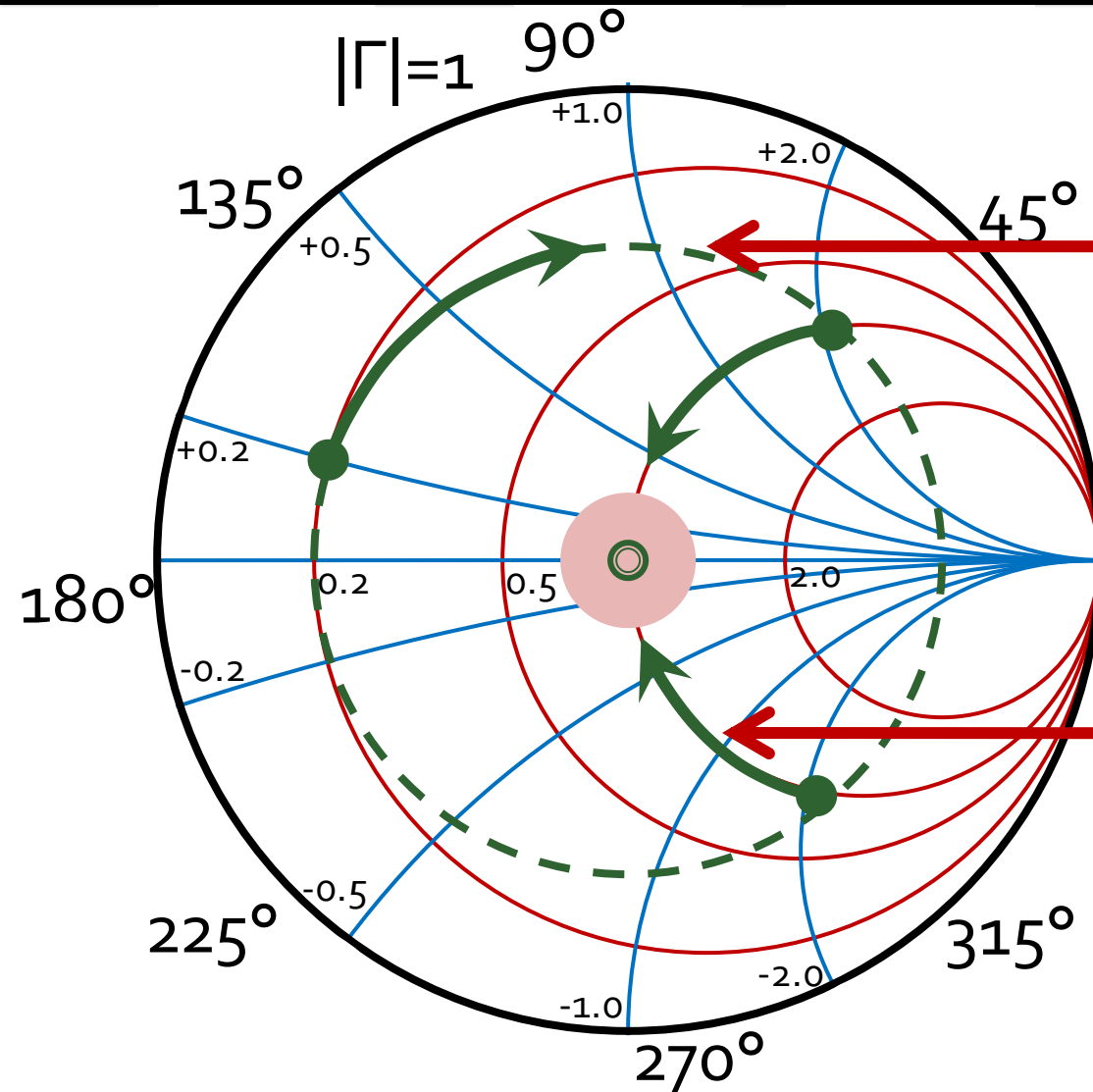
# Matching, series line + series reactance



$$|\Gamma_{in}| = |\Gamma_L|$$

$$r_{in} = 1$$

# Analytical solution, usage

$$\cos(\varphi + 2\theta) = |\Gamma_s|$$

$$\theta_{ss} = \beta \cdot l = \cot^{-1} \frac{\mp 2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}}$$

$$\Gamma_s = 0.555 \angle -29.92^\circ$$

$$|\Gamma_s| = 0.555; \quad \varphi = -29.92^\circ \quad \cos(\varphi + 2\theta) = 0.555 \Rightarrow (\varphi + 2\theta) = \pm 56.28^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

- **"+" solution** ↓

$$(-29.92^\circ + 2\theta) = +56.28^\circ \quad \theta = 43.1^\circ \quad \text{Im } z_s = \frac{+2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} = +1.335$$

$$\theta_{ss} = -\cot^{-1}(\text{Im } z_s) = -36.8^\circ (+180^\circ) \rightarrow \theta_{ss} = 143.2^\circ$$

- **"-" solution** ↓

$$(-29.92^\circ + 2\theta) = -56.28^\circ \quad \theta = -13.2^\circ (+180^\circ) \rightarrow \theta = 166.8^\circ$$

$$\text{Im } z_s = \frac{-2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} = -1.335 \quad \theta_{ss} = -\cot^{-1}(\text{Im } z_s) = 36.8^\circ$$

# Analytical solution, usage

$$(\varphi + 2\theta) = \begin{cases} +56.28^\circ \\ -56.28^\circ \end{cases} \quad \theta = \begin{cases} 43.1^\circ \\ 166.8^\circ \end{cases} \quad \text{Im}[z_s(\theta)] = \begin{cases} +1.335 \\ -1.335 \end{cases} \quad \theta_{ss} = \begin{cases} -36.8^\circ + 180^\circ = 143.2^\circ \\ +36.8^\circ \end{cases}$$

- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

$$l_1 = \frac{43.1^\circ}{360^\circ} \cdot \lambda = 0.120 \cdot \lambda$$

$$l_2 = \frac{143.2^\circ}{360^\circ} \cdot \lambda = 0.398 \cdot \lambda$$

$$l_1 = \frac{166.8^\circ}{360^\circ} \cdot \lambda = 0.463 \cdot \lambda$$

$$l_2 = \frac{36.8^\circ}{360^\circ} \cdot \lambda = 0.102 \cdot \lambda$$





# Stub, observations

- adding or subtracting **180°** ( $\lambda/2$ ) doesn't change the result (full rotation around the Smith Chart)

$$E = \beta \cdot l = \pi = 180^\circ \quad l = k \cdot \frac{\lambda}{2}, \forall k \in \mathbf{N}$$


- if the lines/stubs result with **negative** "length"/ "electrical length" we add  $\lambda/2$  /  $180^\circ$  to obtain physically realizable lines
- adding or subtracting **90°** ( $\lambda/4$ ) change the stub impedance:

$$Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l \quad \Leftrightarrow \quad Z_{in,g} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$

- for the stub we can add or subtract  $90^\circ$  ( $\lambda/4$ ) while in the same time changing **open-circuit**  $\Leftrightarrow$  **short-circuit**

# Microwave Amplifiers

# Amplifier as two-port

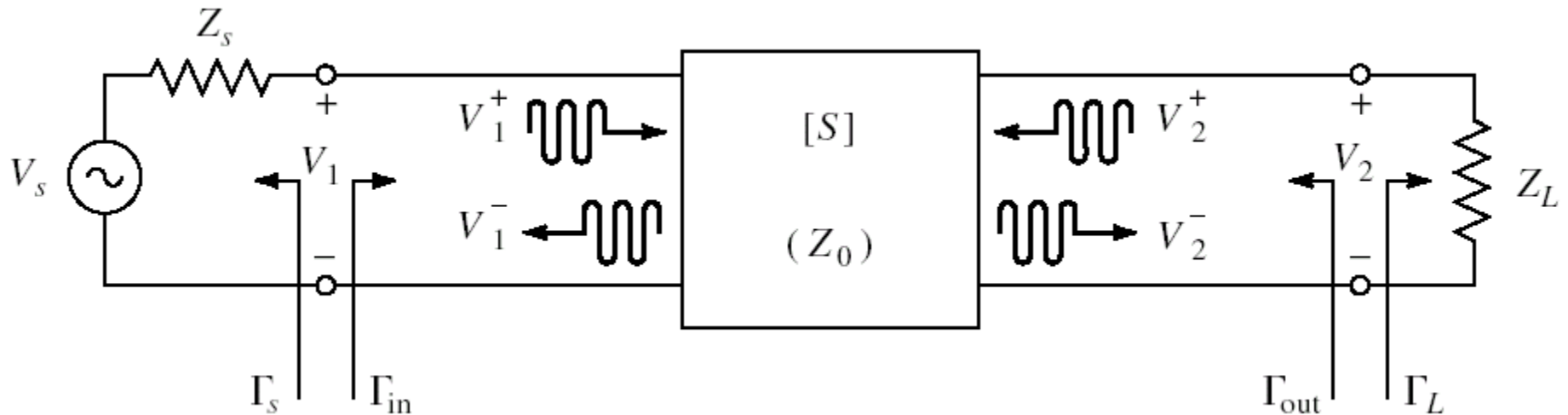


$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_s}{1 - S_{11} \cdot \Gamma_s}$$
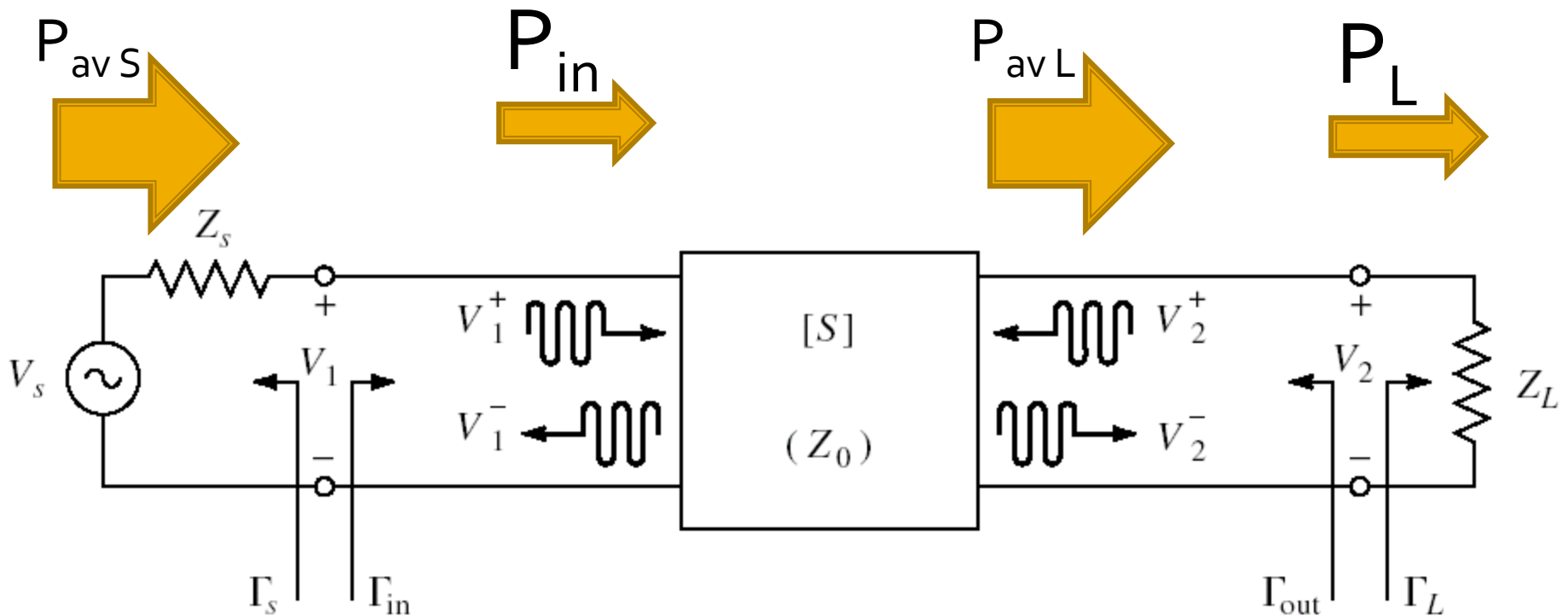
# Power / Matching

- Two ports in which matching influences the power transfer



# Two-Port Power Gains

- **Available** power gain

$$G_A = \frac{P_{av L}}{P_{av S}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2)}{|1 - S_{22} \cdot \Gamma_L|^2 \cdot (1 - |\Gamma_{out}|^2)}$$

- **Transducer** power gain

$$G_T = \frac{P_L}{P_{av S}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2}$$

$$\Gamma_{in} = \Gamma_{in}(\Gamma_L)$$

- **Unilateral transducer** power gain

$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$S_{12} \cong 0$$


$$\Gamma_{in} = S_{11}$$

Input and output can be treated independently

Microwave Amplifiers

# Stability

# Amplifier as two-port

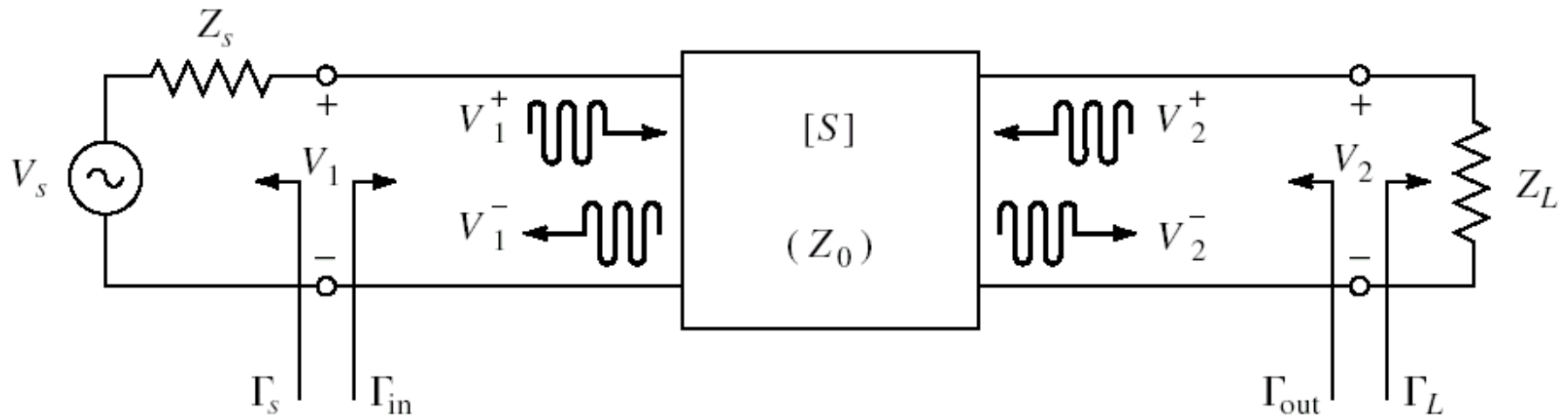


- For an amplifier two-port we are interested in:
  - **stability**
  - power gain
  - noise (sometimes – small signals)
  - linearity (sometimes – large signals)

Microwave Amplifiers

# Power Gain of Microwave Amplifiers




# Amplifier as two-port

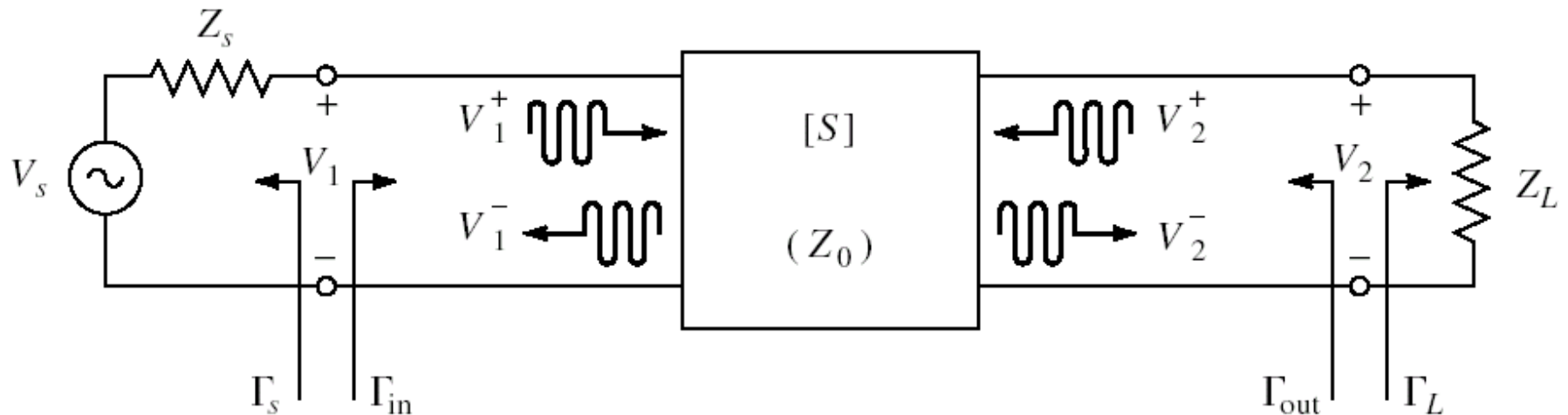

- For an amplifier two-port we are interested in:
  - stability
  - **power gain**
  - noise (sometimes – small signals)
  - linearity (sometimes – large signals)

# Design for Maximum Gain

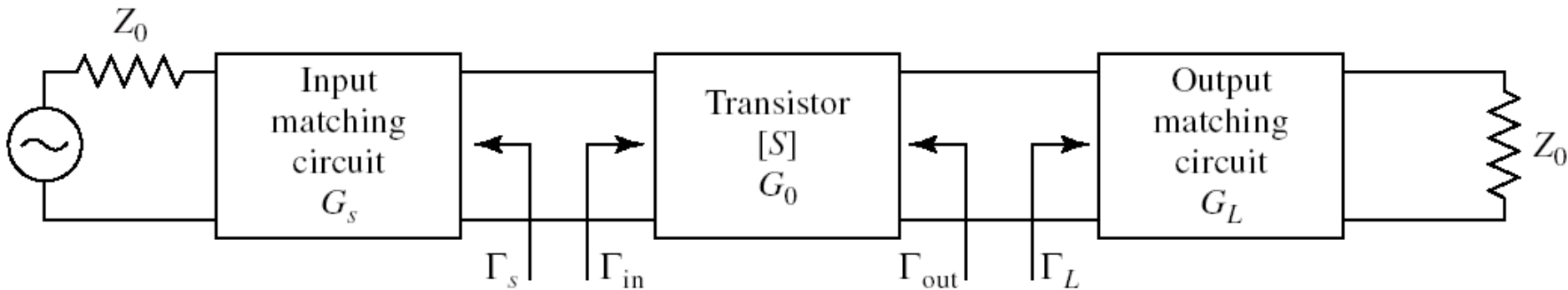

- Maximum power gain (complex conjugate matching):

$$\Gamma_{in} = \Gamma_S^* \quad \Gamma_{out} = \Gamma_L^*$$

- For lossless matching sections

$$G_{T \max} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2} \quad G_{T \max} = \frac{1}{1 - |\Gamma_S|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

- For the general case of the bilateral transistor ( $S_{12} \neq 0$ )

$\Gamma_{in}$  and  $\Gamma_{out}$  depend on each other so the input and output sections must be matched simultaneously

# Simultaneous matching

$$\Delta \cdot (S_{11}^* \cdot S_{22}^* - S_{12}^* \cdot S_{21}^*) = |\Delta|^2$$

$$\Gamma_S^2 \cdot \underbrace{(S_{11} - \Delta \cdot S_{22}^*)}_C + \Gamma_S \cdot \underbrace{(|\Delta|^2 - |S_{11}|^2 + |S_{22}|^2 - 1)}_{-B} + \underbrace{(S_{11}^* - \Delta^* \cdot S_{22})}_{C^*} = 0$$

- A quadratic equation

$$\Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

- Similarly

$$\Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

- With variables defined as:

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases} \quad \begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

# Simultaneous matching

- Simultaneous matching can be achieved **if and only if** the amplifier is **unconditionally stable** at the operating frequency, and  $|\Gamma| < 1$  solutions are those with “-” sign of quadratic solutions

$$\Gamma_S = \frac{B_1 - \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$


$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases}$$

$$\Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

$$\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

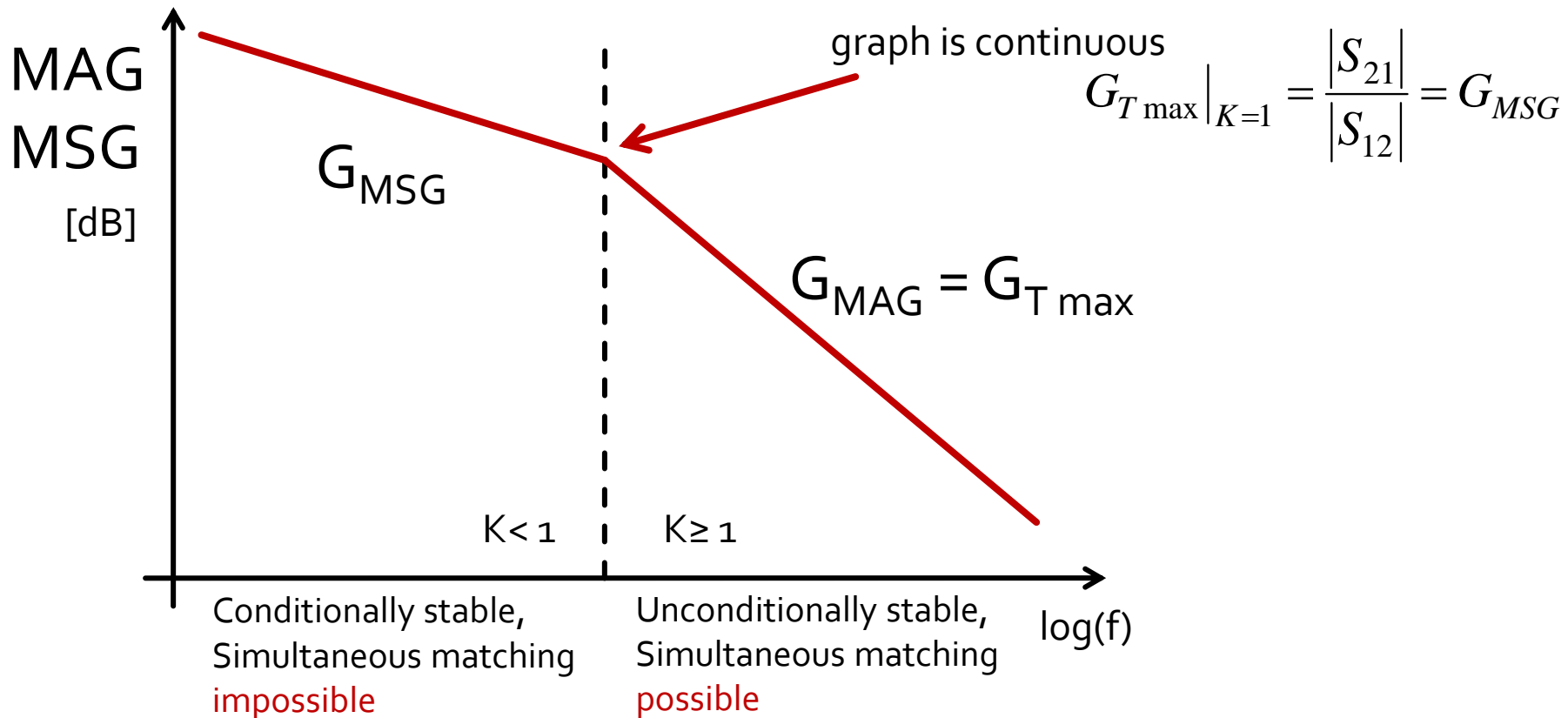
# Maximum Available Gain

- Indicator across full frequency range of the capability to obtain a power gain


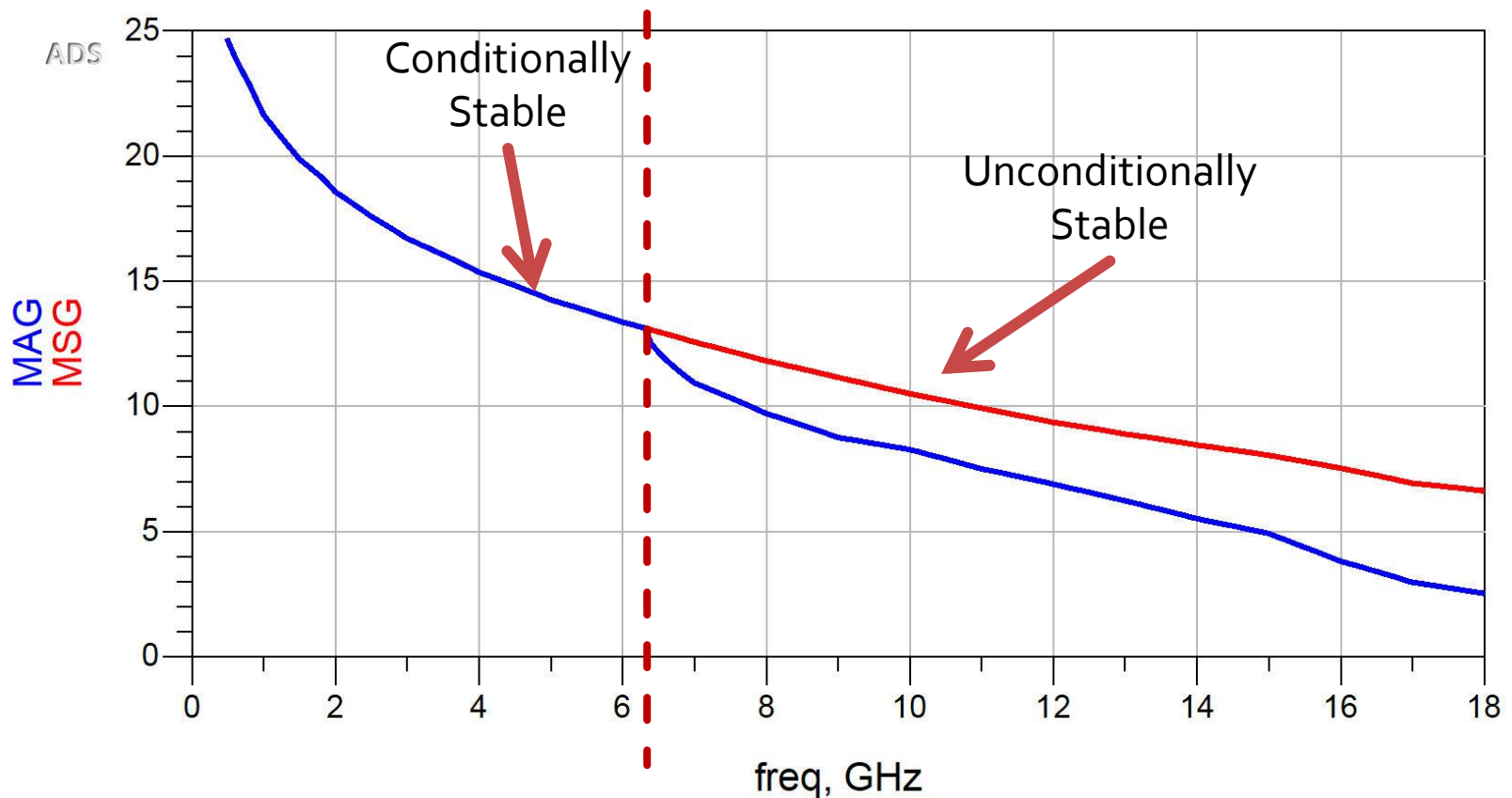
# MAG/MSG

- ATF-34143 at  $V_{ds}=3V$   $I_d=20mA$ .
- @0.5÷18GHz



Microwave Amplifiers

# Design for Specified Gain

# Design for Specified Gain

- Assumes the amplifier device **unilateral**

Input and output can be treated independently

$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$S_{12} \cong 0$$

$$\Gamma_{in} = S_{11}$$

- Maximum power gain

$$\Gamma_S = S_{11}^*$$

$$\Gamma_L = S_{22}^*$$

$$G_{TU \max} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2}$$



# Unilateral figure of merit


- Allows estimation of the error introduced by the unilateral assumption

$$\frac{1}{(1+U)^2} < \frac{G_T}{G_{TU}} < \frac{1}{(1-U)^2} \quad U = \frac{|S_{12}| \cdot |S_{21}| \cdot |S_{11}| \cdot |S_{22}|}{(1-|S_{11}|^2) \cdot (1-|S_{22}|^2)}$$

- We compute U then the maximum and minimum deviation of  $G_{TU}$  from  $G_T$ 
  - this deviation must be accounted in the design as a reserve gain against the target gain

$$-20 \cdot \log(1+U) < G_T [dB] - G_{TU} [dB] < -20 \cdot \log(1-U)$$

# Design for Specified Gain

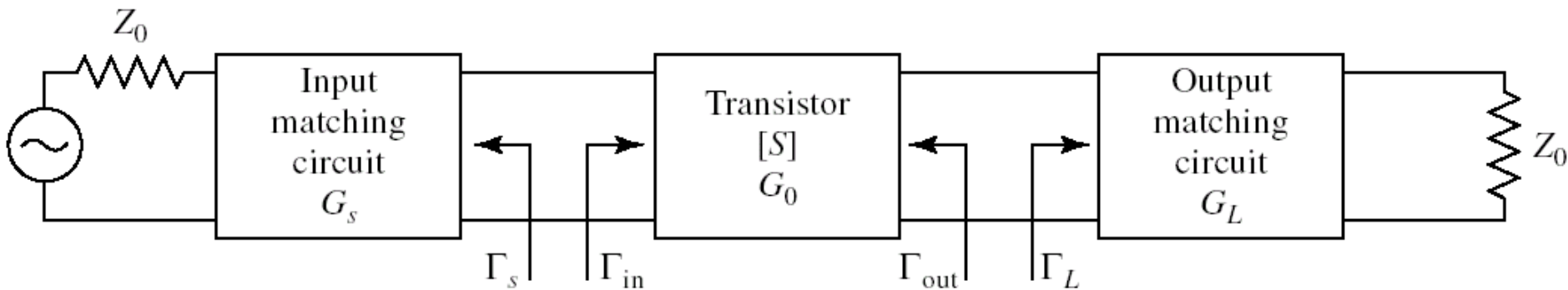

- In the unilateral assumption:

$$G_{TU} = \frac{1 - |\Gamma_s|^2}{|1 - S_{11} \cdot \Gamma_s|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$G_S = \frac{1 - |\Gamma_s|^2}{|1 - S_{11} \cdot \Gamma_s|^2}$$


$$G_S = G_S(\Gamma_s)$$

$$G_0 = |S_{21}|^2$$

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$


$$G_L = G_L(\Gamma_L)$$

# $G_S(\Gamma_S)$

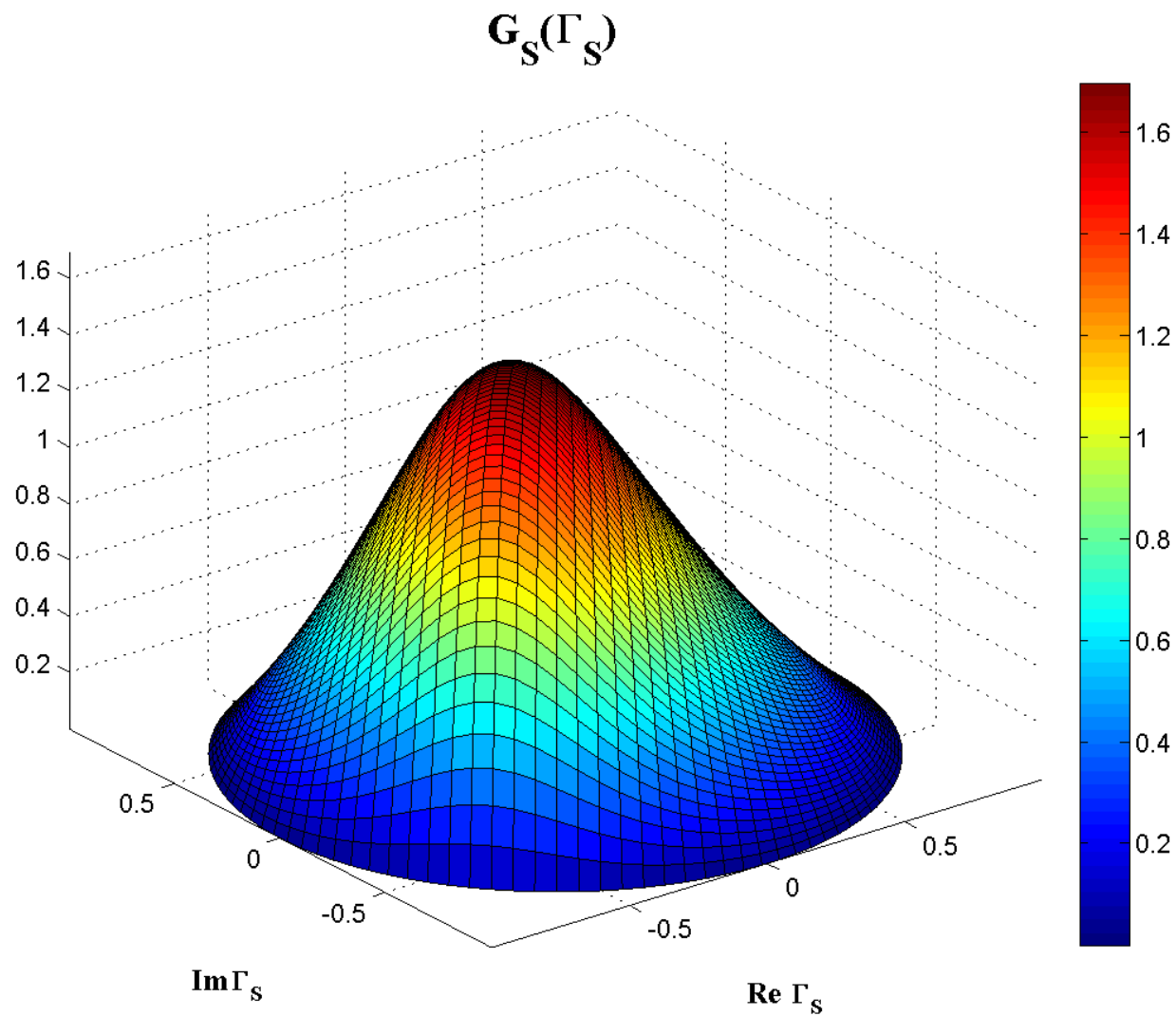


$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2}$$
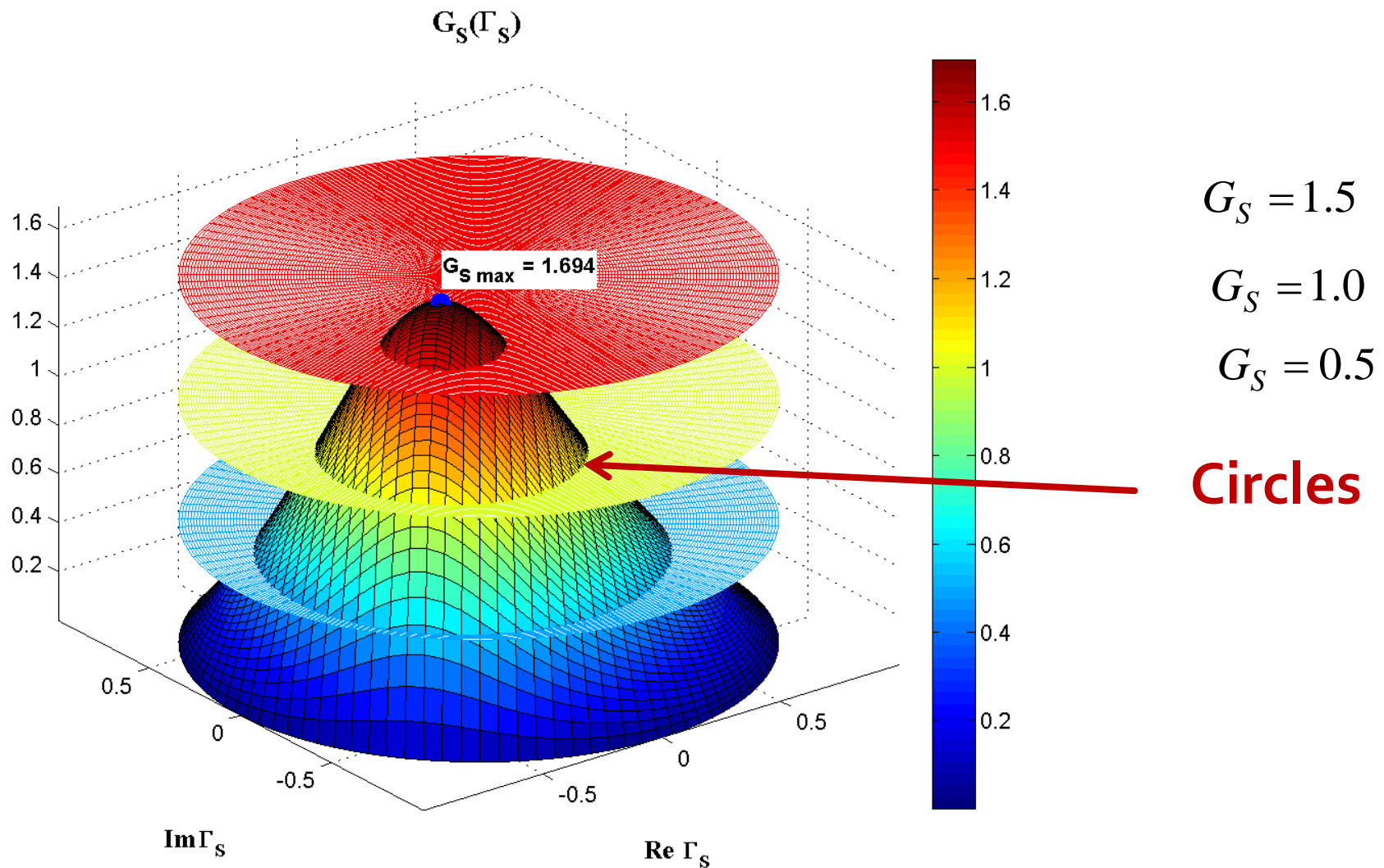
# $G_S(\Gamma_S)$ , constant value contours





# Contour map/lines


contoured peak  
(side view)

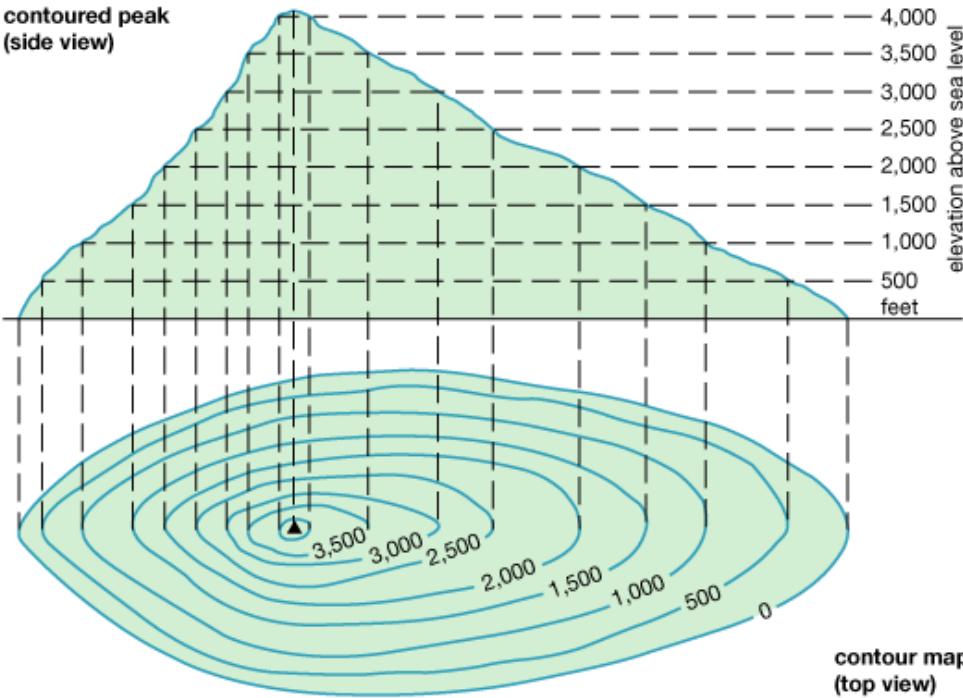

© 2011 Encyclopædia Britannica, Inc.

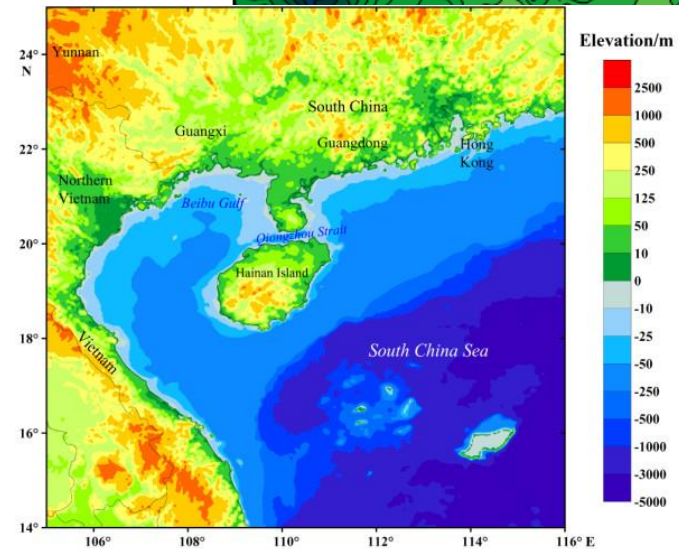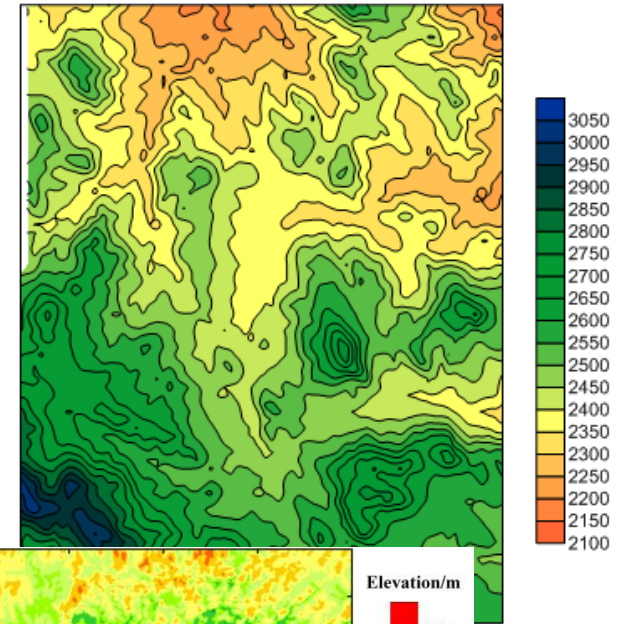


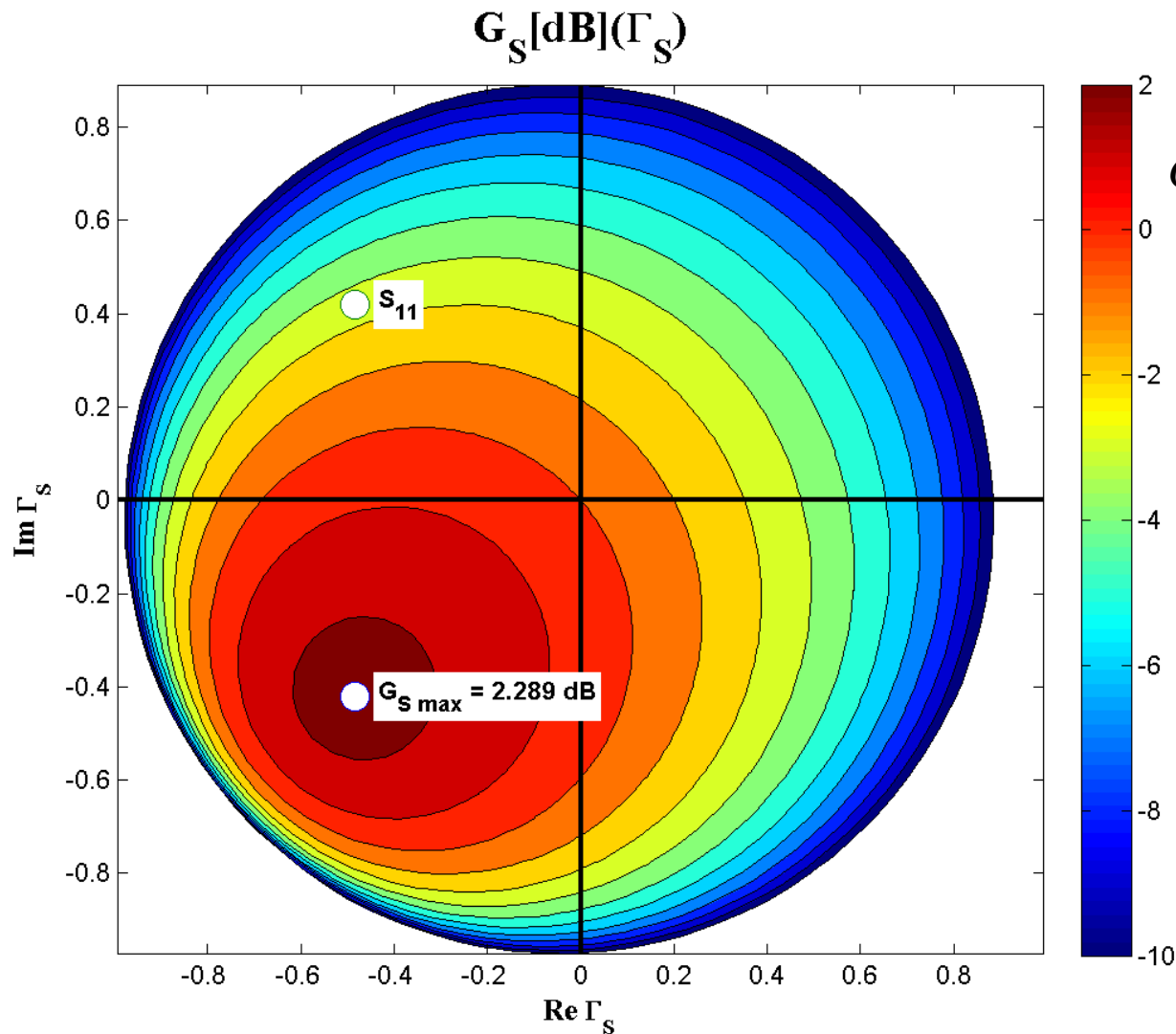
# $G_S[dB](\Gamma_S)$ , constant value contours



$$G_S[dB] = 10 \cdot \log \left( \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \right)$$

$$G_{S \max} = G_S \Big|_{\Gamma_S = S_{11}^*}$$

# ADS

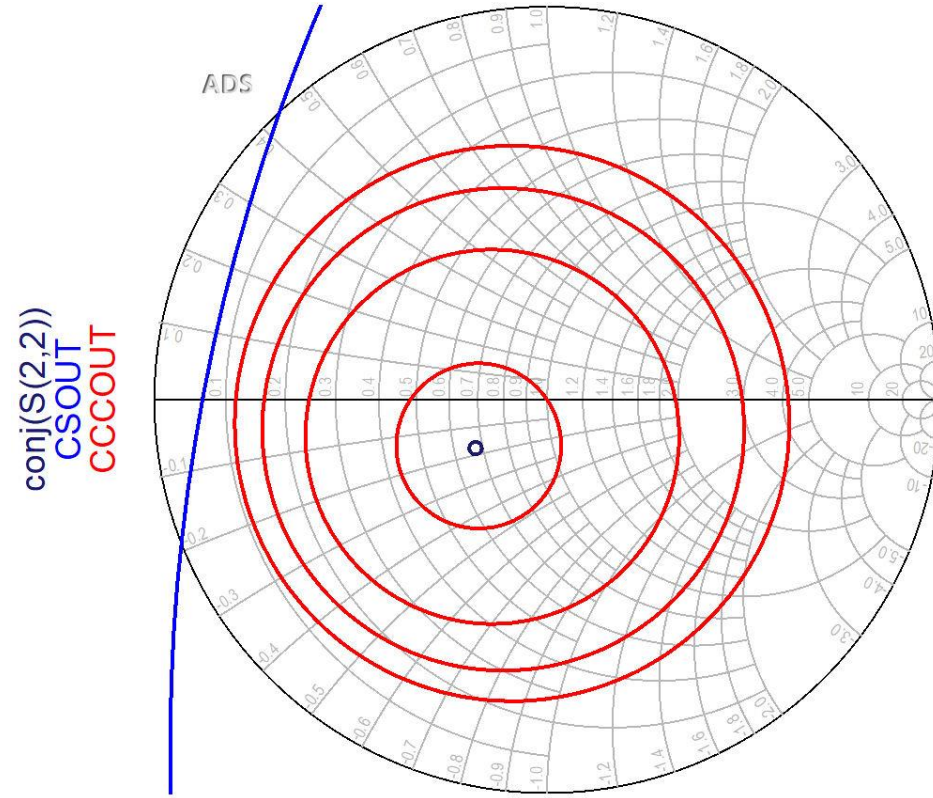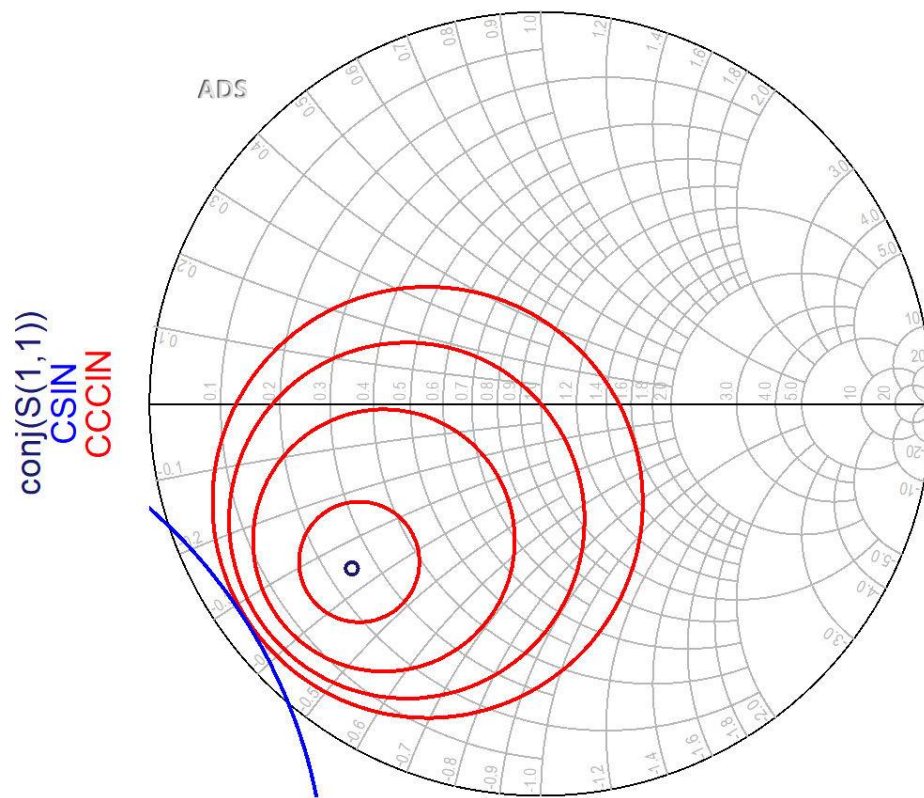

- Circles are plotted for requested values (**in dB!**)
- It is useful to compute  $G_{S_{\max}}$  and  $G_{L_{\max}}$  before
  - in order to request relevant circles

**Continue**


---



Microwave Amplifiers

# Low-Noise Amplifier Design


# Amplifier as two-port

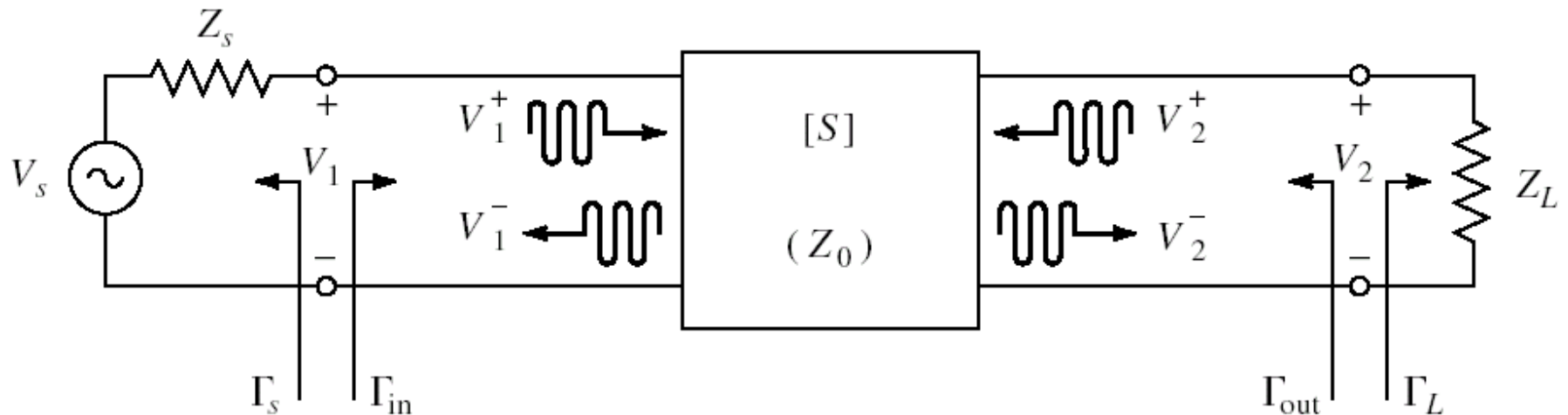

- For an amplifier two-port we are interested in:
  - stability
  - power gain
  - **noise** (sometimes – **small signals**)
  - linearity (sometimes – large signals)
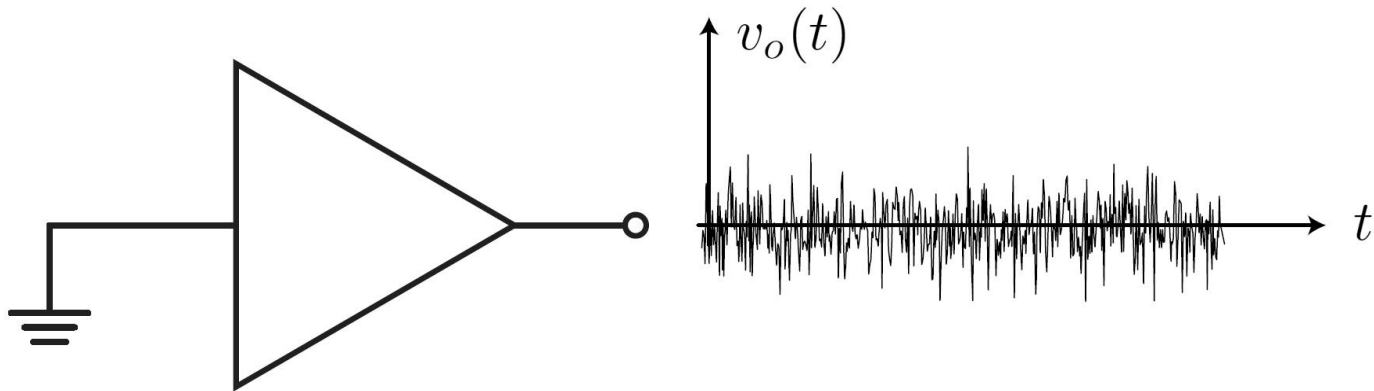
# Noise

- Noise: random fluctuations of the signal




$$\overline{v_n(t)} = \langle v_n(t) \rangle = \frac{1}{T} \int_0^T v_n(t) dt = 0$$

$$\overline{v_n^2(t)} = \langle v_n^2(t) \rangle = \frac{1}{T} \int_0^T v_n^2(t) dt \neq 0$$

$$V_{n(e\text{f})} = \sqrt{\overline{v_n^2(t)}}$$

# Noise

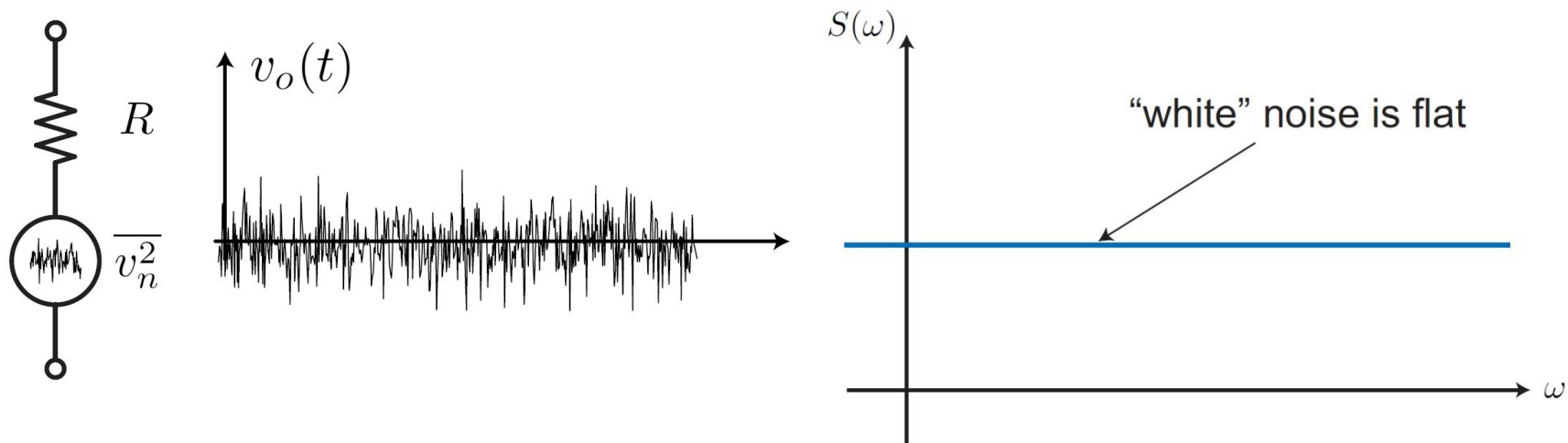


- effective noise voltage

$$V_{n(e\text{f})} = \sqrt{4kTBR}$$

- noise power available (for maximum power transfer with impedance/resistance matching)

$$P_n = kTB$$

# Noise Figure F

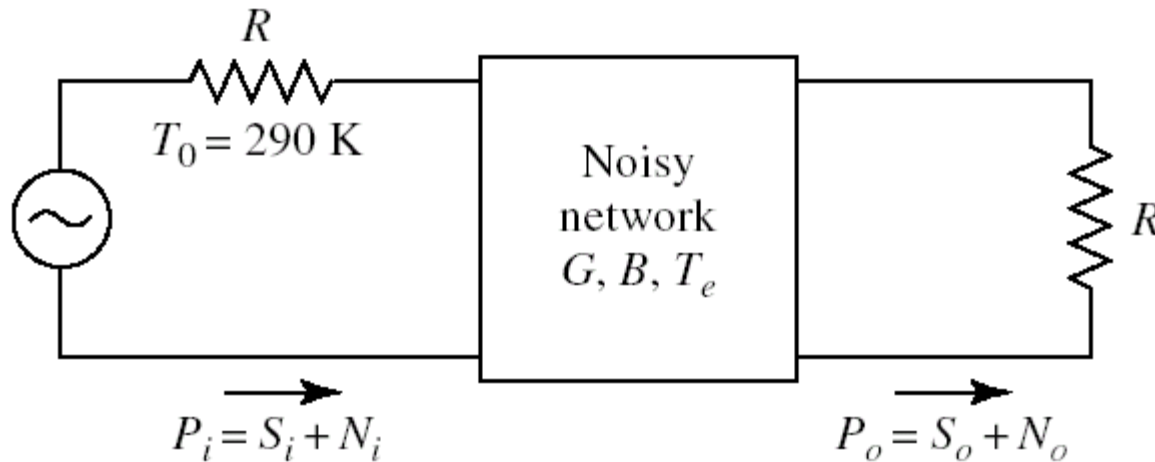


- The noise figure  $F$ , is a measure of the reduction in signal-to-noise ratio between the input and output of a device, when (by definition) the input noise power is assumed to be the noise power resulting from a matched resistor at  $T_0 = 290\text{ K}$  (reference noise conditions)

$$F = \left. \frac{S_i/N_i}{S_o/N_o} \right|_{T_0=290K}$$

$$V_{n(e_f)} = \sqrt{4kTBR}$$

$$P_n = kTB$$


# Noise Figure F

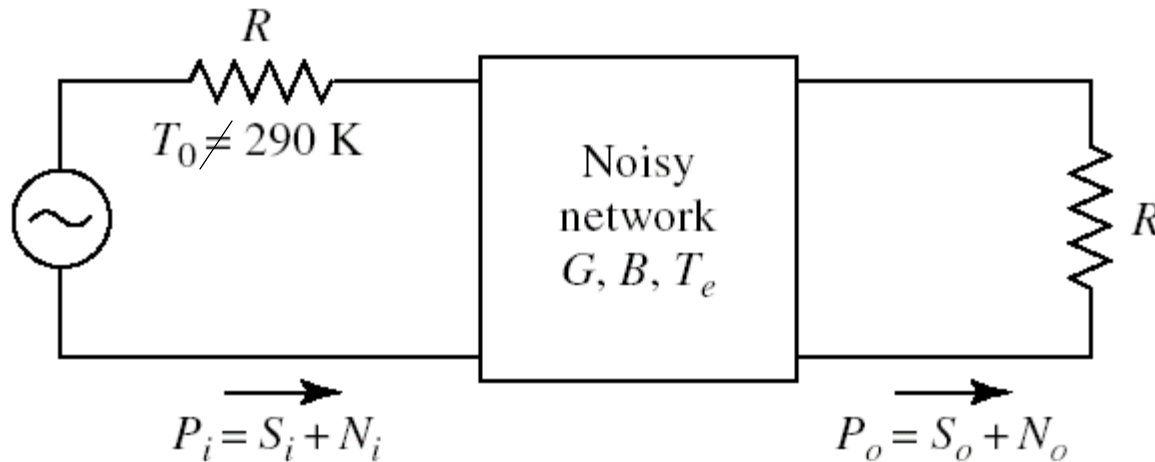

- The noise figure  $F$ , **is not** directly a measure of the reduction in signal-to-noise ratio between the input and output of a device, when the input noise power is different from that of the reference noise conditions


$$F \neq \left. \frac{S_i/N_i}{S_o/N_o} \right|_{T_0 \neq 290 \text{ K}}$$

# Noise Figure F

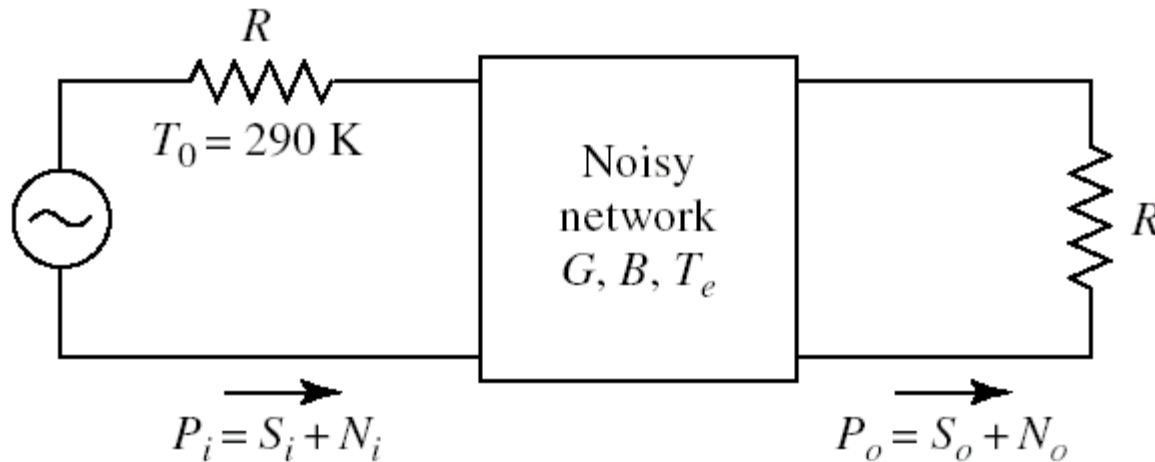

- In general, the output noise power consists of two elements:
  - the input noise power amplified or attenuated by the device (for example amplified with the power gain  $G$  applied also to the desired signal)
  - a noise power generated internally by the network if the network is noisy (this power **does not** depend on the input noise power)

# Noise Figure F

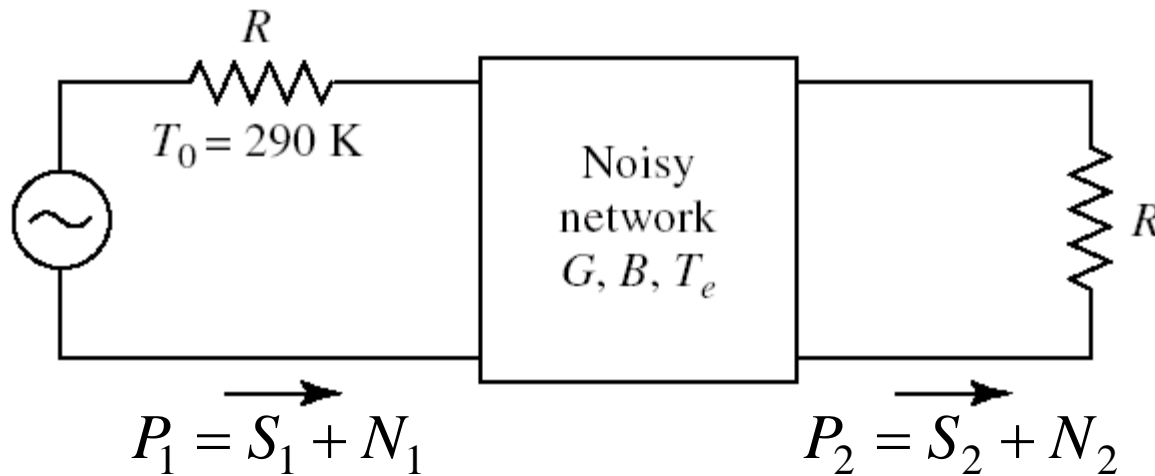

- Estimation of the internally generated noise power can be done using the Noise Figure  $F$  definition:


$$F = \left. \frac{S_1/N_1}{S_2/N_2} \right|_{T_0=290\text{K}, N_1=N_0}$$

$$N_2 = F \cdot N_0 \cdot \frac{S_2}{S_1} = F \cdot N_0 \cdot G$$

$$N_2 = N_0 \cdot G + (F - 1) \cdot N_0 \cdot G$$



# Noise Figure F

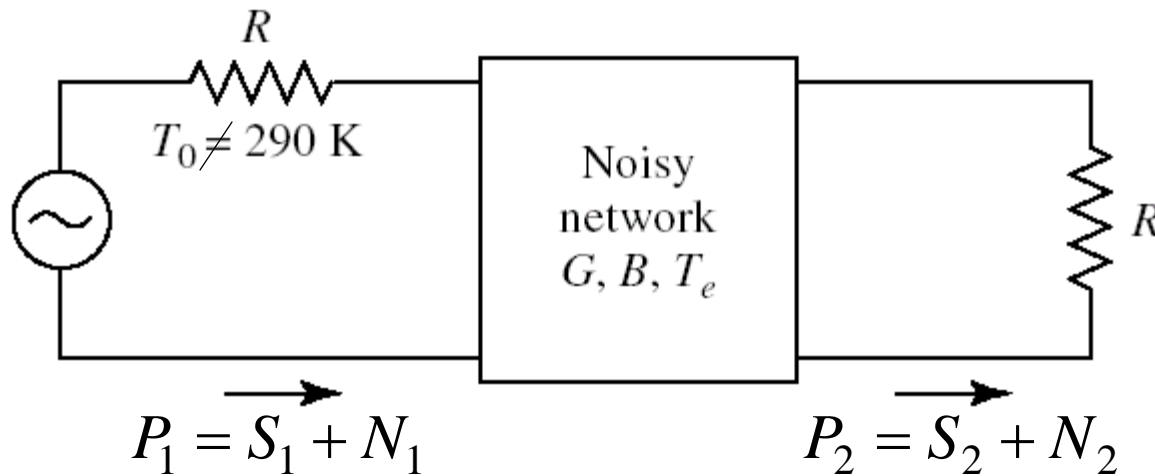



- We identify the two terms:
  - amplified input noise
  - internally generated noise
- When the input noise does not correspond to reference noise conditions ( $N_1 \neq N_0$ )
  - the internally generated noise does not change

$$N_2 = N_0 \cdot G + (F - 1) \cdot N_0 \cdot G$$

$$N_2 = N_1 \cdot G + (F - 1) \cdot N_0 \cdot G$$



# Noise figure of a cascaded system

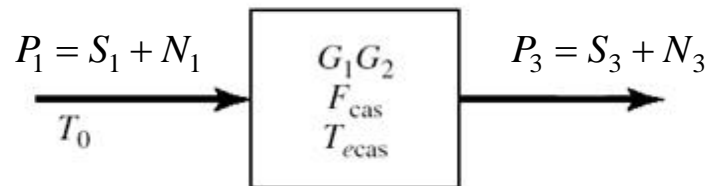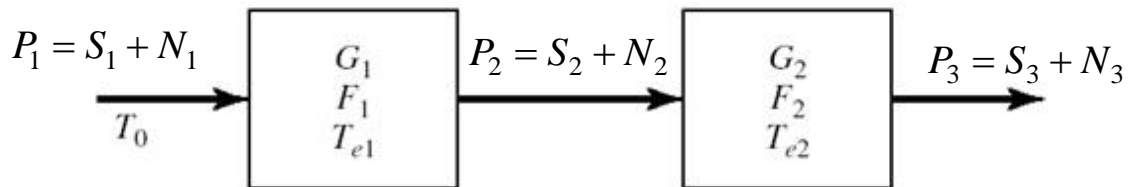

$$N_2 = N_1 \cdot G_1 + (F_1 - 1) \cdot N_0 \cdot G_1$$

$$G_{cas} = G_1 \cdot G_2$$

$$N_3 = N_2 \cdot G_2 + (F_2 - 1) \cdot N_0 \cdot G_2$$



$$N_3 = N_1 \cdot G_{cas} + (F_{cas} - 1) \cdot N_0 \cdot G_{cas}$$



$$N_3 = [N_1 \cdot G_1 + (F_1 - 1) \cdot N_0 \cdot G_1] \cdot G_2 + (F_2 - 1) \cdot N_0 \cdot G_2$$

$$N_3 = N_1 \cdot G_1 \cdot G_2 + (F_1 - 1) \cdot N_0 \cdot G_1 \cdot G_2 + (F_2 - 1) \cdot N_0 \cdot G_2$$

# Noise figure of a cascaded system

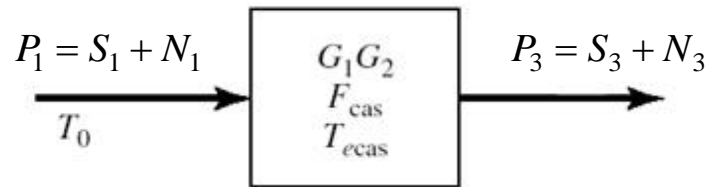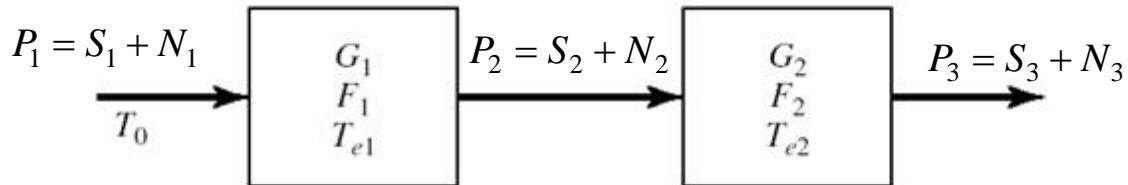


$$N_3 = N_1 \cdot G_1 \cdot G_2 + (F_1 - 1) \cdot N_0 \cdot G_1 \cdot G_2 + (F_2 - 1) \cdot N_0 \cdot G_2$$

$$G_{cas} = G_1 \cdot G_2 \quad N_3 = N_1 \cdot G_{cas} + (F_{cas} - 1) \cdot N_0 \cdot G_{cas}$$


$$(F_1 - 1) \cdot N_0 \cdot G_1 \cdot G_2 + (F_2 - 1) \cdot N_0 \cdot G_2 = (F_{cas} - 1) \cdot N_0 \cdot G_1 \cdot G_2$$

$$F_{cas} = F_1 + \frac{1}{G_1} (F_2 - 1)$$

# Noise figure of a cascaded system

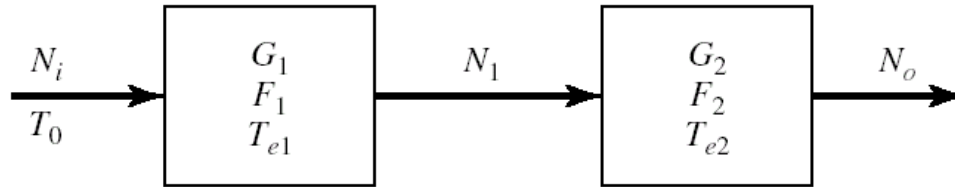

(a)

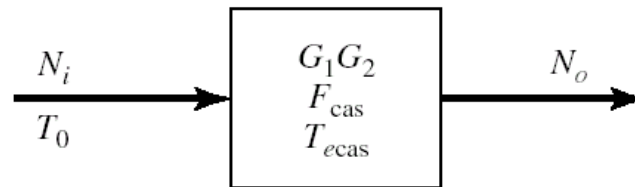

(b)

$$G_{cas} = G_1 \cdot G_2 \qquad F_{cas} = F_1 + \frac{1}{G_1} (F_2 - 1)$$

- Friis Formula (!linear scale)

$$F_{cas} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 \cdot G_2} + \frac{F_4 - 1}{G_1 \cdot G_2 \cdot G_3} + \dots$$

# Friis Formula (noise)

$$F_{cas} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 \cdot G_2} + \frac{F_4 - 1}{G_1 \cdot G_2 \cdot G_3} + \dots$$

- Friis Formula shows that:
  - the overall noise figure of a cascaded system is largely determined by the noise characteristics of the first stage
  - the noise introduced by the following stages is reduced:
    - -1
    - division by G (usually  $G > 1$ )

# Friis Formula (noise)

$$F_{cas} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 \cdot G_2} + \frac{F_4 - 1}{G_1 \cdot G_2 \cdot G_3} + \dots$$


- Effects of Friis Formula:
- in multi stage amplifiers:
  - it's essential that the first stage is as noiseless as possible even if that means sacrificing power gain
  - the following stages can be optimized for power gain
- in single stage amplifiers:
  - in the input matching circuit it's important to have noiseless elements (pure reactance, lossless lines)
  - output matching circuit has less influence on the noise (noise generated at this level appears when the desired signal has already been amplified by the transistor)

$$V_{n(ef)} = \sqrt{4kTBR}$$

$$P_n = kTB$$
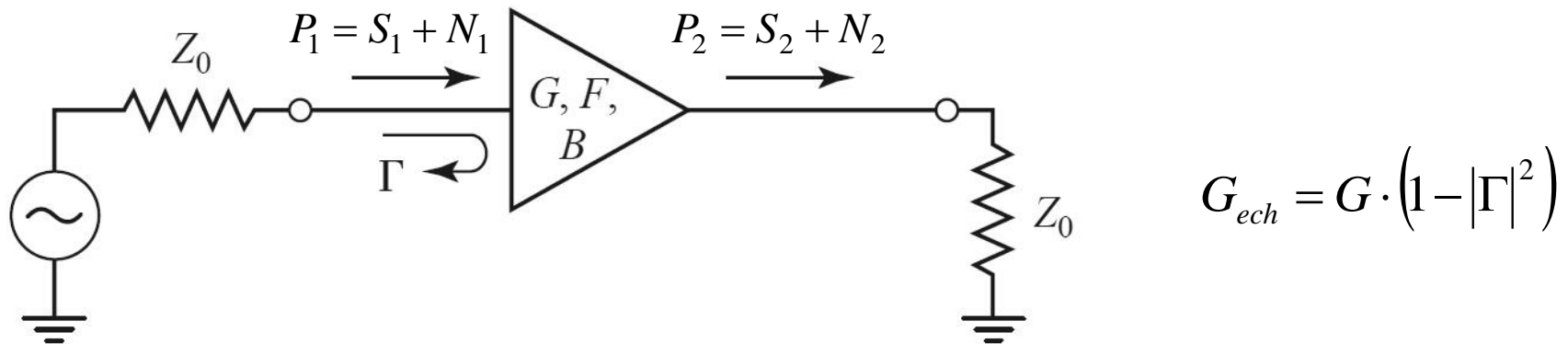
# Noise Figure of a Mismatched Amplifier

- An input mismatched amplifier ( $\Gamma \neq 0$ )



$$N_2 = N_1 \cdot G \cdot (1 - |\Gamma|^2) + (F - 1) \cdot N_0 \cdot G = N_1 \cdot G \cdot (1 - |\Gamma|^2) + \frac{F - 1}{1 - |\Gamma|^2} \cdot N_0 \cdot G \cdot (1 - |\Gamma|^2)$$

$$N_2 = N_1 \cdot G_{ech} + (F_{ech} - 1) \cdot N_0 \cdot G_{ech} \quad F_{ech} = 1 + \frac{F - 1}{1 - |\Gamma|^2} \geq F$$

- Good noise figure **requires** good impedance matching

# Example

- ATF-34143 at  $V_{ds}=3V$   $I_d=20mA$ .

- @5GHz

- $S_{11} = 0.64 \angle 139^\circ$

- $S_{12} = 0.119 \angle -21^\circ$

- $S_{21} = 3.165 \angle 16^\circ$

- $S_{22} = 0.22 \angle 146^\circ$

- $F_{min} = 0.54$  (tipic [dB])

- $\Gamma_{opt} = 0.45 \angle 174^\circ$

- $r_n = 0.03$

```

IATF-34143
IS-PARAMETERS at Vds=3V Id=20mA. LAST UPDATED 01-29-99


# ghz s ma r 50

2.0 0.75 -126 6.306 90 0.088 23 0.26 -120
2.5 0.72 -145 5.438 75 0.095 15 0.25 -140
3.0 0.69 -162 4.762 62 0.102 7 0.23 -156
4.0 0.65 166 3.806 38 0.111 -8 0.22 174
5.0 0.64 139 3.165 16 0.119 -21 0.22 146
6.0 0.65 114 2.706 -5 0.125 -35 0.23 118
7.0 0.66 89 2.326 -27 0.129 -49 0.25 91
8.0 0.69 67 2.017 -47 0.133 -62 0.29 67
9.0 0.72 48 1.758 -66 0.135 -75 0.34 46



!FREQ Fopt GAMMA OPT RN/Zo
!GHZ dB MAG ANG -
2.0 0.19 0.71 66 0.09
2.5 0.23 0.65 83 0.07
3.0 0.29 0.59 102 0.06
4.0 0.42 0.51 138 0.03
5.0 0.54 0.45 174 0.03
6.0 0.67 0.42 -151 0.05
7.0 0.79 0.42 -118 0.10
8.0 0.92 0.45 -88 0.18
9.0 1.04 0.51 -63 0.30
10.0 1.16 0.61 -43 0.46
    
```




# Example

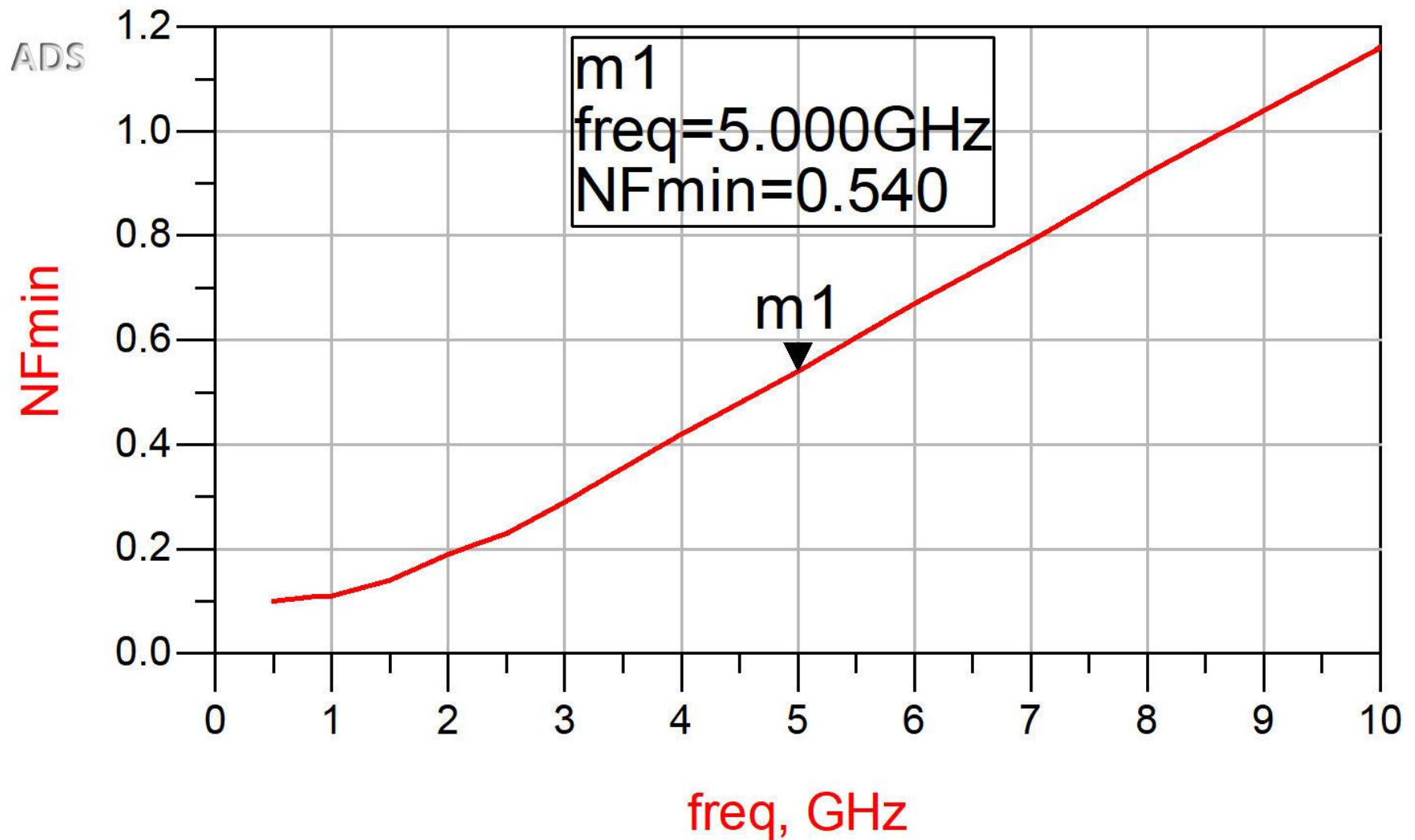



# Stabilization, input series resistor

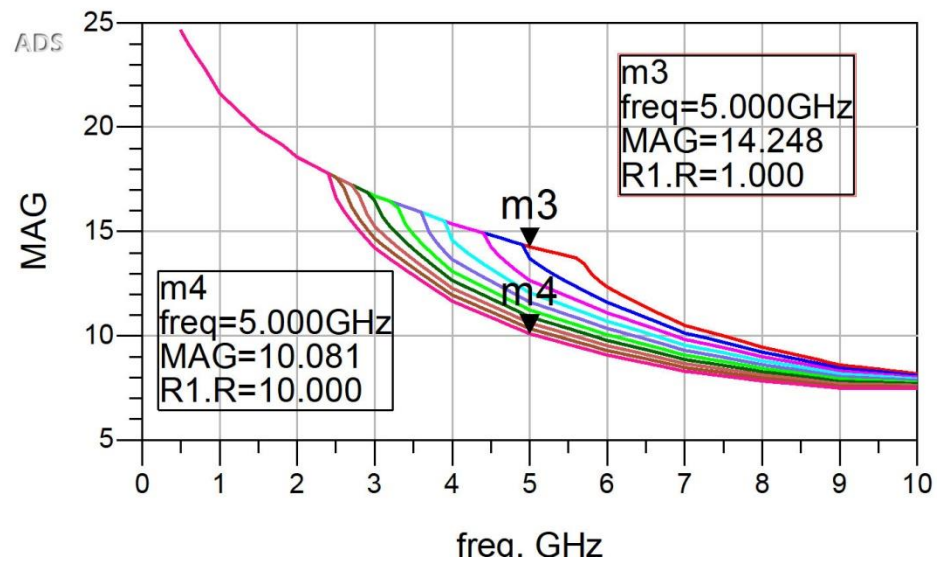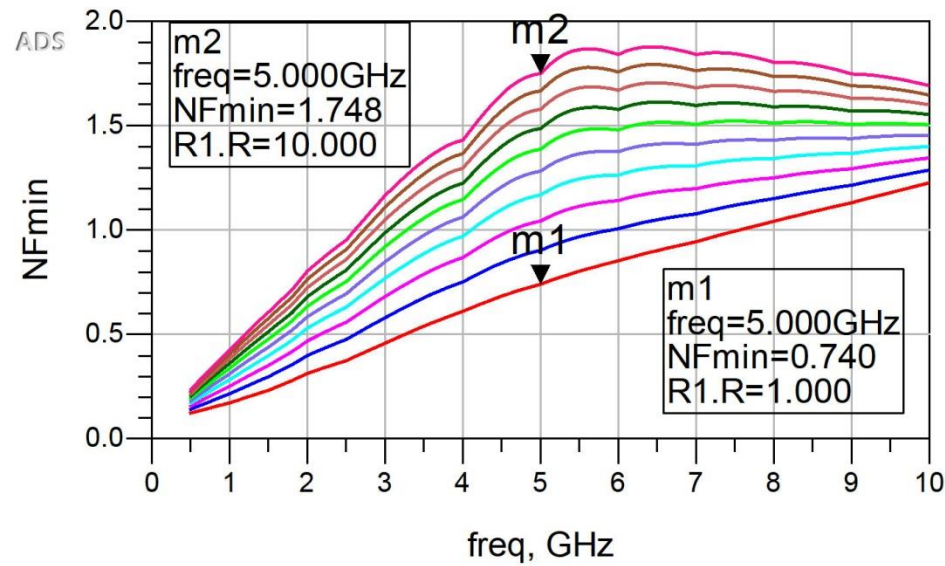


$$R_{SS} = 1 \div 10 \Omega$$

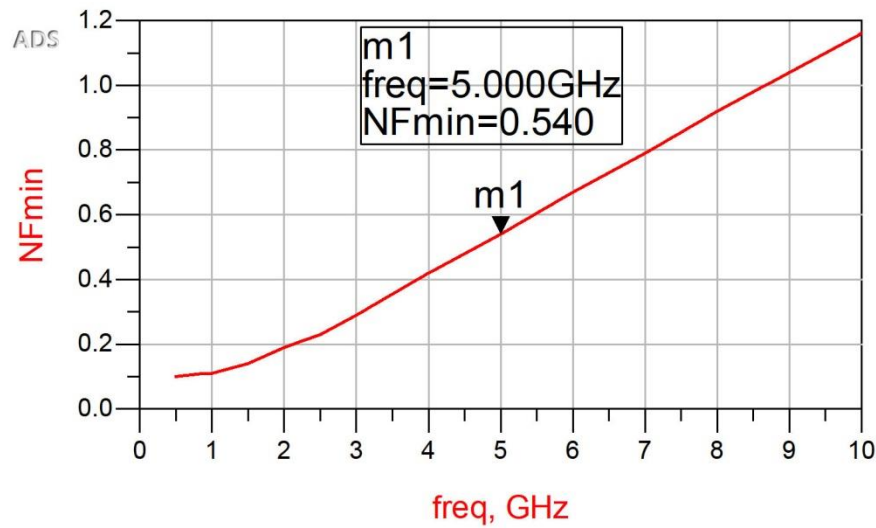



# Stabilization, input shunt resistor

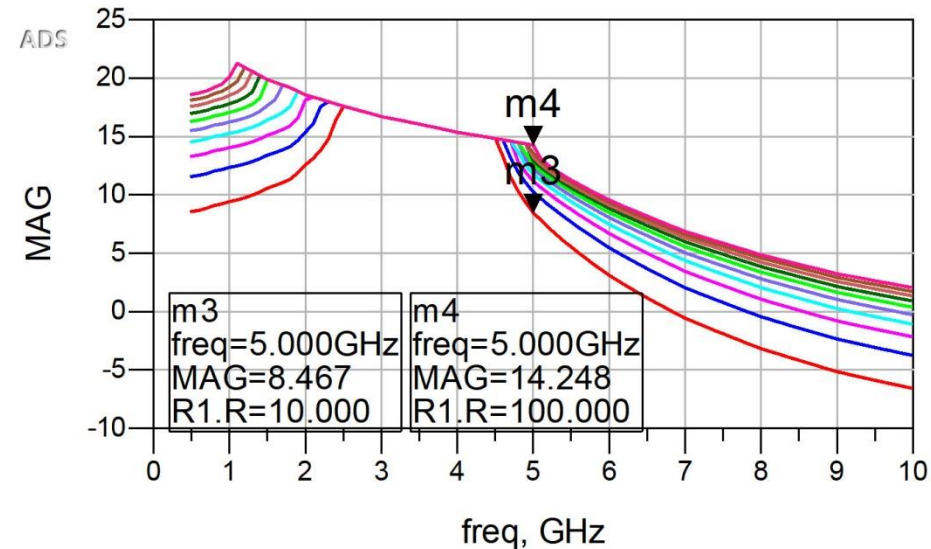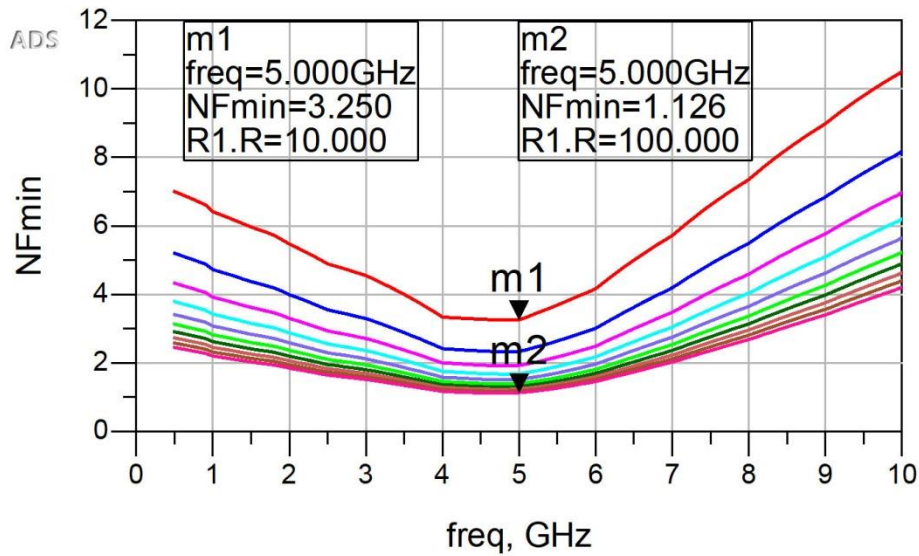


$$R_{PS} = 10 \div 100 \Omega$$

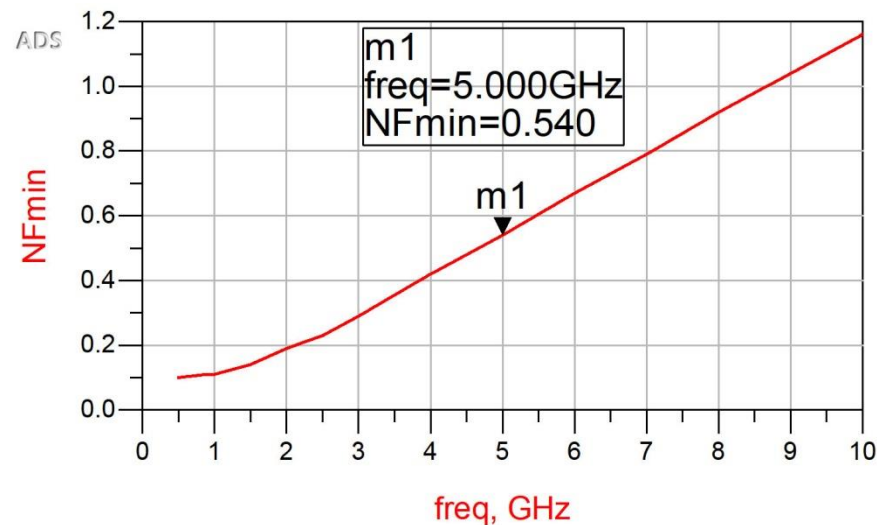



# Stabilization, output series resistor

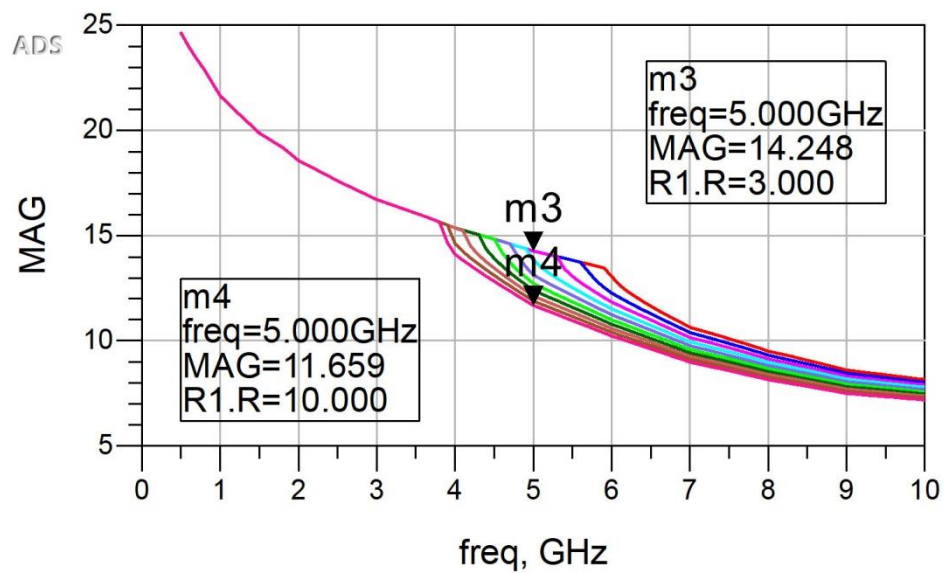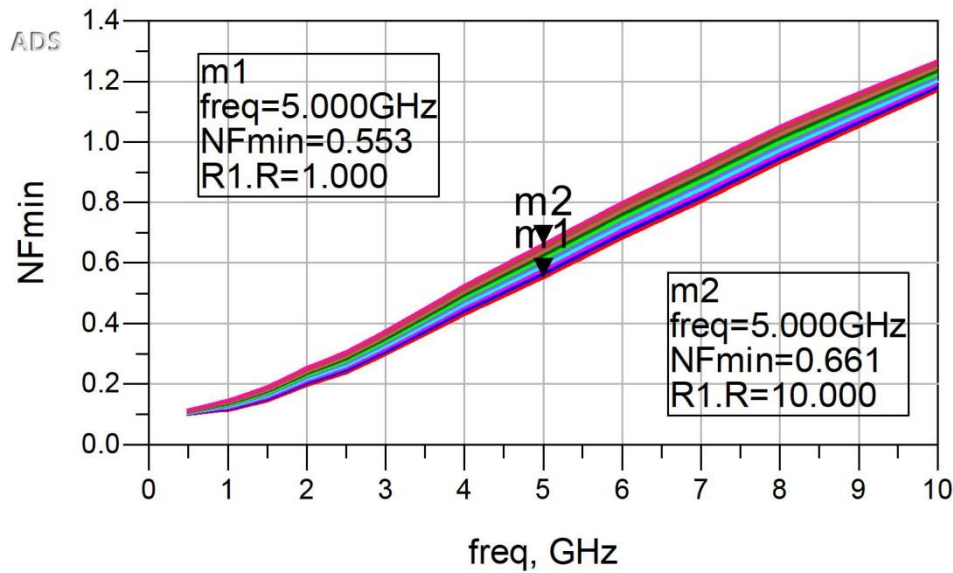


$$R_{SL} = 1 \div 10 \Omega$$

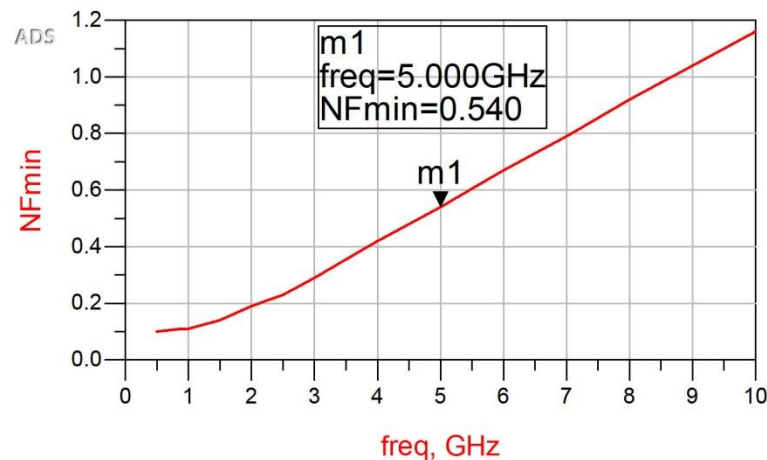

# Stabilization, output shunt resistor

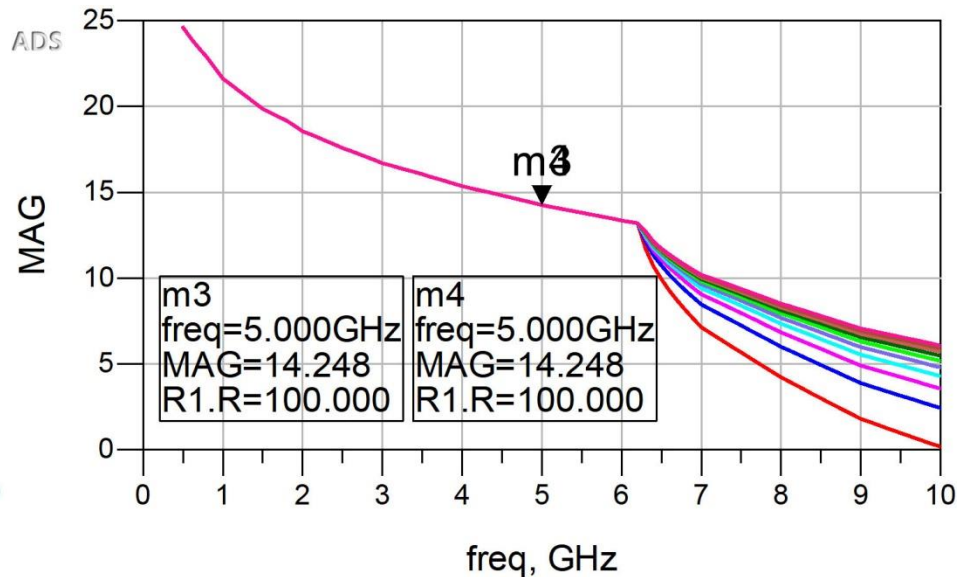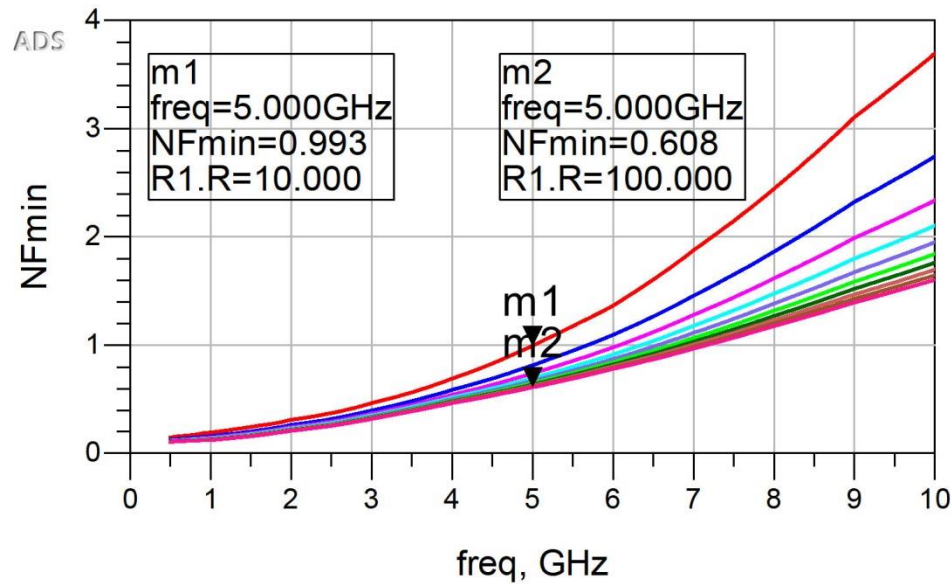

$$R_{PL} = 10 \div 100 \Omega$$

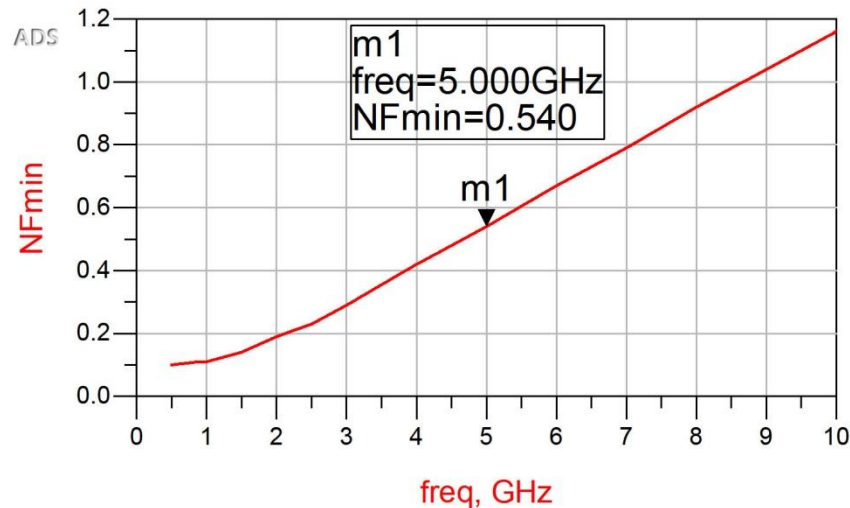

# Noise figure of a two-port amplifier

- 3 noise parameters (2 reals + 1 complex):

$$F_{\min}, r_n = \frac{R_N}{Z_0}, \Gamma_{opt}$$


$$F = F_{\min} + \frac{R_N}{G_S} \cdot |Y_S - Y_{opt}|^2 \quad Y_S = \frac{1}{Z_0} \cdot \frac{1 - \Gamma_S}{1 + \Gamma_S} \quad Y_{opt} = \frac{1}{Z_0} \cdot \frac{1 - \Gamma_{opt}}{1 + \Gamma_{opt}}$$

$$F = F_{\min} + 4 \cdot r_n \cdot \frac{|\Gamma_S - \Gamma_{opt}|^2}{(1 - |\Gamma_S|^2) \cdot |1 + \Gamma_{opt}|^2}$$


- $\Gamma_{opt}$  optimum source reflection coefficient that results in minimum noise figure

$$\Gamma_S = \Gamma_{opt} \Rightarrow F = F_{\min}$$

# $F(\Gamma_S)$

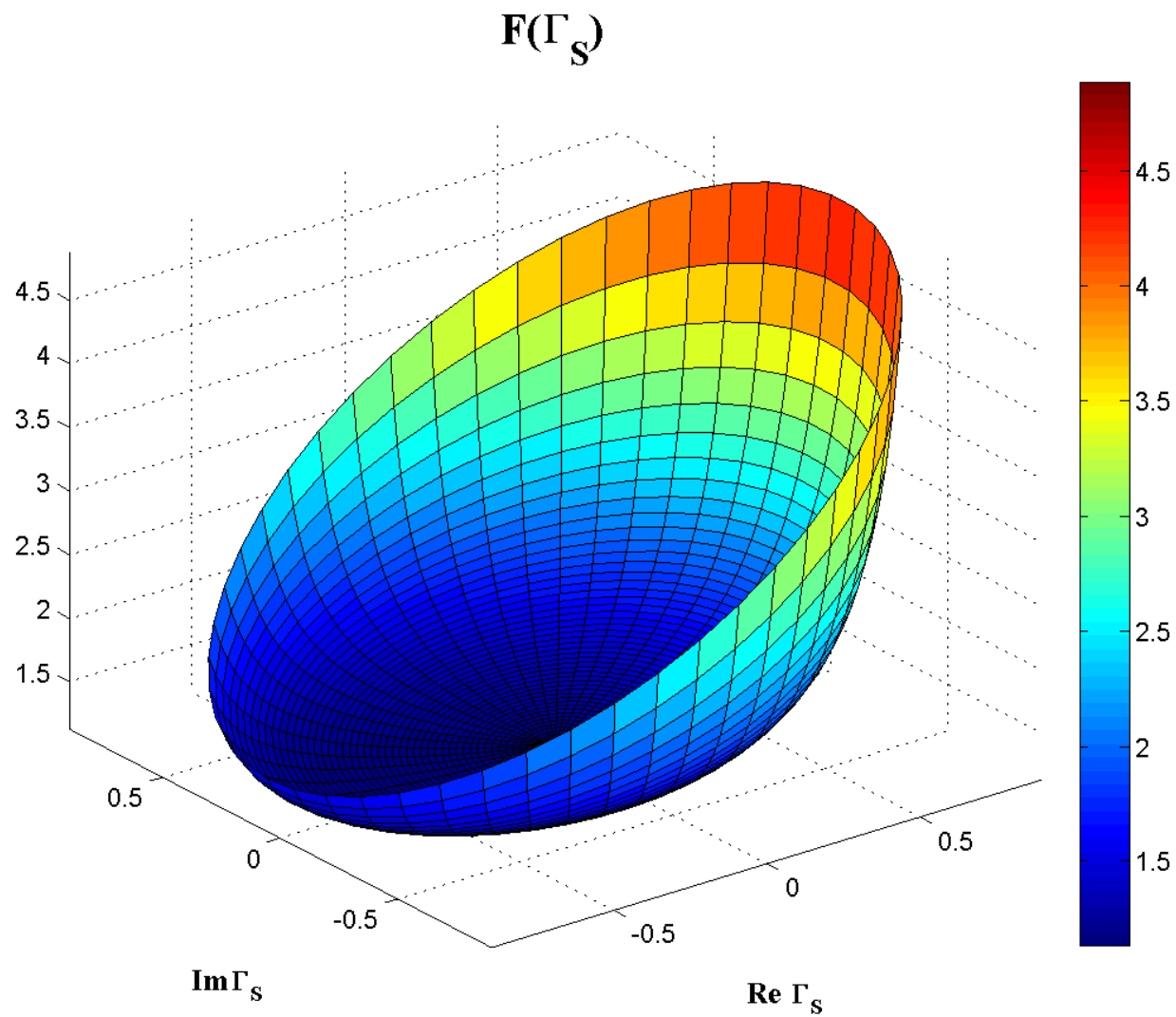


# $F[\text{dB}](\Gamma_S)$

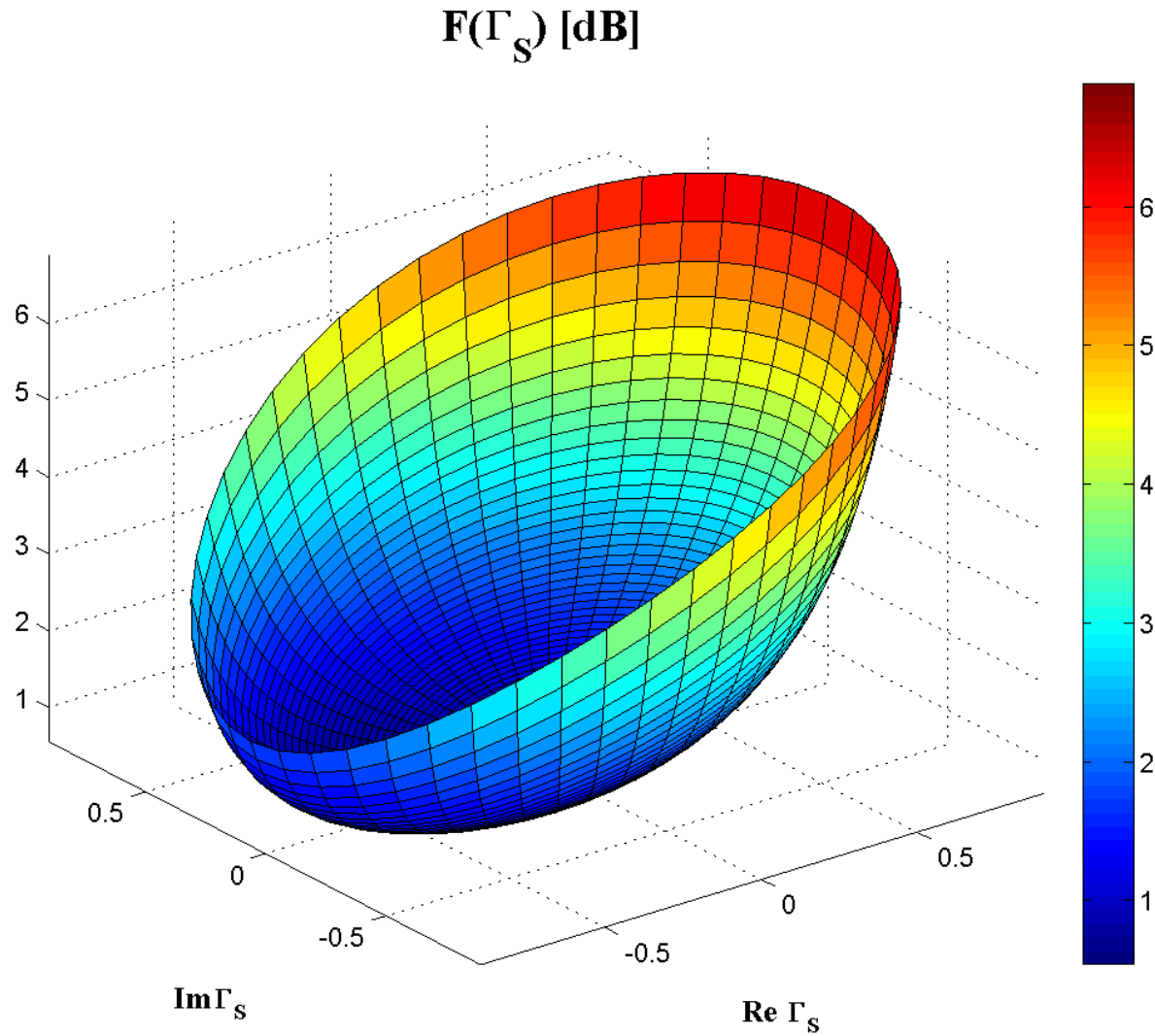



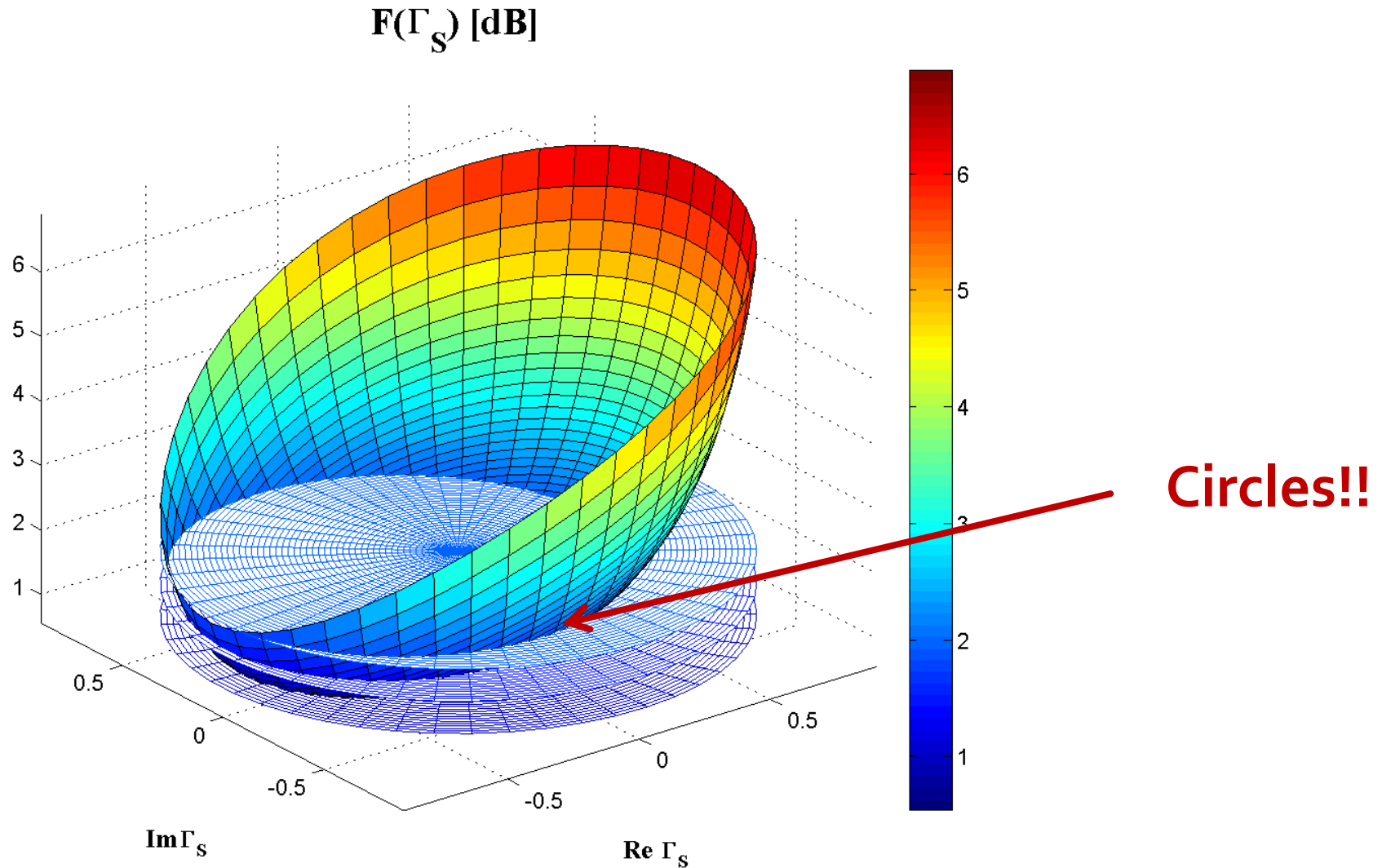
# $F[\text{dB}](\Gamma_s)$ , constant value contours


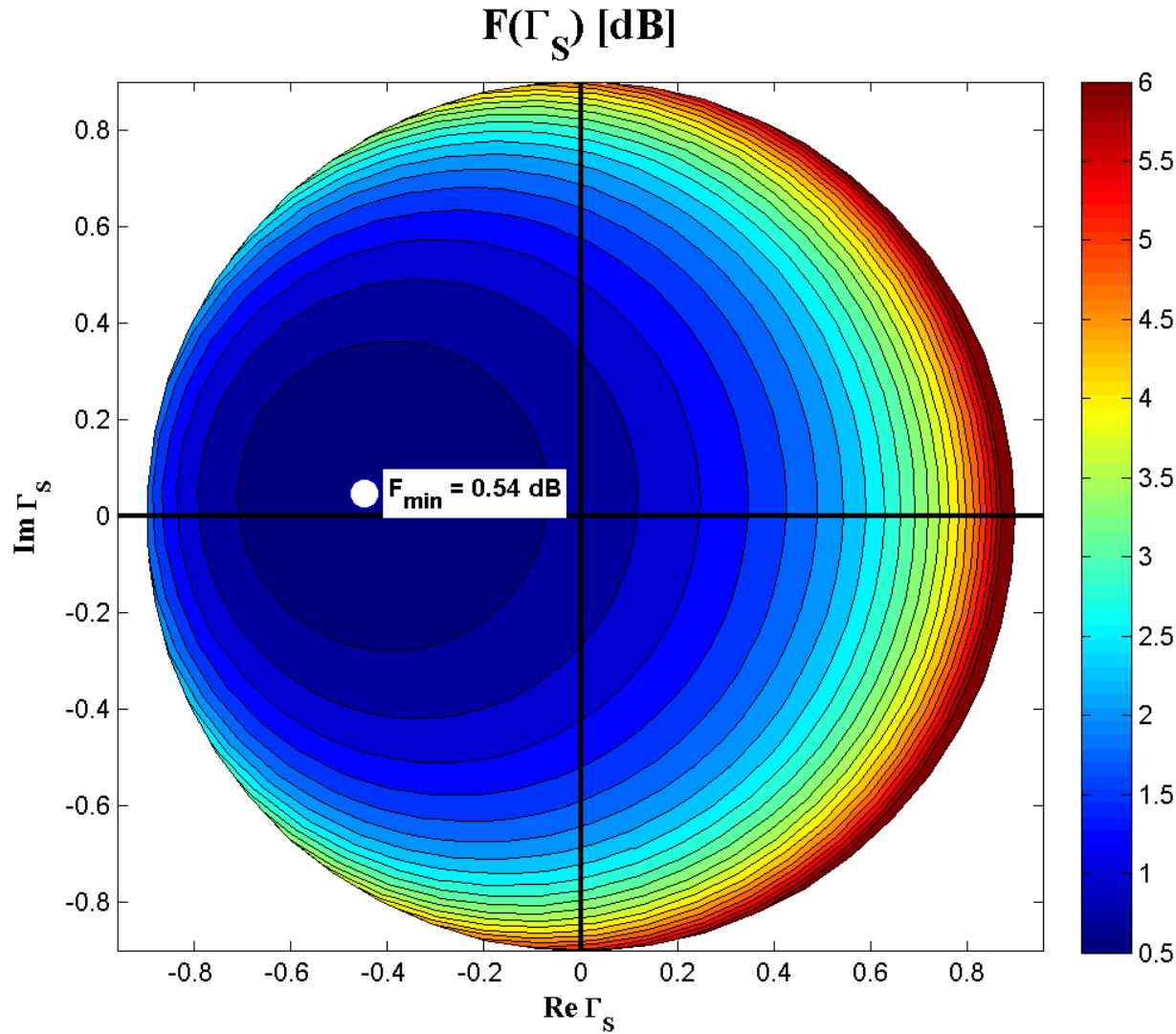
# $G_S[\text{dB}](\Gamma_S)$ , constant value contours



$$\Gamma_{\text{opt}} = 0.45 \angle 174^\circ$$

# Circles of constant noise figure

$$F = F_{\min} + 4 \cdot r_n \cdot \frac{|\Gamma_S - \Gamma_{opt}|^2}{(1 - |\Gamma_S|^2) \cdot |1 + \Gamma_{opt}|^2}$$

- We define N (noise figure parameter)
  - **N** constant for **F** constant

$$N = \frac{|\Gamma_S - \Gamma_{opt}|^2}{1 - |\Gamma_S|^2} = \frac{F - F_{\min}}{4 \cdot r_n} \cdot |1 + \Gamma_{opt}|^2$$

$$(\Gamma_S - \Gamma_{opt}) \cdot (\Gamma_S^* - \Gamma_{opt}^*) = N \cdot (1 - |\Gamma_S|^2)$$

$$\Gamma_S \cdot \Gamma_S^* + N \cdot |\Gamma_S|^2 - (\Gamma_S \cdot \Gamma_{opt}^* - \Gamma_S^* \cdot \Gamma_{opt}) + \Gamma_{opt} \cdot \Gamma_{opt}^* = N$$


$$\Gamma_S \cdot \Gamma_S^* - \frac{\Gamma_S \cdot \Gamma_{opt}^* - \Gamma_S^* \cdot \Gamma_{opt}}{N + 1} + \Gamma_{opt} \cdot \Gamma_{opt}^* = \frac{N - |\Gamma_{opt}|^2}{N + 1} + \frac{|\Gamma_{opt}|^2}{(N + 1)^2}$$

$$|a + b|^2 = (a + b) \cdot (a + b)^* = (a + b) \cdot (a^* + b^*) = \underbrace{|a|^2 + |b|^2}_{\text{blue}} + \underbrace{a^* \cdot b + a \cdot b^*}_{\text{blue}}$$

# Circles of constant noise figure

$$\left| \Gamma_S - \frac{\Gamma_{opt}}{N+1} \right| = \frac{\sqrt{N \cdot (N+1 - |\Gamma_{opt}|^2)}}{N+1}$$

$$|\Gamma_S - C_F| = R_F$$

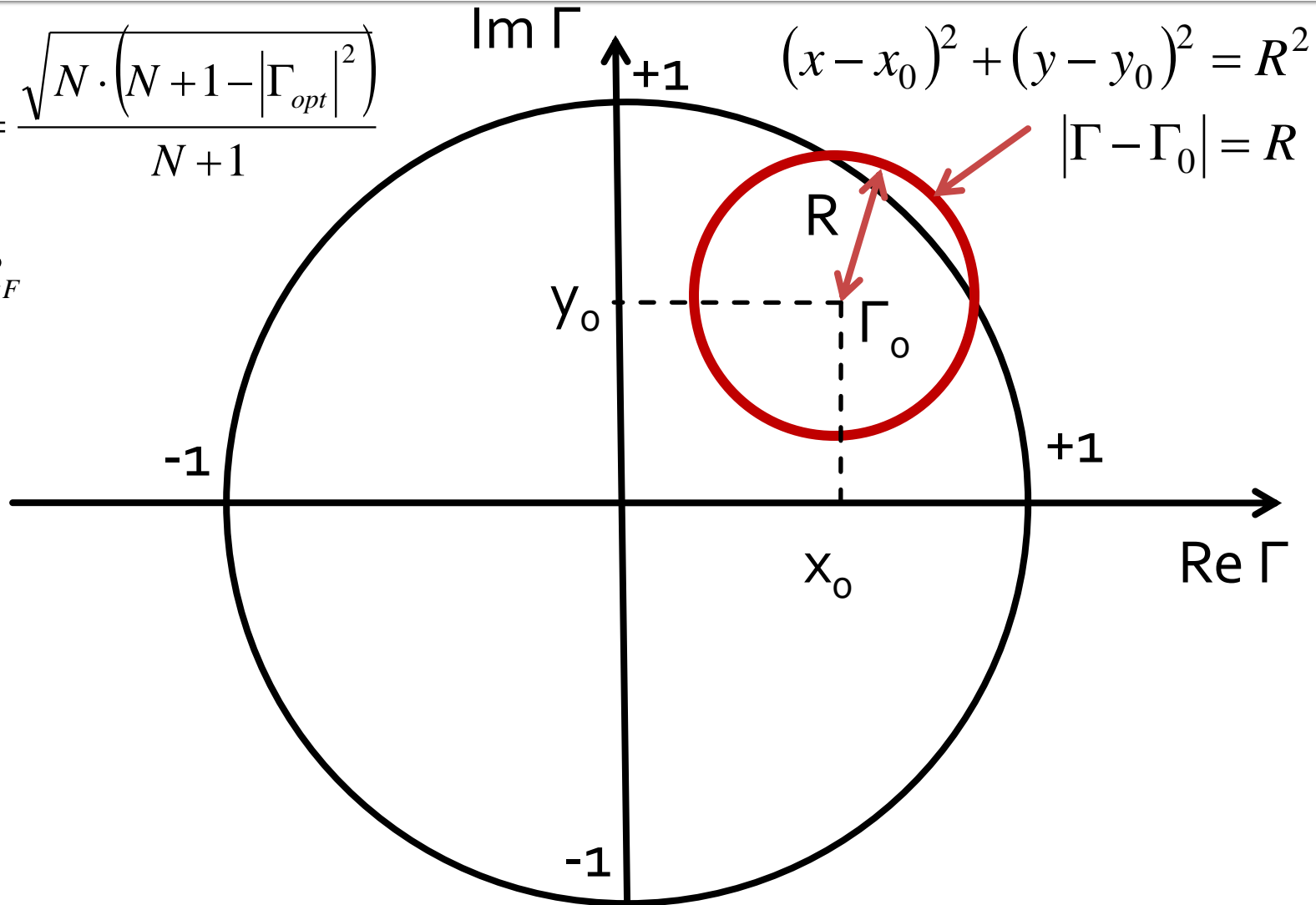


# Circles of constant noise figure

$$\left| \Gamma_S - \frac{\Gamma_{opt}}{N+1} \right| = \frac{\sqrt{N \cdot (N+1 - |\Gamma_{opt}|^2)}}{N+1} \quad N = \frac{F - F_{min}}{4 \cdot r_n} \cdot |1 + \Gamma_{opt}|^2$$

$$|\Gamma_S - C_F| = R_F \quad C_F = \frac{\Gamma_{opt}}{N+1} \quad R_F = \frac{\sqrt{N \cdot (N+1 - |\Gamma_{opt}|^2)}}{N+1}$$

- The locus in the complex plane  $\Gamma_S$  of the points with constant noise figure is a circle
- **Interpretation:** Any reflection coefficient  $\Gamma_S$  which plotted in the complex plane lies **on** the circle drawn for  $F_{circle}$  will lead to a noise factor  $F = F_{circle}$ 
  - Any reflection coefficient  $\Gamma_S$  plotted **outside** this circle will lead to a noise factor  $F > F_{circle}$
  - Any reflection coefficient  $\Gamma_S$  plotted **inside** this circle will lead to a noise factor  $F < F_{circle}$

# ADS

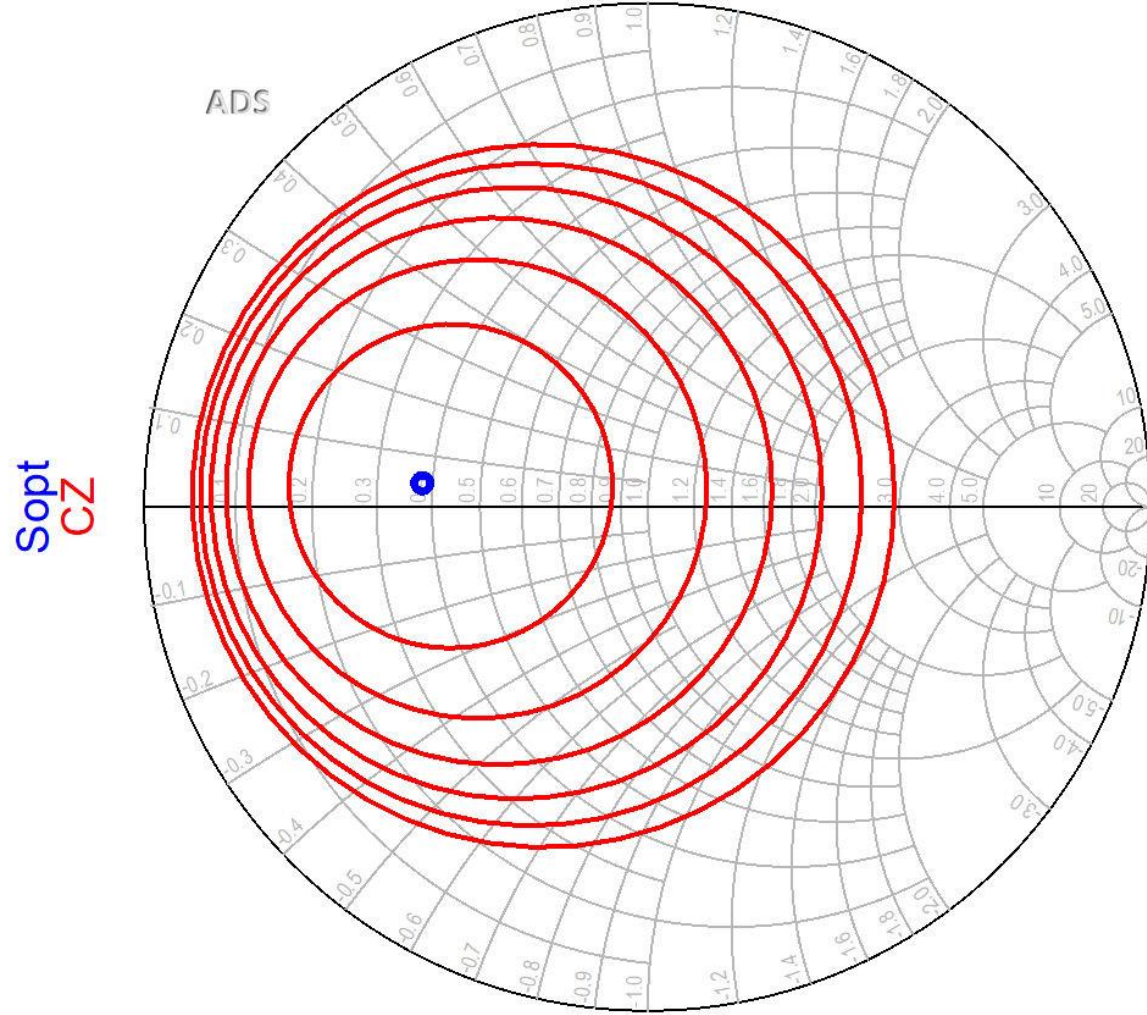


# Circles of constant noise figure

- The noise internally generated by the transistor depends **only** by the input matching circuit
- A minimum noise figure is possible ( $NF_{\min}$  – a datasheet/"s2p file" parameter for the transistor)
- If we design a low noise amplifier (**LNA**) the usual design technique is as follows:
  - design of the input matching circuit solely (largely) for noise optimization
  - design of output matching circuit for gain compensation/optimization (if lossy circuits are used the output matching circuit noise can be added but the transistor noise is not influenced)
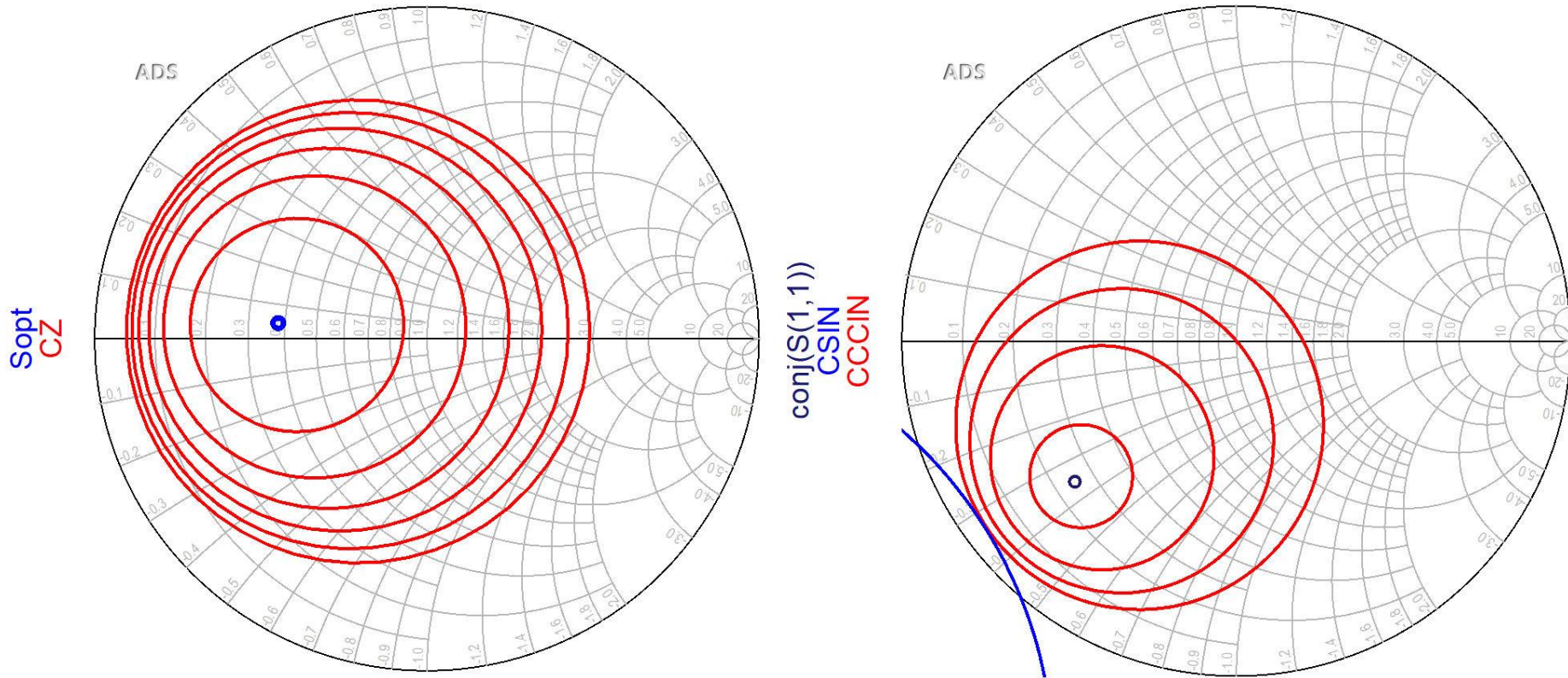
# LNA – Low Noise Amplifier


- Usually a transistor suitable for implementing an LNA at a certain frequency will have input gain circles and noise circles in the same area for  $\Gamma_S$




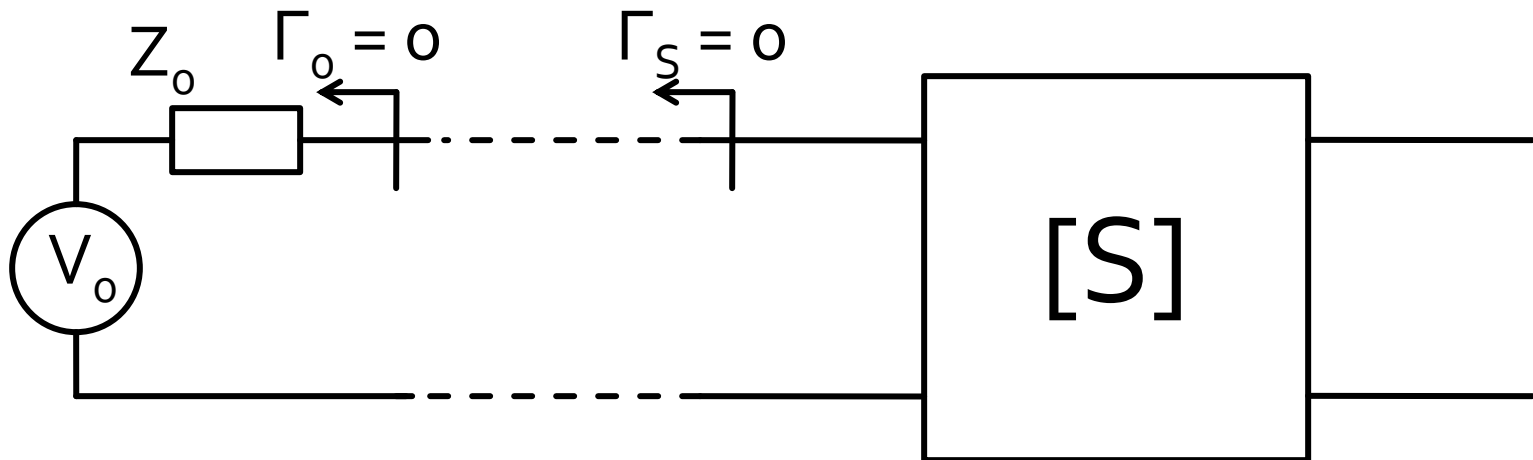
# Matching – 1


- Connecting the amplifier (transistor) directly to the source with  $Z_o$  generate a reflection coefficient seen towards the source equal with  $0$  (complex number,  $\Gamma_o = 0 + 0 \cdot j$ )
  - most of the time this reflection coefficient does not offer optimum noise/gain


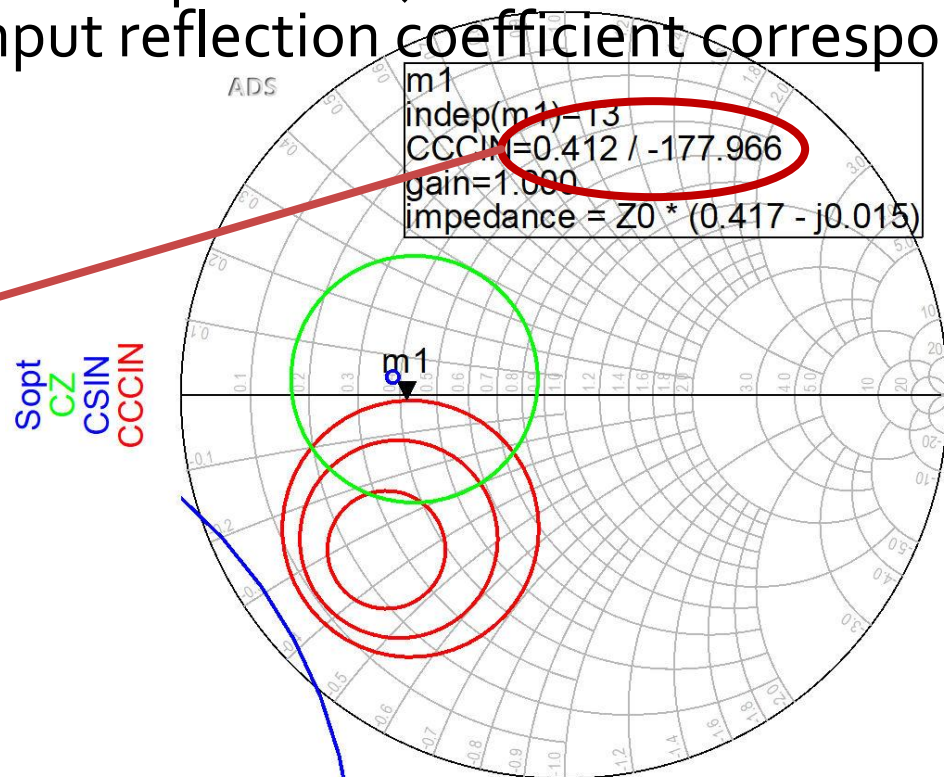
# Matching – 2


- We plot on the complex plane (Smith Chart) the stability/gain/noise circles (depending on the particular application)
- We choose a point with a suitable position relative to these circles (also application dependent)
- We determine the input reflection coefficient corresponding to this point,  $\Gamma_S$

$$\Gamma_S = 0.412 \angle -177.966^\circ$$



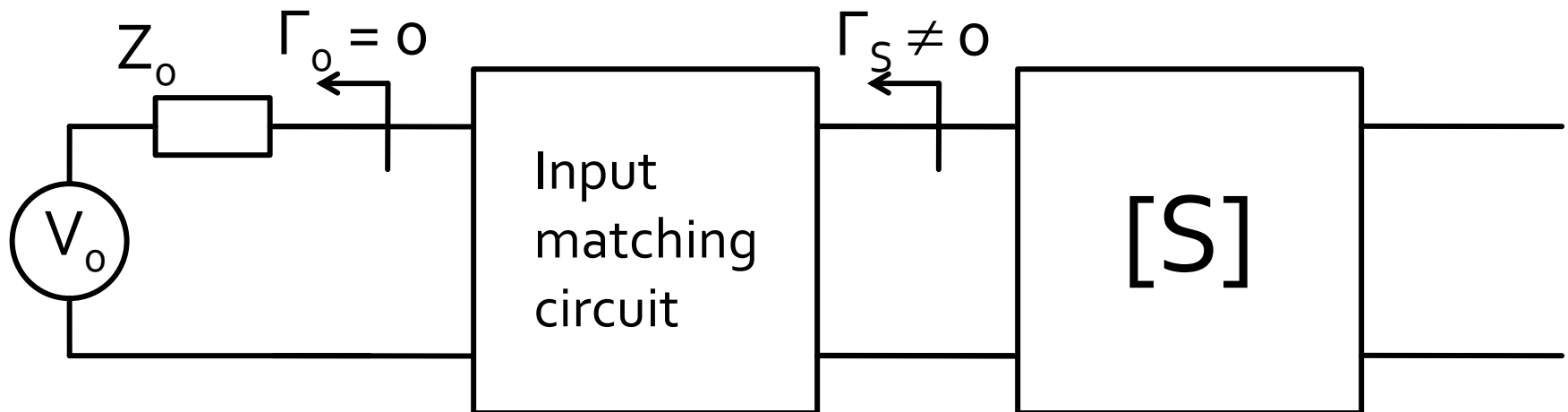
# Matching – 3

- We insert the input matching circuits which allows the transistor to see towards the source the previously determined reflection coefficient  $\Gamma_S$


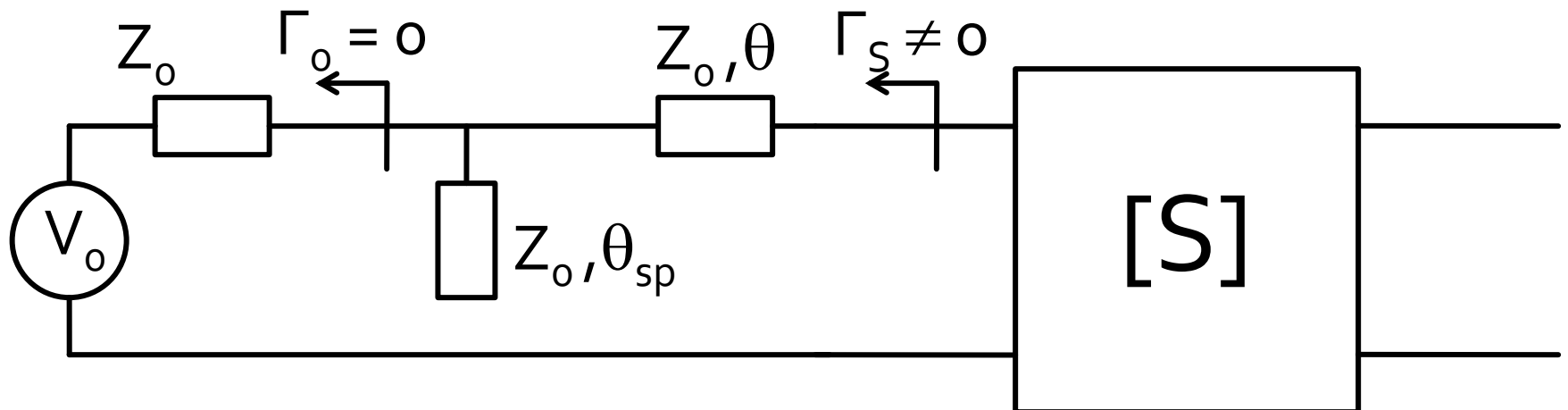
# Matching – 4

- Easiest to design matching section consists in the insertion of (in order from the transistor towards the  $Z_0$  source):
  - a series  $Z_0$  line, with electrical length  $\theta$
  - a shunt stub, open-circuited, made from a  $Z_0$  line, with electrical length  $\theta_{sp}$




# Matching – 5

- Computation depends solely on  $\Gamma_S$  (magnitude and phase)


$$\cos(\varphi_S + 2\theta) = -|\Gamma_S|$$

$$\tan \theta_{sp} = \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

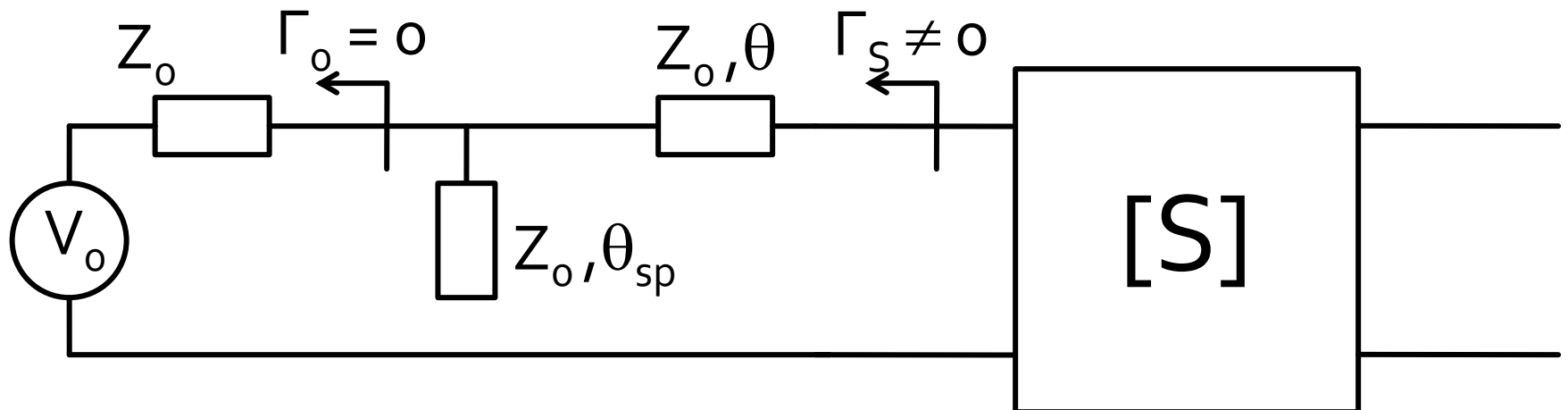- The sign (+/-) chosen for the series line equation imposes the sign used for the shunt stub equation



# Shunt stub matching, L7

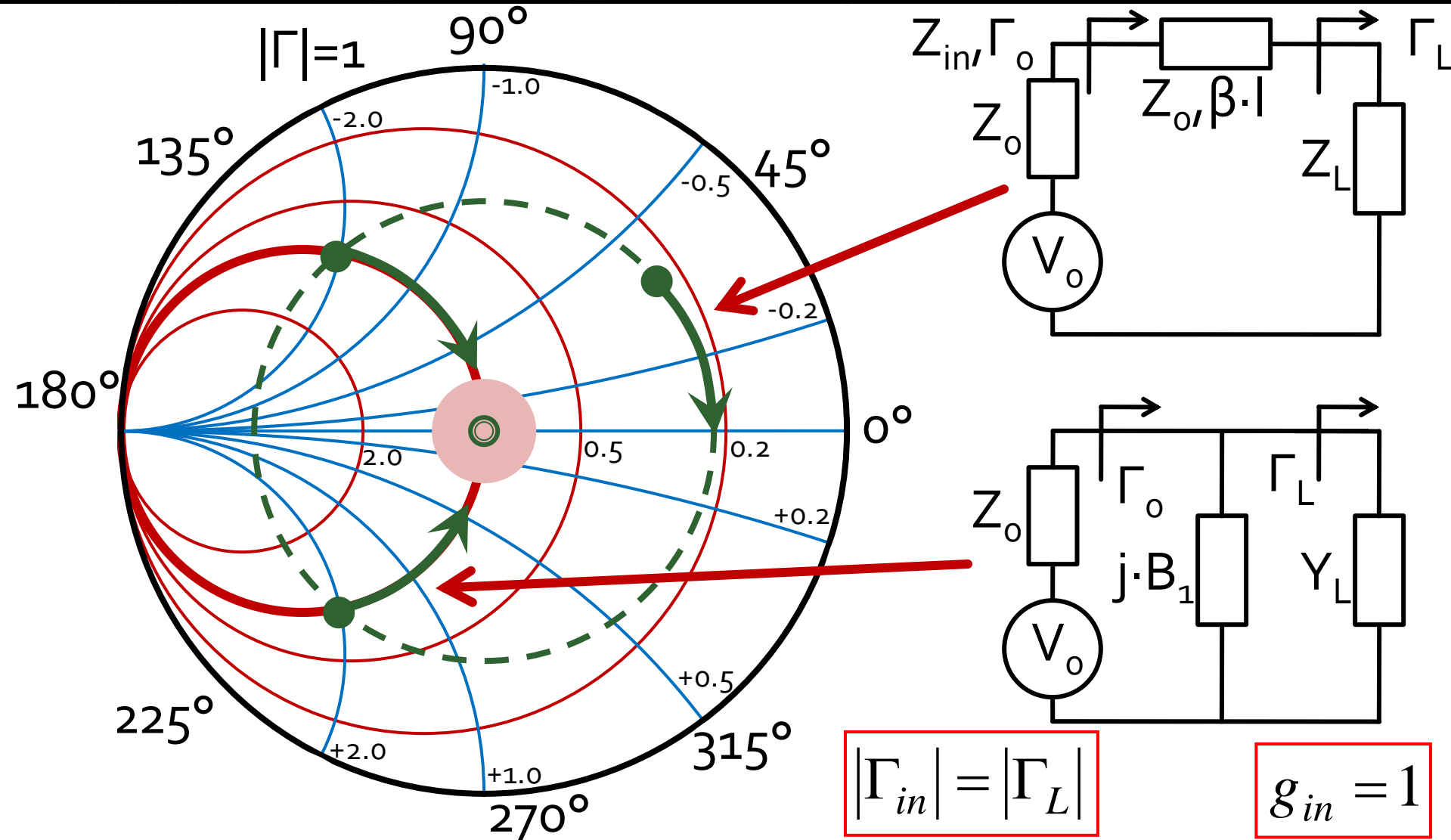

# Example, LNA @ 5 GHz

- ATF-34143 at  $V_{ds}=3V$   $I_d=20mA$ .
- @5GHz
  - $S_{11} = 0.64 \angle 139^\circ$
  - $S_{12} = 0.119 \angle -21^\circ$
  - $S_{21} = 3.165 \angle 16^\circ$  →
  - $S_{22} = 0.22 \angle 146^\circ$
  - $F_{min} = 0.54$  (tipic [dB])
  - $\Gamma_{opt} = 0.45 \angle 174^\circ$
  - $r_n = 0.03$  →

```

IATF-34143
IS-PARAMETERS at Vds=3V Id=20mA. LAST UPDATED 01-29-99

# ghz s ma r 50

2.0 0.75 -126 6.306 90 0.088 23 0.26 -120
2.5 0.72 -145 5.438 75 0.095 15 0.25 -140
3.0 0.69 -162 4.762 62 0.102 7 0.23 -156
4.0 0.65 166 3.806 38 0.111 -8 0.22 174
5.0 0.64 139 3.165 16 0.119 -21 0.22 146
6.0 0.65 114 2.706 -5 0.125 -35 0.23 118
7.0 0.66 89 2.326 -27 0.129 -49 0.25 91
8.0 0.69 67 2.017 -47 0.133 -62 0.29 67
9.0 0.72 48 1.758 -66 0.135 -75 0.34 46

IFREQ Fopt GAMMA OPT RN/Zo
IGHZ dB MAG ANG -
2.0 0.19 0.71 66 0.09
2.5 0.23 0.65 83 0.07
3.0 0.29 0.59 102 0.06
4.0 0.42 0.51 138 0.03
5.0 0.54 0.45 174 0.03
6.0 0.67 0.42 -151 0.05
7.0 0.79 0.42 -118 0.10
8.0 0.92 0.45 -88 0.18
9.0 1.04 0.51 -63 0.30
10.0 1.16 0.61 -43 0.46
    
```

# Example, LNA @ 5 GHz

- Low Noise Amplifier
- At the input matching a compromise is required between:
  - noise (~~input~~ constant noise figure circles)
  - gain (input constant gain circles)
  - stability (input stability circle)
- At the output matching noise **is not influenced**.  
A compromise is required between :
  - gain (output constant gain circles)
  - stability (output stability circle)



# Example, LNA @ 5 GHz

$$U = \frac{|S_{12}| \cdot |S_{21}| \cdot |S_{11}| \cdot |S_{22}|}{(1 - |S_{11}|^2) \cdot (1 - |S_{22}|^2)} = 0.094 \quad -0.783 \text{ dB} < G_T [\text{dB}] - G_{TU} [\text{dB}] < 0.861 \text{ dB}$$

$$G_{TU \max} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2} = 17.83 \quad G_{TU \max} [\text{dB}] = 12.511 \text{ dB}$$


$$G_0 = |S_{21}|^2 = 10.017 = 10.007 \text{ dB}$$

$$G_{S \max} = \frac{1}{1 - |S_{11}|^2} = 1.694 = 2.289 \text{ dB}$$

$$G_{L \max} = \frac{1}{1 - |S_{22}|^2} = 1.051 = 0.215 \text{ dB}$$


- In this particular case  $G_{L \max} = 0.21 \text{ dB}$ , the transistor could be used directly connected to the  $50\Omega$  load
- The absence of the output matching circuit **is not** recommended. While the attainable power gain is low, its absence eliminates the possibility to use it to compensate an improper gain generated by the noise optimization of the input matching circuit

# Input matching circuit

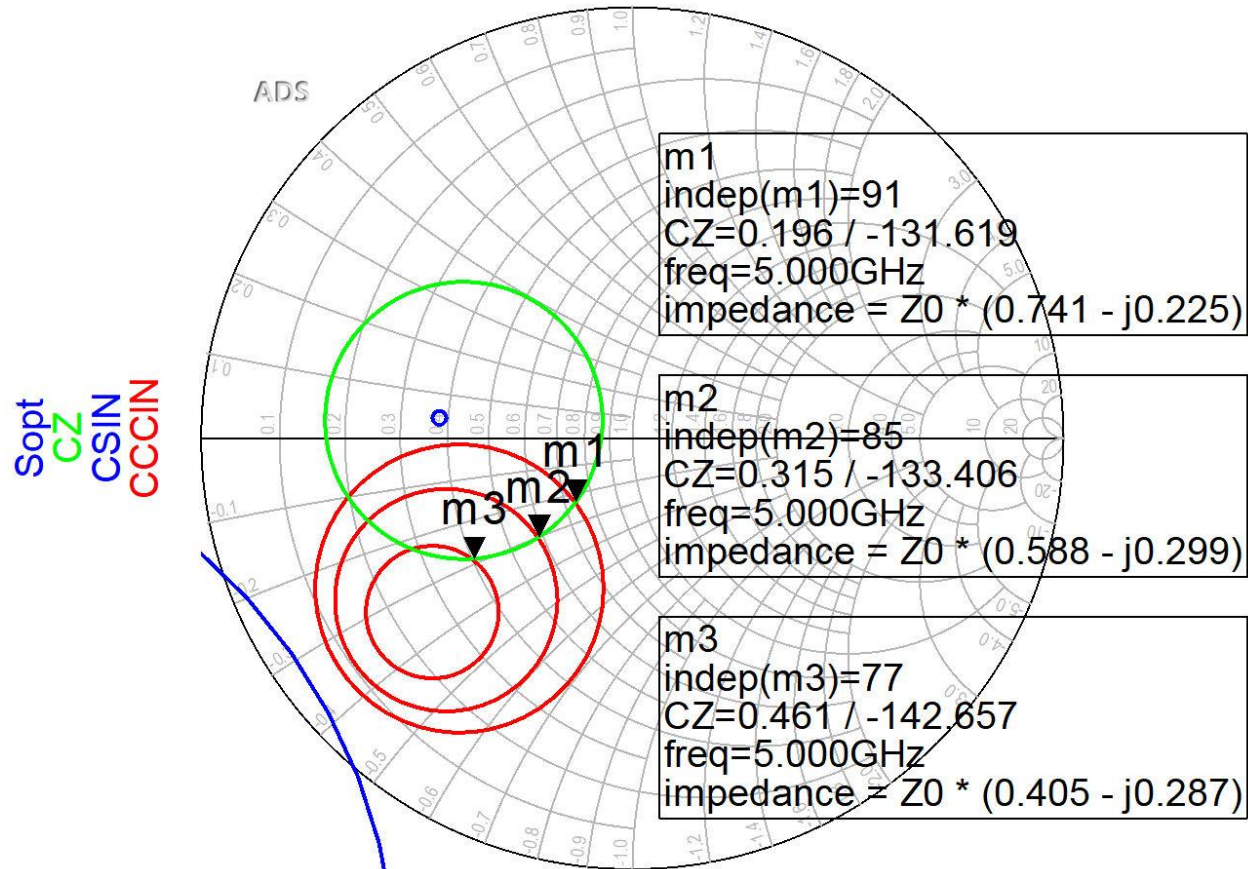

- For the input matching circuit
  - noise circle CZ: 0.75dB
  - input constant gain circles CCCIN: 1dB, 1.5dB, 2 dB
- We choose (small Q → wide bandwidth) position m1

# Input matching circuit

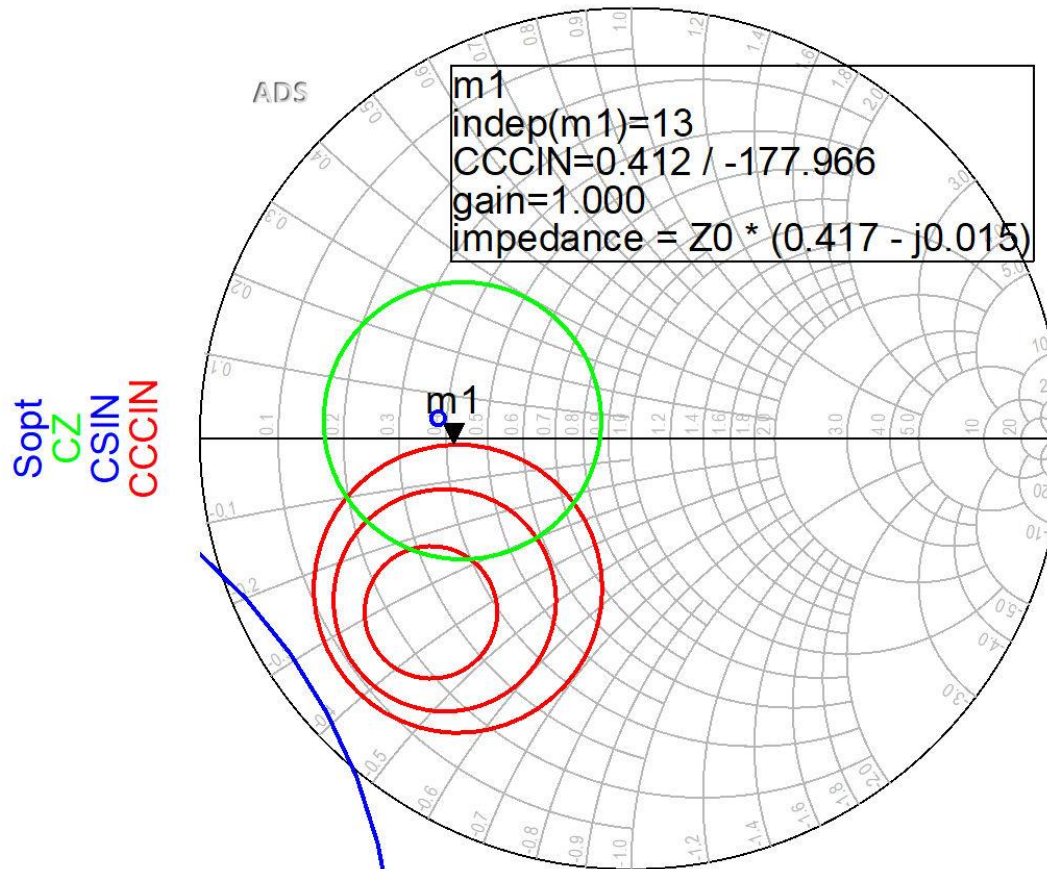

- If we can afford a 1.2dB decrease of the input gain for better NF, Q ( $G_s = 1$  dB), position m1 above is better
- We obtain better (smaller) NF

# Input matching circuit

- Position  $m_1$  in complex plane (Smith Chart)

$$\Gamma_S = 0.412 \angle -178^\circ$$

$$|\Gamma_S| = 0.412; \quad \varphi = -178^\circ$$


$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\text{Im}[y_S(\theta)] = \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$\cos(\varphi + 2\theta) = -0.412 \Rightarrow (\varphi + 2\theta) = \pm 114.33^\circ$$

$$(\varphi + 2\theta) = \begin{cases} +114.33^\circ \\ -114.33^\circ \end{cases} \quad \theta = \begin{cases} 146.2^\circ \\ 31.8^\circ \end{cases} \quad \text{Im}[y_S(\theta)] = \begin{cases} -0.904 \\ +0.904 \end{cases} \quad \theta_{sp} = \begin{cases} 137.9^\circ \\ 42.1^\circ \end{cases}$$

# Output matching circuit

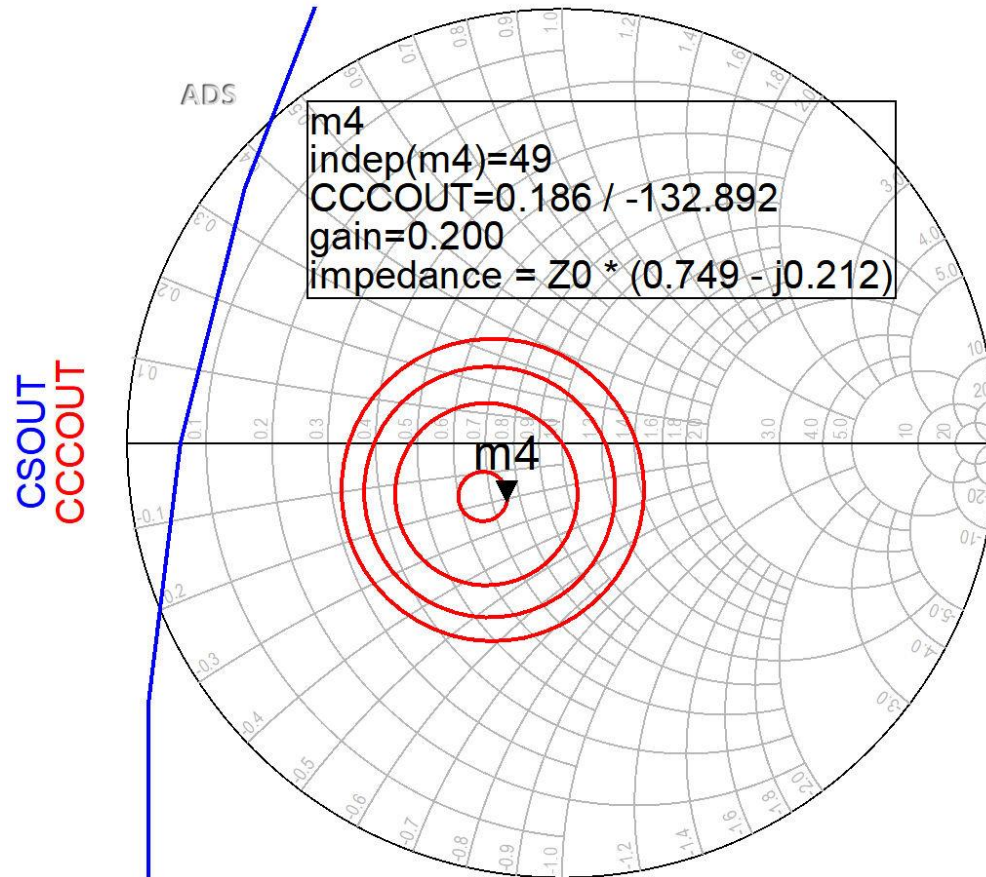

- output constant gain circles CCCOUT: -0.4dB, -0.2dB, 0dB, +0.2dB
- the lack of noise restrictions allows optimization for better gain (close to maximum – position  $m_4$ )

# Output matching circuit

- Position  $m_4$  in complex plane (Smith Chart)

$$\Gamma_L = 0.186 \angle -132.9^\circ$$

$$|\Gamma_L| = 0.186; \quad \varphi = -132.9^\circ$$

$$\cos(\varphi + 2\theta) = -|\Gamma_L|$$

$$\text{Im}[y_L(\theta)] = \frac{-2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}} = -0.379$$

$$\cos(\varphi + 2\theta) = -0.186 \Rightarrow (\varphi + 2\theta) = \pm 100.72^\circ$$

$$(\varphi + 2\theta) = \begin{cases} +100.72^\circ \\ -100.72^\circ \end{cases} \quad \theta = \begin{cases} 116.8^\circ \\ 16.1^\circ \end{cases} \quad \text{Im}[y_L(\theta)] = \begin{cases} -0.379 \\ +0.379 \end{cases} \quad \theta_{sp} = \begin{cases} 159.3^\circ \\ 20.7^\circ \end{cases}$$

# LNA



- We estimate a gain (in unilateral assumption,  $\pm 0.9$  dB)

$$G_T [dB] = G_S [dB] + G_0 [dB] + G_L [dB]$$

$$G_T [dB] = 1 \text{ dB} + 10 \text{ dB} + 0.2 \text{ dB} = 11.2 \text{ dB}$$



- We estimate a noise factor well below 0.75dB (quite close to the minimum  $\sim 0.6$  dB)

# ADS

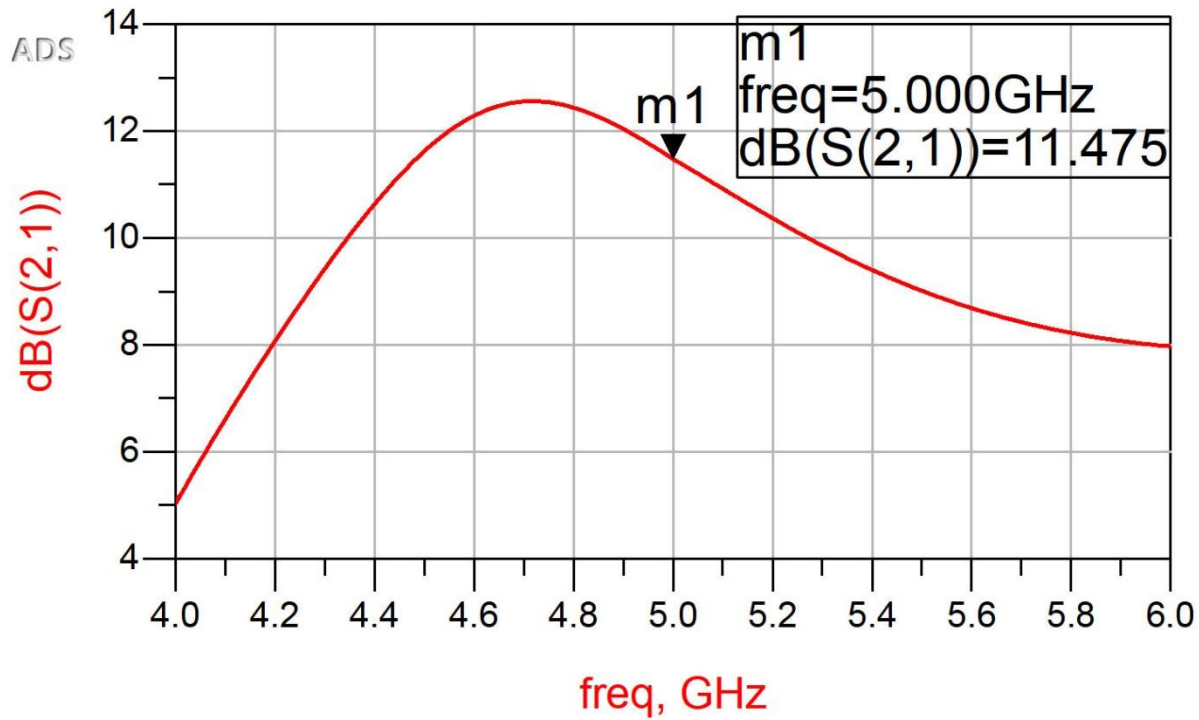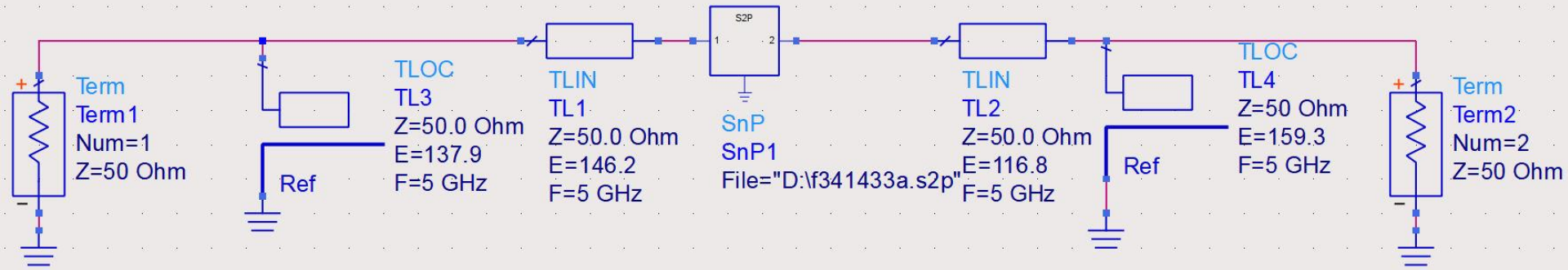



# ADS

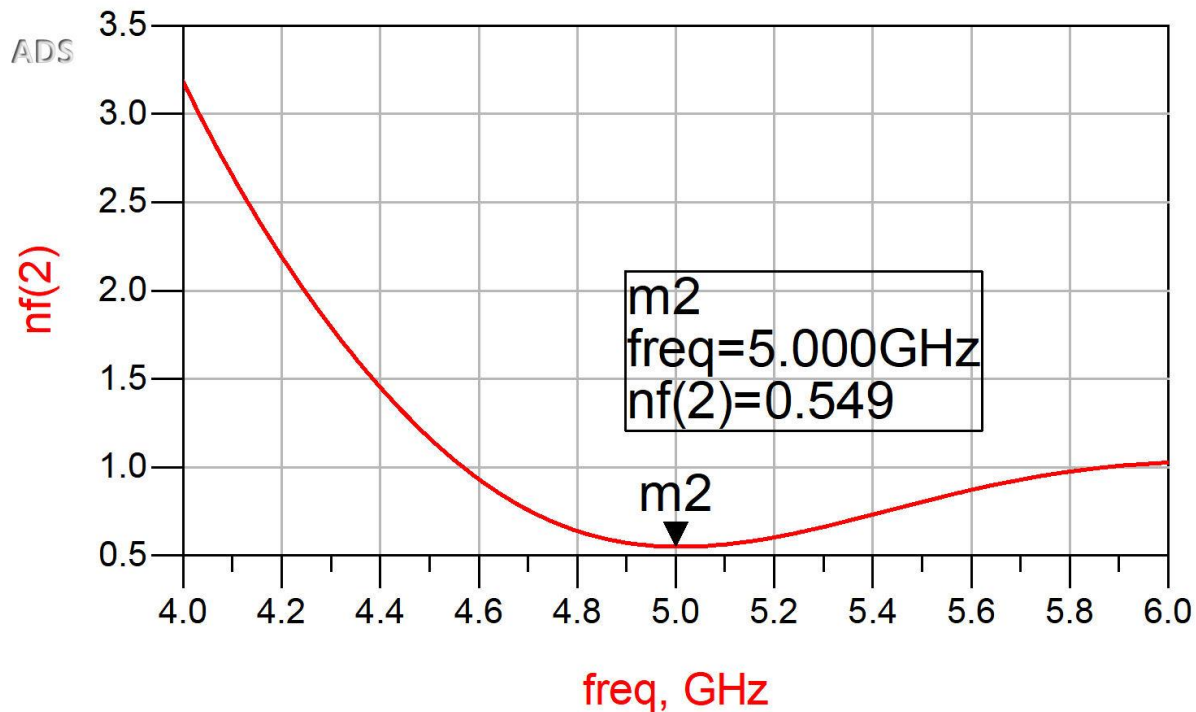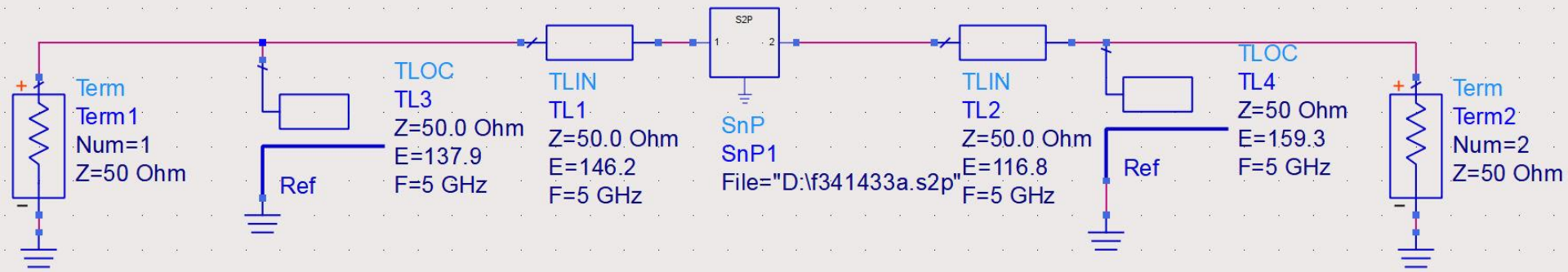


# Microwave Filters

---
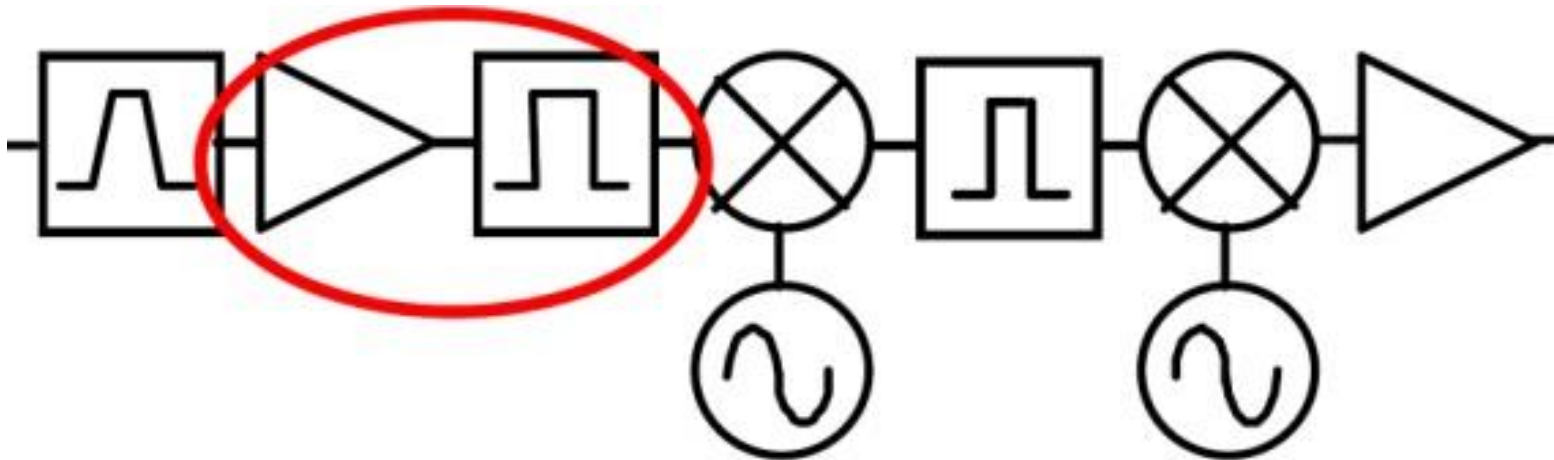
# Assignment

- this structure is frequently encountered in radiocommunication systems



$$P_n = kTB$$

# Microwave Filters

- Two ways of implementing filters in microwave frequency range
  - microwave specific structures (coupled lines, dielectric resonators, periodic structures)
  - **filter synthesis** with lumped elements followed by implementation with transmission lines
- the first strategy leads to more efficient filters but:
  - has lower generality
  - design is often difficult (lack of analytical relationships)

# Filter synthesis

- Filter is designed with lumped elements (L/C) followed by implementation with distributed elements (transmission lines)
  - general
  - analytical relationships easy to implement on the computer
  - efficient
- The preferred procedure is **insertion loss method**

# Insertion loss method

$$P_{LR} = \frac{P_S}{P_L} = \frac{1}{1 - |\Gamma(\omega)|^2}$$

- $|\Gamma(\omega)|^2$  is an even function of  $\omega$

$$|\Gamma(\omega)|^2 = \frac{M(\omega^2)}{M(\omega^2) + N(\omega^2)}$$

$$P_{LR} = 1 + \frac{M(\omega^2)}{N(\omega^2)}$$

- Choosing M and N polynomials appropriately leads to a filter with a completely specified frequency response

# Insertion loss method

- We control the power loss ratio/attenuation introduced by the filter:
  - in the passband (pass all frequencies)
  - in the stopband (reject all frequencies)


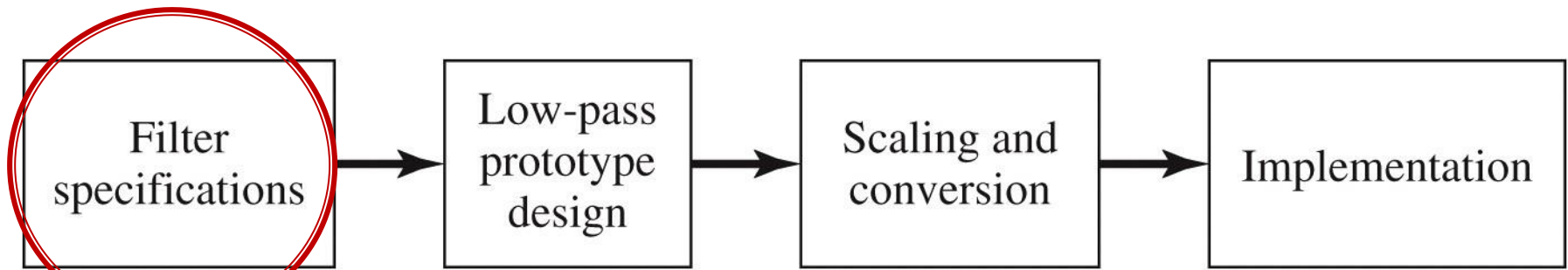


Figure 8.23
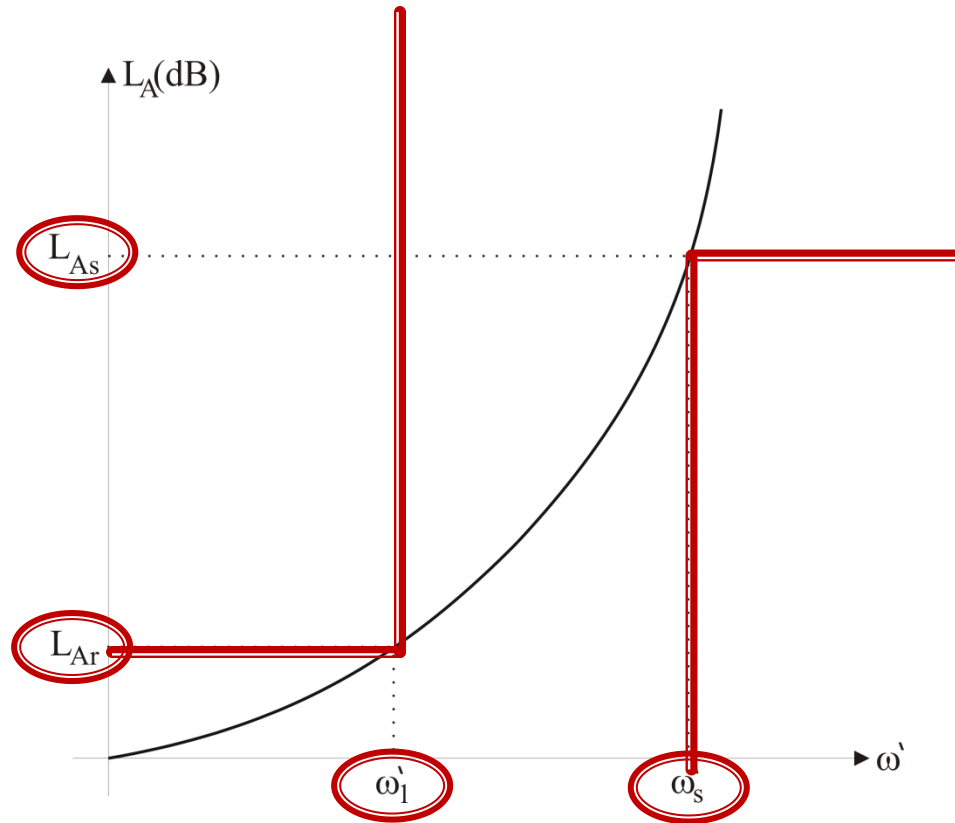
# Filter specifications

- Attenuation
  - in passband
  - in stopband
  - most often in **dB**
- Frequency range
  - passband
  - stopband
  - cutoff frequency  $\omega_1'$   
usually normalized  
(= **1**)





# Insertion loss method

- We choose the right polynomials to design an **low-pass** filter (prototype)
- The low-pass prototype are then converted to the desired other types of filters
  - low-pass, high-pass, bandpass, or bandstop

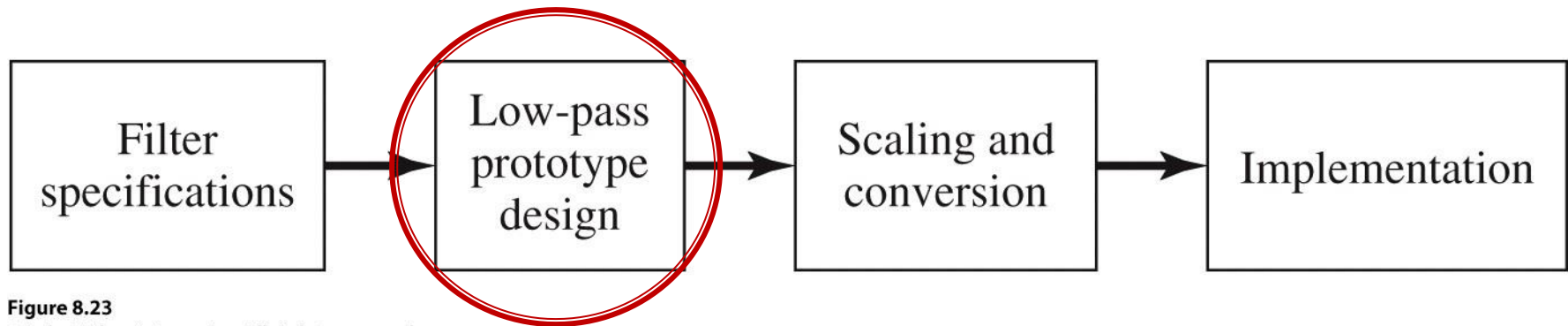


Figure 8.23

# Practical low-pass prototypes responses

- **Maximally flat filters** (Butterworth, binomial): provide the flattest possible passband response
- **Equal ripple filters** (Chebyshev): provide a sharper cutoff but the passband response will have ripples
- **Elliptic function filters**, they have equal-ripple responses in the passband as well as in the stopband,
- **Linear phase filters**, offer linear phase response in the passband to avoid signal distortion (important in some applications)

# Maximally Flat/Equal ripple LPF Prototype

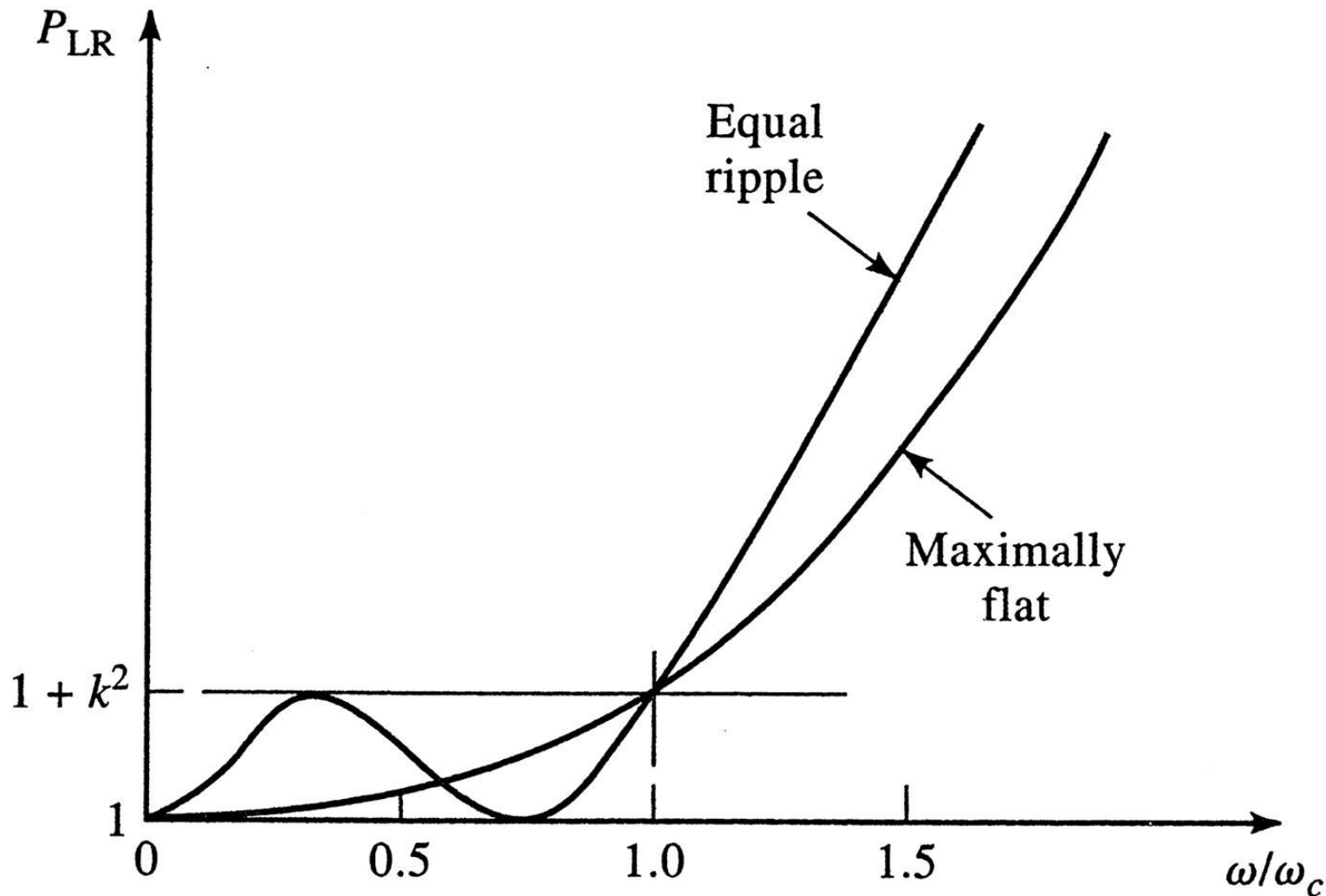


Figure 8.21  
© John Wiley & Sons, Inc. All rights reserved.

# Elliptic function LPF Prototype

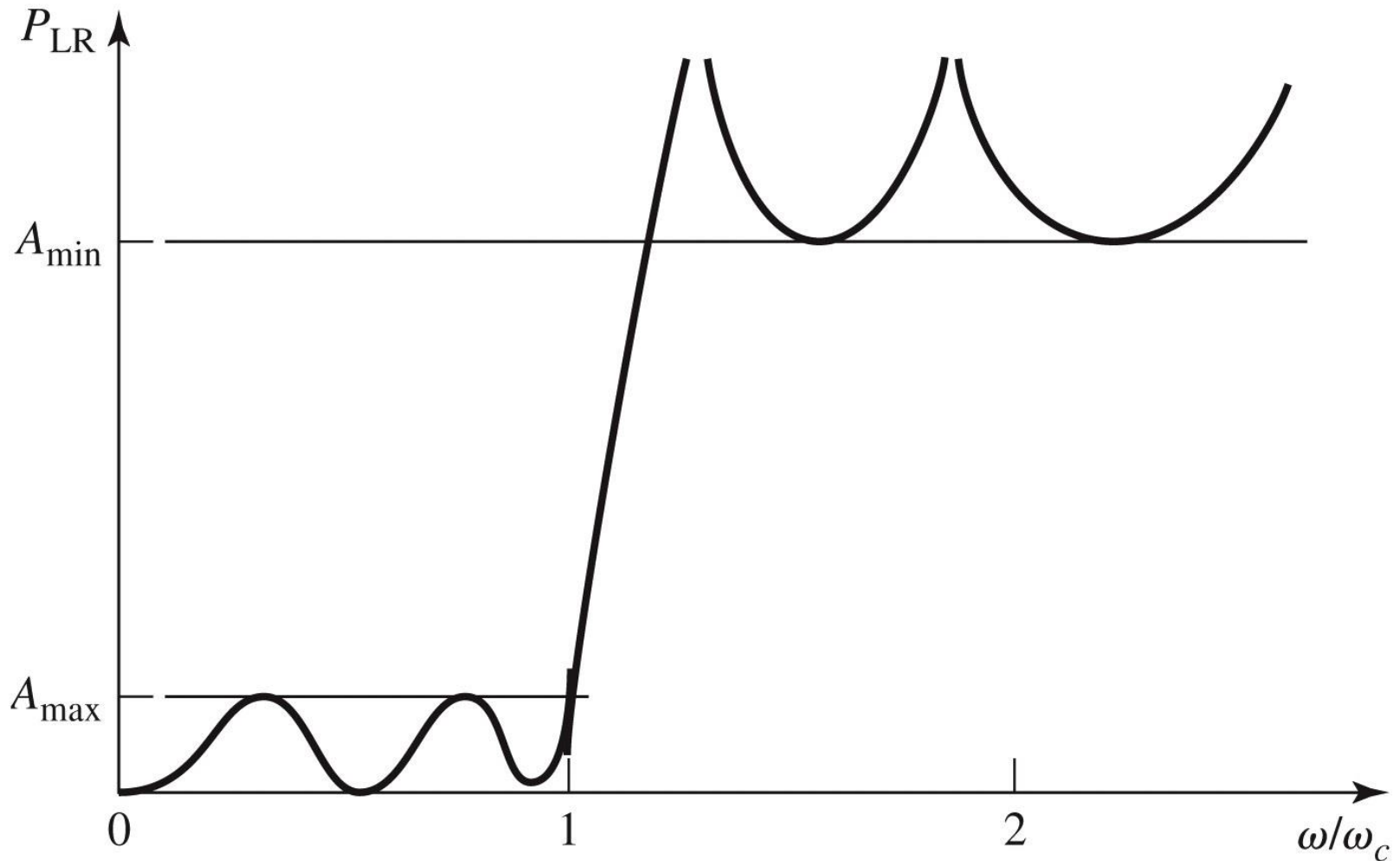


Figure 8.22  
© John Wiley & Sons, Inc. All rights reserved.

# Maximally Flat LPF Prototype

- Polynomial

$$P_{LR} = 1 + k^2 \cdot \left( \frac{\omega}{\omega_c} \right)^{2N}$$

- For  $\omega \gg \omega_c$

$$P_{LR} \approx k^2 \cdot (\omega/\omega_c)^{2N}$$

- attenuation increases at a rate of  $20 \cdot N$  dB/decade
- $k$  gives the attenuation at cutoff frequency (3dB cutoff imposes  $k = 1$ )

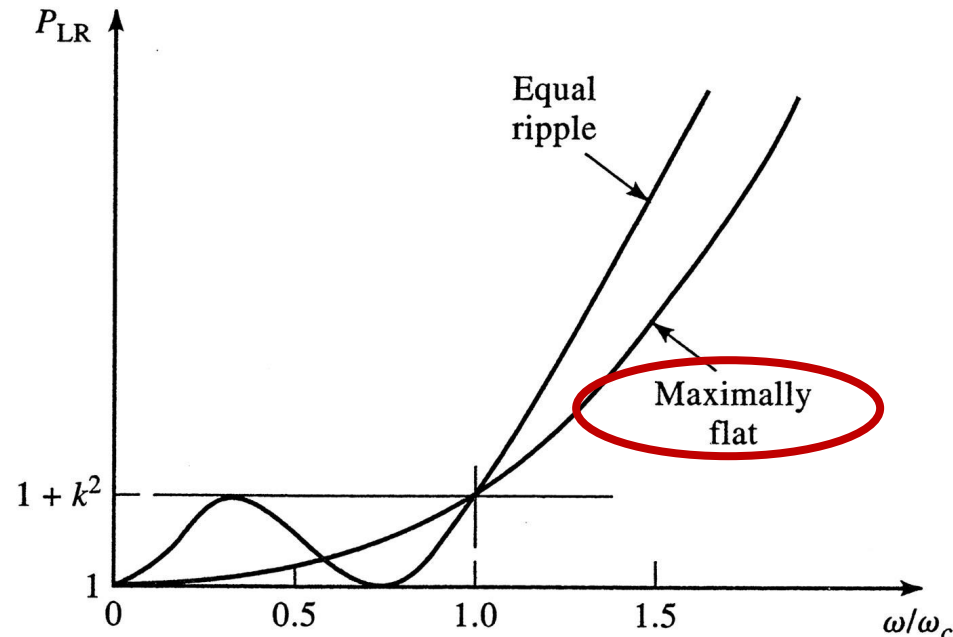


Figure 8.21  
© John Wiley & Sons, Inc. All rights reserved.

# Equal Ripple LPF Prototype

- Polynomial

$$P_{LR} = 1 + k^2 \cdot T_N^2\left(\frac{\omega}{\omega_c}\right)$$

- For  $\omega \gg \omega_c$

$$P_{LR} \approx \frac{k^2}{4} \cdot \left(\frac{2 \cdot \omega}{\omega_c}\right)^{2N}$$

- attenuation increases at a rate of  $20 \cdot N$  dB/decade (**also**)
- attenuation is  $(2^{2N})/4$  greater than the binomial response at any given frequency where  $\omega \gg \omega_c$
- the passband ripples:  $1 + k^2$ ,  $k$  gives the ripple


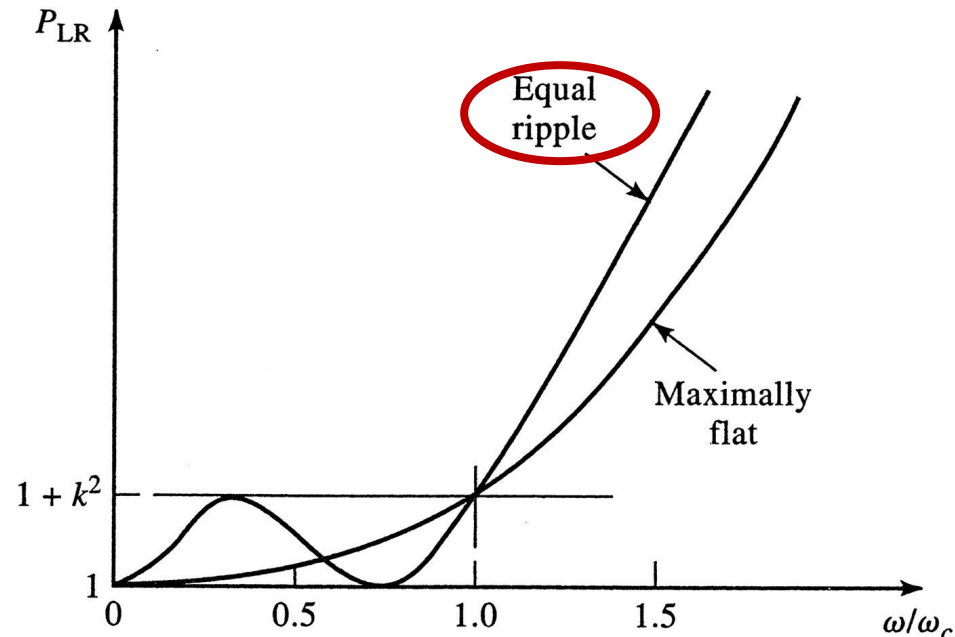


Figure 8.21  
© John Wiley & Sons, Inc. All rights reserved.

# Order (N) of the Maximally Flat filter

$$n \geq \frac{\log \left( \frac{10^{\frac{L_{As}}{10}} - 1}{10^{\frac{L_{Ar}}{10}} - 1} \right)}{2 \cdot \log \frac{\omega'_s}{\omega'_1}}$$


- !attenuations in **dB**

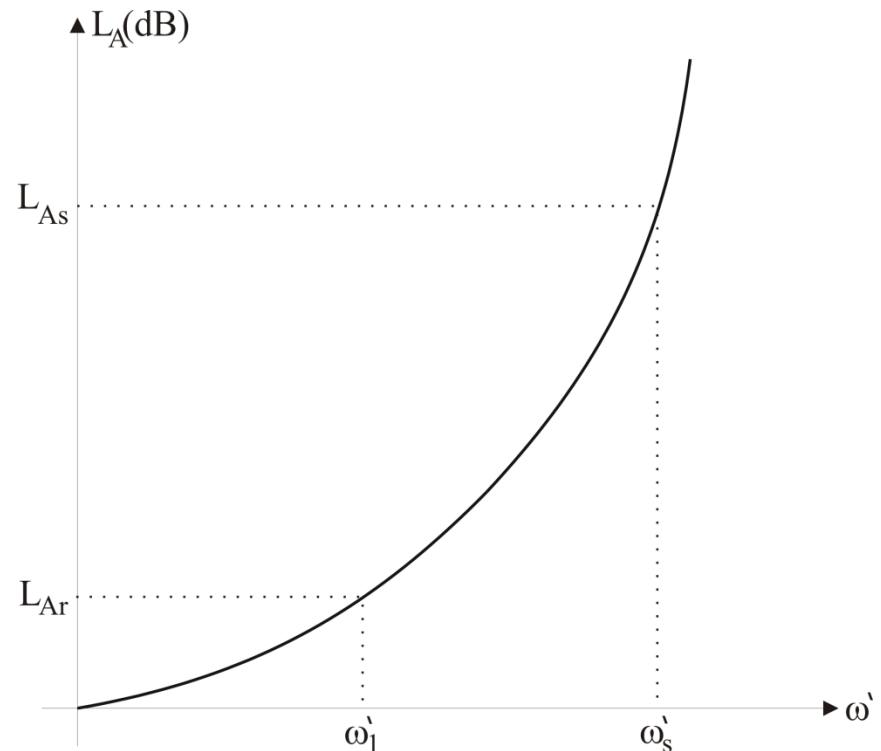

# Order (N) of the Equal Ripple filter


$$n \geq \frac{\cosh^{-1} \left( \sqrt{\frac{10^{\frac{L_{As}}{10}} - 1}{10^{\frac{L_{Ar}}{10}} - 1}} \right)}{\cosh^{-1} \left( \frac{\omega'_s}{\omega'_1} \right)}$$

- !attenuations in **dB**

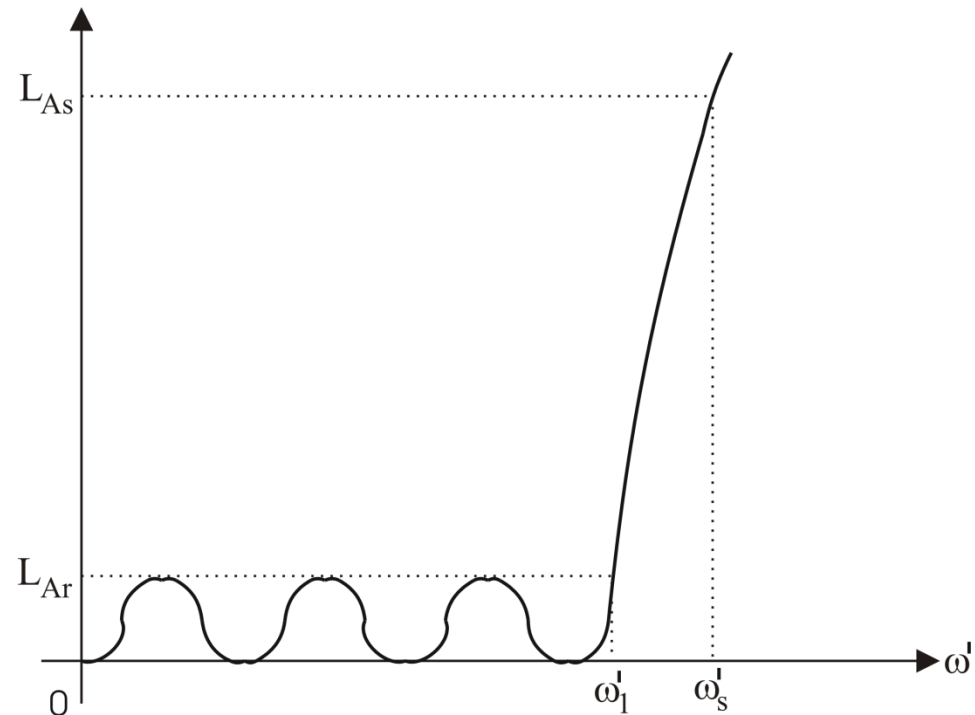




# Maximally flat filter prototypes

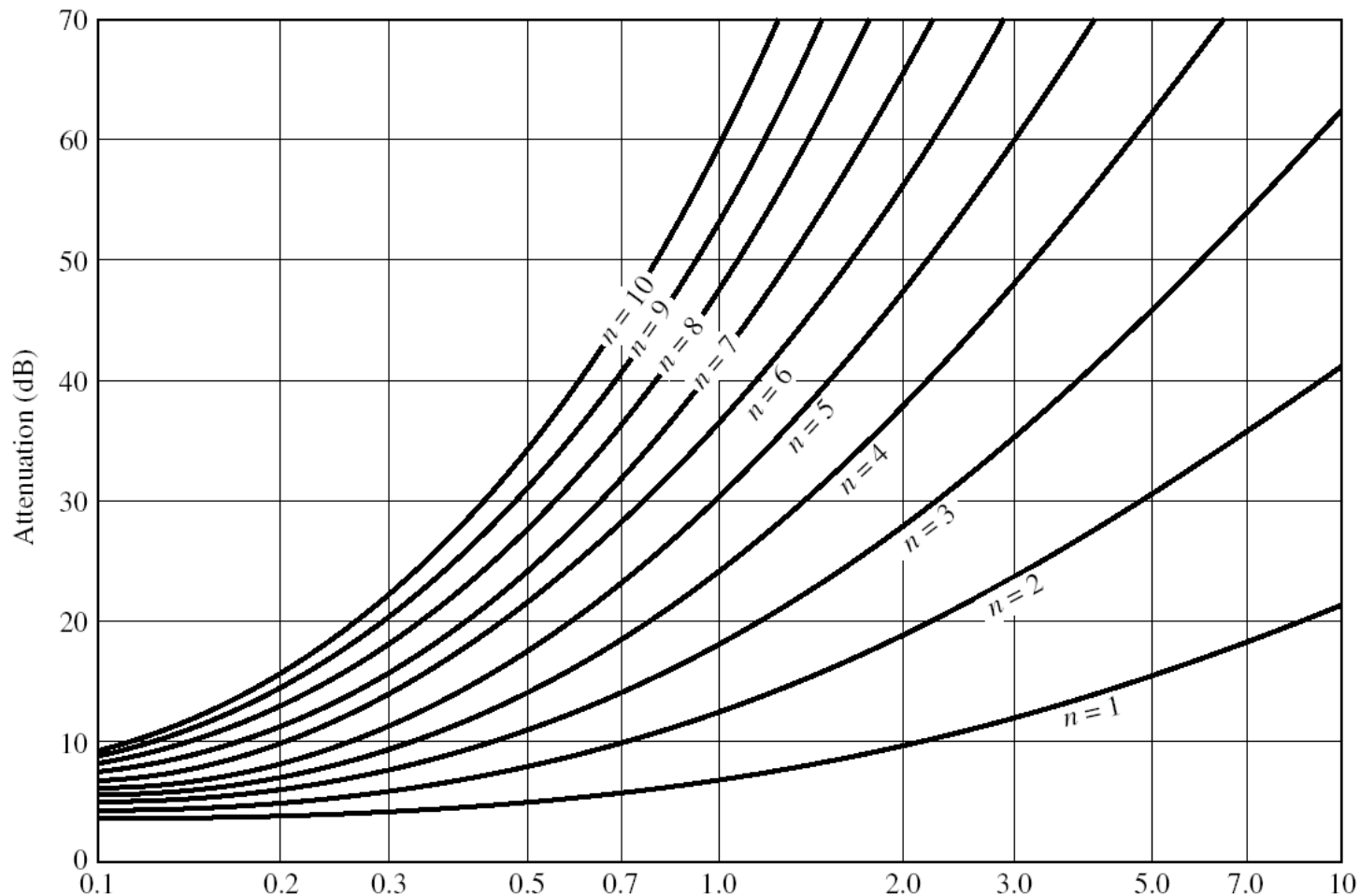

$$\left| \frac{\omega}{\omega_c} \right| - 1$$

Attenuation versus normalized frequency for maximally flat filter prototypes


# 3 dB Equal-ripple filter prototypes

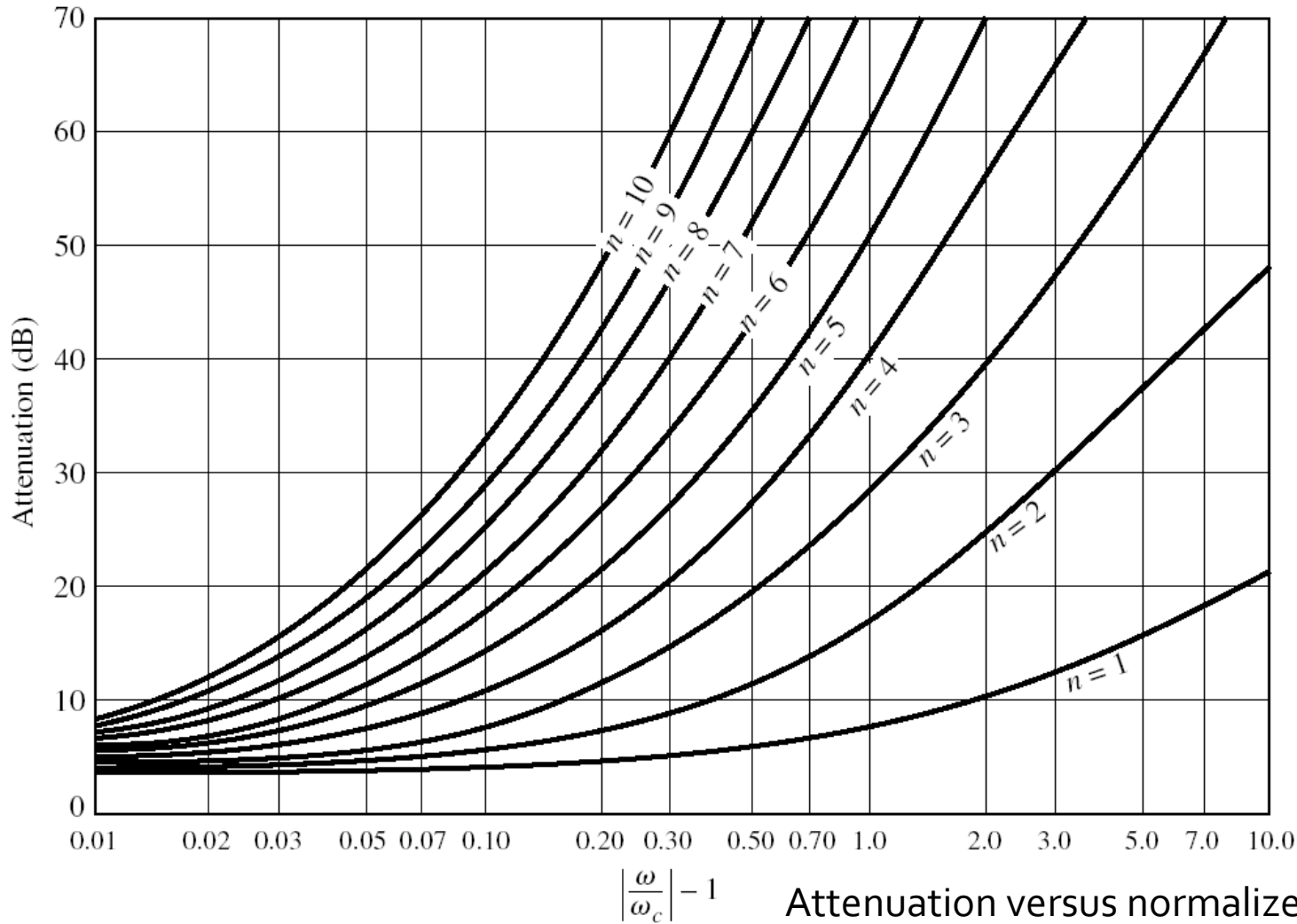

(b)

Attenuation versus normalized frequency for equal-ripple filter prototypes (3dB)


# 0.5 dB Equal-ripple filter prototypes

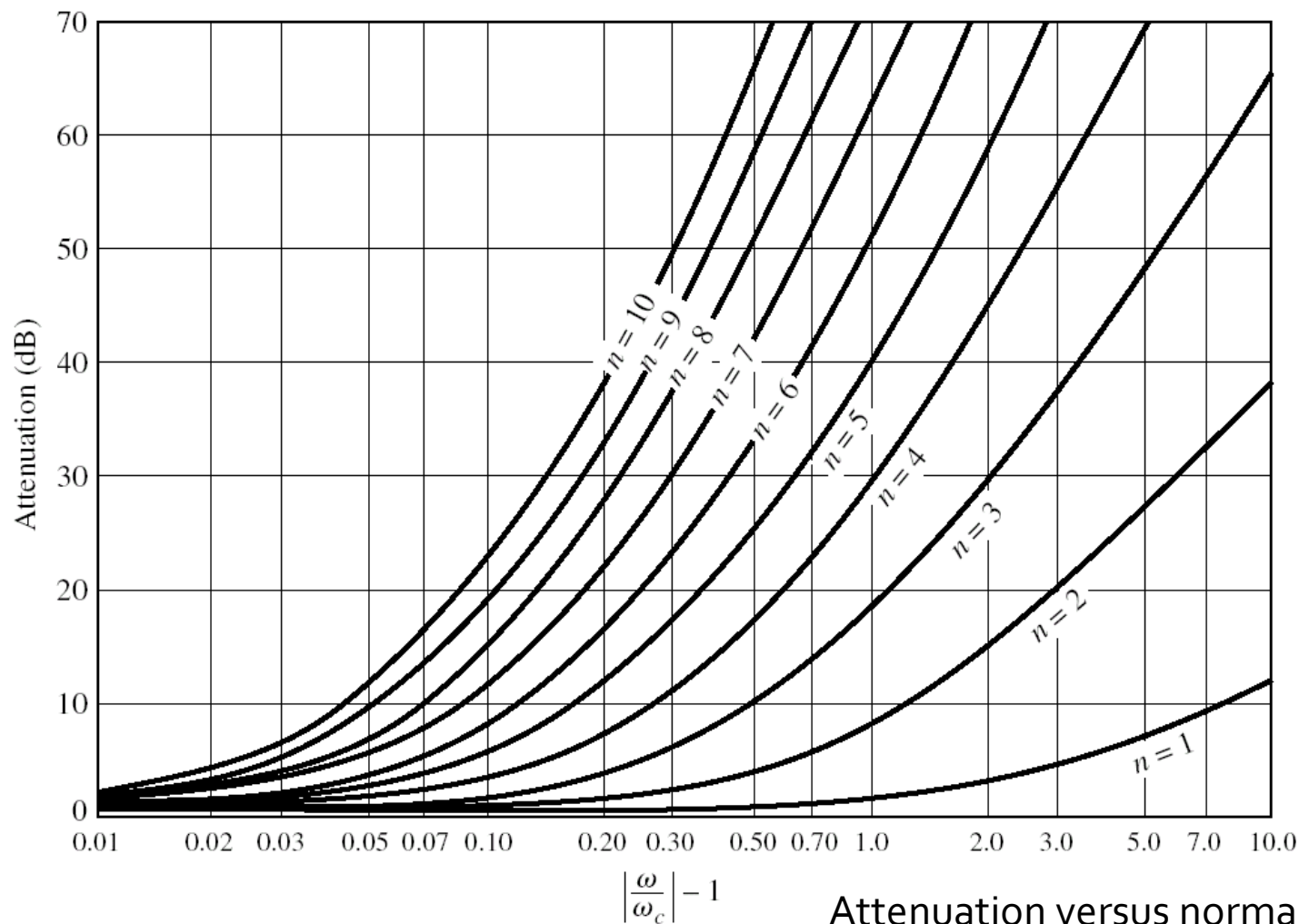


(a)

Attenuation versus normalized frequency for equal-ripple filter prototypes (0.5dB)

# Prototype Filters

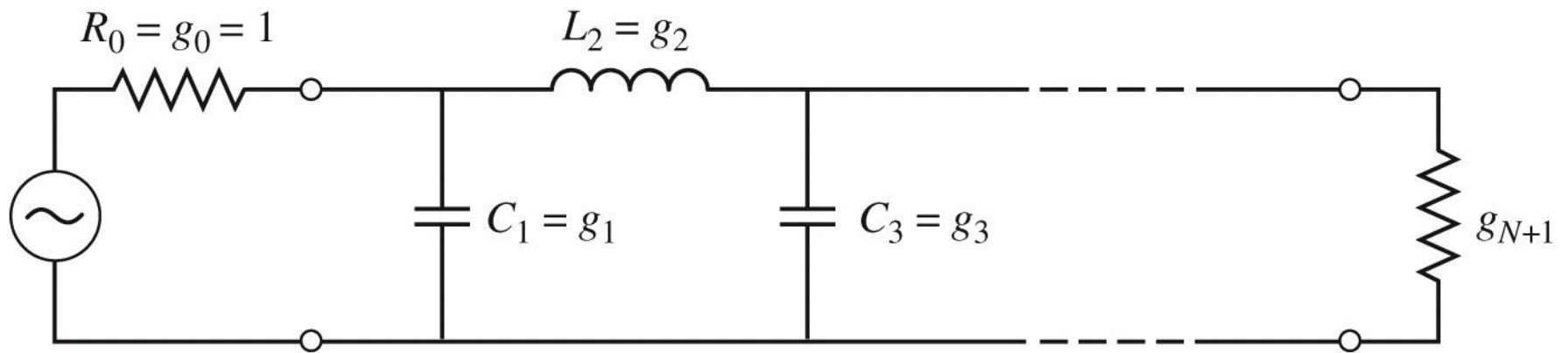

(a)

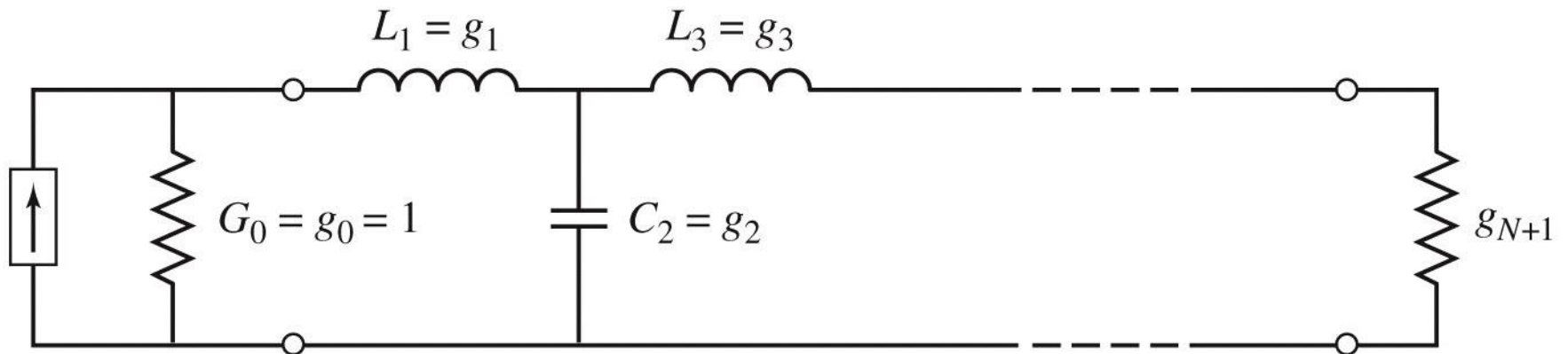

(b)

# Prototype Filters

- Prototype filters are:
  - Low-Pass Filters (**LPF**)
  - cutoff frequency  **$\omega_o = 1 \text{ rad/s}$**  ( $f_o = 0.159 \text{ Hz}$ )
  - connected to a source with  **$R = 1\Omega$**
- The number of reactive elements (L/C) is the order of the filter (N)
- Reactive elements are alternated: series L / shunt C
- There two prototypes with the same response, a prototype beginning with a shunt C element, and a prototype beginning with a series L element

# Prototype Filters

- We define filter parameters  $g_i$ ,  $i=0, N+1$
- $g_i$  are the element values in the prototype filter

$$g_0 = \begin{cases} \text{generator resistance } R'_0 & \text{if } g_1 = C'_1 \\ \text{generator conductance } G'_0 & \text{if } g_1 = L'_1 \end{cases}$$

$$g_k \Big|_{k=1, \overline{N}} = \begin{cases} \text{inductance for series inductors} \\ \text{capacitance for shunt capacitors} \end{cases}$$

$$g_{N+1} = \begin{cases} \text{load resistance } R'_{N+1} & \text{if } g_N = C'_N \\ \text{load conductance } G'_{N+1} & \text{if } g_N = L'_N \end{cases}$$

# Maximally Flat LPF Prototype

- Formulas for filter parameters

$$g_0 = 1$$

$$g_k = 2 \cdot \sin \left[ \frac{(2 \cdot k - 1) \cdot \pi}{2 \cdot N} \right], \quad k = 1, N$$

$$g_{N+1} = 1$$

# Maximally Flat LPF Prototype

**TABLE 8.3** Element Values for Maximally Flat Low-Pass Filter Prototypes ( $g_0 = 1$ ,  $\omega_c = 1$ ,  $N = 1$  to 10)

$N$	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

*Source:* Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.



# Equal-ripple LPF Prototype

- Formulas for filter parameters (iterative)

$$a_k = \sin\left[\frac{(2 \cdot k - 1) \cdot \pi}{2 \cdot N}\right], \quad k = 1, N \quad \beta = \ln\left(\coth \frac{L_{Ar}}{17.37}\right)$$

$$\gamma = \sinh\left(\frac{\beta}{2 \cdot N}\right) \quad b_k = \gamma^2 + \sin^2\left(\frac{k \cdot \pi}{N}\right), \quad k = 1, N$$

$$g_1 = \frac{2 \cdot a_1}{\gamma}$$

$$g_k = \frac{4 \cdot a_{k-1} \cdot a_k}{b_{k-1} \cdot g_{k-1}}, \quad k = 2, N$$

$$g_{N+1} = \begin{cases} 1 & \text{for odd } N \\ \coth^2\left(\frac{\beta}{4}\right) & \text{for even } N \end{cases}$$

**TABLE 8.4** Element Values for Equal-Ripple Low-Pass Filter Prototypes ( $g_0 = 1, \omega_c = 1, N = 1$  to 10, 0.5 dB and 3.0 dB ripple)

0.5 dB Ripple											
$N$	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	0.6986	1.0000									
2	1.4029	0.7071	1.9841								
3	1.5963	1.0967	1.5963	1.0000							
4	1.6703	1.1926	2.3661	0.8419	1.9841						
5	1.7058	1.2296	2.5408	1.2296	1.7058	1.0000					
6	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841				
7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.0000			
8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841		
9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6678	1.2690	1.7504	1.0000	
10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841

3.0 dB Ripple											
$N$	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	1.9953	1.0000									
2	3.1013	0.5339	5.8095								
3	3.3487	0.7117	3.3487	1.0000							
4	3.4389	0.7483	4.3471	0.5920	5.8095						
5	3.4817	0.7618	4.5381	0.7618	3.4817	1.0000					
6	3.5045	0.7685	4.6061	0.7929	4.4641	0.6033	5.8095				
7	3.5182	0.7723	4.6386	0.8039	4.6386	0.7723	3.5182	1.0000			
8	3.5277	0.7745	4.6575	0.8089	4.6990	0.8018	4.4990	0.6073	5.8095		
9	3.5340	0.7760	4.6692	0.8118	4.7272	0.8118	4.6692	0.7760	3.5340	1.0000	
10	3.5384	0.7771	4.6768	0.8136	4.7425	0.8164	4.7260	0.8051	4.5142	0.6091	5.8095

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

- For even  $N$  order of the filter ( $N = 2, 4, 6, 8 \dots$ ) equal-ripple filters **must** closed by a load impedance

$g_{N+1} \neq 1$

- If the application doesn't allow this, supplemental impedance matching is required (quarter-wave transformer, binomial ...) to  $g_L = 1$

# Example

- Design a **3rd order** ~~bandpass~~ filter with **0.5 dB ripples** in passband. ~~The center frequency of the filter should be 1 GHz. The fractional bandwidth of the passband should be 10%, and the impedance 50Ω.~~

# LPF Prototype


- 0.5dB equal-ripple table or design formulas:

- $g_1 = 1.5963 = L_1/C_3,$

- $g_2 = 1.0967 = C_2/L_4,$



- $g_3 = 1.5963 = L_3/C_5,$

- $g_4 = 1.000 = R_L$

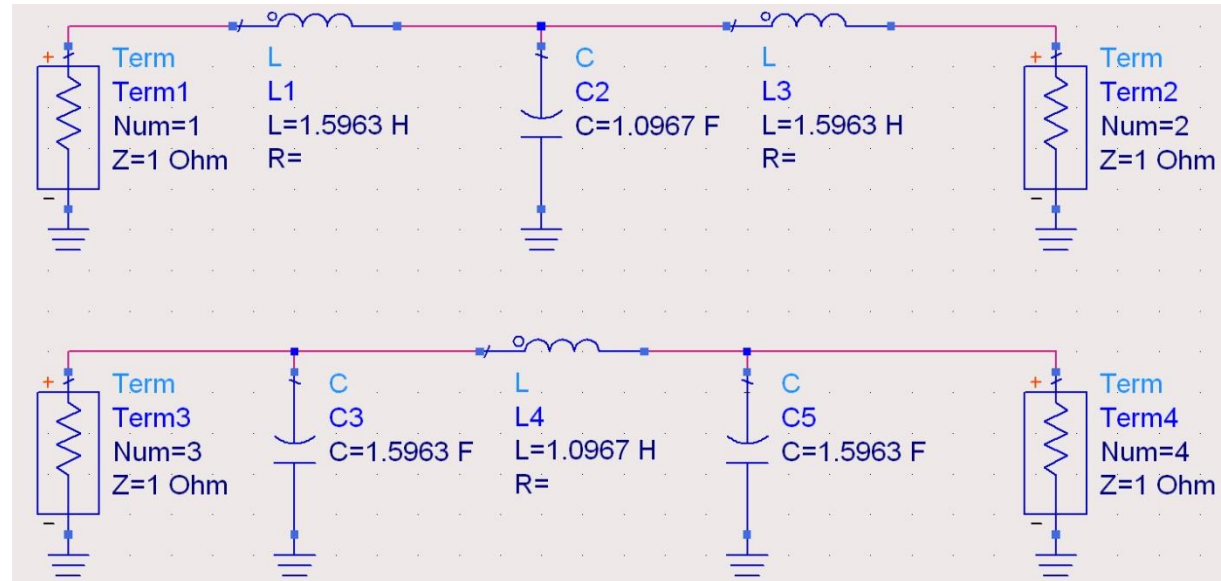
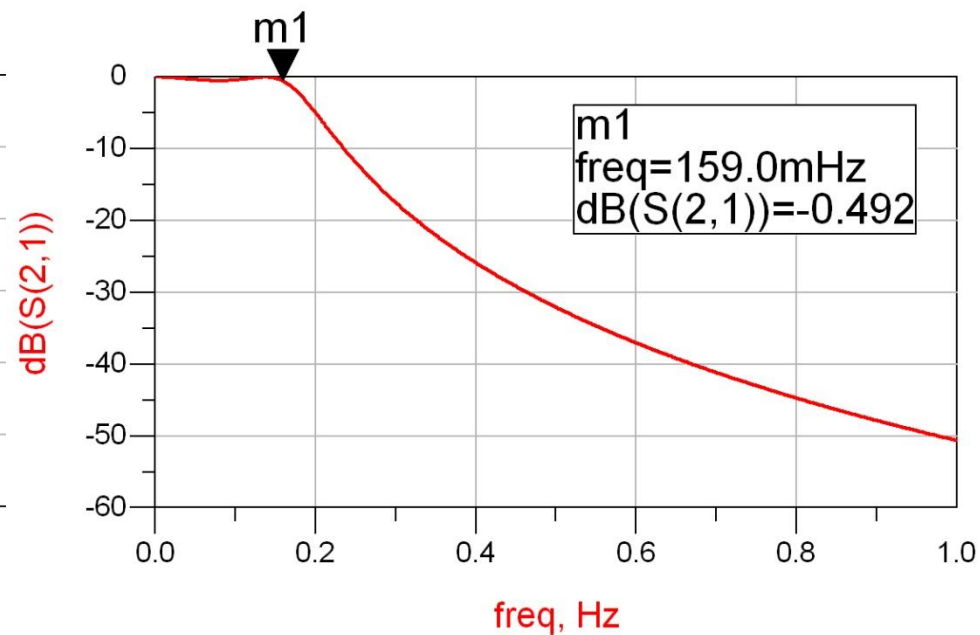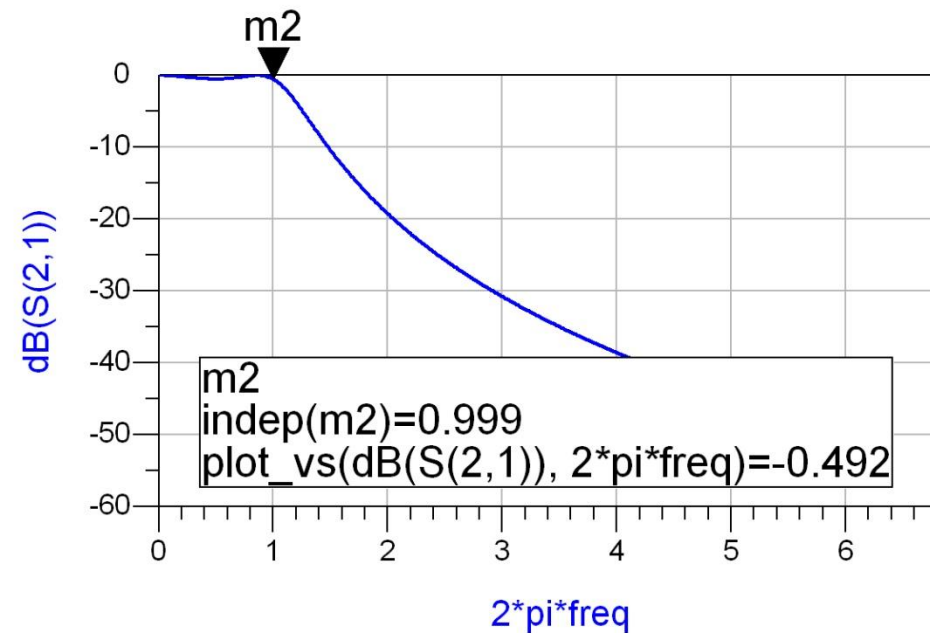
# LPF Prototype

- $\omega_o = 1 \text{ rad/s}$  ( $f_o = \omega_o / 2\pi = 0.159 \text{ Hz}$ )



# Impedance and Frequency Scaling

- After computing prototype filter's elements:
  - Low-Pass Filters (**LPF**)
  - cutoff frequency  **$\omega_o = 1 \text{ rad/s}$**  ( $f_o = 0.159 \text{ Hz}$ )
  - connected to a source with  **$R = 1\Omega$**
- component values can be scaled in terms of impedance and frequency

# Impedance and Frequency Scaling

- LPF Prototype is only used as an intermediate step
  - Low-Pass Filter (LPF)
  - cutoff frequency  $\omega_o = 1 \text{ rad/s}$  ( $f_o = 0.159 \text{ Hz}$ )
  - connected to a source with  $R = 1\Omega$

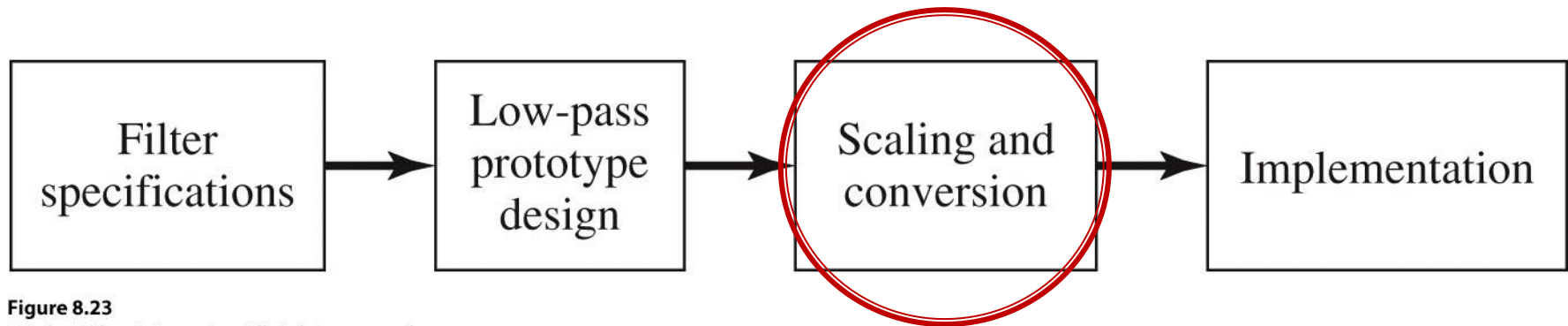


Figure 8.23

# Impedance Scaling

- To design a filter which will work with a source resistance of  $R_0$  we multiply all the impedances of the prototype design by  $R_0$  (" $'$ " denotes scaled values)

$$R'_s = R_0 \cdot (R_s = 1)$$

$$R'_L = R_0 \cdot R_L$$

$$L' = R_0 \cdot L$$

$$C' = \frac{C}{R_0}$$



# Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.etti.tuiasi.ro>
- [rdamian@etti.tuiasi.ro](mailto:rdamian@etti.tuiasi.ro)