

Lecture 12

2023/2024

Microwave Devices and Circuits for Radiocommunications

2023/2024

- 2C/1L, **MDCR**
- **Attendance at minimum 7 sessions (course or laboratory)**
- Lectures- **associate professor Radu Damian**
 - Tuesday 16-18, ~~Online~~, P8
 - E – 50% final grade
 - **problems** + (2p atten. lect.) + (3 tests) + (bonus activity)
 - first test L1: 20-27.02.2024 (t2 and t3 not announced, lecture)
 - 3att.=+0.5p
 - **all materials/equipments authorized**

2023/2024

- Laboratory – **associate professor Radu Damian**
 - Tuesday 08-12, 11.13 / (08:10)
 - L – 25% final grade
 - ADS, 4 sessions
 - Attendance + **personal results**
 - P – 25% final grade
 - ADS, 3 sessions (-1? 20.02.2024)
 - personal homework

Materials

■ <http://rf-opto.etti.tuiasi.ro>

The screenshot shows a web browser window with the URL http://rf-opto.etti.tuiasi.ro/microwave_cd.php?chg_lang=0. The page features a dark blue navigation bar with links for Main, Courses, Master, Staff, Research, Students, and Admin. Below this is a secondary navigation bar with links for Microwave CD, Optical Communications, Optoelectronics, Internet, Antennas, Practica, Networks, and Educational software. The main content area is titled "Microwave Devices and Circuits for Radiocommunications (English)" and includes the following information:

- Course: MDCR (2017-2018)**
- Course Coordinator:** Assoc.P. Dr. Radu-Florin Damian
- Code:** EDOS412T
- Discipline Type:** DOS; Alternative, Specialty
- Credits:** 4
- Enrollment Year:** 4, Sem. 7

Activities

Course: Instructor: Assoc.P. Dr. Radu-Florin Damian, 2 Hours/Week, Specialization Section, Timetable:
Laboratory: Instructor: Assoc.P. Dr. Radu-Florin Damian, 1 Hours/Week, Group, Timetable:

Evaluation

Type: Examen

A: 50%, (Test/Colloquium)
B: 25%, (Seminary/Laboratory/Project Activity)
D: 25%, (Homework/Specialty papers)

Grades

[Aggregate Results](#)

Attendance

[Course](#)
[Laboratory](#)

Lists

[Bonus-uri acumulate \(final\)](#)
[Studenti care nu pot intra in examen](#)

Materials

Course Slides

- [MDCR Lecture 1](#) (pdf, 5.43 MB, en, [↗](#))
- [MDCR Lecture 2](#) (pdf, 3.67 MB, en, [↗](#))
- [MDCR Lecture 3](#) (pdf, 4.76 MB, en, [↗](#))
- [MDCR Lecture 4](#) (pdf, 5.58 MB, en, [↗](#))

On the right side of the screenshot, there is a banner for "RF-OPTO" with the ETTI logo and the University of Technical Sciences (UTS) logo. The banner includes a language selector with "English" (UK flag) and "Romana" (Romanian flag) options. Below the banner is another navigation bar with links for Main, Courses, Master, Staff, Research, Grades, Student List, Exams, and Photos. The "Exams" link is highlighted. Below this is a section titled "Online Exams" with the text: "In order to participate at online exams you must get ready following..."

Site



Microwave and Optoelectronics Laboratory



We are enlisted in the Telecommunications Department of the Electronics, Telecommunication and Information Technology Faculty (ETTI) from the "Gh. Asachi" Technical University (TUJIASI) in Iasi, Romania

We currently cover inside ETTI the fields related to:

- Microwave Circuits and Devices
- Optoelectronics
- Information Technology

Courses

Nr.	Course	Shortcut	Code	Type	Semester	Credits	Weekly	Examination	Link
1	Microwave Devices and Circuits for Radiocommunications	DCMR	DOS412T	DOS	7	4	0P,1L,0S,2C	Exam	details
2	Monolithic Microwave Integrated Circuits	CIMM	RD.IA.207	DOMS	11	6	1.5L,0S,2C,0P	Exam	details
3	Advanced Techniques in the Design of the Radio-communications Systems	TAPSR	RD.IA.103	DIMS	9	6	1.5P,0L,0S,2C	Exam	details
4	Optical Communications	CO	DOS409T	DOS	7	5	0P,1L,0S,3C	Colloquium	details
5	Optical Communications	OC	EDOS409T	DOS	7	5	0P,1L,0S,3C	Exam	details
6	Satellite Communications	CS	RC.IA.104	DIMS	9	6	0L,0S,2C,1.5P	Exam	details
7	Applied Informatics 1	IA1	DOF135	DOF	1	4	0P,1L,0S,2C	Verification	details
8	Applied Informatics 1	AI1	EDOF135	DOF	1	4	0P,1L,0S,2C	Verification	details
9	Databases, Web Programming and Interfacing	DWPI	ITT.IA.601	DIS	11	5	1P,1L,0.25S,1C	Verification	details
10	Web Applications Design	PAW	RC.IA.108	DIMS	10	5	1L,0S,1.5C,1P	Exam	details
11	Optoelectronics	OPTO	DID405M	DID	8	4	0P,1L,0S,2C	Colloquium	details
12	Microwave Devices and Circuits for Radiocommunications (English)	MDCR	EDOS412T	DOS	8	4	0P,1L,0S,2C	Exam	details



Materials

- RF-OPTO
 - <http://rf-opto.etti.tuiasi.ro>
- **David Pozar, “Microwave Engineering”,**
Wiley; 4th edition , 2011
 - 1 exam problem ← Pozar
- Photos
 - sent by email/**online exam > Week4-Week6**
 - used at lectures/laboratory

Online – Registration no.

- access to **online exams** requires the **password** received by email

The password is communicated during the lectures. It is necessary to

Password

Registration no.

Name of the student

Proposed email 1

Proposed email 2

Write the code below

 **RF-OPTO** 

English | Romana |

[Main](#) [Courses](#) [Master](#) [Staff](#) [Research](#) [Students](#)

[Login](#) [Tutoring](#)

Login

Use the Registration no. and your email or the password received by email

Registration no.

Email/Password

Write the code below

Password

■ received by email

Important message from RF-OPTO Inbox x

 **Radu-Florin Damian**
to me, POPESCU ▾

🗨 Romanian ▾ > English ▾ [Translate message](#)



Laboratorul de Microunde si Optoelectronica
Facultatea de Electronica, Telecomunicatii si Tehnologia Informatiei
Universitatea Tehnica "Gh. Asachi" Iasi

In atentie: POPESCU GOPO ION

Parola pentru a accesa examenele pe server-ul **rf-opto** este
Parola: [REDACTED]

Identificati-va pe [server](#), cu parola, cat mai rapid, pentru confirmare.

Memorati acest mesaj intr-un loc sigur, pentru utilizare ulterioara

Attention: POPESCU GOPO ION

The password to access the exams on the **rf-opto** server is
Password: [REDACTED]

Login to the [server](#), with this password, as soon as possible, for confirmation.

Save this message in a safe place for later use

[Reply](#) [Reply all](#) [Forward](#)

Subject	Correspondents
Important message from RF-OPTO	POPESCU GOPO ION
Validation of MD/CR exam from 02/05/2020	[REDACTED]
[REDACTED]	[REDACTED]

From: Me <rdamian@etti.tuiasi.ro> ★
Subject: Important message from RF-OPTO
To: [REDACTED]
Cc: Me <rdamian@etti.tuiasi.ro> ★



Laboratorul de Microunde si Optoelectronica
Facultatea de Electronica, Telecomunicatii si Tehnologia Informatiei
Universitatea Tehnica "Gh. Asachi" Iasi

In atentie: POPESCU GOPO ION

Parola pentru a accesa examenele pe server-ul **rf-opto** este
Parola: [REDACTED]

Identificati-va pe [server](#), cu parola, cat mai rapid, pentru confirmare.

Memorati acest mesaj intr-un loc sigur, pentru utilizare ulterioara

Attention: POPESCU GOPO ION

The password to access the exams on the **rf-opto** server is
Password: [REDACTED]

Login to the [server](#), with this password, as soon as possible, for confirmation.

Save this message in a safe place for later use

Online exam manual

- The online exam app used for:
 - ~~lectures (attendance)~~
 - laboratory
 - project
 - ~~examinations~~

Materials

Other data

[Manual examen on-line](#) (pdf, 2.65 MB, ro, 🇷🇴)

[Simulare Examen](#) (video) (mp4, 65.12 MB, ro, 🇷🇴)

Microwave Devices and Circuits (Englis

Examen online

- always against a **timetable**
 - long period (lecture attendance/laboratory results)
 - ~~short period (tests: 15min, exam: 2h)~~

Announcement 23:59 (10/05/2020)	Support material 00:05 (11/05/2020)	Exam Topics 00:07 (11/05/2020)	Results 00:10 (11/05/2020)	End 00:20 (15/05/2020)	Confirmation 00:20 (16/05/2020)	Next timeframe in: 05 m 43 s Refresh now
---	---	--	--------------------------------------	----------------------------------	---	--

Announcement

This is a "fake" exam, introduced to familiarize you with the server interface and to perform the necessary actions during an exam: thesis scan, selfie, use email for co

Server Time

All exams are based on the server's time zone (it may be different from local time). For reference time on the server is now:

10/05/2020 23:59:16

Online results submission

- many numerical values/files

Schema finala	Rezultate - castig	Rezultate - zgomot	Fisier justificare calcul (factor andrei)	Fisier zap (optional)	T1, fisier parametri S	T2, fisier parametri S	Z1	Z2	Z3	Z4	Z5	Z6	Z7	Ze1	Zo1	Ze2	Zo2	Ze3	Zo3	Ze4	Zo4	Ze5	Zo5	Ze6
86 - 5428 - 259 ...	86 - 5428 - 260 ...	86 - 5428 - 261 ...	86 - 5428 - 316 ...	-	86 - 5428 - 314 ...	86 - 5428 - 315 ...	148.33	155.88	202.12	164.35	180.91	30.29	185.19	79.9	37	68.89	45.14	61.83	45.05	57.97	46.02	61.85	45.05	68.8
86 - 5622 - 259 ...	86 - 5622 - 260 ...	86 - 5622 - 261 ...	86 - 5622 - 316 ...	86 - 5622 - 262 ...	86 - 5622 - 314 ...	86 - 5622 - 315 ...	26.97	153.5	34.64	35.79	55.56	26.212	10.693	0	0	0	0	0	0	0	0	0	0	0
86 - 5488 - 259 ...	86 - 5488 - 260 ...	86 - 5488 - 261 ...	86 - 5488 - 316 ...	86 - 5488 - 262 ...	86 - 5488 - 314 ...	86 - 5488 - 315 ...	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
86 - 5391 - 259 ...	86 - 5391 - 260 ...	86 - 5391 - 261 ...	86 - 5391 - 316 ...	-	-	-	50	50	50	50	50	50	50	70.14	40.39	61.85	44.59	55.7	45.2	54.89	45.38	58.65	45.8	70.0
86 - 5664 - 259 ...	86 - 5664 - 260 ...	86 - 5664 - 261 ...	86 - 5664 - 316 ...	-	86 - 5664 - 314 ...	86 - 5664 - 315 ...	168.02	150.5	178.28	133.75	92.12	121.67	144.48	94.36	36.19	70.77	42.56	65.69	42.05	55.17	42.29	65.59	42.05	70.7
86 - 5665 - 259 ...	86 - 5665 - 260 ...	86 - 5665 - 261 ...	86 - 5665 - 316 ...	-	86 - 5665 - 314 ...	86 - 5665 - 315 ...	162.2	80.8	209.2	140.85	135.1	183.7	167.6	94.58	36.15	78.16	39.77	65.57	45.05	65.57	45.05	78.16	39.77	94.5
86 - 5433 - 259 ...	86 - 5433 - 260 ...	86 - 5433 - 261 ...	86 - 5433 - 316 ...	-	86 - 5433 - 314 ...	86 - 5433 - 315 ...	165.138	106.228	226.157	130.134	72.71	180.177	164.616	101.36	36.11	77.22	42.49	68.02	45.62	60	45.42	68.02	45.62	77.2
86 - 5608 - 259 ...	86 - 5608 - 260 ...	86 - 5608 - 261 ...	86 - 5608 - 316 ...	-	86 - 5608 - 314 ...	86 - 5608 - 315 ...	150.84	152.5	30.94	32.37	54.36	19.837	29.85	64.14	40.145	54.32	46.32	53.8	46.7	53.8	46.7	54.32	46.32	54.9
86 - 5555 - 259 ...	86 - 5555 - 260 ...	86 - 5555 - 261 ...	86 - 5555 - 316 ...	-	86 - 5555 - 314 ...	86 - 5555 - 315 ...	168.001	150.288	178.399	133.115	92.491	121.257	144.126	97.05	36.16	71.13	43.09	65.45	42.12	55.66	42.18	65.45	42.12	71.1

Online results submission

- many numerical values

	Z1	Z2	Z3	Z4	Z5	Z6	Z7
	148.33	155.88	202.12	164.35	180.91	30.29	185.19
	25.97	153.5	34.64	35.79	55.56	26.212	10.692
	0	0	0	0	0	0	0
	50	50	50	50	50	50	50




Online results submission

**Grade = Quality of the work +
+ Quality of the submission**

Impedance Matching

Impedance Matching with Stubs

Smith chart, $r=1$ and $g=1$

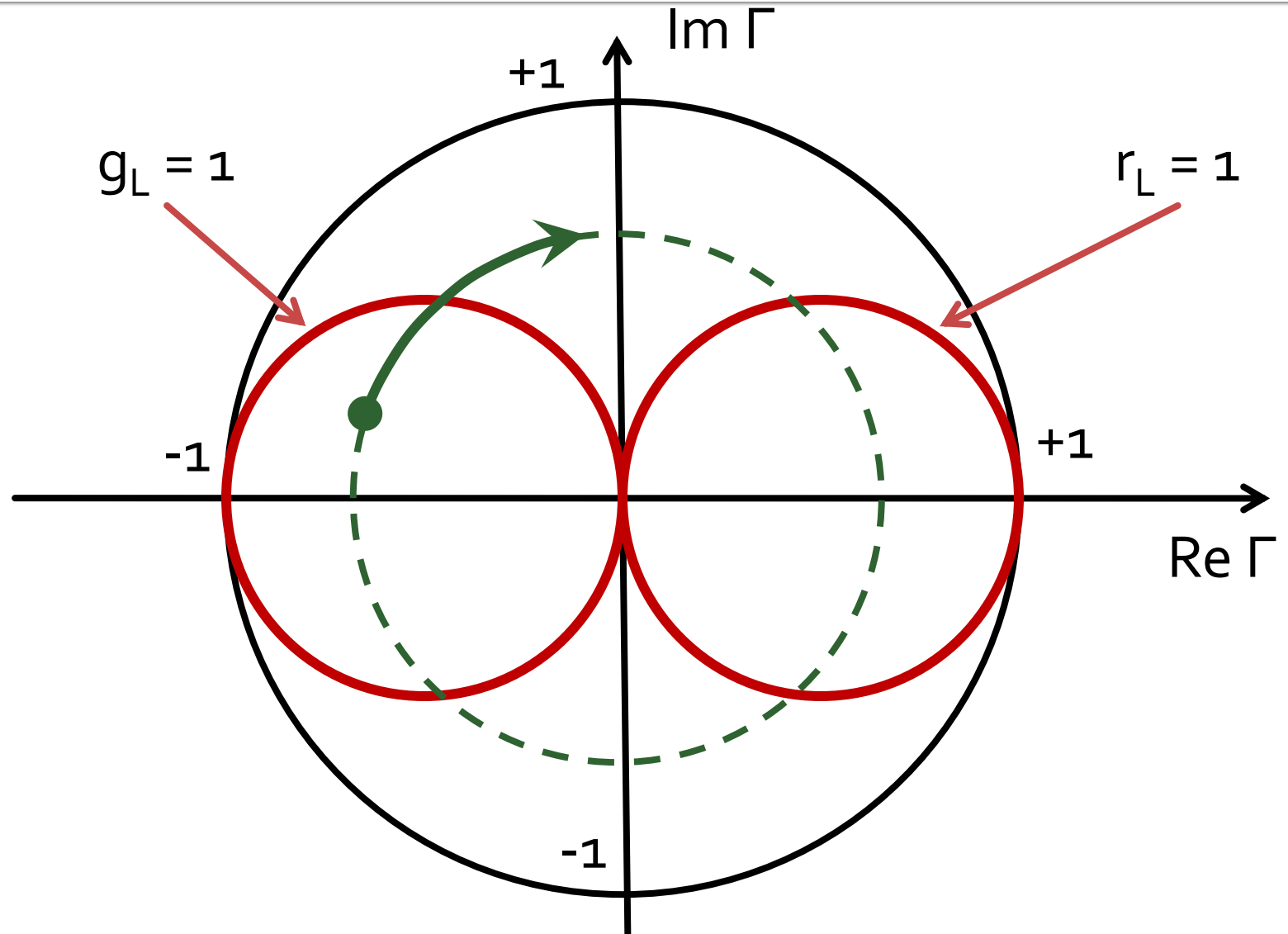


Analytical solutions


Exam / Project

Case 1, Shunt Stub

- Shunt Stub

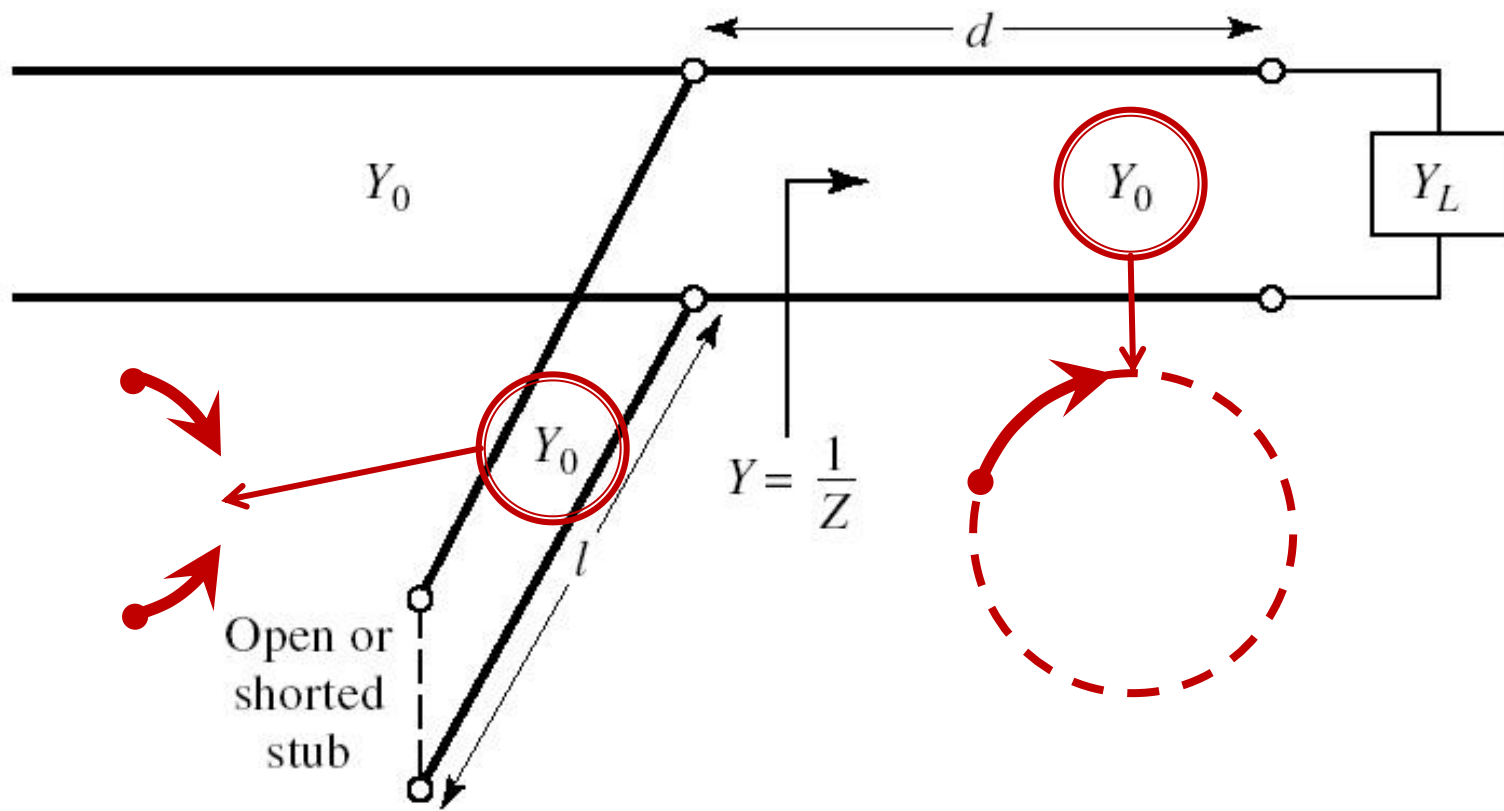

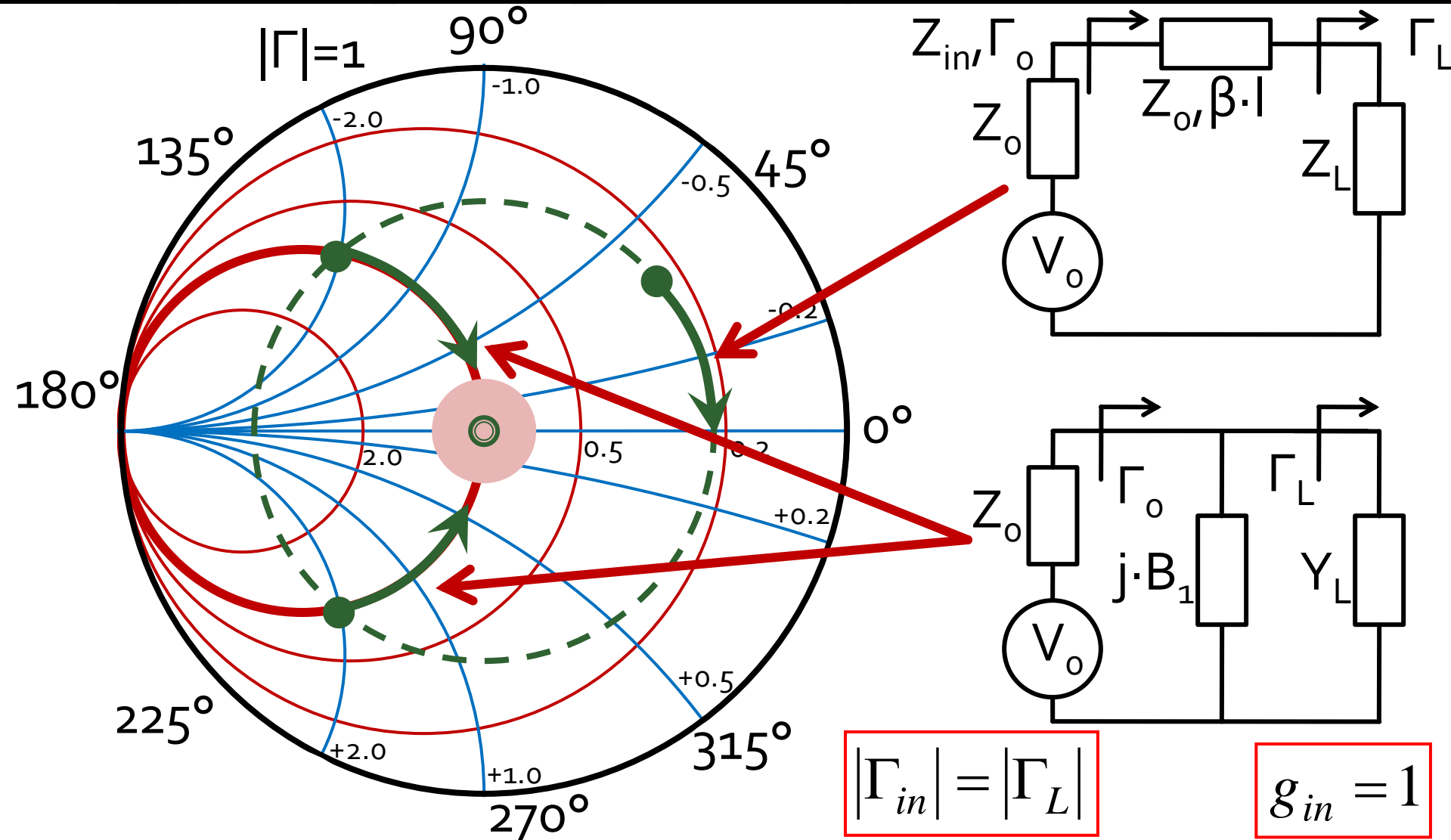Matching, series line + shunt susceptance



Analytical solution, usage

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = 0.593 \angle 46.85^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ \quad \cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **“+” solution** ↓

$$(46.85^\circ + 2\theta) = +126.35^\circ \quad \theta = +39.7^\circ \quad \text{Im } y_S = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.472$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_S) = -55.8^\circ (+180^\circ) \rightarrow \theta_{sp} = 124.2^\circ$$

- **“-” solution** ↓

$$(46.85^\circ + 2\theta) = -126.35^\circ \quad \theta = -86.6^\circ (+180^\circ) \rightarrow \theta = 93.4^\circ$$

$$\text{Im } y_S = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +1.472 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_S) = 55.8^\circ$$

Analytical solution, usage

$$(\varphi + 2\theta) = \begin{cases} +126.35^\circ \\ -126.35^\circ \end{cases} \quad \theta = \begin{cases} 39.7^\circ \\ 93.4^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -1.472 \\ +1.472 \end{cases} \quad \theta_{sp} = \begin{cases} -55.8^\circ + 180^\circ = 124.2^\circ \\ +55.8^\circ \end{cases}$$



- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

$$l_1 = \frac{39.7^\circ}{360^\circ} \cdot \lambda = 0.110 \cdot \lambda$$

$$l_2 = \frac{124.2^\circ}{360^\circ} \cdot \lambda = 0.345 \cdot \lambda$$


$$l_1 = \frac{93.4^\circ}{360^\circ} \cdot \lambda = 0.259 \cdot \lambda$$
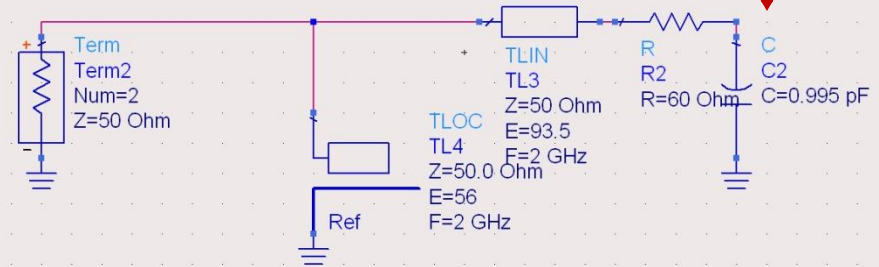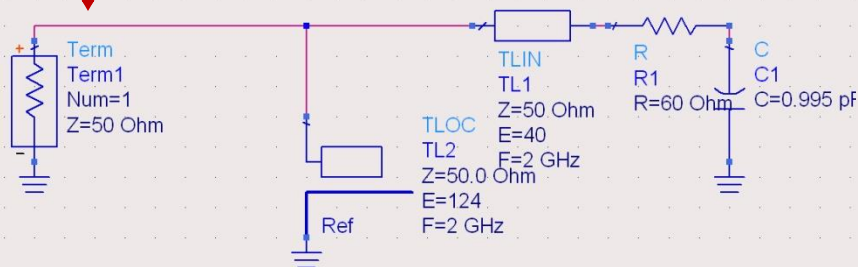
$$l_2 = \frac{55.8^\circ}{360^\circ} \cdot \lambda = 0.155 \cdot \lambda$$






Case 2, Series Stub

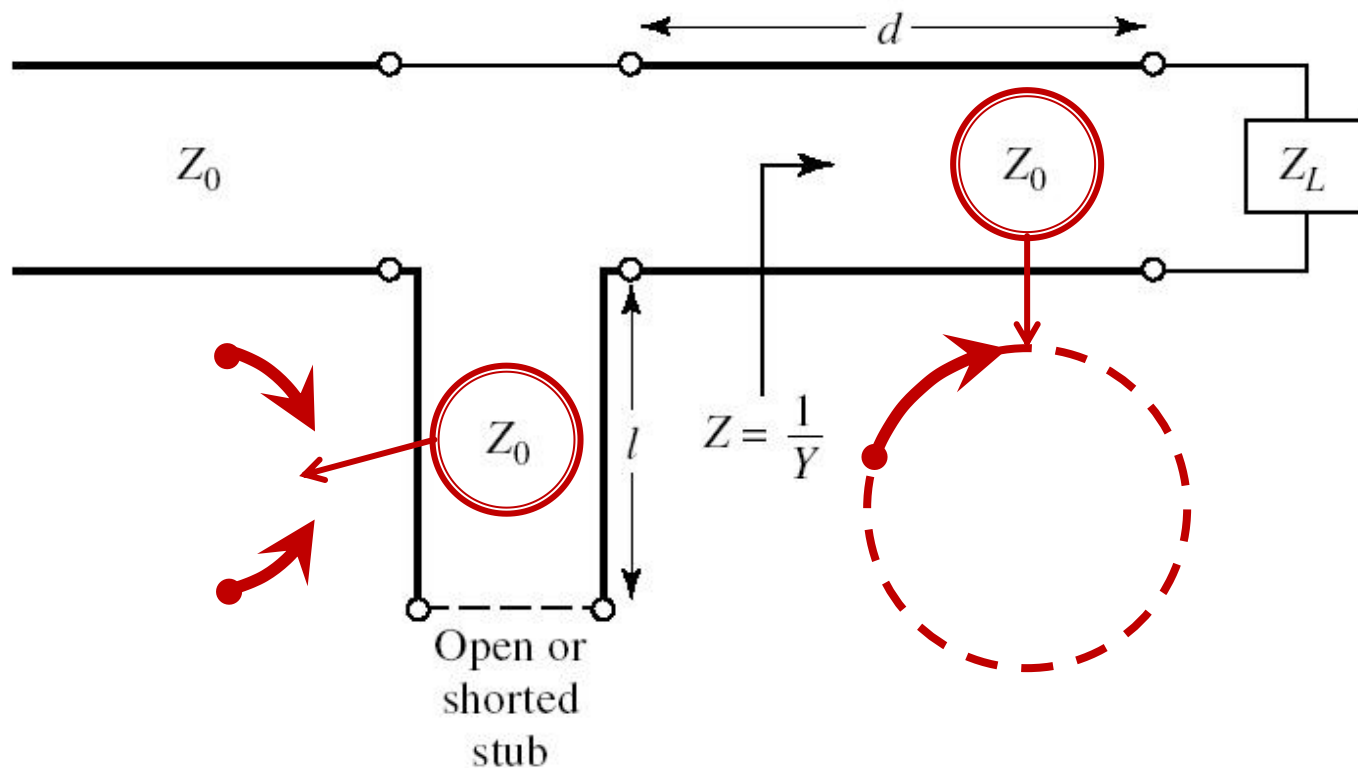- Series Stub
- difficult to realize in single conductor line technologies (microstrip)



Matching, series line + series reactance

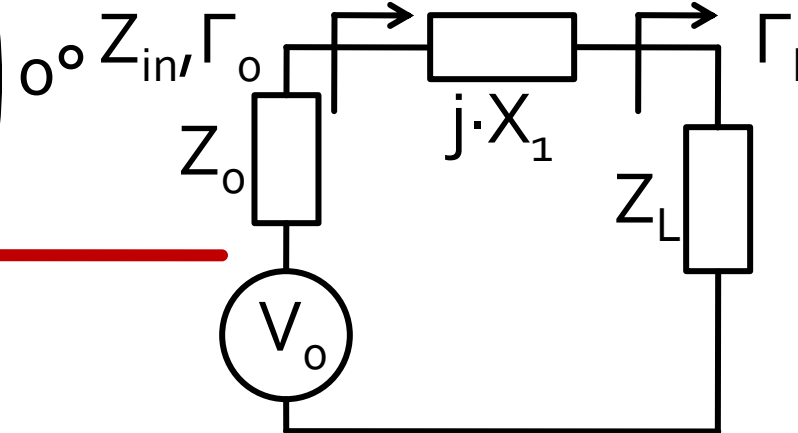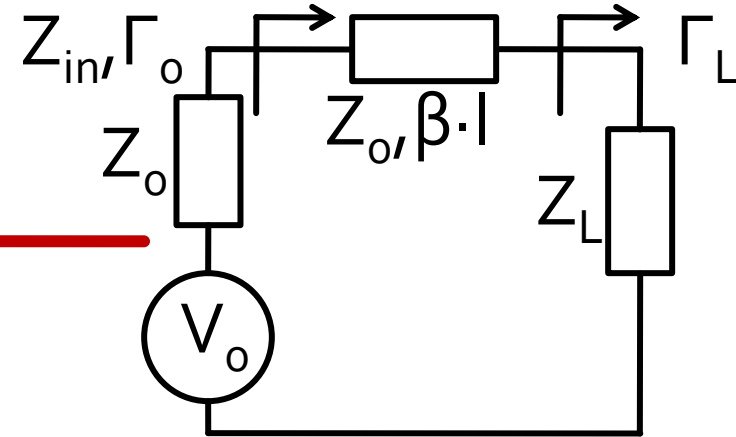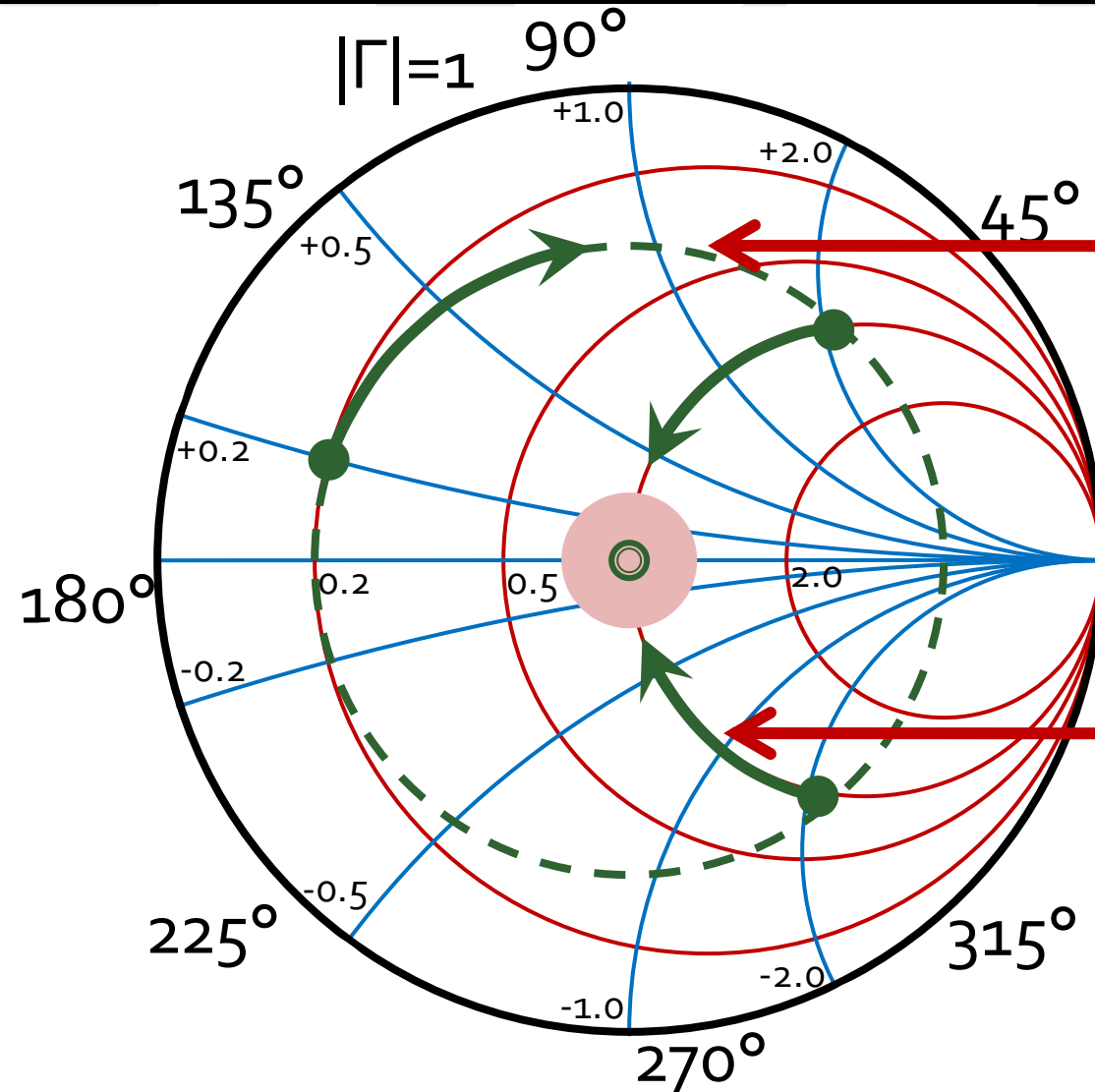

$$|\Gamma_{in}| = |\Gamma_L|$$

$$r_{in} = 1$$

Analytical solution, usage

$$\cos(\varphi + 2\theta) = |\Gamma_s|$$

$$\theta_{ss} = \beta \cdot l = \cot^{-1} \frac{\mp 2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}}$$

$$\Gamma_s = 0.555 \angle -29.92^\circ$$

$$|\Gamma_s| = 0.555; \quad \varphi = -29.92^\circ \quad \cos(\varphi + 2\theta) = 0.555 \Rightarrow (\varphi + 2\theta) = \pm 56.28^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

- **"+" solution** ↓

$$(-29.92^\circ + 2\theta) = +56.28^\circ \quad \theta = 43.1^\circ \quad \text{Im } z_s = \frac{+2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} = +1.335$$

$$\theta_{ss} = -\cot^{-1}(\text{Im } z_s) = -36.8^\circ (+180^\circ) \rightarrow \theta_{ss} = 143.2^\circ$$

- **"-" solution** ↓

$$(-29.92^\circ + 2\theta) = -56.28^\circ \quad \theta = -13.2^\circ (+180^\circ) \rightarrow \theta = 166.8^\circ$$

$$\text{Im } z_s = \frac{-2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} = -1.335 \quad \theta_{ss} = -\cot^{-1}(\text{Im } z_s) = 36.8^\circ$$

Analytical solution, usage

$$(\varphi + 2\theta) = \begin{cases} +56.28^\circ \\ -56.28^\circ \end{cases} \quad \theta = \begin{cases} 43.1^\circ \\ 166.8^\circ \end{cases} \quad \text{Im}[z_s(\theta)] = \begin{cases} +1.335 \\ -1.335 \end{cases} \quad \theta_{ss} = \begin{cases} -36.8^\circ + 180^\circ = 143.2^\circ \\ +36.8^\circ \end{cases}$$

- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

$$l_1 = \frac{43.1^\circ}{360^\circ} \cdot \lambda = 0.120 \cdot \lambda$$

$$l_2 = \frac{143.2^\circ}{360^\circ} \cdot \lambda = 0.398 \cdot \lambda$$

$$l_1 = \frac{166.8^\circ}{360^\circ} \cdot \lambda = 0.463 \cdot \lambda$$

$$l_2 = \frac{36.8^\circ}{360^\circ} \cdot \lambda = 0.102 \cdot \lambda$$



Stub, observations

- adding or subtracting **180°** ($\lambda/2$) doesn't change the result (full rotation around the Smith Chart)

$$E = \beta \cdot l = \pi = 180^\circ \quad l = k \cdot \frac{\lambda}{2}, \forall k \in \mathbf{N}$$

- if the lines/stubs result with **negative** "length"/ "electrical length" we add $\lambda/2$ / 180° to obtain physically realizable lines
- adding or subtracting **90°** ($\lambda/4$) change the stub impedance:


$$Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l \quad \Leftrightarrow \quad Z_{in,g} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$

- for the stub we can add or subtract 90° ($\lambda/4$) while in the same time changing **open-circuit** \Leftrightarrow **short-circuit**

Microwave Amplifiers

Power / Matching

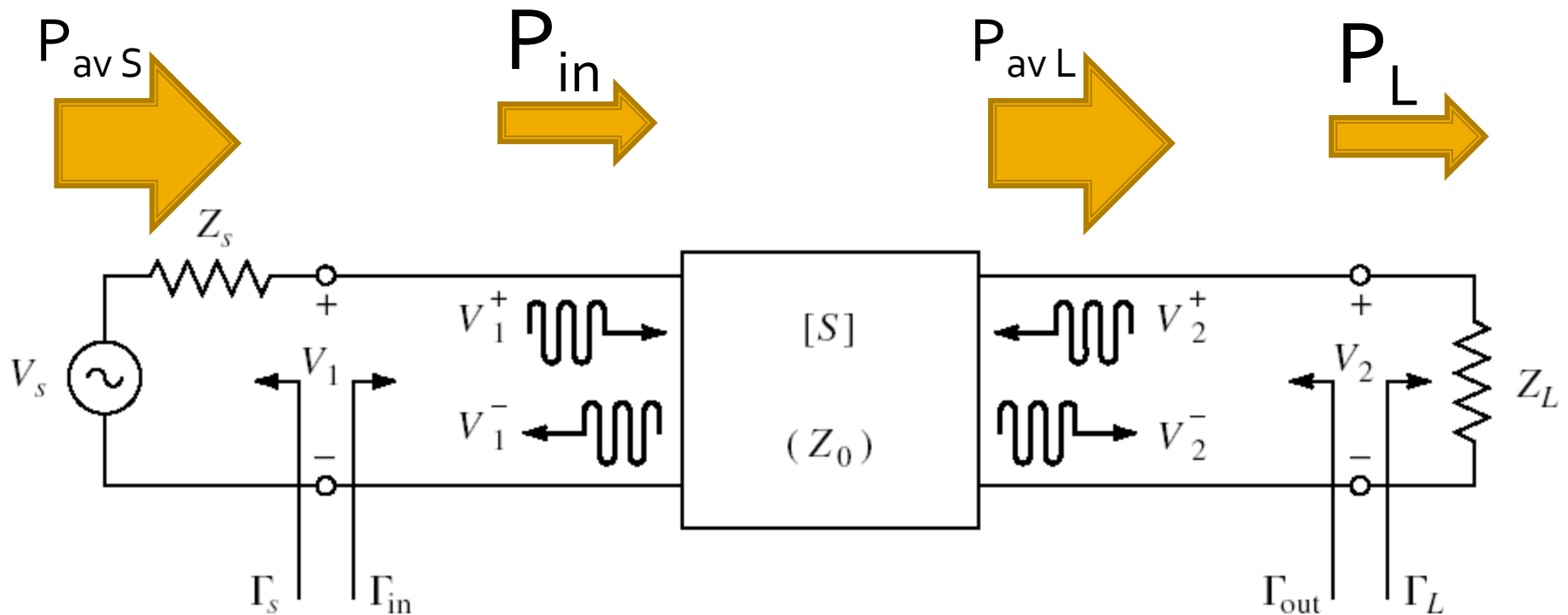- Two ports in which matching influences the power transfer



Two-Port Power Gains

- **Available** power gain

$$G_A = \frac{P_{av L}}{P_{av S}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2)}{|1 - S_{22} \cdot \Gamma_L|^2 \cdot (1 - |\Gamma_{out}|^2)}$$

- **Transducer** power gain

$$G_T = \frac{P_L}{P_{av S}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2}$$

$$\Gamma_{in} = \Gamma_{in}(\Gamma_L)$$

- **Unilateral transducer** power gain


$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$S_{12} \cong 0$$

$$\Gamma_{in} = S_{11}$$


Input and output can be treated independently

Amplifier as two-port

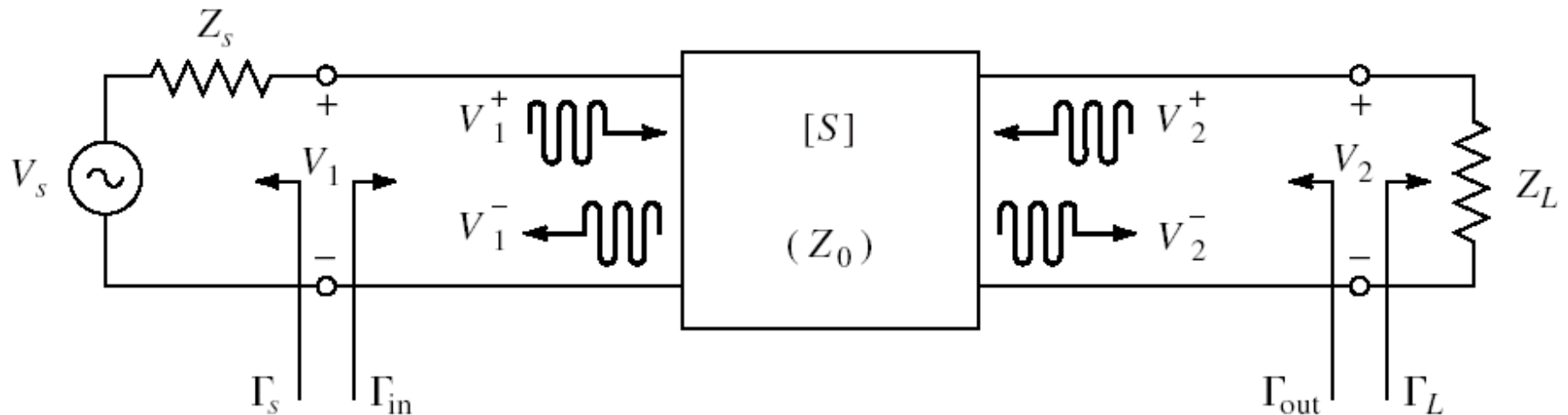


- For an amplifier two-port we are interested in:
 - **stability**
 - power gain
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)

Amplifier as two-port

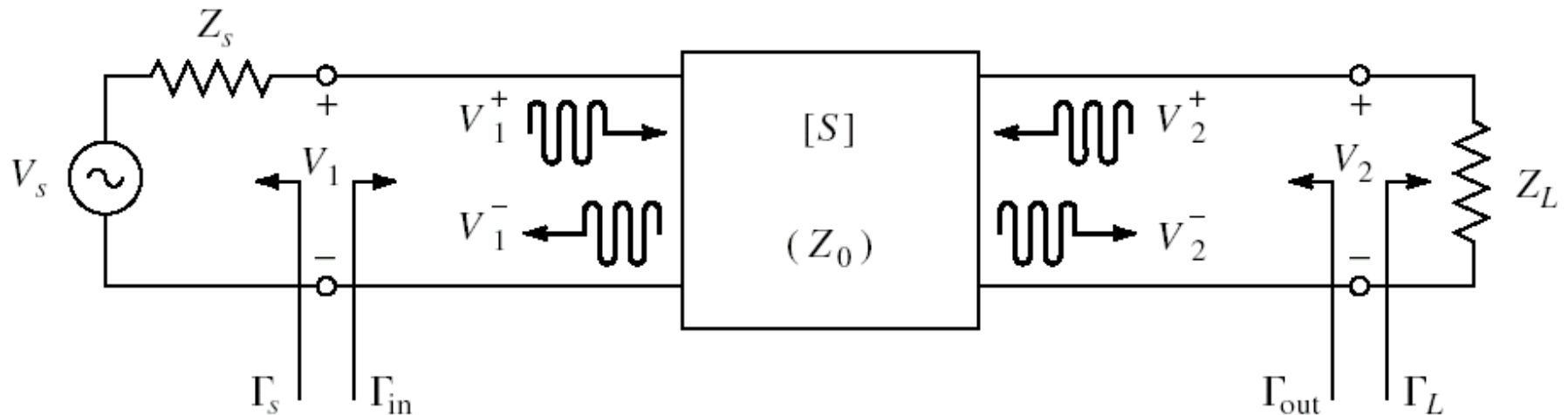

- For an amplifier two-port we are interested in:
 - stability
 - **power gain**
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)

Amplifier as two-port

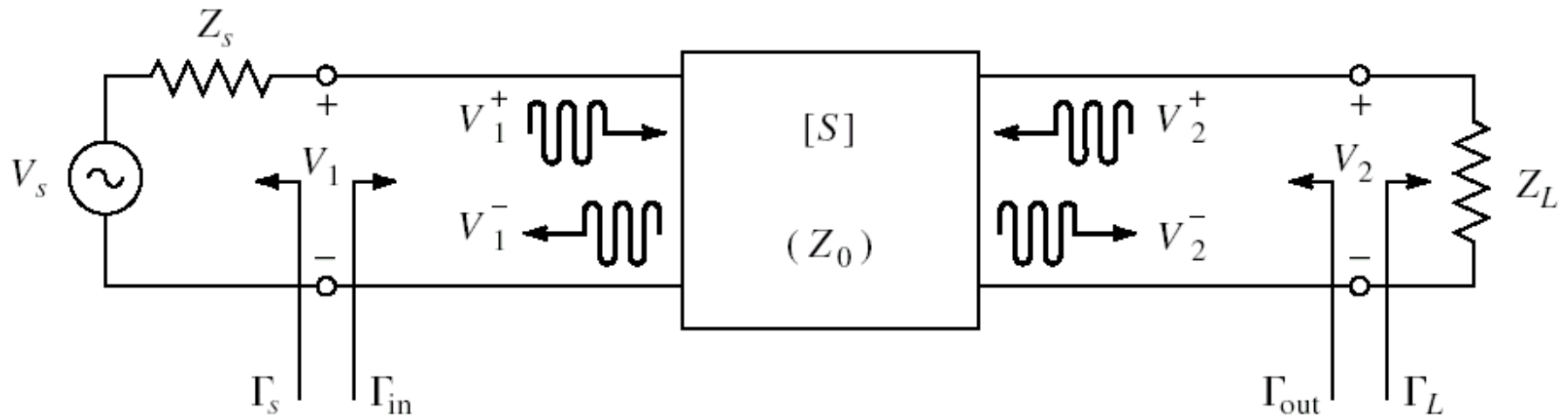

- For an amplifier two-port we are interested in:
 - stability
 - power gain
 - **noise** (sometimes – **small signals**)
 - linearity (sometimes – large signals)

Microwave Filters

Filter synthesis

- Filter is designed with lumped elements (L/C) followed by implementation with distributed elements (transmission lines)
 - general
 - analytical relationships easy to implement on the computer
 - efficient
- The preferred procedure is **insertion loss method**

Insertion loss method

$$P_{LR} = \frac{P_S}{P_L} = \frac{1}{1 - |\Gamma(\omega)|^2}$$

- $|\Gamma(\omega)|^2$ is an even function of ω

$$|\Gamma(\omega)|^2 = \frac{M(\omega^2)}{M(\omega^2) + N(\omega^2)}$$

$$P_{LR} = 1 + \frac{M(\omega^2)}{N(\omega^2)}$$

- Choosing M and N polynomials appropriately leads to a filter with a completely specified frequency response

Insertion loss method

- We control the power loss ratio/attenuation introduced by the filter:
 - in the passband (pass all frequencies)
 - in the stopband (reject all frequencies)


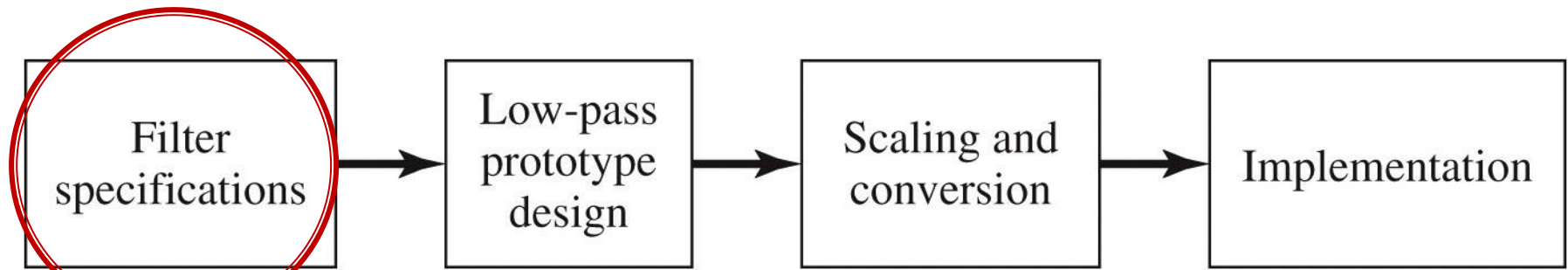


Figure 8.23

Filter specifications

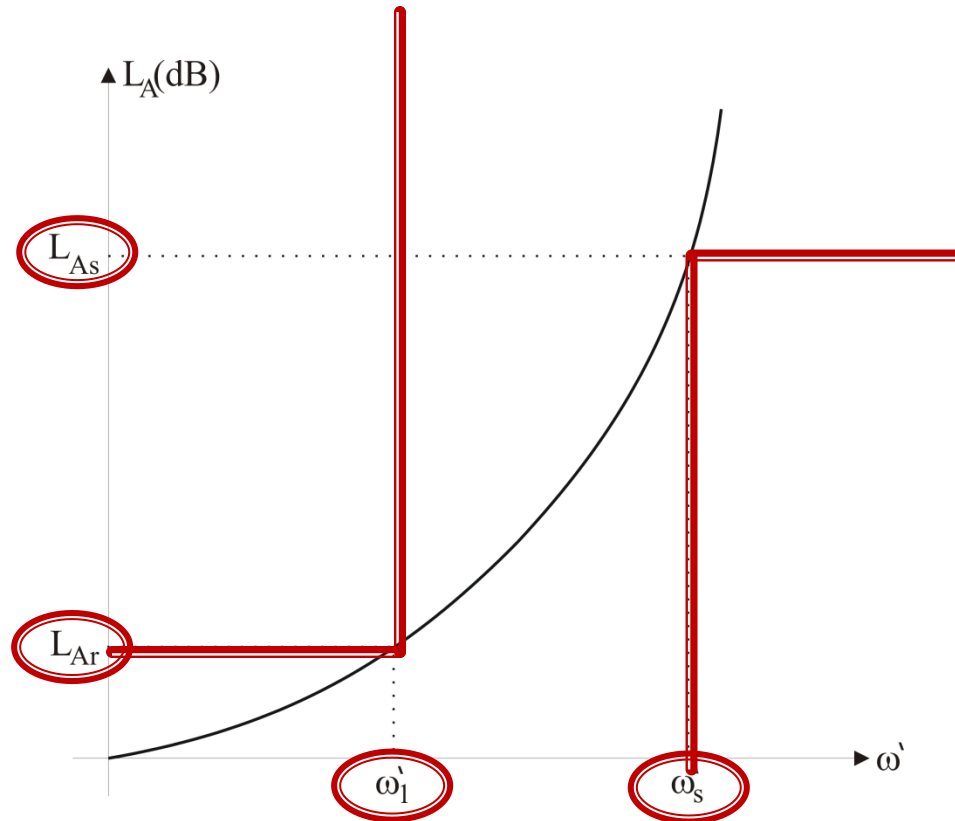- Attenuation
 - in passband
 - in stopband
 - most often in **dB**
- Frequency range
 - passband
 - stopband
 - cutoff frequency ω_1'
usually normalized
(= **1**)



Insertion loss method

- We choose the right polynomials to design an **low-pass** filter (prototype)
- The low-pass prototype are then converted to the desired other types of filters
 - low-pass, high-pass, bandpass, or bandstop

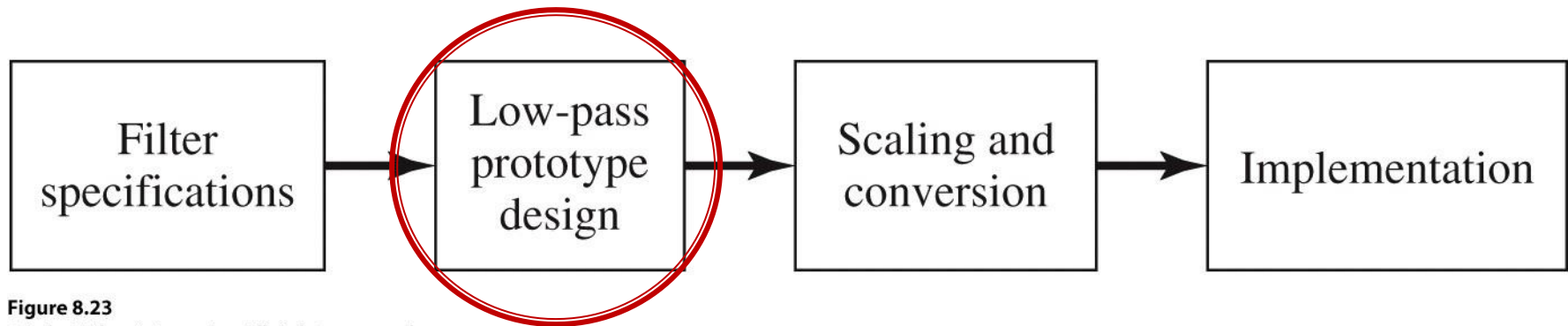


Figure 8.23
© John Wiley & Sons, Inc. All rights reserved.

Maximally Flat/Equal ripple LPF Prototype


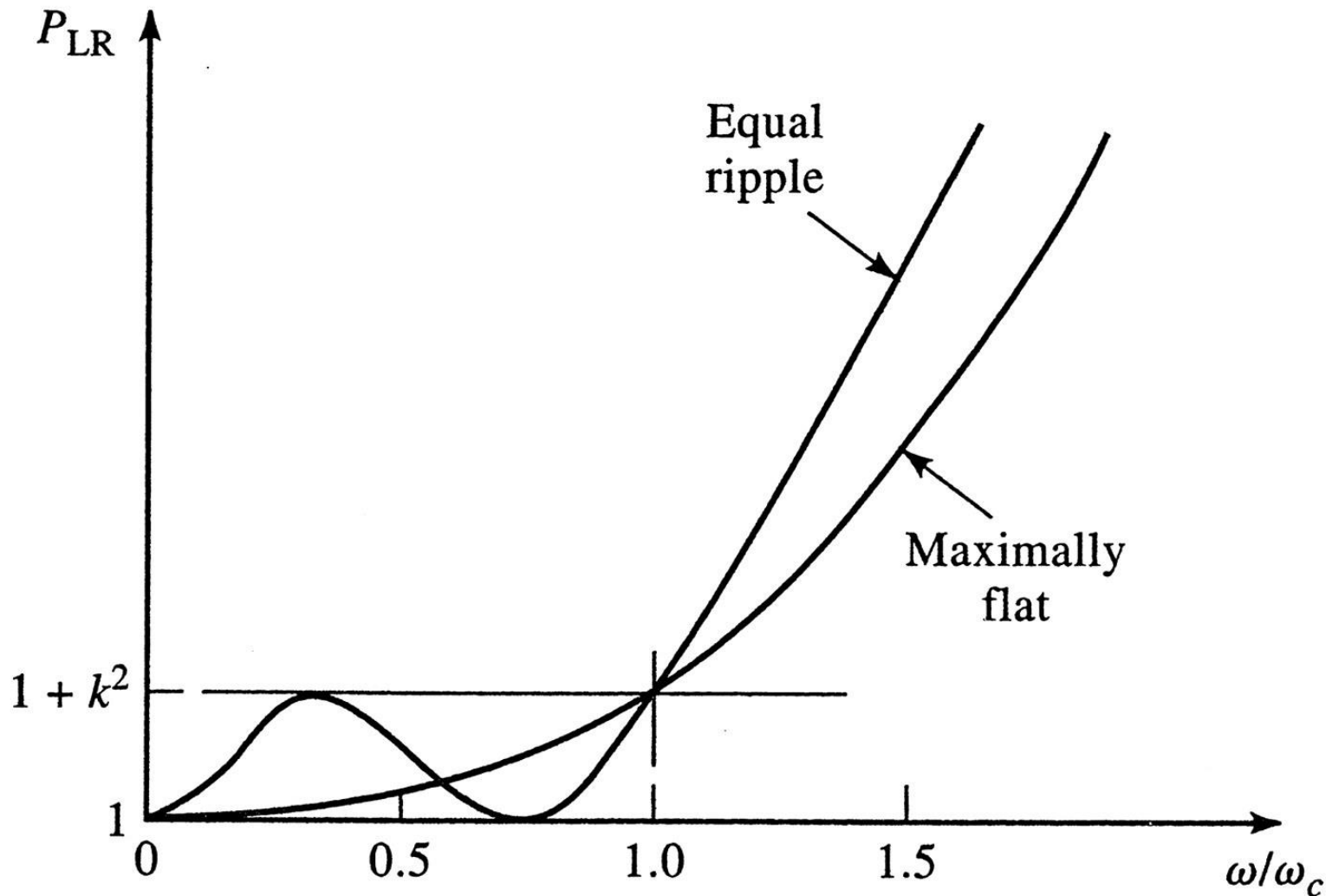



Figure 8.21
© John Wiley & Sons, Inc. All rights reserved.

Maximally flat filter prototypes

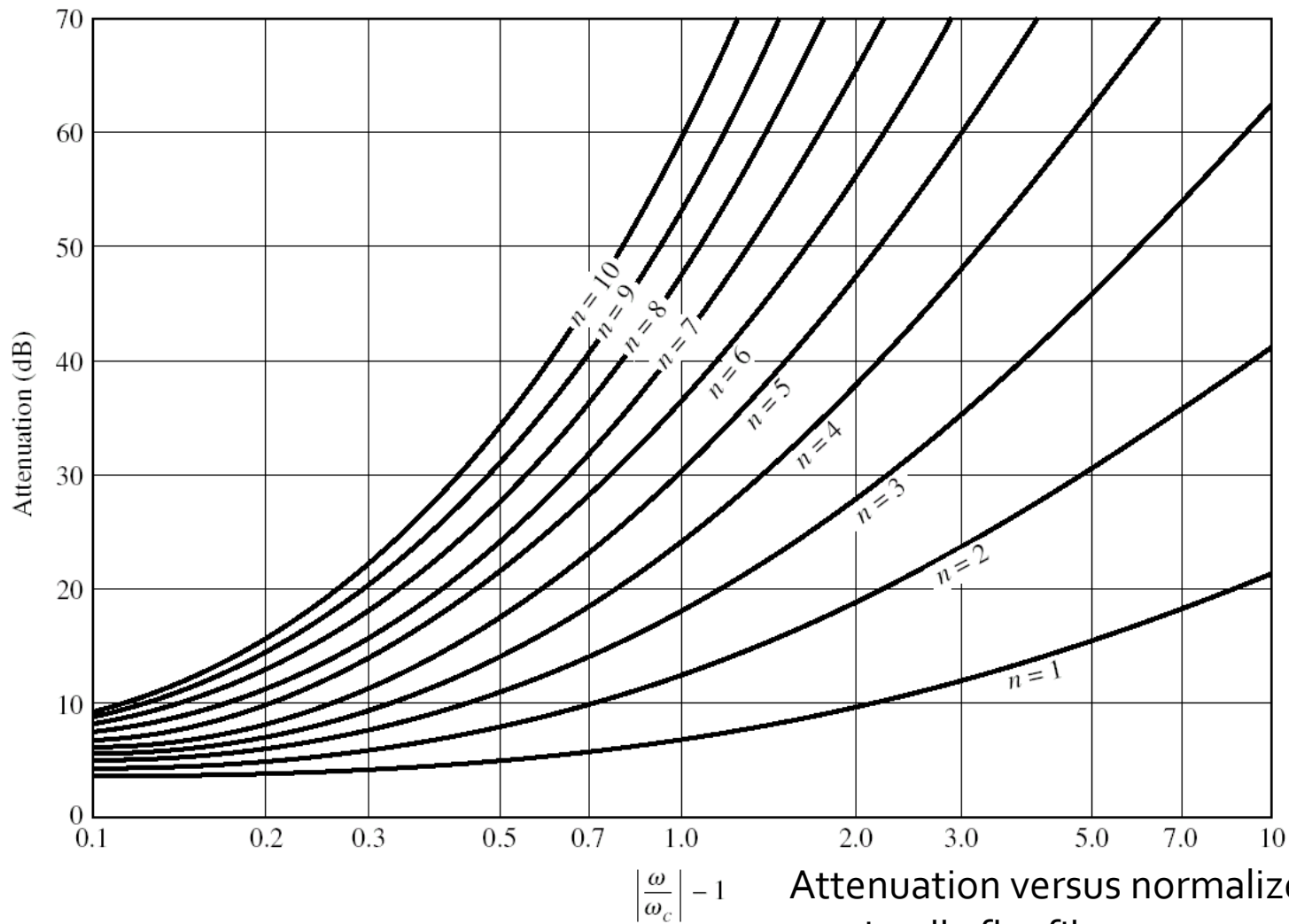


Attenuation versus normalized frequency for maximally flat filter prototypes

Prototype Filters

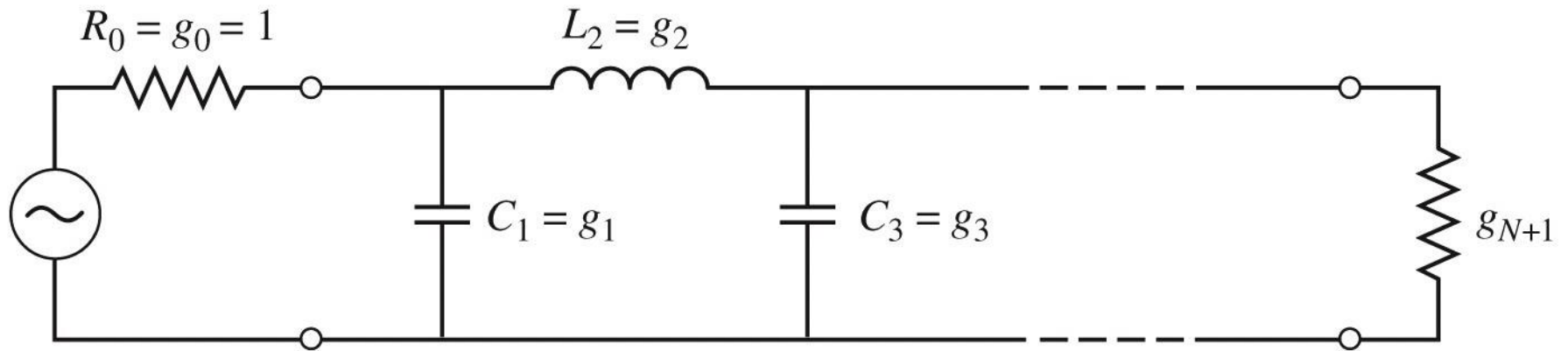

(a)

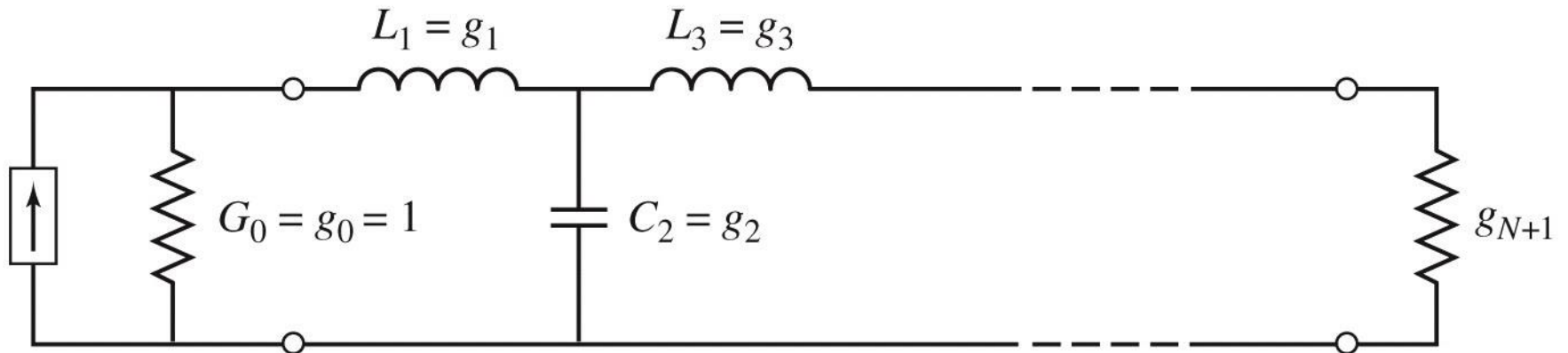

(b)

Maximally Flat LPF Prototype

- Formulas for filter parameters

$$g_0 = 1$$

$$g_k = 2 \cdot \sin \left[\frac{(2 \cdot k - 1) \cdot \pi}{2 \cdot N} \right], \quad k = 1, N$$

$$g_{N+1} = 1$$

Maximally Flat LPF Prototype

TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ($g_0 = 1$, $\omega_c = 1$, $N = 1$ to 10)

N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

Continue

LPF Prototype


- 0.5dB equal-ripple table or design formulas:

- $g_1 = 1.5963 = L_1/C_3,$

- $g_2 = 1.0967 = C_2/L_4,$



- $g_3 = 1.5963 = L_3/C_5,$

- $g_4 = 1.000 = R_L$

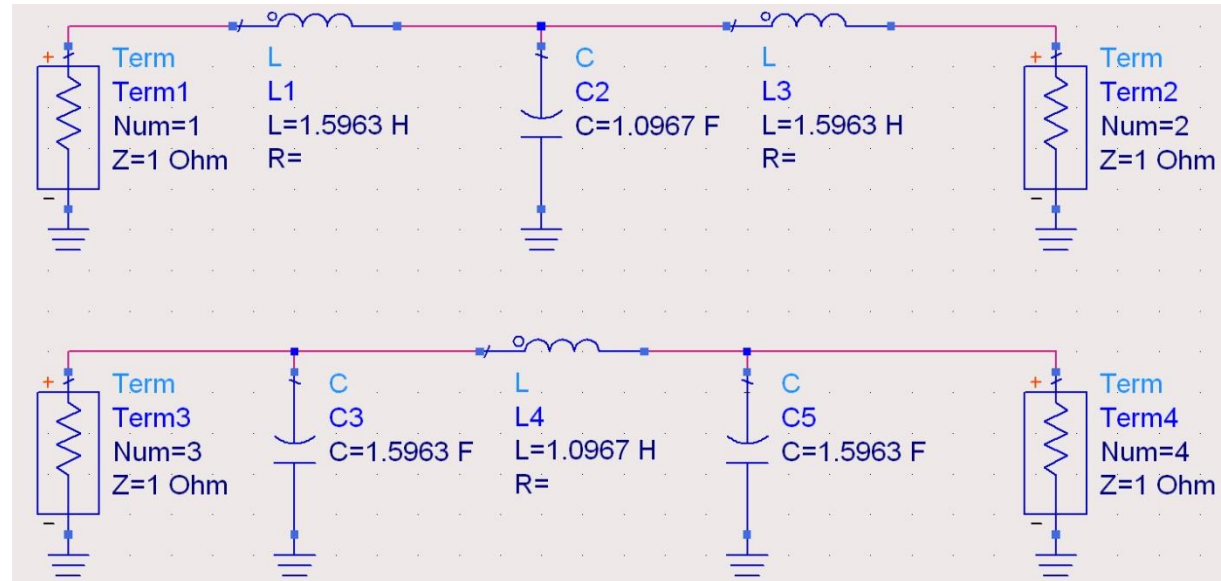

LPF Prototype

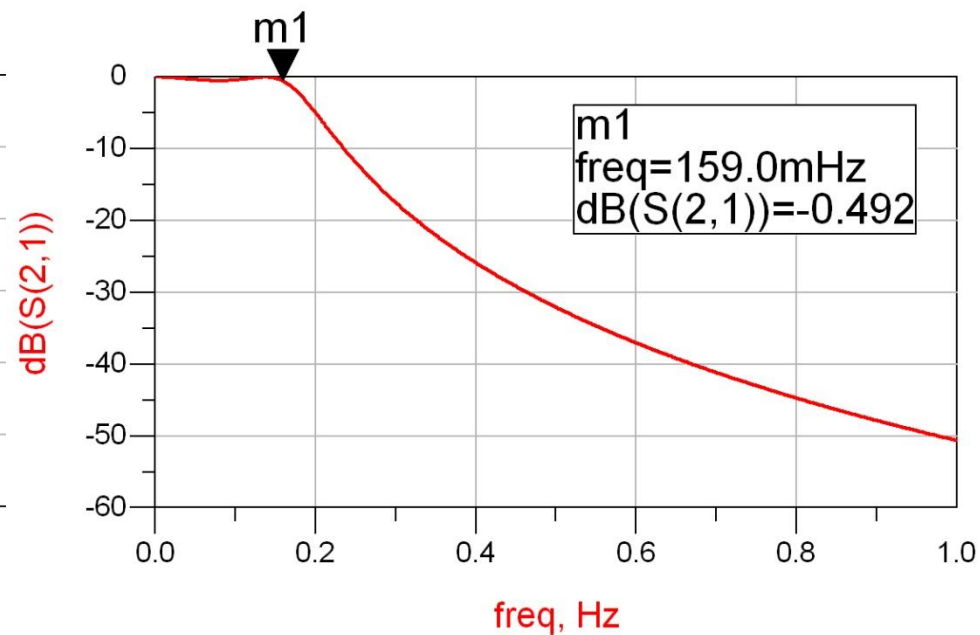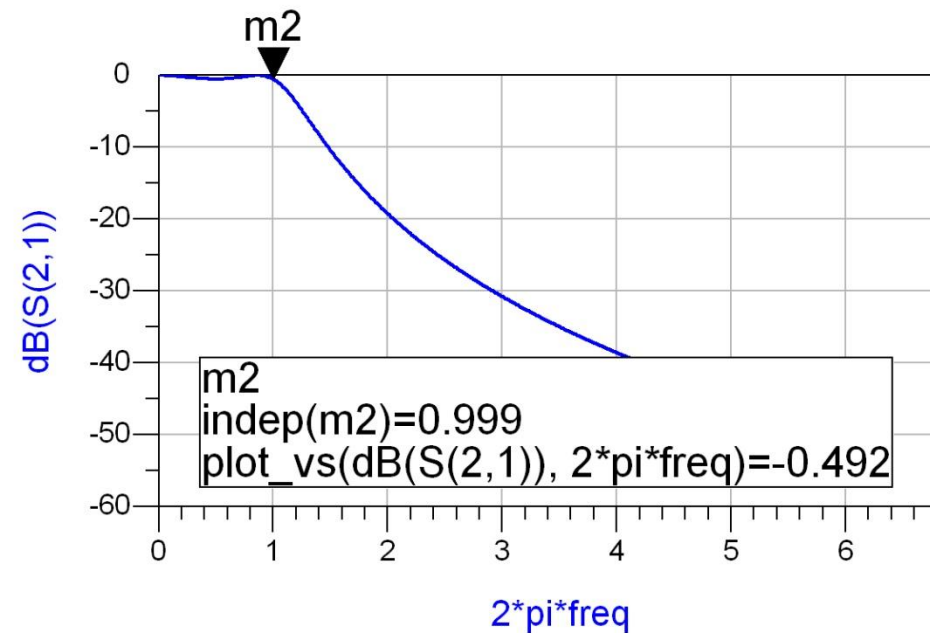- $\omega_o = 1 \text{ rad/s}$ ($f_o = \omega_o / 2\pi = 0.159 \text{ Hz}$)



Impedance and Frequency Scaling

- After computing prototype filter's elements:
 - Low-Pass Filters (**LPF**)
 - cutoff frequency **$\omega_o = 1 \text{ rad/s}$** ($f_o = 0.159 \text{ Hz}$)
 - connected to a source with **$R = 1\Omega$**
- component values can be scaled in terms of impedance and frequency

Impedance and Frequency Scaling

- LPF Prototype is only used as an intermediate step
 - Low-Pass Filter (LPF)
 - cutoff frequency $\omega_o = 1 \text{ rad/s}$ ($f_o = 0.159 \text{ Hz}$)
 - connected to a source with $R = 1\Omega$

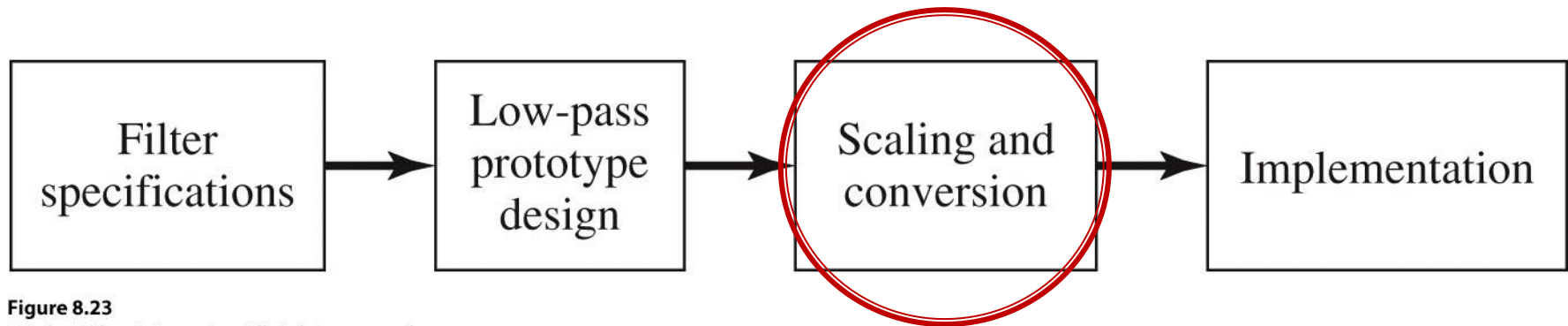


Figure 8.23

Impedance Scaling

- To design a filter which will work with a source resistance of R_0 we multiply all the impedances of the prototype design by R_0 (" $'$ " denotes scaled values)

$$R'_s = R_0 \cdot (R_s = 1)$$


$$R'_L = R_0 \cdot R_L$$

$$L' = R_0 \cdot L$$

$$C' = \frac{C}{R_0}$$


Frequency Scaling

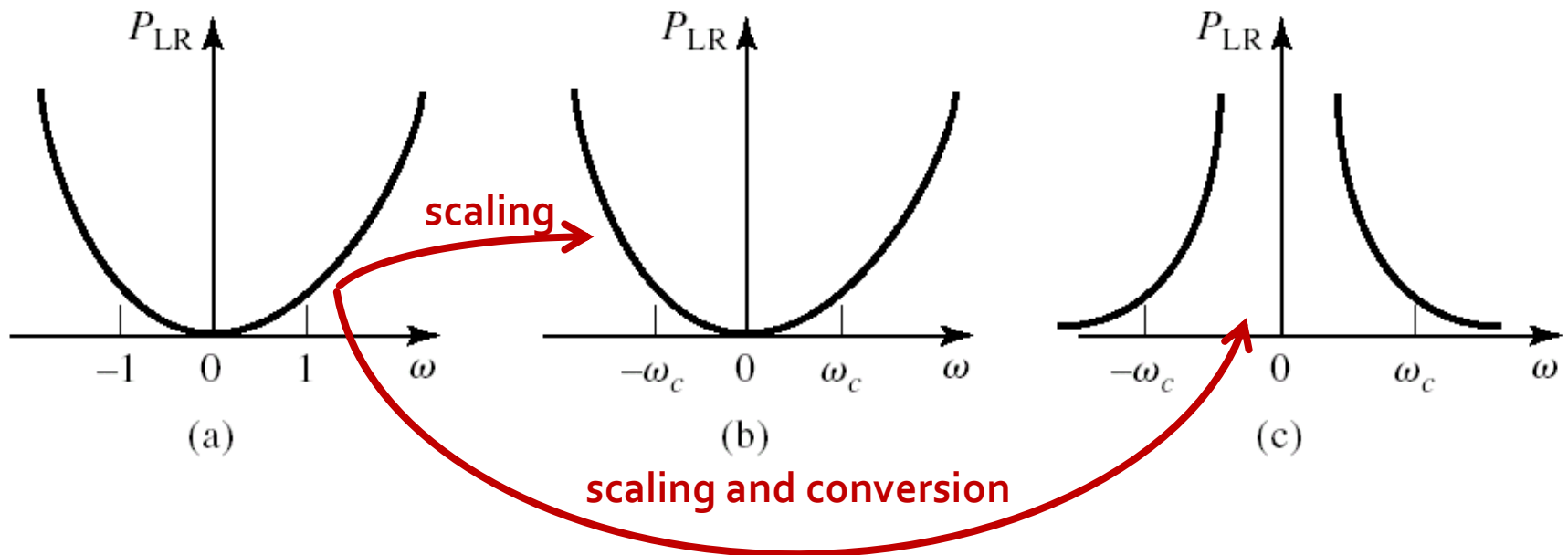- changing the cutoff frequency – (fig. b)
- changing the type (for example LPF \rightarrow HPF – fig. c) requires also conversion



Frequency Scaling

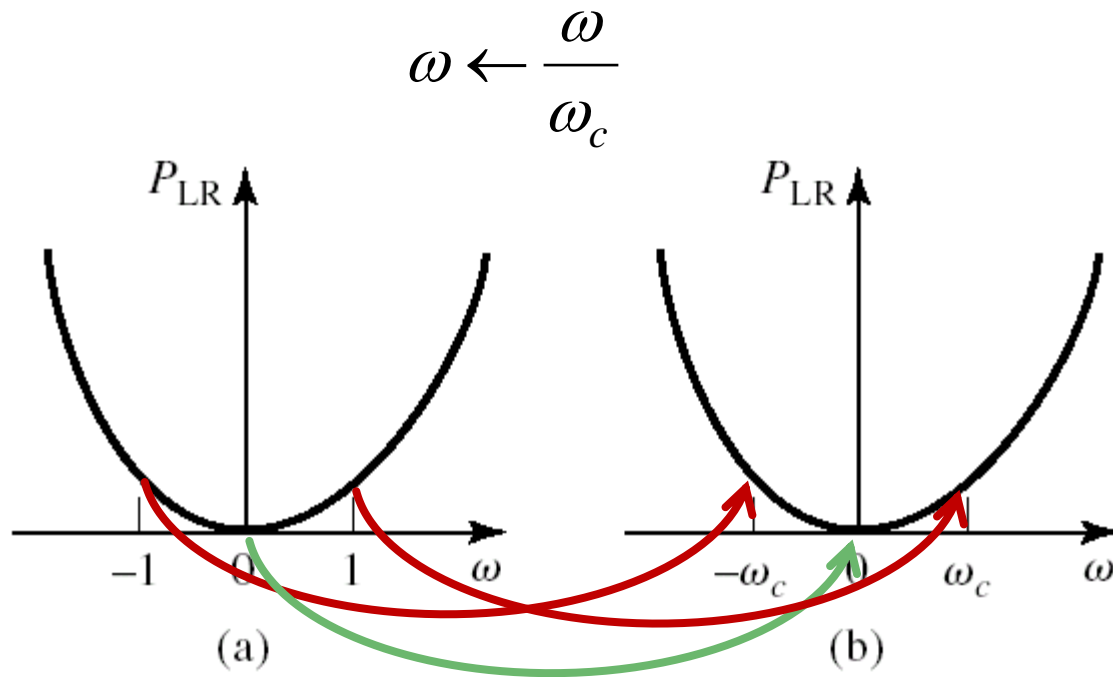- To change the cutoff frequency of a low-pass prototype from unity to ω_c we apply a variable substitution



Frequency Scaling

- To change the cutoff frequency of a low-pass prototype we apply a variable substitution:

$$\omega \leftarrow \frac{\omega}{\omega_c}$$

- Equivalent to the widening of the power loss filter response

$$P'_{LR}(\omega) = P_{LR}\left(\frac{\omega}{\omega_c}\right)$$

$$j \cdot X_k = j \cdot \frac{\omega}{\omega_c} \cdot L_k = j \cdot \omega \cdot L'_k$$

$$j \cdot B_k = j \cdot \frac{\omega}{\omega_c} \cdot C_k = j \cdot \omega \cdot C'_k$$

Frequency Scaling LPF \rightarrow LPF

- New element values for frequency scaling:

$$L'_k = \frac{L_k}{\omega_c} \quad C'_k = \frac{C_k}{\omega_c}$$


- When both impedance and frequency scaling are required:

$$L'_k = \frac{R_0 \cdot L_k}{\omega_c} \quad C'_k = \frac{C_k}{R_0 \cdot \omega_c}$$

Low-pass to high-pass transformation LPF \rightarrow HPF

- Variable substitution for LPF \rightarrow HPF:
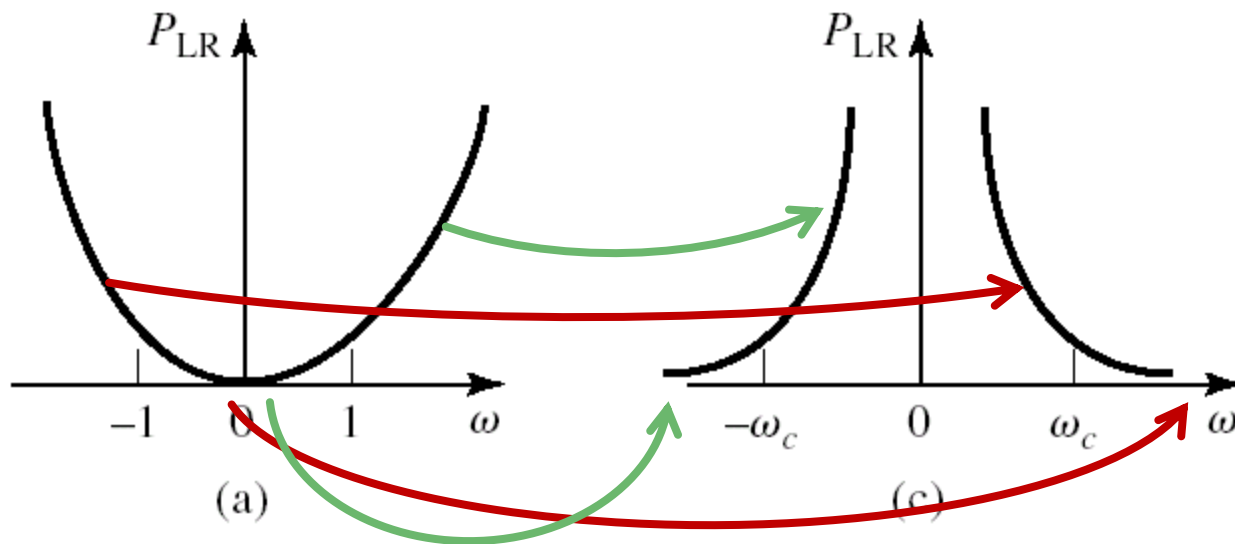
$$\omega \leftarrow -\frac{\omega_c}{\omega}$$



High-pass transformation LPF \rightarrow HPF

- Variable substitution for LPF \rightarrow HPF :

$$\omega \leftarrow -\frac{\omega_c}{\omega}$$
$$j \cdot X_k = -j \cdot \frac{\omega_c}{\omega} \cdot L_k = \frac{1}{j \cdot \omega \cdot C'_k} \quad j \cdot B_k = -j \cdot \frac{\omega_c}{\omega} \cdot C_k = \frac{1}{j \cdot \omega \cdot L'_k}$$

- Impedance scaling can be included

$$C'_k = \frac{1}{R_0 \cdot \omega_c \cdot L_k} \quad L'_k = \frac{R_0}{\omega_c \cdot C_k}$$

- In the schematic series **inductors** must be replaced with series **capacitors**, and shunt **capacitors** must be replaced with shunt **inductors**

Bandpass Transformation LPF \rightarrow BPF

- Variable substitution for LPF \rightarrow BPF:

$$\omega \leftarrow \frac{\omega_0}{\omega_2 - \omega_1} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)$$

- where we use the fractional bandwidth of the passband and the center frequency

$$\Delta = \frac{\omega_2 - \omega_1}{\omega_0} \qquad \omega_0 = \sqrt{\omega_1 \cdot \omega_2}$$


Bandpass Transformation LPF \rightarrow BPF

$$\omega = \omega_0 \rightarrow \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega_0}{\omega_0} - \frac{\omega_0}{\omega_0} \right) = 0$$

$$\omega = -\omega_0 \rightarrow \frac{1}{\Delta} \left(\frac{-\omega_0}{\omega_0} - \frac{\omega_0}{-\omega_0} \right) = 0$$

$$\omega = \omega_1 \rightarrow \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega_1^2 - \omega_0^2}{\omega_0 \cdot \omega_1} \right) = -1$$
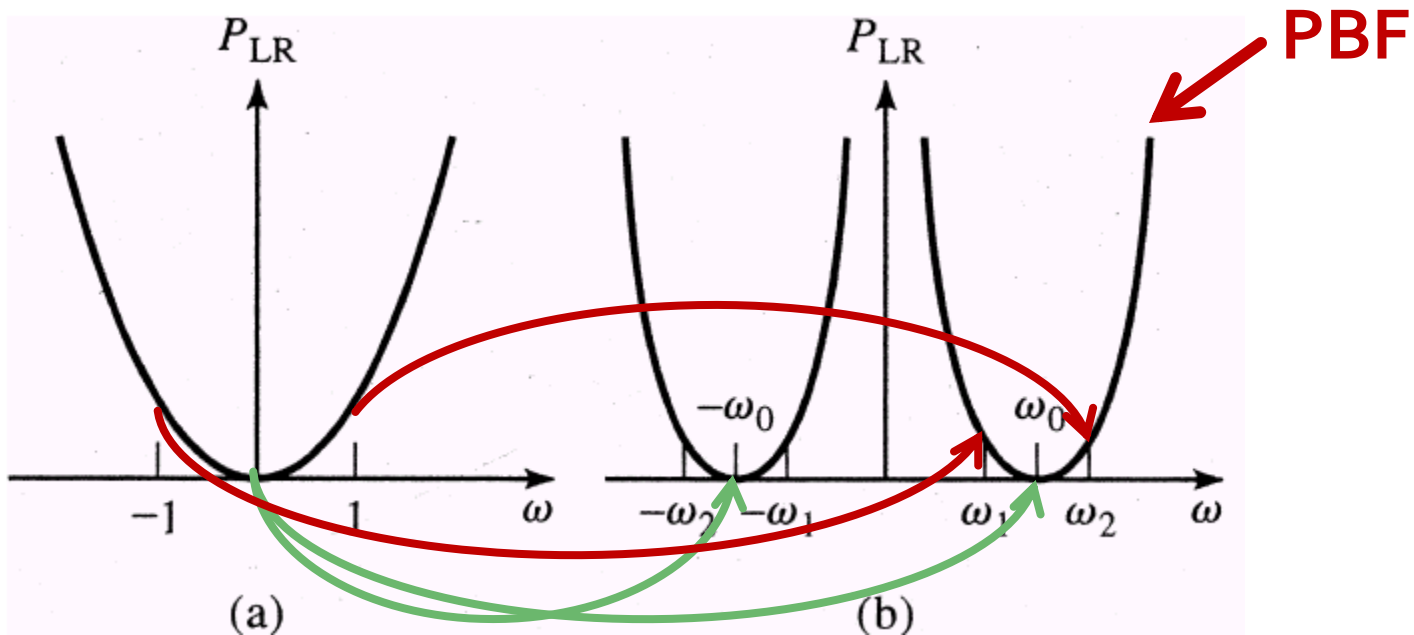
$$\omega = \omega_2 \rightarrow \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega_2^2 - \omega_0^2}{\omega_0 \cdot \omega_2} \right) = 1$$



Bandpass Transformation LPF \rightarrow BPF

$$j \cdot X_k = \frac{j}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \cdot L_k = j \cdot \frac{\omega \cdot L_k}{\Delta \cdot \omega_0} - j \cdot \frac{\omega_0 \cdot L_k}{\Delta \cdot \omega} = j \cdot \omega \cdot L'_k - j \frac{1}{\omega \cdot C'_k}$$
$$j \cdot B_k = \frac{j}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \cdot C_k = j \cdot \frac{\omega \cdot C_k}{\Delta \cdot \omega_0} - j \cdot \frac{\omega_0 \cdot C_k}{\Delta \cdot \omega} = j \cdot \omega \cdot C'_k - j \frac{1}{\omega \cdot L'_k}$$

- A series **inductor** in the prototype filter is transformed to a **series LC circuit in series**



$$L'_k = \frac{L_k}{\Delta \cdot \omega_0} \quad C'_k = \frac{\Delta}{\omega_0 \cdot L_k}$$

- A shunt **capacitor** in the prototype filter is transformed to a **shunt LC circuit in parallel**

$$L'_k = \frac{\Delta}{C_k \cdot \omega_0} \quad C'_k = \frac{C_k}{\omega_0 \cdot \Delta}$$

Bandstop Transformation LPF \rightarrow BSF
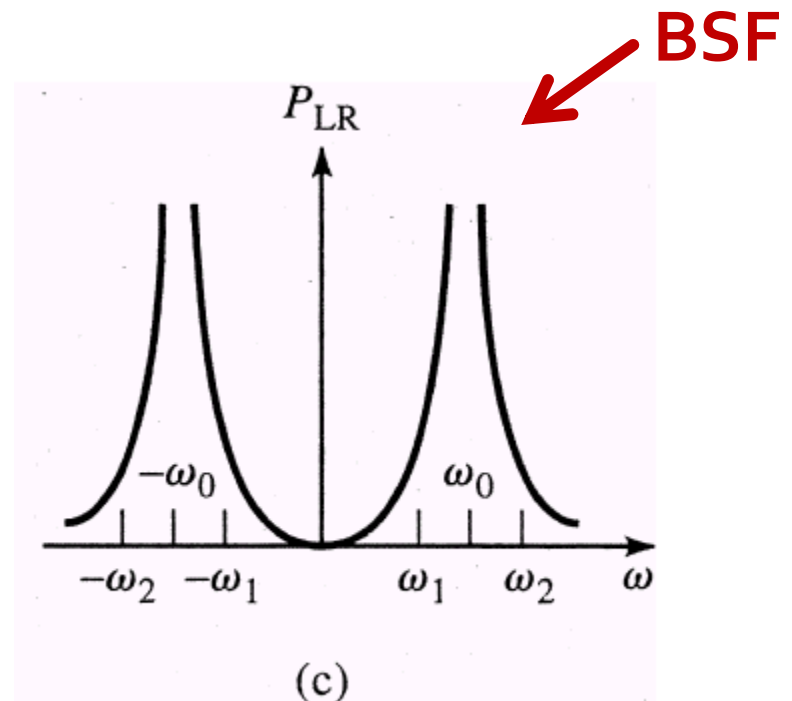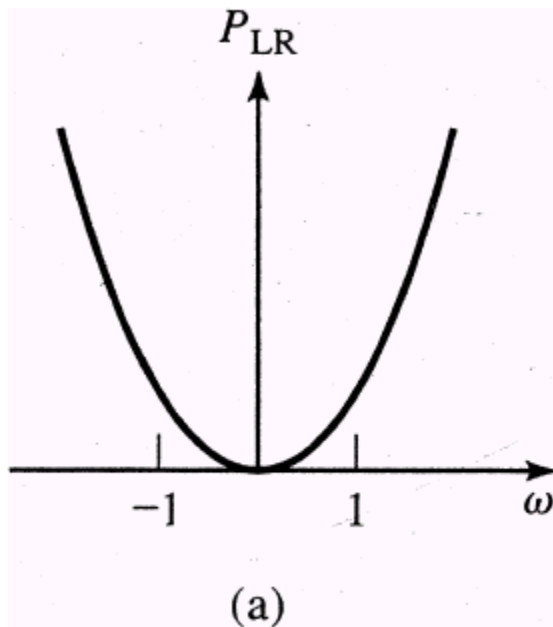
$$\omega \leftarrow -\Delta \cdot \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^{-1} \quad \omega = \omega_0 \rightarrow \frac{-\Delta}{\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)} = \frac{-\Delta}{\left(\frac{\omega_0}{\omega_0} - \frac{\omega_0}{\omega_0} \right)} \rightarrow \pm\infty$$



Bandstop Transformation LPF \rightarrow BSF

$$\omega \leftarrow -\Delta \cdot \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^{-1}$$


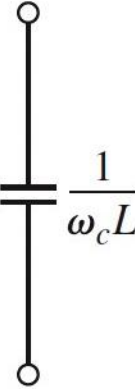
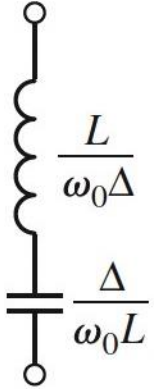
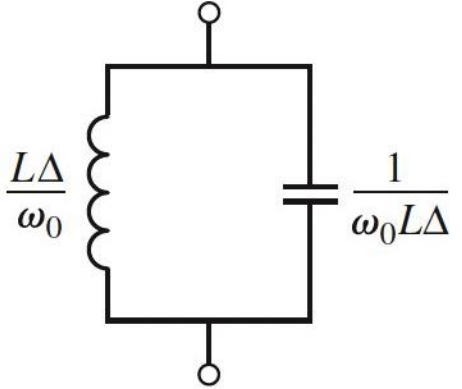
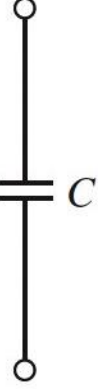
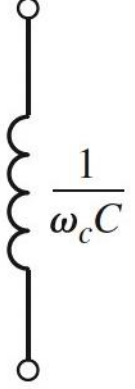
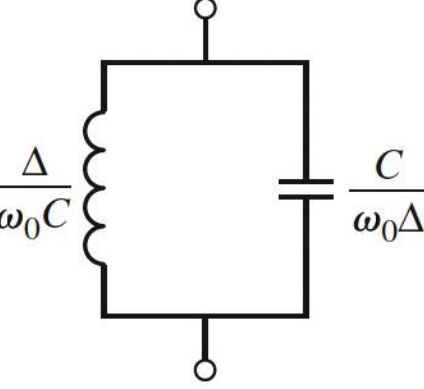
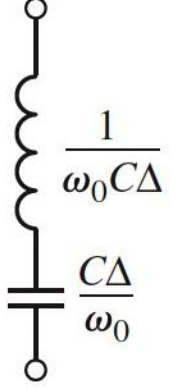
- A series **inductor** in the prototype filter is transformed to a **shunt LC circuit in series**

$$L'_k = \frac{\Delta \cdot L_k}{\omega_0} \quad C'_k = \frac{1}{\omega_0 \cdot \Delta \cdot L_k}$$

- A shunt **capacitor** in the prototype filter is transformed to a **series LC circuit in parallel**

$$L'_k = \frac{1}{\Delta \cdot \omega_0 \cdot C_k} \quad C'_k = \frac{\Delta \cdot C_k}{\omega_0}$$

Summary of Prototype Filter Transformations

Low-pass	High-pass	Bandpass	Bandstop
 <p style="text-align: center;">L</p>	 <p style="text-align: center;">$\frac{1}{\omega_c L}$</p>	 <p style="text-align: center;">$\frac{L}{\omega_0 \Delta}$ $\frac{\Delta}{\omega_0 L}$</p>	 <p style="text-align: center;">$\frac{L\Delta}{\omega_0}$ $\frac{1}{\omega_0 L\Delta}$</p>
 <p style="text-align: center;">C</p>	 <p style="text-align: center;">$\frac{1}{\omega_c C}$</p>	 <p style="text-align: center;">$\frac{\Delta}{\omega_0 C}$ $\frac{C}{\omega_0 \Delta}$</p>	 <p style="text-align: center;">$\frac{1}{\omega_0 C\Delta}$ $\frac{C\Delta}{\omega_0}$</p>

Example

- Design a 3rd order **bandpass** filter with 0.5 dB ripples in passband. The **center frequency** of the filter should be 1 GHz. The **fractional bandwidth** of the passband should be 10%, and the **impedance** 50Ω.

$$\omega_0 = 2 \cdot \pi \cdot 1 \text{ GHz} = 6.283 \cdot 10^9 \text{ rad / s}$$

$$\Delta = 0.1$$

LPF Prototype


- 0.5dB equal-ripple table or design formulas:

- $g_1 = 1.5963 = L_1/C_3,$

- $g_2 = 1.0967 = C_2/L_4,$



- $g_3 = 1.5963 = L_3/C_5,$

- $g_4 = 1.000 = R_L$

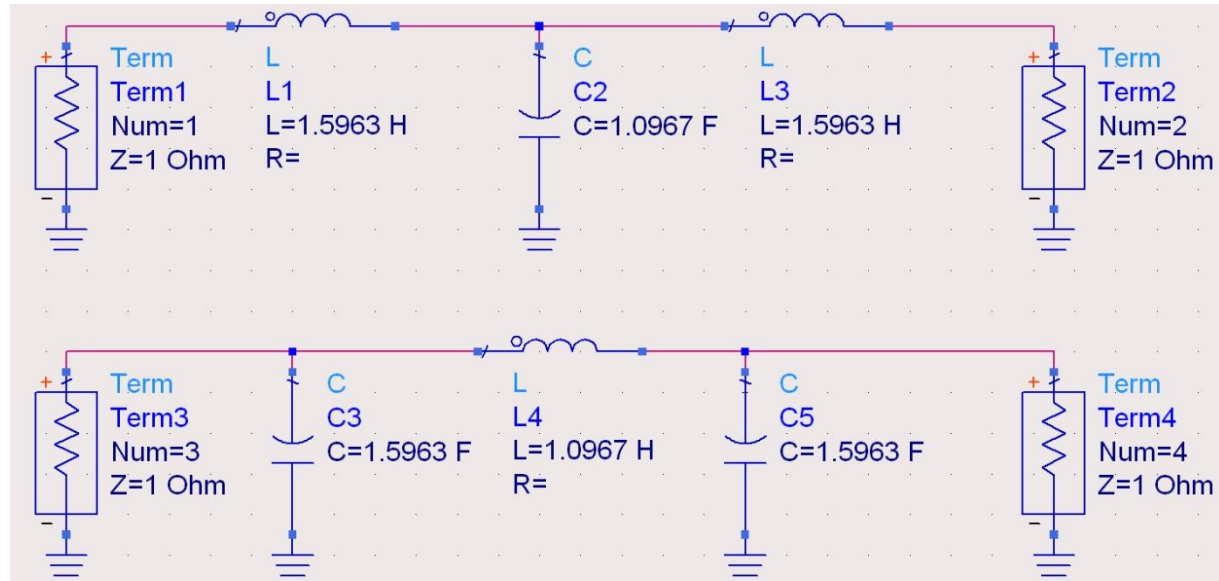

LPF Prototype

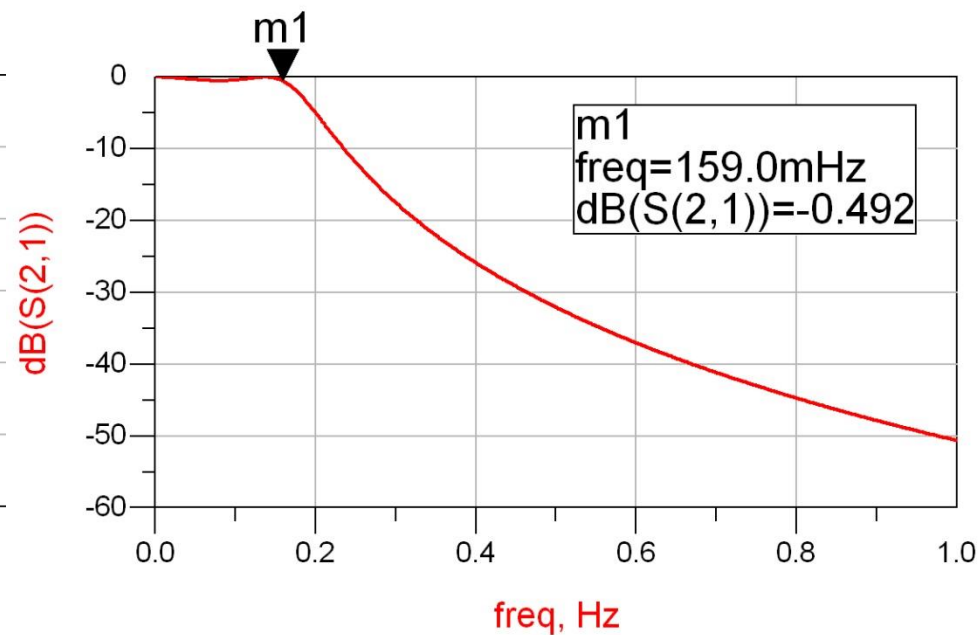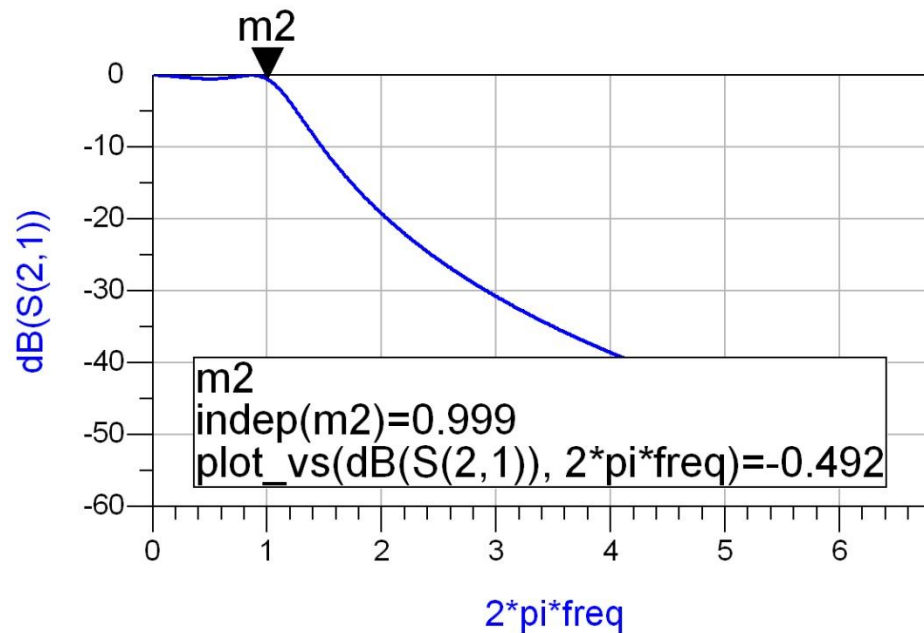- $\omega_o = 1 \text{ rad/s}$ ($f_o = \omega_o / 2\pi = 0.159 \text{ Hz}$)



Bandpass Transformation / BPF

$$\omega_0 = 2 \cdot \pi \cdot 1 \text{GHz} = 6.283 \cdot 10^9 \text{ rad/s} \quad \Delta = \frac{\Delta\omega}{\omega_0} = \frac{\Delta f}{f_0} = 0.1 \quad R_0 = 50 \Omega$$

$$g_1 = 1.5963 = L_1,$$

$$g_3 = 1.5963 = L_3,$$

$$g_2 = 1.0967 = C_2,$$

$$g_4 = 1.000 = R_L$$

$$L'_1 = \frac{L_1 \cdot R_0}{\Delta \cdot \omega_0} = 127.0 \text{ nH}$$

$$C'_1 = \frac{\Delta}{\omega_0 \cdot L_1 \cdot R_0} = 0.199 \text{ pF}$$



$$L'_2 = \frac{\Delta \cdot R_0}{\omega_0 \cdot C_2} = 0.726 \text{ nH}$$

$$C'_2 = \frac{C_2}{\Delta \cdot \omega_0 \cdot R_0} = 34.91 \text{ pF}$$

$$L'_3 = \frac{L_3 \cdot R_0}{\Delta \cdot \omega_0} = 127.0 \text{ nH}$$

$$C'_3 = \frac{\Delta}{\omega_0 \cdot L_3 \cdot R_0} = 0.199 \text{ pF}$$

ADS

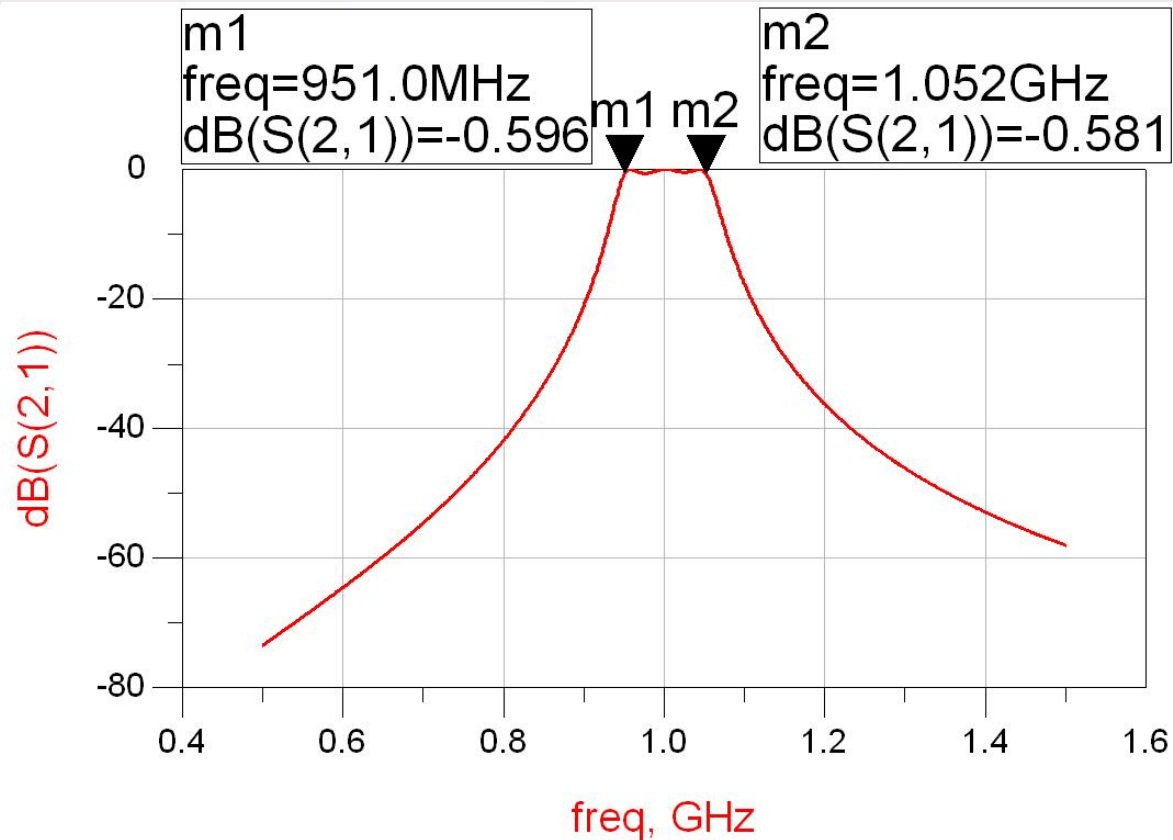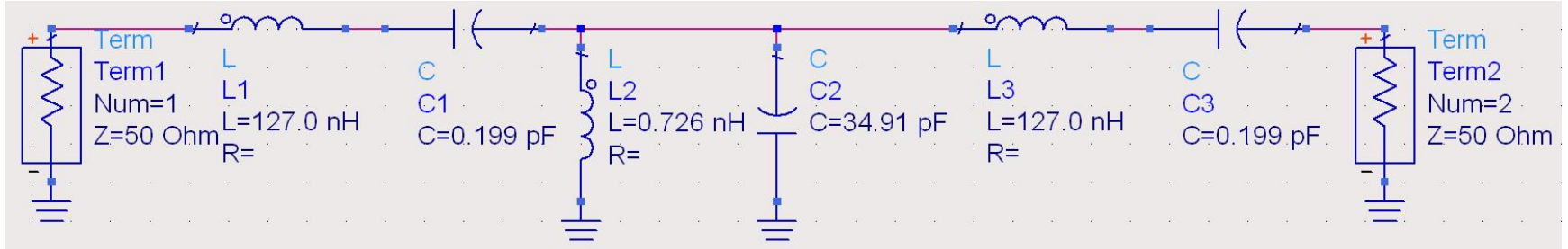

Microwave Filters Implementation

Microwave Filters Implementation

- The lumped-element (L, C) filter design generally works well **only** at low frequencies (RF):
 - lumped-element inductors and capacitors are generally available only for a limited range of values, and can be difficult to implement at microwave frequencies
 - difficulty to obtain the (very low) required tolerance for elements

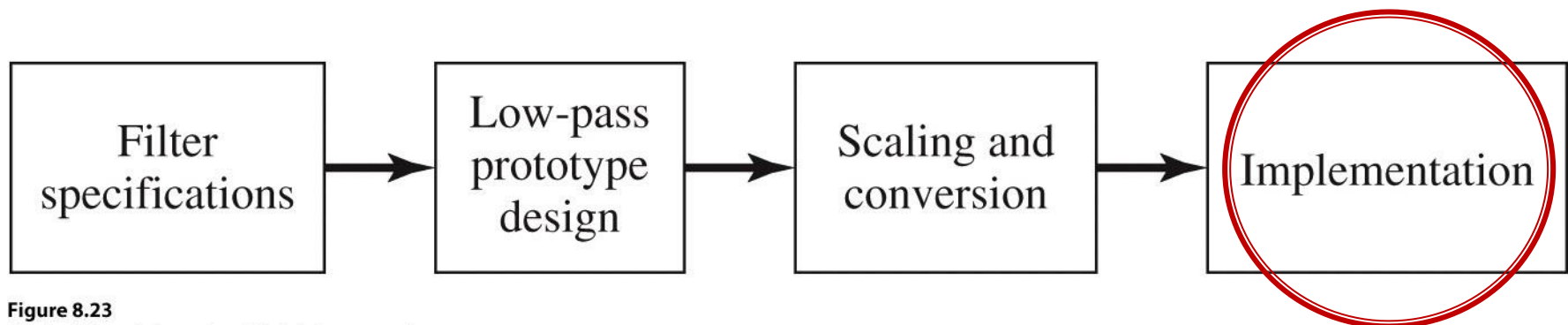


Figure 8.23

Richards' Transformation

- Impedance seen at the input of a line loaded with Z_L

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

- We prefer the load impedance to be:

- open circuit ($Z_L = \infty$) $Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l$

- short circuit ($Z_L = 0$) $Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l$

- Input impedance is:

- capacitive $Z_{in,oc} = j \cdot X_C = \frac{1}{j \cdot B_C}$ $Z_0 \leftrightarrow \frac{1}{C}$ $\tan \beta \cdot l \leftrightarrow \omega$

- inductive $Z_{in,sc} = j \cdot X_L$ $Z_0 \leftrightarrow L$ $\tan \beta \cdot l \leftrightarrow \omega$

Richards' Transformation

- Variable substitution

$$\Omega = \tan \beta \cdot l = \tan \left(\frac{\omega \cdot l}{v_p} \right)$$

- With this variable substitution we define:

- reactance of an inductor

$$j \cdot X_L = j \cdot \Omega \cdot L = j \cdot L \cdot \tan \beta \cdot l$$

- susceptance of a capacitor



$$j \cdot B_C = j \cdot \Omega \cdot C = j \cdot C \cdot \tan \beta \cdot l$$

- The equivalent filter in Ω has a cutoff frequency at:

$$\Omega = 1 = \tan \beta \cdot l \quad \rightarrow \quad \beta \cdot l = \frac{\pi}{4} \quad \rightarrow \quad l = \frac{\lambda}{8}$$

Richards' Transformation

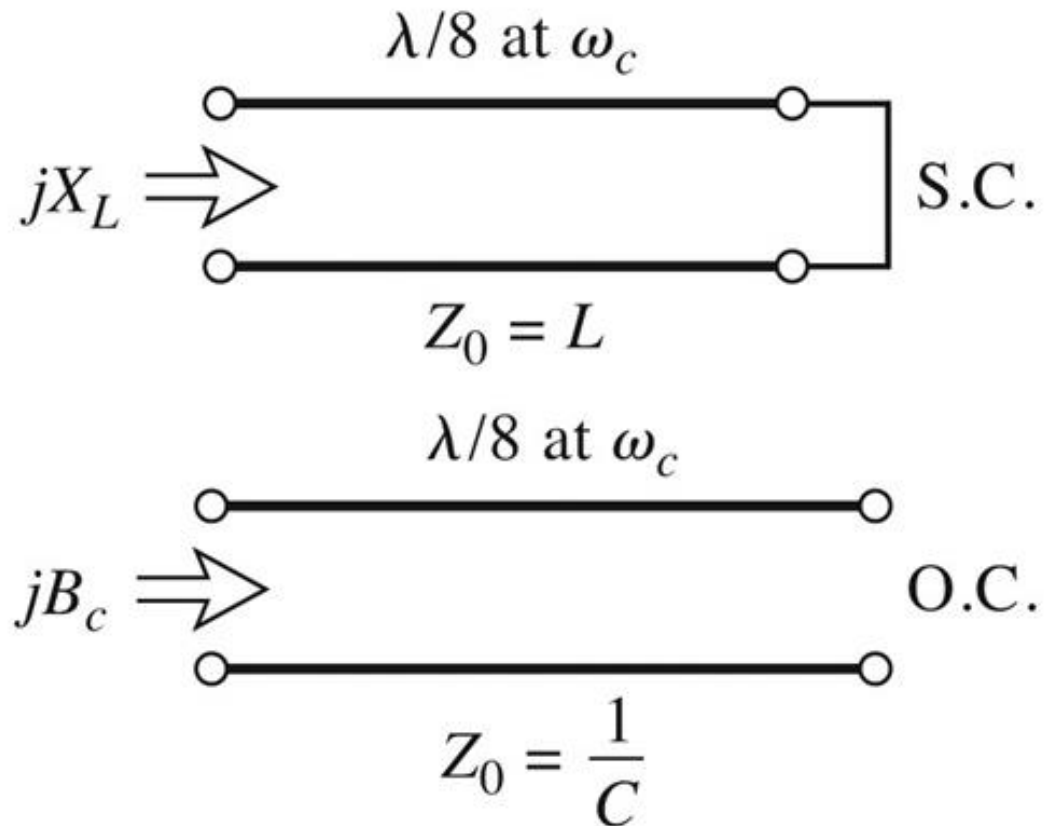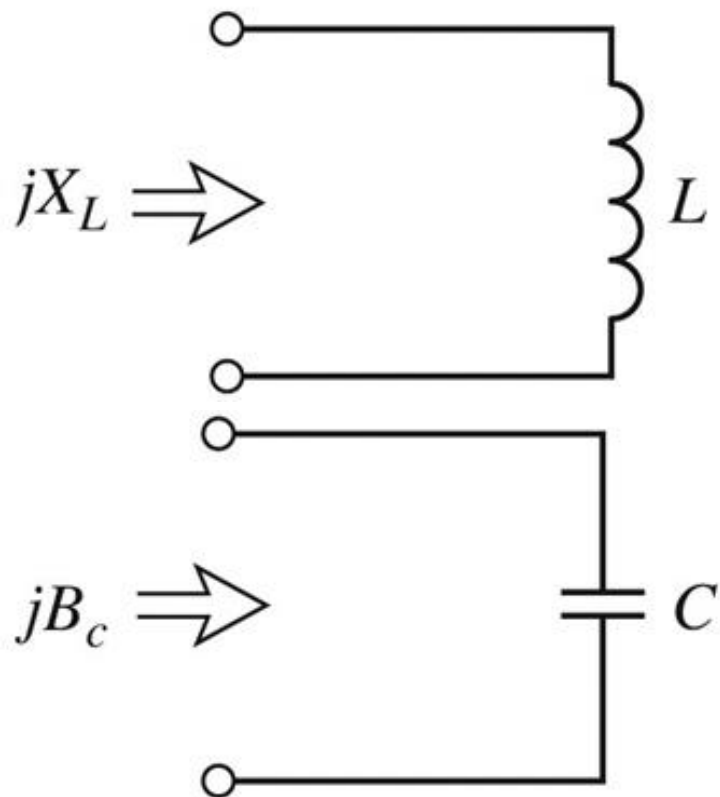- allows implementation of the inductors and capacitors with lines **after** the transformation of the LPF prototype to the required type (LPF/HPF/BPF/BSF)



Richards' Transformation

- By choosing the open-circuited or short-circuited lines to be $\lambda/8$ at the desired cutoff frequency (ω_c) and the corresponding characteristic impedances (L/C from LPF prototype) we will obtain at frequencies around ω_c a behavior similar to that of the prototype filter.
 - At frequencies far from ω_c the behavior of the filter will no longer be identical to that of the prototype (in specific situations the correct behavior must be **verified**)
 - Frequency scaling is simplified: choosing the appropriate physical length of the line to have the electrical length $\lambda/8$ at the desired cutoff frequency
- All lines will have equal electrical lengths ($\lambda/8$) and thus comparable physical lengths, so the lines are called **commensurate** lines

Richards' Transformation

- At the frequency $\omega = 2 \cdot \omega_c$ the lines will be $\lambda/4$ long
long
$$l = \frac{\lambda}{4} \Rightarrow \beta \cdot l = \frac{\pi}{2} \Rightarrow \tan \beta \cdot l \rightarrow \infty$$
- an supplemental attenuation pole will occur at $2 \cdot \omega_c$ (LPF):
 - inductances (usually in series) $Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l \rightarrow \infty$
 - capacitances (usually shunt) $Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l \rightarrow 0$

Richards' Transformation

- the periodicity of tan function implies the periodicity of the filter implemented with lines
 - the filter response will be repeated every $4 \cdot \omega_c$

$$\tan(\alpha + \pi) = \tan \alpha$$

$$\beta \cdot l \Big|_{\omega=\omega_c} = \frac{\pi}{4} \Rightarrow \frac{\omega_c \cdot l}{v_p} = \frac{\pi}{4} \Rightarrow \pi = \frac{(4 \cdot \omega_c) \cdot l}{v_p}$$

$$Z_{in}(\omega) = Z_{in}(\omega + 4 \cdot \omega_c) \Rightarrow P_{LR}(\omega) = P_{LR}(\omega + 4 \cdot \omega_c)$$

$$P_{LR}(4 \cdot \omega_c) = P_{LR}(0)$$



$$P_{LR}(3 \cdot \omega_c) = P_{LR}(-\omega_c)$$

$$P_{LR}(5 \cdot \omega_c) = P_{LR}(\omega_c)$$

Example

- Low-pass filter 4th order, 4 GHz cutoff frequency, maximally flat design (working with 50Ω source and load)
- maximally flat table or formulas:
 - $g_1 = 0.7654 = L_1$
 - $g_2 = 1.8478 = C_2$
 - $g_3 = 1.8478 = L_3$
 - $g_4 = 0.7654 = C_4$
 - $g_5 = 1$ (**does not** need supplemental impedance matching – required only for even order equal-ripple filters)

LPF Prototype

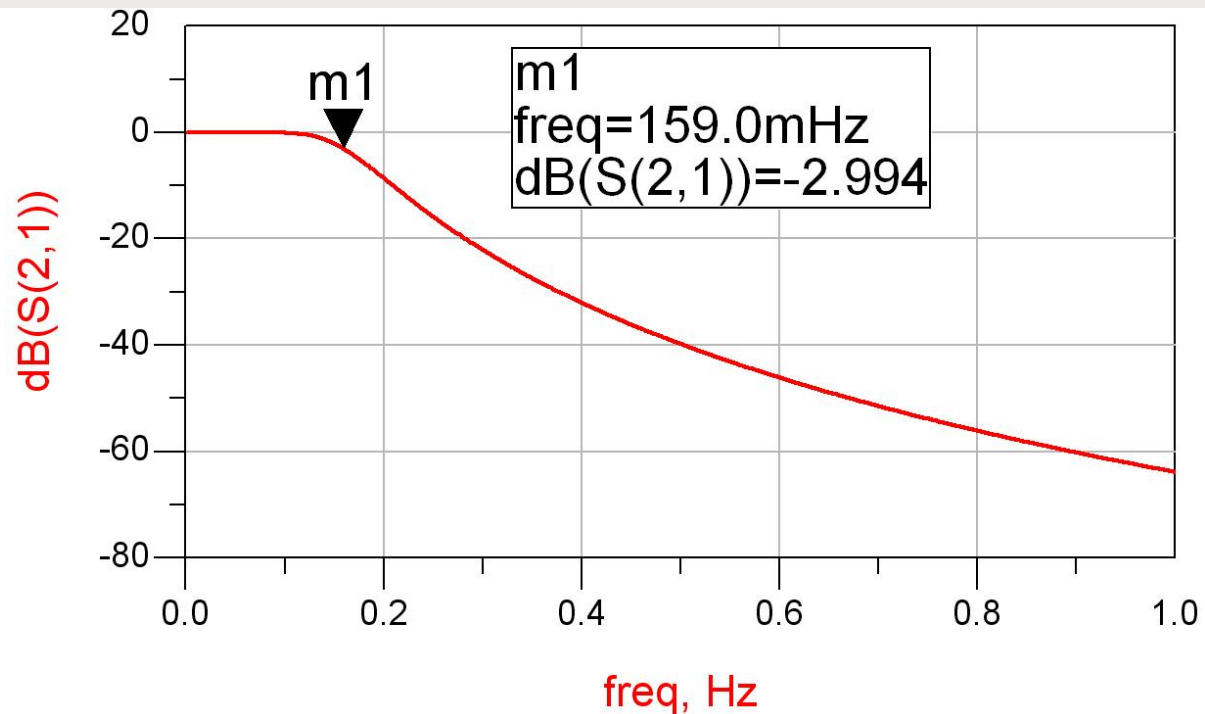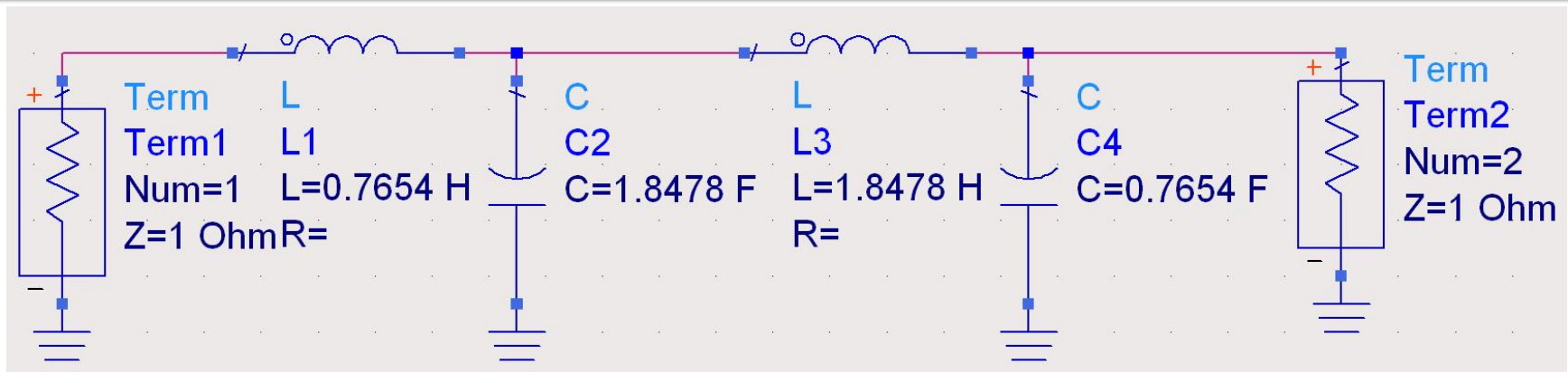

Lumped elements

$$\omega_c = 2 \cdot \pi \cdot 4\text{GHz} = 2.5133 \cdot 10^{10} \text{rad/s}$$

$$g_1 = 0.7654 = L_1,$$

$$g_2 = 1.8478 = C_2,$$

$$g_3 = 1.8478 = L_3,$$

$$g_4 = 0.7654 = C_4,$$

$$g_5 = 1 = RL$$



$$L'_1 = \frac{R_0 \cdot L_1}{\omega_c} = 1.523 \text{nH}$$

$$C'_2 = \frac{C_2}{R_0 \cdot \omega_c} = 1.470 \text{pF}$$

$$L'_3 = \frac{R_0 \cdot L_3}{\omega_c} = 3.676 \text{nH}$$

$$C'_4 = \frac{C_4}{R_0 \cdot \omega_c} = 0.609 \text{pF}$$



Lumped elements – ADS

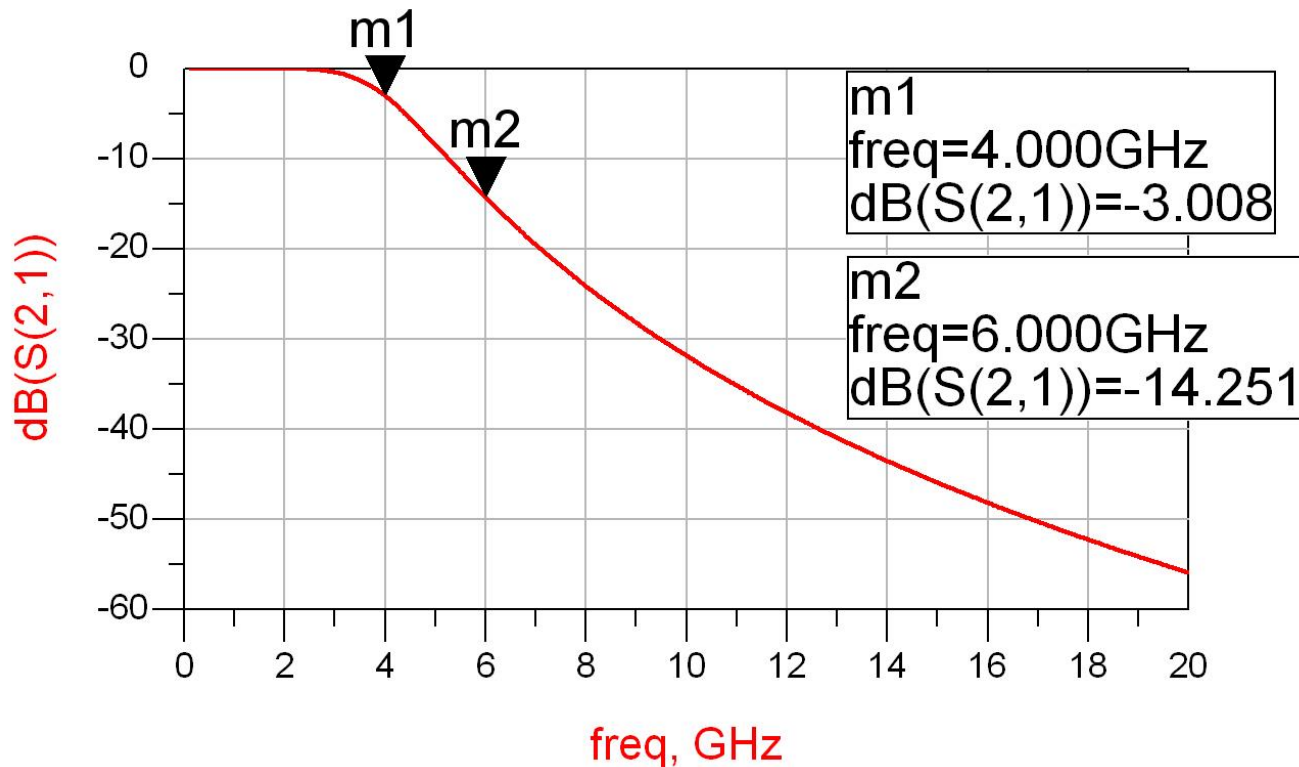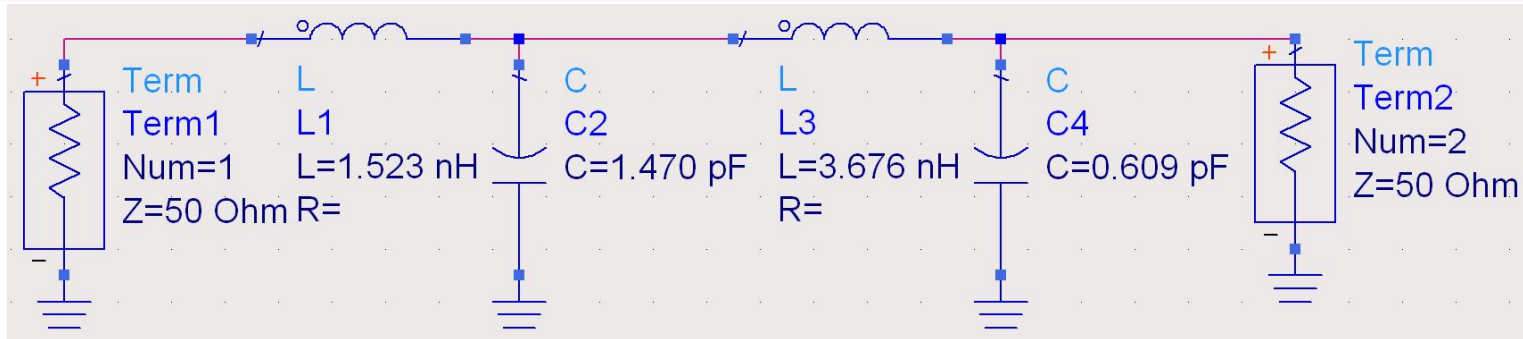

Richards' Transformation


- LPF Prototype parameters:
 - $g_1 = 0.7654 = L_1$
 - $g_2 = 1.8478 = C_2$
 - $g_3 = 1.8478 = L_3$
 - $g_4 = 0.7654 = C_4$
- Normalized line impedances
 - $z_1 = 0.7654 = \text{series / short circuit}$ $Z_0 \leftrightarrow \frac{1}{C}$
 - $z_2 = 1 / 1.8478 = 0.5412 = \text{shunt / open circuit}$
 - $z_3 = 1.8478 = \text{series / short circuit}$ $Z_0 \leftrightarrow L$
 - $z_4 = 1 / 0.7654 = 1.3065 = \text{shunt / open circuit}$
- Impedance scaling by multiplying with $Z_0 = 50\Omega$
- All lines must have the length equal to $\lambda/8$ (electrical length $E = 45^\circ$) at 4GHz

Richards' Transformation – ADS

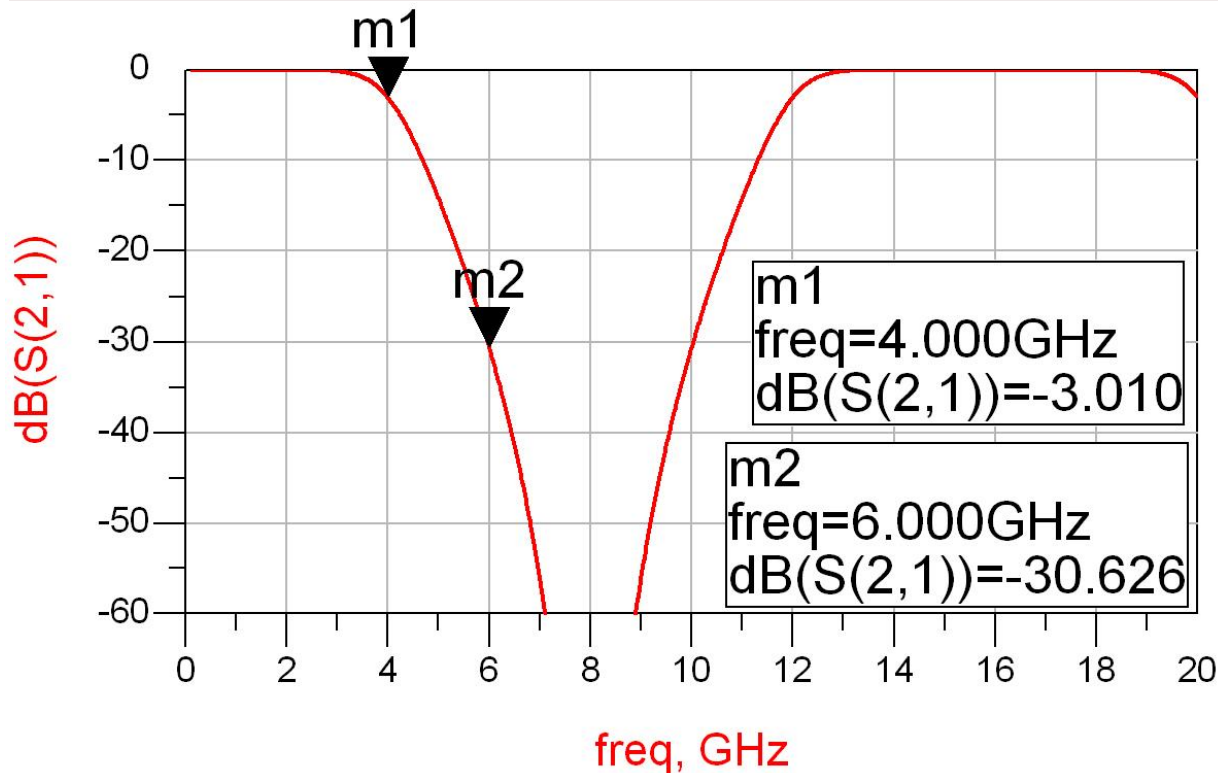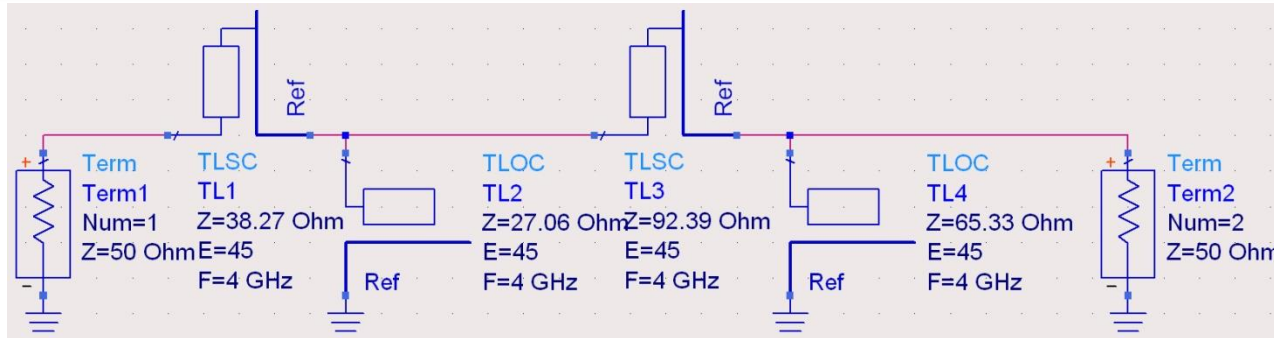

Richards' Transformation

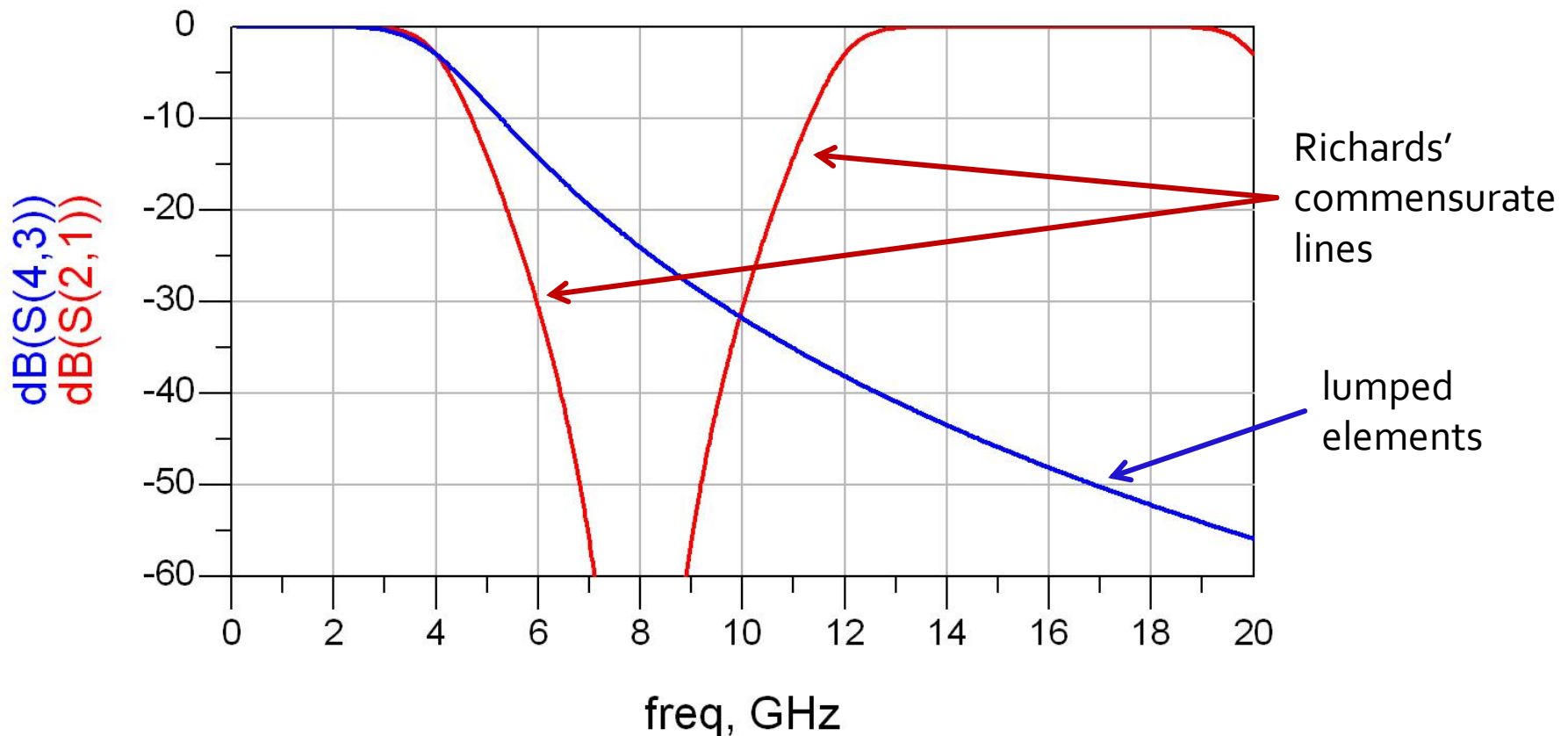- Filters implemented with Richards' Transformation
 - beneficiate from the supplemental pole at $2 \cdot \omega_c$
 - have the major disadvantage of frequency periodicity, a supplemental non-periodic LPF must be inserted if needed



Equal-ripple prototype



- For even N order of the filter (N = 2, 4, 6, 8 ...)
equal-ripple filters **must** closed by a non-standard load impedance **$g_{N+1} \neq 1$**
- If the application doesn't allow this,
supplemental impedance matching is
required (quarter-wave transformer,
binomial ...) to **$g_L = 1$**

$$g_{N+1} \neq 1 \rightarrow R \neq R_0 \quad (50\Omega)$$

Observation: even order equal-ripple


- Same filter, 3dB equal-ripple
- 3dB equal-ripple tables or formulas:
 - $g_1 = 3.4389 = L_1$
 - $g_2 = 0.7483 = C_2$
 - $g_3 = 4.3471 = L_3$
 - $g_4 = 0.5920 = C_4$
 - $g_5 = 5.8095 = R_L$
- Line impedances
 - $Z_1 = 3.4389 \cdot 50\Omega = 171.945\Omega = \text{series / short circuit}$
 - $Z_2 = 50\Omega / 0.7483 = 66.818\Omega = \text{shunt / open circuit}$
 - $Z_3 = 4.3471 \cdot 50\Omega = 217.355\Omega = \text{series / short circuit}$
 - $Z_4 = 50\Omega / 0.5920 = 84.459\Omega = \text{shunt / open circuit}$
 - $R_L = 5.8095 \cdot 50\Omega = 295.475\Omega = \text{load}$

Even order equal-ripple – ADS

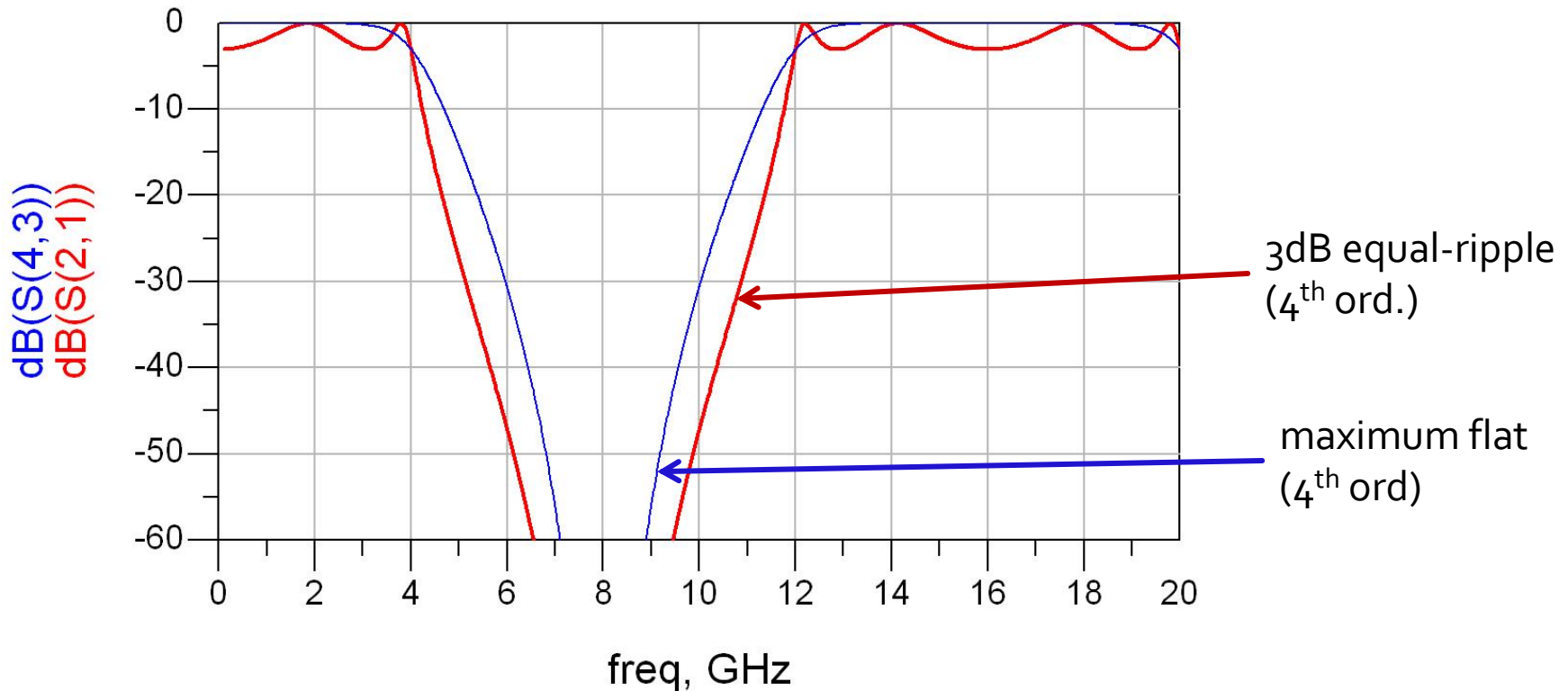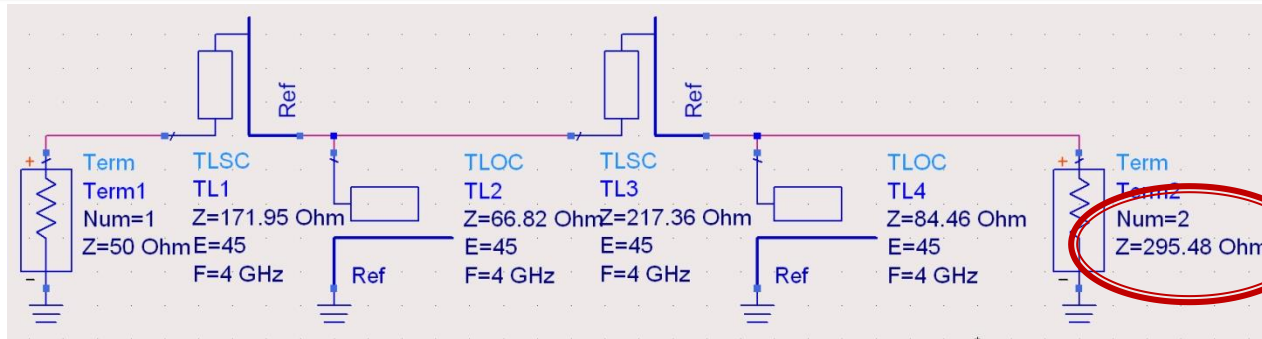

Observation: even order equal-ripple

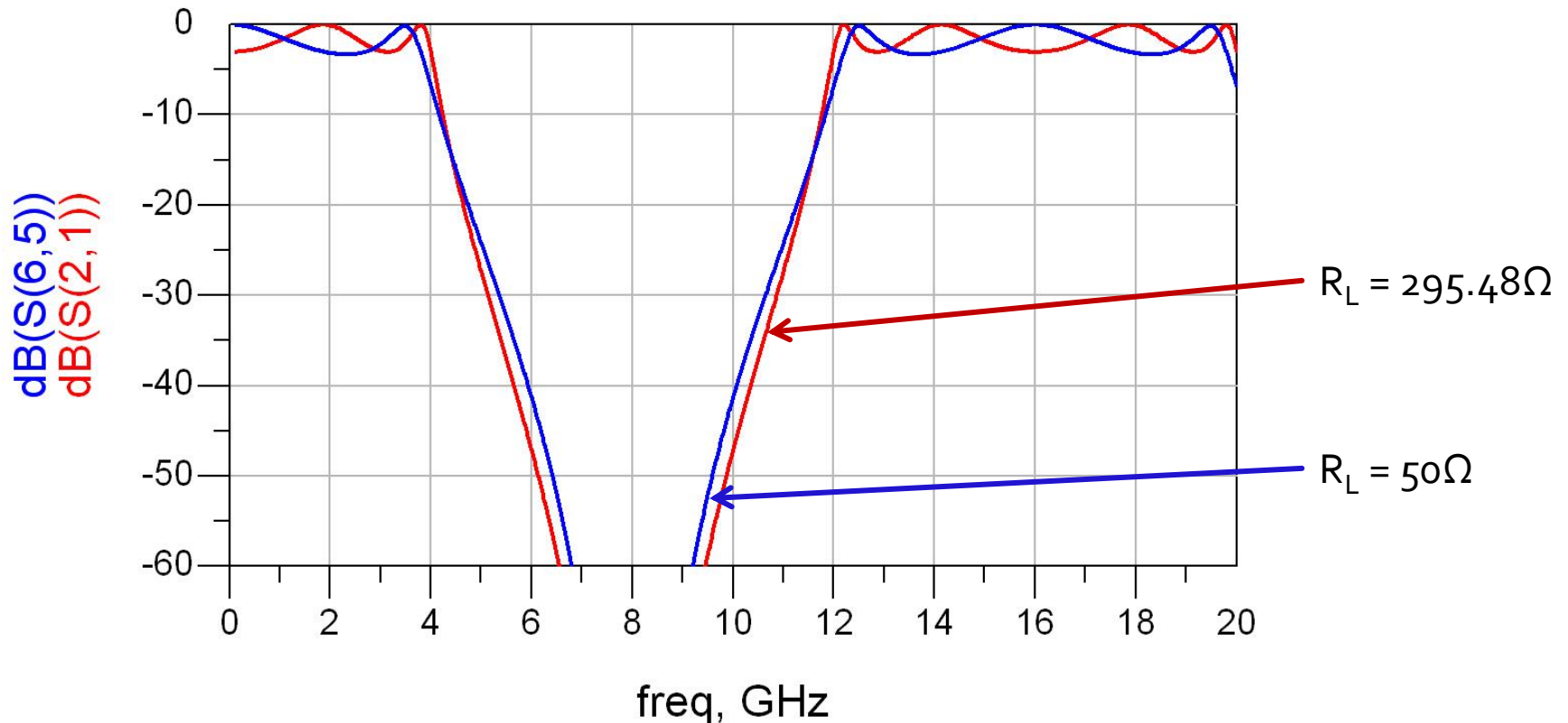- Even order equal-ripple filters need output matching towards 50Ω for precise results.
Example:



Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.etti.tuiasi.ro>
- rdamian@etti.tuiasi.ro