

Lecture 2

2018/2019


# Microwave Devices and Circuits for Radiocommunications

# 2018/2019

- 2C/1L, **MDCR**
- Attendance at minimum 7 sessions (course + laboratory)
- Lectures- **associate professor Radu Damian**
  - Friday 09-11, ? Ill.34, Il.13
  - E – 50% final grade
  - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
    - 3p=+0.5p
  - all materials/equipments authorized
- Laboratory – **associate professor Radu Damian**
  - Wednesday 12-14, Il.12 odd weeks
  - L – 25% final grade
  - P – 25% final grade

# Materials

■ <http://rf-opto.etti.tuiasi.ro>

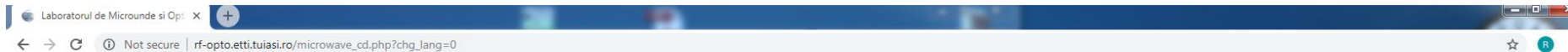

Main **Courses** Master Staff Research Students Admin

**Microwave CD** Optical Communications Optoelectronics Internet Antennas Practica Networks Educational software

## Microwave Devices and Circuits for Radiocommunications (English)

### Course: MDCR (2017-2018)

**Course Coordinator:** Assoc.P. Dr. Radu-Florin Damian  
**Code:** EDOS412T  
**Discipline Type:** DOS; Alternative, Specialty  
**Credits:** 4  
**Enrollment Year:** 4, Sem. 7

### Activities

**Course:** Instructor: Assoc.P. Dr. Radu-Florin Damian, 2 Hours/Week, Specialization Section, Timetable:  
**Laboratory:** Instructor: Assoc.P. Dr. Radu-Florin Damian, 1 Hours/Week, Group, Timetable:

### Evaluation

Type: **Examen**

**A:** 50%, (Test/Colloquium)  
**B:** 25%, (Seminary/Laboratory/Project Activity)  
**D:** 25%, (Homework/Specialty papers)

### Grades

[Aggregate Results](#)

### Attendance

[Course](#)  
[Laboratory](#)

### Lists

[Bonus-uri acumulate \(final\)](#)  
[Studenti care nu pot intra in examen](#)

### Materials

#### Course Slides


[MDCR Lecture 1](#) (pdf, 5.43 MB, en, [ps](#))  
[MDCR Lecture 2](#) (pdf, 3.67 MB, en, [ps](#))  
[MDCR Lecture 3](#) (pdf, 4.76 MB, en, [ps](#))  
[MDCR Lecture 4](#) (pdf, 5.58 MB, en, [ps](#))

# Photos

Grupa 5403

Nr. Student	Prezent	Nr. Student	Prezent	Nr. Student	Prezent
1 ANGHIELUS IONUT-MARIUS	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:	2 ANTIGHIN FLORIN-RAZVAN	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:	3 ANTONICA BIANCA	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:
4 APOSTOL PAVEL-MANUEL	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:	5 BALASCA IULIAN-PETRU	<input checked="" type="checkbox"/> Puncte: 0 Nota: 0 Obs:	6 BOSTAN ANDREI-PETRICIA	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:
7 BOTEZAT EMANUEL	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:	8 BUTUNOI GEORGE-MADALIN	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:	9 CHILEA SALUCA-MARIA	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:
10 CHERITOI ECATERINA	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:	11 COJOC MARIUS	<input checked="" type="checkbox"/> Puncte: 0 Nota: 0 Obs:	12 COJOCARI AURA-FLORINA	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:

Nr. Student	Prezent
2 ANTIGHIN FLORIN-RAZVAN	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:

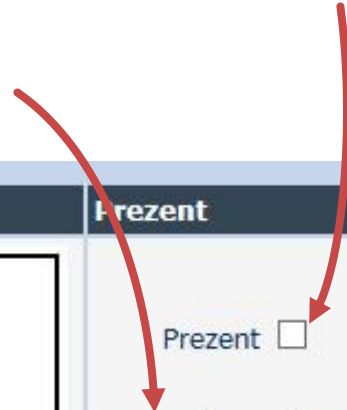

# Access

## ■ Not customized



A student profile page with a blue background. On the left is a blurred photo of a student. To the right, under the heading "Date:", is a table with student details. Below this is a link "Acceseaza ca acest student" circled in red. At the bottom is a table of grades for the subject "Tehnologii Web".

**Date:**

Grupa	5304 (2015/2016)
Specializarea	Tehnologii si sisteme de telecomunicatii
Marca	5184

[Acceseaza ca acest student](#)

**Note obtinute**

Disciplina	Tip	Data	Descriere	Nota	Puncte	Obs.
TW			Tehnologii Web			
N		17/01/2014	Nota finala	10	-	
A		17/01/2014	Colocviu Tehnologii Web 2013/2014	10	7.55	
B		17/01/2014	Laborator Tehnologii Web 2013/2014	9	-	
D		17/01/2014	Tema Tehnologii Web 2013/2014	9	-	



A login form with a blue background. It contains fields for "Nume" (Name), "Email", and "Cod de verificare" (Verification code). The "Email" and "Cod de verificare" fields are circled in red. Below the verification code field is a large, stylized alphanumeric code "344bd9f" and a "Trimite" (Send) button.

Nume  
IACOBSCUN

Email

Cod de verificare

344bd9f

Trimite


# Proiect 2018/2019

- factorul "andrei" =  $-2p$

2017/8



# Course Objective

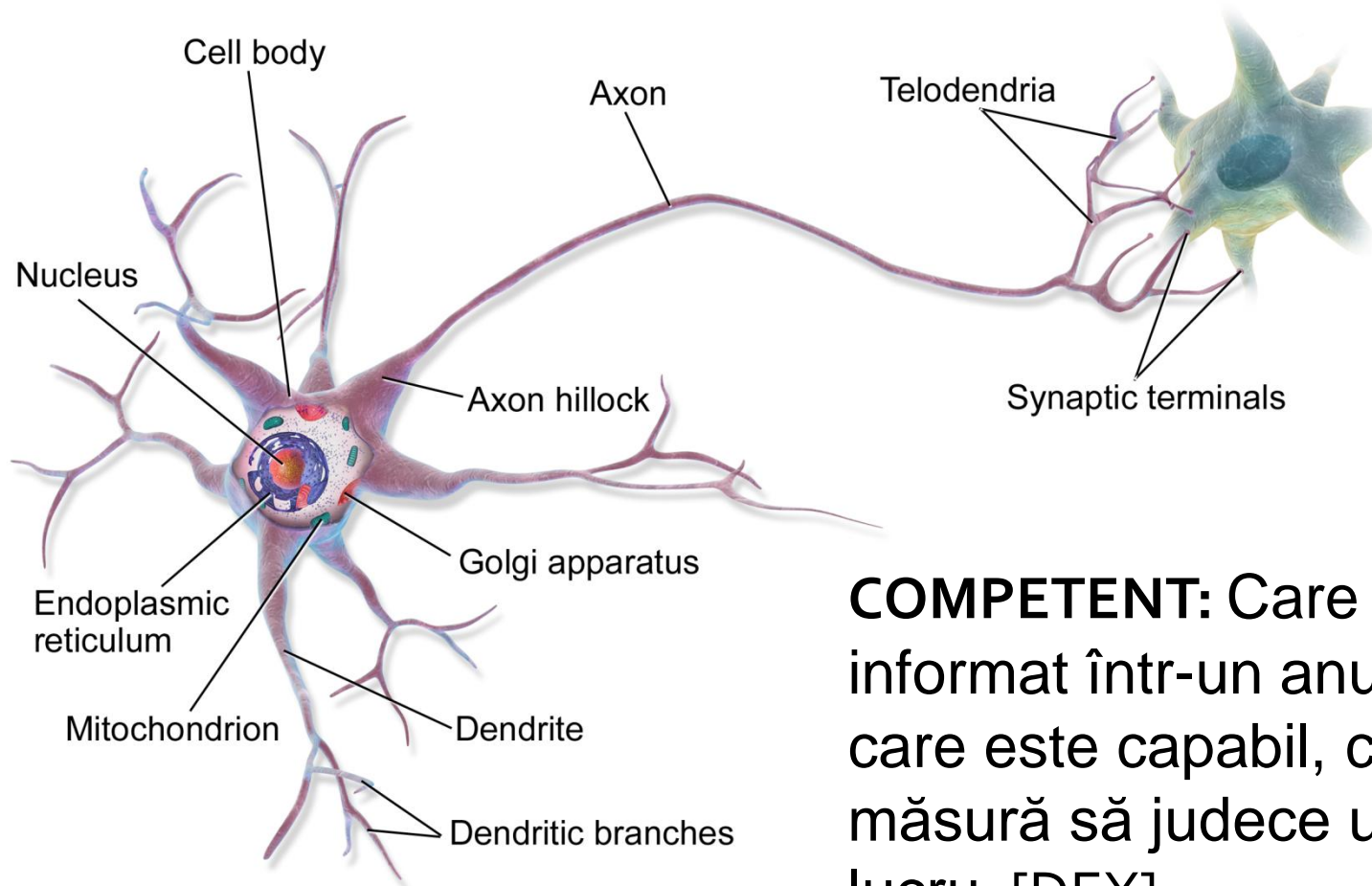

**COMPETENT:** Care este bine informat într-un anumit domeniu; care este capabil, care este în măsură să judece un anumit lucru. [DEX]

~1930





# Technology

> 2010



< 1950

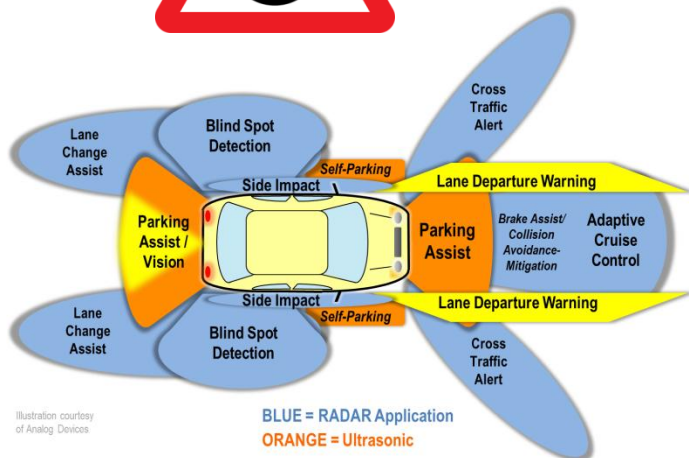


Illustration courtesy of Analog Devices

# Examen: Logarithmic scales

$$\text{dB} = 10 \cdot \log_{10} (P_2 / P_1)$$

0 dB	= 1
+ 0.1 dB	= 1.023 (+2.3%)
+ 3 dB	= 2
+ 5 dB	= 3
+ 10 dB	= 10
-3 dB	= 0.5
-10 dB	= 0.1
-20 dB	= 0.01
-30 dB	= 0.001

$$\text{dBm} = 10 \cdot \log_{10} (P / 1 \text{ mW})$$

0 dBm	= 1 mW
3 dBm	= 2 mW
5 dBm	= 3 mW
10 dBm	= 10 mW
20 dBm	= 100 mW
-3 dBm	= 0.5 mW
-10 dBm	= 100 $\mu$ W
-30 dBm	= 1 $\mu$ W
-60 dBm	= 1 nW

$$[\text{dBm}] + [\text{dB}] = [\text{dBm}]$$

$$[\text{dBm/Hz}] + [\text{dB}] = [\text{dBm/Hz}]$$

$$[x] + [\text{dB}] = [x]$$


# Examen

- Complex numbers arithmetic!!!!
- $z = a + j \cdot b ; j^2 = -1$

# Introduction

---

# Microwaves

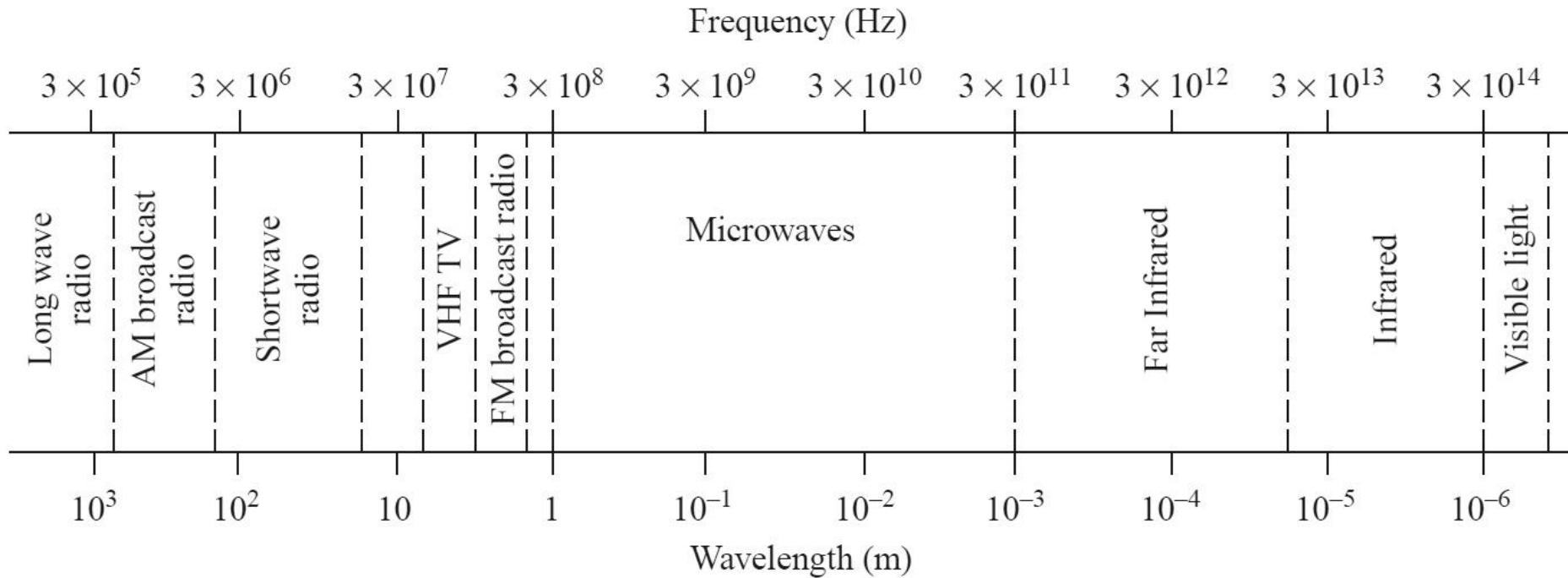

- typically
  - $f \approx 1 \div 3 \text{GHz} - 300 \text{GHz}$
  - $\lambda \approx 1 \text{mm} - 10 \text{cm}$

# ~ Microwaves

- Electrical Length (Phase Length)
  - $l$  – physical length
  - $E = \beta \cdot l$  – electrical Length

$$E = \beta \cdot l = \frac{2\pi}{\lambda} \cdot l = 2\pi \cdot \left( \frac{l}{\lambda} \right)$$

$$E = \beta \cdot l = \frac{2\pi}{c_0} \cdot (l \cdot f \cdot \sqrt{\epsilon_r})$$

V, I vary  
~ useless


- Dependency
  - antenna gain
  - Radar cross-section

# Electrical Length

- Behavior (and description) of any circuit depends on his electrical length at the particular frequency of interest

- $E \approx 0 \rightarrow$  Kirchhoff
- $E > 0 \rightarrow$  wave propagation
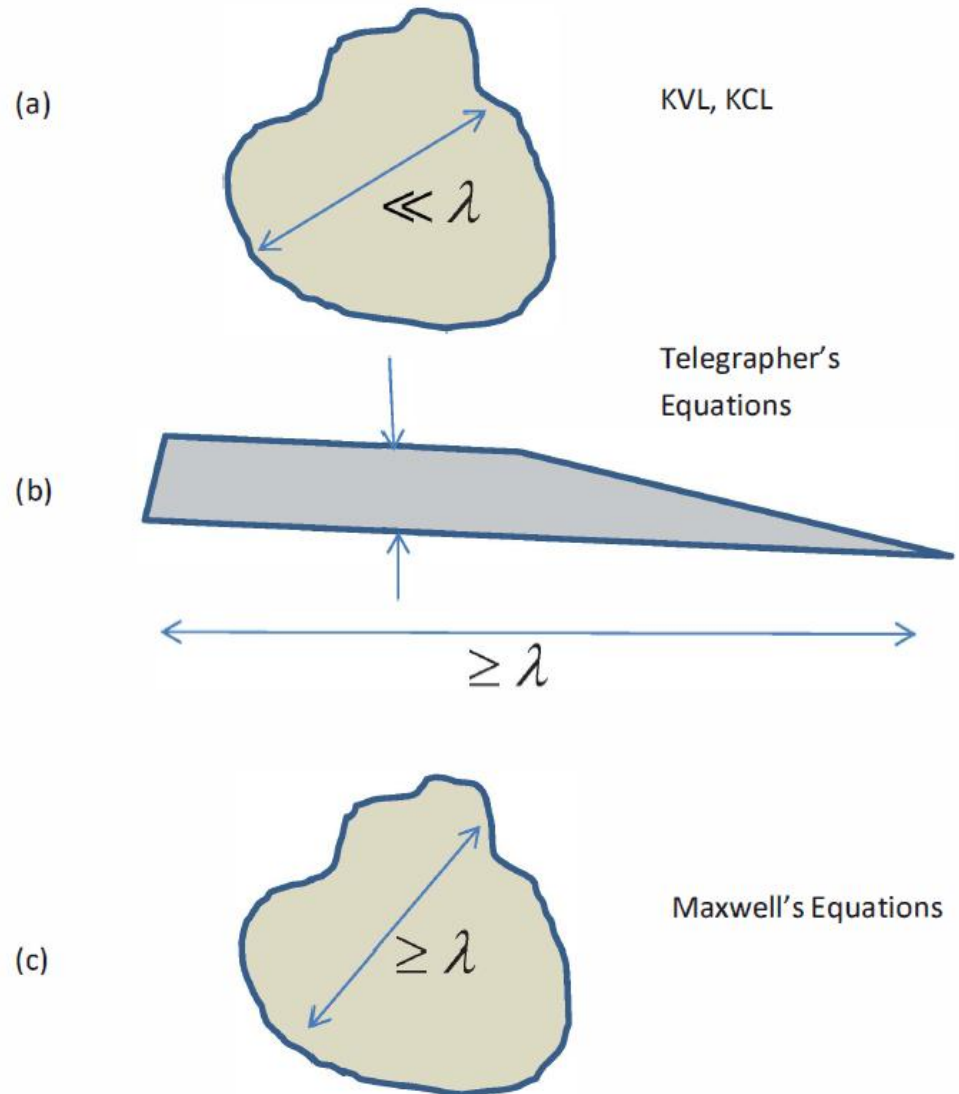
$$E = \beta \cdot l = \frac{2\pi}{\lambda} \cdot l = 2\pi \cdot \left( \frac{l}{\lambda} \right)$$



# Maxwell's Equations

$$\nabla \times E = -\frac{\partial B}{\partial t}$$

$$\nabla \times H = \frac{\partial D}{\partial t} + J$$

$$\nabla \cdot D = \rho$$

$$\nabla \cdot B = 0$$

$$\nabla \cdot J = -\frac{\partial \rho}{\partial t}$$

## ■ Constitutive equations

$$D = \varepsilon \cdot E$$

$$B = \mu \cdot H$$

$$J = \sigma \cdot E$$

## • Vacuum


$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

$$\varepsilon_0 = 8,854 \times 10^{-12} \text{ F/m}$$

$$c_0 = \frac{1}{\sqrt{\varepsilon_0 \cdot \mu_0}} = 2,99790 \cdot 10^8 \text{ m/s}$$



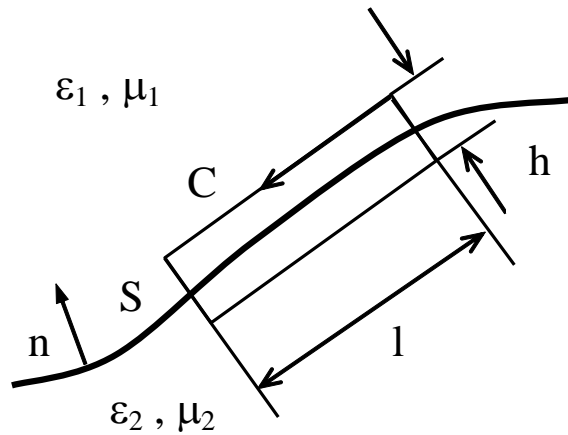
# Interface conditions on the interface between two different media



a)

$$n \times (E_1 - E_2) = 0$$

$$n \times (H_1 - H_2) = J_S$$

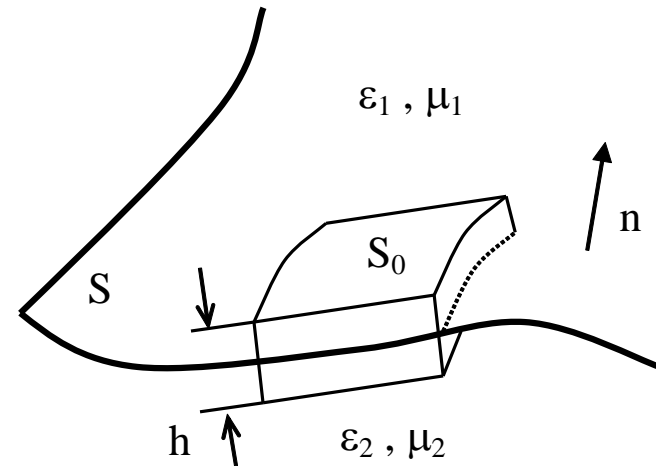

b)

$$n \cdot (D_1 - D_2) = \rho_S$$

$$n \cdot (B_1 - B_2) = 0$$

- If one of the media is a perfect conductor (metal) all fields are annulled inside

# Electromagnetic fields with harmonic time dependence

$$X = X_0 e^{j\omega t} \quad \frac{\partial X}{\partial t} = j \cdot \omega \cdot X$$

$$g(\omega) = \int_{-\infty}^{\infty} f(t) \cdot e^{-j\omega t} dt \quad f(t) = \int_{-\infty}^{\infty} g(\omega) \cdot e^{j\omega t} d\omega$$

- Maxwell's Equations more simple

$$\nabla^2 E + \omega^2 \epsilon \mu E = j\omega \mu J + \frac{1}{\epsilon} \nabla \rho$$

$$\nabla^2 H + \omega^2 \epsilon \mu H = -\nabla \times J$$


$$\nabla \cdot E = \frac{\rho}{\epsilon}$$

$$\nabla \cdot H = 0$$

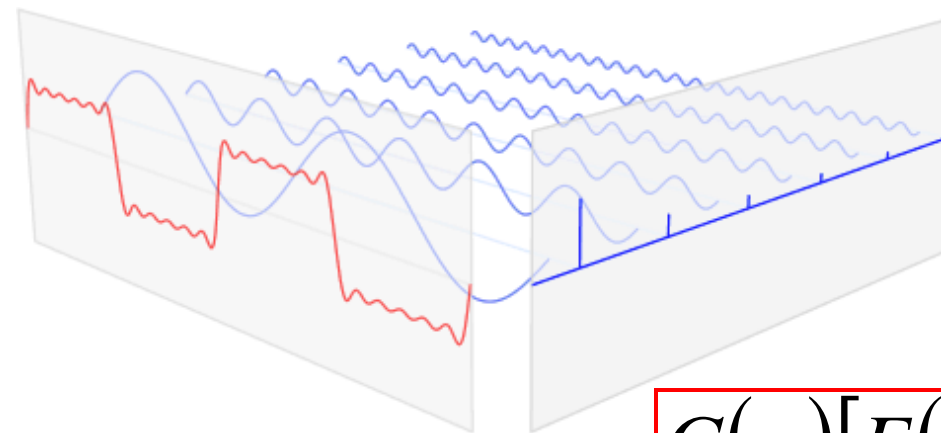
# Mathematical models

- particular cases where analytical solution exists
  - harmonic signals, Fourier Transform, frequency spectrum

$$X = X_0 e^{j \cdot \omega \cdot t} \quad \frac{\partial X}{\partial t} = j \cdot \omega \cdot X \quad g(\omega) = \int_{-\infty}^{\infty} f(t) \cdot e^{-j\omega t} dt \quad f(t) = \int_{-\infty}^{\infty} g(\omega) \cdot e^{j\omega t} d\omega$$




$$G(\omega)[F(\omega)]$$

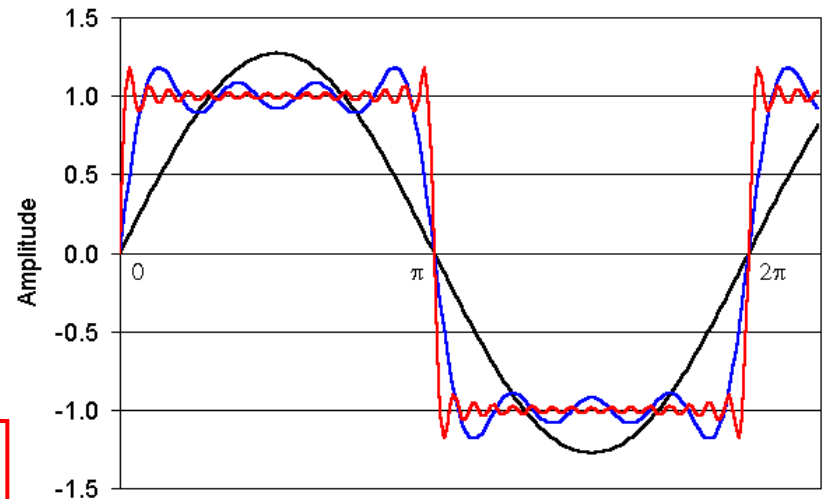

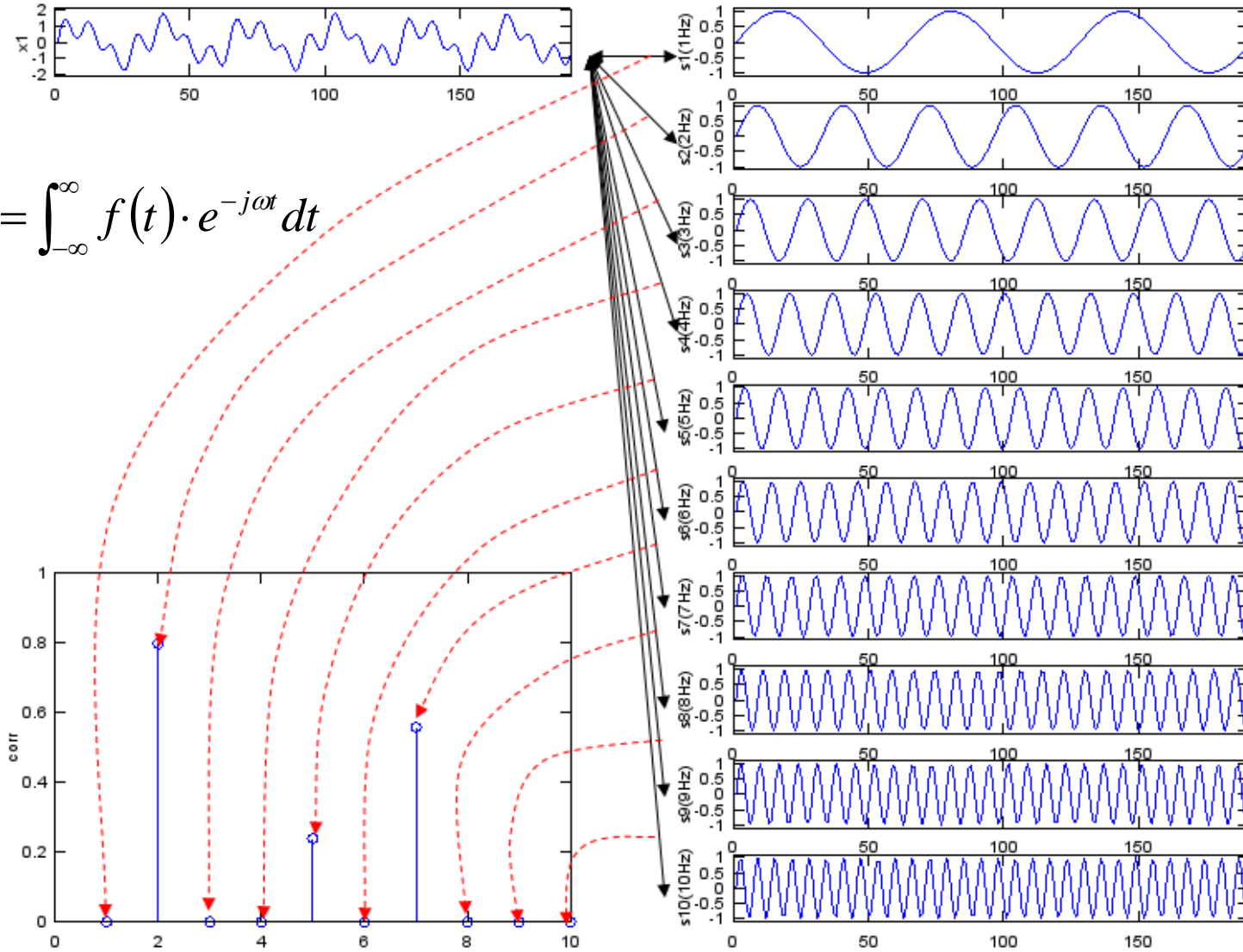
# Mathematical models

$$g(\omega) = \int_{-\infty}^{\infty} f(t) \cdot e^{-j\omega t} dt$$



# Mathematical models

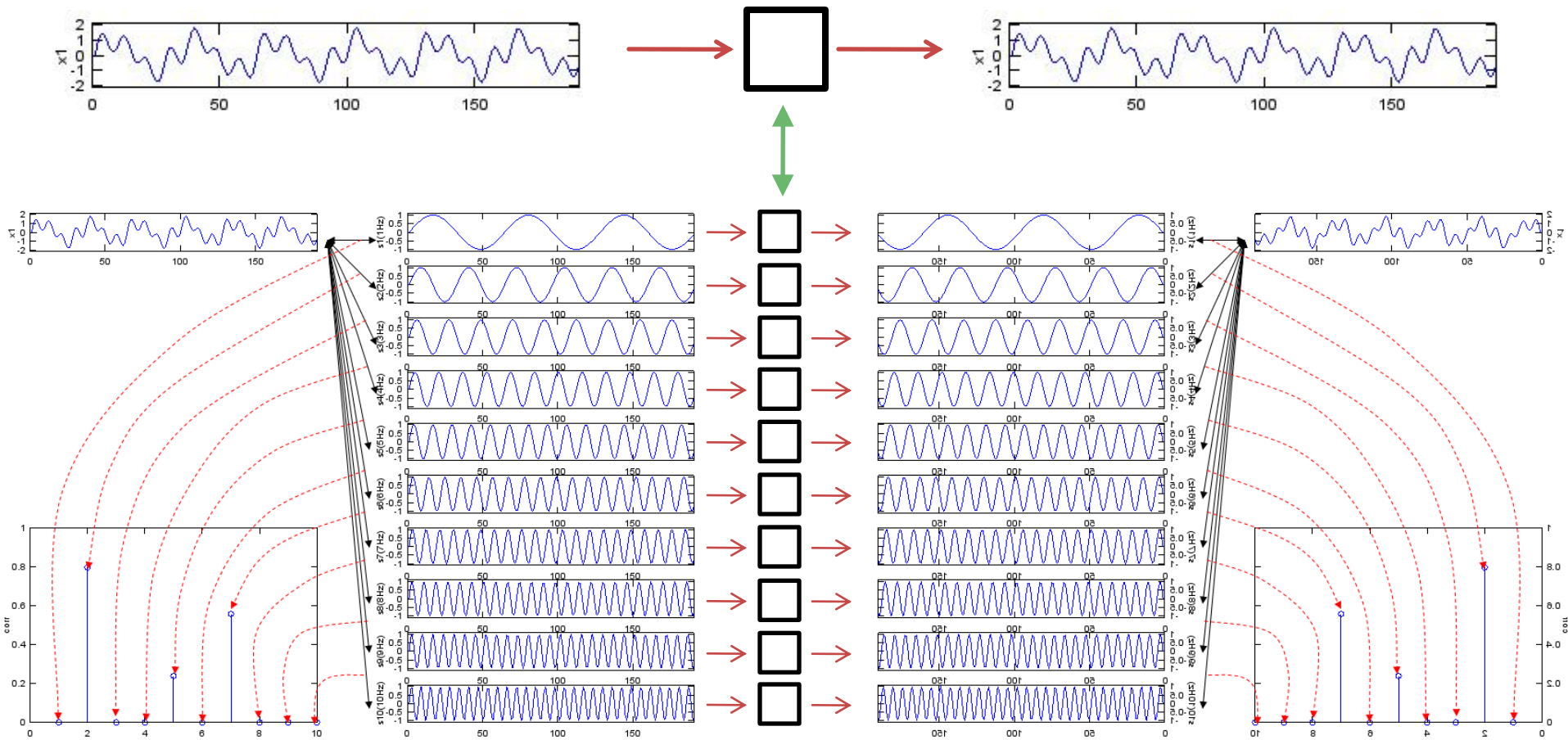

$$F(\omega) = \int_{-\infty}^{\infty} f(t) \cdot e^{-j\omega t} dt$$

$$G(\omega)[F(\omega)]$$

$$g(t) = \int_{-\infty}^{\infty} G(\omega) \cdot e^{j\omega t} d\omega$$

# Wave equations

- Helmholtz equations or Wave equations

Medium void of free electric charges


$$\nabla^2 E - \gamma^2 E = 0$$

$$\nabla^2 H - \gamma^2 H = 0$$

$$\gamma^2 = -\omega^2 \epsilon \mu + j\omega \mu \sigma$$

$\gamma$  – propagation constant (known also as phase constant or wave number)

# Solutions of the wave equations

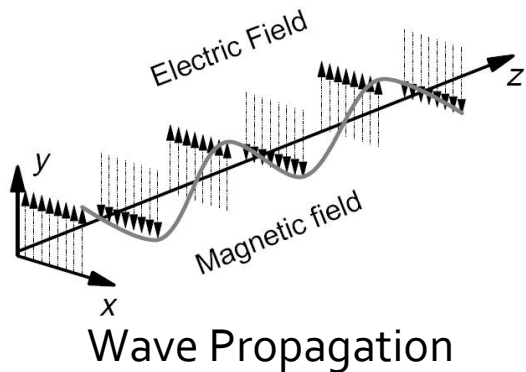


Electric field only in Oy direction, ← through judicious choice  
 wave traveling after Oz direction ← of the coordinate system

$$E_y = E_+ e^{-\gamma \cdot z} + E_- e^{\gamma \cdot z}$$

$$\gamma = \sqrt{-\omega^2 \epsilon \mu + j \omega \mu \sigma} = \alpha + j \cdot \beta$$

If we have only the positive direction wave  $E_+ \Rightarrow A$
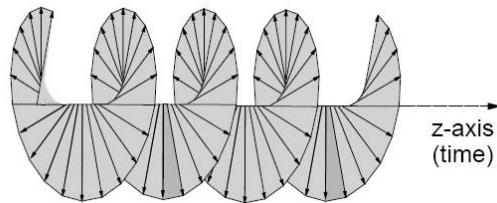
$$E_y = A e^{-(\alpha + j \cdot \beta) \cdot z}$$



Circular Polarization


Harmonic Field

$$E_y = A \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t - \beta \cdot z)}$$

Amplitude

Attenuation

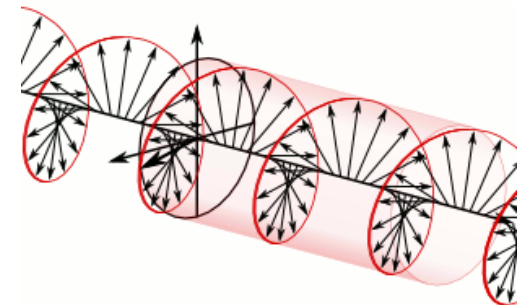Wave Propagation  
 (simultaneous space and  
 time variation)



# Attenuation

$$E_y(z_1) = Ct \cdot e^{-\alpha \cdot z_1} \cdot e^{j(\omega t - \beta \cdot z_1)}$$

$$E_y(z_2) = Ct \cdot e^{-\alpha \cdot z_2} \cdot e^{j(\omega t - \beta \cdot z_2)}$$

$$W, P \sim \int E^2$$

$$A = \frac{P_2}{P_1} = \frac{Ct^2 \cdot e^{-2\alpha \cdot z_2}}{Ct^2 \cdot e^{-2\alpha \cdot z_1}} = e^{-2\alpha \cdot (z_2 - z_1)}$$

$$A[dB] = 10 \log_{10} \frac{P_2}{P_1} = 10 \log_{10} \left[ e^{-2\alpha \cdot (z_2 - z_1)} \right]$$


$$A[dB] = -20 \cdot \alpha \cdot (z_2 - z_1) \log_{10} e = -8.686 \cdot \alpha \cdot (z_2 - z_1)$$

$$A / L [dB / km] = -8.686 \cdot \alpha < 0$$

- ▶ Attenuation usually expressed in **dB/km**
  - ▶ most of the time a positive value is used
  - ▶ “-” sign = **implied** by the word used



# Plane wave parameters

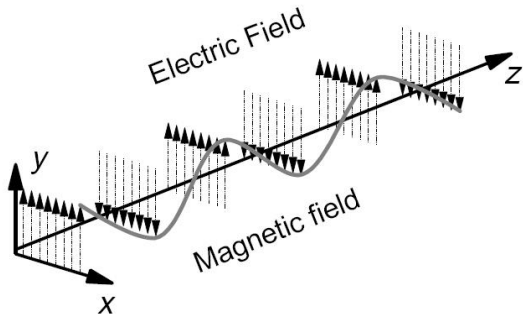

$$\nabla \times \mathbf{E} = -j\omega\mu \cdot \mathbf{H}$$

$$H_x = \frac{j\gamma \cdot E_y}{\omega\mu}$$

Lossless Medium,  $\sigma = 0$

$$\gamma = j\omega \cdot \sqrt{\epsilon\mu}$$

$$\eta = \frac{E_y}{H_x} = \sqrt{\frac{\mu}{\epsilon}}$$

intrinsic impedance of the medium

$$E_y = A \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega \cdot t - \beta \cdot z)}$$

constant phase points:  $(\omega \cdot t - \beta \cdot z) = \text{const}$

Phase velocity

$$v_p = \frac{dz}{dt} = \frac{\omega}{\beta} = \frac{1}{\sqrt{\epsilon\mu}}$$



Group velocity

$$v_g = \frac{dz}{dt} = \frac{d\omega}{d\beta}$$

in dispersive media where  $\beta = \beta(\omega)$
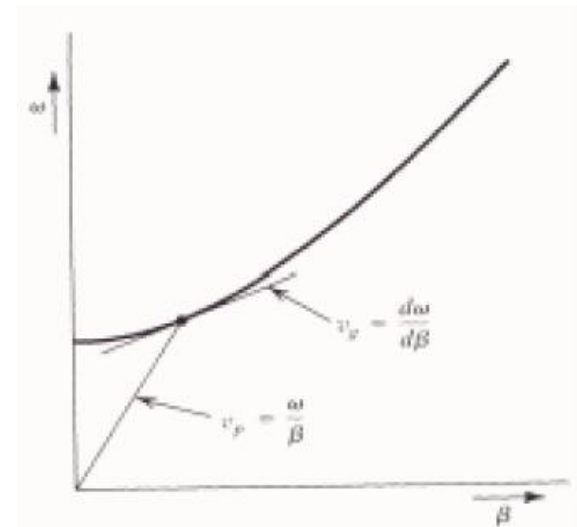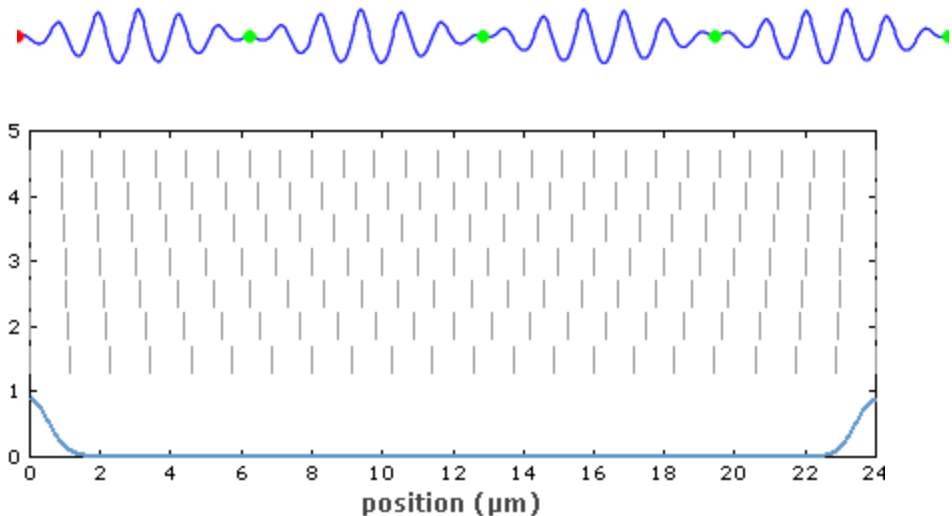
# Group and phase velocities

- Phase velocity – **virtual** speed at which a constant phase point travels (in certain conditions might be greater than the speed of light)
- Group velocity – speed at which the signal (energy, information) propagates (always less or equal to the speed of light in that medium)



# Plane wave parameters

- In vid

$$\eta_0 = \sqrt{\frac{\mu_0}{\epsilon_0}} = 377\Omega \quad v = v_g = c_0 \quad c_0 = \frac{1}{\sqrt{\epsilon_0 \cdot \mu_0}} = 2,99790 \cdot 10^8 \text{ m/s}$$

$$\lambda_0 = \frac{2\pi}{\beta} = \frac{c_0}{f} \quad T = \frac{2\pi}{\omega} = \frac{1}{f}$$

Space periodicity

Time periodicity

- In mediu nedispersiv  $\epsilon_r$


$$c = \frac{1}{\sqrt{\epsilon \cdot \mu_0}} = \frac{1}{\sqrt{\epsilon_0 \epsilon_r \cdot \mu_0}} = \frac{c_0}{\sqrt{\epsilon_r}}$$

$$n = \sqrt{\epsilon_r} \quad \text{refractive index of a medium}$$

$$c = \frac{c_0}{n}$$

$$T = \frac{2\pi}{\omega} = \frac{1}{f}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{c}{f}$$

$$\lambda = \frac{c_0}{\sqrt{\epsilon_r} \cdot f} = \frac{\lambda_0}{\sqrt{\epsilon_r}}$$


# Solutions of the wave equations

$E_y = E^+ e^{-\gamma \cdot z} + E^- e^{\gamma \cdot z}$  Electric field only in Oy direction, ← through judicious choice  
wave traveling after Oz direction ← of the coordinate system

$$\gamma = \sqrt{-\omega^2 \epsilon \mu + j \omega \mu \sigma} = \alpha + j \cdot \beta$$

## ■ wave

- incident
- reflected

## ■ wave

- direct
- inverse

$$E_y = E^+ \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t - \beta \cdot z)}$$

$$(\omega \cdot t - \beta \cdot z) = \text{const}$$

$$E_y = E^- \cdot e^{\alpha \cdot z} \cdot e^{j(\omega t + \beta \cdot z)}$$

$$(\omega \cdot t + \beta \cdot z) = \text{const}$$

points of  
constant  
phase

# Solutions of the wave equations

- wave

- incident
- reflected

$$E_y = E^+ \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t - \beta \cdot z)} + E^- \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t + \beta \cdot z)}$$

$$H_z = H^+ \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t - \beta \cdot z)} + H^- \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t + \beta \cdot z)}$$

- wave

- direct
- inverse

$$V(z) = V^+ \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t - \beta \cdot z)} + V^- \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t + \beta \cdot z)}$$

$$I(z) = I^+ \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t - \beta \cdot z)} + I^- \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t + \beta \cdot z)}$$

$$V(z) = V^+ \cdot e^{j(\omega t - \beta \cdot z)} + V^- \cdot e^{j(\omega t + \beta \cdot z)}$$

# Modes in delimited media





- Electromagnetic fields with harmonic time dependence
  - Maxwell's Equations simplified

$$X = X_0 e^{j \cdot \omega \cdot t} \quad \frac{\partial X}{\partial t} = j \cdot \omega \cdot X \quad g(\omega) = \int_{-\infty}^{\infty} f(t) \cdot e^{-j\omega t} dt \quad f(t) = \int_{-\infty}^{\infty} g(\omega) \cdot e^{j\omega t} d\omega$$



- In delimited media the solutions of Maxwell's Equations must also verify boundary conditions
  - solutions must respect some supplemental conditions
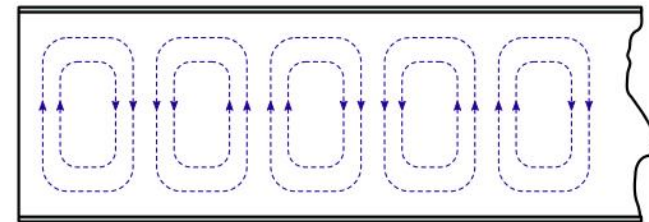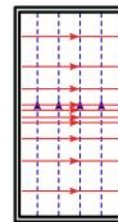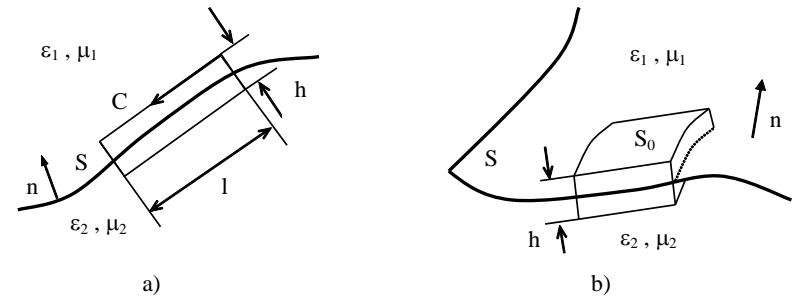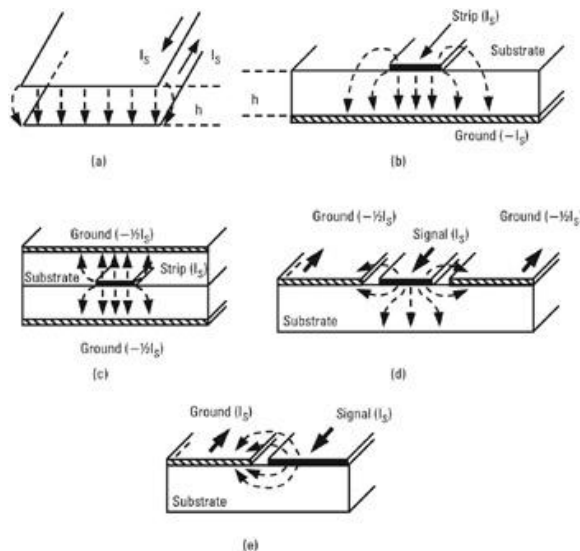
# Modes in delimited media

- Electric field must always be normal on an electric wall or annulled
- Magnetic field must always be tangent to an electric wall or annulled




TE<sub>10</sub>

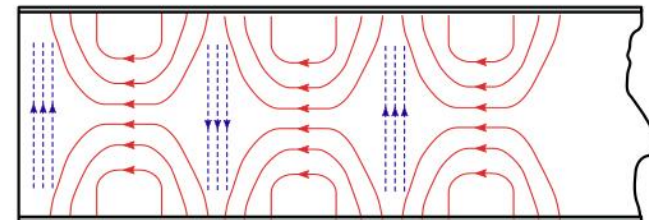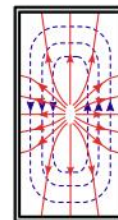

TM<sub>11</sub>

# Moduri in medii delimitate

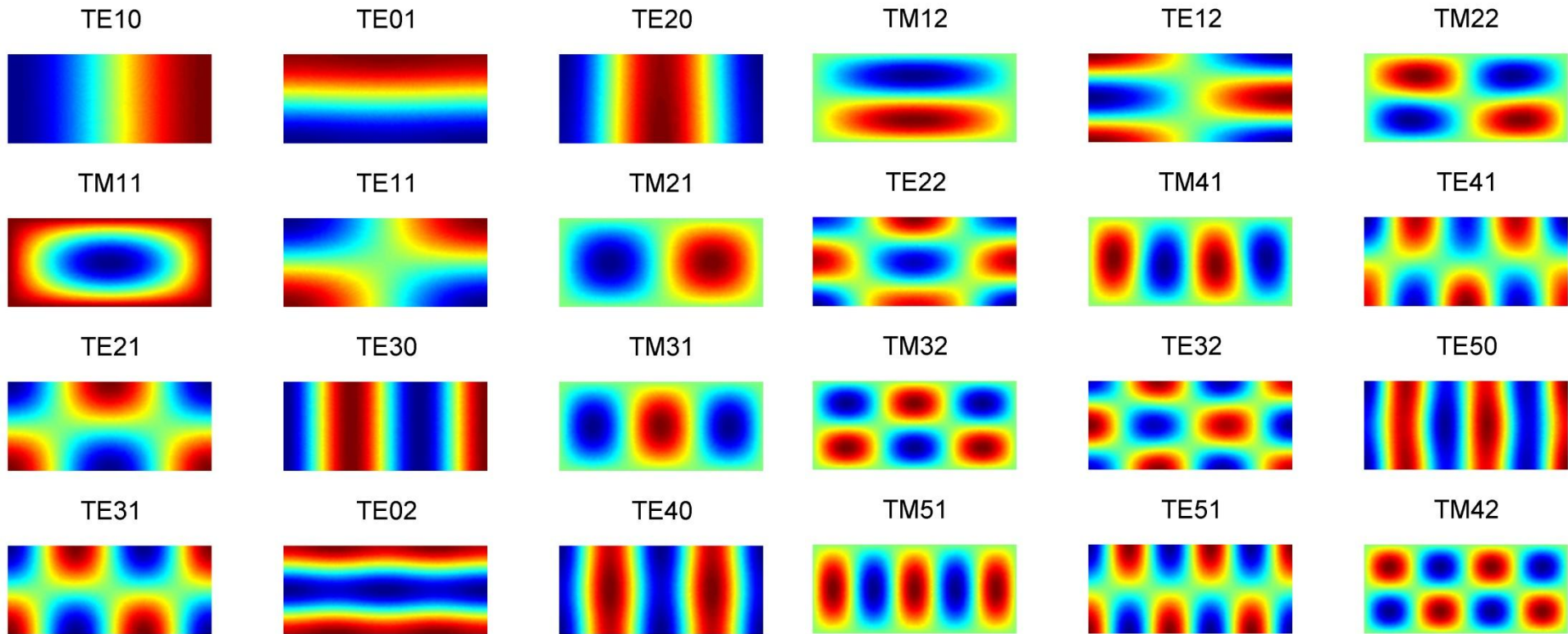

- Similar with Fourier Transform

$$g(\omega) = \int_{-\infty}^{\infty} f(t) \cdot e^{-j\omega t} dt \quad f(t) = \int_{-\infty}^{\infty} g(\omega) \cdot e^{j\omega t} d\omega$$

$$E^+, E^- = \sum_1^{\infty} A_i \cdot Mod_i$$


$$A_i = \langle E, Mod_i \rangle$$



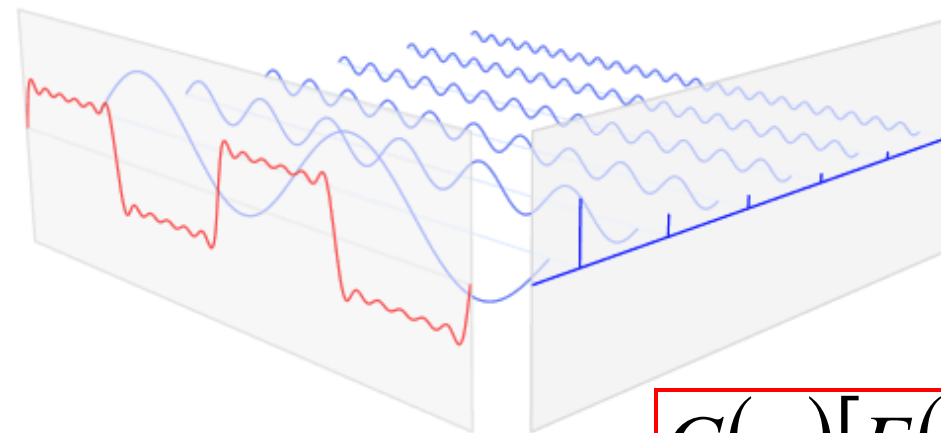
# Mathematical modeling

- particular cases where analytical solution exists
  - harmonic signals, Fourier Transform, frequency spectrum

$$X = X_0 e^{j \cdot \omega \cdot t} \quad \frac{\partial X}{\partial t} = j \cdot \omega \cdot X \quad g(\omega) = \int_{-\infty}^{\infty} f(t) \cdot e^{-j\omega t} dt \quad f(t) = \int_{-\infty}^{\infty} g(\omega) \cdot e^{j\omega t} d\omega$$




$$G(\omega)[F(\omega)]$$

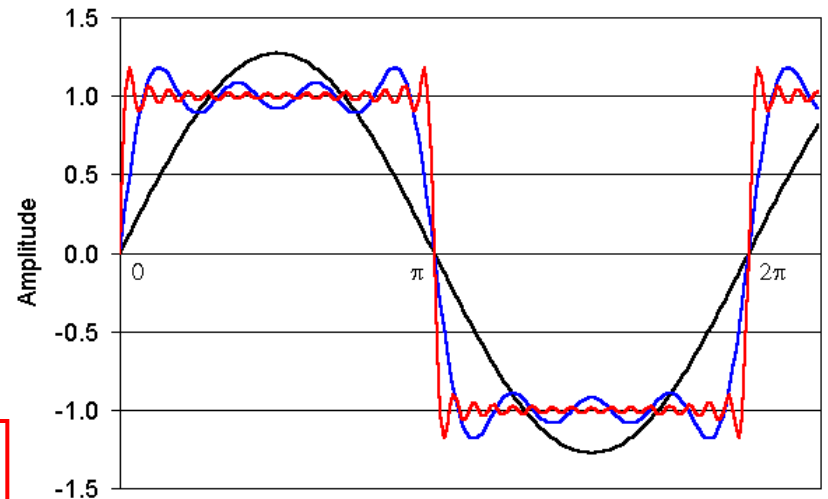

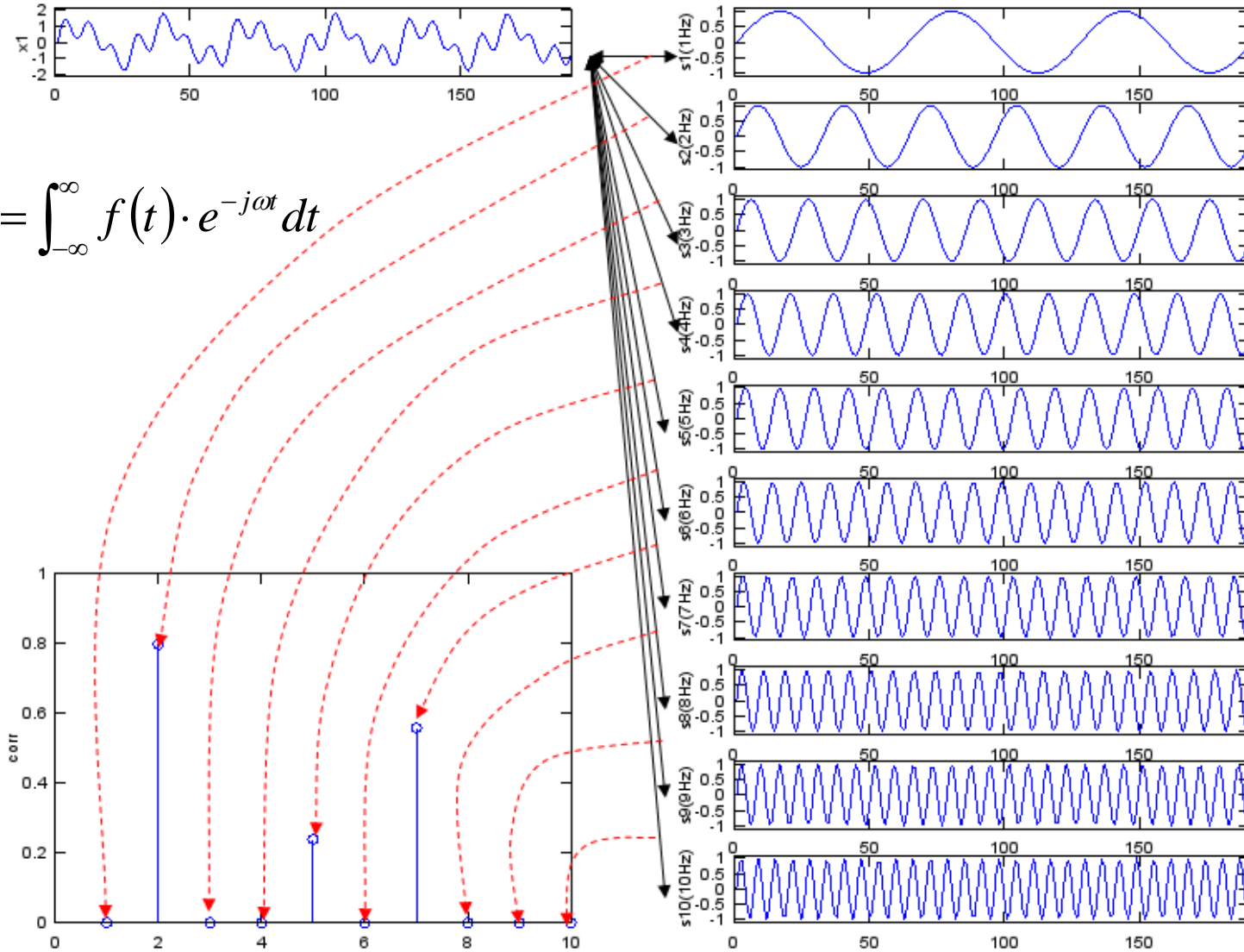
# Mathematical modeling

$$g(\omega) = \int_{-\infty}^{\infty} f(t) \cdot e^{-j\omega t} dt$$



# Mathematical modeling

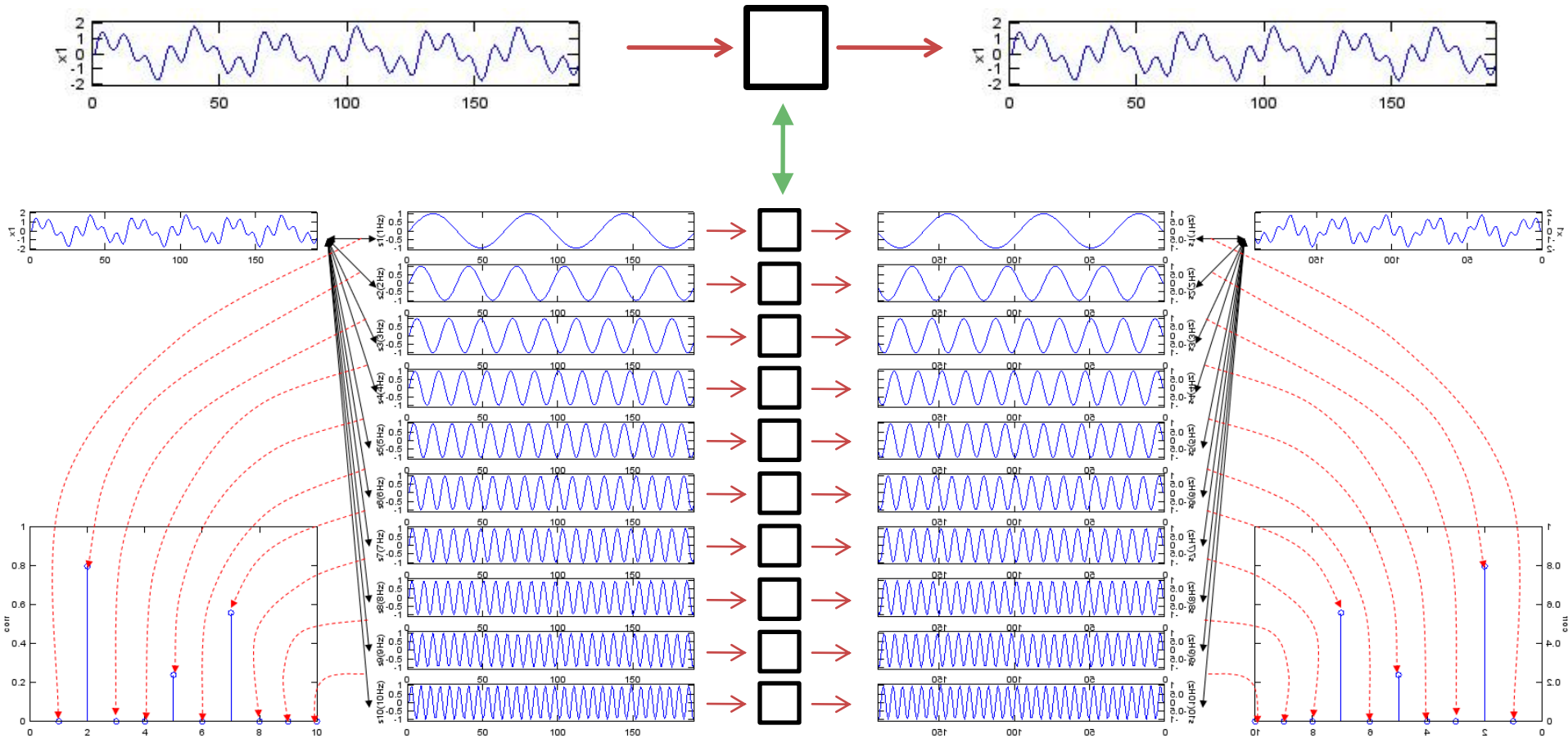

$$F(\omega) = \int_{-\infty}^{\infty} f(t) \cdot e^{-j\omega t} dt$$

$$G(\omega) [F(\omega)]$$

$$g(t) = \int_{-\infty}^{\infty} G(\omega) \cdot e^{j\omega t} d\omega$$

# Mathematical modeling

- particular cases where analytical solution exists

- wave in a single direction  $E^+ (E^+)$ ,  $E^- (E^-)$

- wave

- incident

$$E_y = E^+ \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t - \beta \cdot z)} + E^- \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t + \beta \cdot z)}$$


- reflected

$$E_{IN} = E_{1+} e^{-\gamma \cdot z} + E_{1-} e^{\gamma \cdot z} \longrightarrow \square \longrightarrow E_{OUT} = E_{2+} e^{-\gamma \cdot z} + E_{2-} e^{\gamma \cdot z}$$

- wave


- direct

- inverse

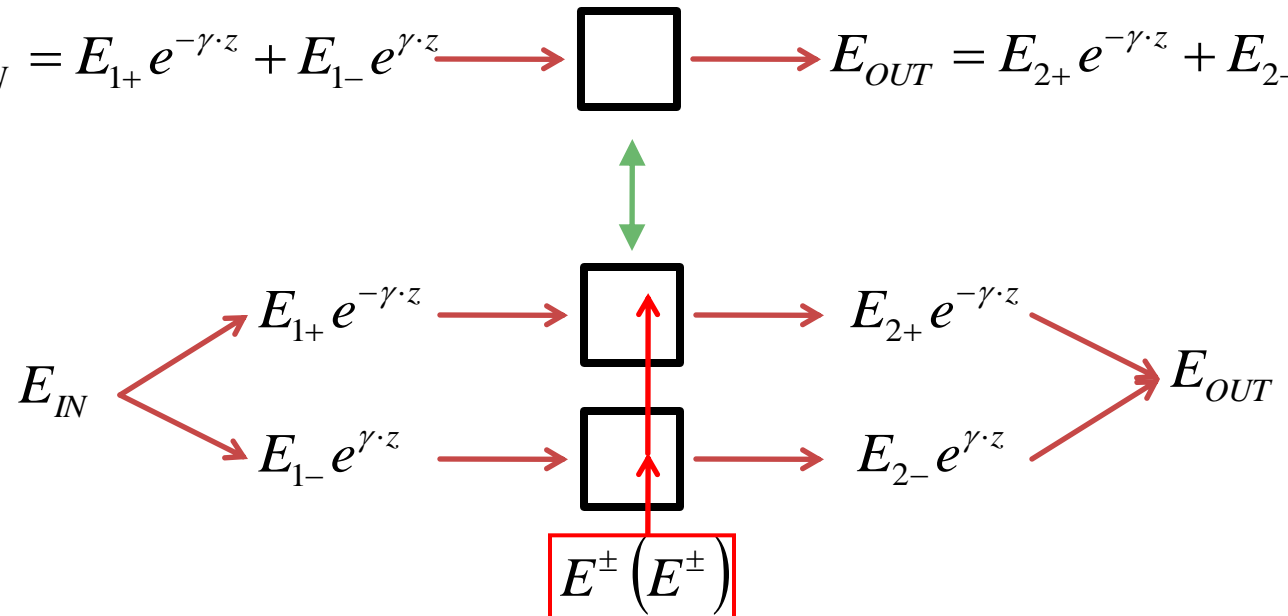

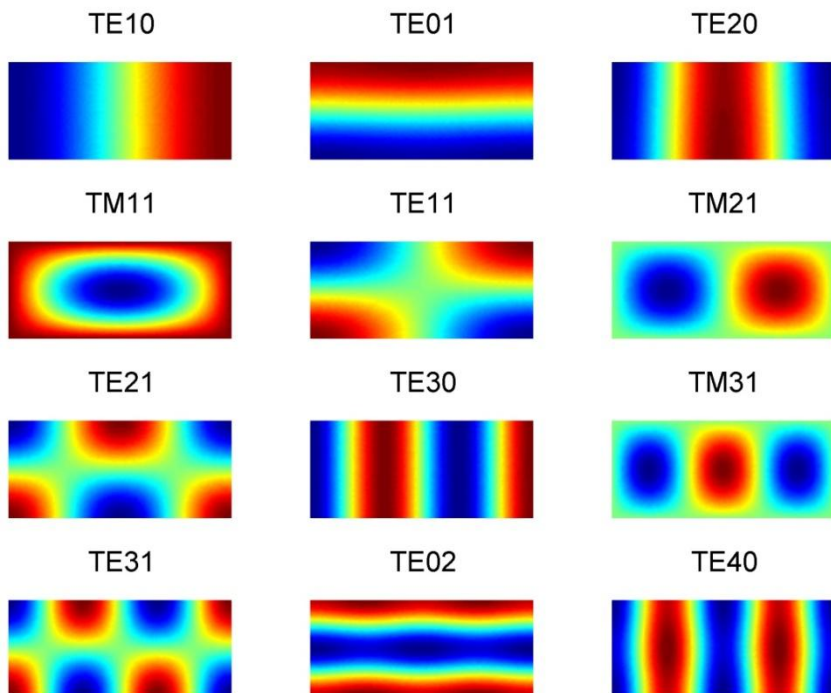
# Mathematical modeling



- particular cases where analytical solution exists
  - modes in delimited media  $B_i(A_i)$


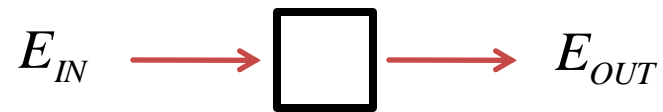
$$E = \sum_1^{\infty} A_i \cdot Mod_i \quad A_i = \langle E, Mod_i \rangle$$



$$A_i = \langle E_{IN}, Mod_i \rangle$$

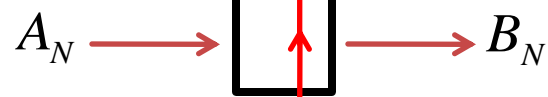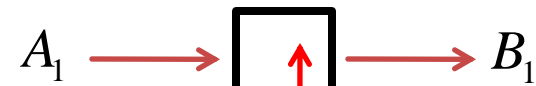



$$E_{OUT} = \sum_1^N B_i \cdot Mod_i$$

# TEM transmission lines

---

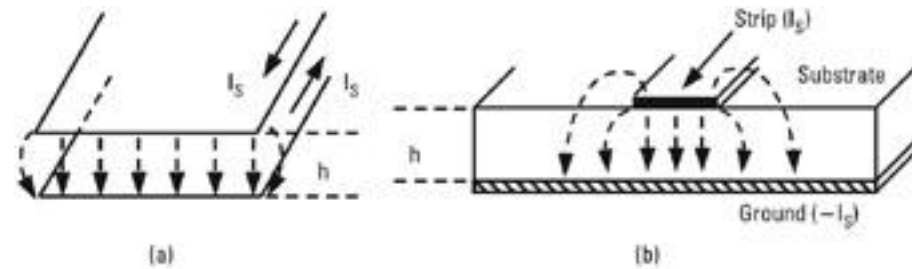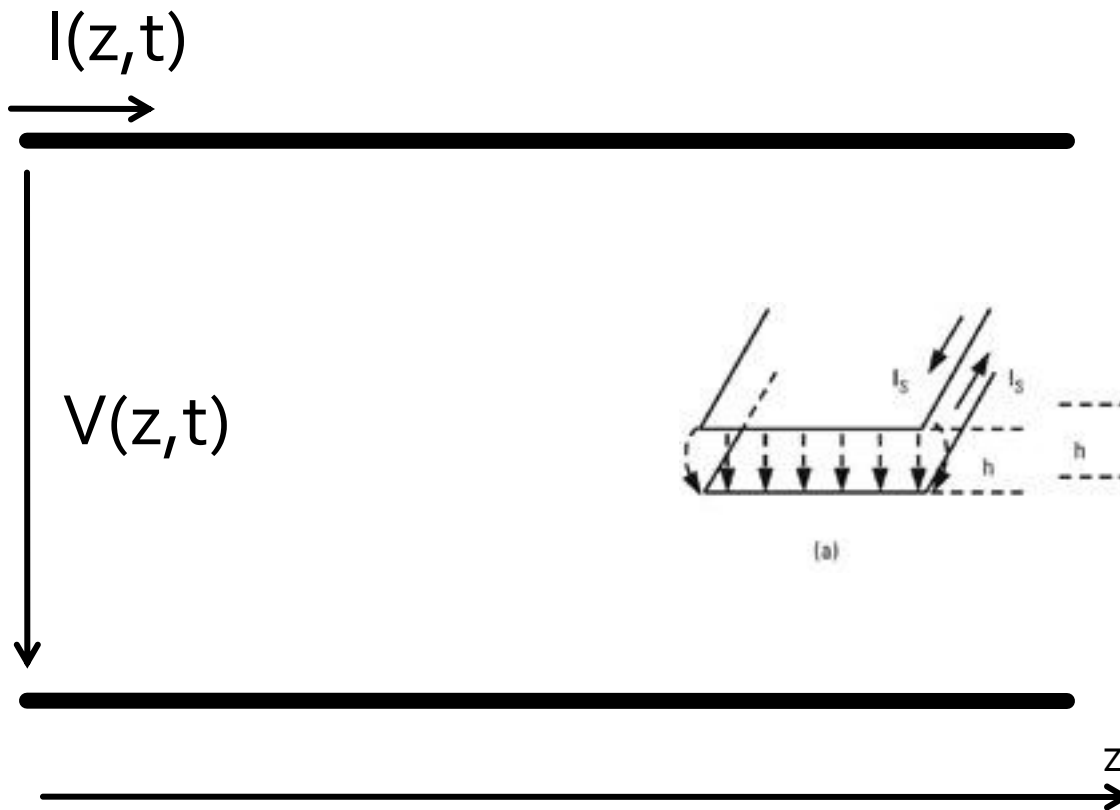
# Transmission line

- TEM wave propagation, at least two conductors


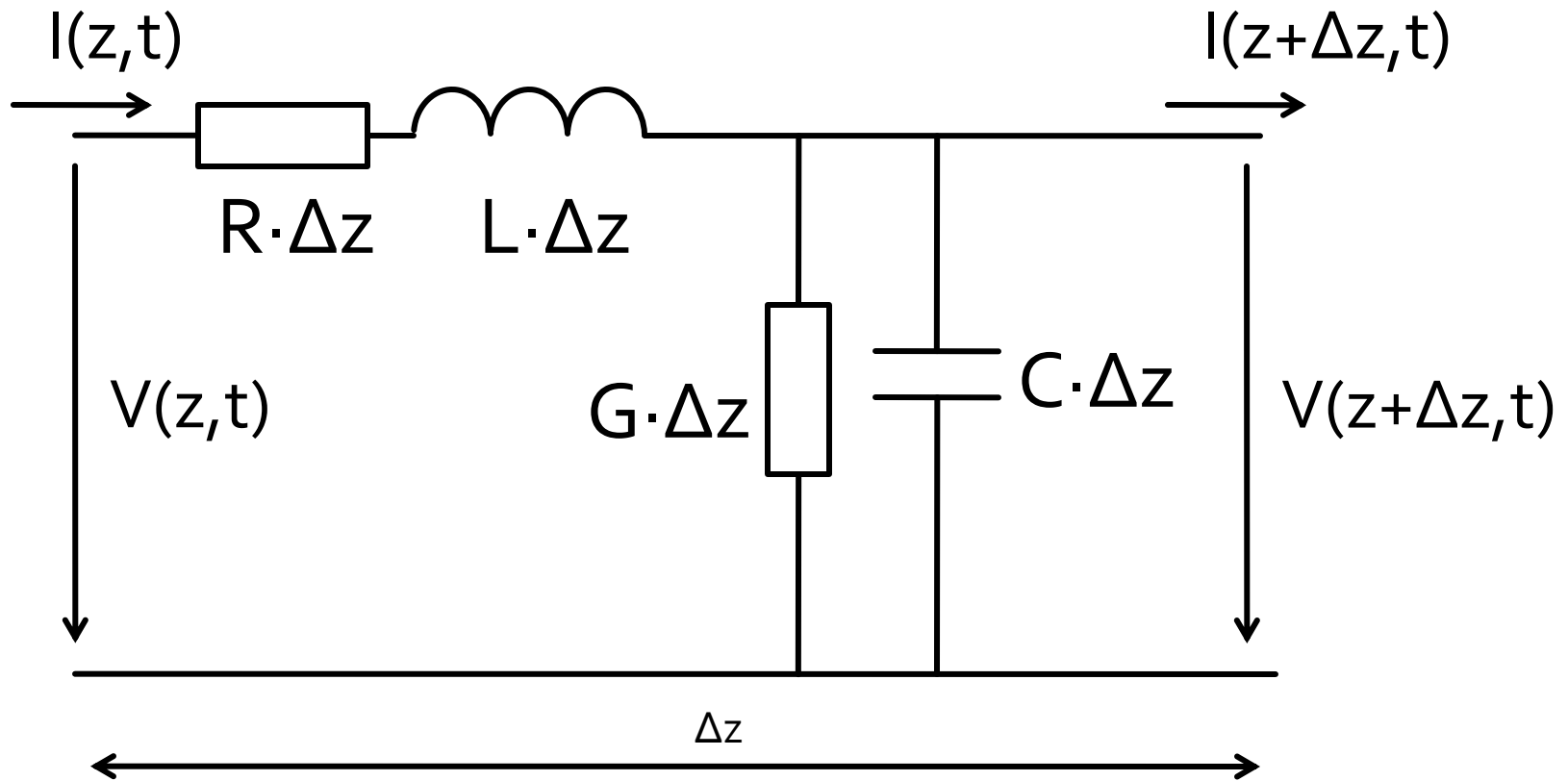
# Transmission line equivalent model

- TEM wave propagation, at least two conductors





# Telegrapher equations

- time domain

$$\frac{\partial v(z,t)}{\partial z} = -R \cdot i(z,t) - L \cdot \frac{\partial i(z,t)}{\partial t} \quad \text{K II}$$

$$\frac{\partial i(z,t)}{\partial z} = -G \cdot v(z,t) - C \cdot \frac{\partial v(z,t)}{\partial t} \quad \text{K I}$$

- harmonic signals

$$\frac{dV(z)}{dz} = -(R + j \cdot \omega \cdot L) \cdot I(z)$$

$$\frac{dI(z)}{dz} = -(G + j \cdot \omega \cdot C) \cdot V(z)$$


$$\left/ \frac{d}{dz} (\dots) \right.$$

# Solution

$$\frac{d^2V(z)}{dz^2} - \gamma^2 \cdot V(z) = 0$$

$$\frac{d^2I(z)}{dz^2} - \gamma^2 \cdot I(z) = 0$$

$$\gamma = \alpha + j \cdot \beta = \sqrt{(R + j \cdot \omega \cdot L) \cdot (G + j \cdot \omega \cdot C)}$$


$$\nabla^2 E - \gamma^2 E = 0$$

$$\nabla^2 H - \gamma^2 H = 0$$

$$E_y = E_+ e^{-\gamma \cdot z} + E_- e^{\gamma \cdot z}$$

$$\gamma^2 = -\omega^2 \epsilon \mu + j \omega \mu \sigma$$

# Solutions

$$\left\{ \begin{array}{l} V(z) = V_0^+ e^{-\gamma \cdot z} + V_0^- e^{\gamma \cdot z} \\ I(z) = I_0^+ e^{-\gamma \cdot z} + I_0^- e^{\gamma \cdot z} \end{array} \right. \quad \gamma = \alpha + j \cdot \beta = \sqrt{(R + j \cdot \omega \cdot L) \cdot (G + j \cdot \omega \cdot C)}$$

$$V(z) = V_0^+ e^{-\gamma \cdot z} + V_0^- e^{\gamma \cdot z}$$

$$\frac{dV(z)}{dz} = -(R + j \cdot \omega \cdot L) \cdot I(z)$$

$$Z_0 \equiv \frac{R + j \cdot \omega \cdot L}{\gamma} = \sqrt{\frac{R + j \cdot \omega \cdot L}{G + j \cdot \omega \cdot C}}$$

$$\frac{V_0^+}{I_0^+} = Z_0 = -\frac{V_0^-}{I_0^-}$$

$$I(z) = \frac{\gamma}{R + j \cdot \omega \cdot L} (V_0^+ e^{-\gamma \cdot z} - V_0^- e^{\gamma \cdot z})$$

- Characteristic impedance of the line

$$\lambda = \frac{2\pi}{\beta} \quad v_f = \frac{\omega}{\beta} = \lambda \cdot f$$

# The lossless line

- $R=G=0$

$$\gamma = \alpha + j \cdot \beta = \sqrt{(R + j \cdot \omega \cdot L) \cdot (G + j \cdot \omega \cdot C)} = j \cdot \omega \cdot \sqrt{L \cdot C}$$

$$\alpha = 0 \quad ; \quad \beta = \omega \cdot \sqrt{L \cdot C}$$

$$Z_0 = \sqrt{\frac{R + j \cdot \omega \cdot L}{G + j \cdot \omega \cdot C}} = \sqrt{\frac{L}{C}}$$

- $Z_0$  is **real**


$$V(z) = V_0^+ e^{-j \cdot \beta \cdot z} + V_0^- e^{j \cdot \beta \cdot z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j \cdot \beta \cdot z} - \frac{V_0^-}{Z_0} e^{j \cdot \beta \cdot z}$$

$$\lambda = \frac{2\pi}{\omega \cdot \sqrt{LC}}$$

$$v_f = \frac{1}{\sqrt{LC}}$$

# The lossless line

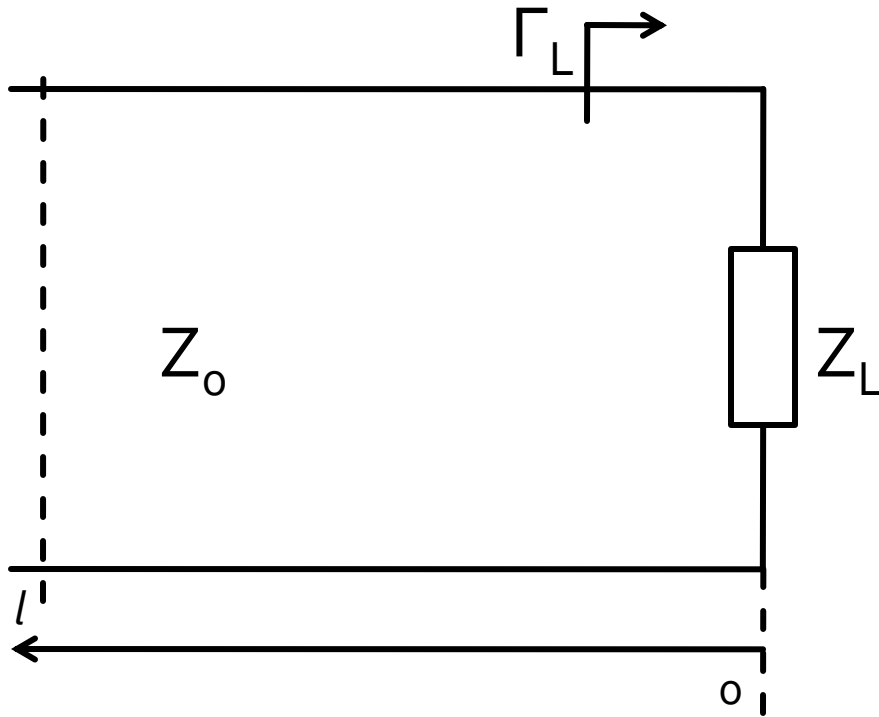

$$V(z) = V_0^+ e^{-j\beta \cdot z} + V_0^- e^{j\beta \cdot z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta \cdot z} - \frac{V_0^-}{Z_0} e^{j\beta \cdot z}$$

$$Z_L = \frac{V(0)}{I(0)} \quad Z_L = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \cdot Z_0$$

- voltage reflection coefficient

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

- $Z_0$  real

# The lossless line

- voltage reflection coefficient seen at the input of the line

$$V(z) = V_0^+ e^{-j\beta \cdot z} + V_0^- e^{j\beta \cdot z}$$

$$\Gamma = \Gamma(z) = \frac{V_0^-(z)}{V_0^+(z)}$$


$$V(0) = V_0^+ + V_0^- \quad \Gamma(0) = \Gamma_L = \frac{V_0^-}{V_0^+}$$

$$V(-l) = V_0^+ e^{j\beta \cdot l} + V_0^- e^{-j\beta \cdot l}$$

$$\Gamma(-l) = \Gamma_{IN} = \frac{V_0^- \cdot e^{-j\beta \cdot l}}{V_0^+ \cdot e^{j\beta \cdot l}} = \Gamma(0) \cdot e^{-2j\beta \cdot l}$$

$$|\Gamma(-l)| = |\Gamma(0)| \cdot |e^{-2j\beta \cdot l}| = |\Gamma(0)|$$
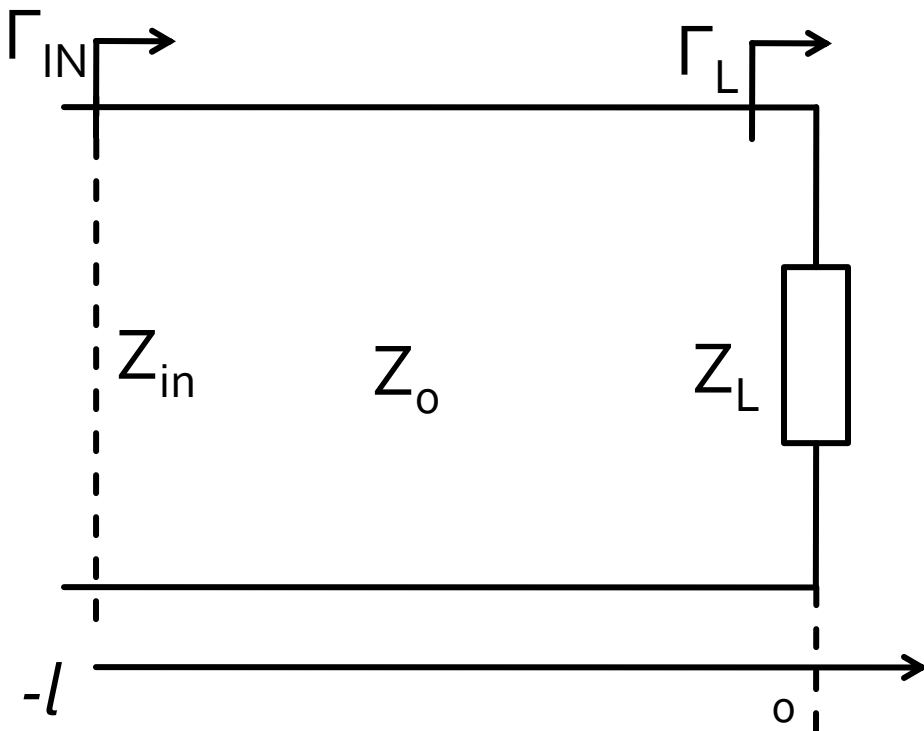
$$\Gamma(-l) = \Gamma(0) \cdot e^{-2j\beta \cdot l}$$



# The lossless line

$$V(z) = V_0^+ \cdot (e^{-j\beta \cdot z} + \Gamma \cdot e^{j\beta \cdot z}) \quad I(z) = \frac{V_0^+}{Z_0} \cdot (e^{-j\beta \cdot z} - \Gamma \cdot e^{j\beta \cdot z})$$


- time-average Power flow along the line

$$P_{\text{avg}} = \frac{1}{2} \text{Re}\{V(z)I(z)^*\} = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \text{Re}\{1 - \Gamma^* e^{-2j\beta z} + \Gamma e^{2j\beta z} - |\Gamma|^2\}$$

$$P_{\text{avg}} = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} (1 - |\Gamma|^2)$$

- Total power delivered to the load = Incident power – “Reflected” power
- Return “Loss” [dB]  $RL = -20 \log |\Gamma| \text{ dB}$ .

# The lossless line

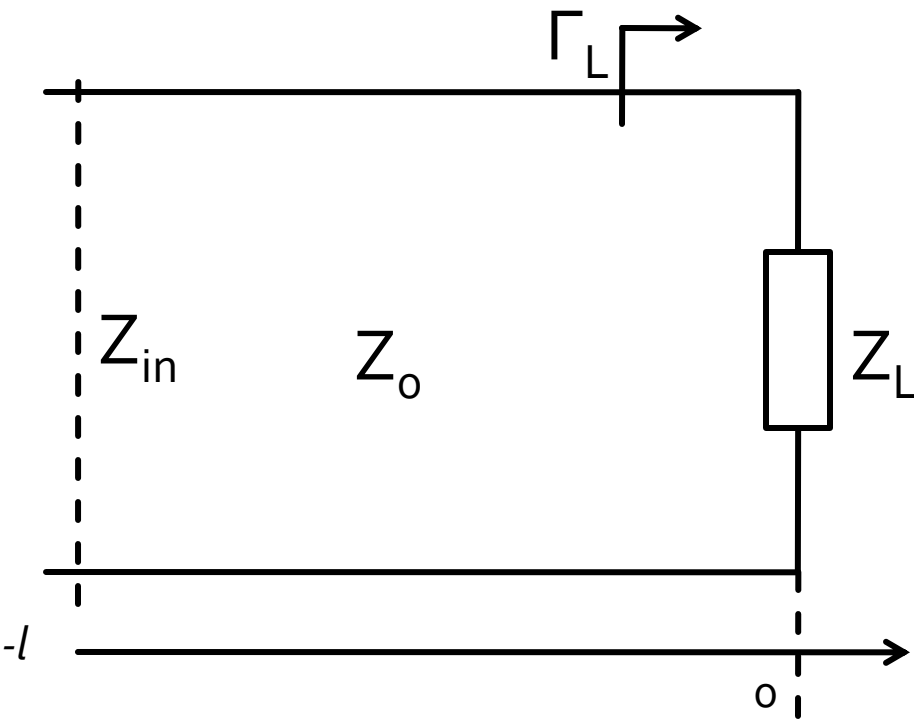

$$V(-l) = V_0^+ e^{j\beta \cdot l} + V_0^- e^{-j\beta \cdot l}$$

$$I(-l) = \frac{V_0^+}{Z_0} e^{j\beta \cdot l} - \frac{V_0^-}{Z_0} e^{-j\beta \cdot l}$$

$$Z_{in} = \frac{V(-l)}{I(-l)} \quad Z_{in} = Z_0 \cdot \frac{1 + \Gamma \cdot e^{-2j\beta \cdot l}}{1 - \Gamma \cdot e^{-2j\beta \cdot l}}$$

- the **input impedance** seen looking toward the load

$$Z_{in} = Z_0 \cdot \frac{(Z_L + Z_0) \cdot e^{j\beta \cdot l} + (Z_L - Z_0) \cdot e^{-j\beta \cdot l}}{(Z_L + Z_0) \cdot e^{j\beta \cdot l} - (Z_L - Z_0) \cdot e^{-j\beta \cdot l}}$$

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan(\beta \cdot l)}{Z_0 + j \cdot Z_L \cdot \tan(\beta \cdot l)}$$




# The lossless line

- the **input impedance** seen looking toward the load

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$
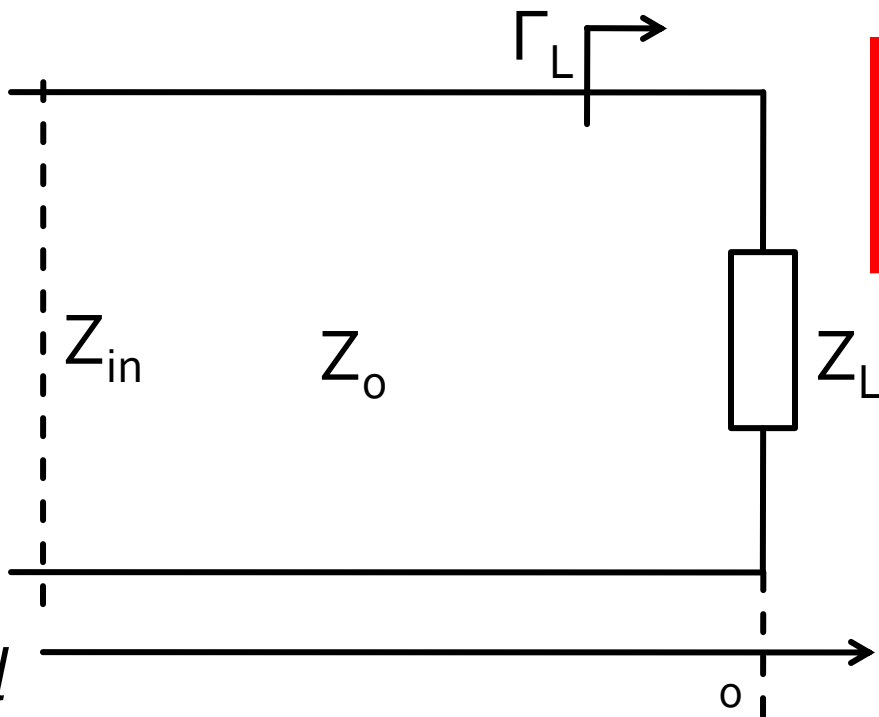
# The lossless line


- input impedance of a length  $l$  of transmission line with characteristic impedance  $Z_0$ , loaded with an arbitrary impedance  $Z_L$



$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$
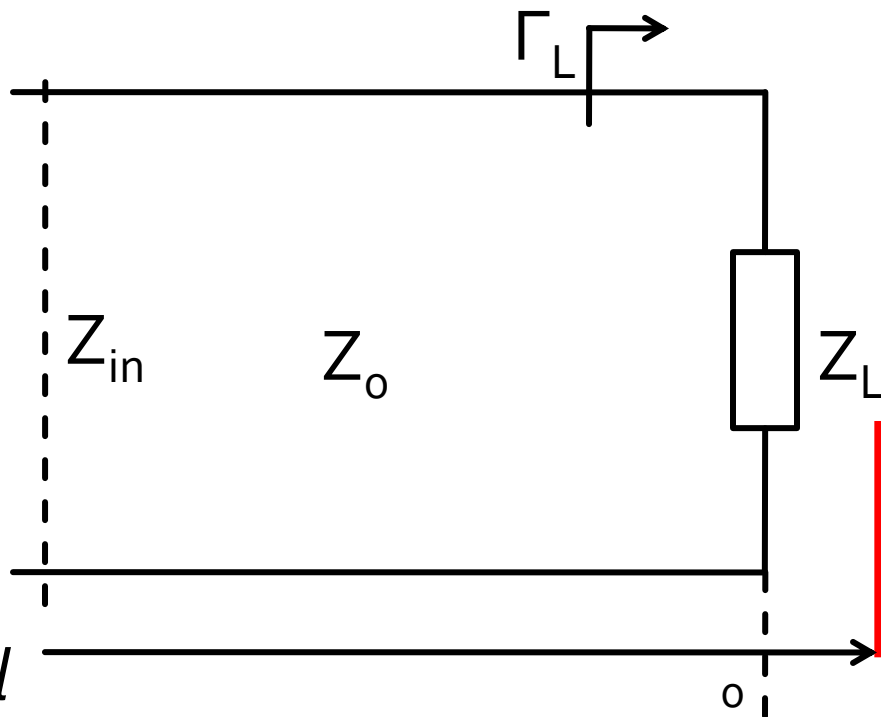
# The lossless line

- input impedance is **frequency dependent** through  $\beta \cdot l$



$$v_f = \frac{\omega}{\beta} = \lambda \cdot f \quad \lambda = \frac{2\pi}{\beta}$$
$$\beta \cdot l = \frac{2\pi}{\lambda} \cdot l = \frac{2\pi \cdot f}{v_f} \cdot l = \frac{2\pi \cdot l}{v_f} \cdot f$$

frequency dependence is **periodical**, imposed by the tan trigonometric function

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$


# The lossless line, special cases

- $l = k \cdot \lambda/2$      $\beta \cdot l = \frac{2\pi}{\lambda} \cdot l = k \cdot \pi$      $\tan \beta \cdot l = 0$

$$Z_{in} = Z_0$$

- $l = \lambda/4 + k \cdot \lambda/2$      $\tan \beta \cdot l \rightarrow \infty$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

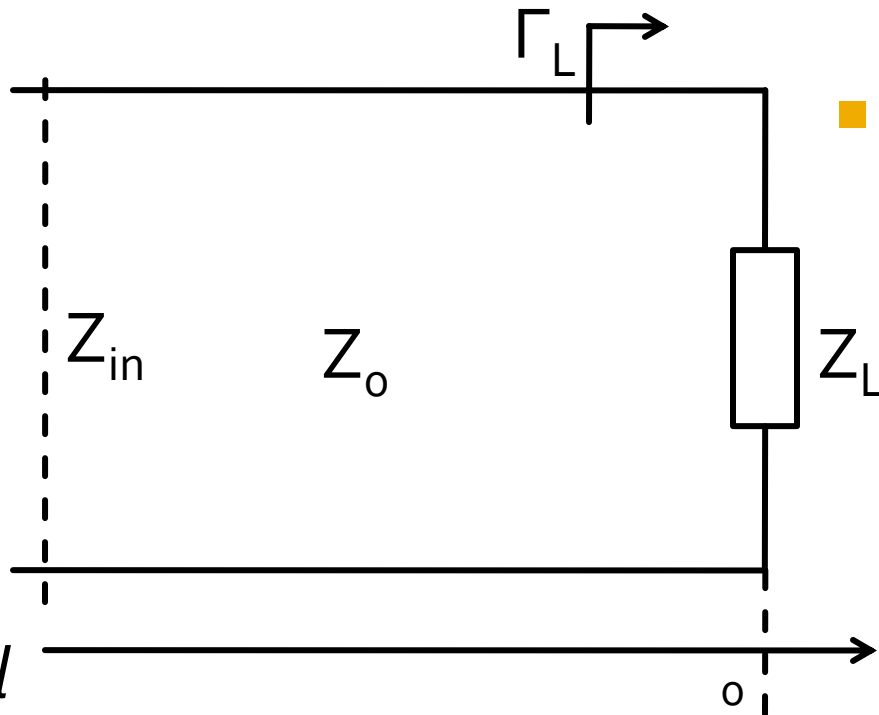

- quarter-wave transformer




$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

# Short-circuited transmission line

- $Z_L = 0$
- purely imaginary for any length  $l$ 
  - +/-  $\rightarrow$  depending on  $l$  value

$$Z_{in} = j \cdot Z_0 \cdot \tan \beta \cdot l$$
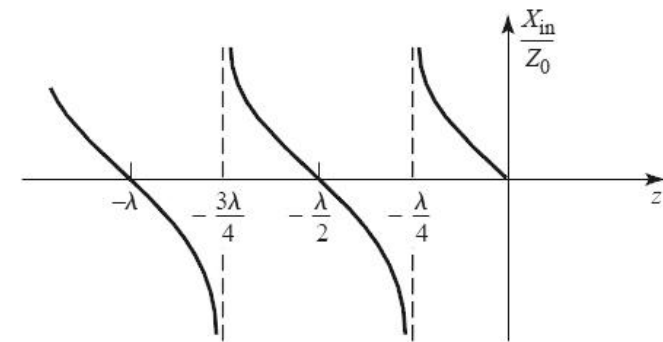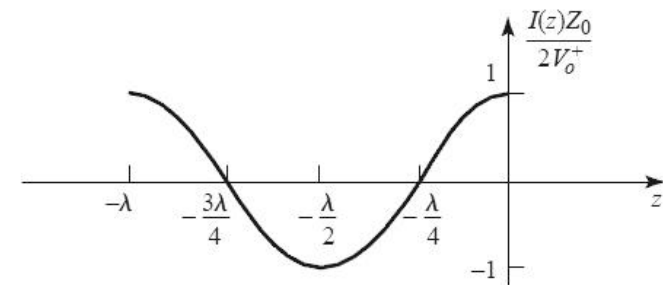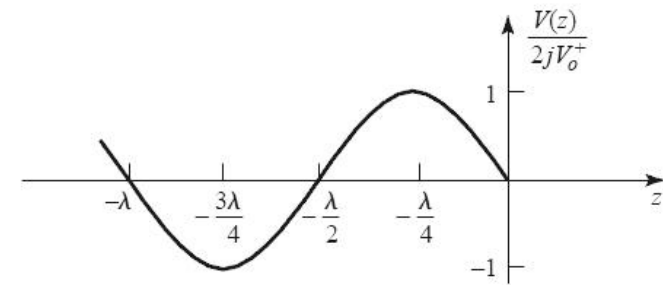
$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan(\beta \cdot l)}{Z_0 + j \cdot Z_L \cdot \tan(\beta \cdot l)}$$






# Open-circuited transmission line

- $Z_L = \infty \rightarrow 1/Z_L = 0$
- purely imaginary for any length  $l$ 
  - +/-  $\rightarrow$  depending on  $l$  value

$$Z_{in} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$
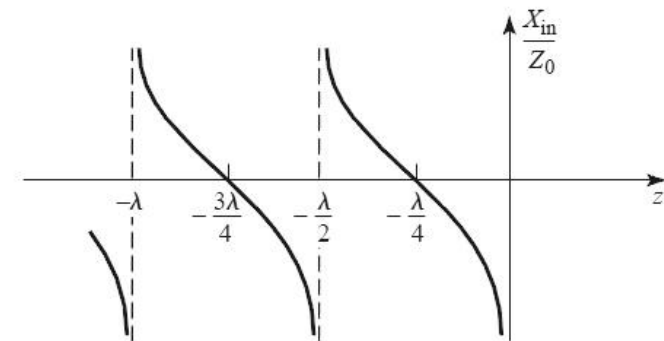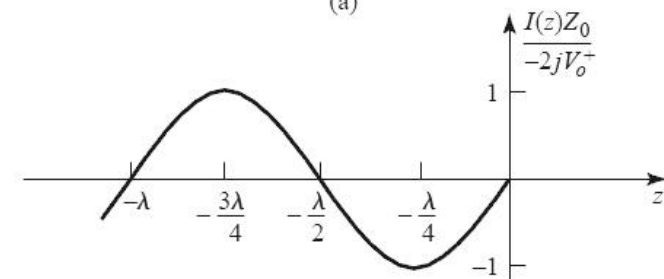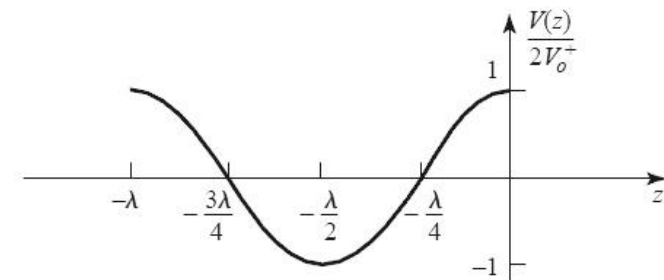
$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan(\beta \cdot l)}{Z_0 + j \cdot Z_L \cdot \tan(\beta \cdot l)}$$



(c)

# Voltage standing wave ratio

$$V(z) = V_0^+ \cdot (e^{-j\beta \cdot z} + \Gamma \cdot e^{j\beta \cdot z}) \quad |V(z)| = |V_0^+| \cdot |e^{-j\beta \cdot z}| \cdot |1 + \Gamma \cdot e^{2j\beta \cdot z}| \quad \Gamma = |\Gamma| \cdot e^{j\theta}$$

$$|V(z)| = |V_0^+| \cdot |1 + |\Gamma| \cdot e^{\theta + 2j\beta \cdot z}|$$

maximum magnitude value for  $e^{\theta + 2j\beta \cdot z} = 1$

$$V_{\max} = |V_0^+| \cdot (1 + |\Gamma|)$$

minimum magnitude value for  $e^{\theta + 2j\beta \cdot z} = -1$

$$V_{\min} = |V_0^+| \cdot (1 - |\Gamma|)$$


- SWR is defined as the ratio between maximum and minimum

- (Voltage) Standing Wave Ratio

$$VSWR = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

- real number  $1 \leq VSWR < \infty$
- a measure of the mismatch (SWR = 1 means a matched line)

# The lossless line +/-

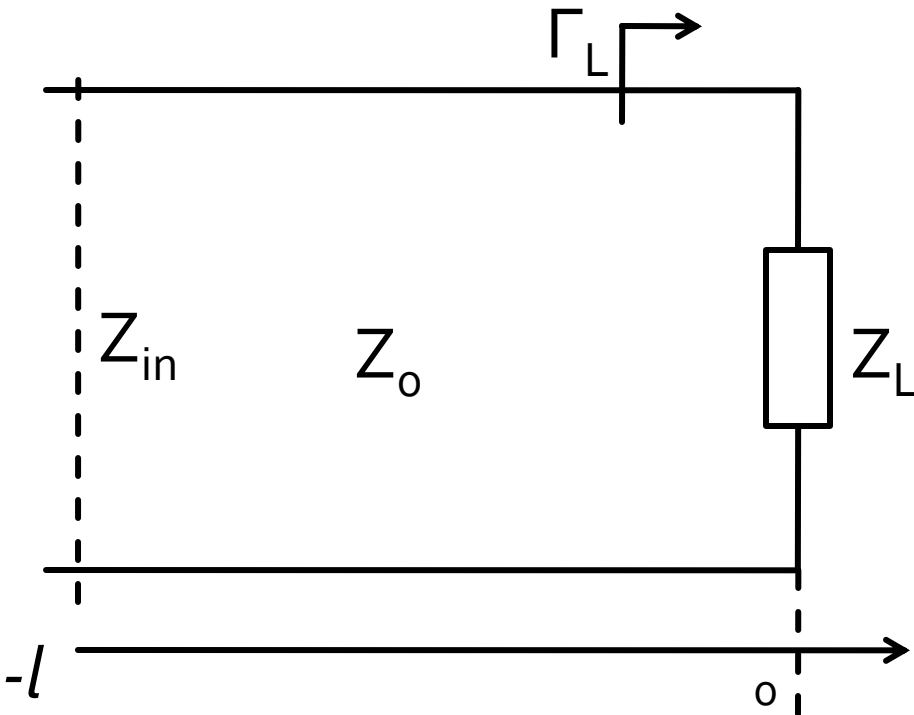

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

$$V(z) = V_0^+ e^{-\gamma \cdot z} + V_0^- e^{\gamma \cdot z}$$

$$I(z) = I_0^+ e^{-\gamma \cdot z} + I_0^- e^{\gamma \cdot z}$$

$$\Gamma(-l) = \Gamma(0) \cdot e^{-2j \cdot \beta \cdot l}$$

$$\Gamma_{in} = \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}$$




Impedance Matching

# Laboratory no. 1

---
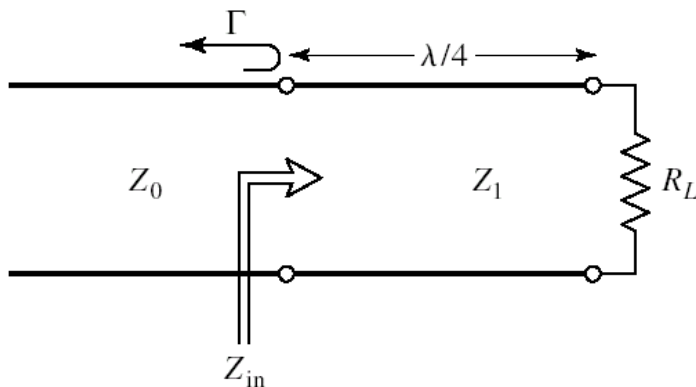
# The quarter-wave transformer

- Feed line – input line with characteristic impedance  $Z_0$
- Real load impedance  $R_L$
- We desire matching the load to the fider with a second line with the length  $\lambda/4$  and characteristic impedance  $Z_1$




$$Z_{in} = Z_1 \frac{1 + \Gamma e^{-2j\beta l}}{1 - \Gamma e^{-2j\beta l}}$$

$$\Gamma_o = \frac{V_0^-}{V_0^+} = \frac{R_L - Z_1}{R_L + Z_1}$$

$$Z_{in} = Z_1 \frac{R_L + jZ_1 \tan(\beta l)}{Z_1 + jR_L \tan(\beta l)}$$

# The quarter-wave transformer

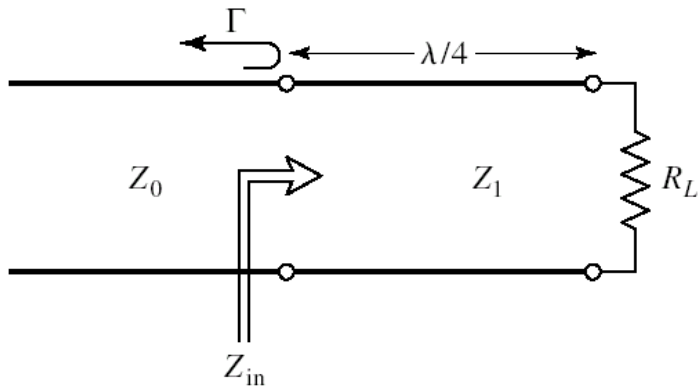

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$\beta \cdot l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}$$


$$Z_{in} = \frac{Z_1^2}{R_L}$$

$$\Gamma_{in} = \frac{Z_1^2 - Z_0 \cdot R_L}{Z_1^2 + Z_0 \cdot R_L} \quad \Gamma_{in} = 0 \quad Z_1 = \sqrt{Z_0 R_L}$$

- In the feed line ( $Z_0$ ) we have only progressive wave
- In the quarter-wave line ( $Z_1$ ) we have standing waves
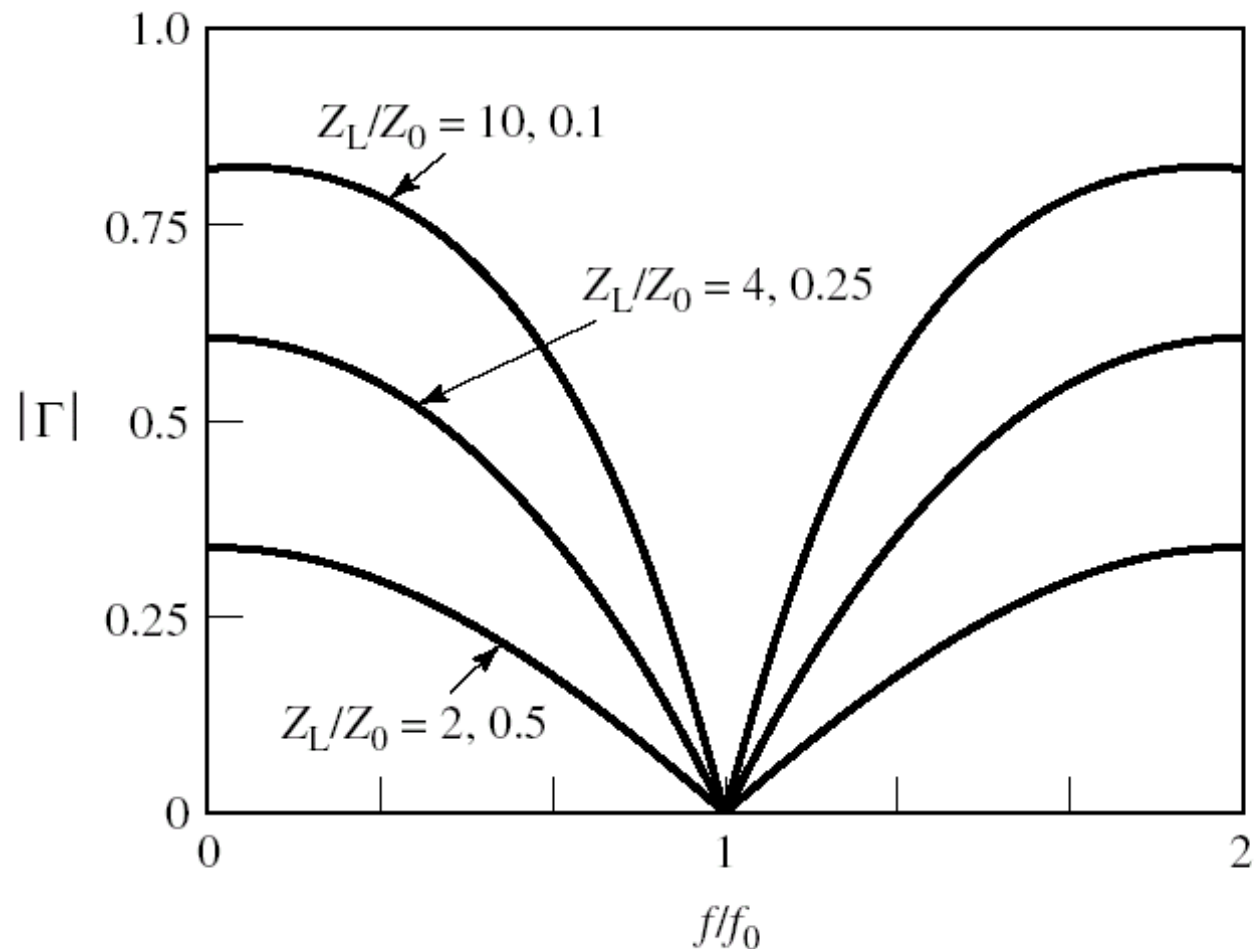
# Frequency response


- Bandwidth depends on the initial mismatch



increased bandwidth  
for smaller load  
mismatches

# Simulation

## ■ ADS Simulation

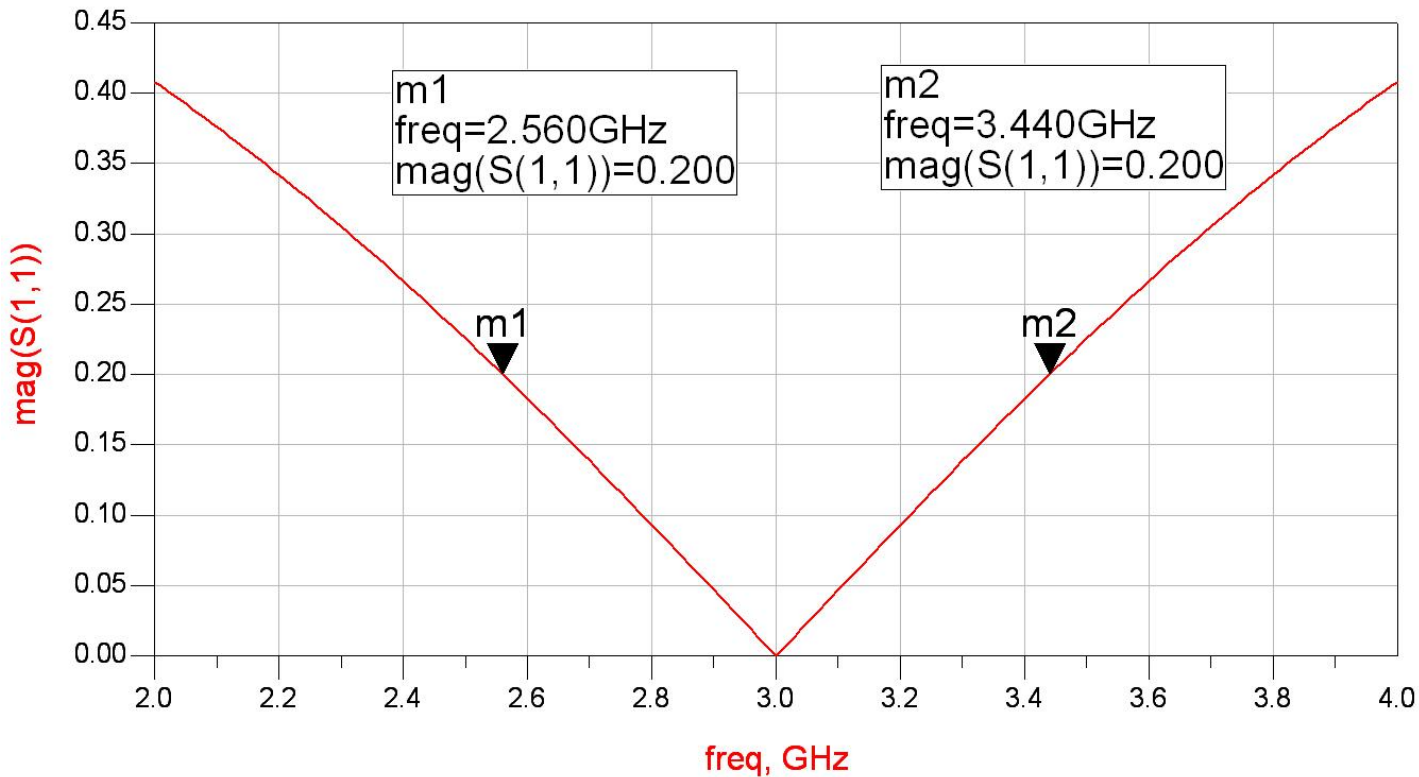


$$\Delta f = 0.88 \text{GHz}$$

$$|\Gamma(3\text{GHz})| = 3 \cdot 10^{-5}$$

$$\frac{\Delta f}{f_0} = \frac{0.88}{3} = 0.2933$$


# Full bandwidth simulation

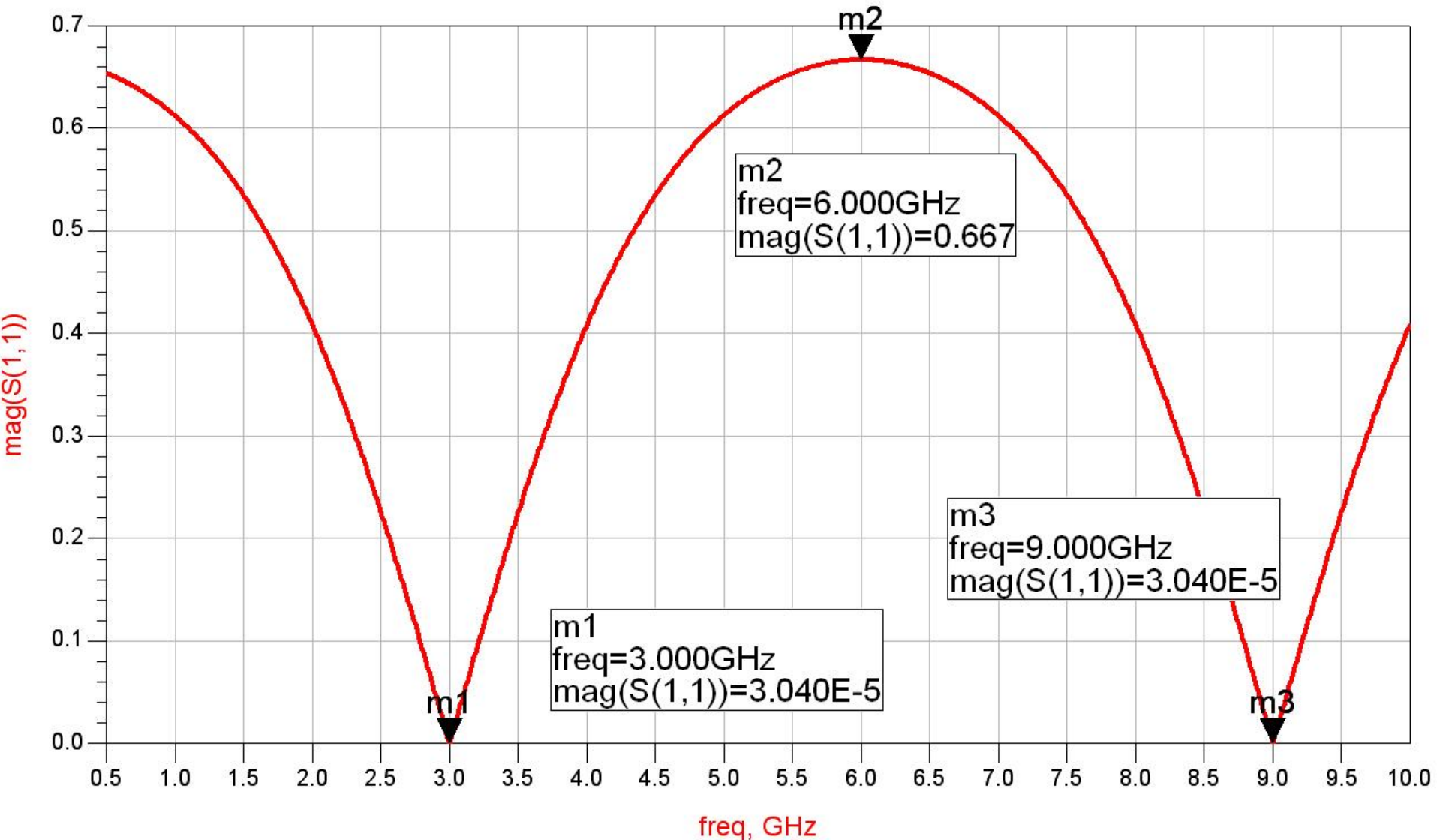

# Multisection Impedance Transformer

- The quarter-wave transformer can match any real load to any feed line impedance
- If a greater bandwidth for the match is required we must use multiple sections of transmission lines transformers:
  - binomial
  - Chebyshev

# Multisection transformers

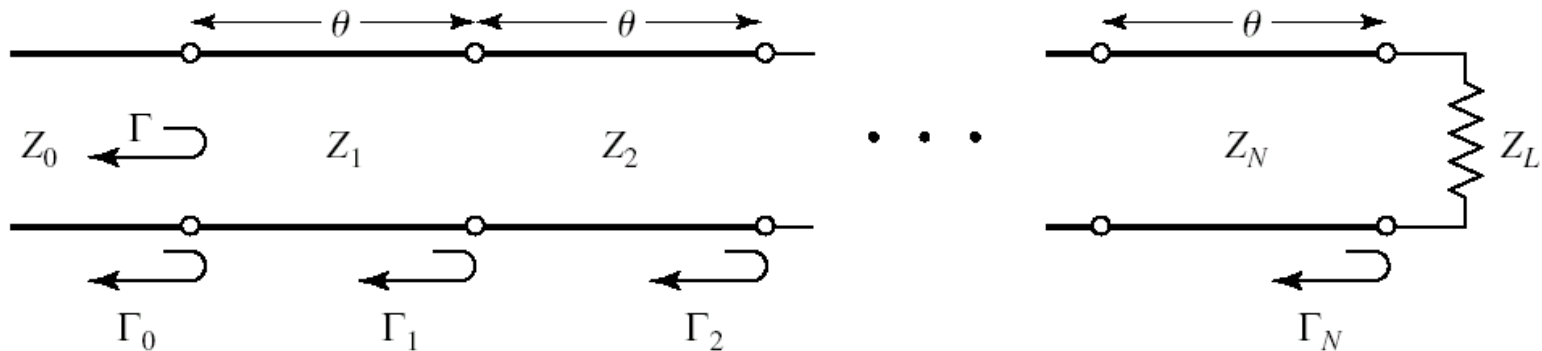

- We also assume that all impedances **increase or decrease monotonically** across the transformer
- This implies that all reflection coefficients will be real and of the same sign
- Previously, 1 section  $\Gamma \cong \Gamma_1 + \Gamma_3 \cdot e^{-2j\theta} \Rightarrow$

$$\Gamma(\theta) = \Gamma_0 + \Gamma_1 \cdot e^{-2j\theta} + \Gamma_2 \cdot e^{-4j\theta} + \dots + \Gamma_N \cdot e^{-2jN\theta}$$

$$\Gamma_1 = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$


$$\Gamma_n = \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n}$$

$n = 1, N-1$

$$\Gamma_N = \frac{Z_L - Z_N}{Z_L + Z_N}$$




# Bandwidth / Binomial

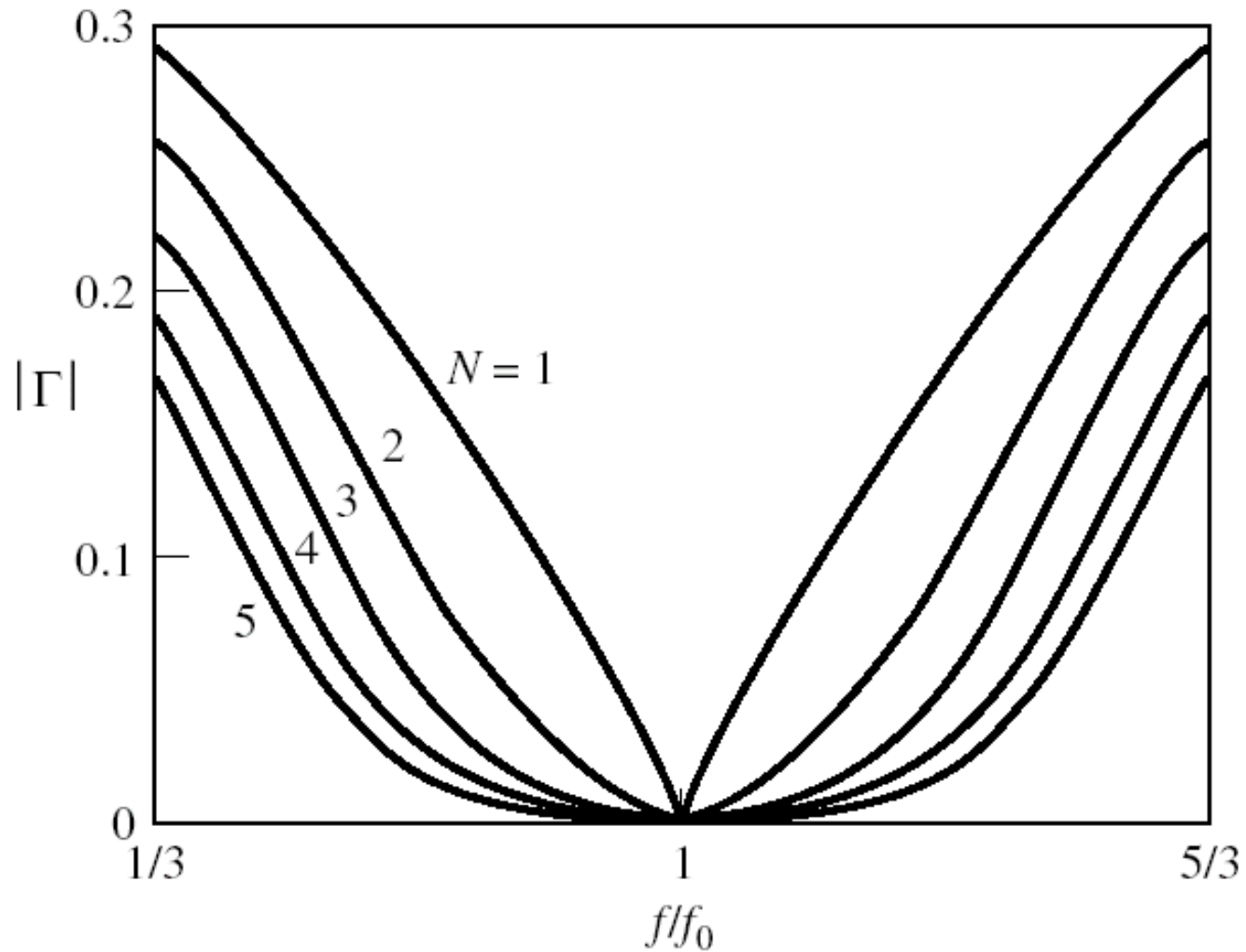

# Simulation


- Similarly Lab. 1

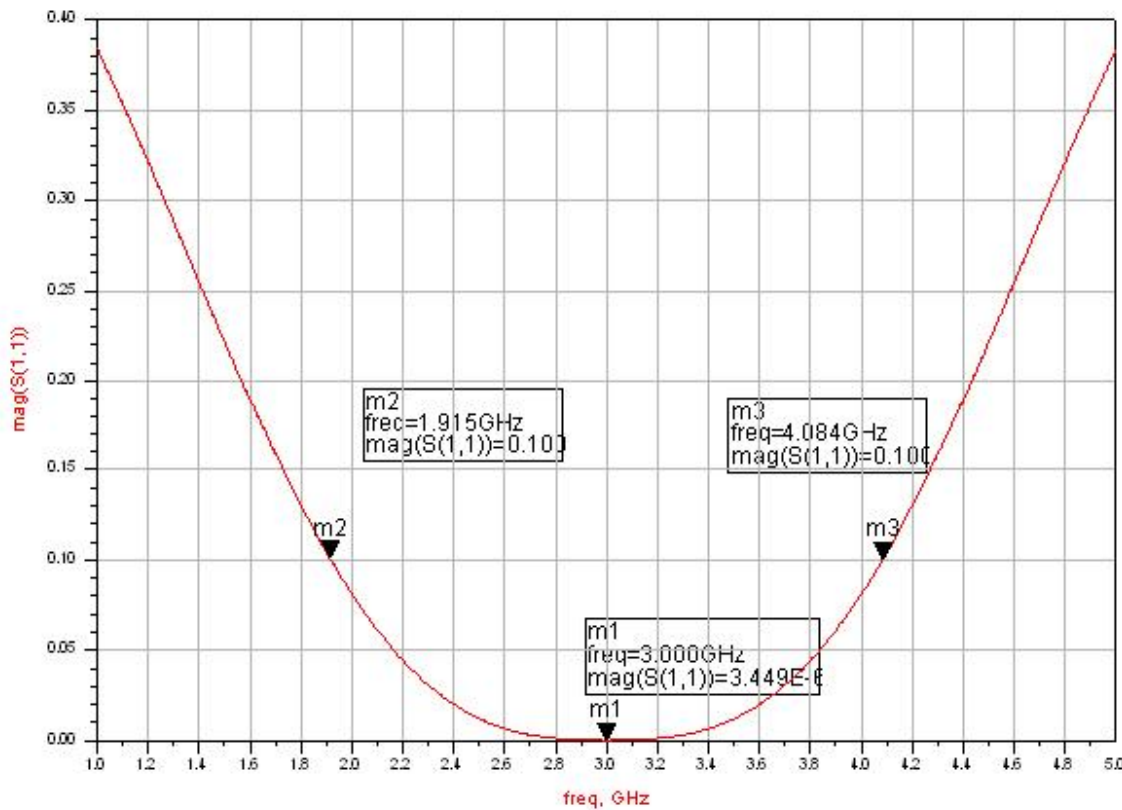

$$\Delta f = 2.169 \text{GHz}$$


$$|\Gamma(3\text{GHz})| = 3.5 \cdot 10^{-6}$$

# Bandwidth / Chebyshev

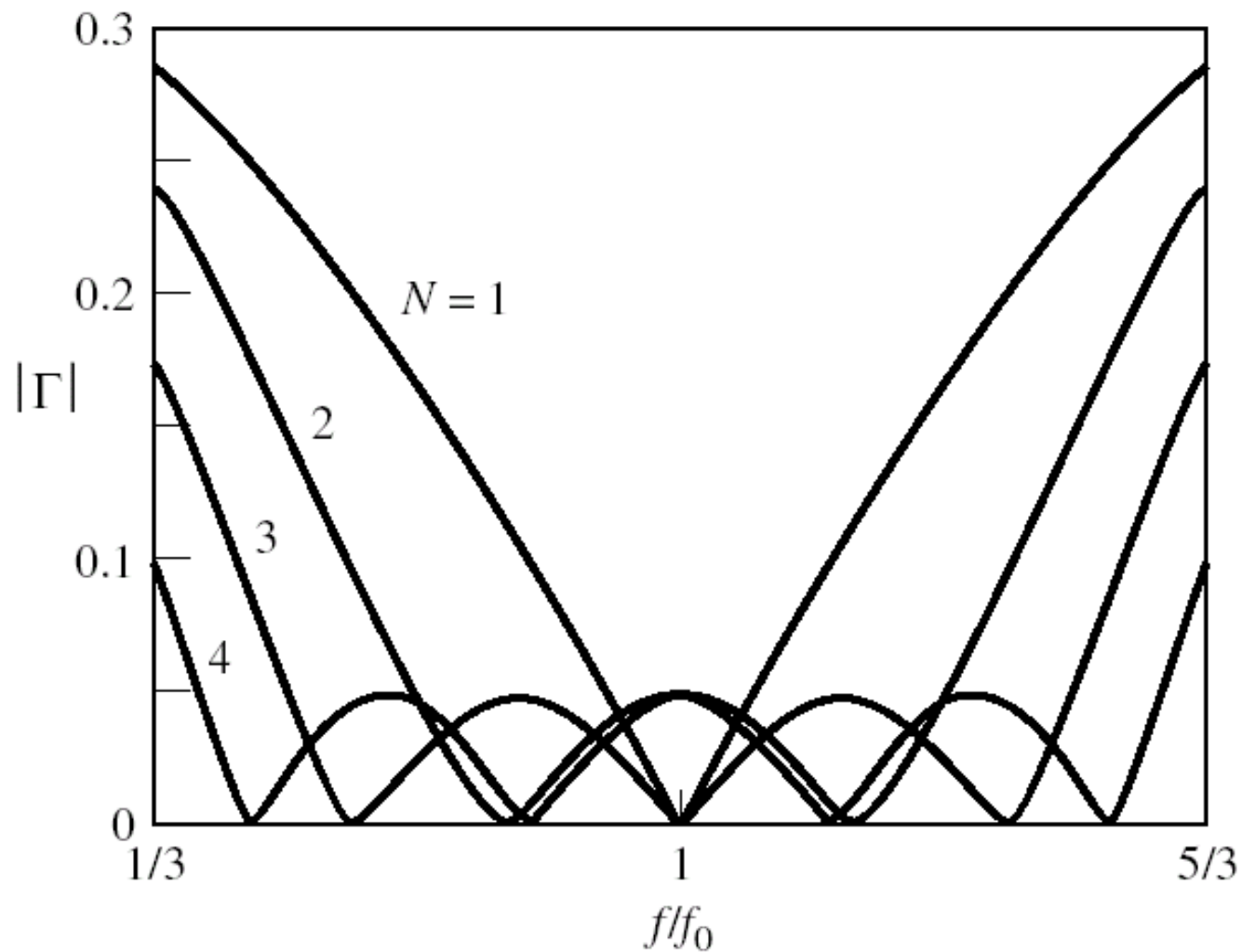

# Simulation

## ■ Similarly Lab. 1

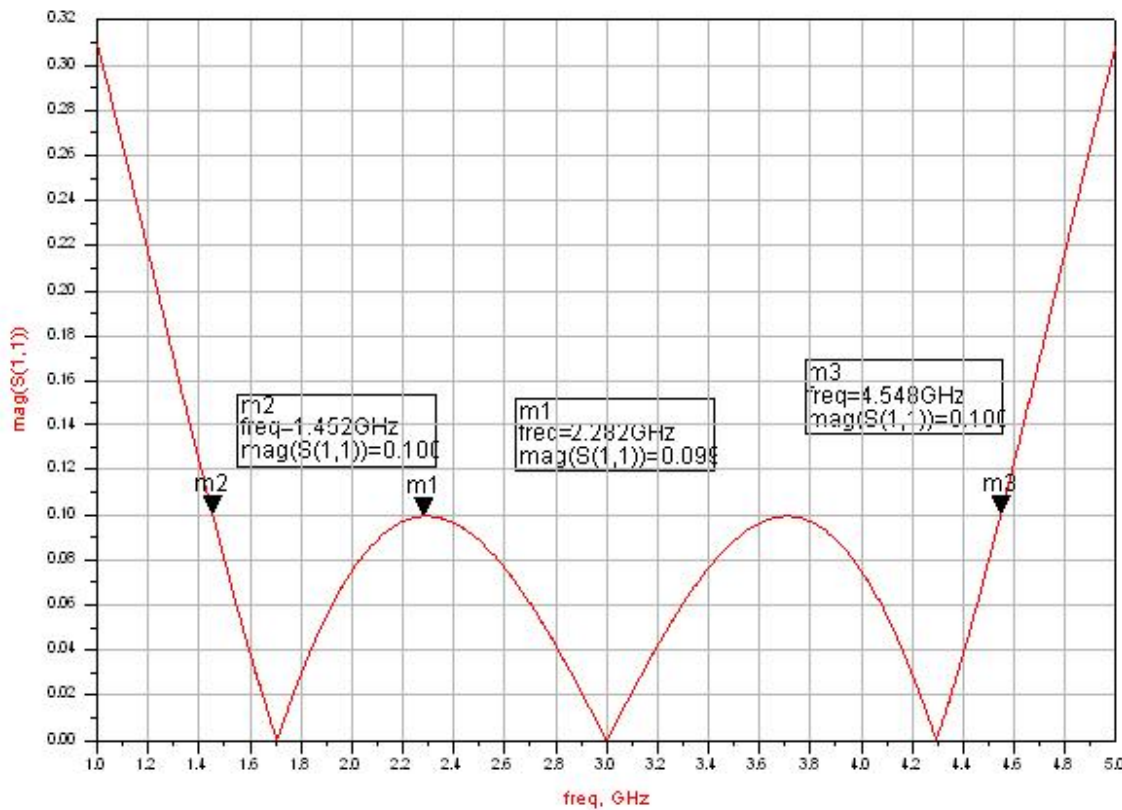

$$\Delta f = 3.096 \text{GHz}$$

$$|\Gamma(3 \text{GHz})| = 4.17 \cdot 10^{-5}$$

$$|\Gamma(2.282 \text{GHz})| = 0.09925$$

# Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.etti.tuiasi.ro>
- [rdamian@etti.tuiasi.ro](mailto:rdamian@etti.tuiasi.ro)