

Lecture 3
2018/2019

Microwave Devices and Circuits for Radiocommunications

2018/2019

- 2C/1L, **MDCR**
- Attendance at minimum 7 sessions (course + laboratory)
- Lectures- **associate professor Radu Damian**
 - Friday 09-11, ? Ill.34, Il.13
 - E – 50% final grade
 - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
 - 3p=+0.5p
 - all materials/equipments authorized
- Laboratory – **associate professor Radu Damian**
 - Wednesday 12-14, Il.12 odd weeks
 - L – 25% final grade
 - P – 25% final grade

Materials

■ <http://rf-opto.etti.tuiasi.ro>

Laboratorul de Microunde si Opti X

Not secure | rf-opto.etti.tuiasi.ro/microwave_cd.php?chg_lang=0

Main **Courses** Master Staff Research Students Admin

Microwave CD Optical Communications Optoelectronics Internet Antennas Practica Networks Educational software

Microwave Devices and Circuits for Radiocommunications (English)

Course: MDCR (2017-2018)

Course Coordinator: Assoc.P. Dr. Radu-Florin Damian
Code: EDOS412T
Discipline Type: DOS; Alternative, Specialty
Credits: 4
Enrollment Year: 4, Sem. 7

Activities

Course: Instructor: Assoc.P. Dr. Radu-Florin Damian, 2 Hours/Week, Specialization Section, Timetable:
Laboratory: Instructor: Assoc.P. Dr. Radu-Florin Damian, 1 Hours/Week, Group, Timetable:

Evaluation

Type: **Examen**

A: 50%, (Test/Colloquium)
B: 25%, (Seminary/Laboratory/Project Activity)
D: 25%, (Homework/Specialty papers)

Grades

[Aggregate Results](#)

Attendance

[Course](#)
[Laboratory](#)

Lists

[Bonus-uri acumulate \(final\)](#)
[Studenti care nu pot intra in examen](#)

Materials

Course Slides

[MDCR Lecture 1](#) (pdf, 5.43 MB, en, [ps](#))
[MDCR Lecture 2](#) (pdf, 3.67 MB, en, [ps](#))
[MDCR Lecture 3](#) (pdf, 4.76 MB, en, [ps](#))
[MDCR Lecture 4](#) (pdf, 5.58 MB, en, [ps](#))

Photos

Nr. Student	Student	Prezent	Nr. Student	Student	Prezent	Nr. Student	Student	Prezent
1	ANGHELUS IONUT-MARIUS	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:	2	ANTIGHIN FLORIN-RAZVAN	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:	3	ANTONICA BIANCA	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:
4	APOSTOL PAVEL-MANUEL	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:	5	BALASCA VALIAN-PETRU	<input checked="" type="checkbox"/> Puncte: 0 Nota: 0 Obs:	6	BOSTAN ANDREI-PETRICIA	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:
7	BOTEZAT EMANUEL	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:	8	BUTUNOI GEORGE-MADALIN	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:	9	CHILEA SALUCA-MARIA	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:
10	CHERITOIU ECATERINA	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:	11	COJOC MARIUS	<input checked="" type="checkbox"/> Puncte: 0 Nota: 0 Obs:	12	COJOCARIU AURA-FLORINA	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:

Nr. Student	Student	Prezent
2	ANTIGHIN FLORIN-RAZVAN	<input type="checkbox"/> Puncte: 0 Nota: 0 Obs:

Access

■ Not customized



A student profile page with a photo of a man, a 'Date:' section with a table, and a 'Note obtinute' table. A red circle highlights the link 'Acceseaza ca acest student' and an arrow points from it to the right.

Date:

Grupa	5304 (2015/2016)
Specializarea	Tehnologii si sisteme de telecomunicatii
Marca	5184

[Acceseaza ca acest student](#)

Note obtinute

Disciplina	Tip	Data	Descriere	Nota	Puncte	Obs.
TW			Tehnologii Web			
N		17/01/2014	Nota finala	10	-	
A		17/01/2014	Colocviu Tehnologii Web 2013/2014	10	7.55	
B		17/01/2014	Laborator Tehnologii Web 2013/2014	9	-	
D		17/01/2014	Tema Tehnologii Web 2013/2014	9	-	



A login form with fields for 'Nume', 'Email', and 'Cod de verificare'. The 'Email' and 'Cod de verificare' fields are circled in red. A red arrow points from the link in the previous image to the 'Email' field. A 'Trimite' button is at the bottom.

Nume
IACOBSCUN

Email

Cod de verificare


344bd9f

Trimite

Proiect 2018/2019

- factorul "andrei" = $-2p$

2017/8

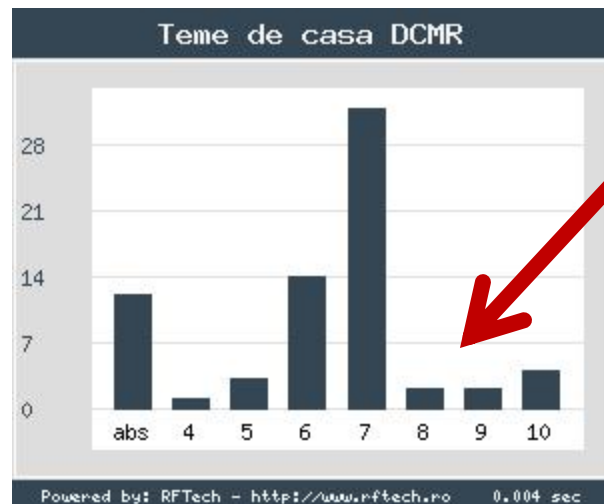

Examen: Logarithmic scales

$$\text{dB} = 10 \cdot \log_{10} (P_2 / P_1)$$

0 dB	= 1
+ 0.1 dB	= 1.023 (+2.3%)
+ 3 dB	= 2
+ 5 dB	= 3
+ 10 dB	= 10
-3 dB	= 0.5
-10 dB	= 0.1
-20 dB	= 0.01
-30 dB	= 0.001

$$\text{dBm} = 10 \cdot \log_{10} (P / 1 \text{ mW})$$

0 dBm	= 1 mW
3 dBm	= 2 mW
5 dBm	= 3 mW
10 dBm	= 10 mW
20 dBm	= 100 mW
-3 dBm	= 0.5 mW
-10 dBm	= 100 μ W
-30 dBm	= 1 μ W
-60 dBm	= 1 nW

$$[\text{dBm}] + [\text{dB}] = [\text{dBm}]$$

$$[\text{dBm/Hz}] + [\text{dB}] = [\text{dBm/Hz}]$$

$$[x] + [\text{dB}] = [x]$$

Examen

- Complex numbers arithmetic!!!!
- $z = a + j \cdot b ; j^2 = -1$


Introduction

Electrical Length

- Behavior (and description) of any circuit depends on his electrical length at the particular frequency of interest

- $E \approx 0 \rightarrow$ Kirchhoff
- $E > 0 \rightarrow$ wave propagation
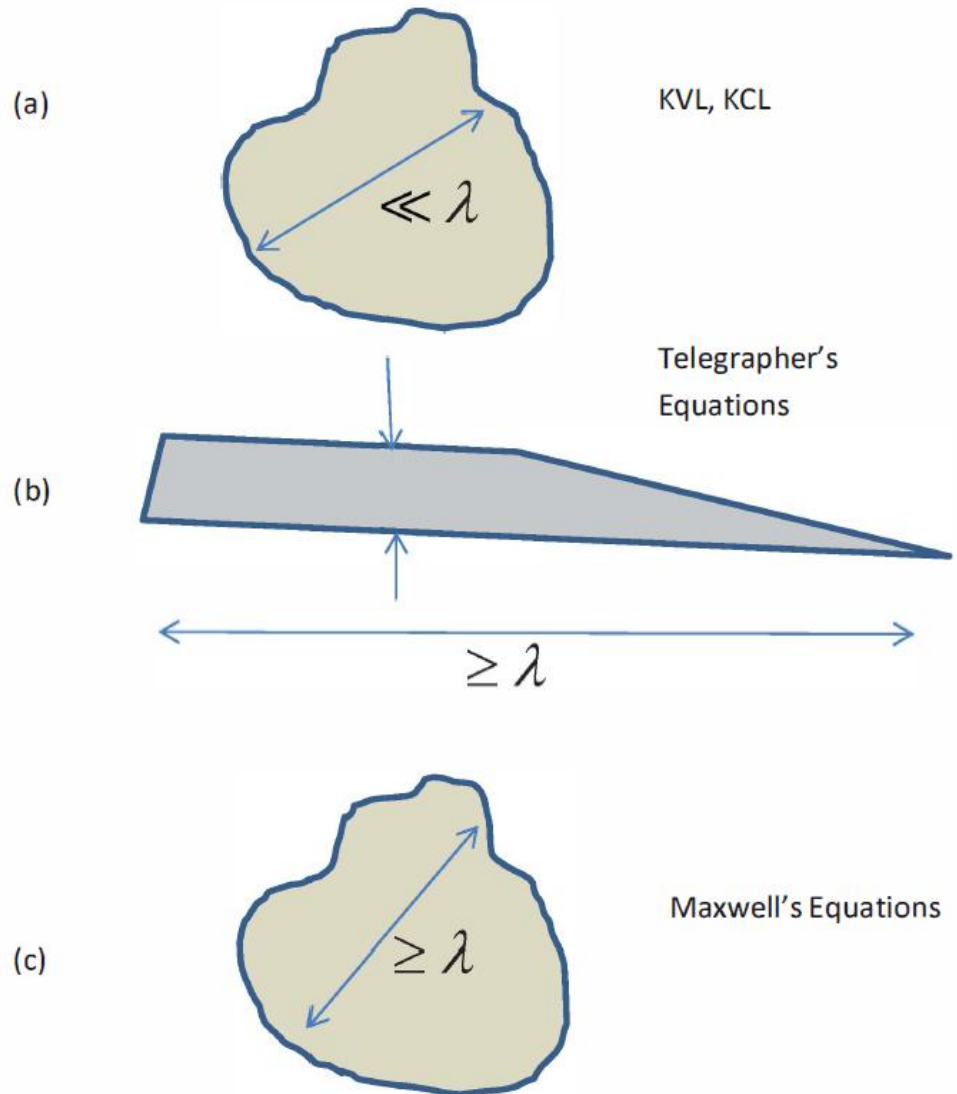
$$E = \beta \cdot l = \frac{2\pi}{\lambda} \cdot l = 2\pi \cdot \left(\frac{l}{\lambda}\right)$$




Mathematical models

- particular cases where analytical solution exists
 - harmonic signals, Fourier Transform, frequency spectrum


$$X = X_0 e^{j \cdot \omega \cdot t} \quad \frac{\partial X}{\partial t} = j \cdot \omega \cdot X$$

$$g(\omega) = \int_{-\infty}^{\infty} f(t) \cdot e^{-j\omega t} dt$$

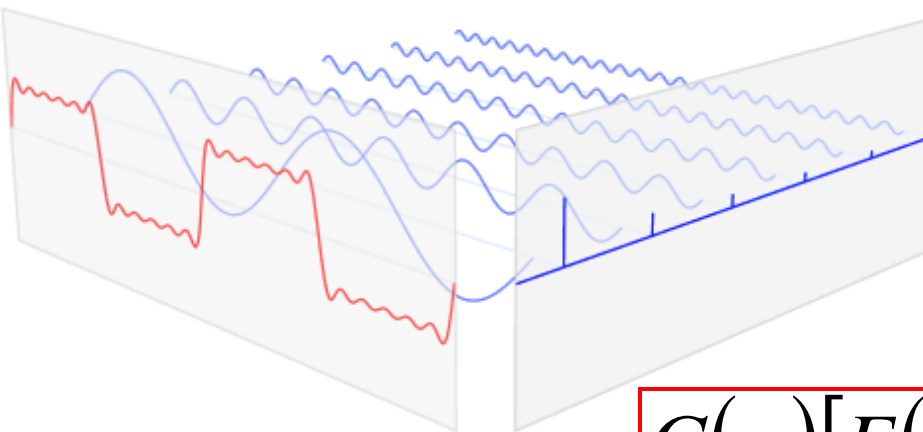
$$f(t) = \int_{-\infty}^{\infty} g(\omega) \cdot e^{j\omega t} d\omega$$



$$G(\omega)[F(\omega)]$$

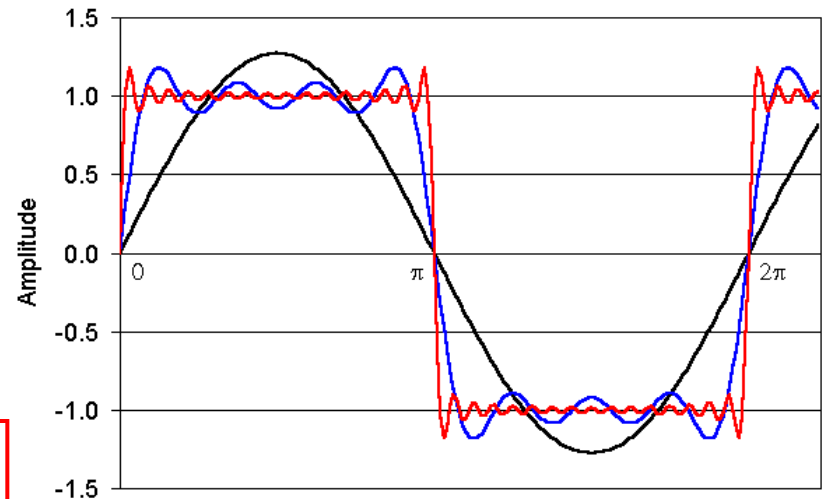

Mathematical modeling

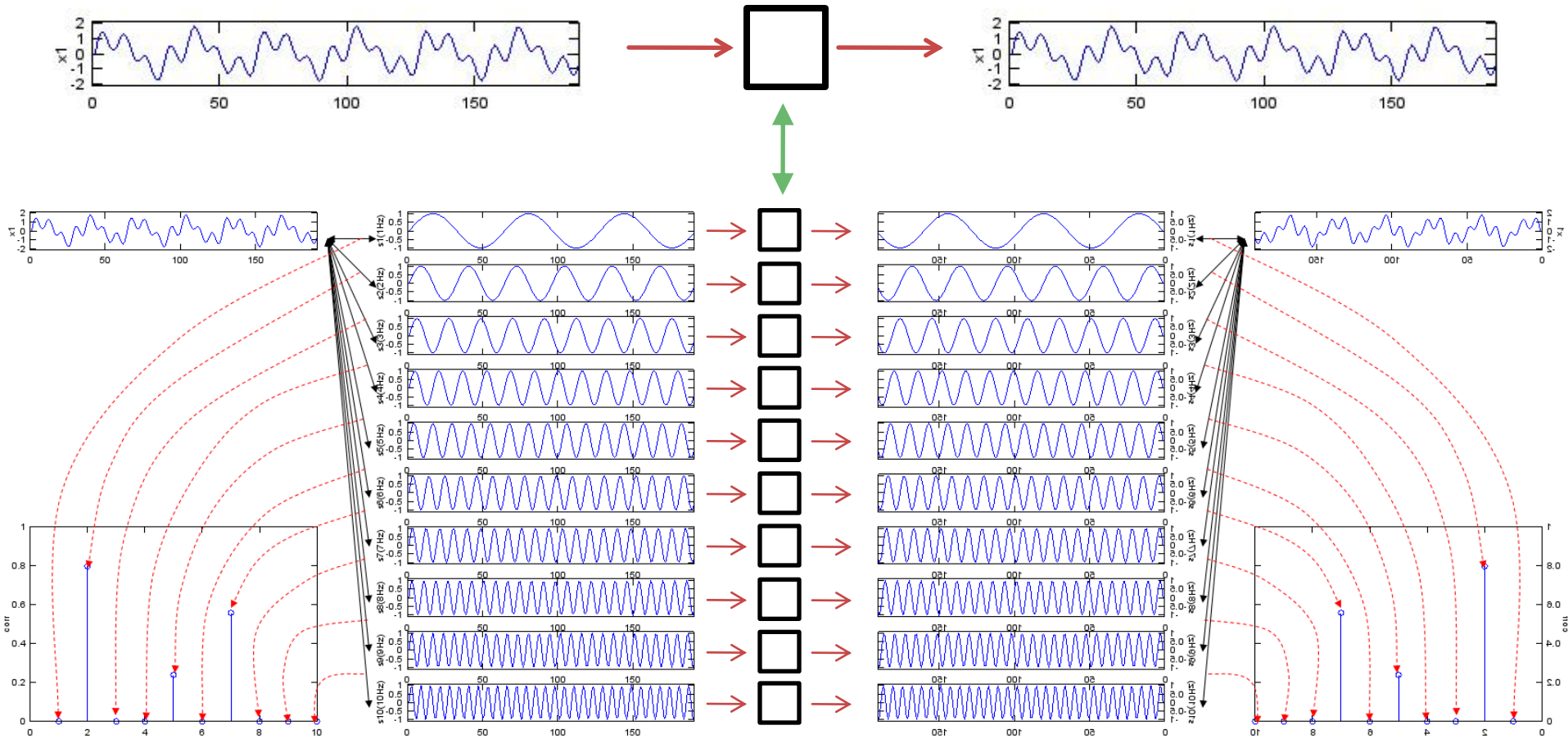

$$F(\omega) = \int_{-\infty}^{\infty} f(t) \cdot e^{-j\omega t} dt$$

$$G(\omega)[F(\omega)]$$

$$g(t) = \int_{-\infty}^{\infty} G(\omega) \cdot e^{j\omega t} d\omega$$

Mathematical modeling

- particular cases where analytical solution exists

- wave in a single direction $E^+ (E^+)$, $E^- (E^-)$

- wave

- incident

$$E_y = E^+ \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t - \beta \cdot z)} + E^- \cdot e^{-\alpha \cdot z} \cdot e^{j(\omega t + \beta \cdot z)}$$


- reflected

$$E_{IN} = E_{1+} e^{-\gamma \cdot z} + E_{1-} e^{\gamma \cdot z} \longrightarrow \square \longrightarrow E_{OUT} = E_{2+} e^{-\gamma \cdot z} + E_{2-} e^{\gamma \cdot z}$$

- wave


- direct

- inverse

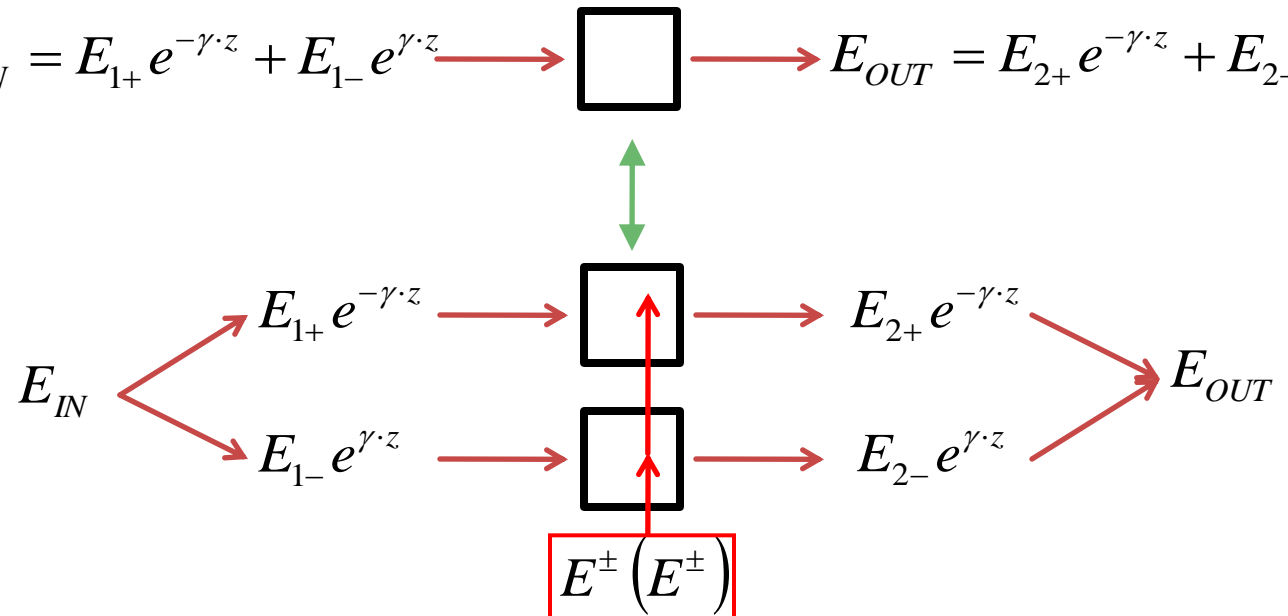


Mathematical modeling


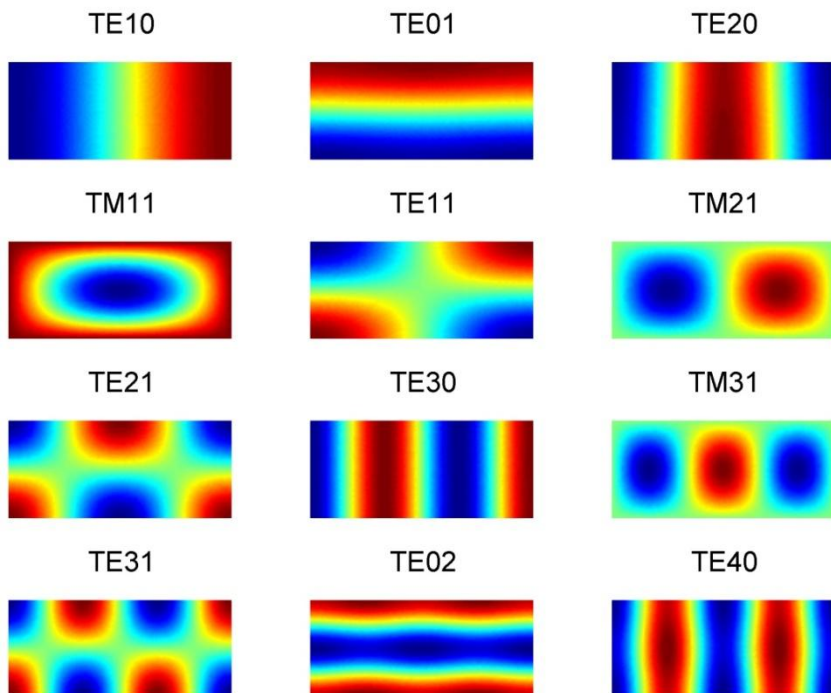
- particular cases where analytical solution exists
 - modes in delimited media $B_i(A_i)$


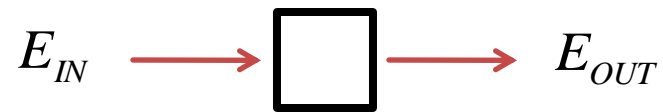
$$E = \sum_1^{\infty} A_i \cdot Mod_i \quad A_i = \langle E, Mod_i \rangle$$



$$A_i = \langle E_{IN}, Mod_i \rangle$$

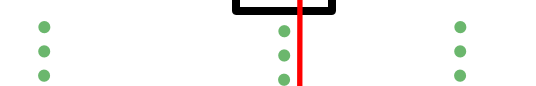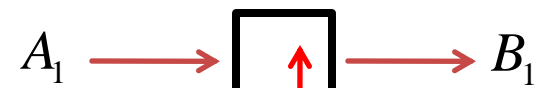



$$B_i(A_i)$$

$$E_{OUT} = \sum_1^N B_i \cdot Mod_i$$

TEM transmission lines


Transmission line

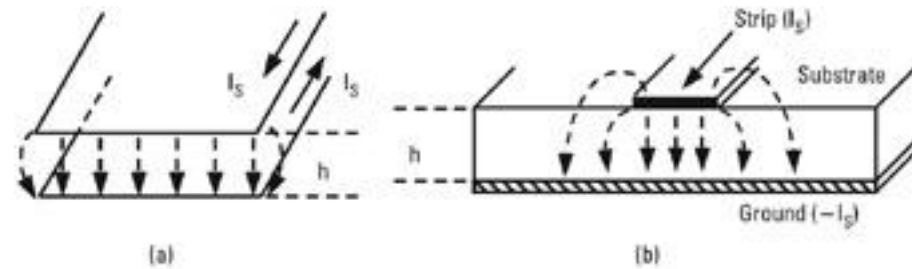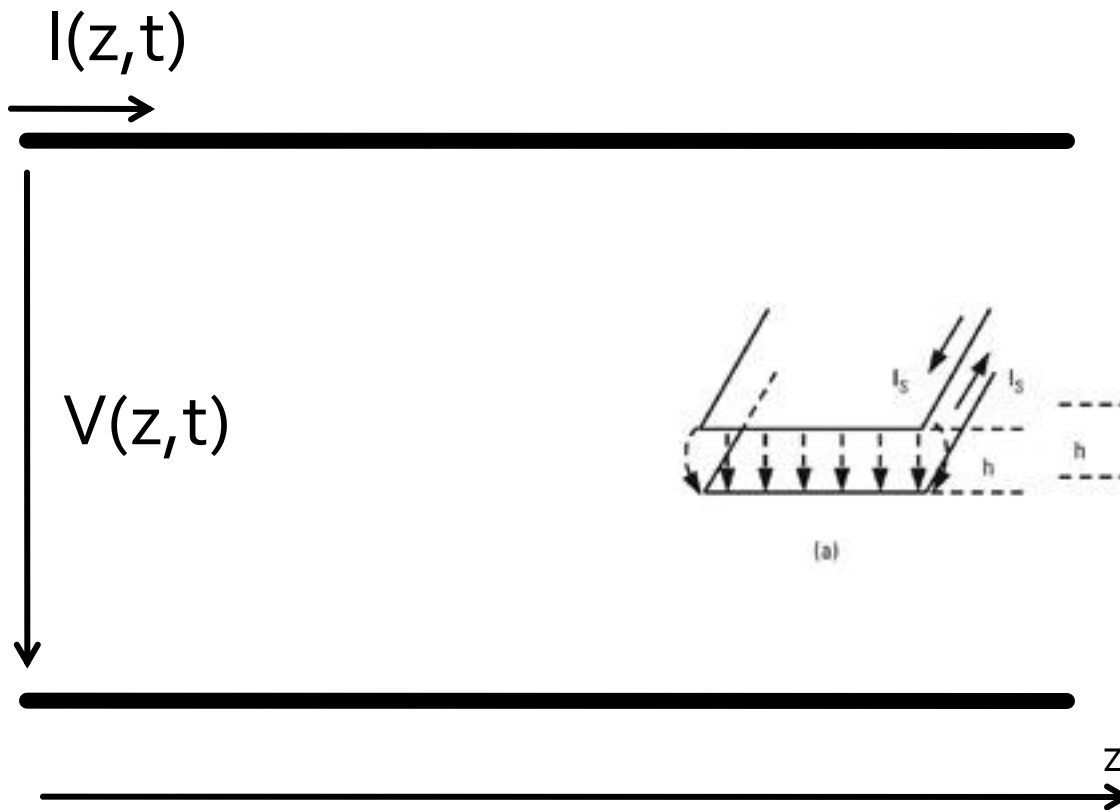- TEM wave propagation, at least two conductors



Transmission line equivalent model

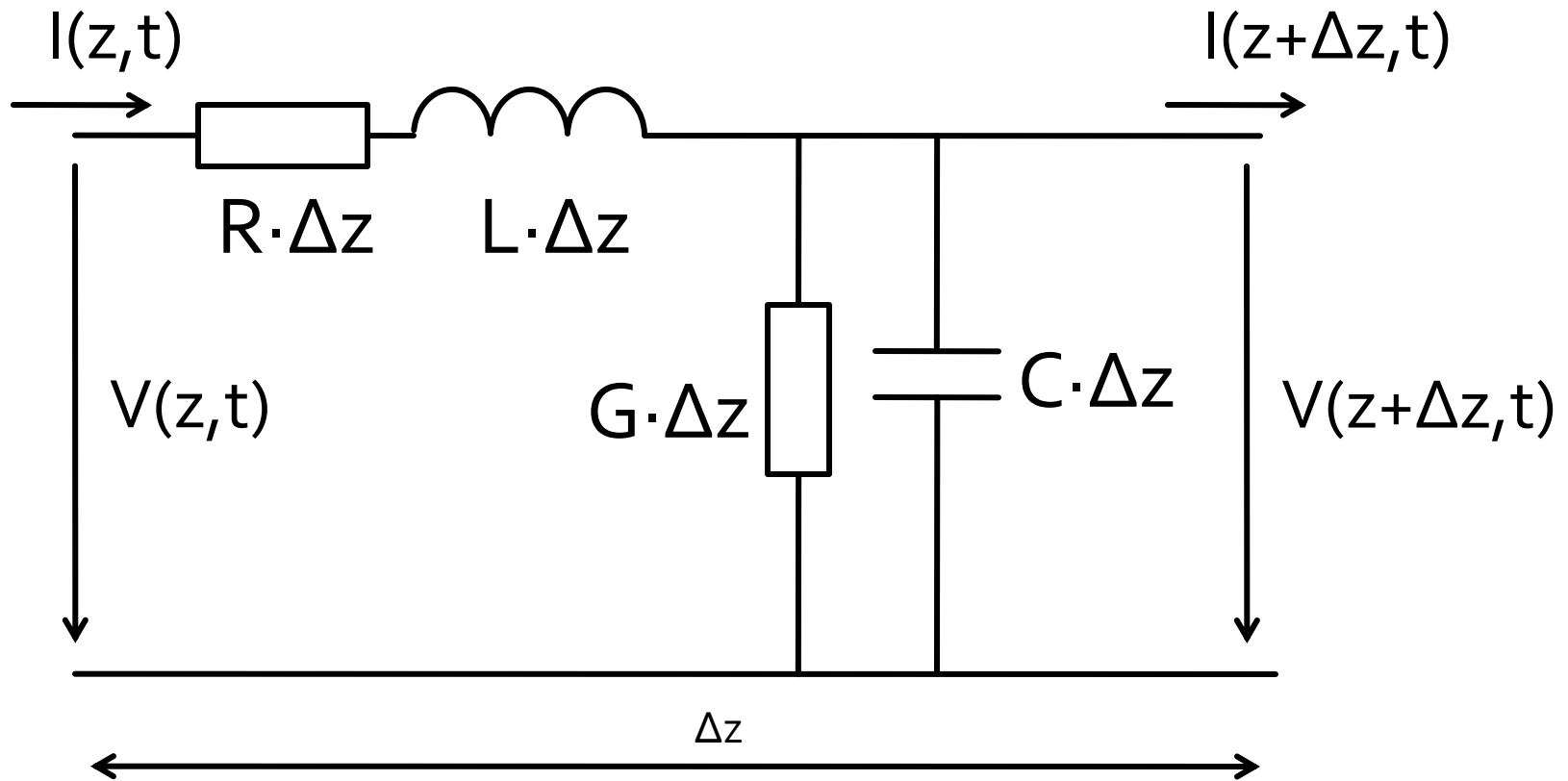- TEM wave propagation, at least two conductors



Solutions

$$\left\{ \begin{array}{l} V(z) = V_0^+ e^{-\gamma \cdot z} + V_0^- e^{\gamma \cdot z} \\ I(z) = I_0^+ e^{-\gamma \cdot z} + I_0^- e^{\gamma \cdot z} \end{array} \right. \quad \gamma = \alpha + j \cdot \beta = \sqrt{(R + j \cdot \omega \cdot L) \cdot (G + j \cdot \omega \cdot C)}$$

$$V(z) = V_0^+ e^{-\gamma \cdot z} + V_0^- e^{\gamma \cdot z}$$

$$\frac{dV(z)}{dz} = -(R + j \cdot \omega \cdot L) \cdot I(z)$$

$$Z_0 \equiv \frac{R + j \cdot \omega \cdot L}{\gamma} = \sqrt{\frac{R + j \cdot \omega \cdot L}{G + j \cdot \omega \cdot C}}$$

$$\frac{V_0^+}{I_0^+} = Z_0 = -\frac{V_0^-}{I_0^-}$$

$$I(z) = \frac{\gamma}{R + j \cdot \omega \cdot L} (V_0^+ e^{-\gamma \cdot z} - V_0^- e^{\gamma \cdot z})$$

- Characteristic impedance of the line

$$\lambda = \frac{2\pi}{\beta} \quad v_f = \frac{\omega}{\beta} = \lambda \cdot f$$

The lossless line

- **Lossless:** $R=G=0$

$$\gamma = \alpha + j \cdot \beta = \sqrt{(R + j \cdot \omega \cdot L) \cdot (G + j \cdot \omega \cdot C)} = j \cdot \omega \cdot \sqrt{L \cdot C}$$

$$\alpha = 0 \quad ; \quad \beta = \omega \cdot \sqrt{L \cdot C}$$

$$Z_0 = \sqrt{\frac{R + j \cdot \omega \cdot L}{G + j \cdot \omega \cdot C}} = \sqrt{\frac{L}{C}}$$

- Z_0 is **real**


$$V(z) = V_0^+ e^{-j \cdot \beta \cdot z} + V_0^- e^{j \cdot \beta \cdot z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j \cdot \beta \cdot z} - \frac{V_0^-}{Z_0} e^{j \cdot \beta \cdot z}$$

$$\lambda = \frac{2\pi}{\omega \cdot \sqrt{LC}}$$

$$v_f = \frac{1}{\sqrt{LC}}$$

The lossless line

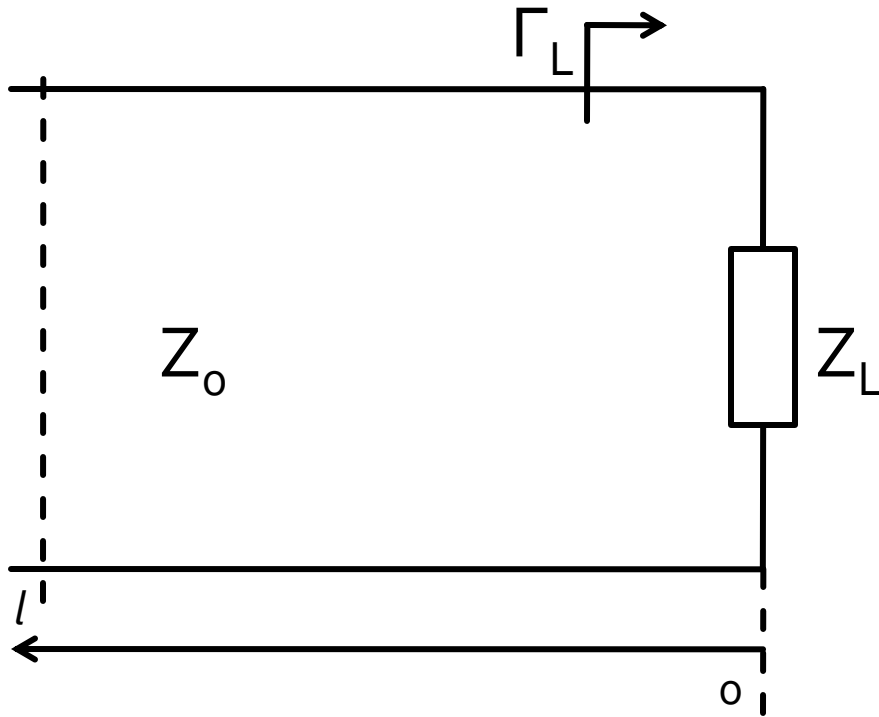

$$V(z) = V_0^+ e^{-j\beta \cdot z} + V_0^- e^{j\beta \cdot z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta \cdot z} - \frac{V_0^-}{Z_0} e^{j\beta \cdot z}$$

$$Z_L = \frac{V(0)}{I(0)} \quad Z_L = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \cdot Z_0$$

- voltage reflection coefficient

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

- Z_0 real

The lossless line

- voltage reflection coefficient seen at the input of the line

$$V(z) = V_0^+ e^{-j\beta \cdot z} + V_0^- e^{j\beta \cdot z}$$

$$\Gamma = \Gamma(z) = \frac{V_0^-(z)}{V_0^+(z)}$$

$$V(0) = V_0^+ + V_0^- \quad \Gamma(0) = \Gamma_L = \frac{V_0^-}{V_0^+}$$


$$V(-l) = V_0^+ e^{j\beta \cdot l} + V_0^- e^{-j\beta \cdot l}$$

$$\Gamma(-l) = \Gamma_{IN} = \frac{V_0^- \cdot e^{-j\beta \cdot l}}{V_0^+ \cdot e^{j\beta \cdot l}} = \Gamma(0) \cdot e^{-2j\beta \cdot l}$$

$$|\Gamma(-l)| = |\Gamma(0)| \cdot |e^{-2j\beta \cdot l}| = |\Gamma(0)|$$

$$\Gamma_{IN} = \Gamma_L \cdot e^{-2j\beta \cdot l}$$

$$|\Gamma_{IN}| = |\Gamma_L|$$

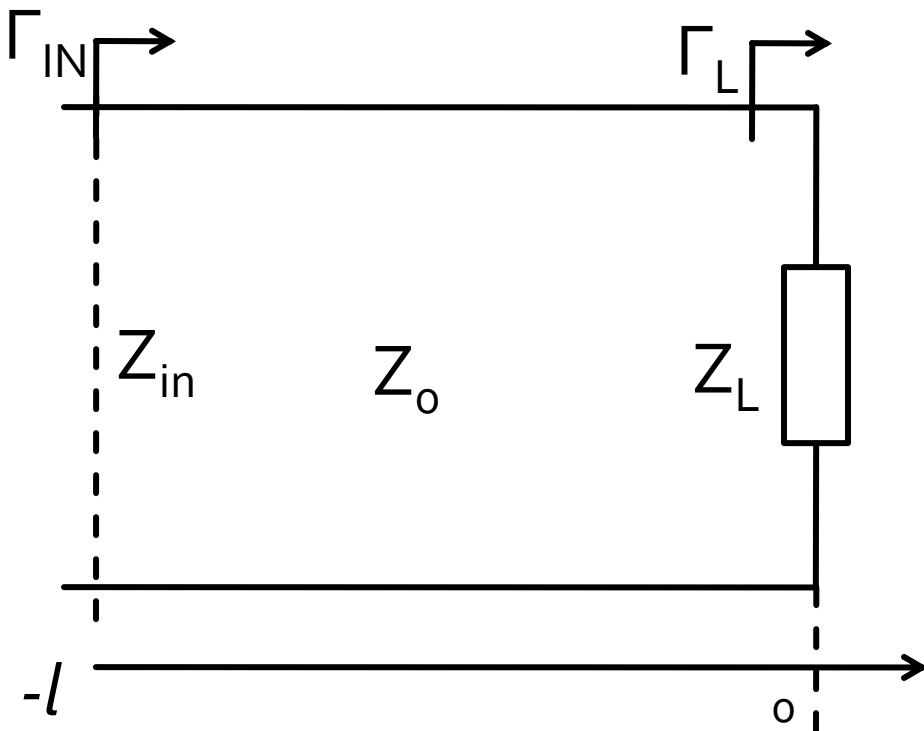

The lossless line


$$V(z) = V_0^+ \cdot (e^{-j\beta \cdot z} + \Gamma \cdot e^{j\beta \cdot z}) \quad I(z) = \frac{V_0^+}{Z_0} \cdot (e^{-j\beta \cdot z} - \Gamma \cdot e^{j\beta \cdot z})$$

- time-average Power flow along the line

$$P_{avg} = \frac{1}{2} \cdot \text{Re}\{V(z) \cdot I(z)^*\} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot \text{Re}\left\{1 - \Gamma^* \cdot \underbrace{e^{-2j\beta \cdot z} + \Gamma \cdot e^{2j\beta \cdot z}}_{(z - z^*) = \text{Im}} - |\Gamma|^2\right\}$$
$$P_{avg} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot (1 - |\Gamma|^2)$$

- Total power delivered to the load = Incident power – “Reflected” power
- Return “Loss” [dB] $RL = -20 \cdot \log|\Gamma|$ [dB]

The lossless line

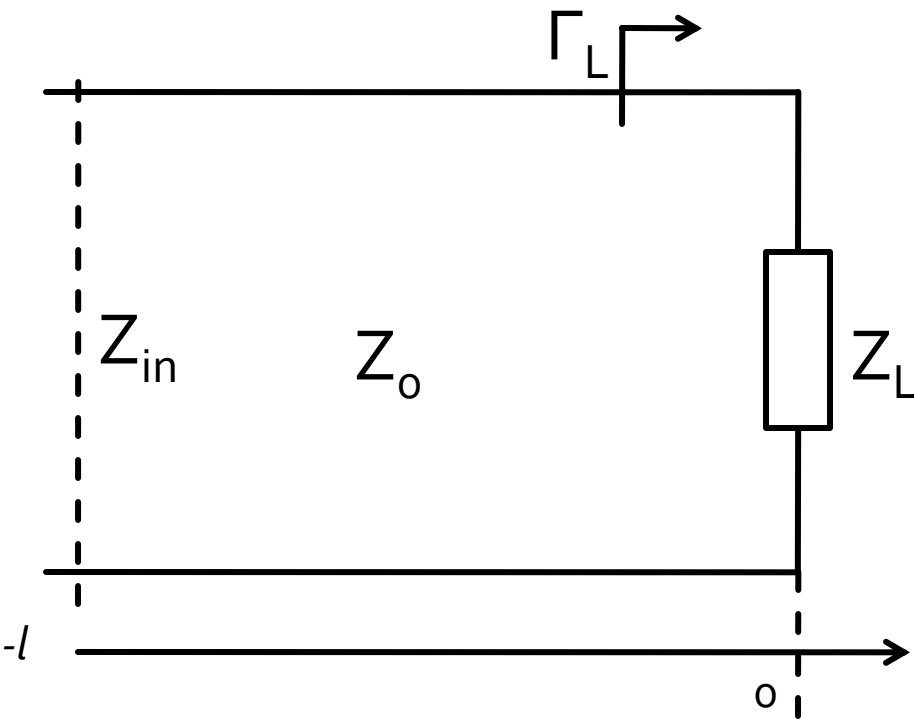

$$V(-l) = V_0^+ e^{j\beta \cdot l} + V_0^- e^{-j\beta \cdot l}$$

$$I(-l) = \frac{V_0^+}{Z_0} e^{j\beta \cdot l} - \frac{V_0^-}{Z_0} e^{-j\beta \cdot l}$$

$$Z_{in} = \frac{V(-l)}{I(-l)} \quad Z_{in} = Z_0 \cdot \frac{1 + \Gamma \cdot e^{-2j\beta \cdot l}}{1 - \Gamma \cdot e^{-2j\beta \cdot l}}$$

- the **input impedance** seen looking toward the load

$$Z_{in} = Z_0 \cdot \frac{(Z_L + Z_0) \cdot e^{j\beta \cdot l} + (Z_L - Z_0) \cdot e^{-j\beta \cdot l}}{(Z_L + Z_0) \cdot e^{j\beta \cdot l} - (Z_L - Z_0) \cdot e^{-j\beta \cdot l}}$$

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan(\beta \cdot l)}{Z_0 + j \cdot Z_L \cdot \tan(\beta \cdot l)}$$


The lossless line

- the **input impedance** seen looking toward the load

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

The lossless line

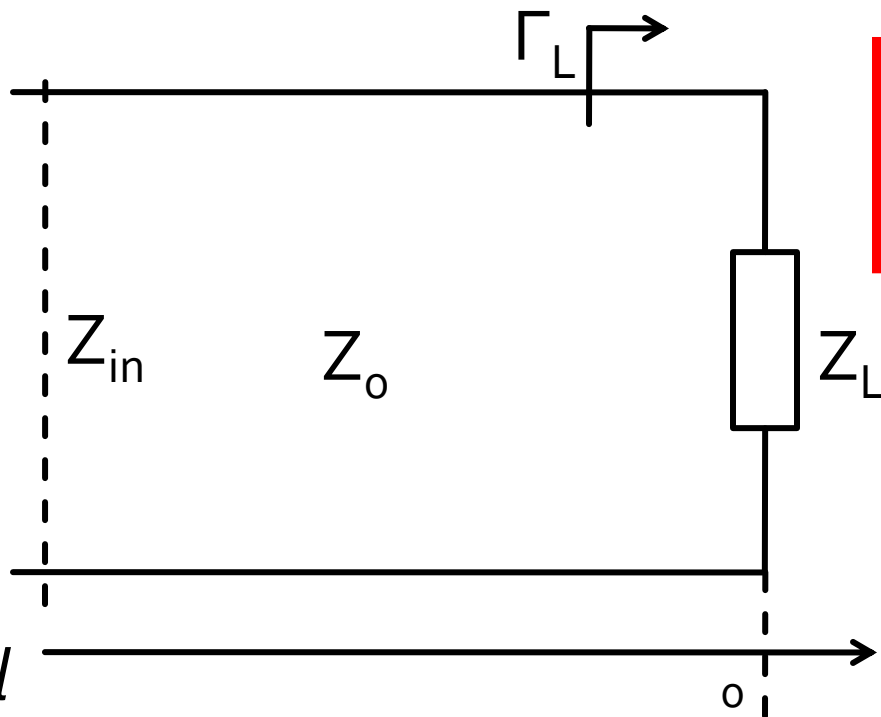
- input impedance of a length l of transmission line with characteristic impedance Z_0 , loaded with an arbitrary impedance Z_L



$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

The lossless line

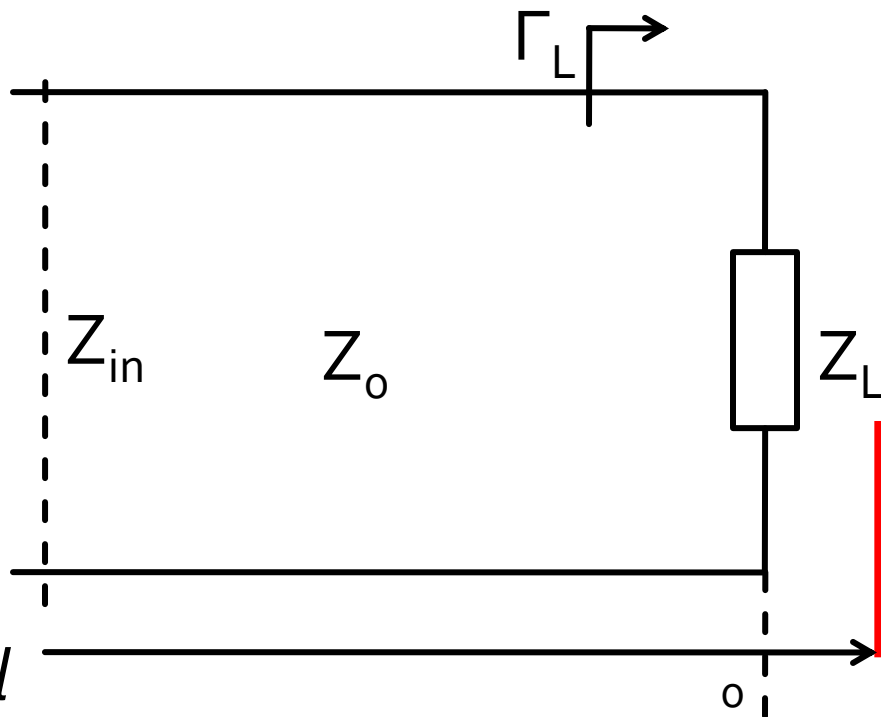- input impedance is **frequency dependent** through $\beta \cdot l$



$$v_f = \frac{\omega}{\beta} = \lambda \cdot f \quad \lambda = \frac{2\pi}{\beta}$$
$$\beta \cdot l = \frac{2\pi}{\lambda} \cdot l = \frac{2\pi \cdot f}{v_f} \cdot l = \frac{2\pi \cdot l}{v_f} \cdot f$$

frequency dependence is **periodical**, imposed by the tan trigonometric function

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$


The lossless line, special cases

- $l = k \cdot \lambda/2$ $\beta \cdot l = \frac{2\pi}{\lambda} \cdot l = k \cdot \pi$ $\tan \beta \cdot l = 0$

$$Z_{in} = Z_0$$

- $l = \lambda/4 + k \cdot \lambda/2$ $\tan \beta \cdot l \rightarrow \infty$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

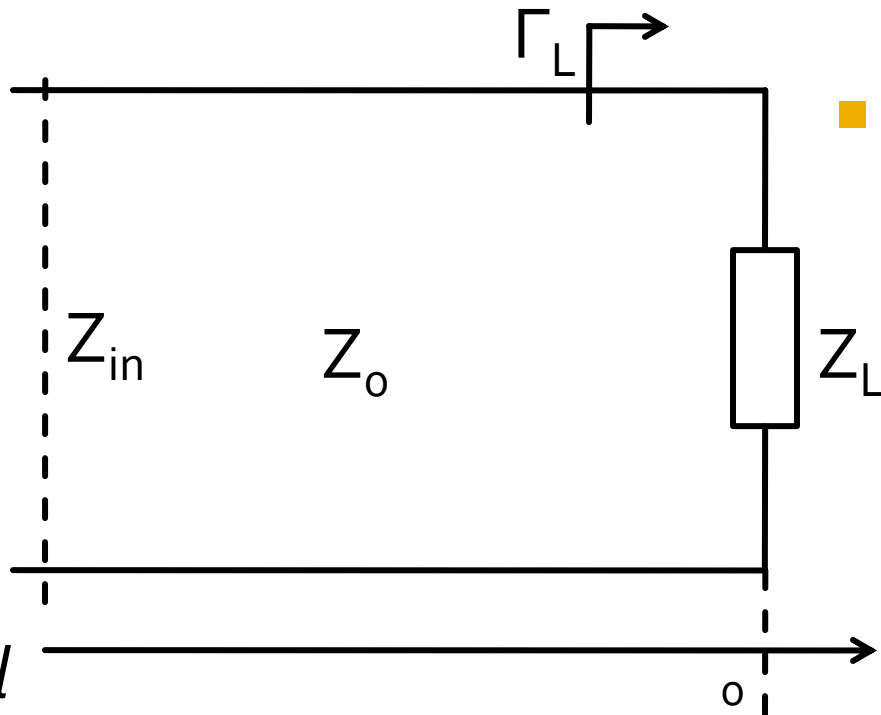

- quarter-wave transformer


$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

Short-circuited transmission line


- $Z_L = 0$
- purely imaginary for any length l
 - +/- \rightarrow depending on l value

$$Z_{in} = j \cdot Z_0 \cdot \tan \beta \cdot l$$

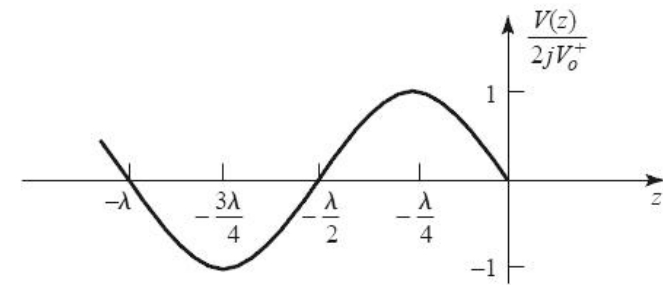
$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan(\beta \cdot l)}{Z_0 + j \cdot Z_L \cdot \tan(\beta \cdot l)}$$



(a)

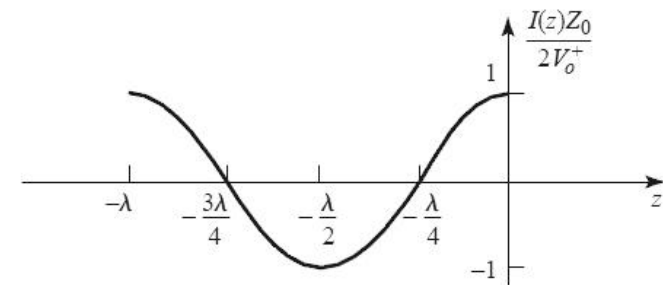

(b)

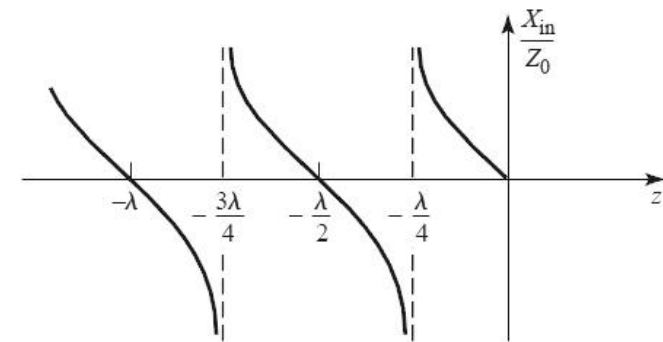




(c)

Open-circuited transmission line


- $Z_L = \infty \rightarrow 1/Z_L = 0$
- purely imaginary for any length l
 - +/- \rightarrow depending on l value

$$Z_{in} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$

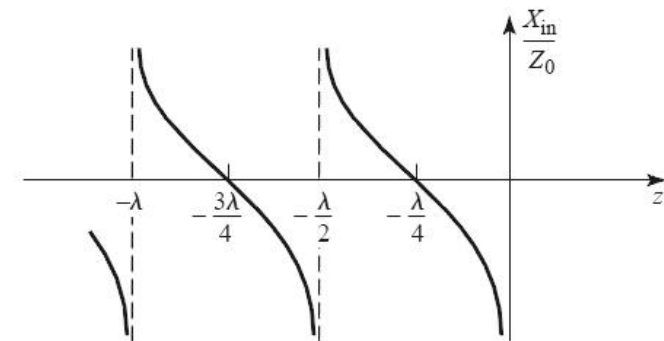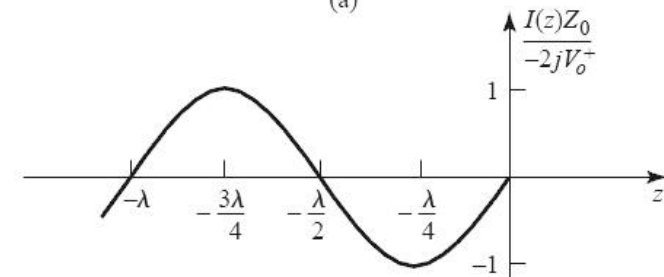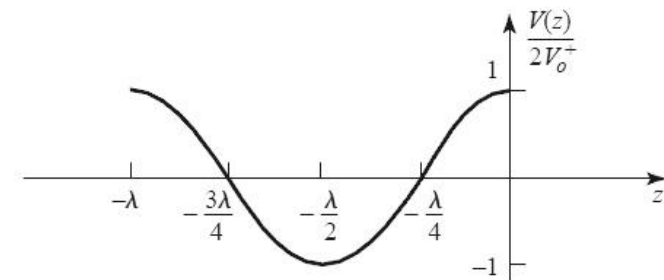
$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan(\beta \cdot l)}{Z_0 + j \cdot Z_L \cdot \tan(\beta \cdot l)}$$




Examples

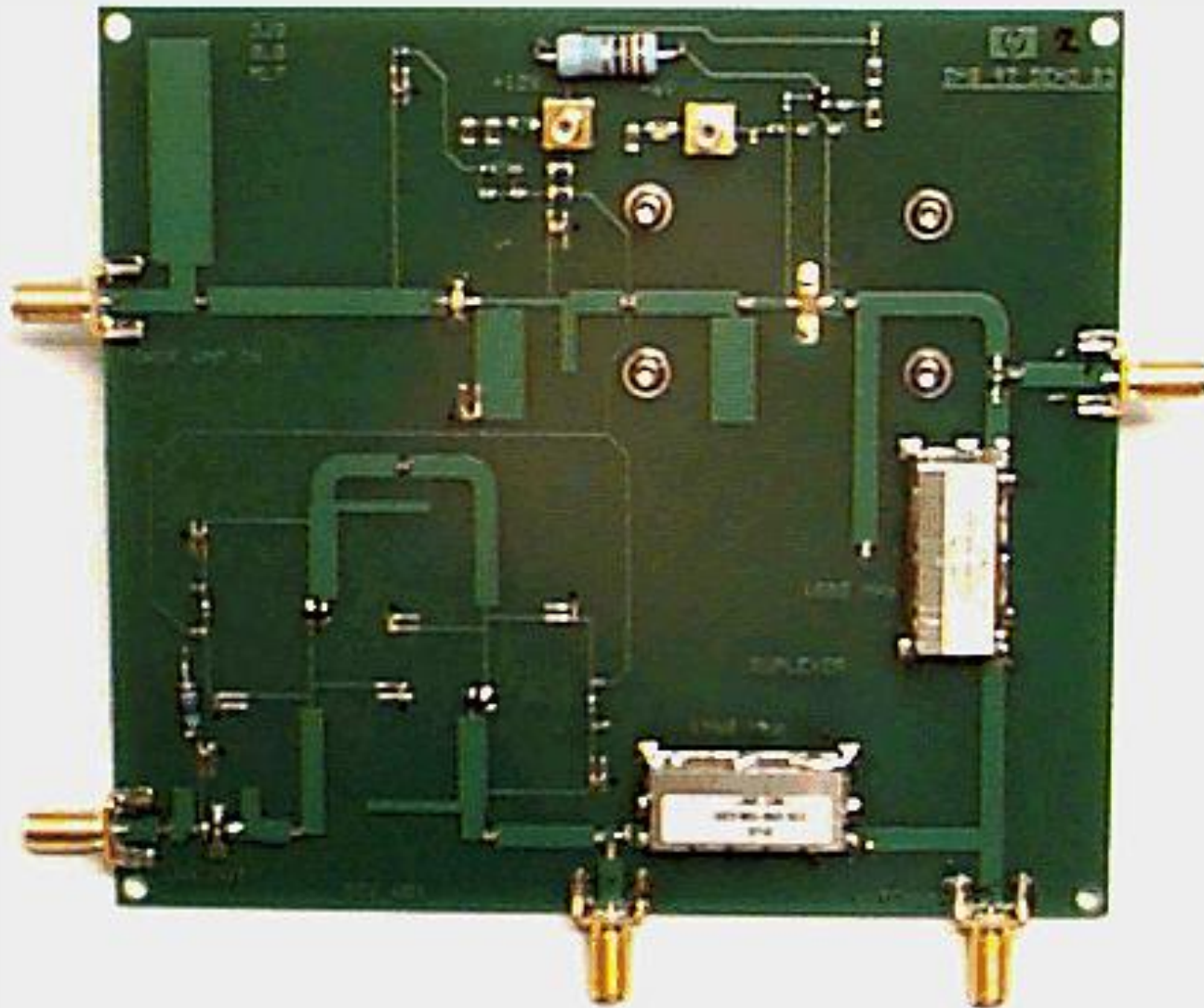

Examples

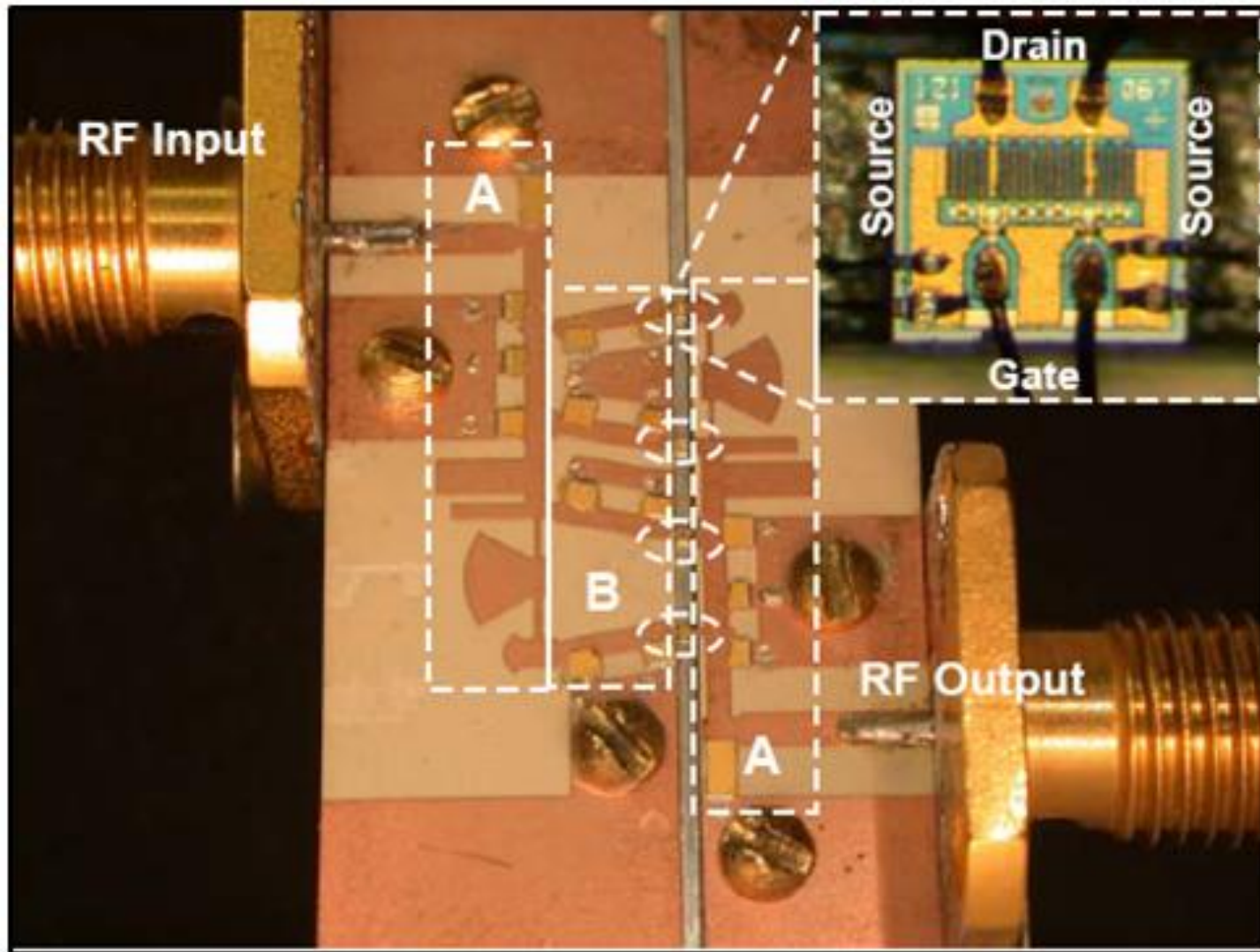


Examples

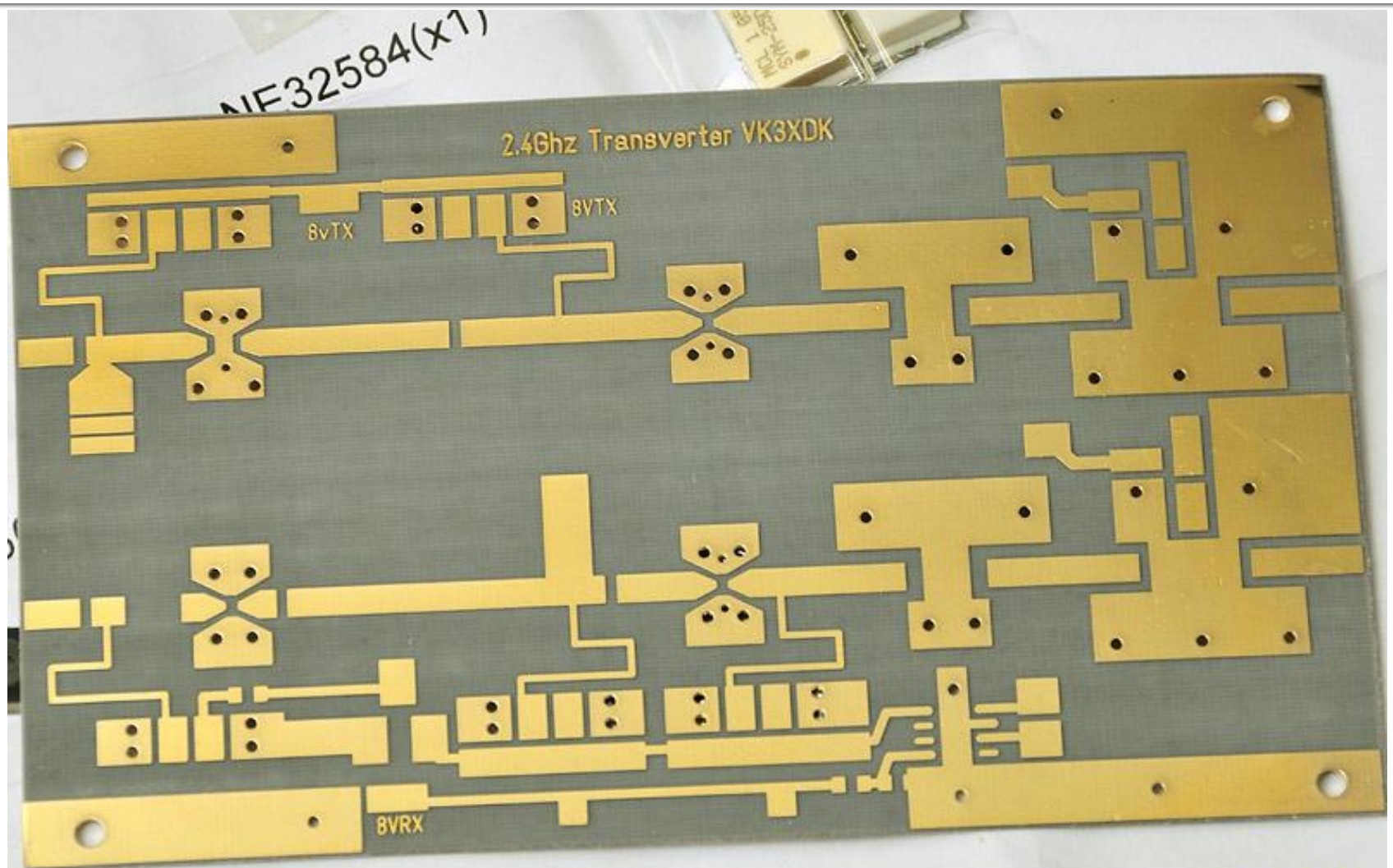


VK4CP

Examples

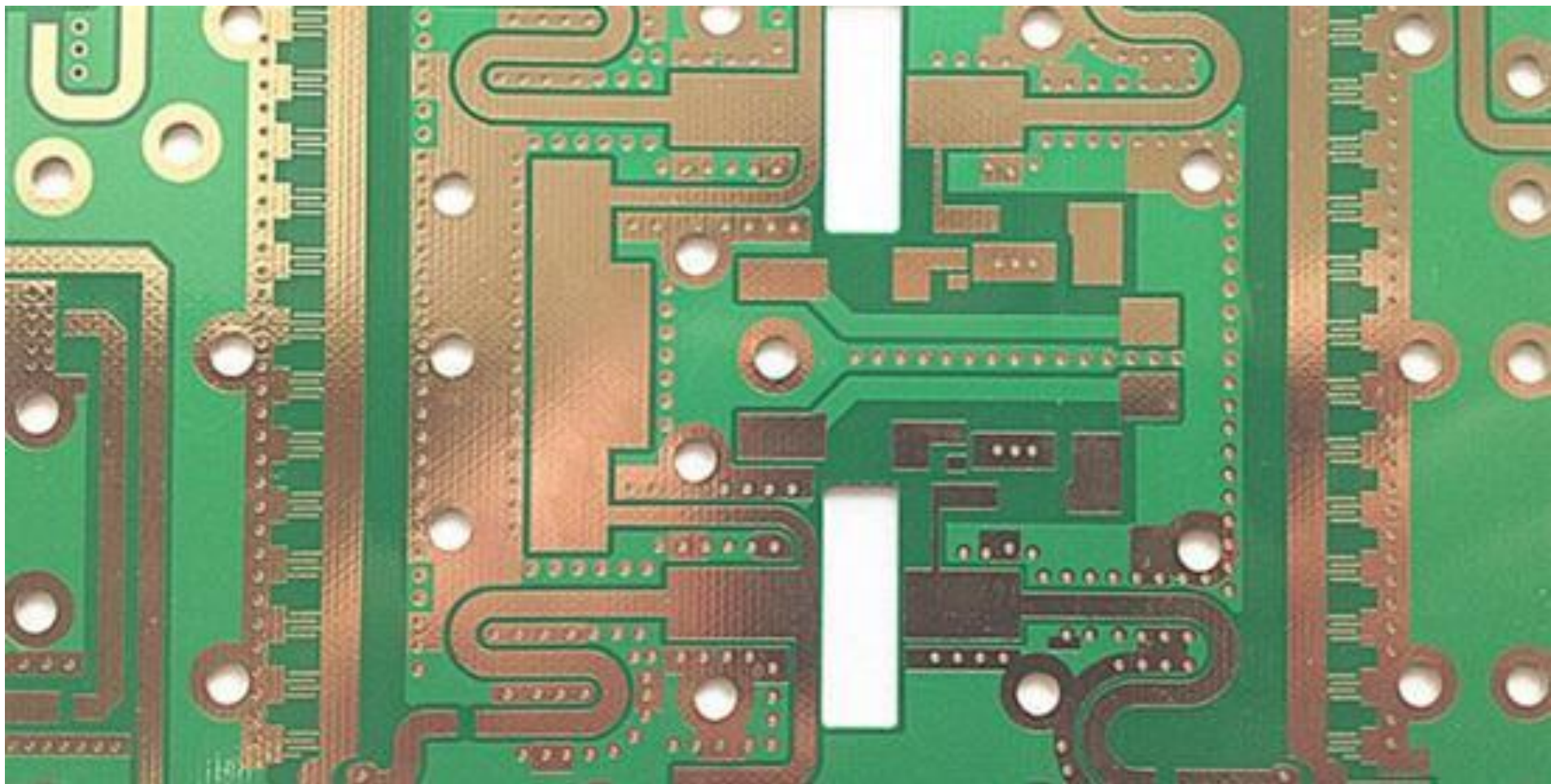

Examples

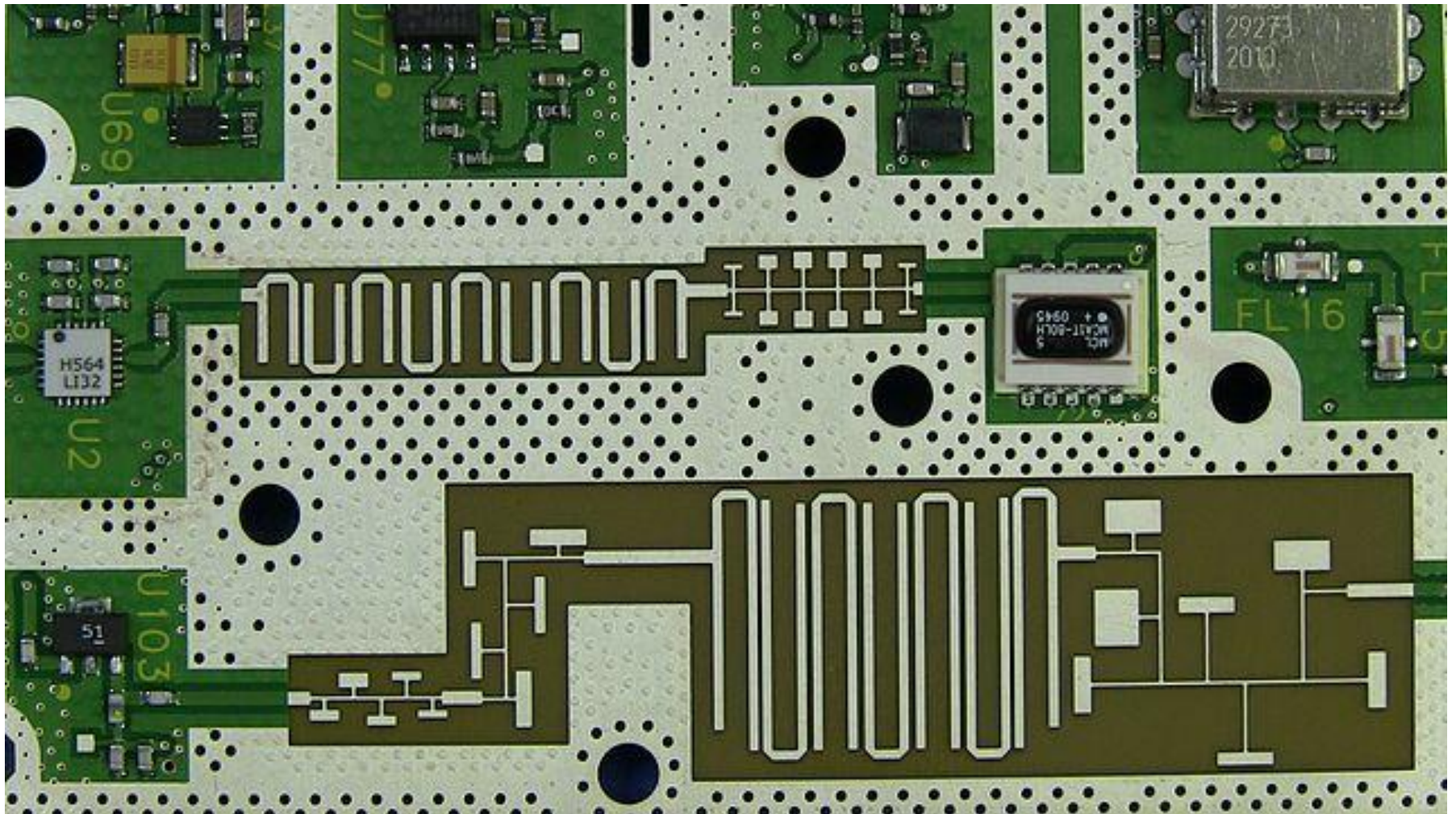

Voltage standing wave ratio

$$V(z) = V_0^+ \cdot (e^{-j\beta \cdot z} + \Gamma \cdot e^{j\beta \cdot z}) \quad |V(z)| = |V_0^+| \cdot |e^{-j\beta \cdot z}| \cdot |1 + \Gamma \cdot e^{2j\beta \cdot z}| \quad \Gamma = |\Gamma| \cdot e^{j\theta}$$

$$|V(z)| = |V_0^+| \cdot |1 + |\Gamma| \cdot e^{\theta + 2j\beta \cdot z}|$$

maximum magnitude value for $e^{\theta + 2j\beta \cdot z} = 1$

$$V_{\max} = |V_0^+| \cdot (1 + |\Gamma|)$$

minimum magnitude value for $e^{\theta + 2j\beta \cdot z} = -1$

$$V_{\min} = |V_0^+| \cdot (1 - |\Gamma|)$$


- SWR is defined as the ratio between maximum and minimum

- (Voltage) Standing Wave Ratio

$$VSWR = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

- real number $1 \leq VSWR < \infty$
- a measure of the mismatch (SWR = 1 means a matched line)

The lossless line +/-

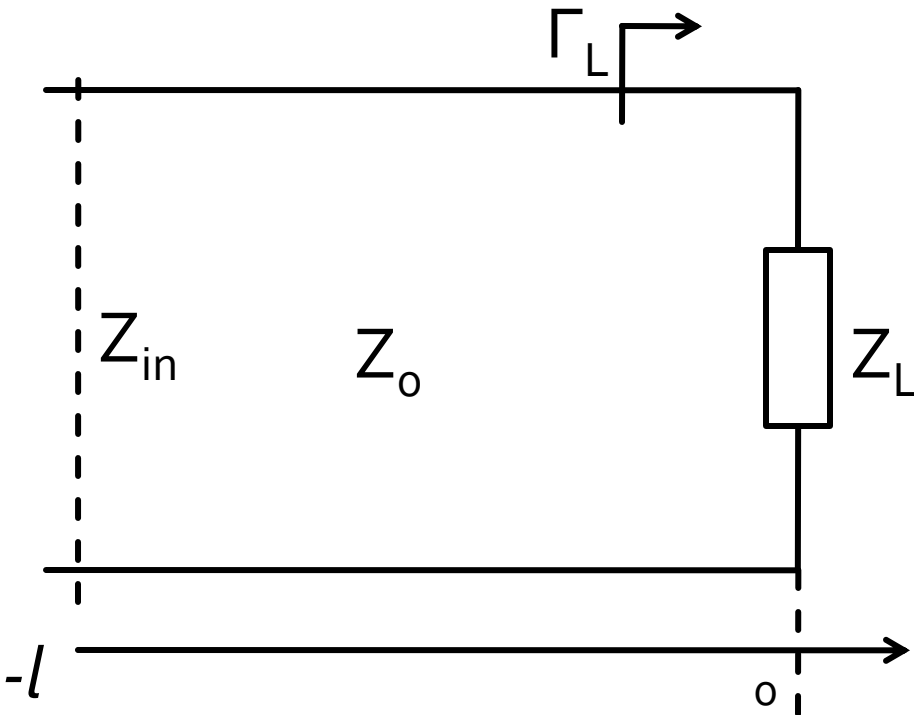

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

$$V(z) = V_0^+ e^{-\gamma \cdot z} + V_0^- e^{\gamma \cdot z}$$

$$I(z) = I_0^+ e^{-\gamma \cdot z} + I_0^- e^{\gamma \cdot z}$$

$$\Gamma(-l) = \Gamma(0) \cdot e^{-2j \cdot \beta \cdot l}$$


$$\Gamma_{in} = \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}$$

Impedance Matching with Impedance Transformers (Lab 1)

Impedance Matching

Matching


- Source matched to load ?

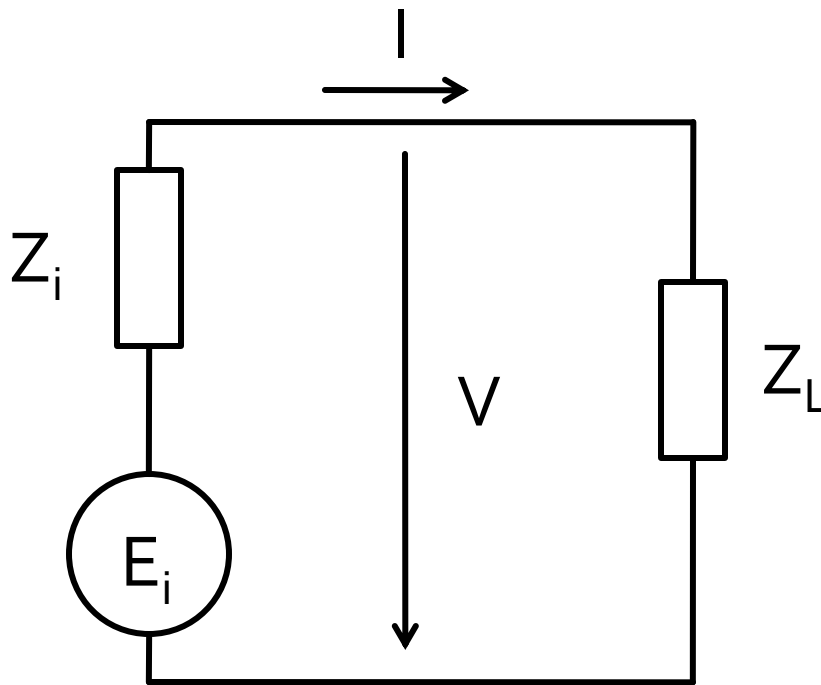

- impedance values ?
- existence of reflections ?

Matching, real impedances

- Source matched to load

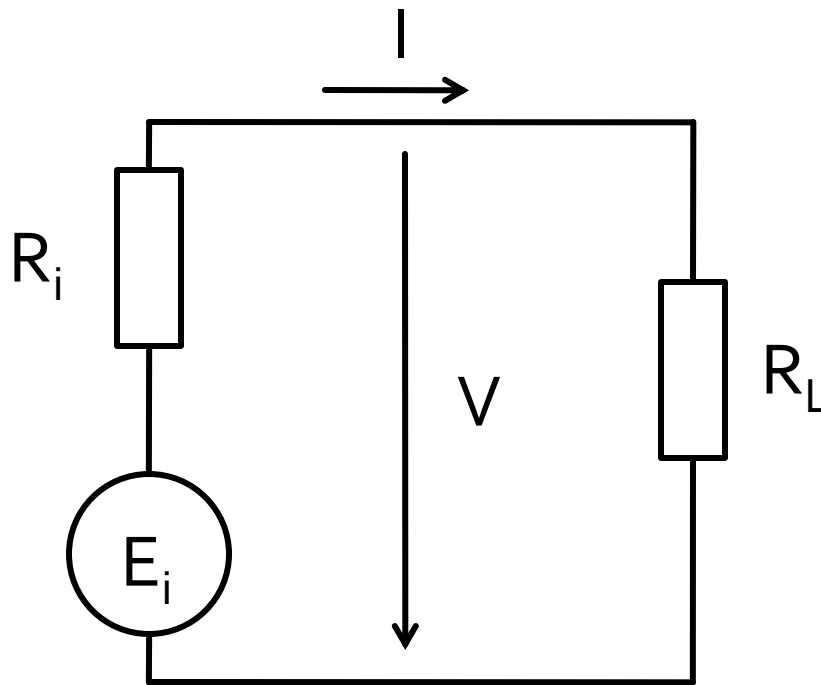

$$I = \frac{E_i}{R_i + R_L}$$

$$V = \frac{E_i \cdot R_L}{R_i + R_L}$$

$$P_L = R_L \cdot I^2$$


$$P_L = \frac{R_L \cdot E_i^2}{(R_i + R_L)^2}$$

Matching, real impedances

$$P_L = R_L \cdot I^2 \quad P_L = \frac{R_L \cdot E_i^2}{(R_i + R_L)^2}$$


- Power dissipated on load
 - $R_i = 50\Omega$
 - $R_L = 0 \rightarrow P_L = 0$
 - $R_L = \infty \rightarrow P_L = 0$

Matching, real impedances

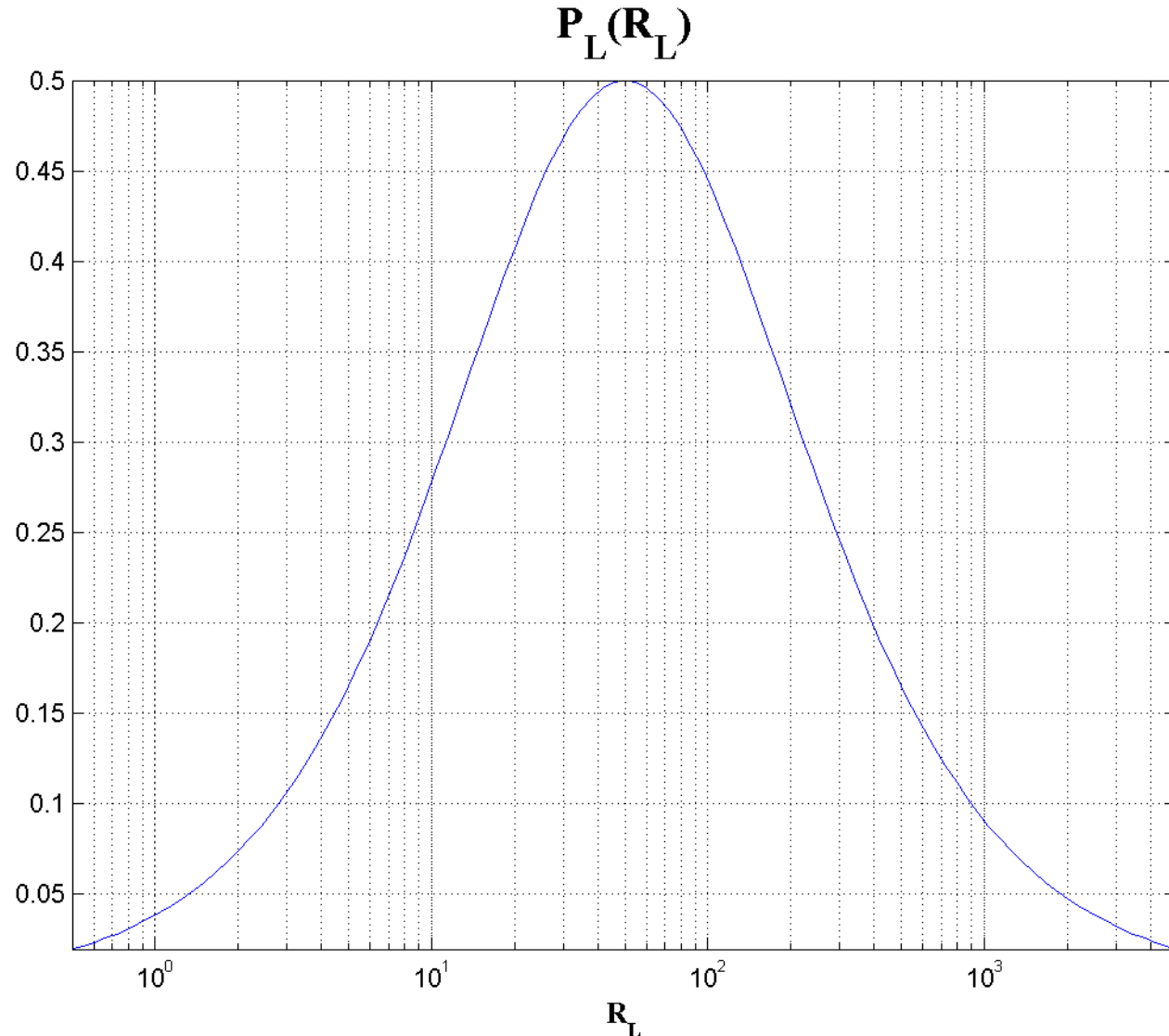

Matching, complex impedances

- Source matched to load

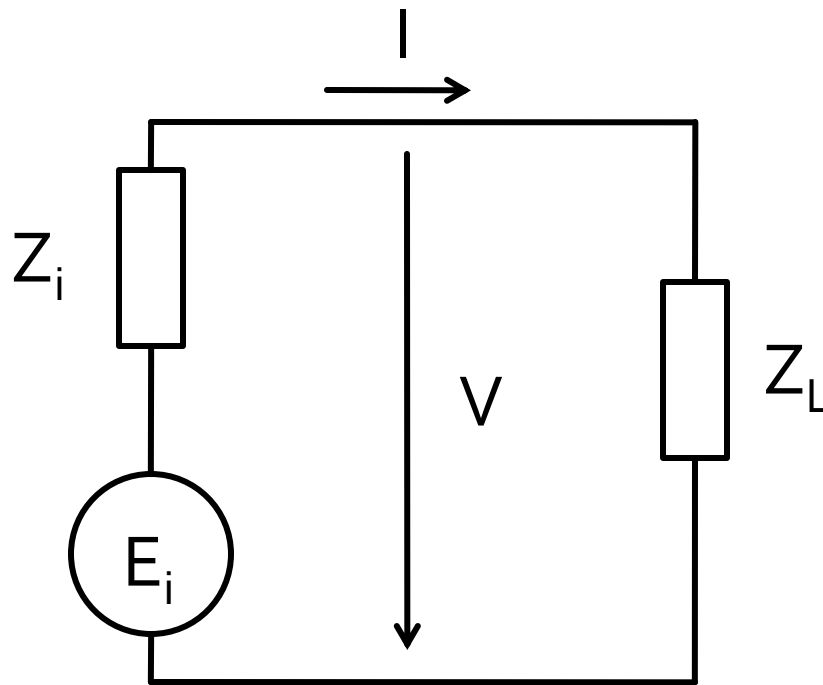

$$I = \frac{E_i}{Z_i + Z_L}$$

$$V = \frac{E_i \cdot Z_L}{Z_i + Z_L}$$

$$P_L = \operatorname{Re}\{Z_L \cdot |I|^2\}$$

$$P_L = \operatorname{Re}\{Z_L\} \cdot \left| \frac{E_i}{Z_i + Z_L} \right|^2$$

Matching

$$P_L = \frac{R_L \cdot |E_i|^2}{|Z_i + Z_L|^2} = \frac{R_L \cdot |E_i|^2}{|(R_i + R_L) + j \cdot (X_i + X_L)|^2}$$

$$|a + j \cdot b| = \sqrt{a^2 + b^2}$$


$$P_L = \frac{R_L \cdot |E_i|^2}{(R_i + R_L)^2 + (X_i + X_L)^2}$$

- Matching
 - maximum power transmitted to the load
 - condition?


Matching, example

- $E = 10\text{V}$
- $Z_i = 50\ \Omega + j\cdot 50\ \Omega$
- $P_L(Z_L)$?


$$P_L = \frac{R_L \cdot |E_i|^2}{(R_i + R_L)^2 + (X_i + X_L)^2}$$

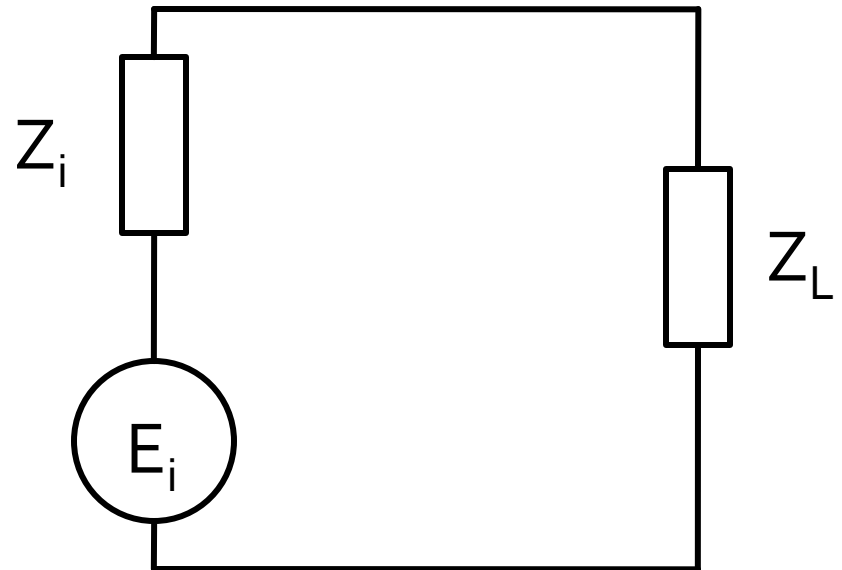

Matching, example

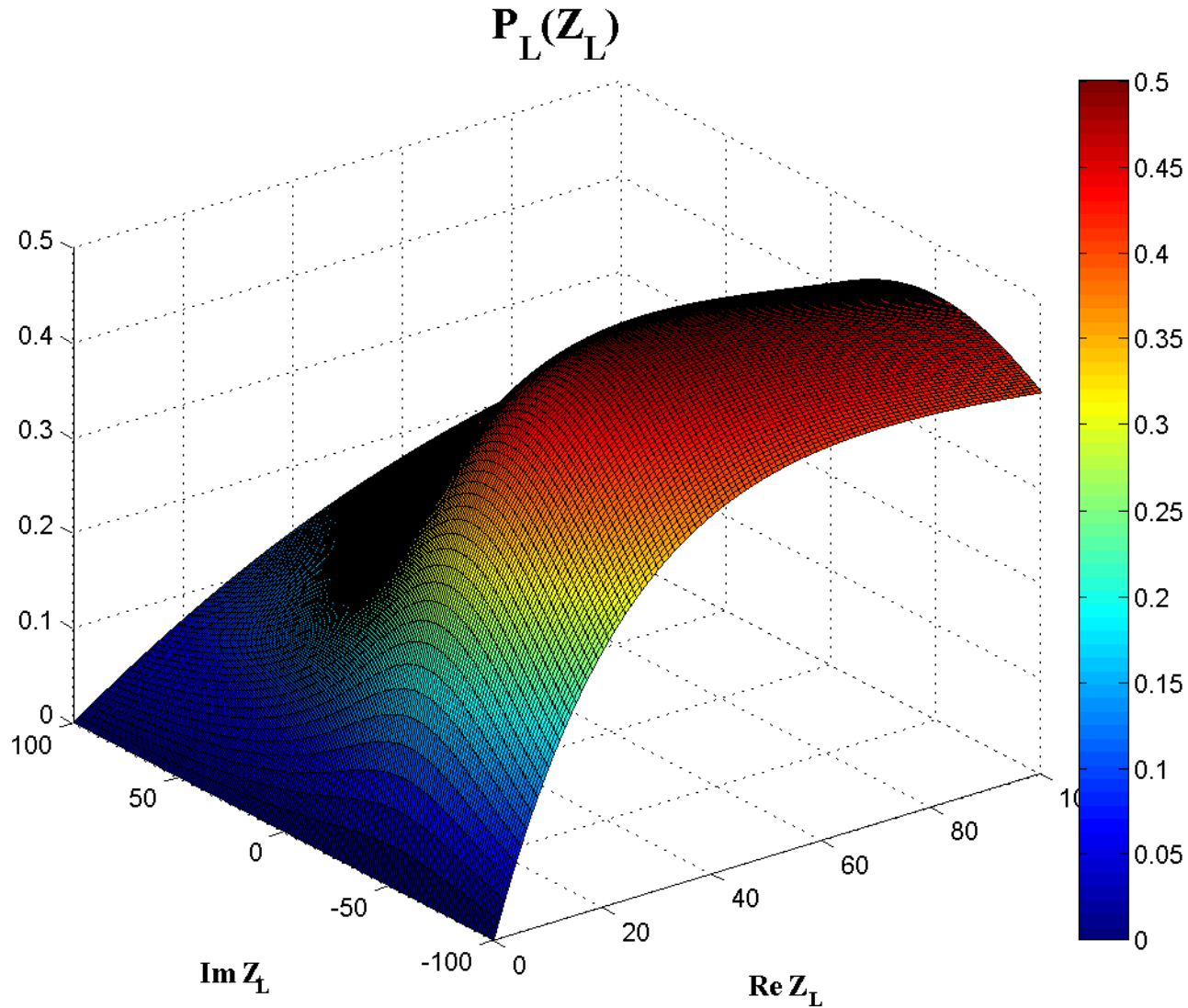

Matching, example

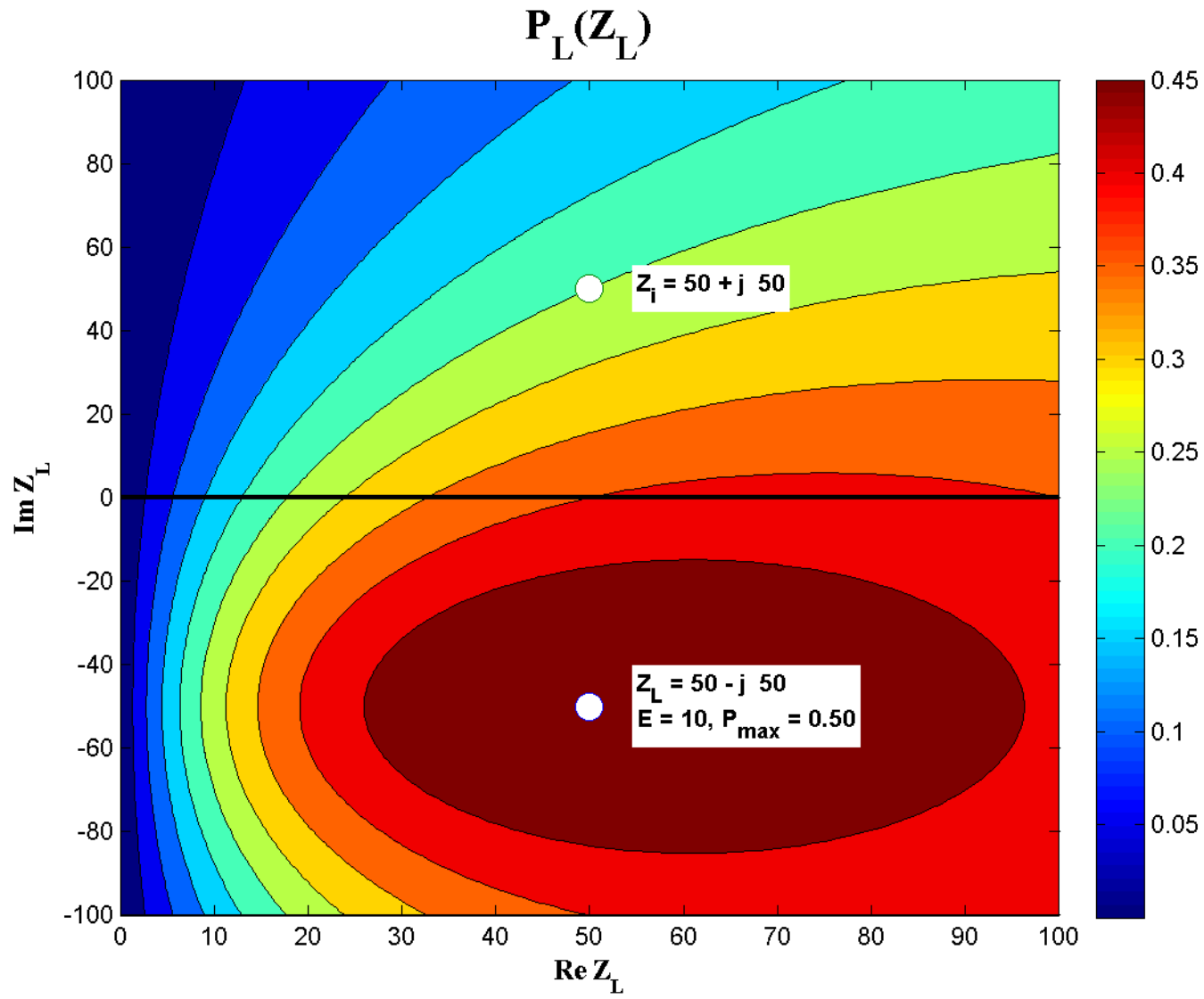

Matching , from the point of view of power transmission

$$R_i > 0, R_L > 0 \quad P_L = \frac{|E_i|^2}{4R_i + \frac{(R_i - R_L)^2}{R_L} + \frac{(X_i + X_L)^2}{R_L}}$$


$$P_{L\max} = \frac{|E_i|^2}{4R_i} \equiv P_a \quad R_L = R_i, X_L = -X_i$$

- P_a : Available Power


$$Z_L = Z_i^*$$

Reflection coefficient


- Any impedance Z_0 chosen as reference

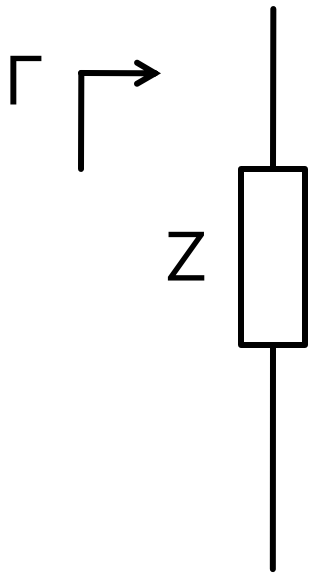

$$\Gamma = \frac{Z - Z_0^*}{Z + Z_0}$$

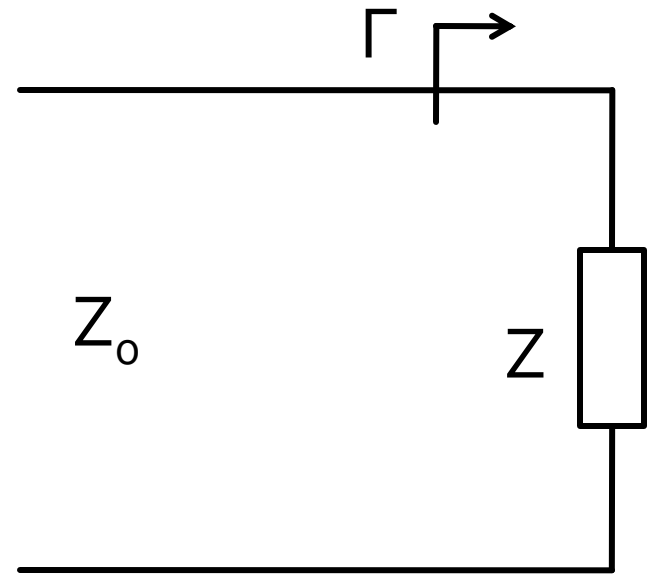

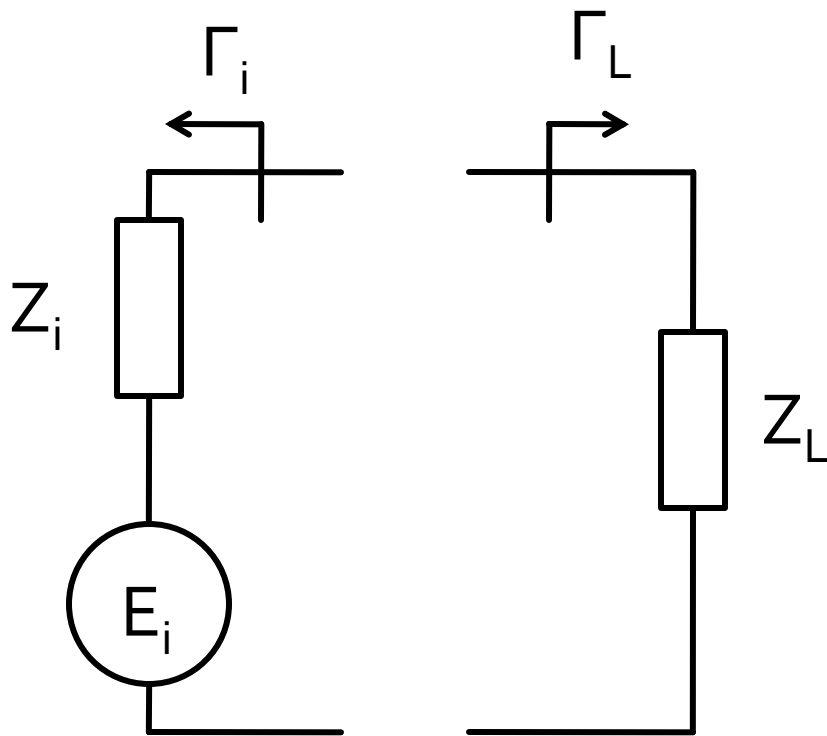Matching , from the point of view of power transmission




$$\Gamma_i = \frac{Z_i - Z_0^*}{Z_i + Z_0}$$

$$\Gamma_i = \frac{(R_i - R_0) + j \cdot (X_i + X_0)}{(R_i + R_0) + j \cdot (X_i + X_0)}$$

$$\Gamma_L = \frac{Z_L - Z_0^*}{Z_L + Z_0}$$

$$\Gamma_L = \frac{(R_L - R_0) + j \cdot (X_L + X_0)}{(R_L + R_0) + j \cdot (X_L + X_0)}$$

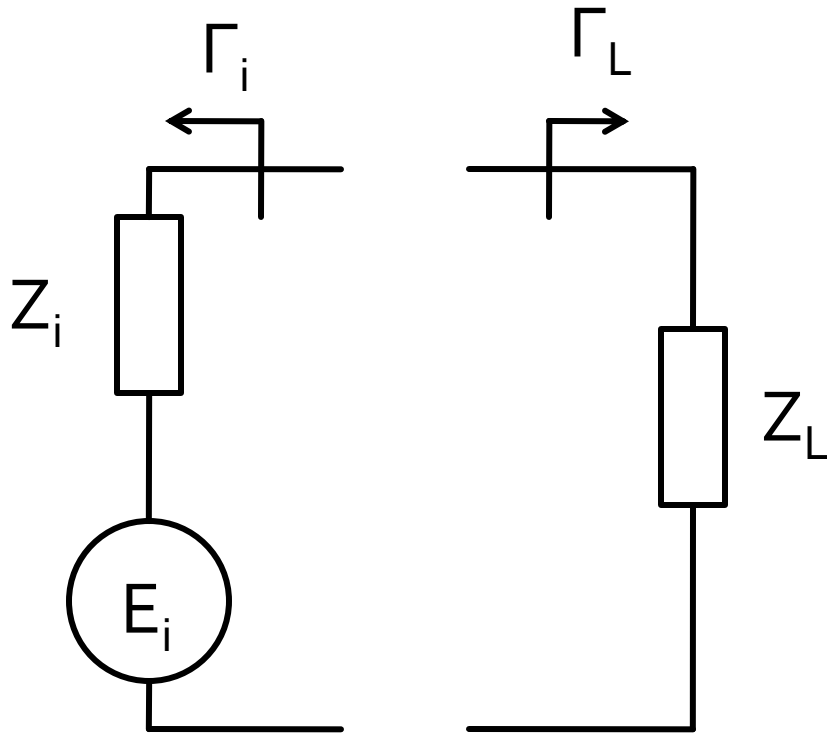Matching , from the point of view of power transmission



$$\Gamma_i = \frac{Z_i - Z_0^*}{Z_i + Z_0} = 1 - \frac{Z_0 + Z_0^*}{Z_i + Z_0}$$

$$\Gamma_L = \frac{Z_L - Z_0^*}{Z_L + Z_0} = 1 - \frac{Z_0 + Z_0^*}{Z_L + Z_0}$$

$$\Gamma_i^* = 1 - \frac{Z_0^* + Z_0}{Z_i^* + Z_0^*} = 1 - \frac{Z_0^* + Z_0}{Z_L + Z_0^*}$$

Matching , from the point of view of power transmission


$$Z_L = Z_i^*$$

If we choose a real Z_0


$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

$$\Gamma_L = \Gamma_i^*$$

- complex numbers
- in the complex plane

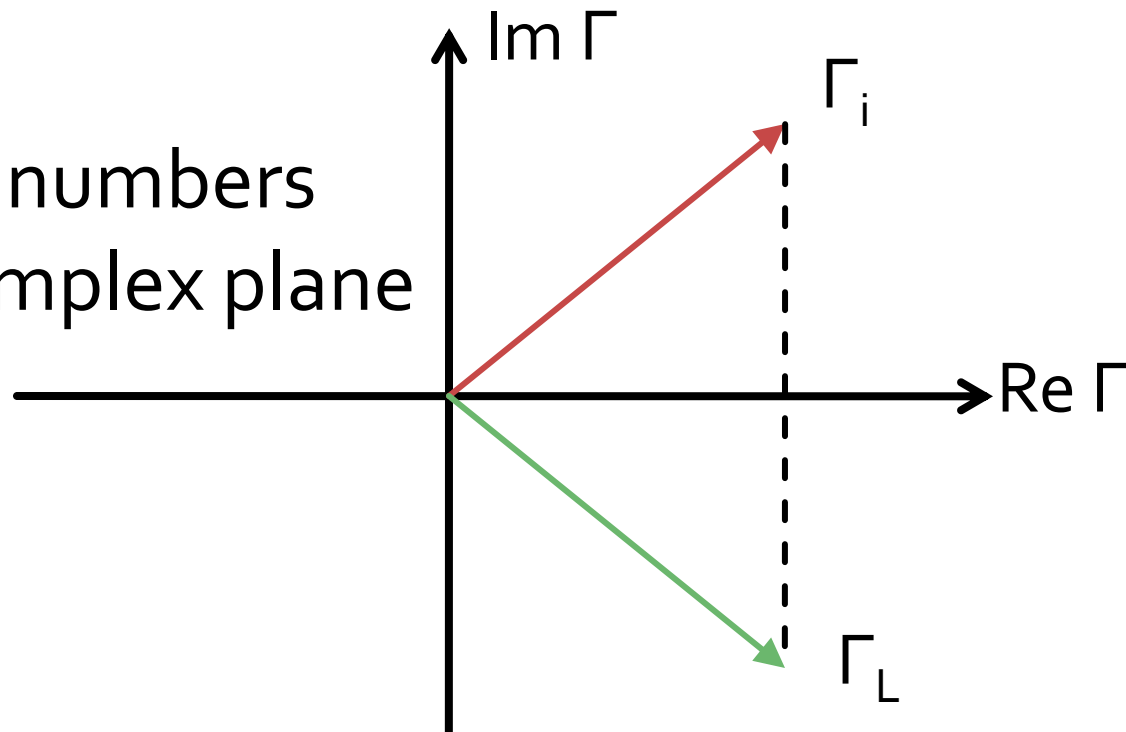


Reflection and power / Model

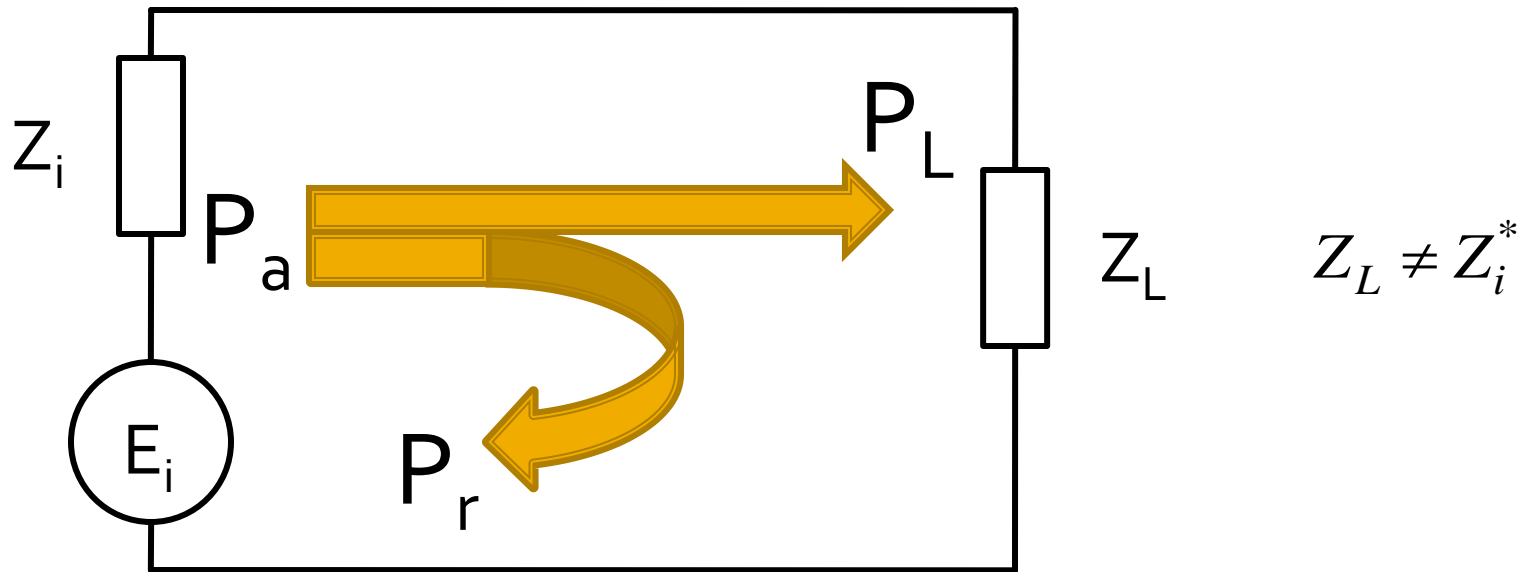


- ~~Power reflection~~
- Power of the reflected wave

Reflection and power / Model

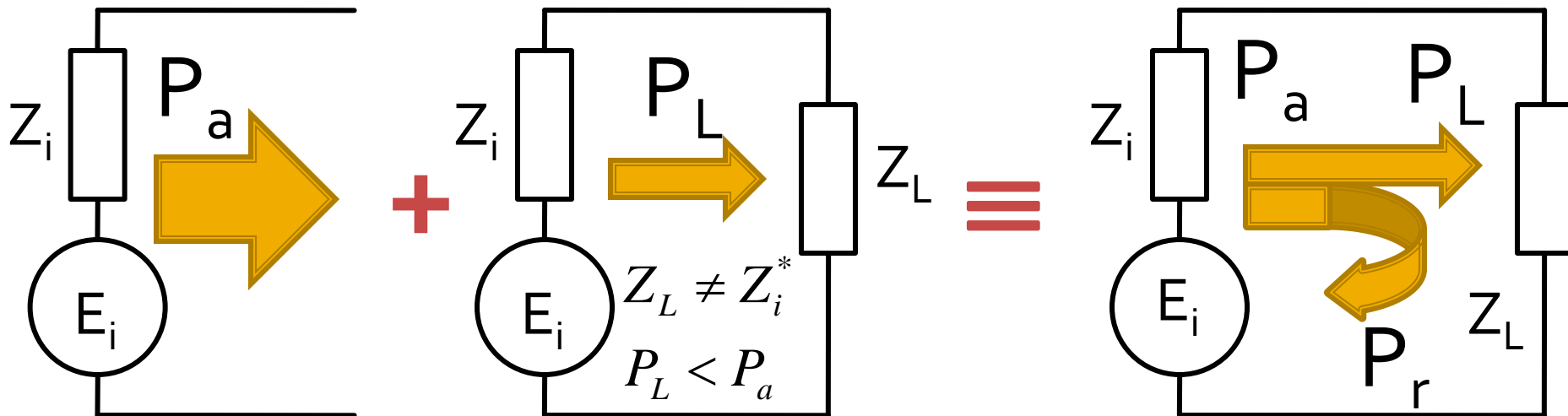


- The source has the ability to send to the load a certain maximum power (available power) P_a
- For a particular load the power sent to the load is less than the maximum (mismatch) $P_L < P_a$
- The phenomenon is **"as if"** (model) some of the power is reflected $P_r = P_a - P_L$
- The power is a **scalar** !

Reflection coefficient

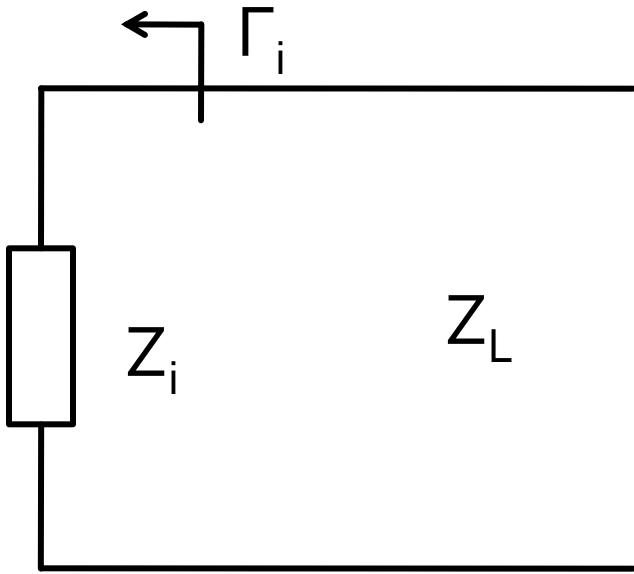
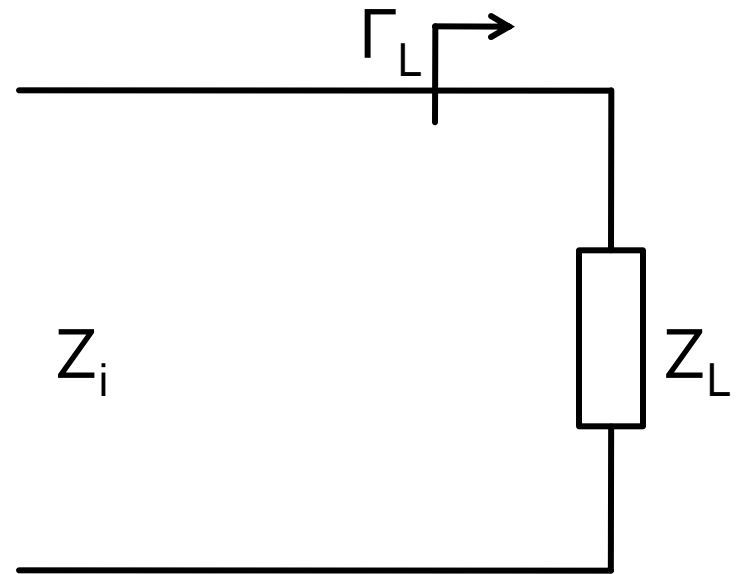
$$\Gamma_i = \frac{Z_i - Z_L^*}{Z_i + Z_L}$$



$$\Gamma_L = \frac{Z_L - Z_i^*}{Z_L + Z_i}$$


Reflection coefficient

$$\Gamma_i = \frac{(R_i - R_L) + j \cdot (X_i + X_L)}{(R_i + R_L) + j \cdot (X_i + X_L)} \quad \Gamma_L = \frac{(R_L - R_i) + j \cdot (X_L + X_i)}{(R_L + R_i) + j \cdot (X_L + X_i)}$$

$$|\Gamma_i| = \frac{|(R_i - R_L) + j \cdot (X_i + X_L)|}{|(R_i + R_L) + j \cdot (X_i + X_L)|} = \frac{\sqrt{(R_i - R_L)^2 + (X_i + X_L)^2}}{\sqrt{(R_i + R_L)^2 + (X_i + X_L)^2}} = |\Gamma_L|$$

$$|\Gamma_i| = |\Gamma_L| \equiv |\Gamma|$$

Reflection and power / Model

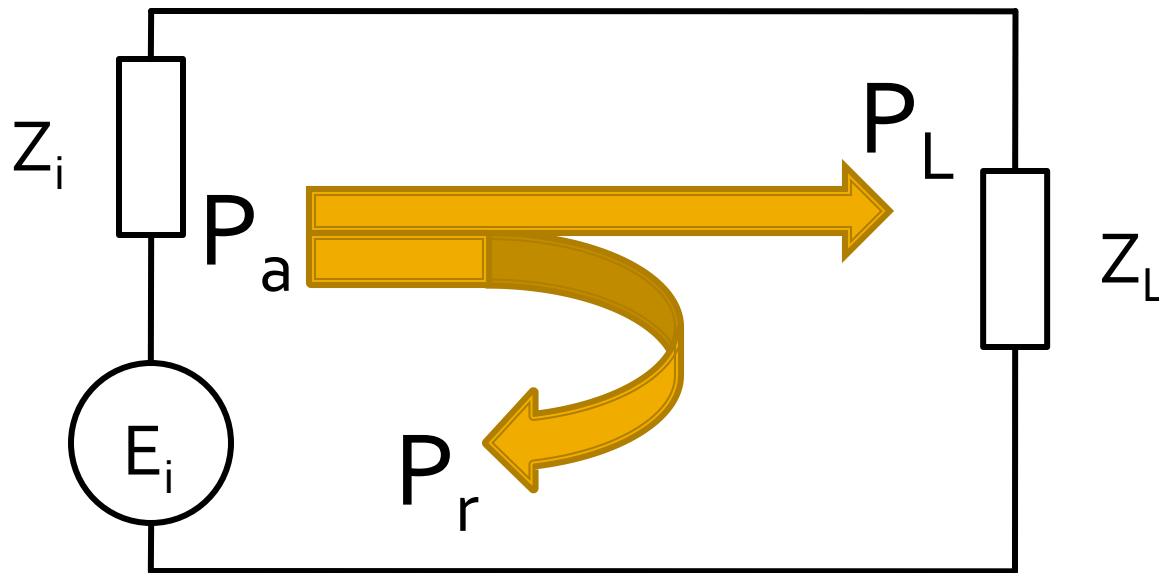

$$P_a = \frac{|E_i|^2}{4R_i}$$

$$P_L = \frac{R_L \cdot |E_i|^2}{(R_i + R_L)^2 + (X_i + X_L)^2}$$

$$P_r = P_a - P_L = \frac{|E_i|^2}{4R_i} - \frac{R_L \cdot |E_i|^2}{(R_i + R_L)^2 + (X_i + X_L)^2} = \frac{|E_i|^2}{4R_i} \cdot \left[1 - \frac{4R_L \cdot R_i}{(R_i + R_L)^2 + (X_i + X_L)^2} \right]$$

$$P_r = \frac{|E_i|^2}{4R_i} \cdot \left[\frac{(R_i - R_L)^2 + (X_i + X_L)^2}{(R_i + R_L)^2 + (X_i + X_L)^2} \right] = P_a \cdot |\Gamma|^2$$

- $|\Gamma|^2$ is a power reflection coefficient

The quarter-wave transformer



S-PARAMETERS


S_Param

SP1


Start=0.5 GHz

Stop=5.5 GHz

Step=0.001 GHz

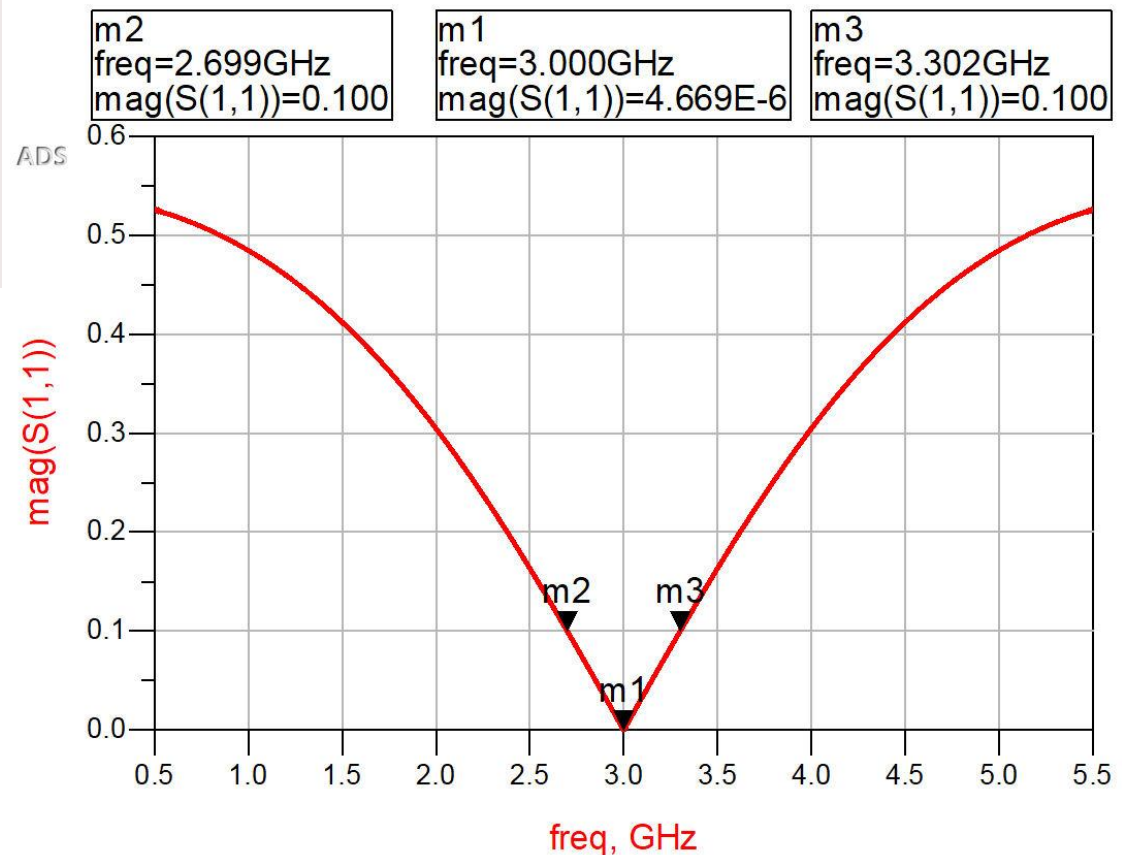


Binomial multisection transformer

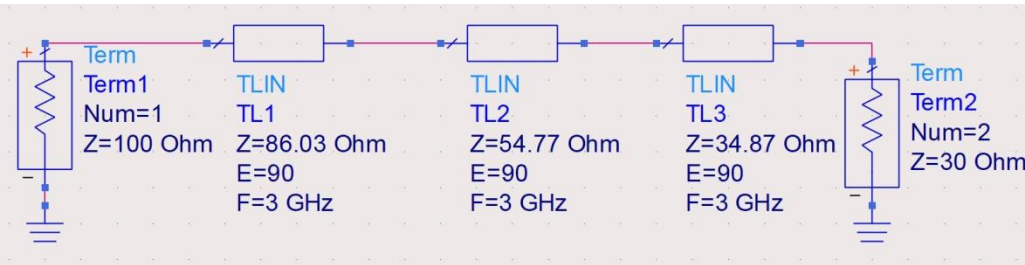

 S-PARAMETERS

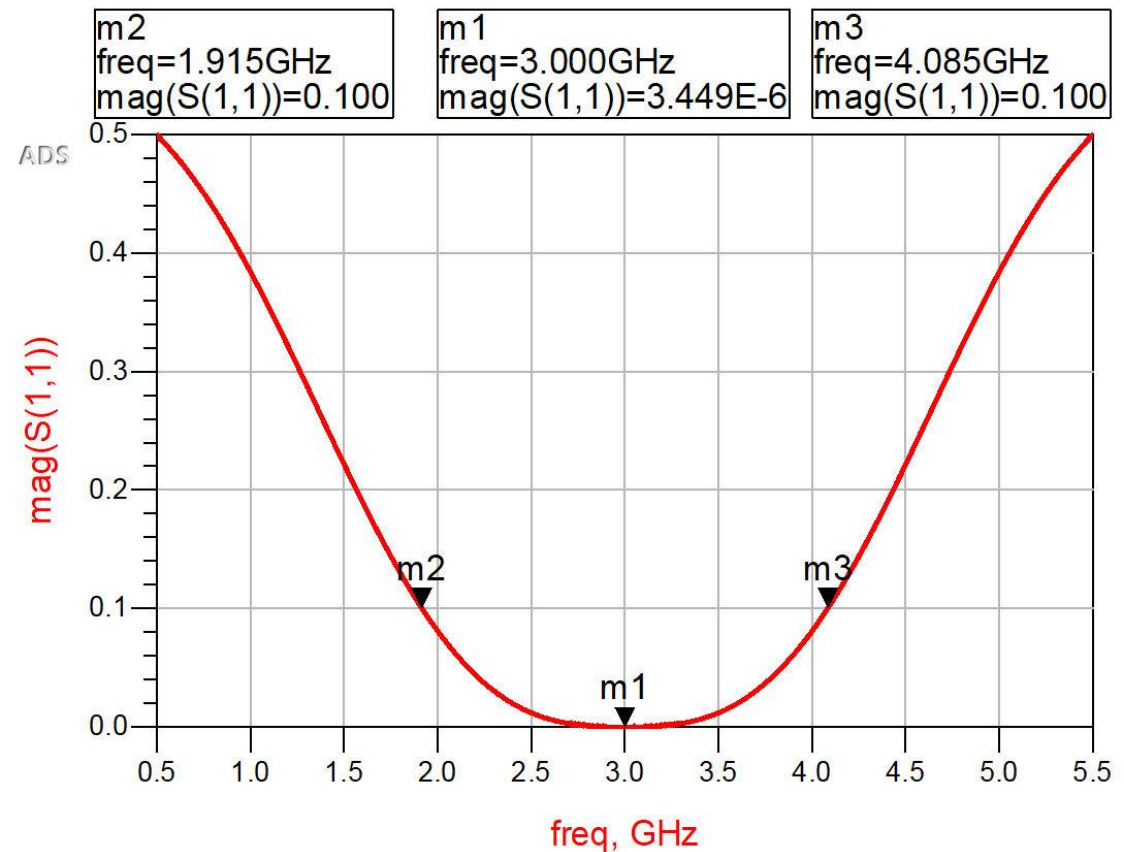S_Param
SP1
Start=0.5 GHz
Stop=5.5 GHz
Step=0.001 GHz




Chebyshev multisection transformer



 S-PARAMETERS

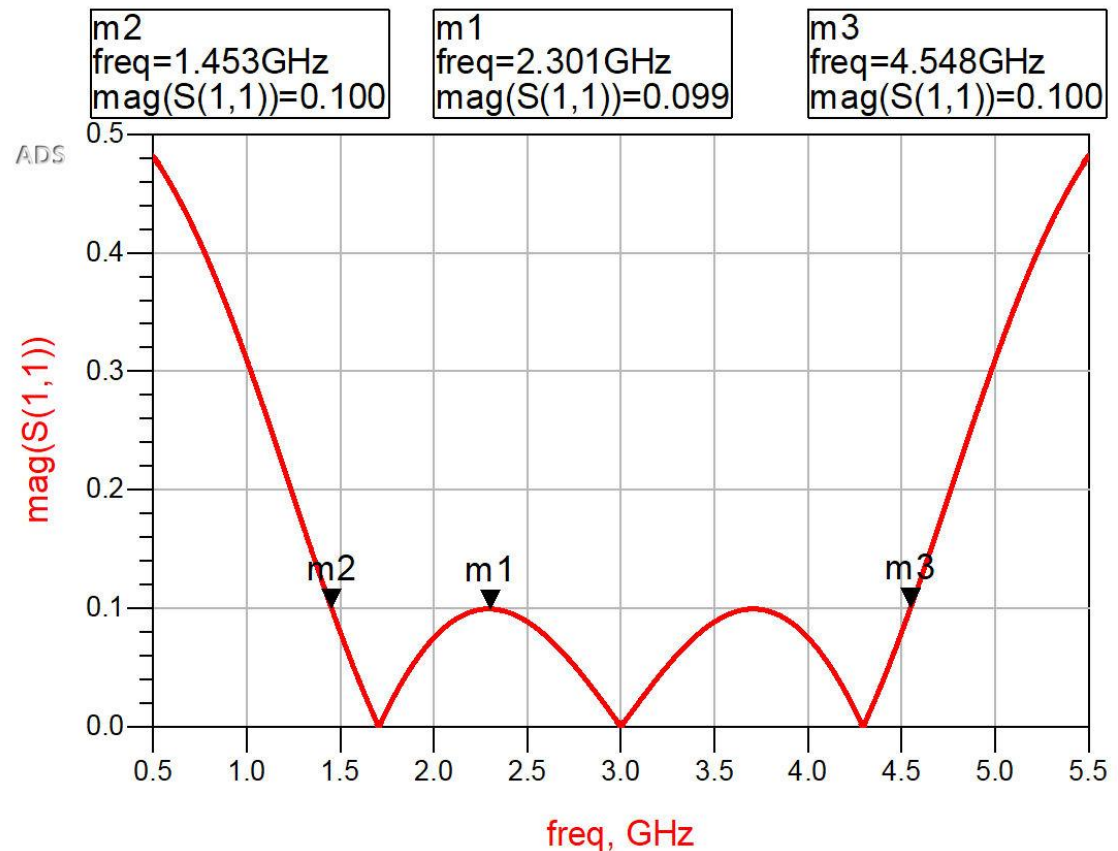
S_Param
SP1
Start=0.5 GHz
Stop=5.5 GHz
Step=0.001 GHz




Microwave Network Analysis

Network Analysis

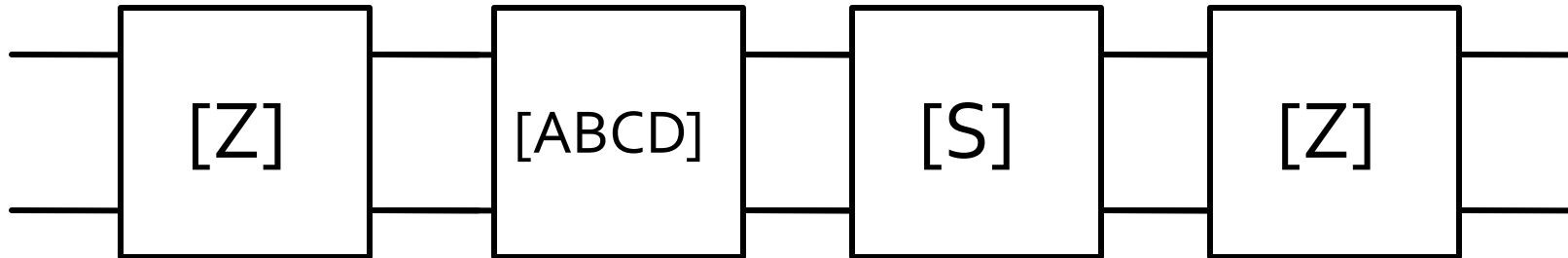- We try to separate a complex circuit into individual blocks
- These are analyzed separately (decoupled from the rest of the circuit) and are characterized only by the port level signals (**black box**)
- Network-level analysis allows you to put together individual block results and get a total result for the entire circuit



Impedance matrix – Z

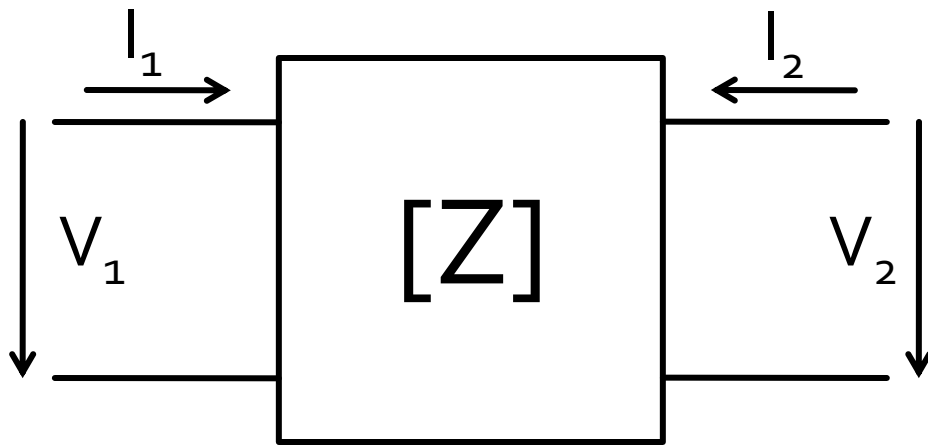

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_1 = Z_{11} \cdot I_1 + Z_{12} \cdot I_2$$


$$V_2 = Z_{21} \cdot I_1 + Z_{22} \cdot I_2$$

$$V_1 = Z_{11} \cdot I_1 \Big|_{I_2=0} \quad Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

- Z_{11} – input impedance with open-circuited output

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \quad Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

Admittance matrix – Y

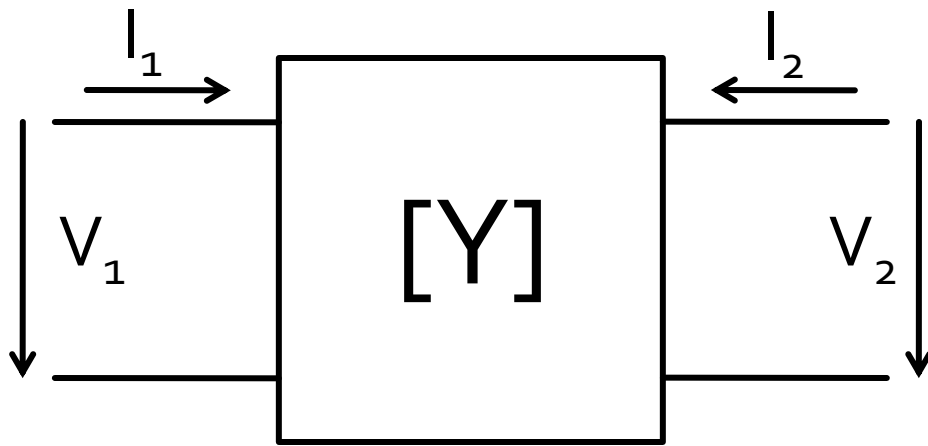

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = Y_{11} \cdot V_1 + Y_{12} \cdot V_2$$


$$I_2 = Y_{21} \cdot V_1 + Y_{22} \cdot V_2$$

$$I_1 = Y_{11} \cdot V_1 \Big|_{V_2=0} \quad Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

- Y_{11} – input admittance with short-circuited output

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} \quad Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \quad Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

Hybrid matrices – H and G

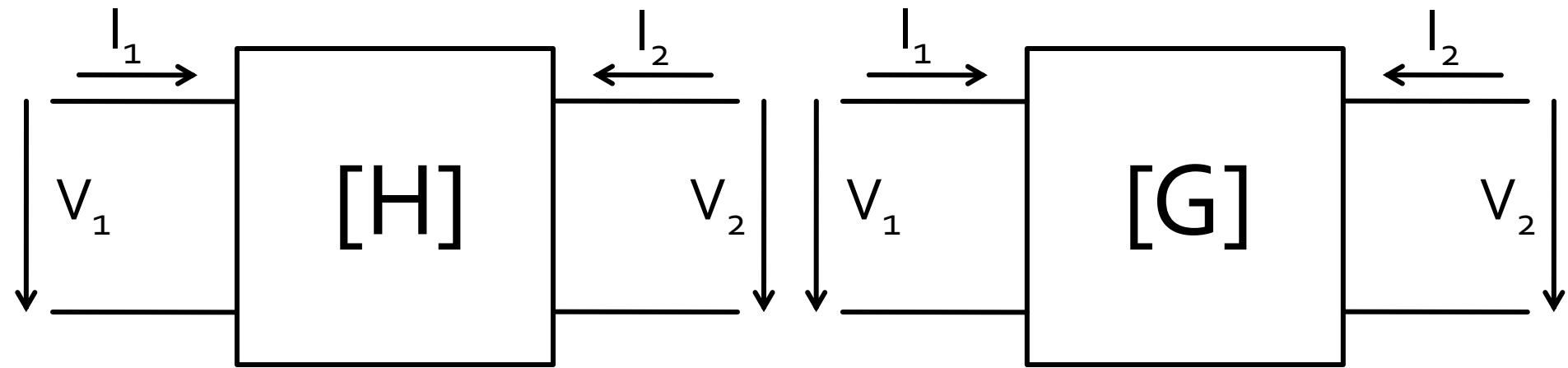

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} H_{11} & H_{12} \\ H_{21} & H_{22} \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$H_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0 \text{ sau } H_{22} \rightarrow \infty}$$

- h_{21E} widely used for Bipolar Transistors, common emitter topology (or β , $h_{22E} \gg$)


Network Analysis

- Each matrix is best suited for a particular mode of port excitation (V, I)
 - matrix H in common emitter connection for TB: I_B, V_{CE}
 - matrices provide the associated quantities depending on the “attack” ones
- Traditional notation of Z, Y, G, H parameters is in lowercase (z, y, g, h)
- In microwave analysis we prefer the notation in uppercase to avoid confusion with the normalized parameters

$$z = \frac{Z}{Z_0} \quad y = \frac{Y}{Y_0} = \frac{1/Z}{1/Z_0} = \frac{Z_0}{Z} = Z_0 \cdot Y$$

$$z_{11} = \frac{Z_{11}}{Z_0} \quad y_{11} = \frac{Y_{11}}{Y_0} = Z_0 \cdot Y_{11}$$

ABCD (transmission) matrix

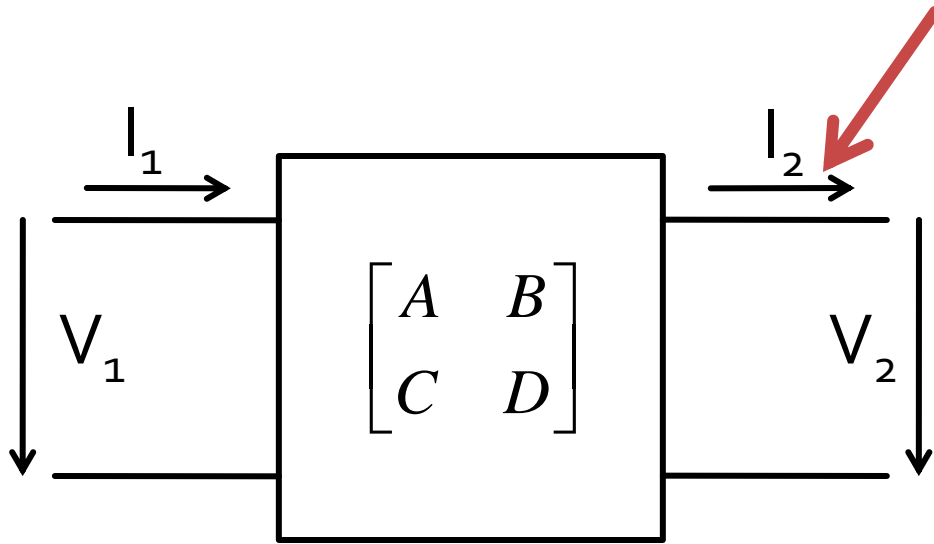

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \cdot \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$V_1 = A \cdot V_2 + B \cdot I_2$$

$$I_1 = C \cdot V_2 + D \cdot I_2$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \frac{1}{A \cdot D - B \cdot C} \cdot \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$


$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0}$$



ABCD (transmission) matrix

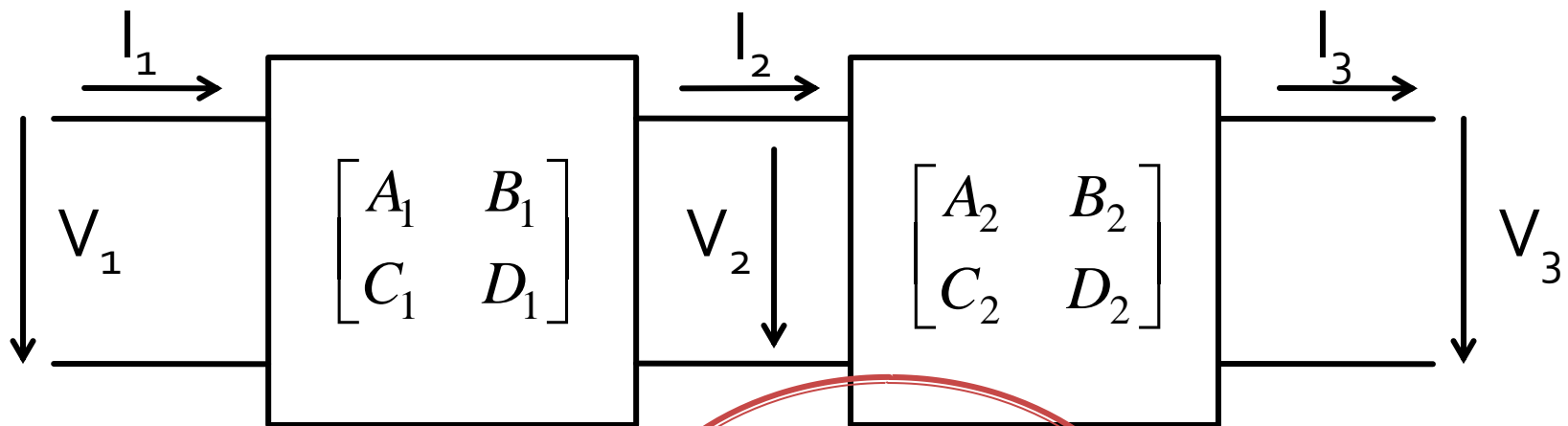- This 2X2 matrix characterizes the “input”/“output” relation
- Allows easy chaining of multiple two-ports



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \cdot \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \cdot \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \cdot \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

ABCD (transmission) matrix

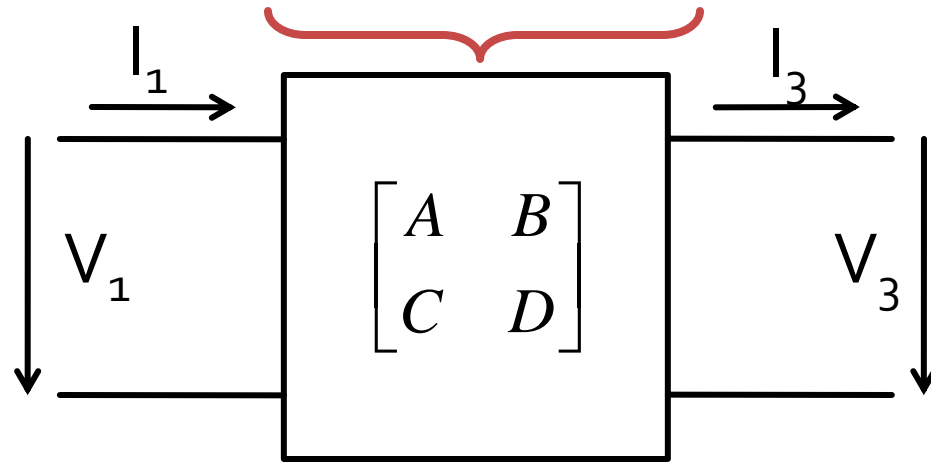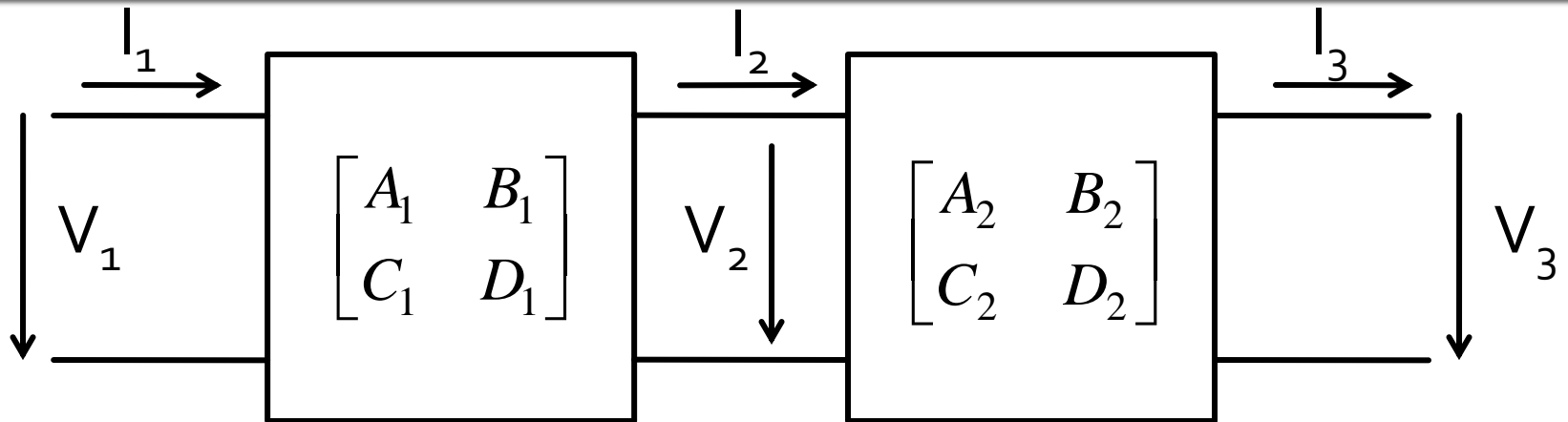


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \cdot \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

ABCD (transmission) matrix

- suitable **only** for two-port networks (Z, Y can be easily extended for multiport / n -ports)
- allows easy coupling of multiple elements
- allows the calculation of complex circuits with one input and one output by breaking them in individual component blocks
- a library of ABCD matrices for elementary two-port networks can be built up

Library of ABCD matrices

- Series impedance

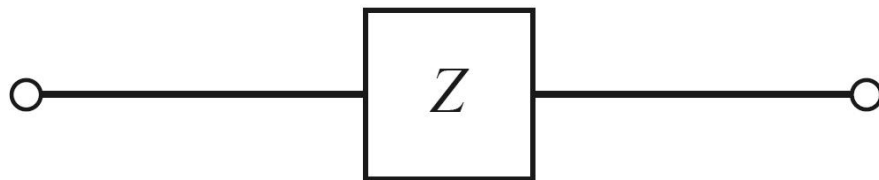

$$A = 1$$

$$B = Z$$

$$C = 0$$

$$D = 1$$

$$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1$$


$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0} = \frac{V_1}{V_1/Z} = Z$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = 0$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0} = \frac{I_1}{I_1} = 1$$

Library of ABCD matrices

- Shunt admittance

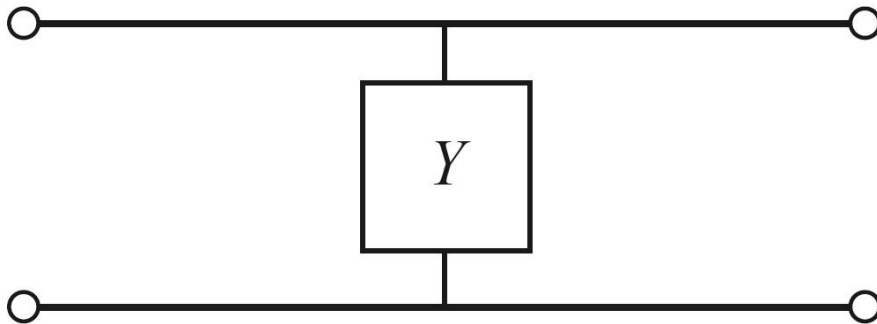


$$\begin{array}{ll} A=1 & B=0 \\ C=Y & D=1 \end{array}$$

$$\begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

Homework!

Library of ABCD matrices

- Transmission line

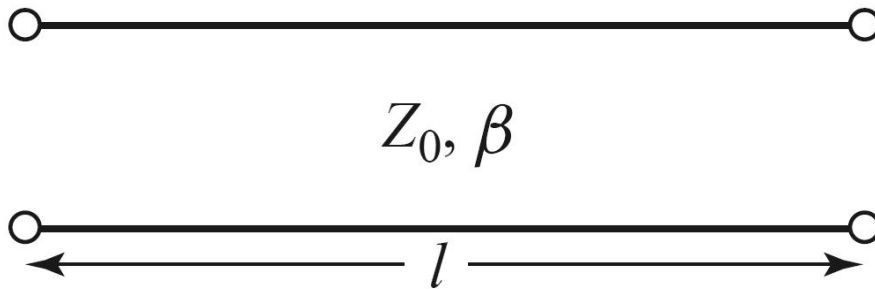

$$A = \cos \beta \cdot l$$

$$B = j \cdot Z_0 \cdot \sin \beta \cdot l$$

$$C = j \cdot Y_0 \cdot \sin \beta \cdot l$$

$$D = \cos \beta \cdot l$$


Homework!

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

$$\begin{bmatrix} \cos \beta \cdot l & j \cdot Z_0 \cdot \sin \beta \cdot l \\ j \cdot Y_0 \cdot \sin \beta \cdot l & \cos \beta \cdot l \end{bmatrix}$$

Library of ABCD matrices

- Transformer

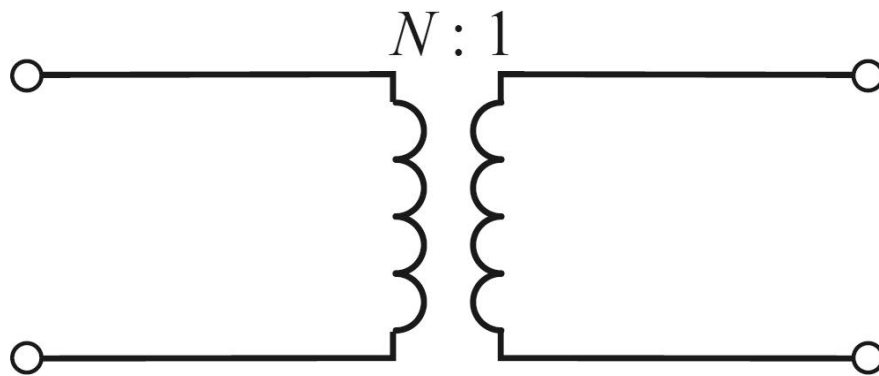

$$A = N$$

$$B = 0$$

$$C = 0$$


$$D = \frac{1}{N}$$

$$\begin{bmatrix} N & 0 \\ 0 & \frac{1}{N} \end{bmatrix}$$

Homework!

Library of ABCD matrices

- π network

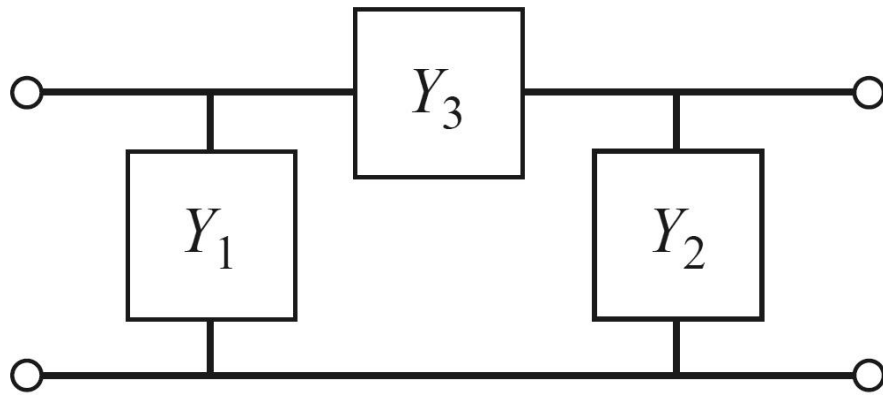

$$A = 1 + \frac{Y_2}{Y_3}$$

$$B = \frac{1}{Y_3}$$


$$C = Y_1 + Y_2 + \frac{Y_1 \cdot Y_2}{Y_3}$$

$$D = 1 + \frac{Y_1}{Y_3}$$

Homework!

Library of ABCD matrices

- T network

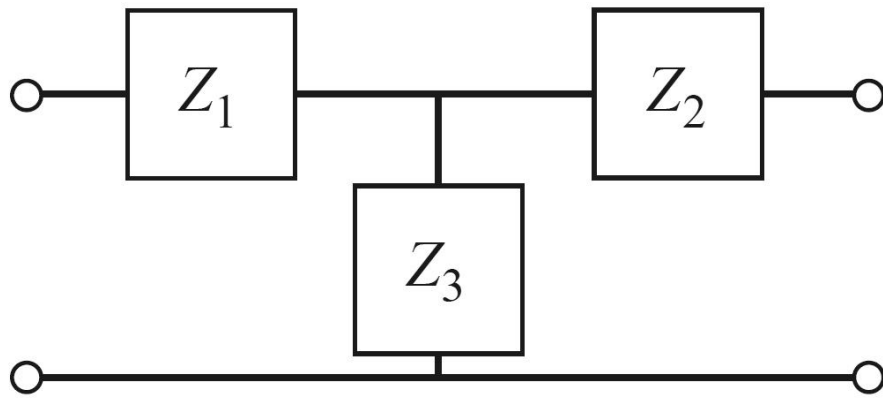

$$A = 1 + \frac{Z_1}{Z_3}$$

$$B = Z_1 + Z_2 + \frac{Z_1 \cdot Z_2}{Z_3}$$


$$C = \frac{1}{Z_3}$$

$$D = 1 + \frac{Z_2}{Z_3}$$

Homework!

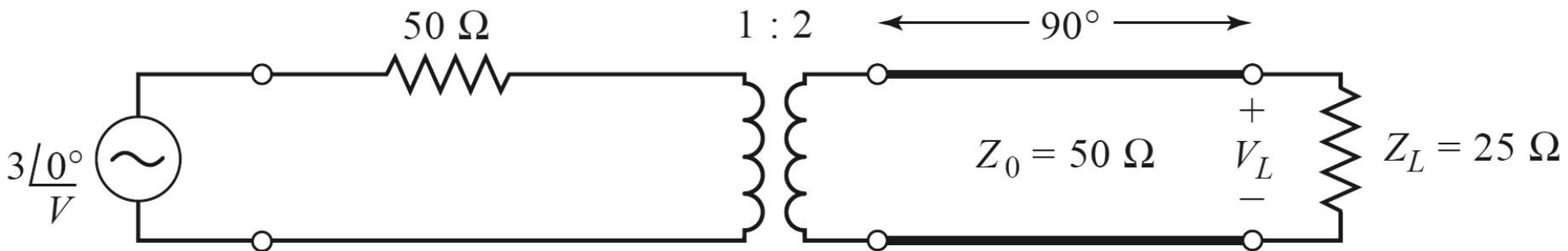
Example for ABCD matrix

- Find the voltage V_L across the load resistor in the circuit shown below



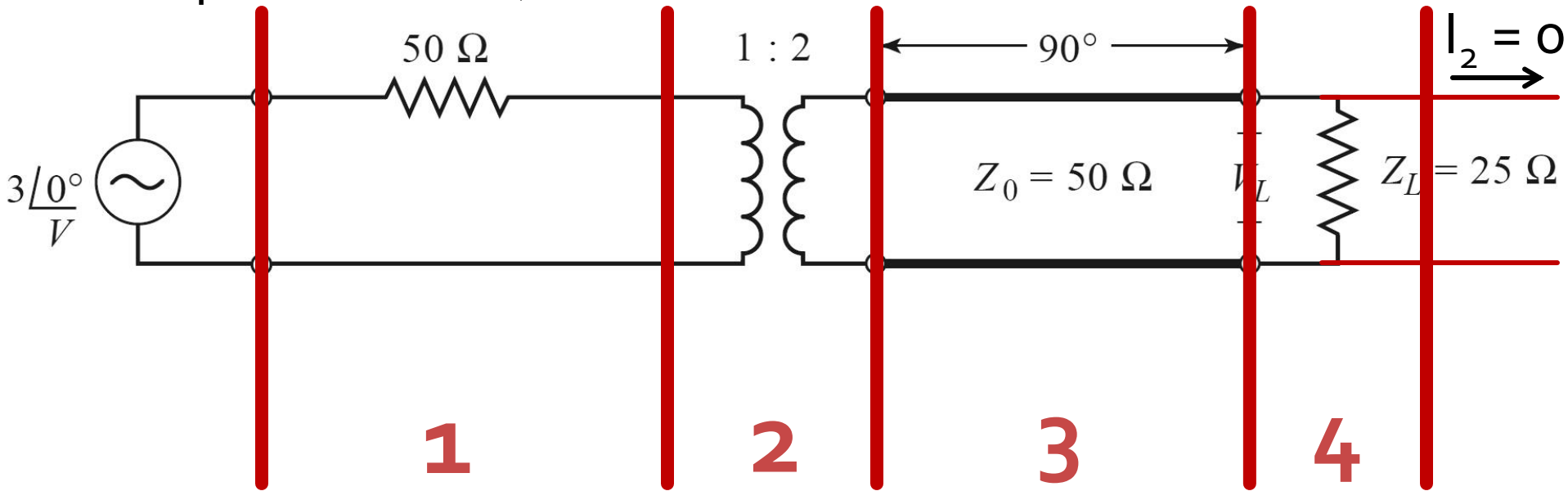Example for ABCD matrix


- We break the circuit in elementary sections
- Sources are left outside
- If necessary, input and output ports are created (and left open-circuited)



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = M_1 \cdot M_2 \cdot M_3 \cdot M_4 \quad V_1 = A \cdot V_2 + B \cdot I_2 \Big|_{I_2=0} \quad V = A \cdot V_L \rightarrow V_L = \frac{V}{A}$$

Example for ABCD matrix


- M_1 , series impedance

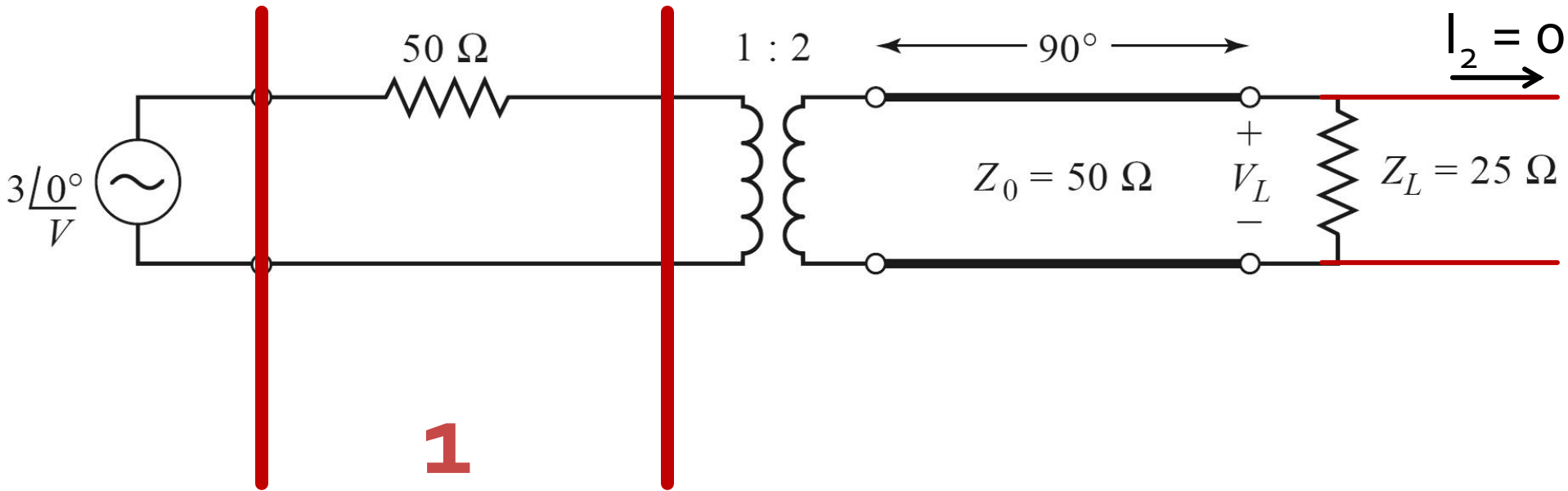

$$M_1 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 50 \\ 0 & 1 \end{bmatrix}$$

Example for ABCD matrix


- M_2 , 1:2 transformer

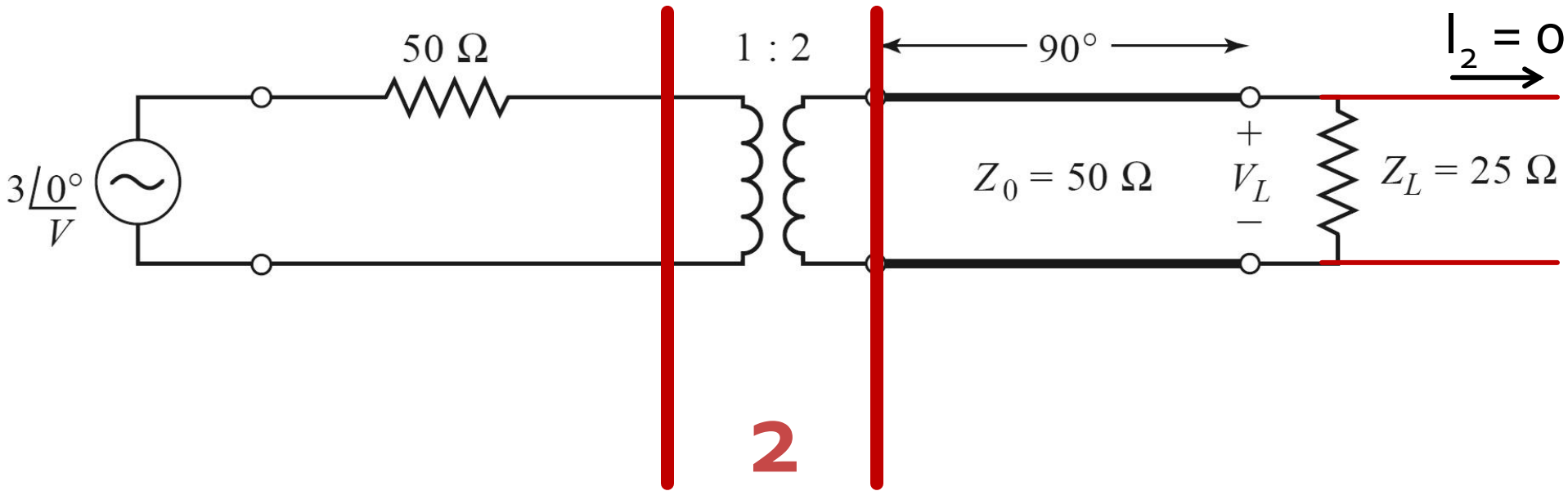

$$M_2 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1/2 & 0 \\ 0 & 2 \end{bmatrix}$$

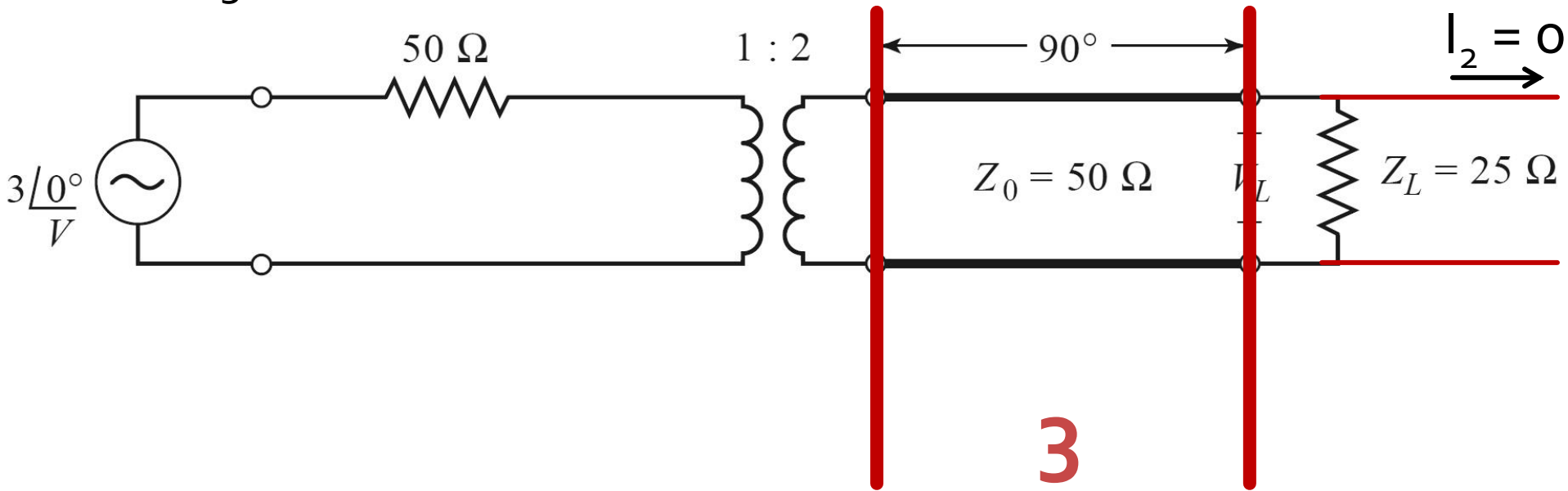Example for ABCD matrix


- M_3 , series transmission line, $E = 90^\circ$



$$M_3 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0 & 50 \cdot j \\ j & 0 \end{bmatrix}$$


Example for ABCD matrix

- M_4 , shunt impedance/admittance

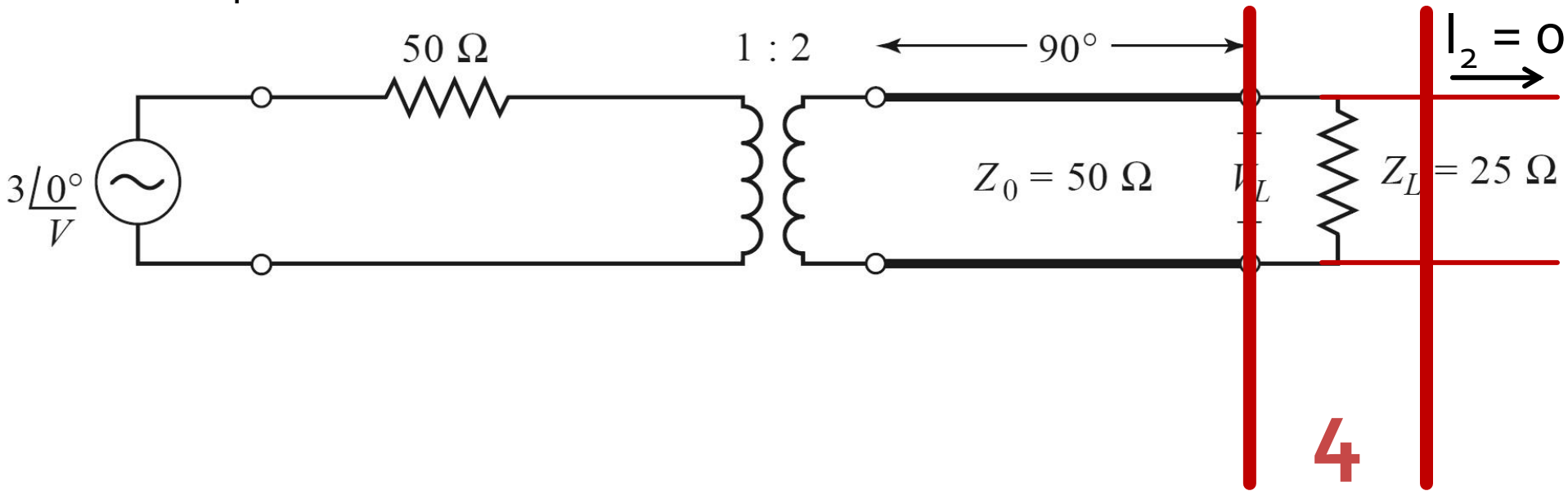

$$M_4 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{25} & 1 \end{bmatrix}$$

Example for ABCD matrix

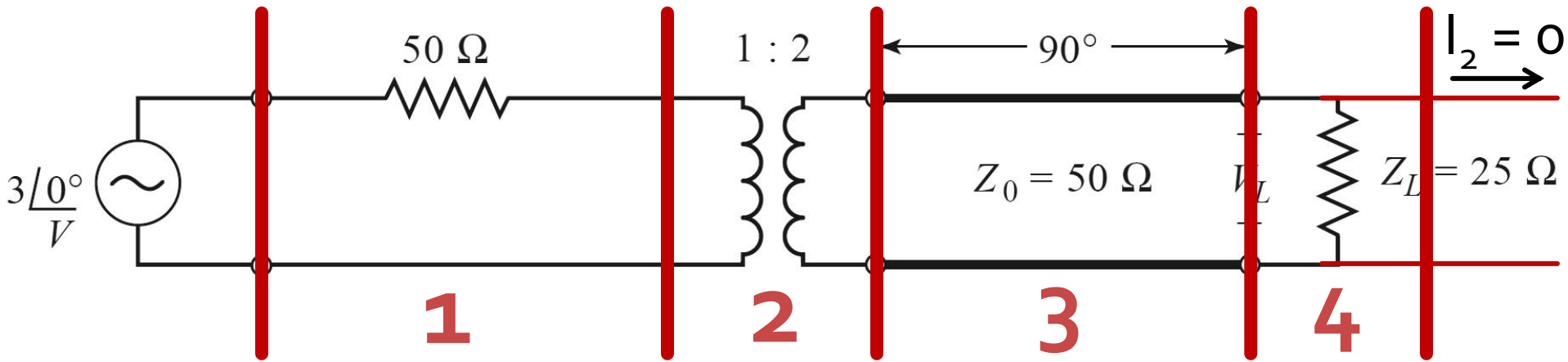

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 50 \\ 0 & 1 \end{bmatrix} \cdot \begin{bmatrix} 1 & 0 \\ 0 & 2 \end{bmatrix} \cdot \begin{bmatrix} 0 & 50 \cdot j \\ j & 0 \end{bmatrix} \cdot \begin{bmatrix} 1 & 0 \\ \frac{1}{25} & 1 \end{bmatrix} = \begin{bmatrix} 3 \cdot j & 25 \cdot j \\ \frac{j}{25} & 0 \end{bmatrix}$$

$$V_L = \frac{V}{A} = \frac{3\angle 0^\circ}{3 \cdot j} = 1\angle 90^\circ$$

Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.etti.tuiasi.ro>
- rdamian@etti.tuiasi.ro