

Lecture 5  
2017/2018

# Microwave Devices and Circuits for Radiocommunications

# Materials

- RF-OPTO
  - <http://rf-opto.etti.tuiasi.ro>
- **David Pozar, “Microwave Engineering”,**  
Wiley; 4th edition , 2011
  - 1 exam problem ← Pozar
- Photos
  - sent by email: [rdamian@etti.tuiasi.ro](mailto:rdamian@etti.tuiasi.ro)
  - used at lectures/laboratory

# Photos

Grupa 5403

| Nr. | Student                  | Prezent                                                  | Nr. | Student                   | Prezent                                                             | Nr. | Student                   | Prezent                                                  |
|-----|--------------------------|----------------------------------------------------------|-----|---------------------------|---------------------------------------------------------------------|-----|---------------------------|----------------------------------------------------------|
| 1   | ANGHELUS<br>DOMIT-MARIUS | <input type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs: | 2   | ANTIGHIN<br>FLORIN-RAZVAN | <input type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs:            | 3   | ANTONICA<br>BIANCA        | <input type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs: |
| 4   | APOSTOL<br>PAVEL-MANUEL  | <input type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs: | 5   | BALASCA<br>TALIAN-PETRU   | <input checked="" type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs: | 6   | BOSTAN<br>ANDREI-PETRICU  | <input type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs: |
| 7   | BOTEZAT<br>EMANUEL       | <input type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs: | 8   | BUTUNOI<br>GEORGE-MADALIN | <input type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs:            | 9   | CHILEA<br>SALUCA-MARIA    | <input type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs: |
| 10  | CHRISTOIU<br>ECATERINA   | <input type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs: | 11  | COJOC<br>MARIUS           | <input checked="" type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs: | 12  | COJOCARIU<br>AUSA-FLORINA | <input type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs: |

| Nr. | Student                   | Prezent                                                  |
|-----|---------------------------|----------------------------------------------------------|
| 2   | ANTIGHIN<br>FLORIN-RAZVAN | <input type="checkbox"/><br>Puncte: 0<br>Nota: 0<br>Obs: |

# Access

## ■ Not customized



A screenshot of a student profile page. On the left is a small, pixelated portrait of a man. To the right of the portrait, the text "Date:" is followed by a table containing student information. Below the table, there is a link "Acceseaza ca acest student" which is circled in red. At the bottom of the page is a table titled "Note obtinute" (Obtained Grades) with columns for Discipline, Type, Date, Description, Grade, Points, and Observations. The table contains four rows of data for the subject "Tehnologii Web".

**Date:**

|               |                                          |
|---------------|------------------------------------------|
| Grupa         | 5304 (2015/2016)                         |
| Specializarea | Tehnologii si sisteme de telecomunicatii |
| Marca         | 5184                                     |

[Acceseaza ca acest student](#)

**Note obtinute**

| Disciplina | Tip | Data       | Descriere                          | Nota | Puncte | Obs. |
|------------|-----|------------|------------------------------------|------|--------|------|
| TW         |     |            | Tehnologii Web                     |      |        |      |
|            | N   | 17/01/2014 | Nota finala                        | 10   | -      |      |
|            | A   | 17/01/2014 | Colocviu Tehnologii Web 2013/2014  | 10   | 7.55   |      |
|            | B   | 17/01/2014 | Laborator Tehnologii Web 2013/2014 | 9    | -      |      |
|            | D   | 17/01/2014 | Tema Tehnologii Web 2013/2014      | 9    | -      |      |



A screenshot of a login form. It has a light blue background. The form contains several input fields and a button. The "Nume" (Name) field is filled with "IACOBSCUIN" and is underlined in red. The "Email" field is empty and circled in red. The "Cod de verificare" (Verification code) field is empty and circled in red. Below the verification code field is a large, stylized blue number "344bd9f" with a grid pattern over it. At the bottom is a button labeled "Trimite" (Send).

Nume  
IACOBSCUIN

Email

Cod de verificare

344bd9f

Trimite

# Software

- ADS 2016
- EmPro 2015
- based on IP from outside university or campus



Date:

|               |                              |
|---------------|------------------------------|
| Grupa         | 5601 (2017/2018)             |
| Specializarea | Master Retele de Comunicatii |
| Marca         | 857                          |

[Acceseaza ca acest student](#) | [Cere acces la licente](#)

Note obtinute

| Disciplina | Tip | Data       | Descriere                                        | Nota | Puncte | Obs. |
|------------|-----|------------|--------------------------------------------------|------|--------|------|
| TMPAW      |     |            | Tehnici moderne de proiectare a aplicatiilor web |      |        |      |
|            | N   | 29/05/2017 | Nota finala                                      | 10   | -      |      |

Nume

Email

Cod de verificare

Trimite

# Software

## Advanced Design System Premier High-Frequency and High Speed Design Platform

2016.01



© Keysight Technologies 1985-2016

Advanced Design System

Select a product license

You have more than one product

Description

ADS Inclusive

GoldenGate All In

Update Availability

Legend: License available License in use or not available

ADS Inclusive


License is available

Number of licenses: 50

Used: 3


Version: 2018.07

Expires: 30-jul-

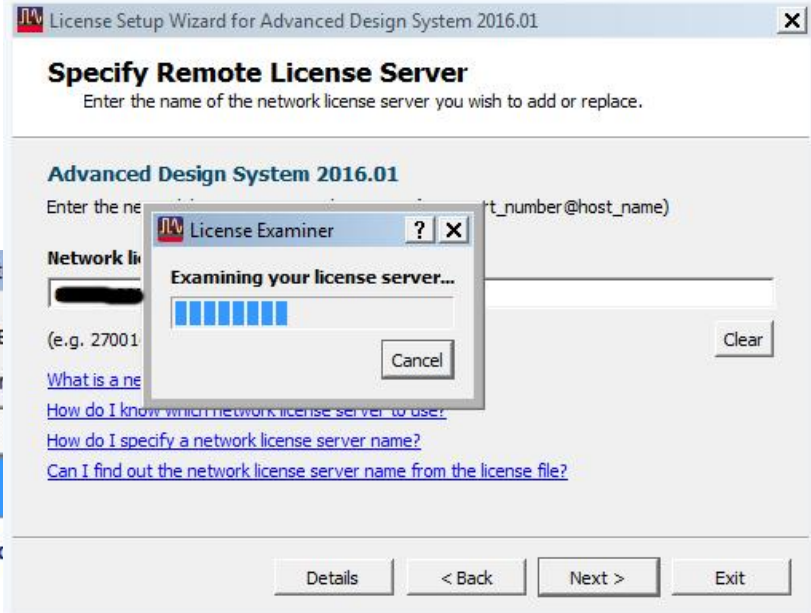


# Matching

- Source matched to load ?

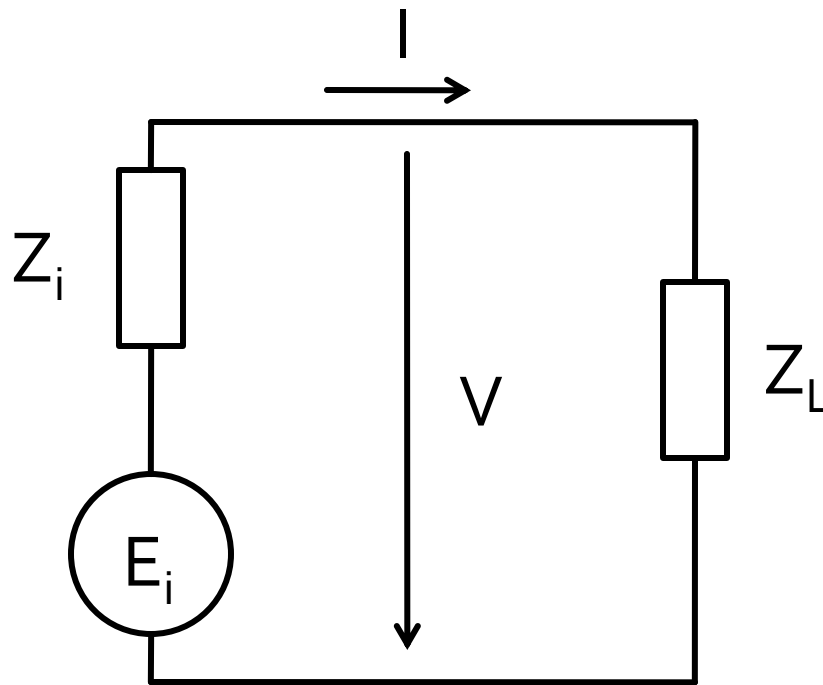

- impedance values ?
- existence of reflections ?


# Matching, example

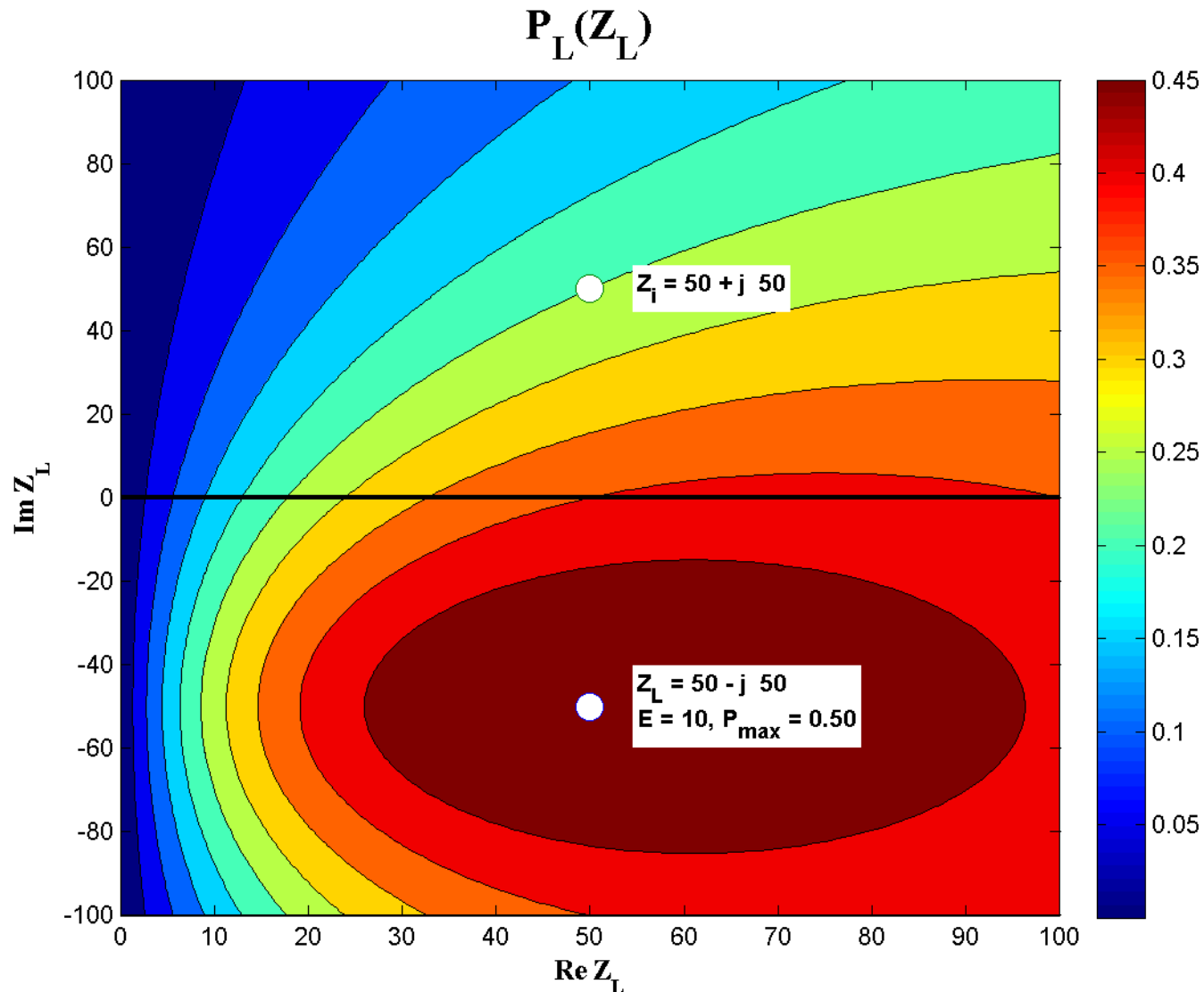

$$Z_L = Z_i^*$$

$$\Gamma_L = \Gamma_i^*$$

# Reflection and power / Model

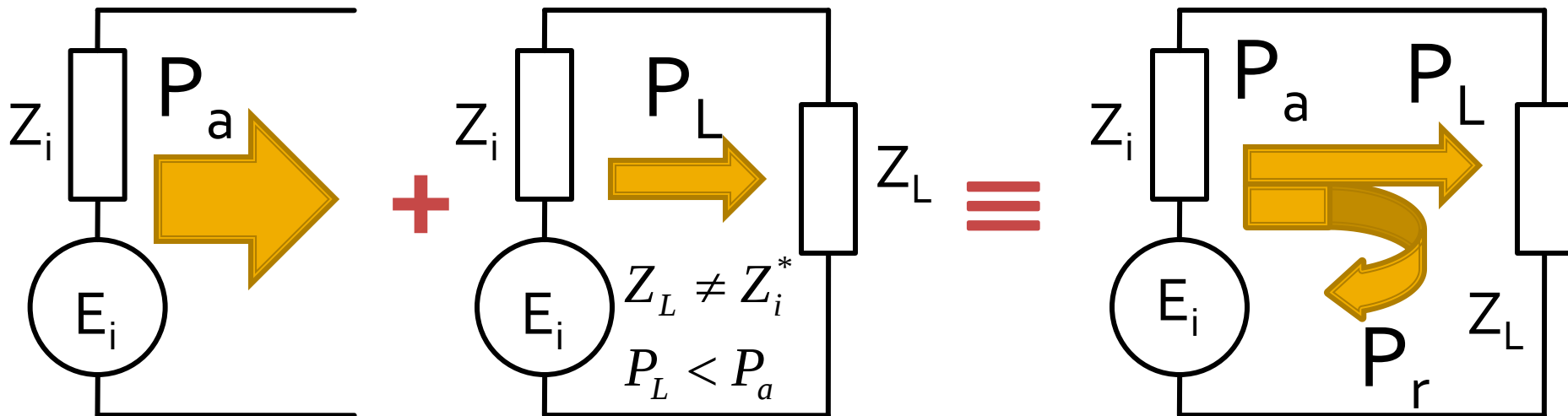


- The source has the ability to send to the load a certain maximum power (available power)  $P_a$
- For a particular load the power sent to the load is less than the maximum (mismatch)  $P_L < P_a$
- The phenomenon is **"as if"** (model) part of the input power is reflected  $P_r = P_a - P_L$
- The power is a **scalar** !

# TEM transmission lines
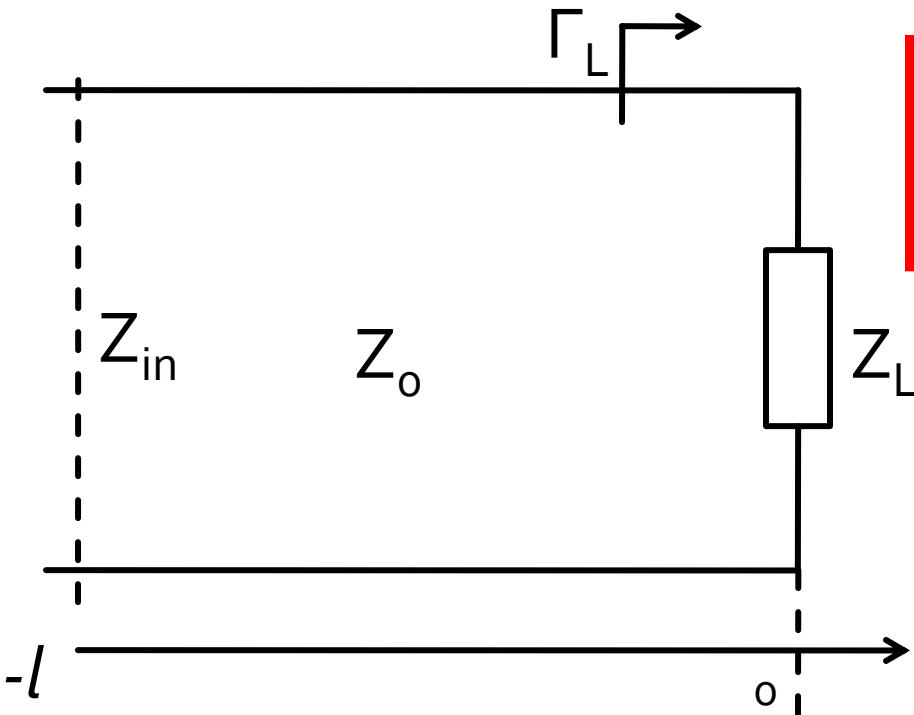
# The lossless line


- input impedance of a length  $l$  of transmission line with characteristic impedance  $Z_0$ , loaded with an arbitrary impedance  $Z_L$



$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

# Microwave Network Analysis

# ABCD (transmission) matrix

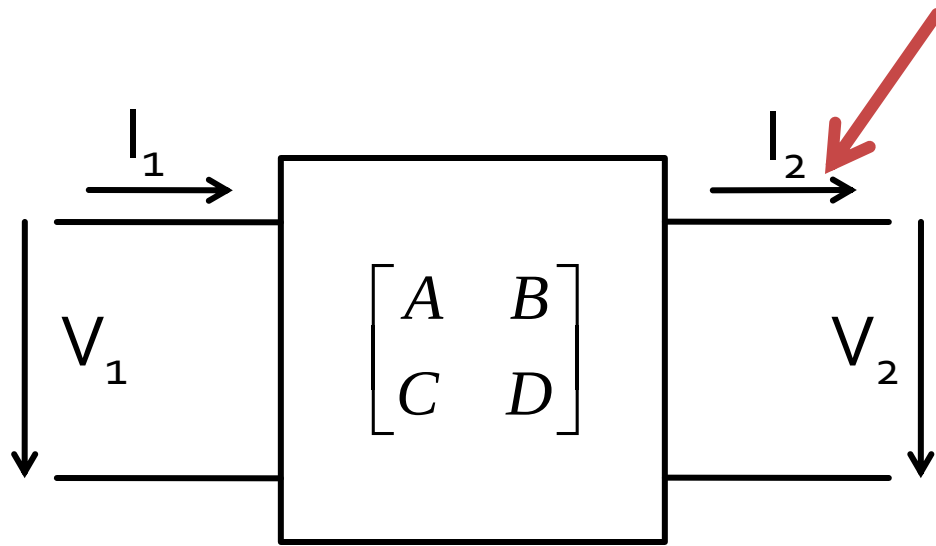

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \cdot \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$V_1 = A \cdot V_2 + B \cdot I_2$$

$$I_1 = C \cdot V_2 + D \cdot I_2$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \frac{1}{A \cdot D - B \cdot C} \cdot \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$


$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0}$$
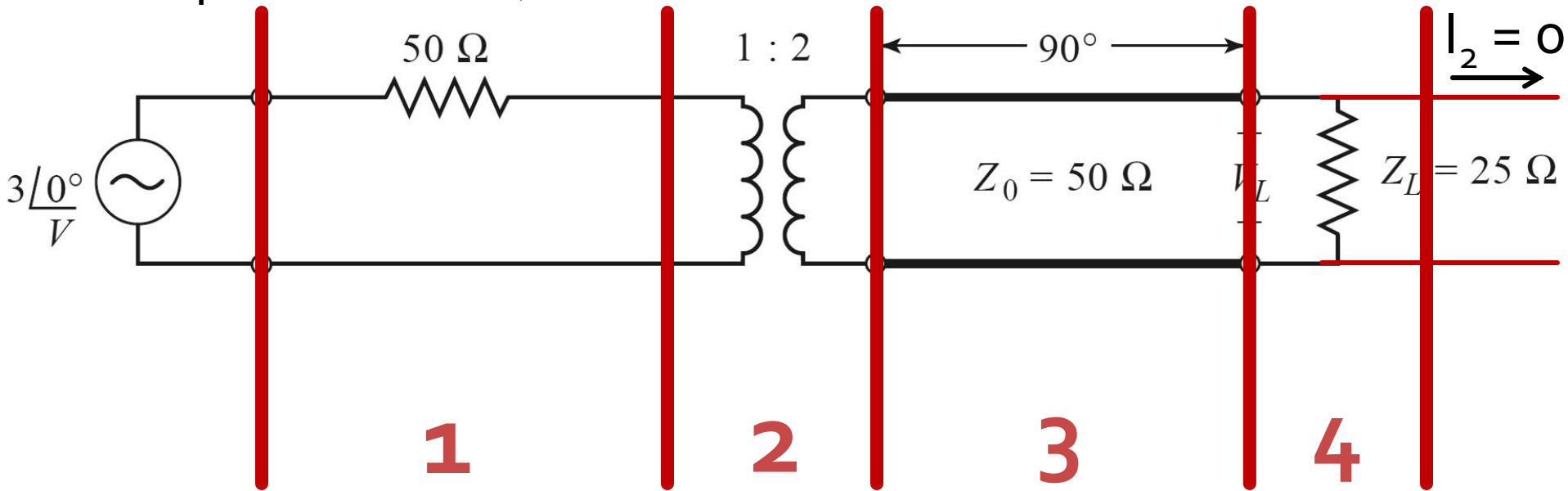
# Example for ABCD matrix


- We break the circuit in elementary sections
- Sources are left outside
- If necessary, input and output ports are created (and left open-circuited)



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = M_1 \cdot M_2 \cdot M_3 \cdot M_4 \quad V_1 = A \cdot V_2 + B \cdot I_2 \Big|_{I_2=0} \quad V = A \cdot V_L \rightarrow V_L = \frac{V}{A}$$

# Scattering matrix – S

- Scattering parameters

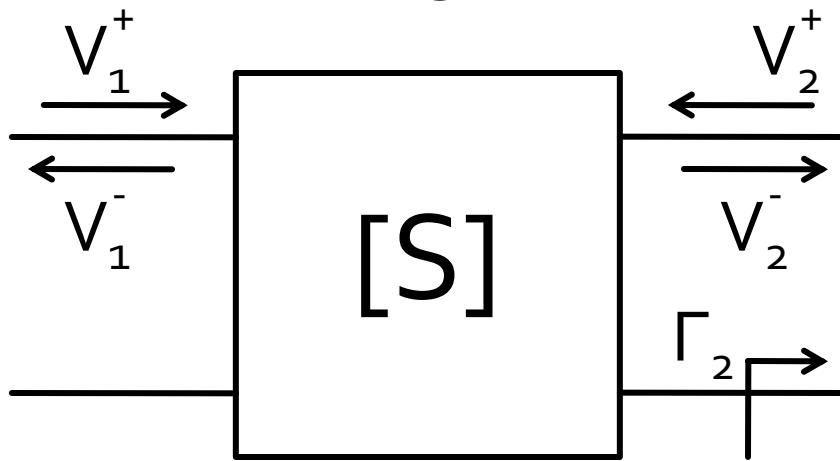


$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0}$$

- $V_2^+ = 0$  meaning: port 2 is terminated in matched load to avoid reflections towards the port

$$\Gamma_2 = 0 \rightarrow V_2^+ = 0$$

# Scattering matrix – S

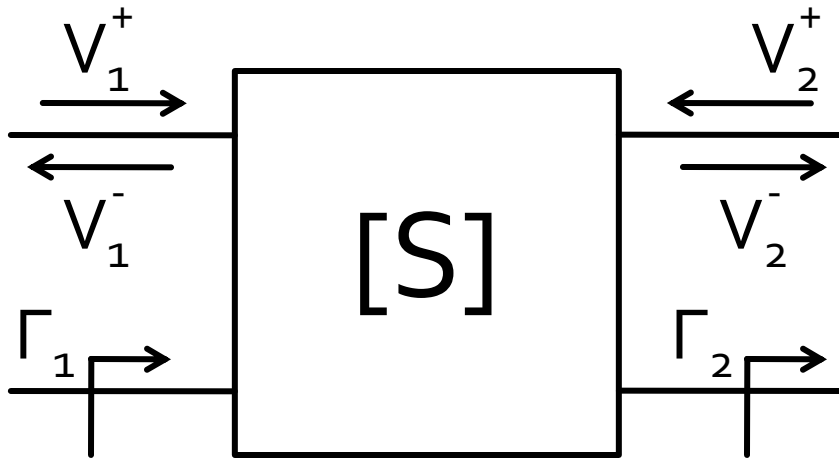

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$
$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+=0} = \Gamma_1|_{\Gamma_2=0}$$
$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+=0} = T_{21}|_{\Gamma_2=0}$$

- $S_{11}$  is the reflection coefficient seen looking into port **1** when port **2** is terminated in matched load
- $S_{21}$  is the transmission coefficient from port **1** (**second index**) to port **2** (**first index**) when port **2** is terminated in matched load

# Generalized Scattering Parameters

- We define the power wave amplitudes  $a$  and  $b$

$$a = \frac{V + Z_R \cdot I}{2 \cdot \sqrt{R_R}} \quad \text{the incident power wave} \quad Z_R = R_R + j \cdot X_R$$

$$b = \frac{V - Z_R^* \cdot I}{2 \cdot \sqrt{R_R}} \quad \text{the reflected power wave}$$


Any complex impedance,  
named reference impedance

- Total voltage and current in terms of the power wave amplitudes

$$V = \frac{Z_R^* \cdot a + Z_R \cdot b}{\sqrt{R_R}}$$

$$I = \frac{a - b}{\sqrt{R_R}}$$

# Scattering matrix – S

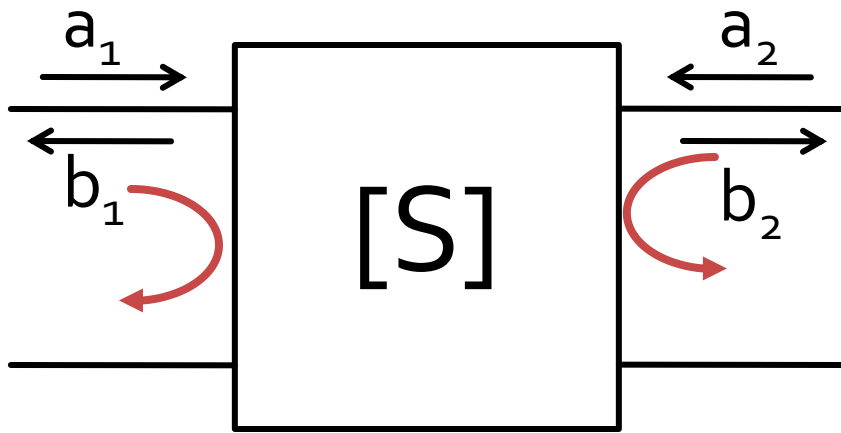


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

- $S_{11}$  and  $S_{22}$  are reflection coefficients at ports 1 and 2 when the other port is matched

# Scattering matrix – S

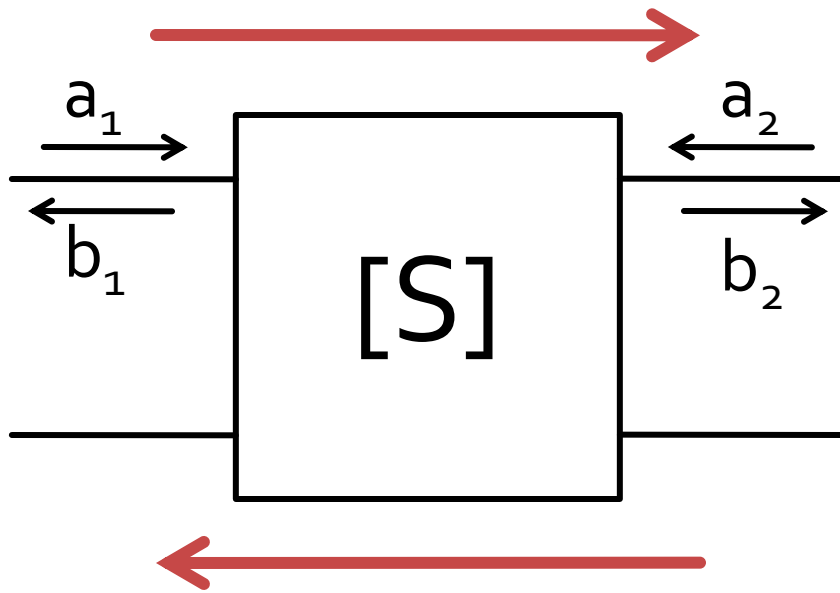


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$$

- $S_{21}$  and  $S_{12}$  are signal amplitude gain when the other port is matched

# Scattering matrix – S

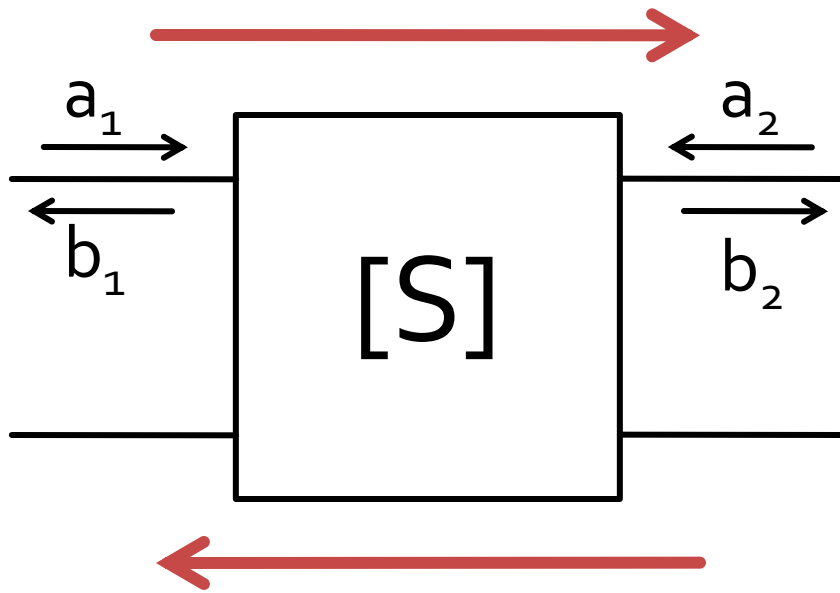

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- $a, b$ 
  - information about signal power **AND** signal phase
- $S_{ij}$ 
  - network effect (gain) over signal power **including** phase information

# Measuring S parameters - VNA

- Vector Network Analyzer

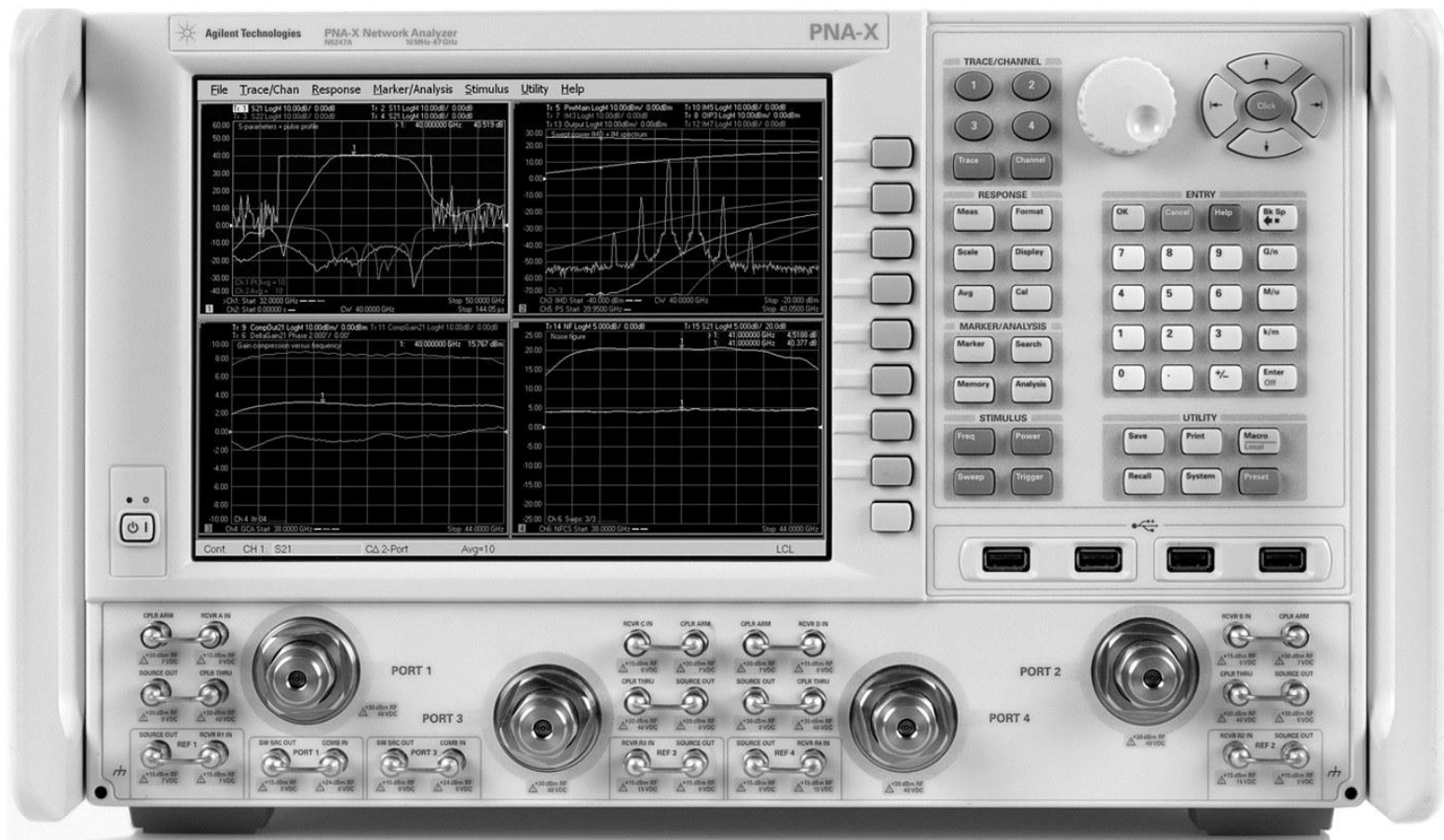


Figure 4.7  
Courtesy of Agilent Technologies

# Power dividers and directional couplers

# Power dividers and couplers

- Desired functionality:
  - division
  - combining
- of signal power

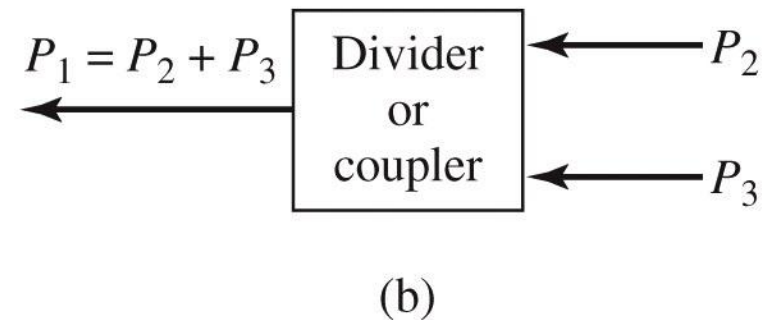
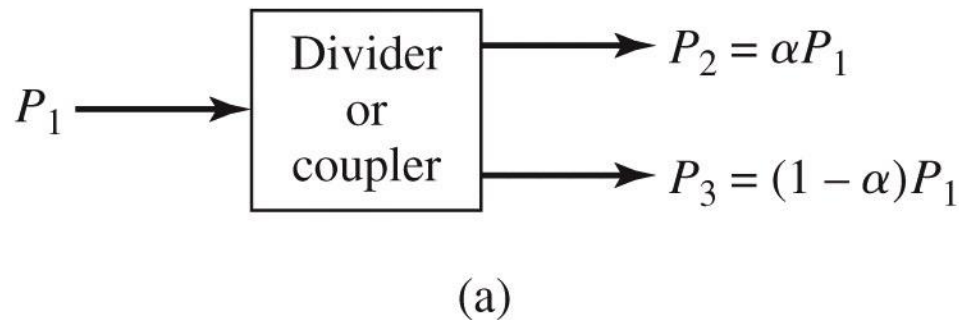


Figure 7.1  
© John Wiley & Sons, Inc. All rights reserved.

# Three-Port Networks

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

- 6 equations / 3 unknowns
  - no solution is possible
- A three-port network **cannot** be simultaneously:
  - reciprocal
  - lossless
  - matched at all ports
- If any one of these three conditions is relaxed, then a physically realizable device is possible

# Four-Port Networks


- A four-port network simultaneously:
  - matched at all ports
  - reciprocal
  - lossless
- is **always directional**
  - the signal power injected into one port is transmitted **only towards two** of the other three ports

$$[S] = \begin{bmatrix} 0 & \alpha & \beta \cdot e^{j\theta} & 0 \\ \alpha & 0 & 0 & \beta \cdot e^{j\phi} \\ \beta \cdot e^{j\theta} & 0 & 0 & \alpha \\ 0 & \beta \cdot e^{j\phi} & \alpha & 0 \end{bmatrix}$$

Directional Couplers

# Laboratory no. 2

# Directional Coupler

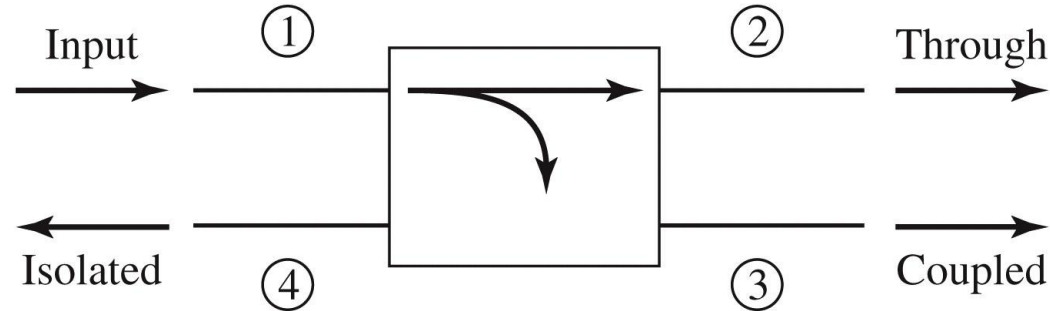

$$|S_{12}|^2 = \alpha^2 = 1 - \beta^2$$

$$|S_{13}|^2 = \beta^2$$

Cuplaj

$$C = 10 \log \frac{P_1}{P_3} = -20 \cdot \log(\beta) [\text{dB}]$$

Directivitate

$$D = 10 \log \frac{P_3}{P_4} = 20 \cdot \log \left( \frac{\beta}{|S_{14}|} \right) [\text{dB}]$$

Izolare

$$I = 10 \log \frac{P_1}{P_4} = -20 \cdot \log |S_{14}| [\text{dB}]$$

$$I = D + C, \text{ dB}$$

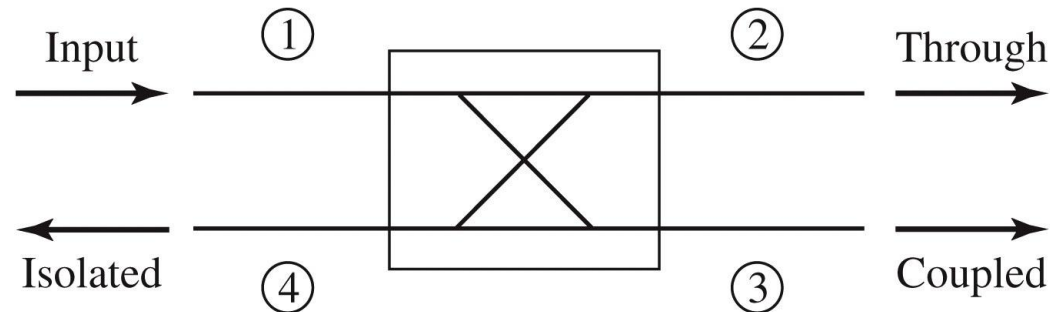


Figure 7.4  
© John Wiley & Sons, Inc. All rights reserved.

# Quadrature coupler

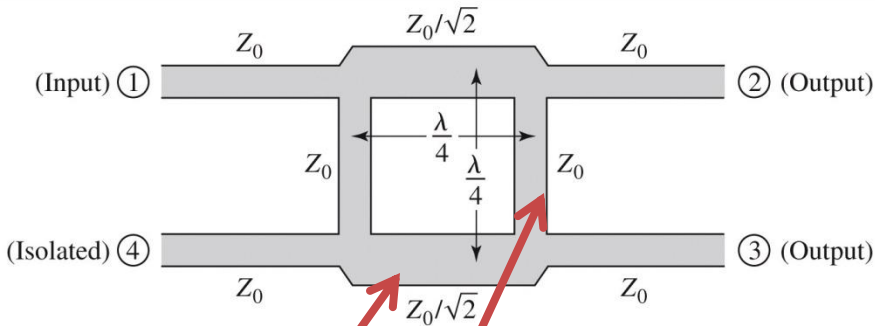


Figure 7.21  
© John Wiley & Sons, Inc. All rights reserved.

$$y_2^2 = 1 + y_1^2$$

$$|\beta| = \frac{\sqrt{y_2^2 - 1}}{y_2}$$

$$C[\text{dB}] = -20 \cdot \log_{10} \frac{\sqrt{y_2^2 - 1}}{y_2}$$



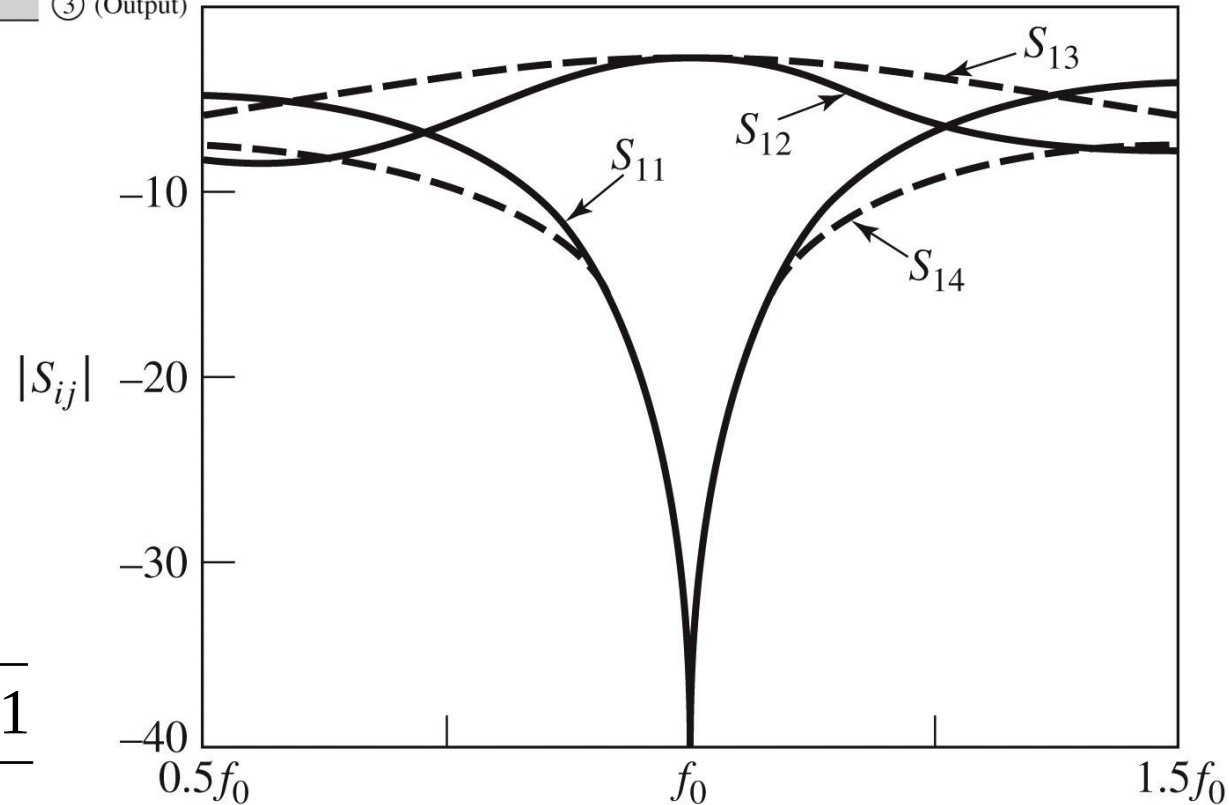


Figure 7.25  
© John Wiley & Sons, Inc. All rights reserved.

# Quadrature coupler

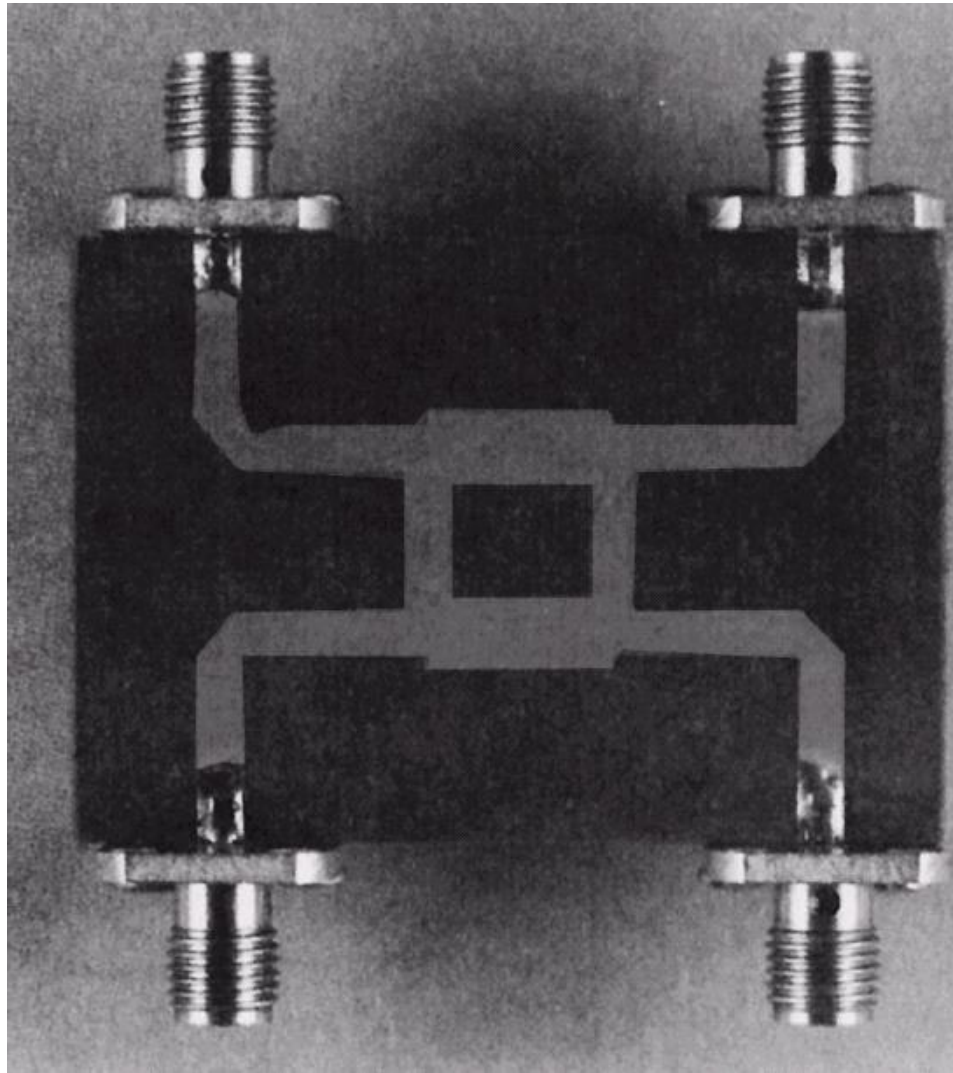

# Ring coupler

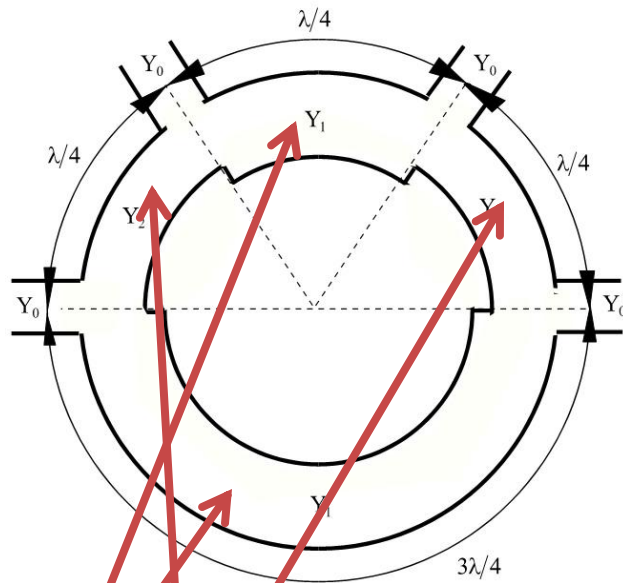

$$y_1^2 + y_2^2 = 1$$

$$|\beta| = y_1$$

$$C \text{ [dB]} = -20 \cdot \log_{10}(y_1)$$

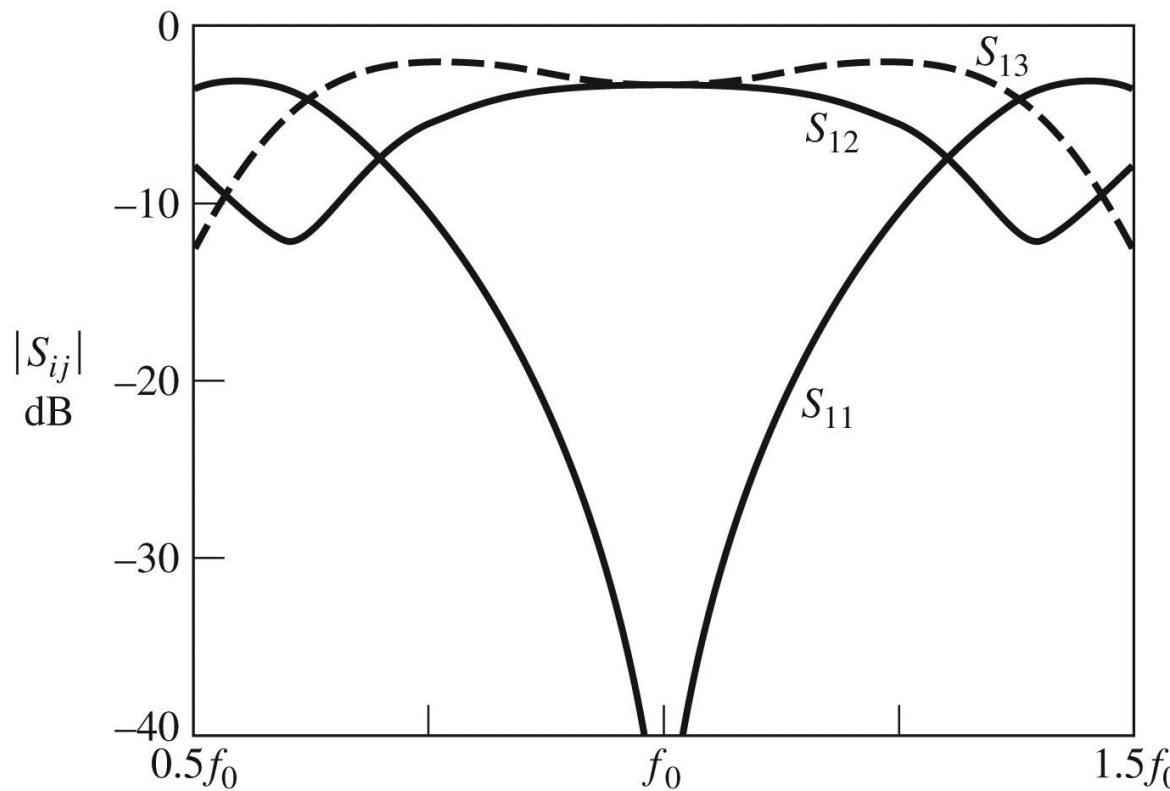


Figure 7.46  
© John Wiley & Sons, Inc. All rights reserved.

# Ring coupler


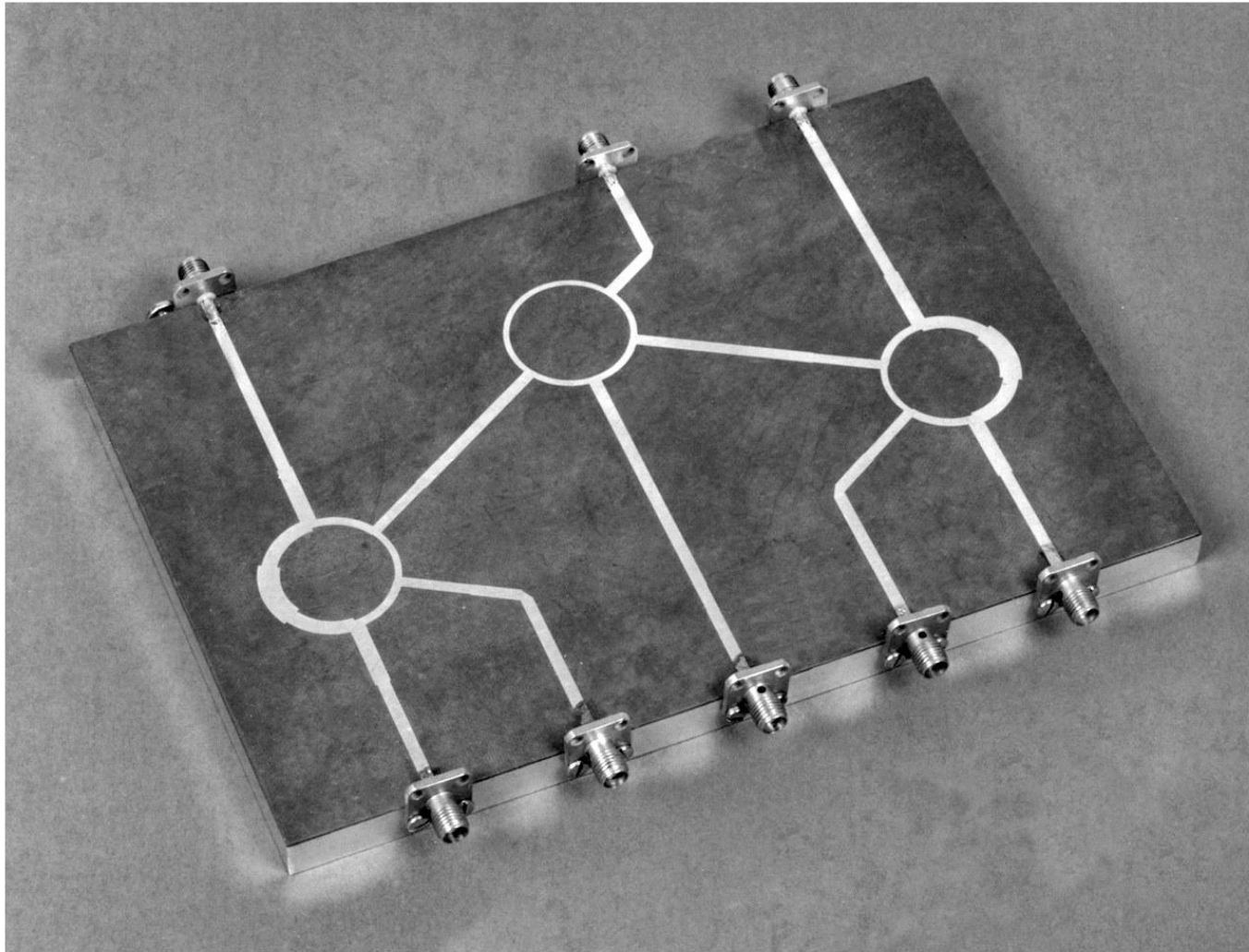


Figure 7.43  
Courtesy of M. D. Abouzahra, MIT Lincoln Laboratory, Lexington, Mass.

# Coupled lines coupler

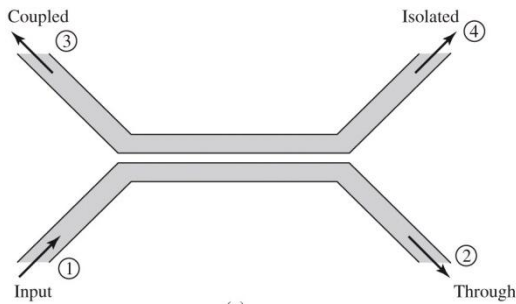

$$Z_{ce} Z_{co} = Z_0^2$$

$$|\beta| = \frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}}$$

$$C \text{ [dB]} = -20 \cdot \log_{10} \left( \frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}} \right)$$


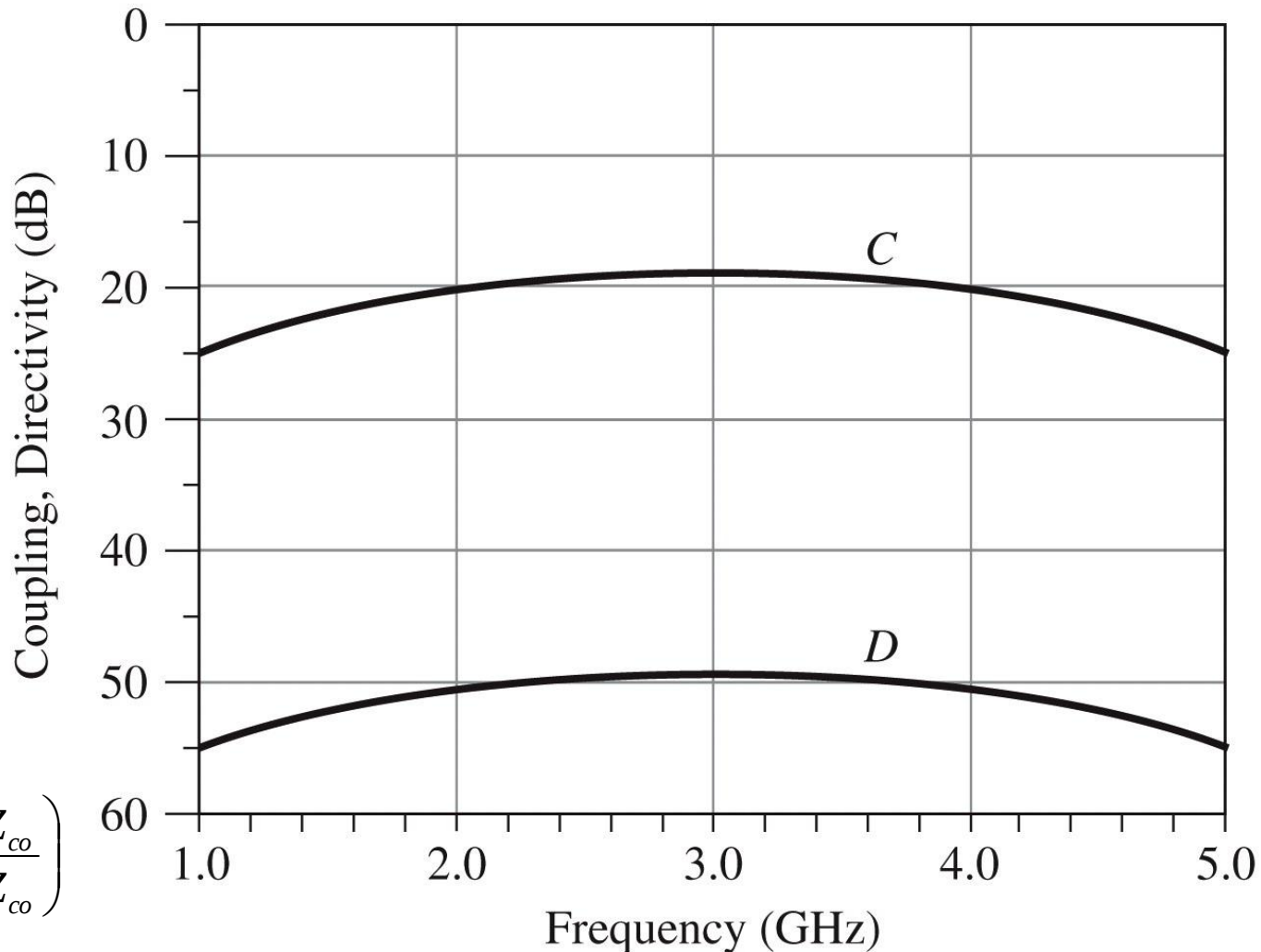


Figure 7.34  
© John Wiley & Sons, Inc. All rights reserved.


# Coupled lines coupler

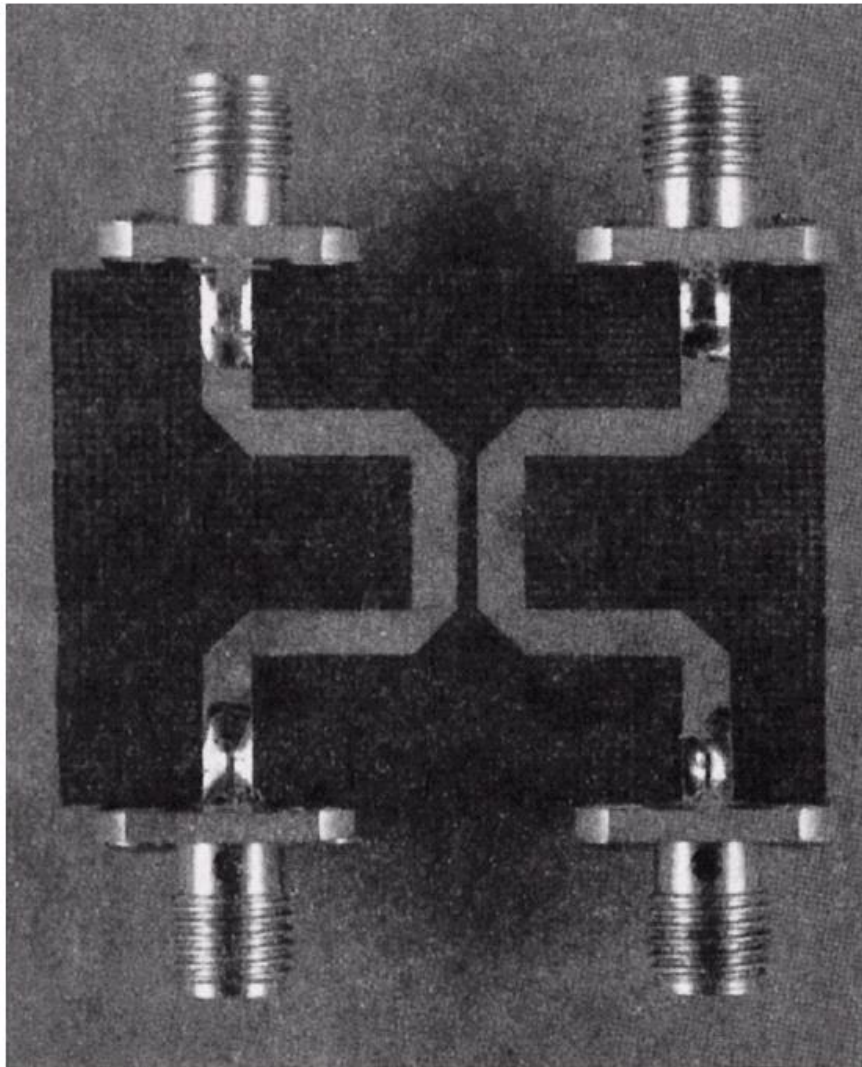

# Microwave Network Analysis
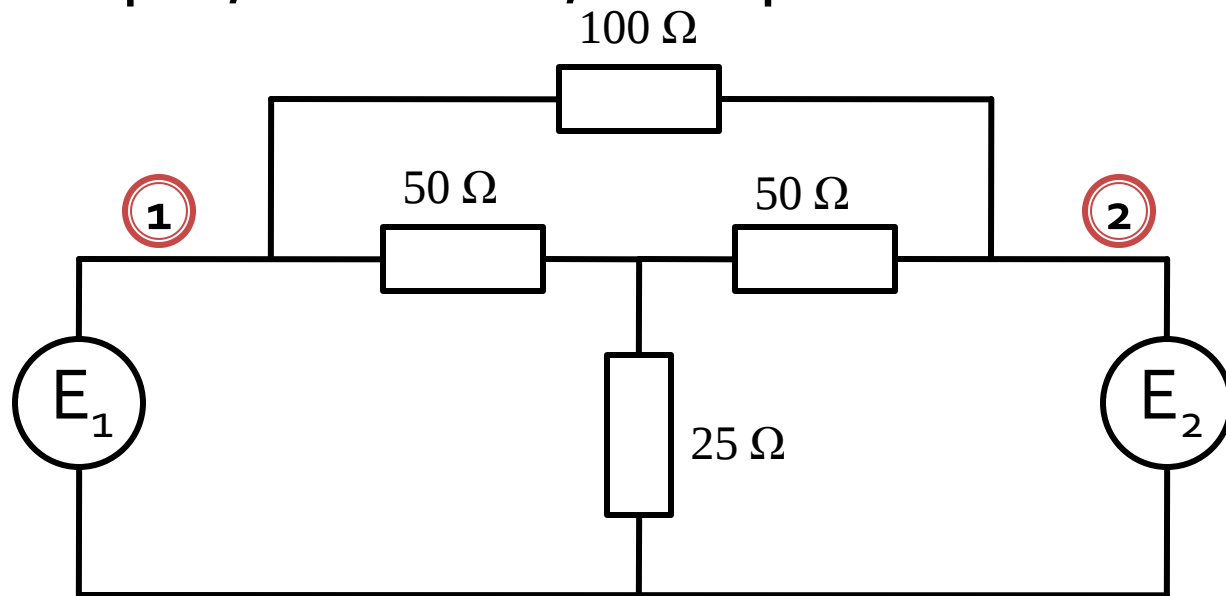
# Even/Odd Mode Analysis


- useful method, necessary even for multiple ports
- example, resistors, two port circuit



# Even/Odd Mode Analysis


- assume we want to compute  $Y_{11}$
- $E_2 = 0$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

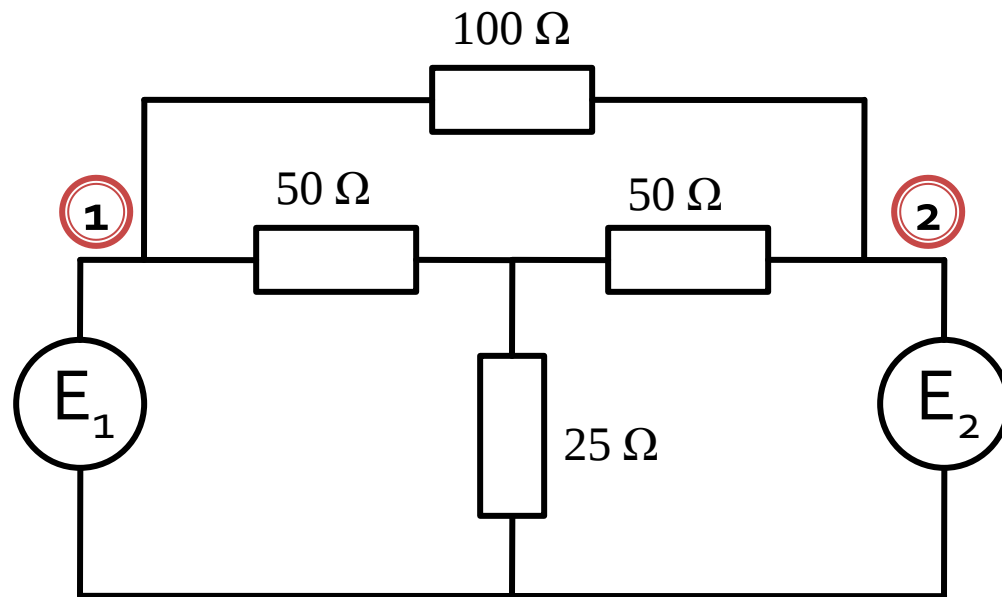

$$R_{ech} = 100\Omega || (50\Omega + 25\Omega || 50\Omega) =$$


$$= 100\Omega || (50\Omega + 16.67\Omega) = 100\Omega || 66.67\Omega = 40\Omega$$

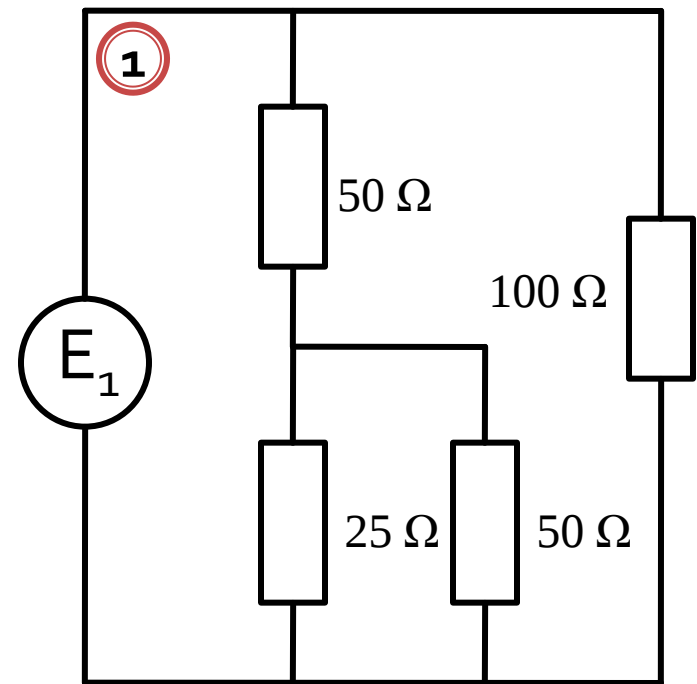

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = 0.025S$$


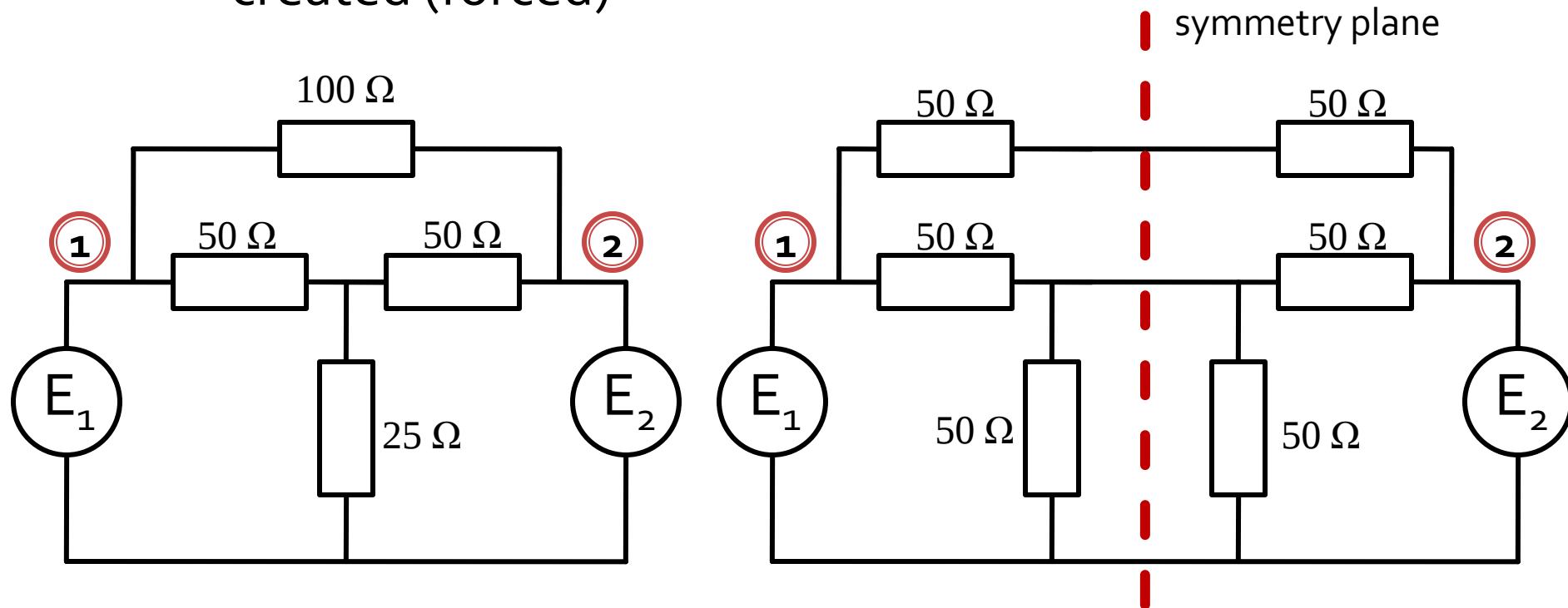
# Even/Odd Mode Analysis

- Even/Odd mode analysis benefit from the existence of symmetry planes in the circuit
  - existing or
  - created (forced)



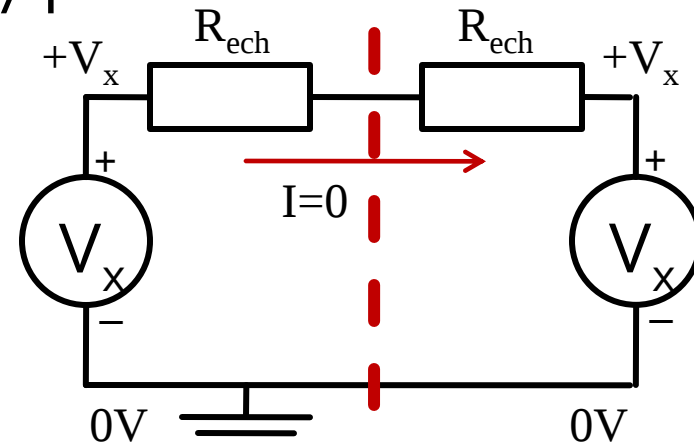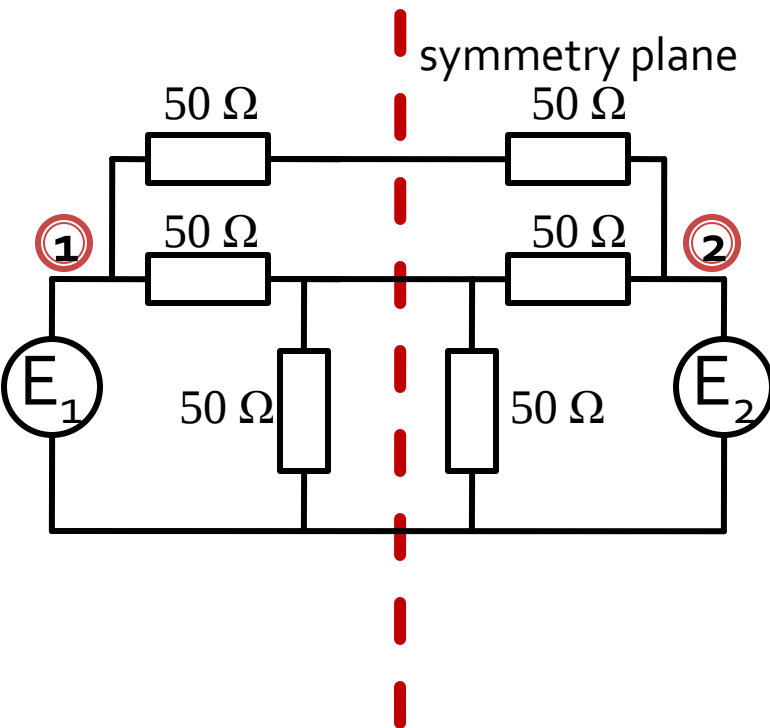
# Even/Odd Mode Analysis

- when exciting the ports with symmetric/anti-symmetric sources the symmetry planes are transformed into:
  - open circuit
  - virtual ground




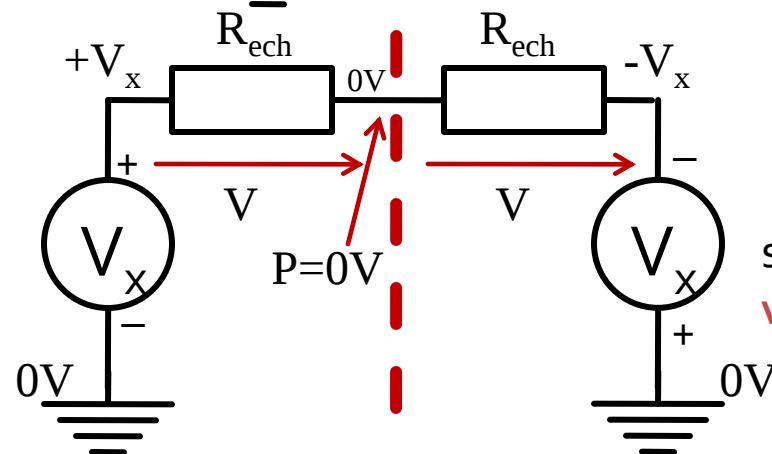
$I = 0, \forall V_x$   
 symmetry plane  
 open circuit



$P = 0, \forall V_x$   
 symmetry plane  
 virtual ground
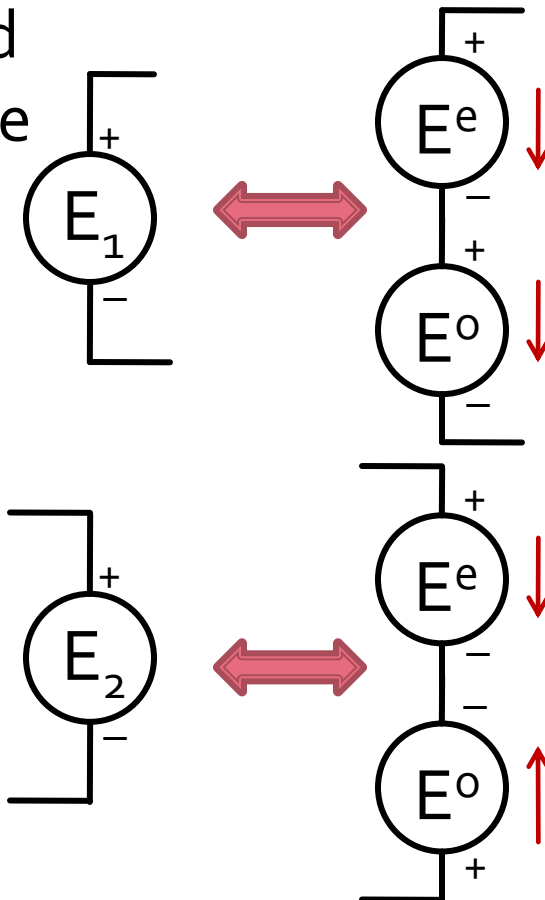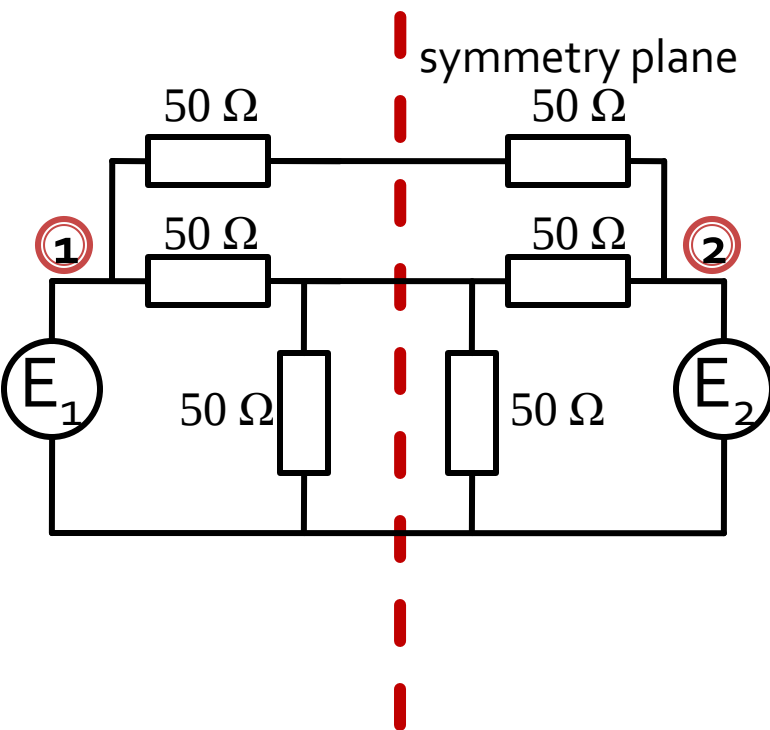
# Even/Odd Mode Analysis

- the combination of any two sources is equivalent for linear circuits with the superposition of:
  - a symmetric source and
  - a anti-symmetric source



$$E_1 = E^e + E^o$$

$$E_2 = E^e - E^o$$

$$E^e = \frac{E_1 + E_2}{2}$$

$$E^o = \frac{E_1 - E_2}{2}$$

# Even/Odd Mode Analysis

- In linear circuits the **superposition principle** is always true
  - the response caused by two or more stimuli is the sum of the responses that would have been caused by each stimulus individually

$$\begin{aligned}\text{Response (Source1 + Source2)} &= \\ &= \text{Response (Source1)} + \text{Response (Source2)}\end{aligned}$$


$$\text{Response (ODD + EVEN)} = \text{Response (ODD)} + \text{Response (EVEN)}$$



We can benefit from existing symmetries !!

# Even/Odd Mode Analysis

■ example

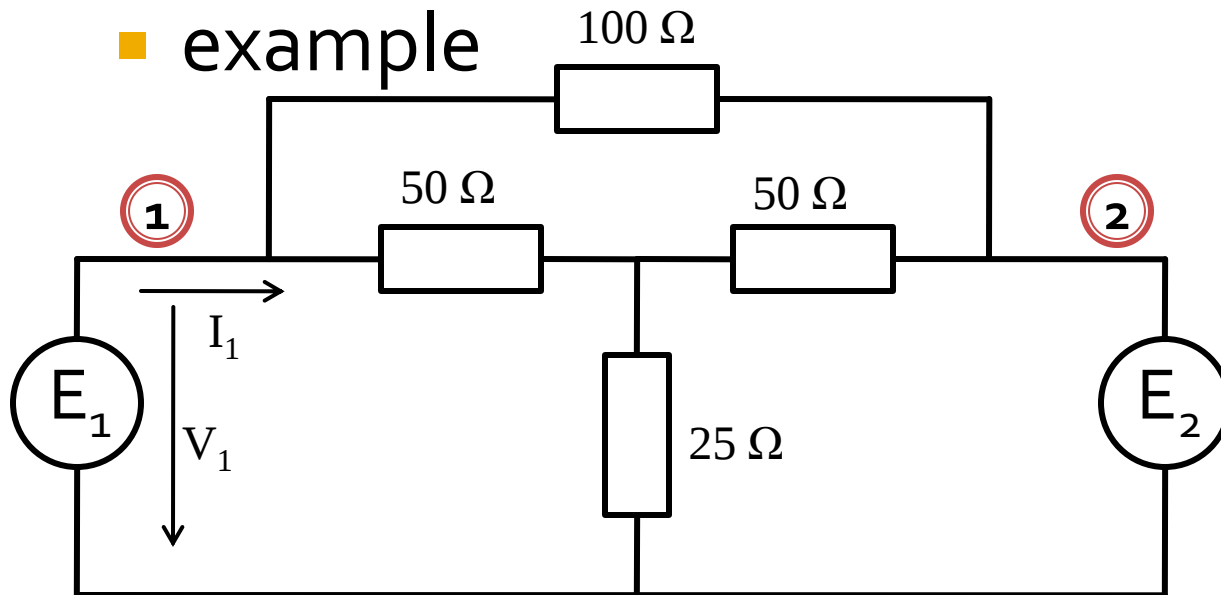


$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$V_2 \equiv E_2 = 0 \Rightarrow$$


$$E^e = \frac{E_1}{2}$$

$$E^o = \frac{E_1}{2}$$

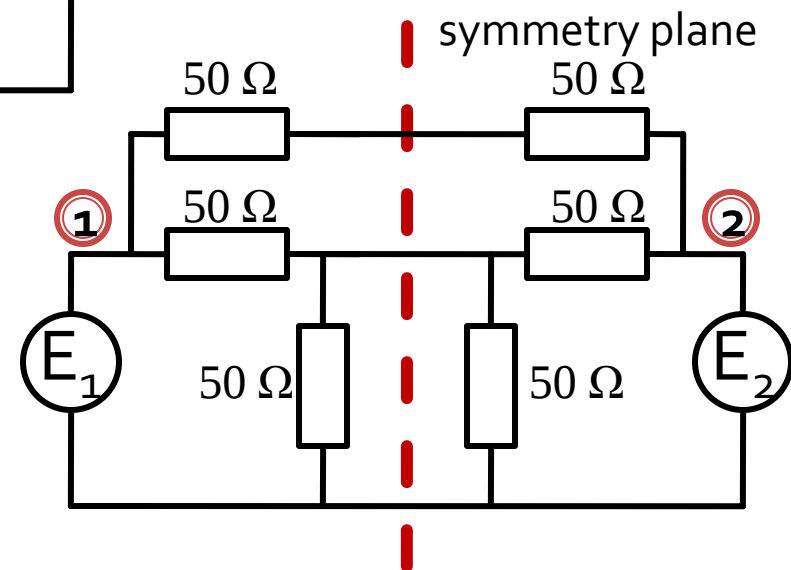


# Even/Odd Mode Analysis

- Even/Odd mode analysis

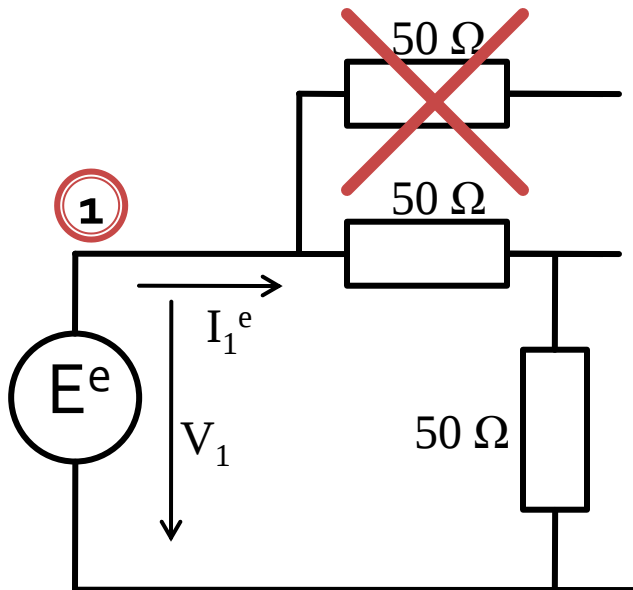

$$R_{ech}^e = 50\Omega + 50\Omega = 100\Omega$$
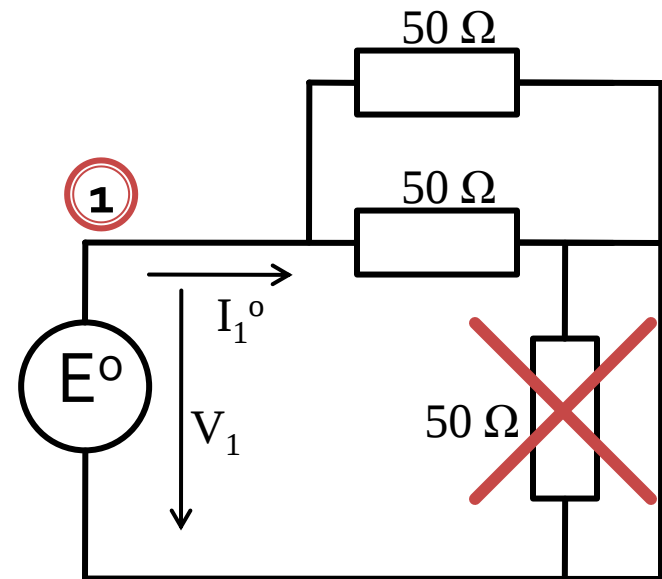
$$I_1^e = \frac{E^e}{R_{ech}^e} = \frac{E_1/2}{100\Omega} = \frac{E_1}{200\Omega}$$




$$R_{ech}^o = 50\Omega || 50\Omega = 25\Omega$$

$$I_1^o = \frac{E^o}{R_{ech}^o} = \frac{E_1/2}{25\Omega} = \frac{E_1}{50\Omega}$$

# Even/Odd Mode Analysis

- superposition principle

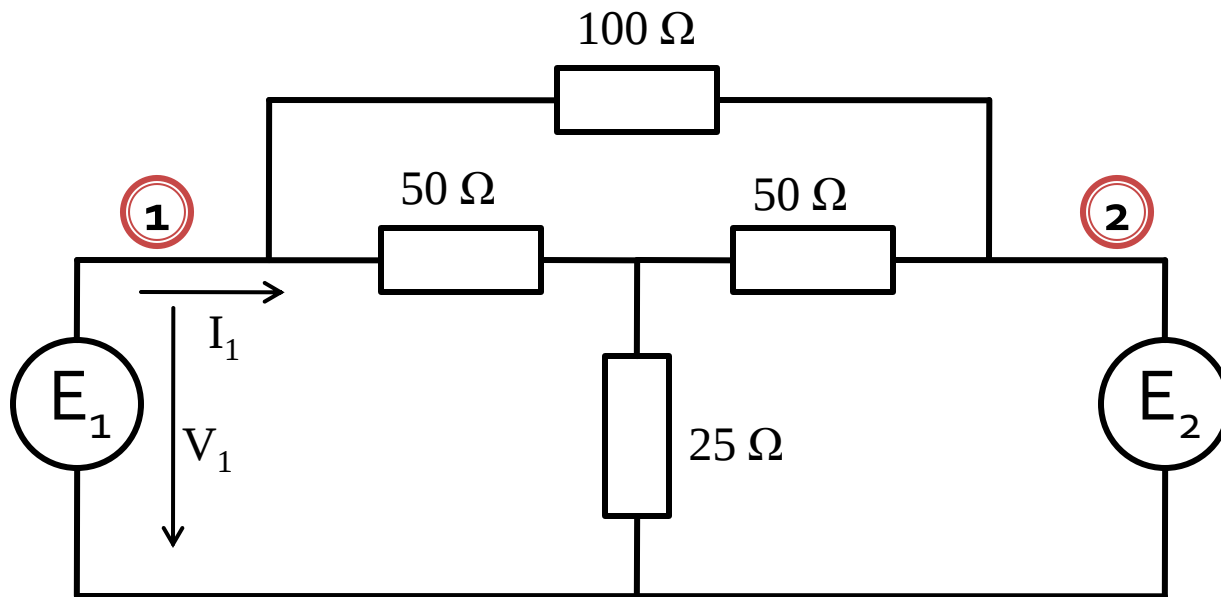

$$I_1 = I_1^e + I_1^o$$

$$V_1 = V_1^e + V_1^o$$

$$I_1 = I_1^e + I_1^o = \frac{E_1}{200\Omega} + \frac{E_1}{50\Omega} = \frac{E_1}{40\Omega}$$

$$V_1 = V_1^e + V_1^o = E_1$$

$$Y_{11} = \frac{I_1}{V_1} = \frac{1}{40\Omega} = 0.025S$$

# Even/Odd Mode Analysis

- In linear circuits we can use the superposition principle
- advantages
  - reduction of the circuit complexity
  - decrease in the number of ports (**main** advantage)

$$\text{Response}(\text{ODD} + \text{EVEN}) = \text{Response}(\text{ODD}) + \text{Response}(\text{EVEN})$$




We can benefit from existing symmetries !!


Impedance Matching

# The Smith Chart


# The Smith Chart

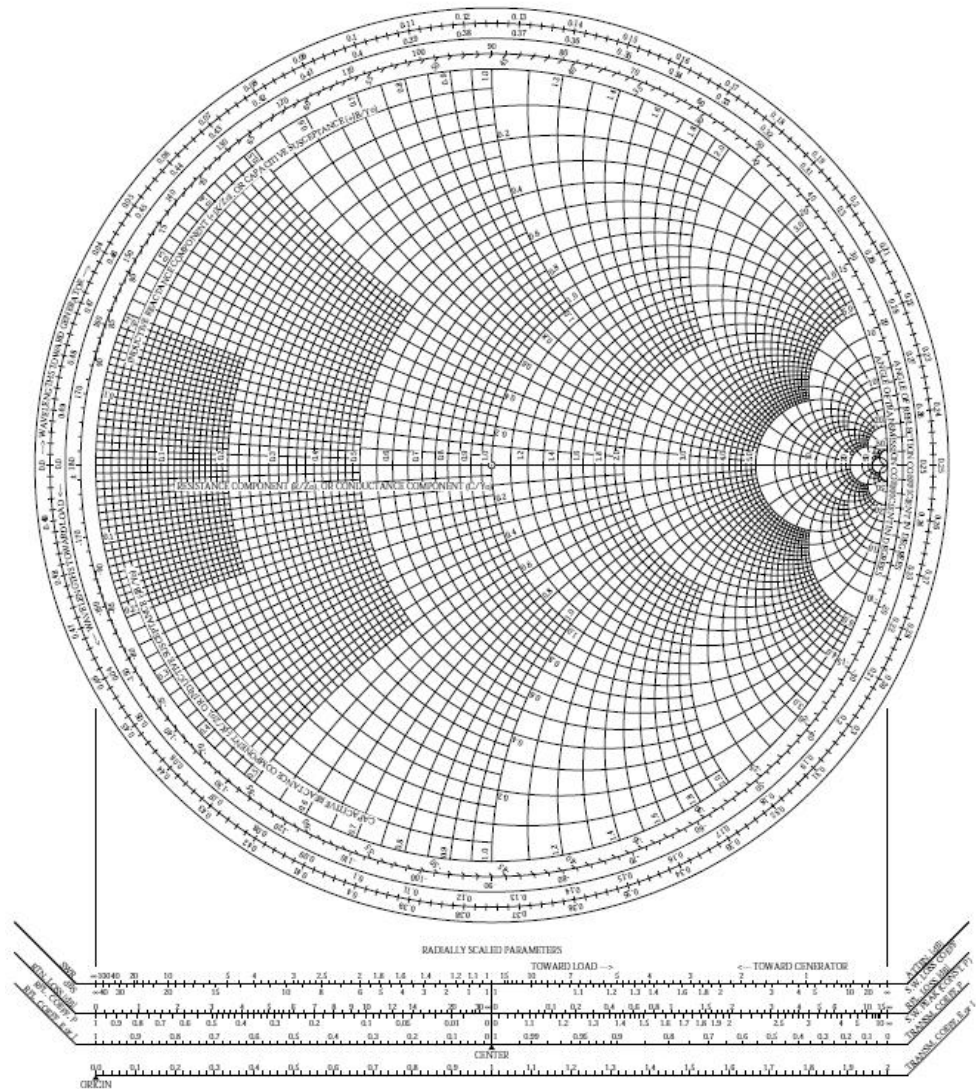



# The Smith Chart

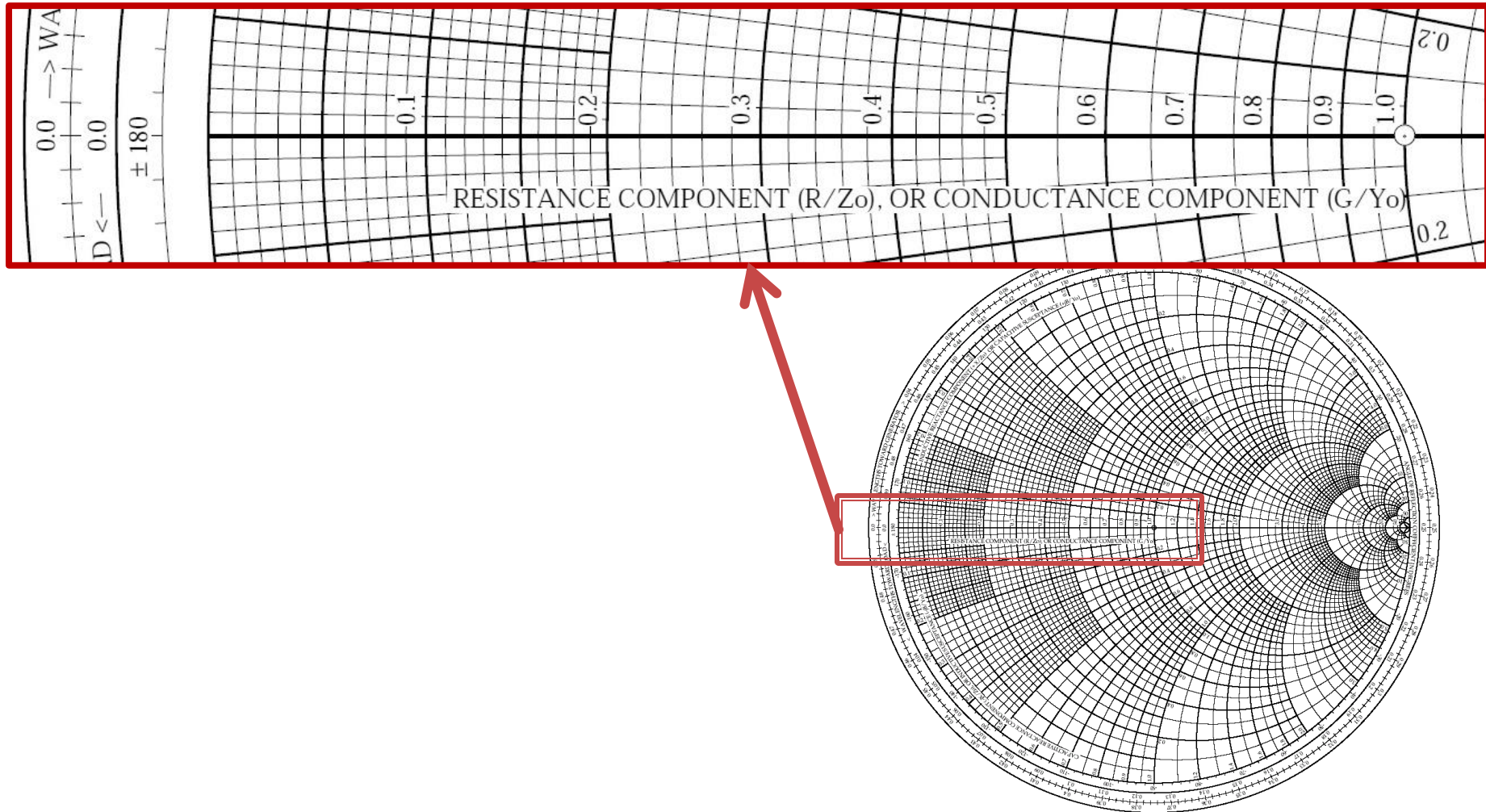


# The Smith Chart

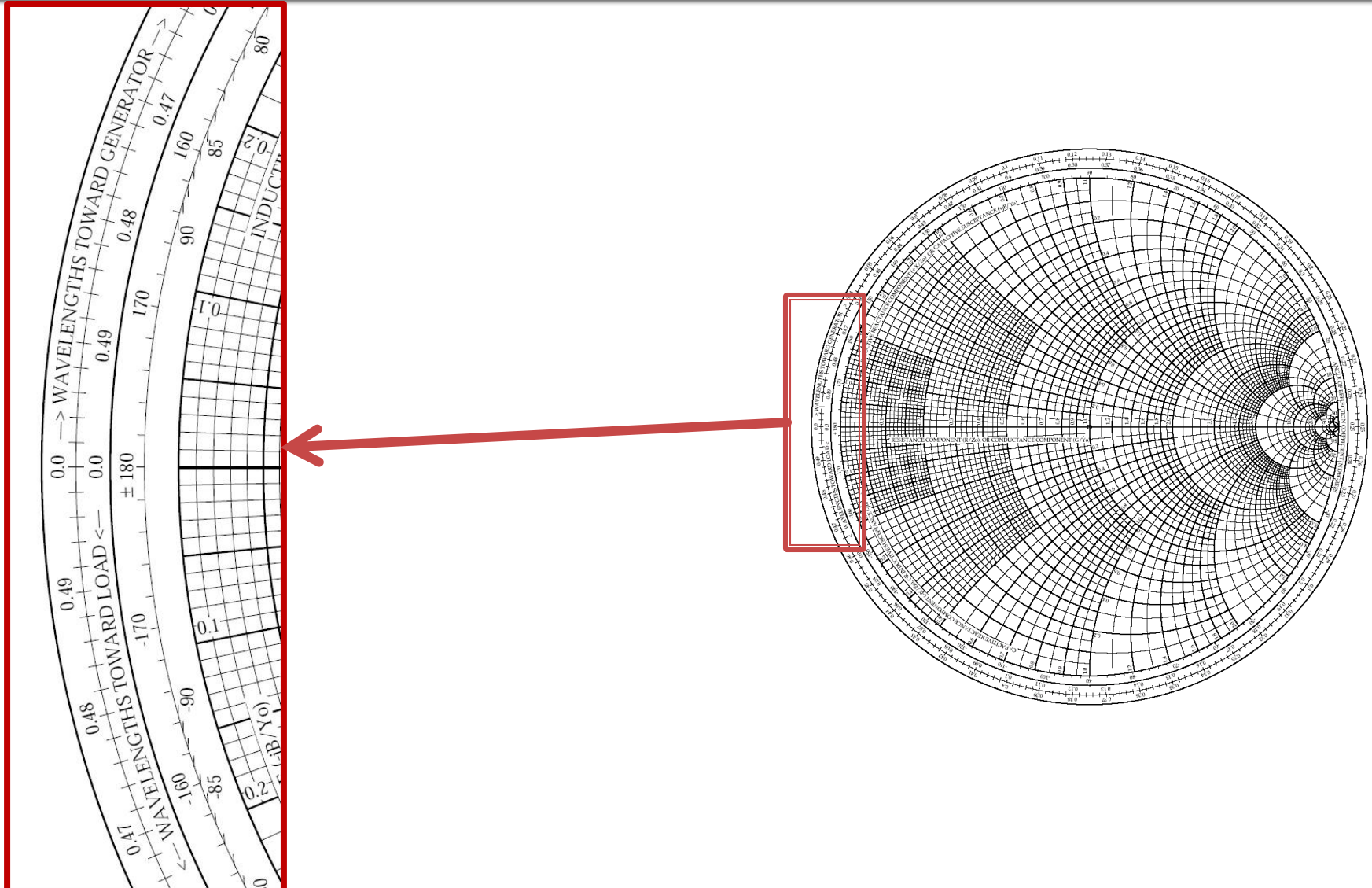


# The Smith Chart

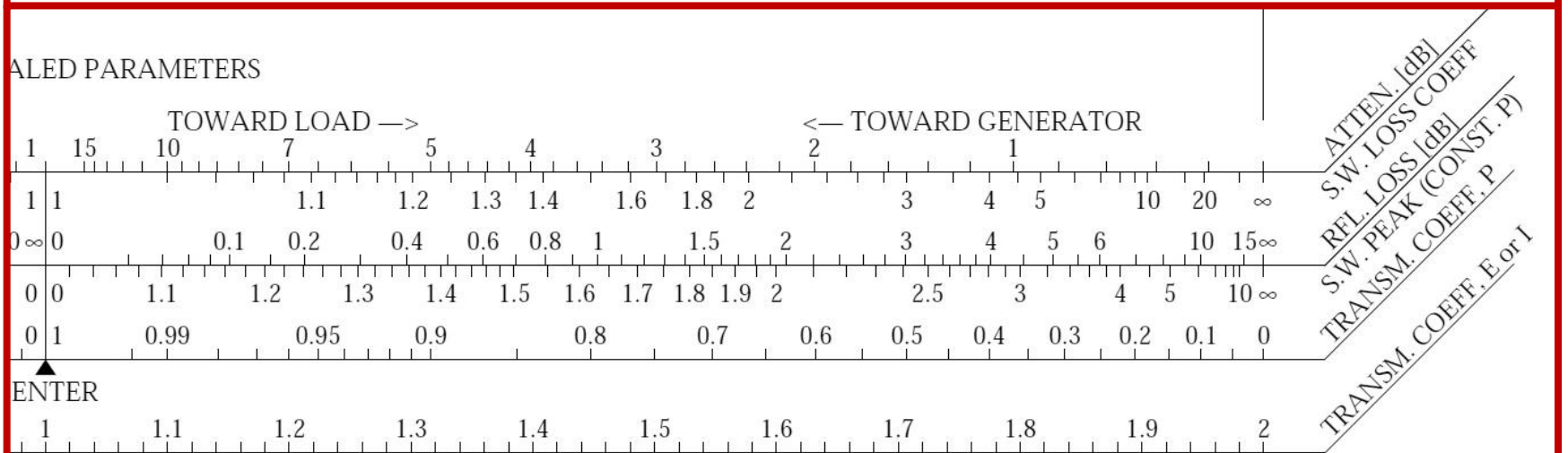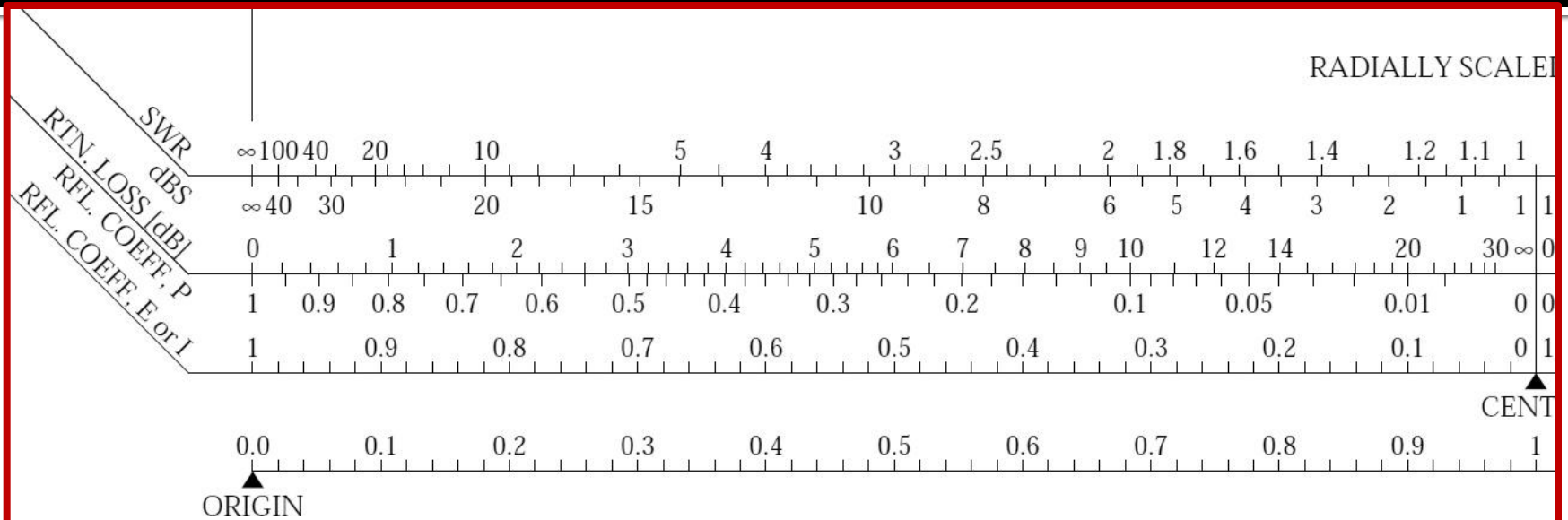


# The Smith Chart

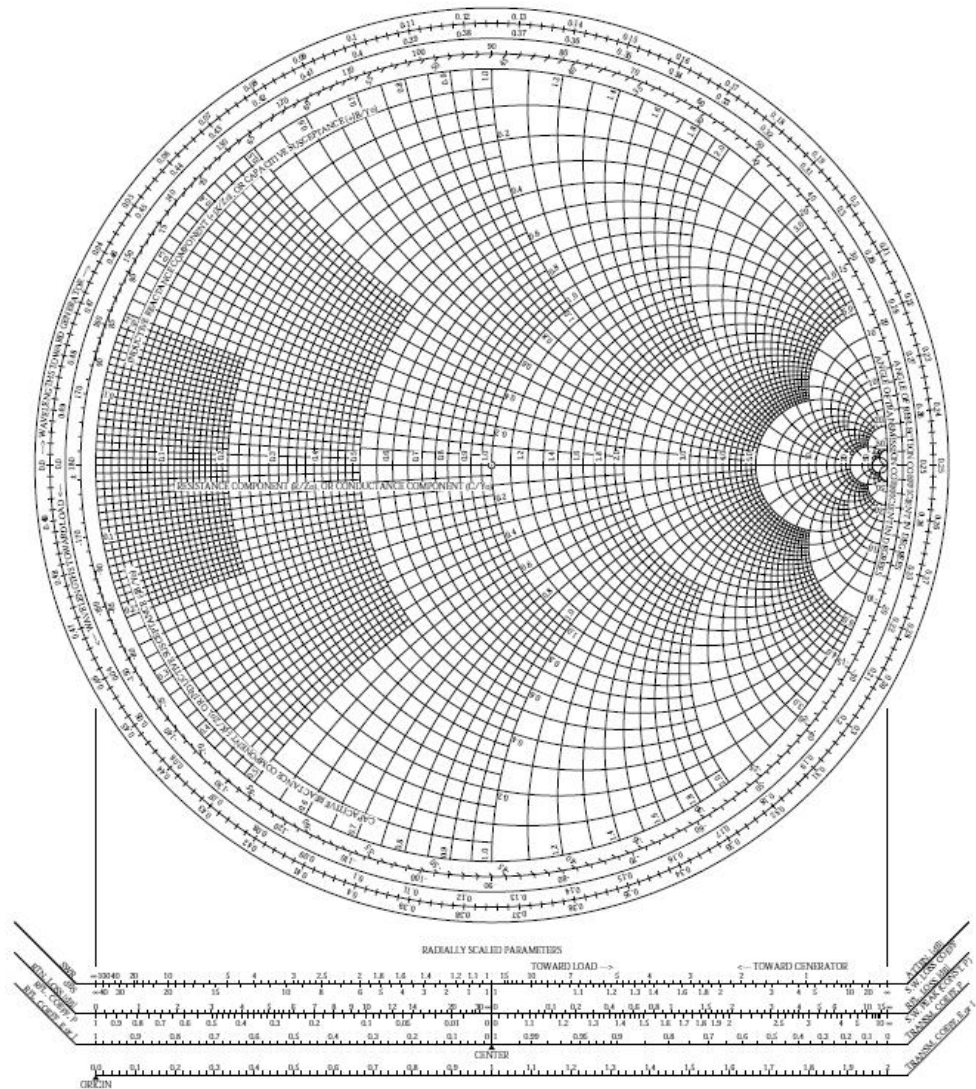


# The Smith Chart

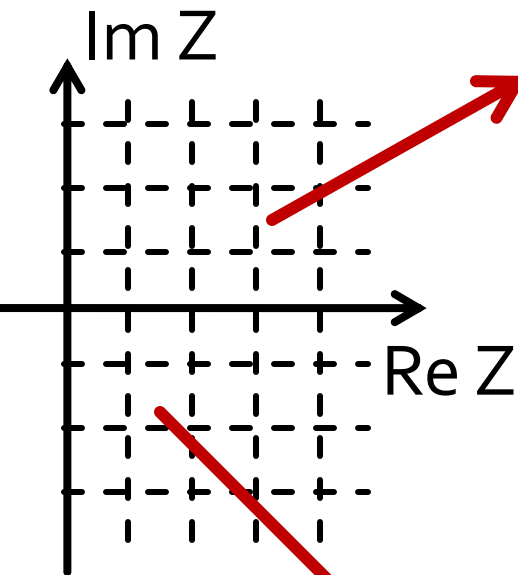
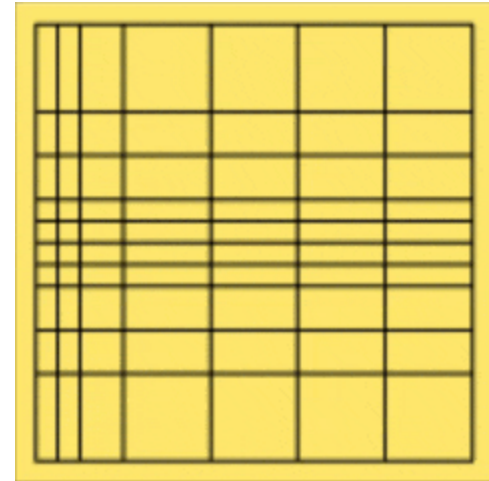
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$



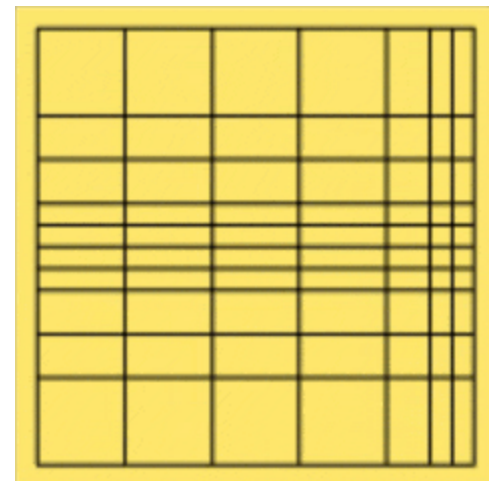
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Y_0 - Y_L}{Y_0 + Y_L} = \frac{1 - y_L}{1 + y_L}$$


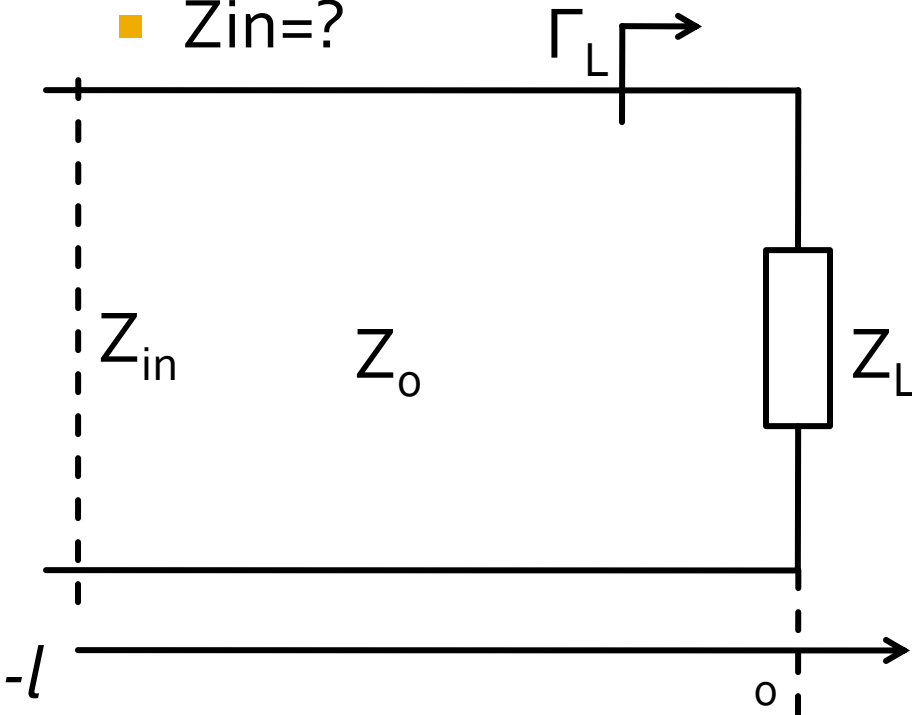
# Traditional usage

- transmission line
  - $100\Omega$  characteristic impedance
  - $0.3\lambda$  length
  - $Z_L = 40\Omega + j \cdot 70\Omega$  load
- $Z_{in} = ?$



$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

$$Z_{in} = 36.5340\Omega - j \cdot 61.1190\Omega$$

# Traditional usage


- transmission line
  - 100Ω impedance
  - 0.3λ length
  - $Z_L = 40\Omega + j \cdot 70\Omega$  load
- normalization with  $Z_0 = 100\Omega$

$$z_L = \frac{Z_L}{Z_0} = 0.4 + j \cdot 0.7$$


- movement with 0.3λ on a line with  $Z_0 = 100\Omega$  (circle)

- from  $z_L$  (0.105λ)
- to  $z_{in}$  (0.405λ)

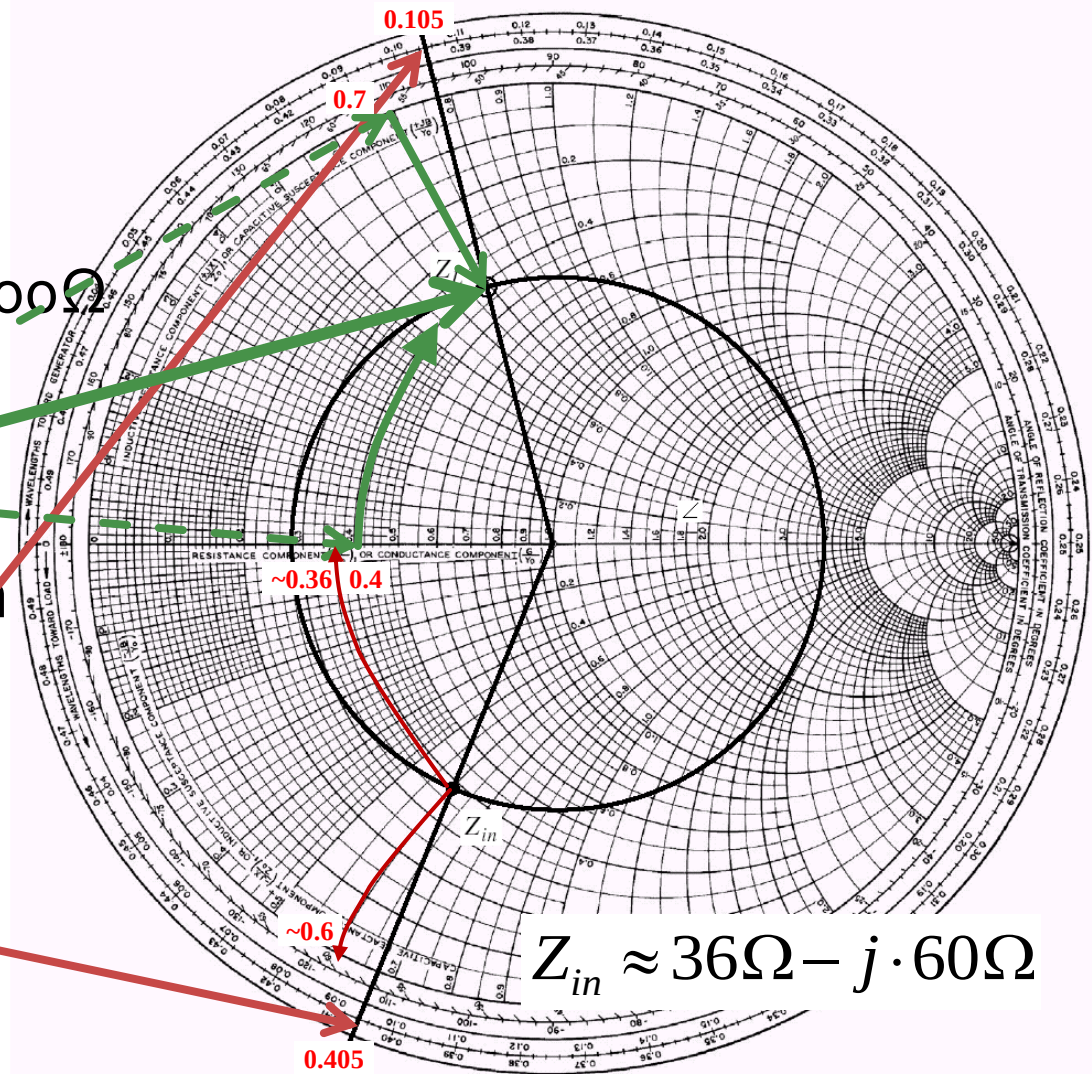
$$z_{in} \approx 0.36 - j \cdot 0.6 = \frac{Z_{in}}{Z_0}$$



# The Smith Chart



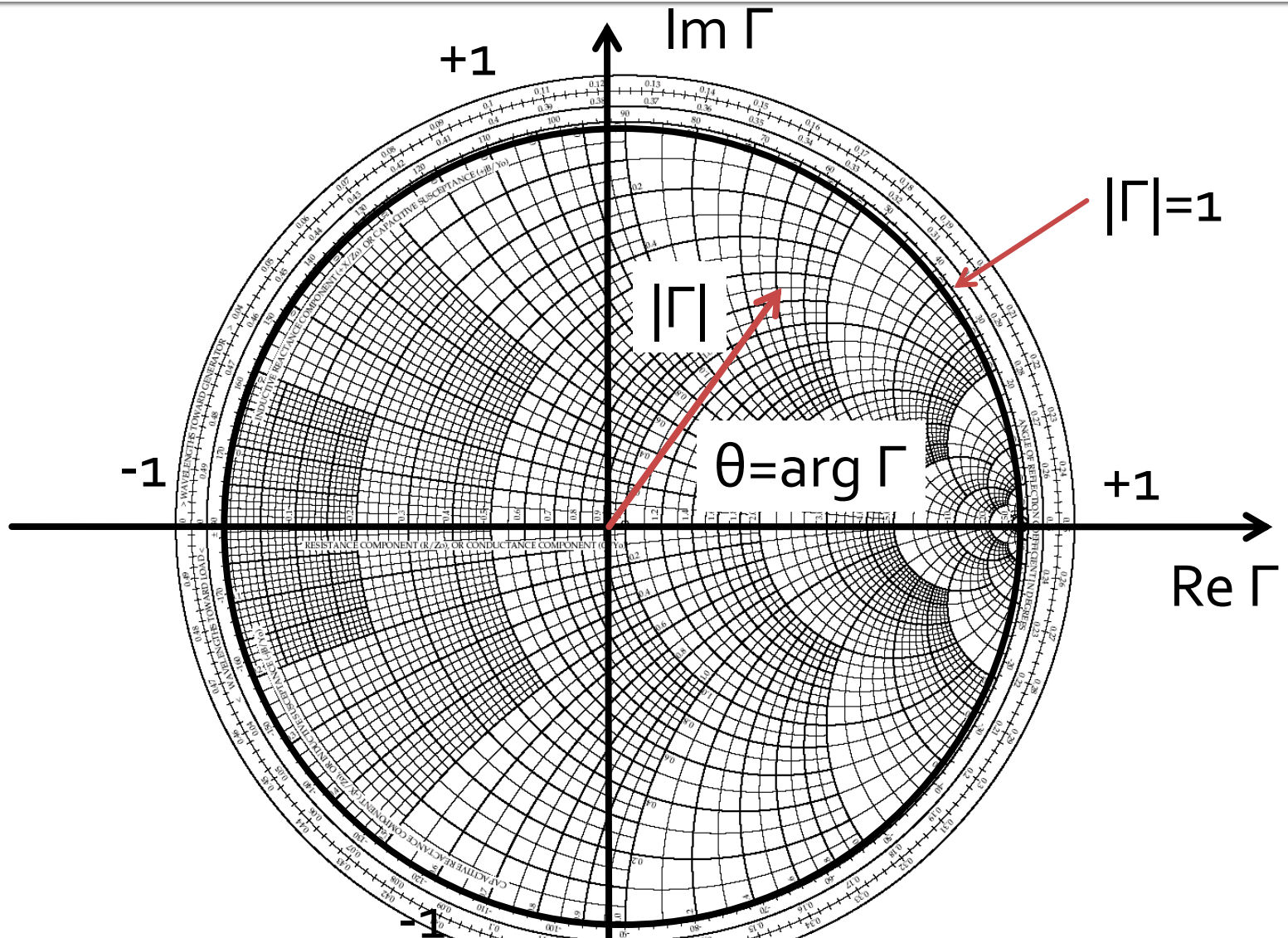


# The Smith Chart



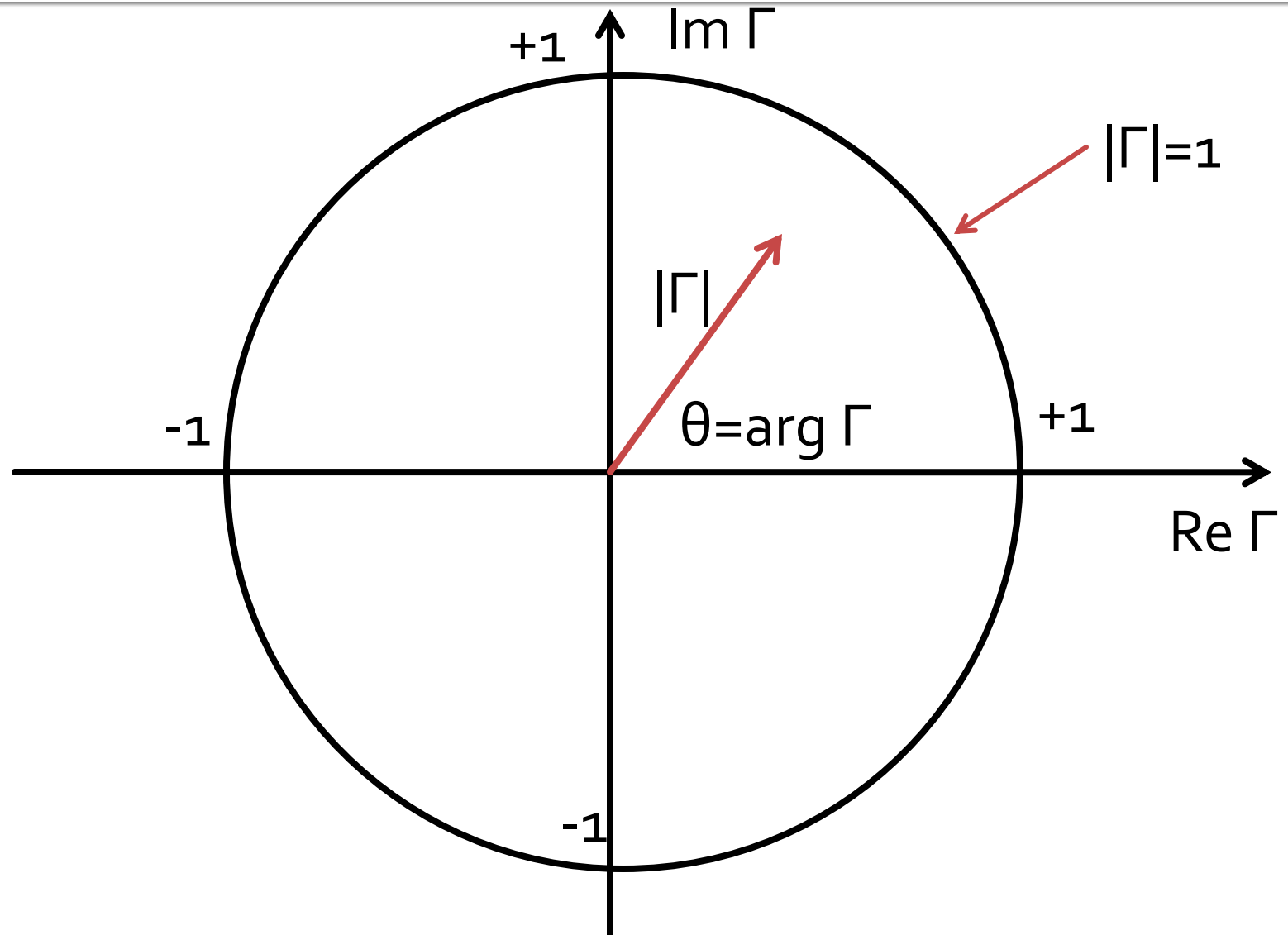

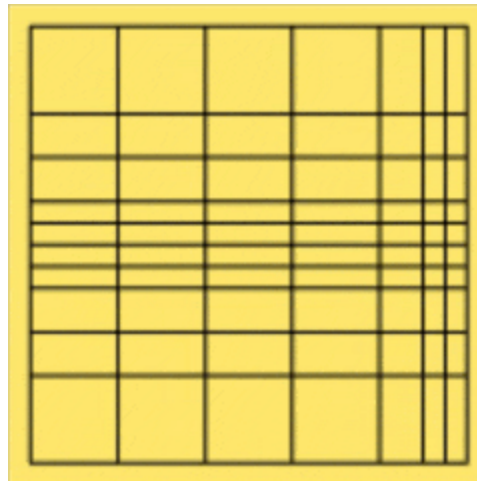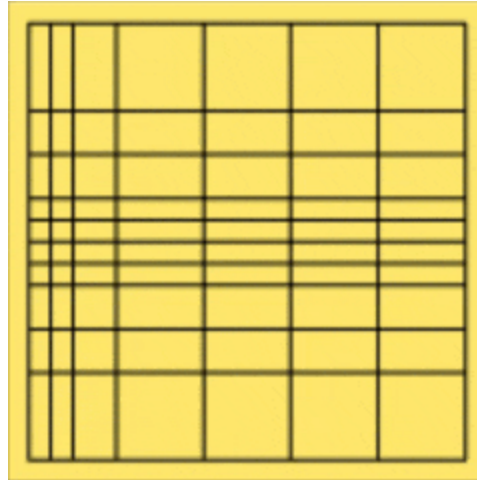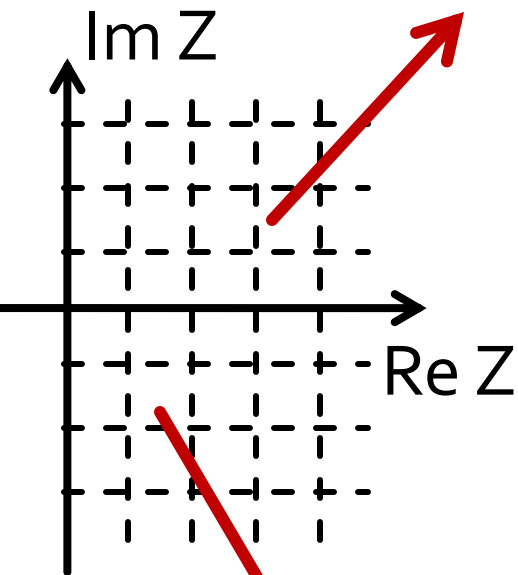
# The Smith Chart


$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$


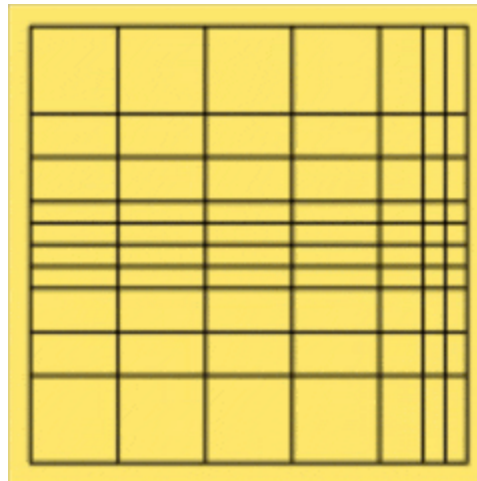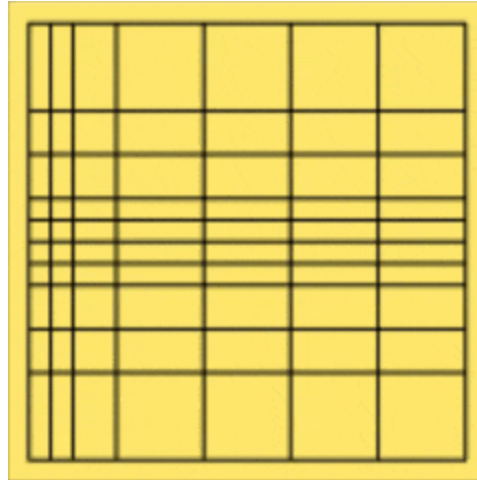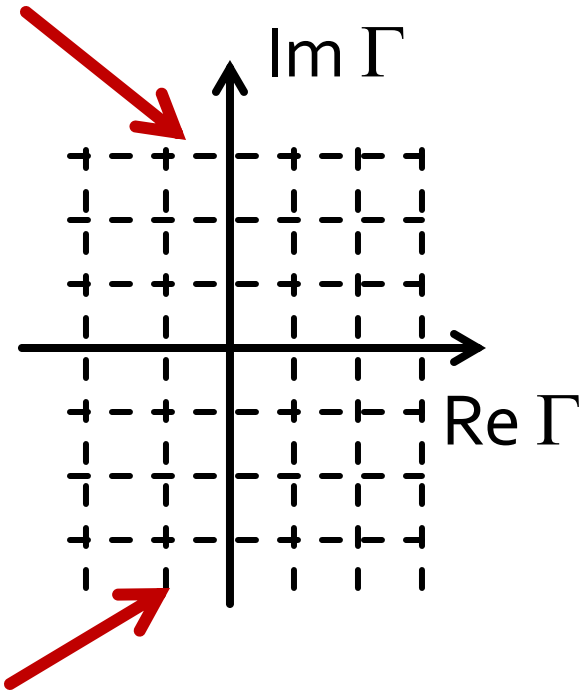
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Y_0 - Y_L}{Y_0 + Y_L} = \frac{1 - y_L}{1 + y_L}$$



# The Smith Chart

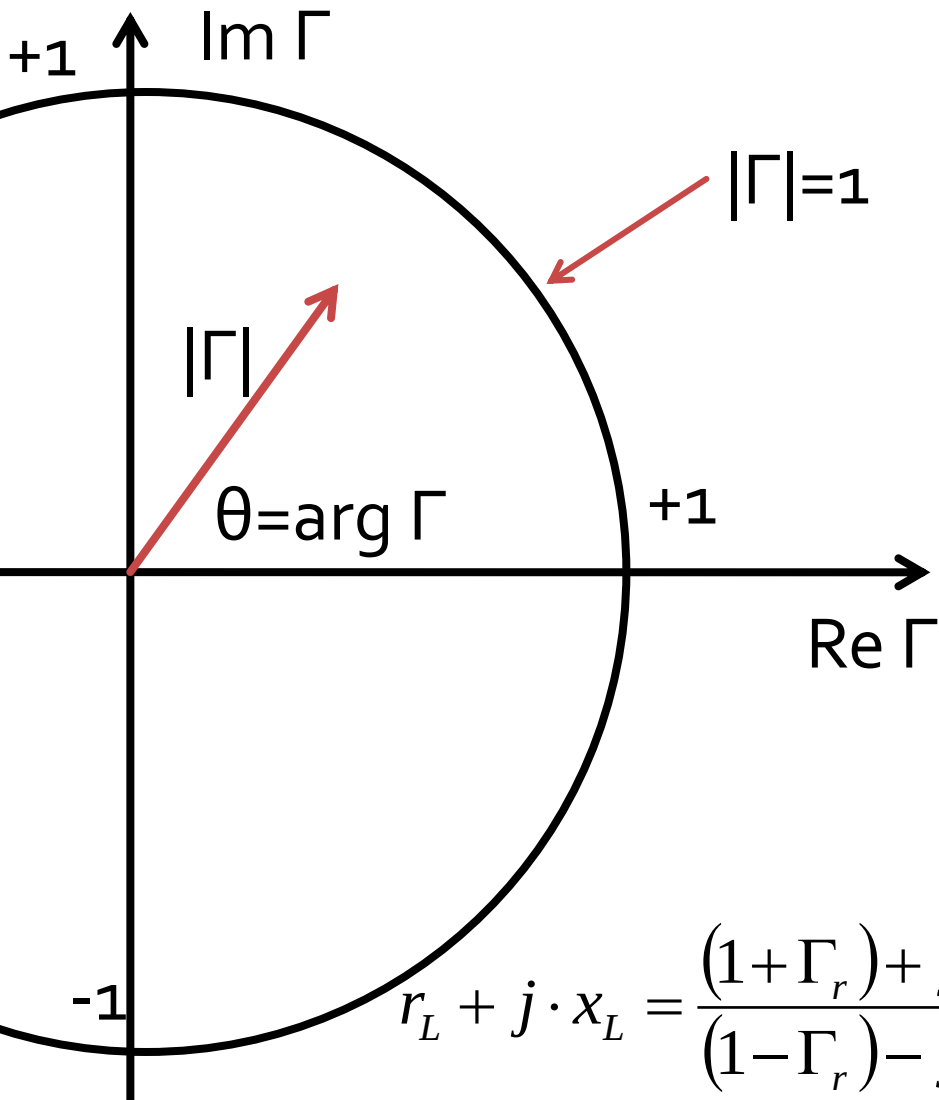

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1} = |\Gamma| \cdot e^{j\theta}$$

$$z_L = \frac{Z_L}{Z_0} \quad y_L = \frac{Y_L}{Y_0} = \frac{Z_0}{Z_L}$$


normalization  $Z_L \rightarrow z_L$  allows using the same chart for any reference impedance  $Z_0$  (the plot becomes independent of the chosen  $Z_0$ )

$$\Gamma = \Gamma_r + j \cdot \Gamma_i$$

$$z_L = \frac{1 + |\Gamma| \cdot e^{j\theta}}{1 - |\Gamma| \cdot e^{j\theta}} = r_L + j \cdot x_L$$

$$r_L + j \cdot x_L = \frac{(1 + \Gamma_r) + j \cdot \Gamma_i}{(1 - \Gamma_r) - j \cdot \Gamma_i} = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} + j \cdot \frac{2 \cdot \Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

# The Smith Chart

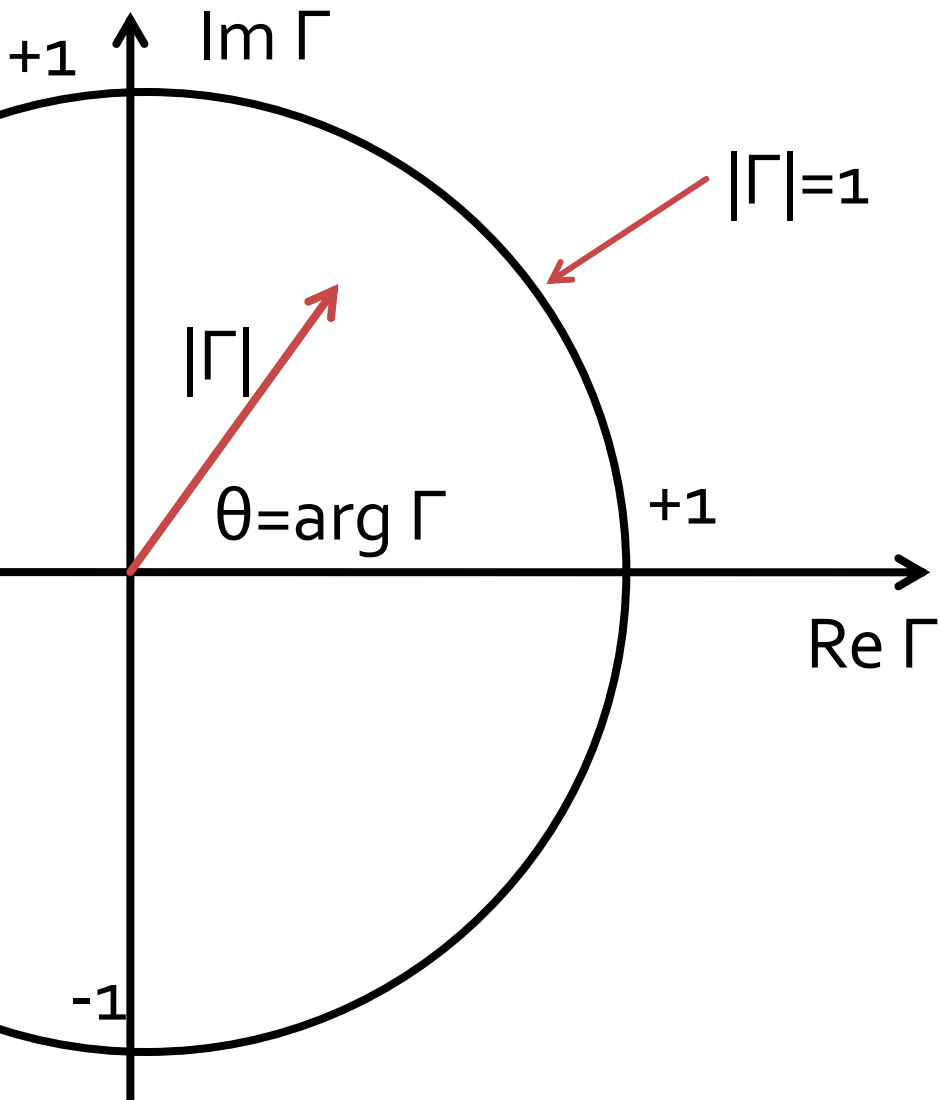

$$r_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$


$$x_L = \frac{2 \cdot \Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

■ Rearranged


$$\left( \Gamma_r - \frac{r_L}{1 + r_L} \right)^2 + \Gamma_i^2 = \left( \frac{1}{1 + r_L} \right)^2$$

$$(\Gamma_r - 1)^2 + \left( \Gamma_i - \frac{1}{x_L} \right)^2 = \left( \frac{1}{x_L} \right)^2$$

# The Smith Chart

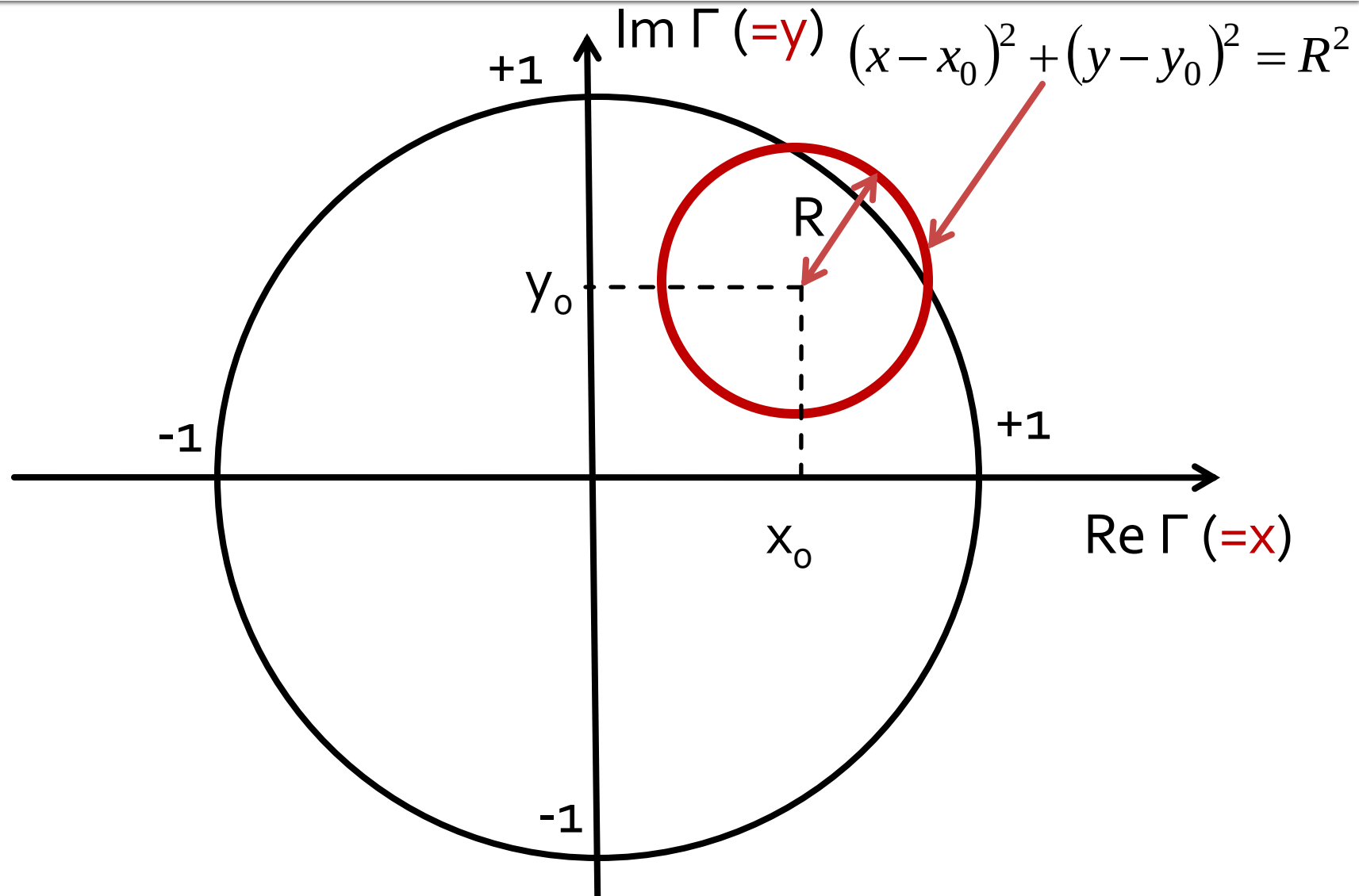

# The Smith Chart

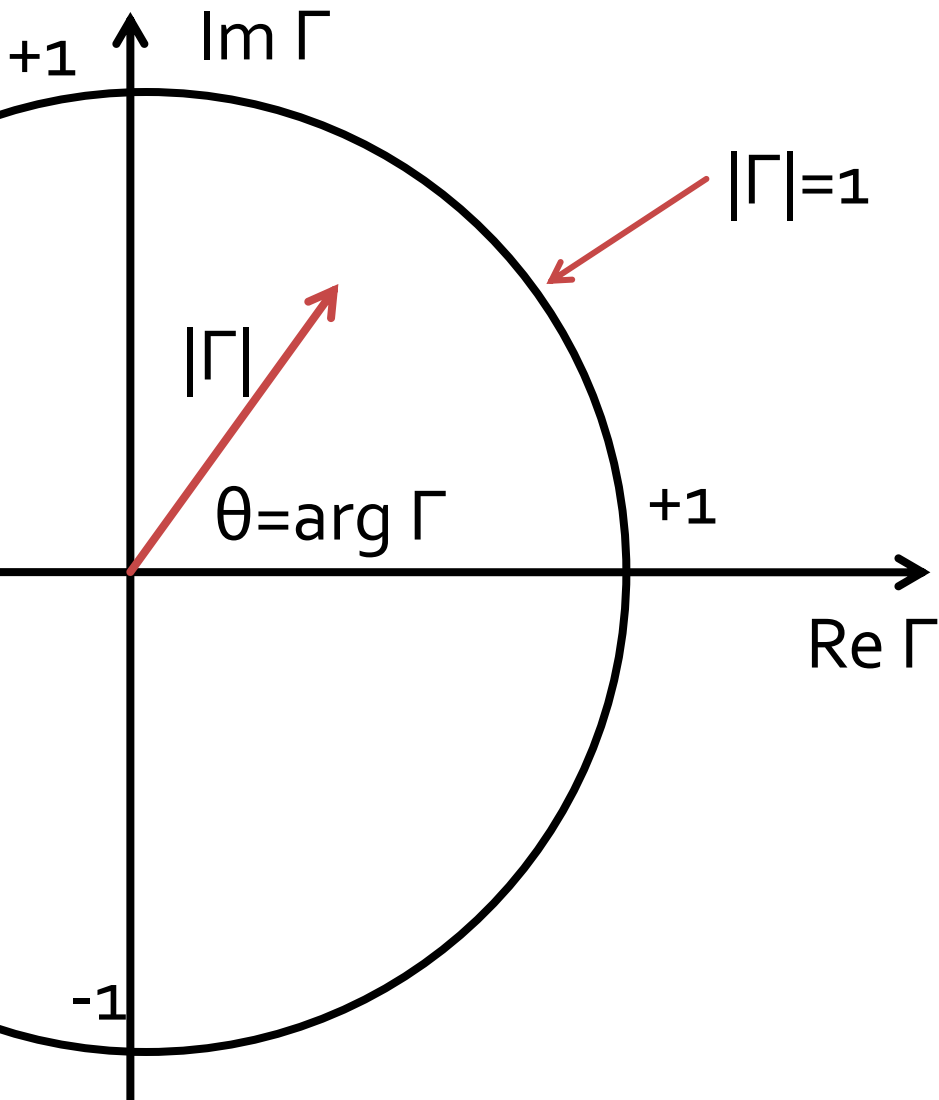

$$\left( \Gamma_r - \frac{r_L}{1+r_L} \right)^2 + \Gamma_i^2 = \left( \frac{1}{1+r_L} \right)^2$$

$$(\Gamma_r - 1)^2 + \left( \Gamma_i - \frac{1}{x_L} \right)^2 = \left( \frac{1}{x_L} \right)^2$$

- **Circles** in the  $(\Gamma_r, \Gamma_i)$  complex plane

$$(x - x_0)^2 + (y - y_0)^2 = R^2$$

# The Smith Chart, resistance


$$\left( \Gamma_r - \frac{r_L}{1+r_L} \right)^2 + \Gamma_i^2 = \left( \frac{1}{1+r_L} \right)^2$$


$$(x - x_0)^2 + (y - y_0)^2 = R^2$$

$$\begin{cases} x_0 = \frac{r_L}{1+r_L} \\ y_0 = 0 \\ R = \frac{1}{1+r_L} \end{cases}$$

- The locus (the set of all points whose location satisfies one or more specified conditions) of the points generated by all impedances having normalized resistance  $r_L$  is a circle which:
  - have its **center on the horizontal axis** ( $y_0=0$ )  $\left( 1 - \frac{r_L}{1+r_L} \right)^2 + 0 = \left( \frac{1}{1+r_L} \right)^2$
  - passes through  **$x=1, y=0$**  point, whatever  $x_0, r_L$
  - have its radius between 0 and 1
    - tends to 0 for large  $r_L$
    - tends to 1 for small  $r_L$
  - when  $r_L$  is **1** passes also through **origin**  $\left( 0 - \frac{r_L}{1+r_L} \right)^2 = \left( \frac{1}{1+r_L} \right)^2 \leftrightarrow r_L = 1$

# The Smith Chart, resistance

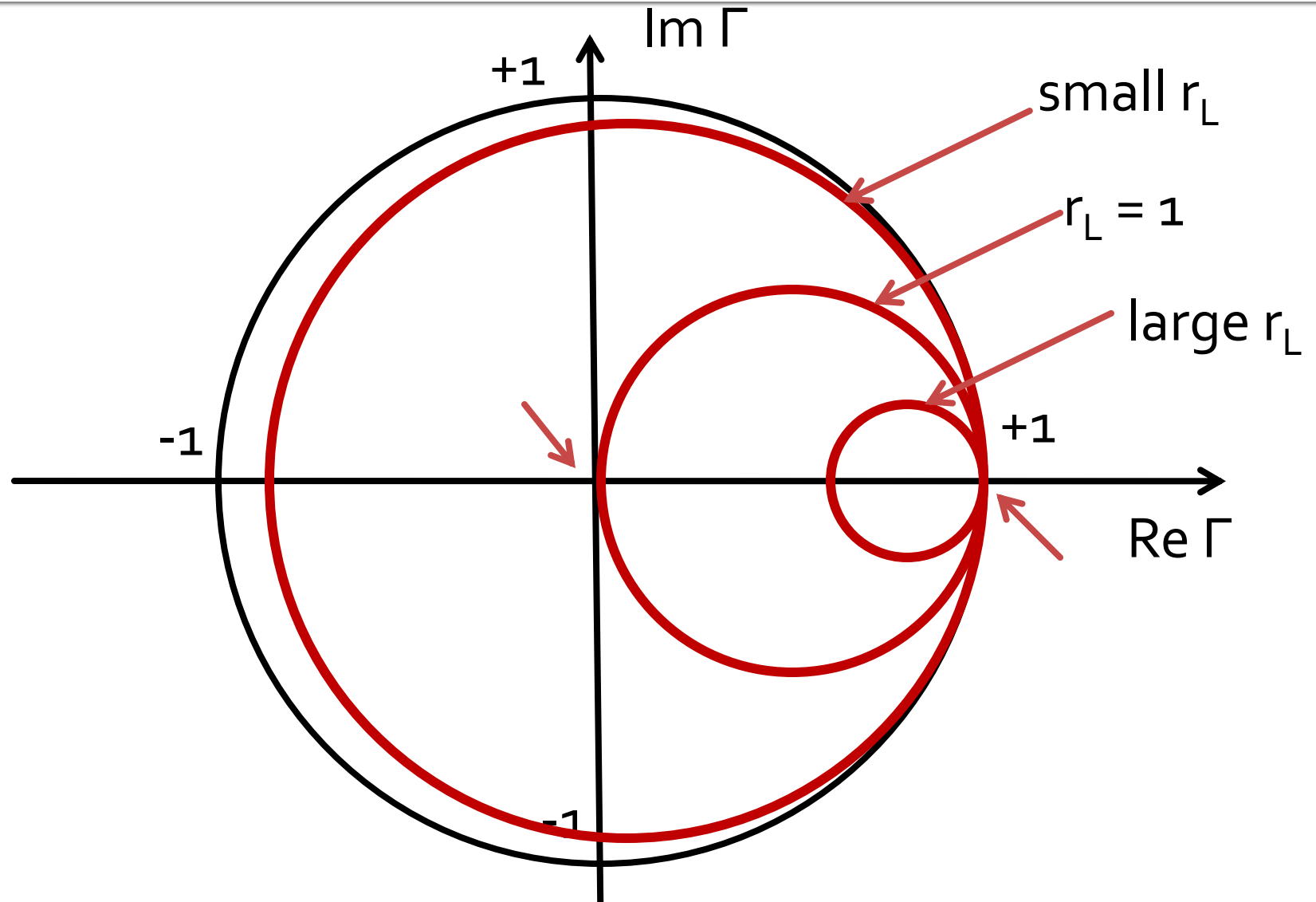

# The Smith Chart, reactance



$$(\Gamma_r - 1)^2 + \left( \Gamma_i - \frac{1}{x_L} \right)^2 = \left( \frac{1}{x_L} \right)^2$$


$$(x - x_0)^2 + (y - y_0)^2 = R^2$$

$$\left\{ \begin{array}{l} x_0 = 1 \\ y_0 = \frac{1}{x_L} \\ R = \frac{1}{x_L} \end{array} \right.$$


- The locus of the points generated by all impedances having normalized resistance  $x_L$  is a circle which:
  - have its **center on a line parallel with the vertical axis** ( $x_0=1$ )
  - passes through  **$x=1, y=0$**  point, whatever  $x_0, x_L$
  - have its radius between 0 and  $\infty$ 
    - tends to 0 for large  $|x_L|$
    - tends to  $\infty$  for small  $|x_L|$
  - when  $x_L$  is **0** transforms itself in the **horizontal axis**
  - if  $x_L > 0$  the circle is above the horizontal axis, otherwise is below it

$$0 + \left( 0 - \frac{1}{x_L} \right)^2 = \left( \frac{1}{x_L} \right)^2$$


# The Smith Chart, reactance

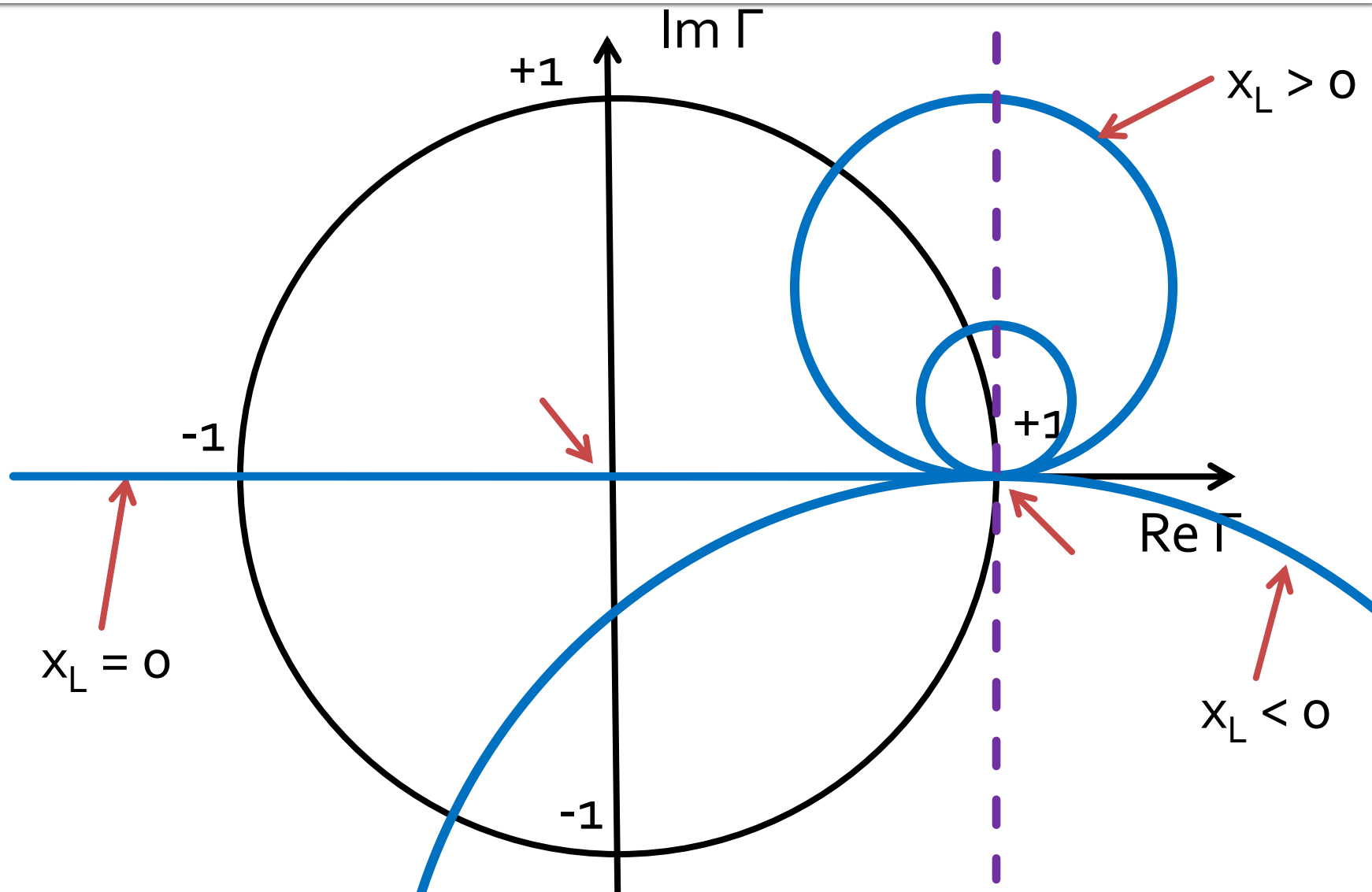


# The Smith Chart, impedance

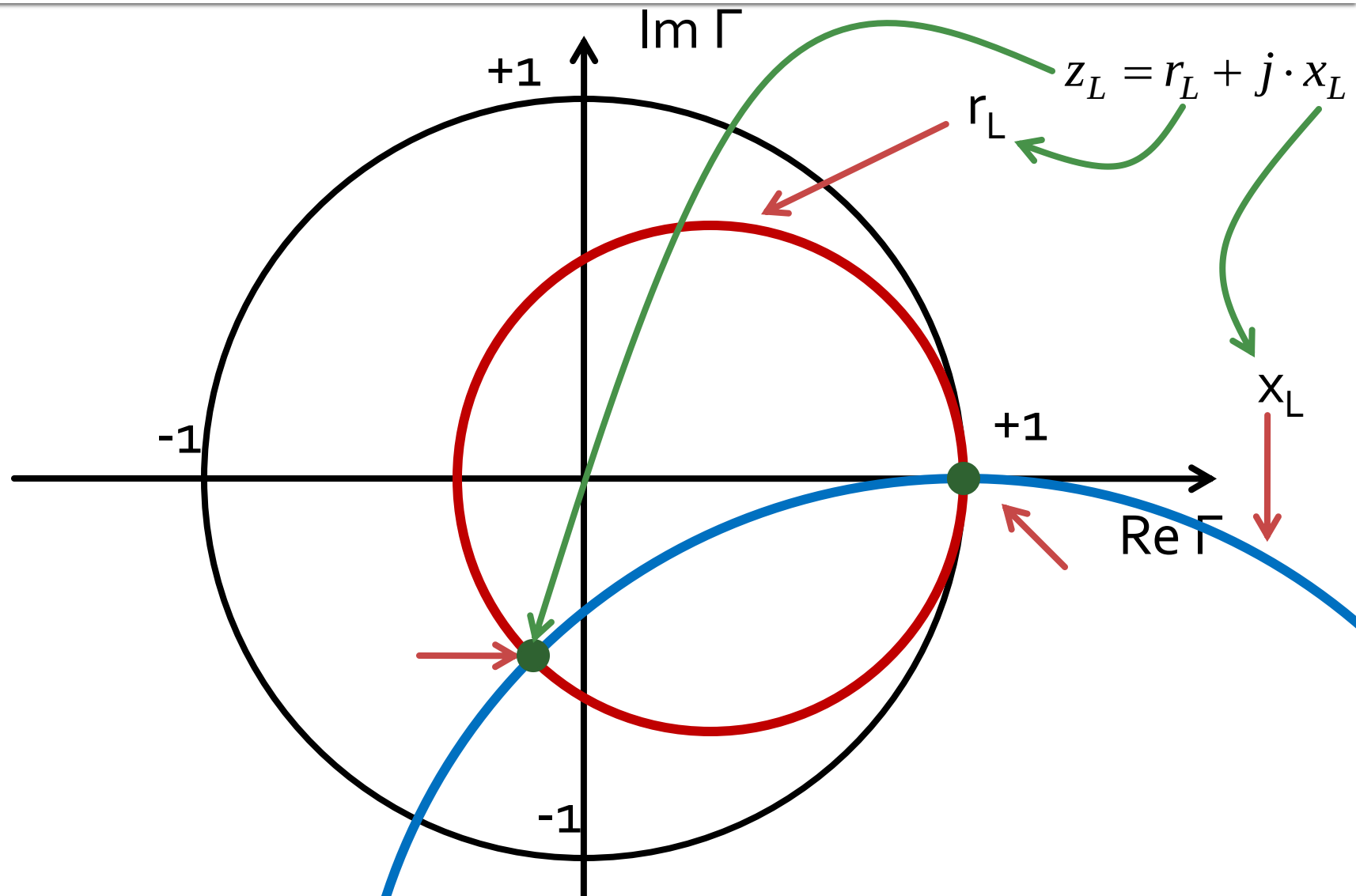

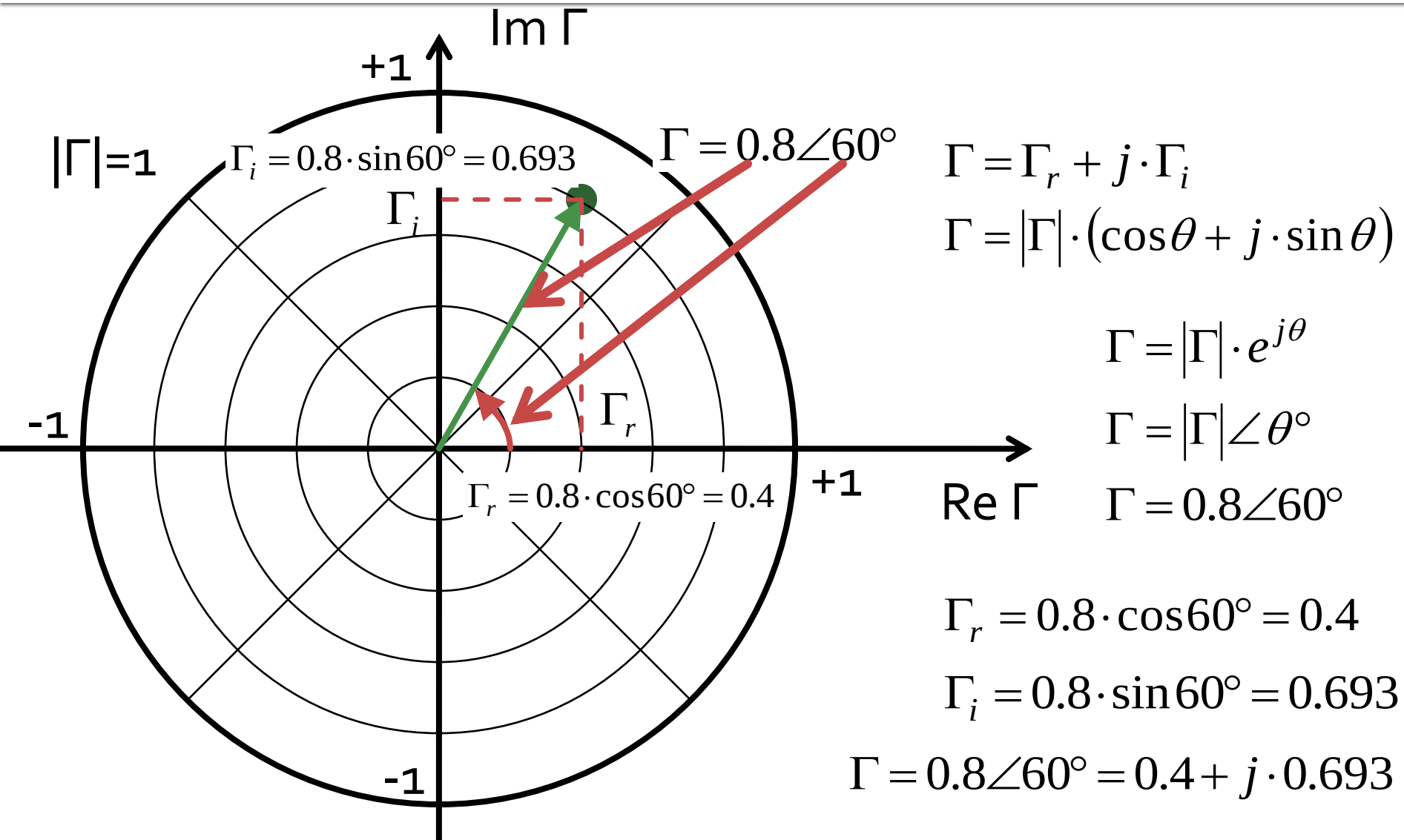
# The Smith Chart, reflection coefficient, Cartesian coordinate system


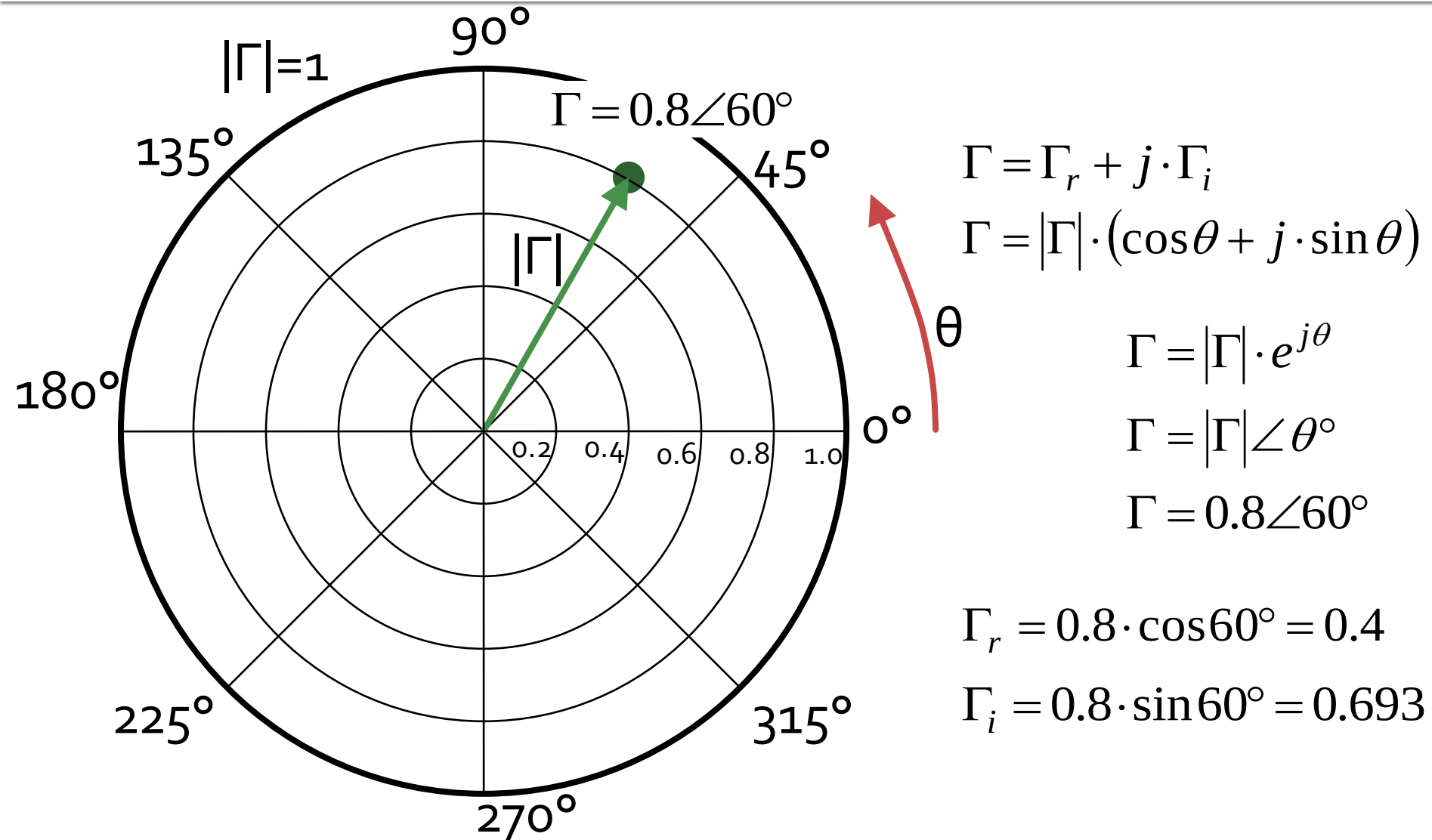
# The Smith Chart, reflection coefficient, Polar coordinate system


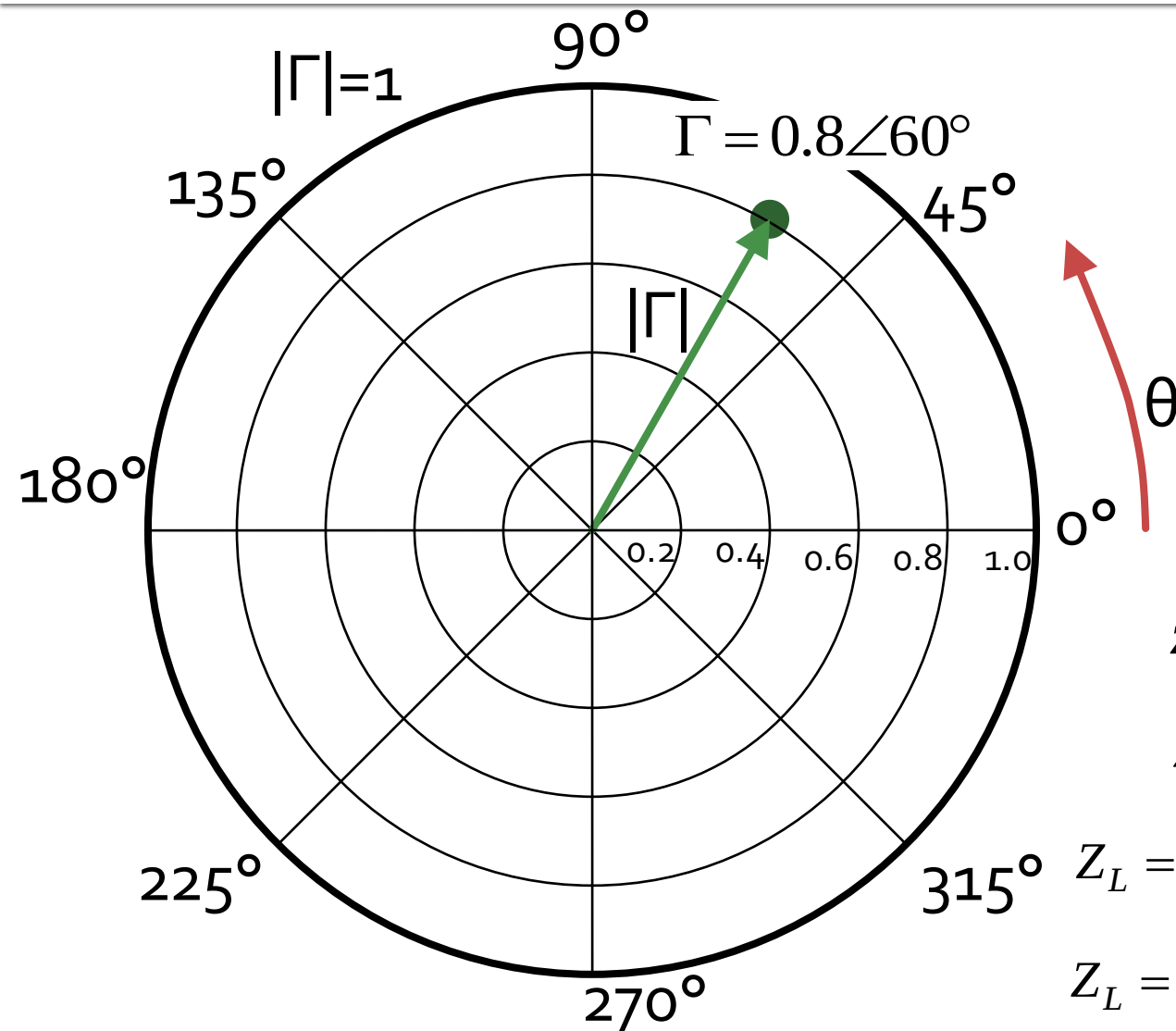
# The Smith Chart, reflection coefficient, impedance



$$\Gamma = |\Gamma| \cdot e^{j\theta}$$

$$\Gamma = |\Gamma| \angle \theta^\circ$$

$$\Gamma = 0.8 \angle 60^\circ$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$

$$z_L = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + 0.8 \angle 60^\circ}{1 - 0.8 \angle 60^\circ}$$


$$z_L = 0.429 + j \cdot 1.65$$

$$Z_L = Z_0 \cdot \frac{1 + \Gamma}{1 - \Gamma} = 50\Omega \cdot \frac{1 + 0.8 \angle 60^\circ}{1 - 0.8 \angle 60^\circ}$$


$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$
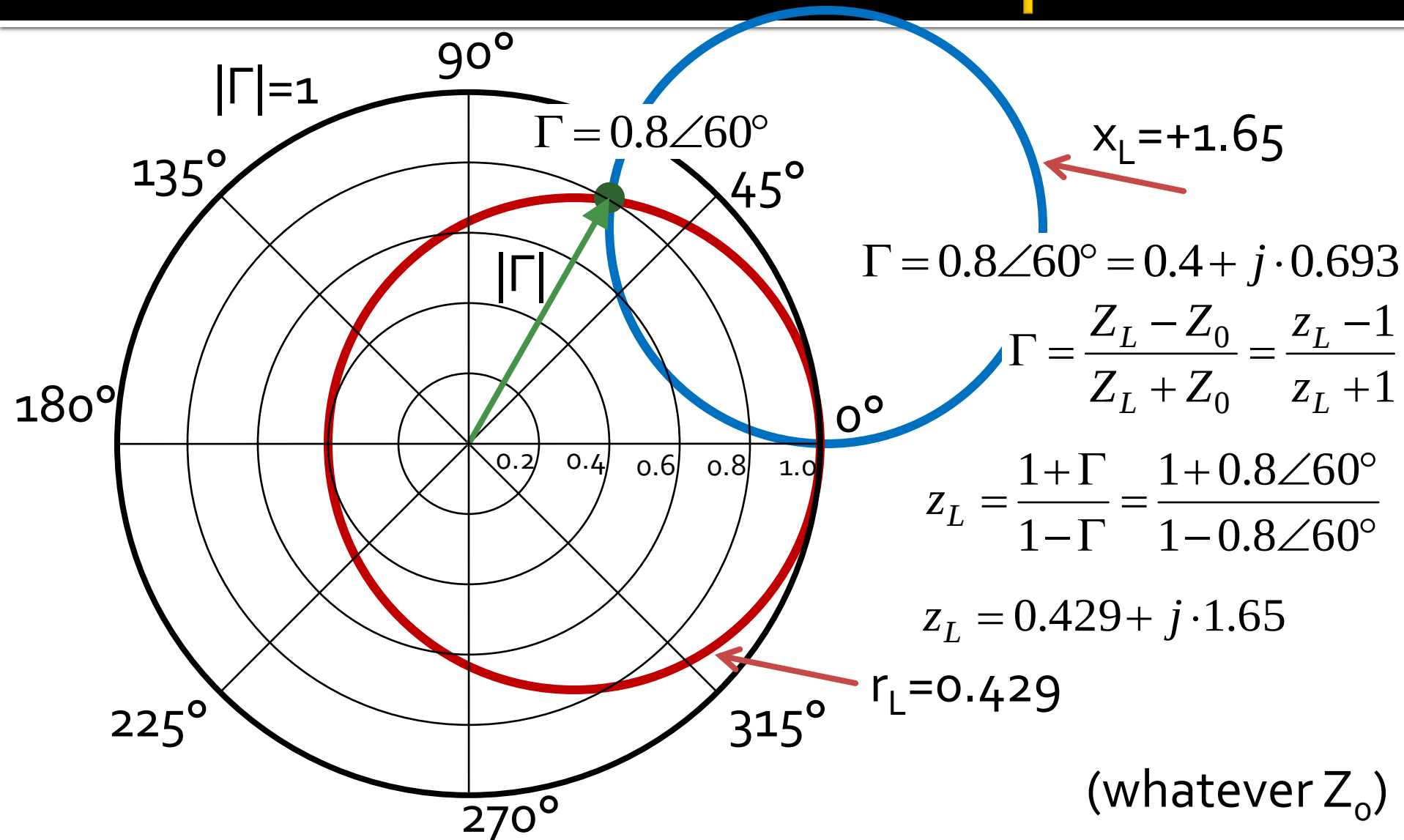
# Equivalence



reflection coefficient  $\Leftrightarrow$  impedance


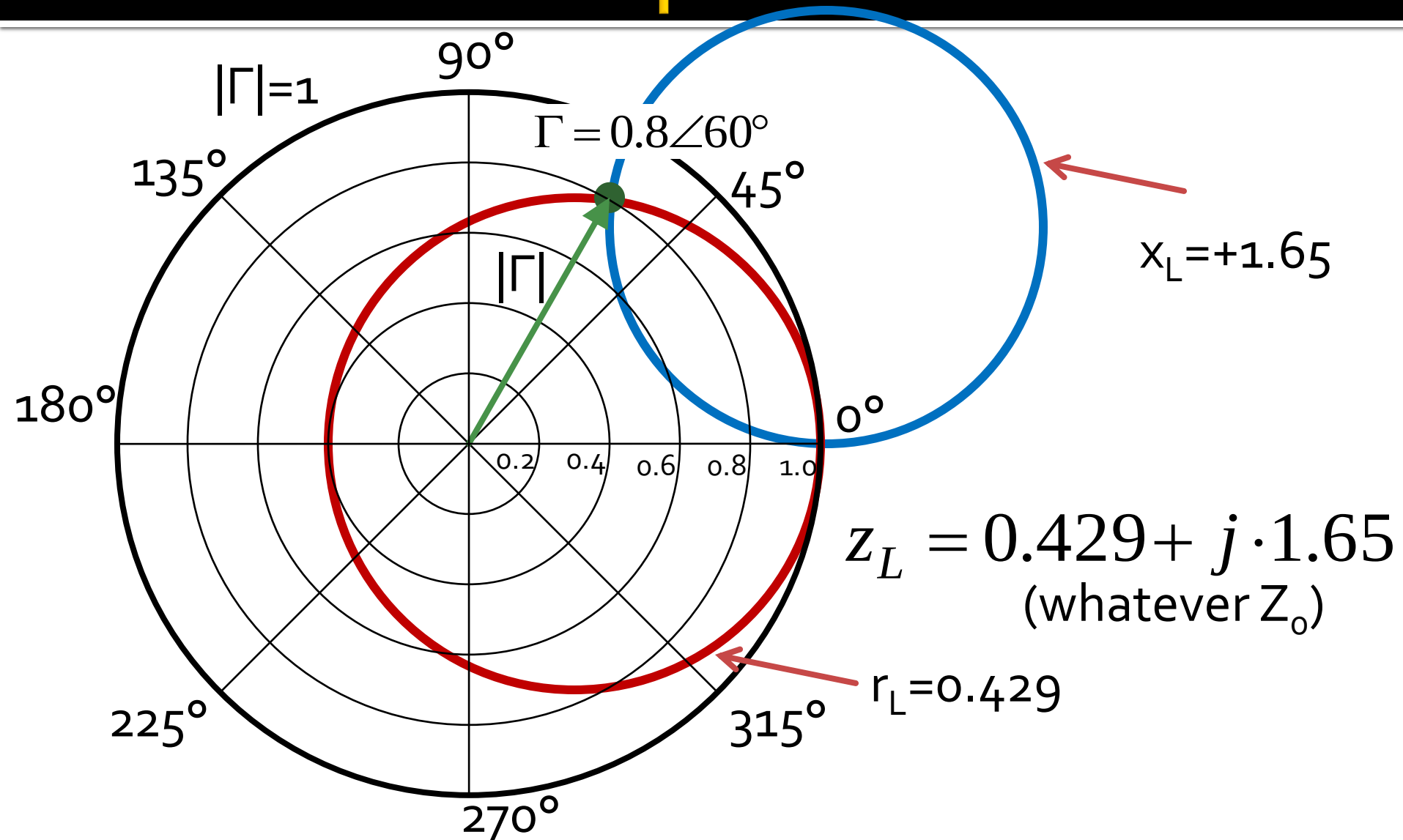
# The Smith Chart, reflection coefficient $\Leftrightarrow$ impedance


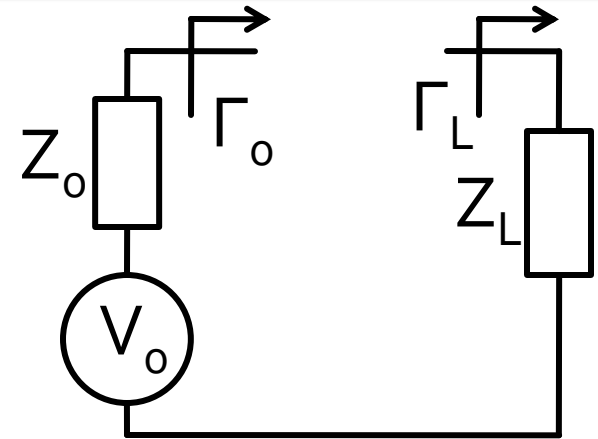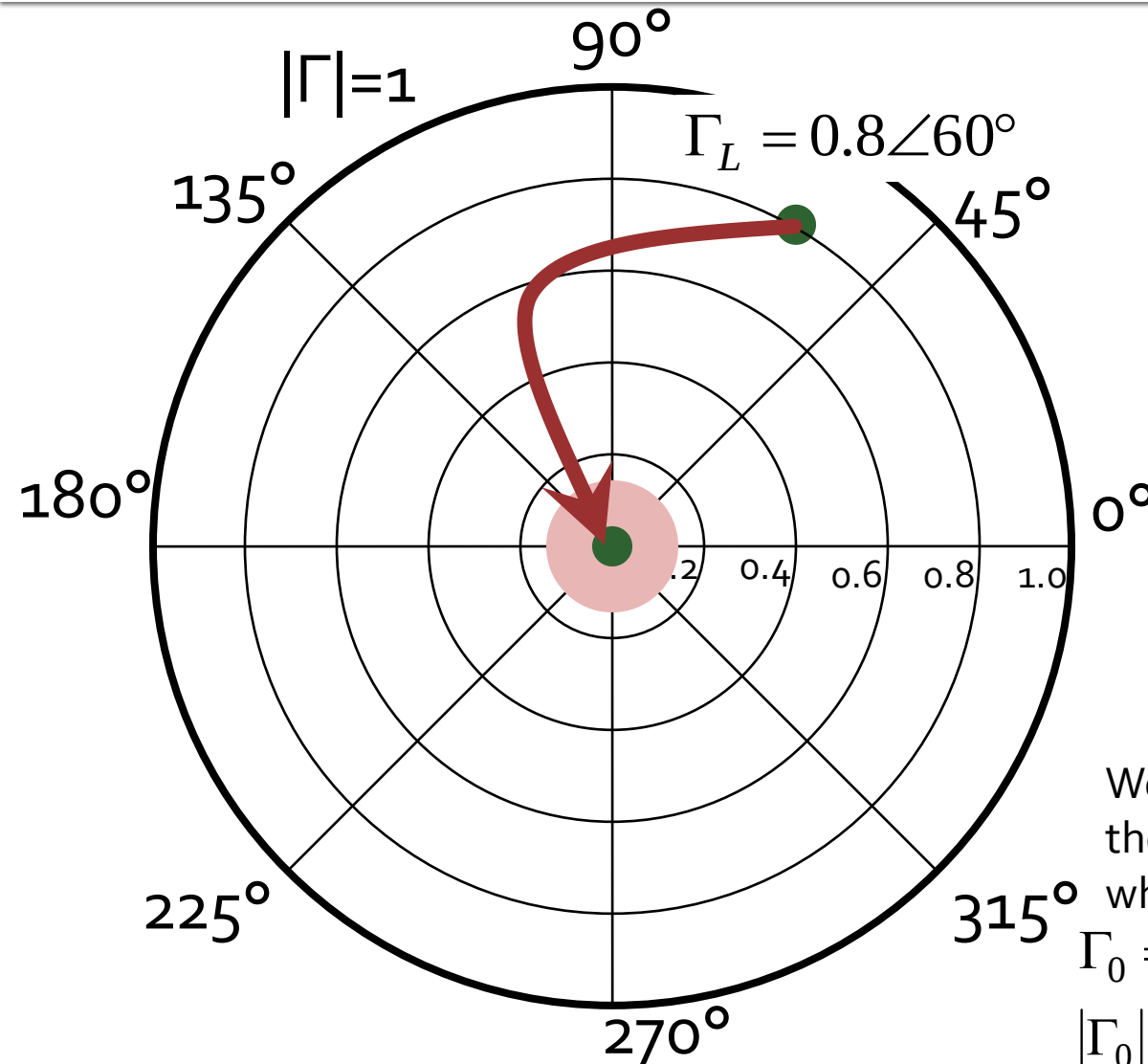
# The Smith Chart, reflection coefficient, matching



Matching  $Z_L$  load to  $Z_o$  source.  
We normalize  $Z_L$  over  $Z_o$

$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

$$z_L = 0.429 + j \cdot 1.65$$

$$\Gamma_L = 0.8\angle 60^\circ$$


We must move the point denoting the reflection coefficient in the area where with a  $Z_o$  source we have:

$$\Gamma_o = 0 \quad \text{perfect match}$$


$$|\Gamma_o| \leq \Gamma_m \quad \text{"good enough" match}$$

# Example

## ■ Laboratory 1

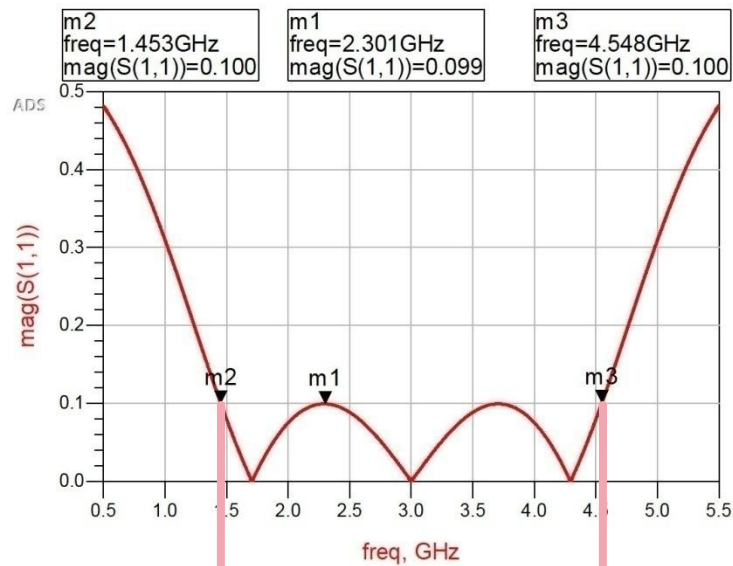


$$|\Gamma_0| \leq \Gamma_m$$

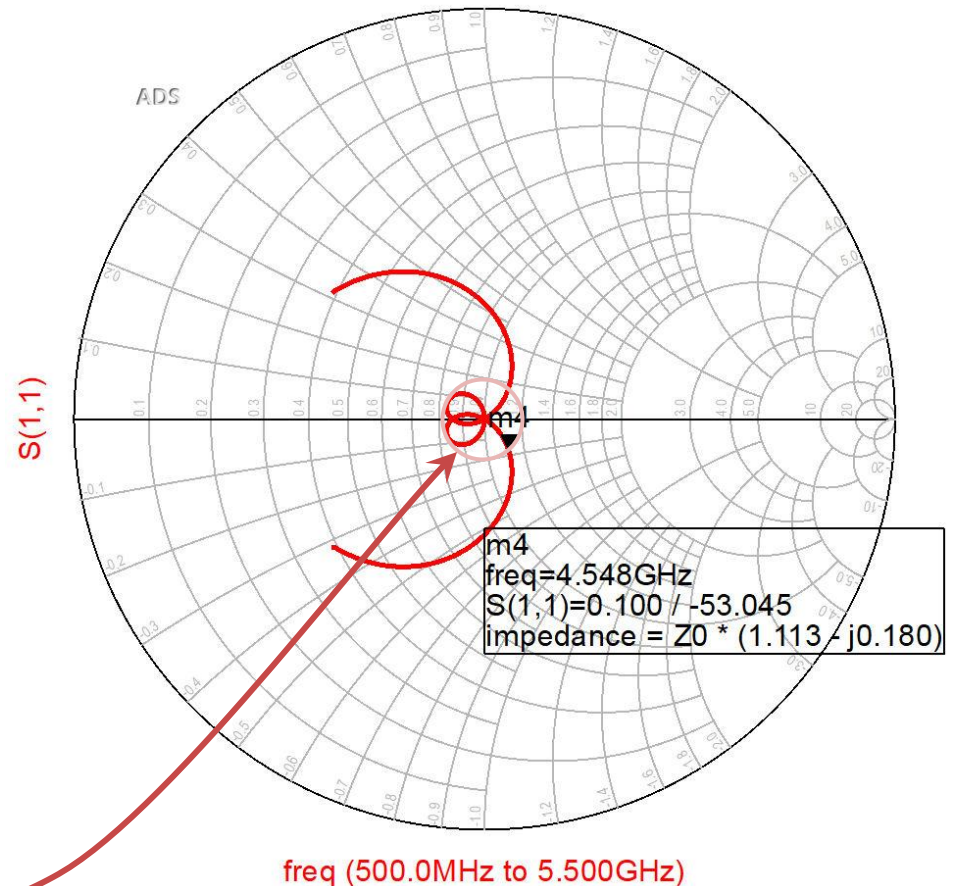


# Example

## ■ Laboratory 1

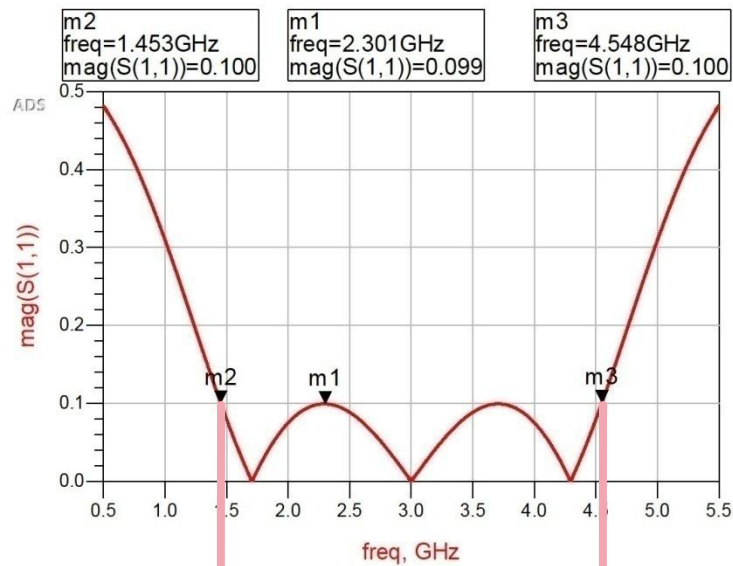



$$|\Gamma_0| \leq \Gamma_m$$

$S(1,1)$

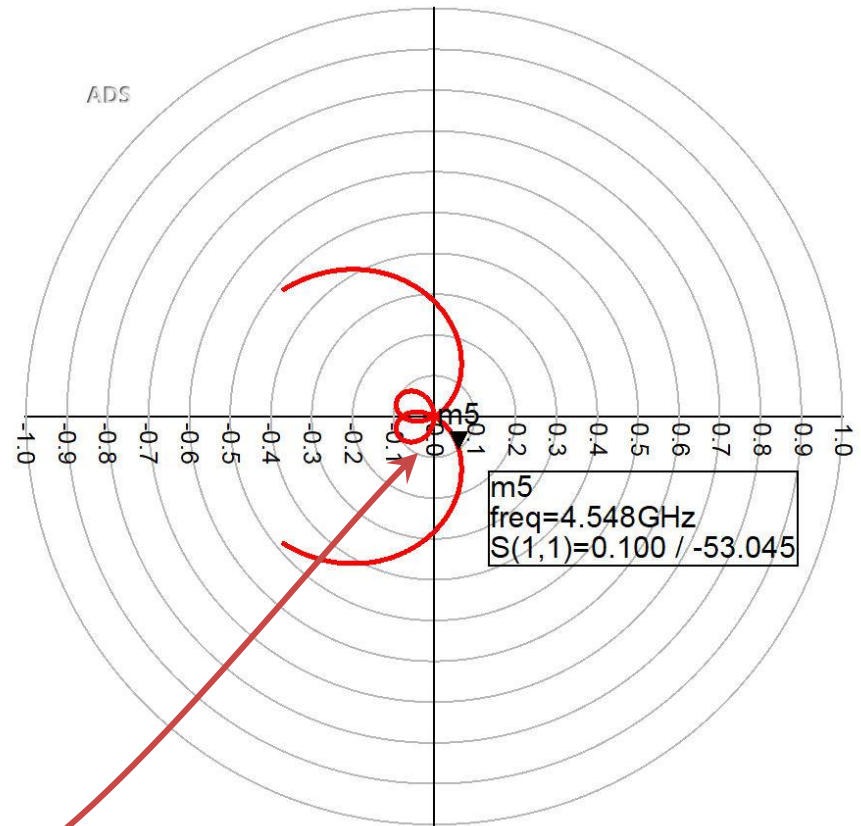

freq (500.0MHz to 5.500GHz)
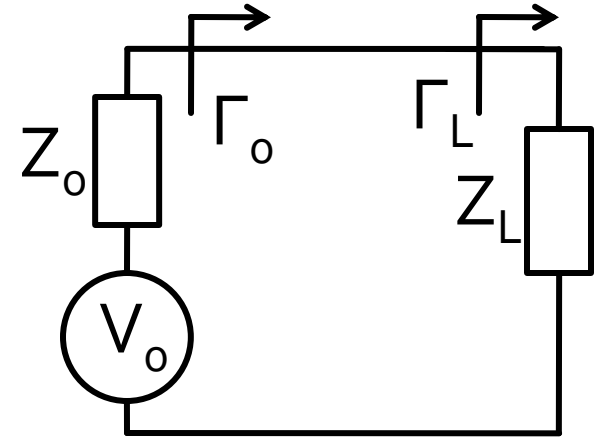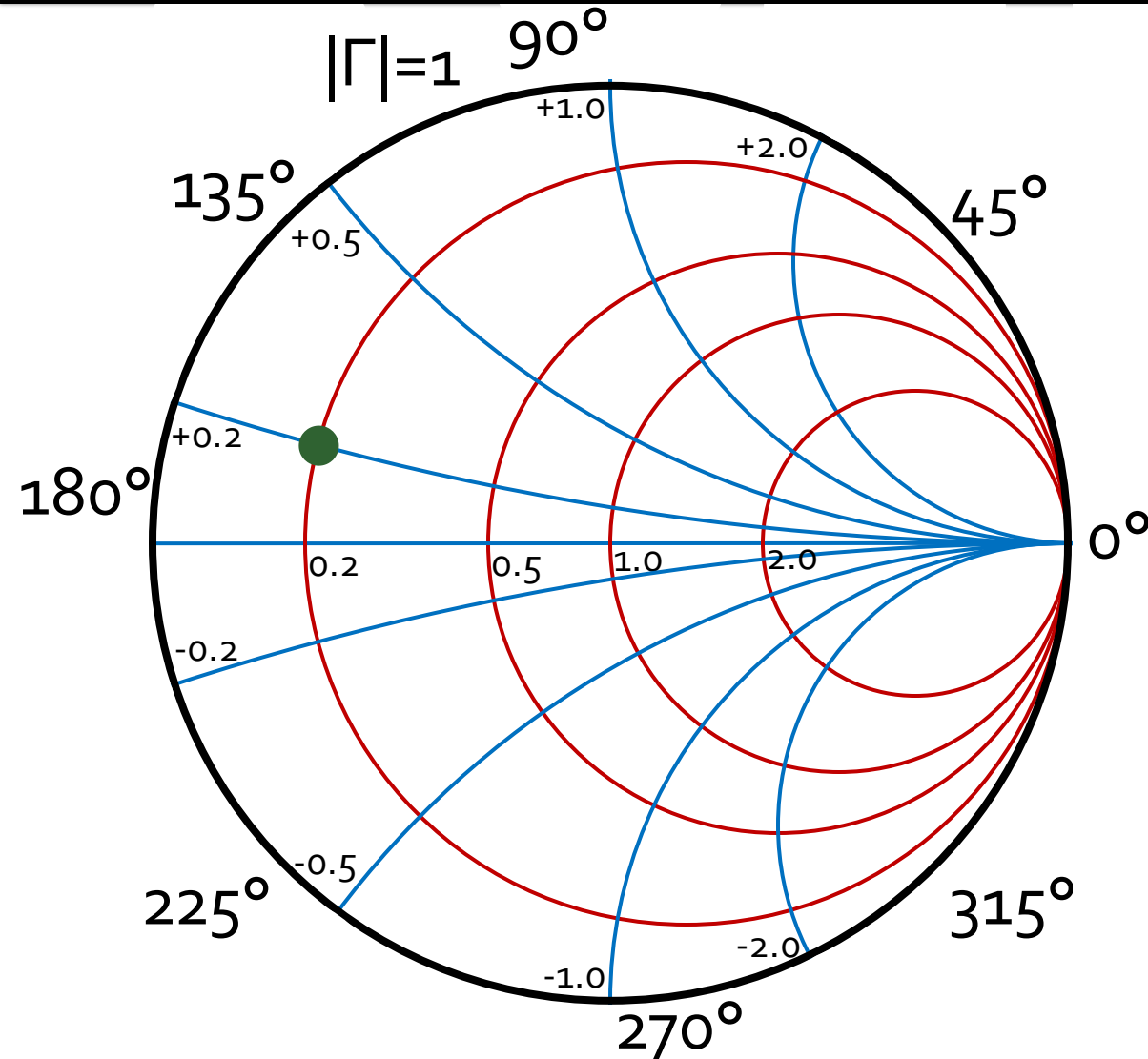
# The Smith Chart, impedance/reflection coefficient





$$Z_0 = 50\Omega$$

$$Z_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = 0.2 + j \cdot 0.2$$

$$\Gamma_L = \Gamma_0 = 0.678 \angle 156.5^\circ$$

# The Smith Chart, series reactance

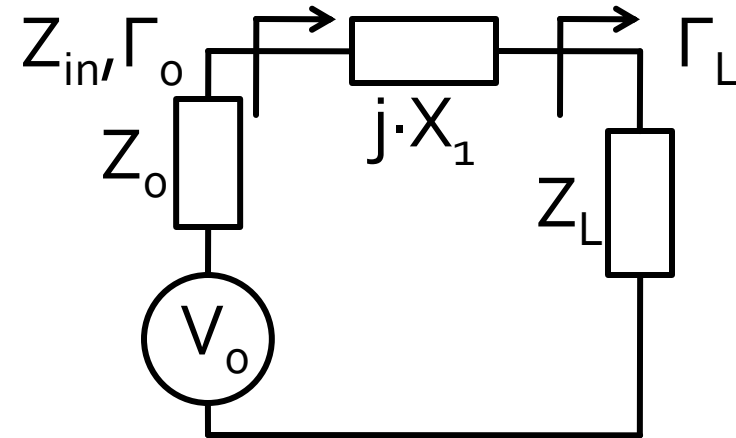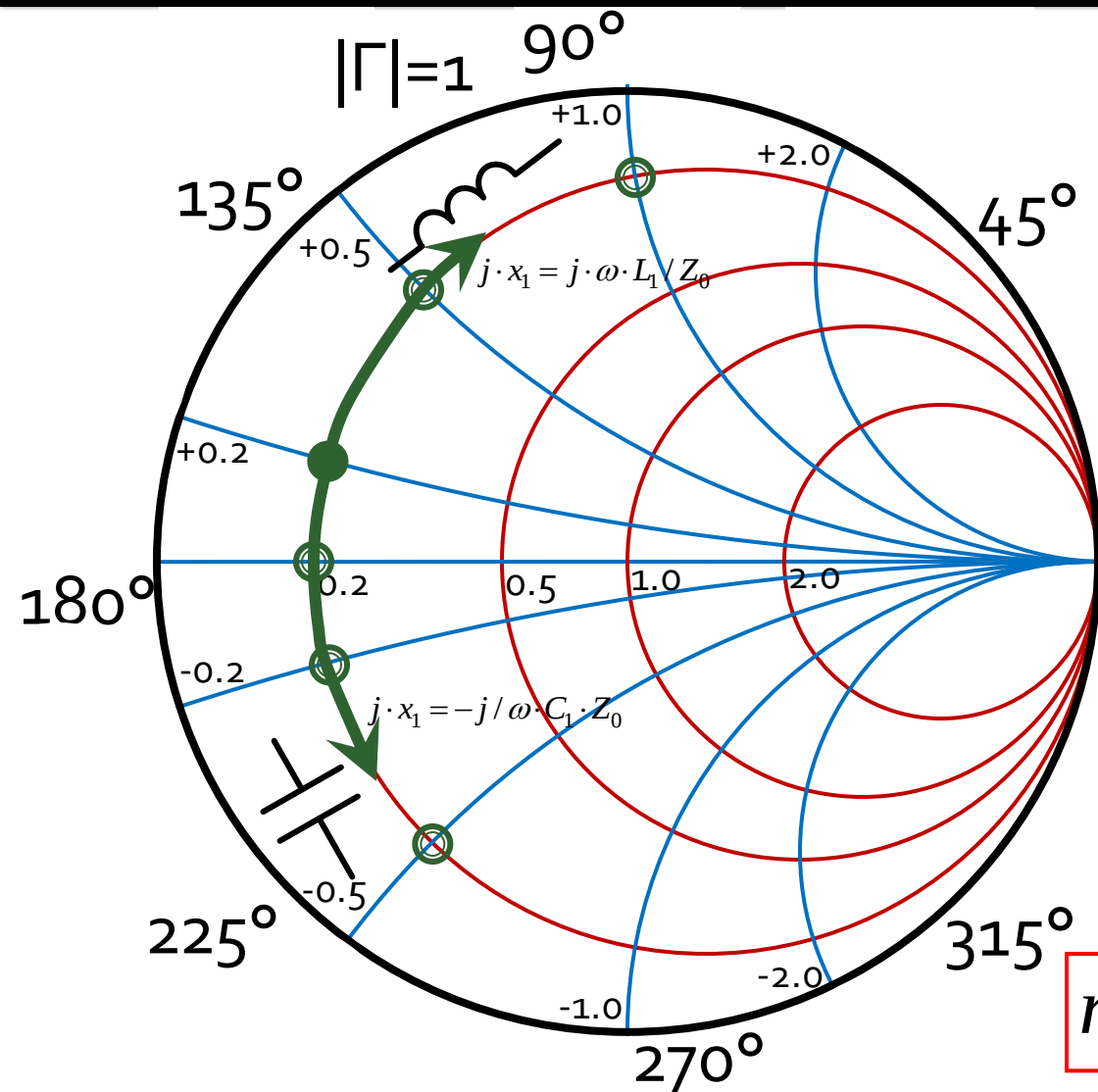

$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$

$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_L + j \cdot X_1 = R_L + j \cdot (X_L + X_1)$$


$$z_{in} = r_L + j \cdot (x_L + x_1)$$

$$j \cdot x_1 = j \cdot \omega \cdot L_1 / Z_0 > 0$$

$$j \cdot x_1 = -j / \omega \cdot C_1 \cdot Z_0 < 0$$

$$r_{in} = r_L$$

# ADS, Smith Chart, series reactance

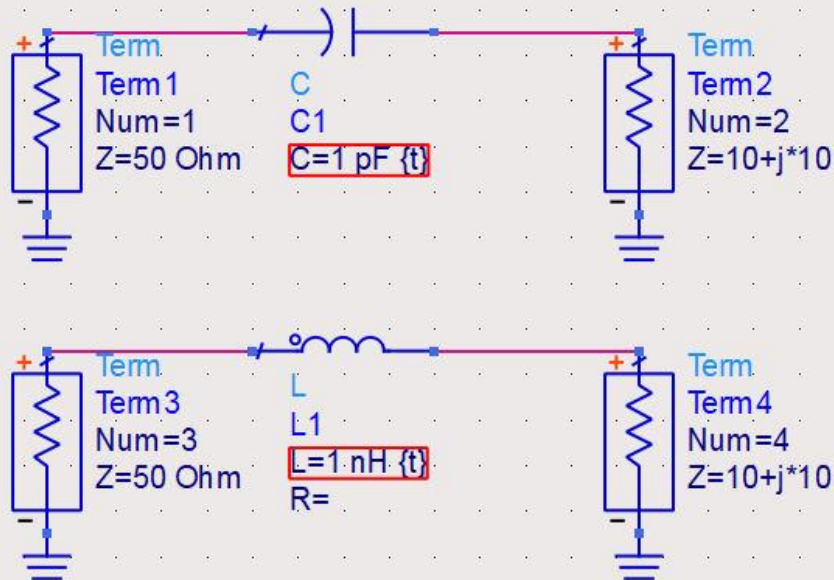

S-PARAMETERS

S\_Param  
SP1

Freq=1.0 GHz



**Tune Parameters**

Simulate  
While Slider Moves  
Tune


Parameters  
Include Opt Params  
Enable/Disable...  
☐ Display Full Name  
☐ Snap Slider to Step

Traces and Values  
Store... Recall...  
Trace Visibility...  
Reset Values  
Close Unassociated Data Displays  
Update Schematic  
Close Help



adaptare\_LC\_lib:X:S:schematic

| C1.C (pF) |        | L1.L (nH) |       |
|-----------|--------|-----------|-------|
| Value     | 39.605 |           | 0.895 |
| Max       | 50     |           | 40    |
| Min       | 0.5    |           | 0.5   |
| Step      | 0.1    |           | 0.1   |
| Scale     | Lin    |           | Lin   |

# ADS, Smith Chart, series reactance

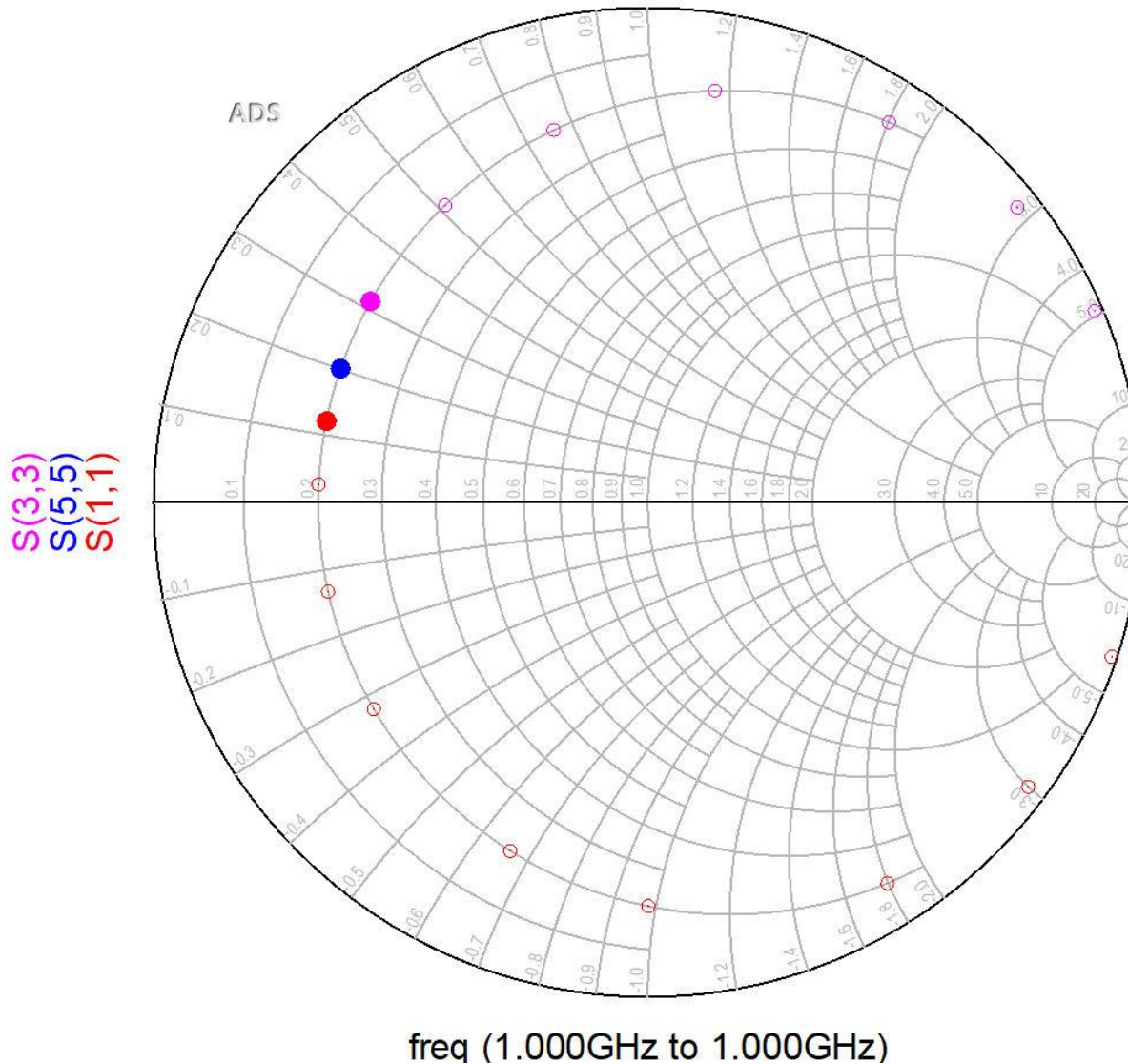

# The Smith Chart, series resistance

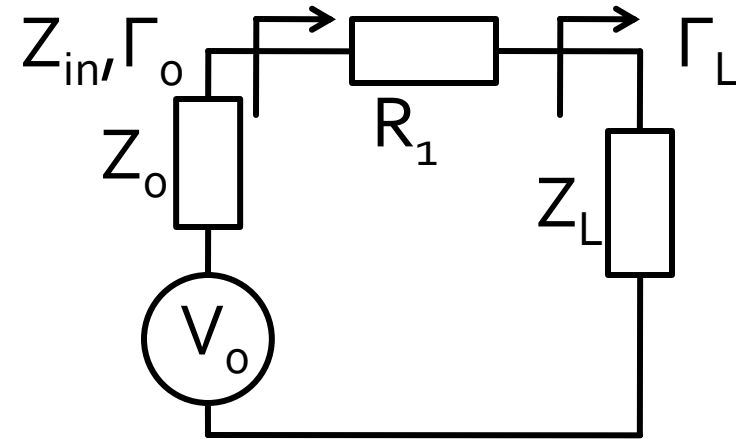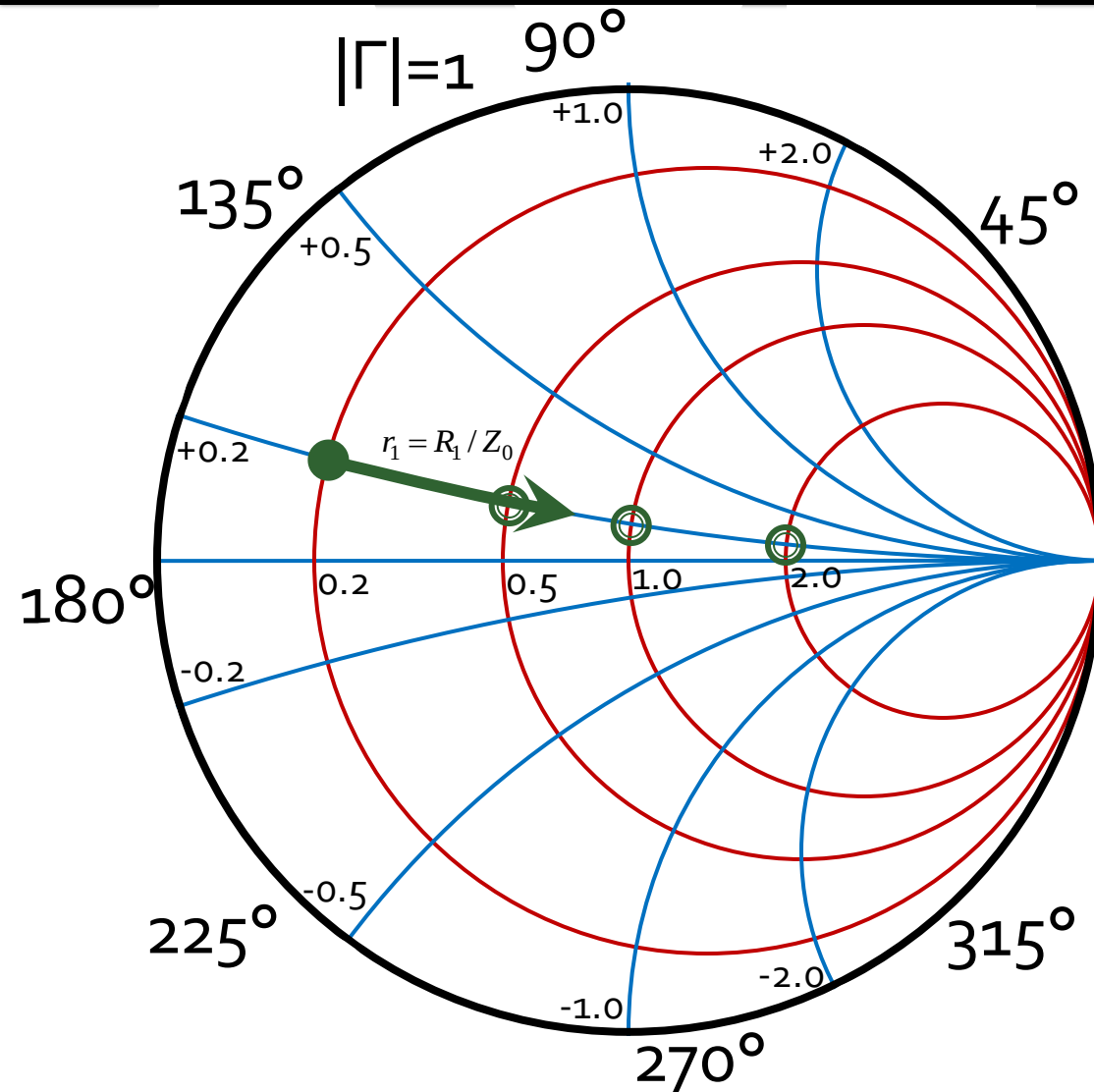

$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$


$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_L + R_1 = (R_L + R_1) + j \cdot X_L$$



$$z_{in} = z_L + r_1 = (r_L + r_1) + j \cdot x_L$$

$$x_{in} = x_L \quad r_{in} = r_L + R_1 / Z_0$$

# ADS, Smith Chart, series resistance

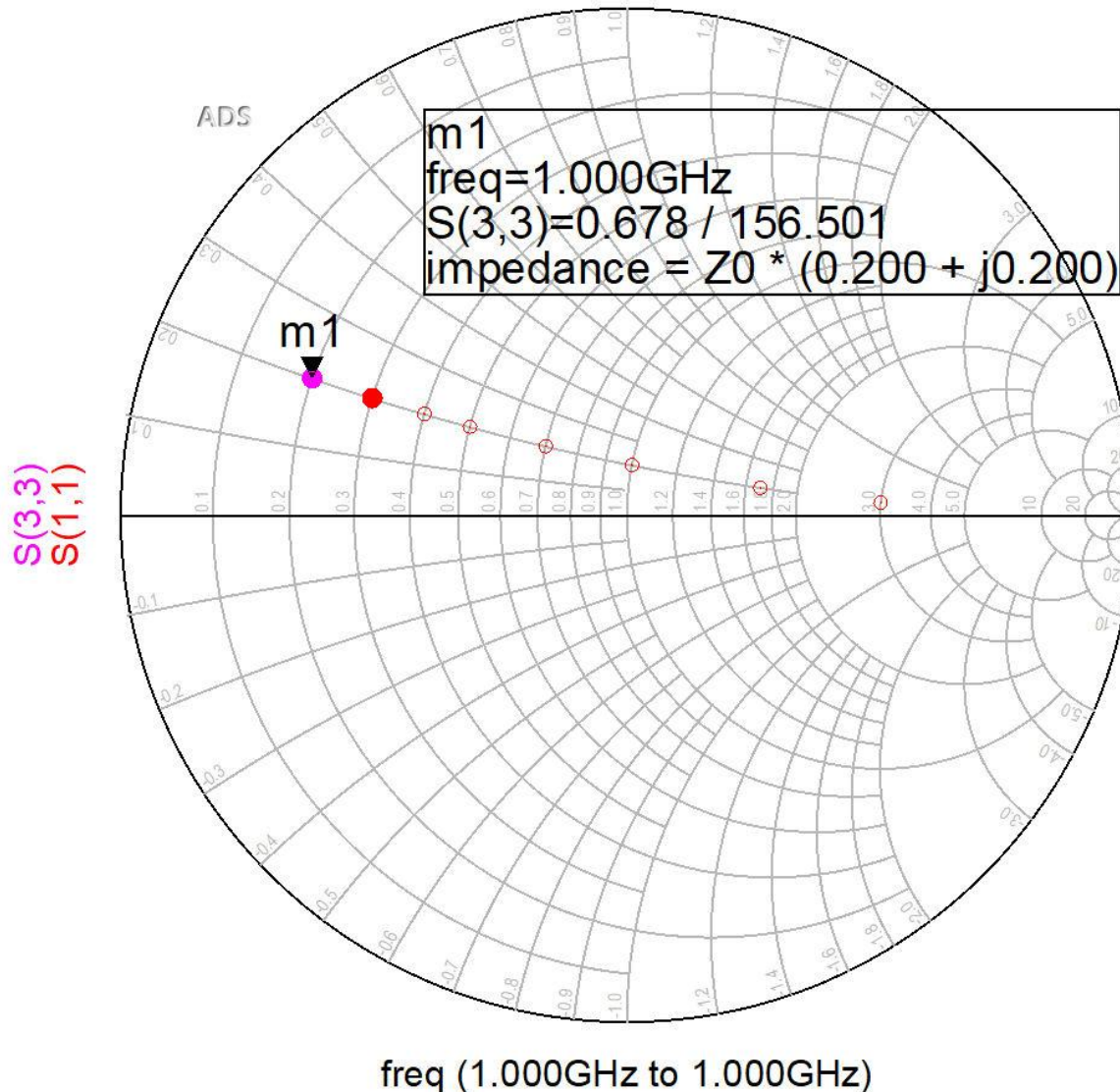
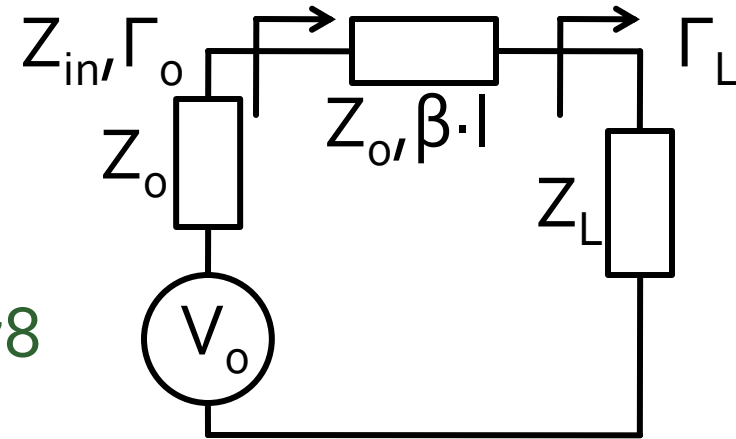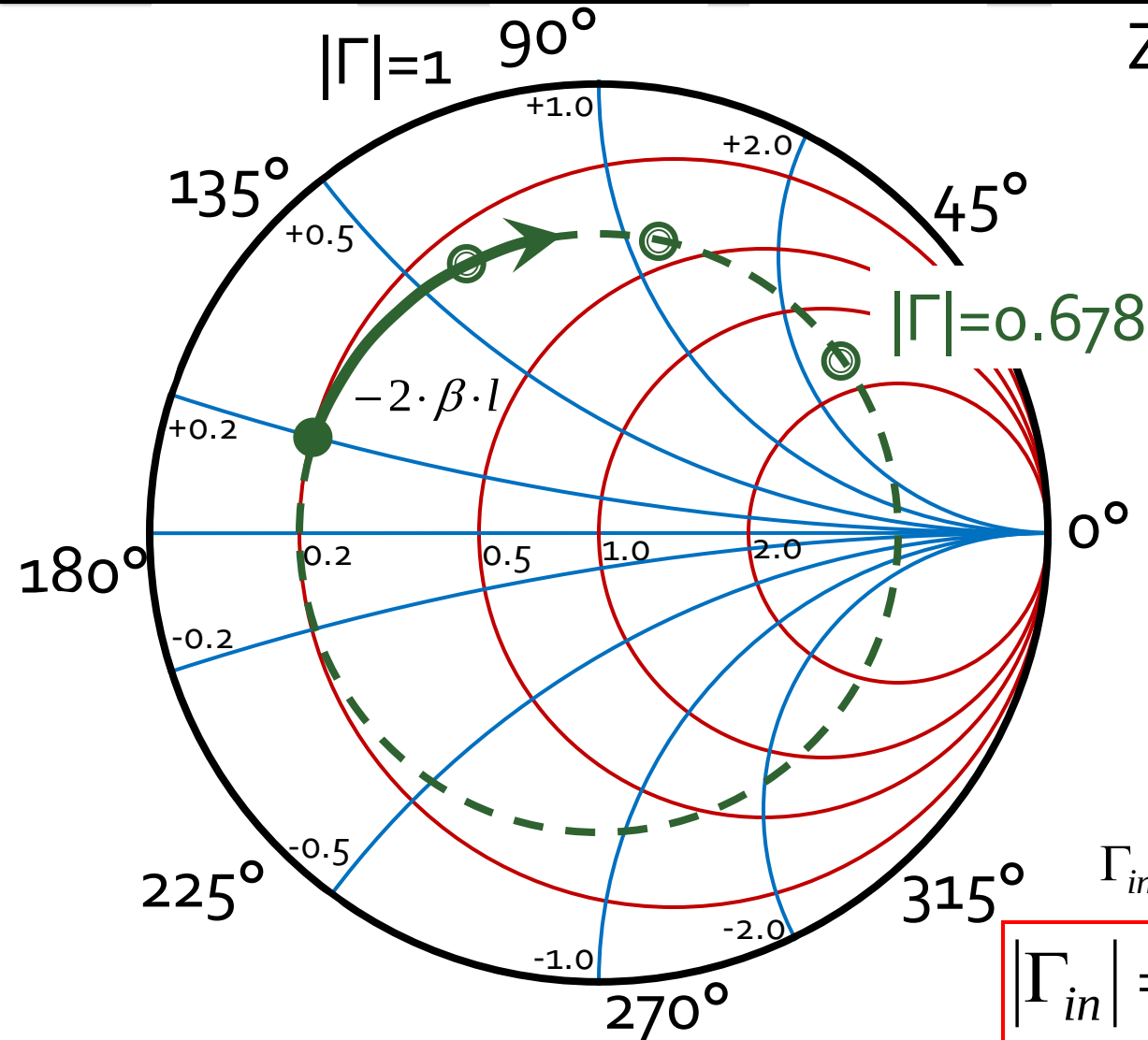
# The Smith Chart, series transmission line, $Z_0$



$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$


$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_0 \cdot \frac{1 + \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}}{1 - \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}}$$


$$\Gamma_{in} = \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}$$

$$|\Gamma_{in}| = |\Gamma_L| \quad \arg(\Gamma_{in}) = \arg(\Gamma_L) - 2 \cdot \beta \cdot l$$

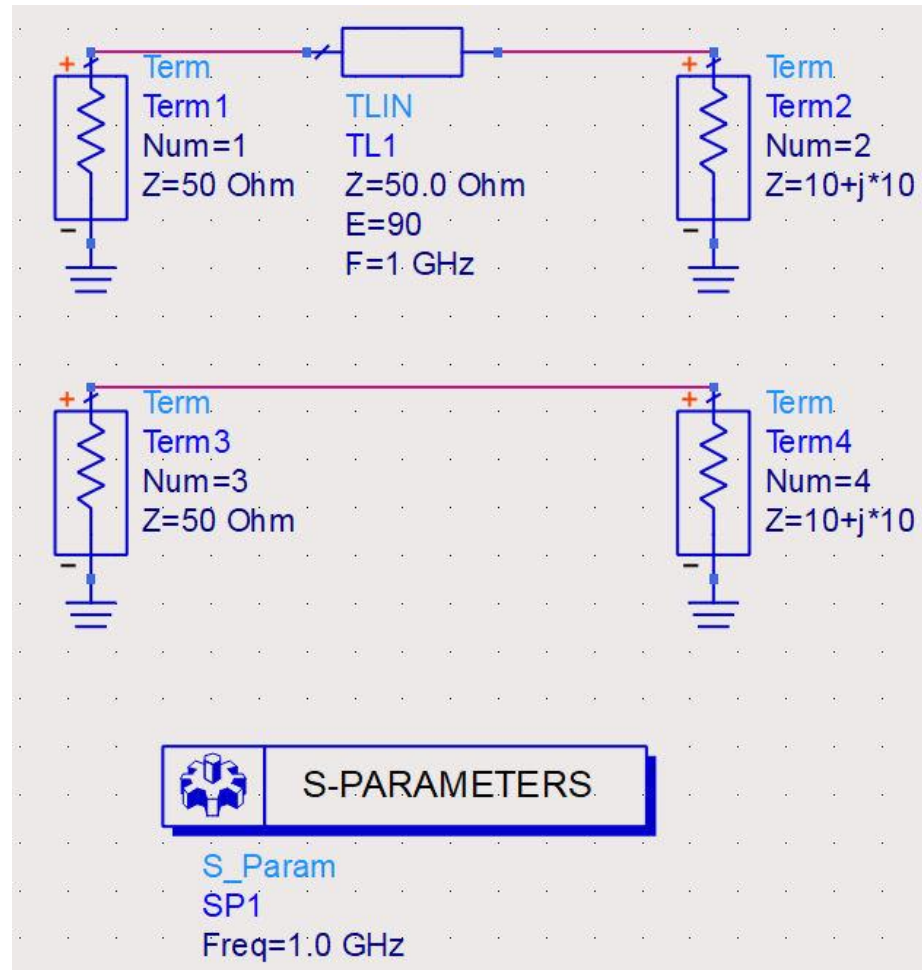
# ADS, Smith Chart, series transmission line



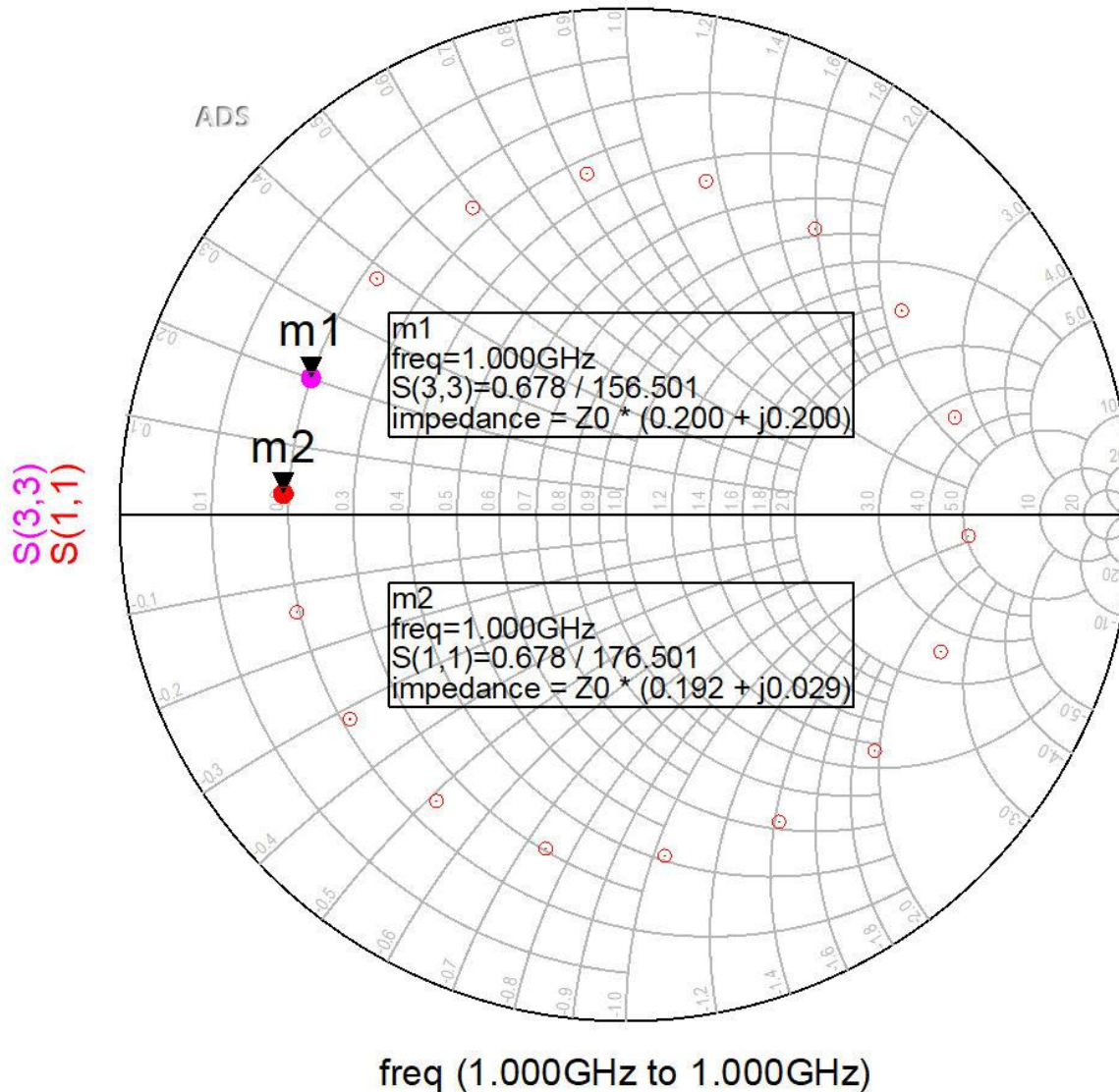
# ADS, Smith Chart, series transmission line



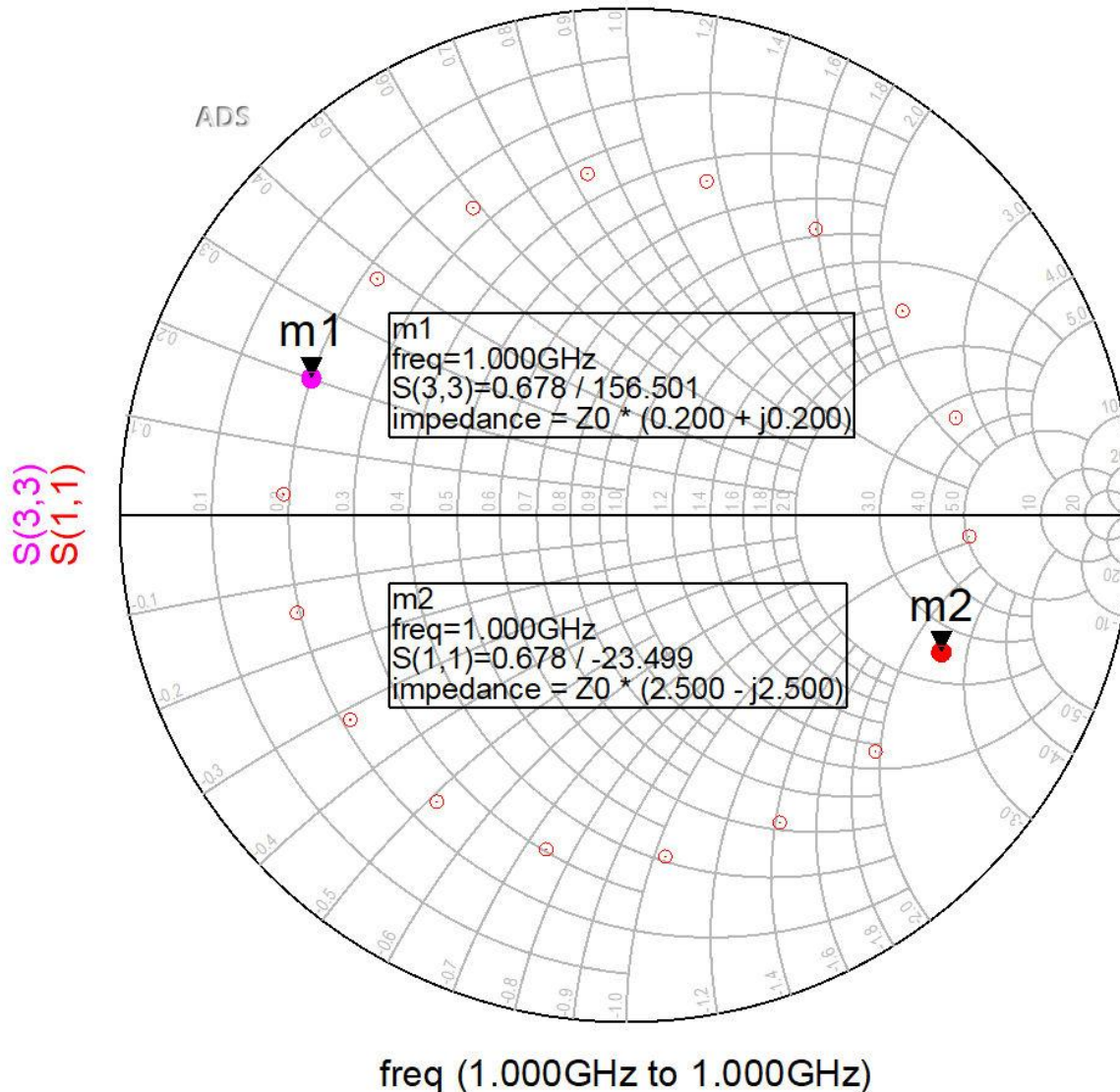
# ADS, Smith Chart, series transmission line, $E=90^\circ$



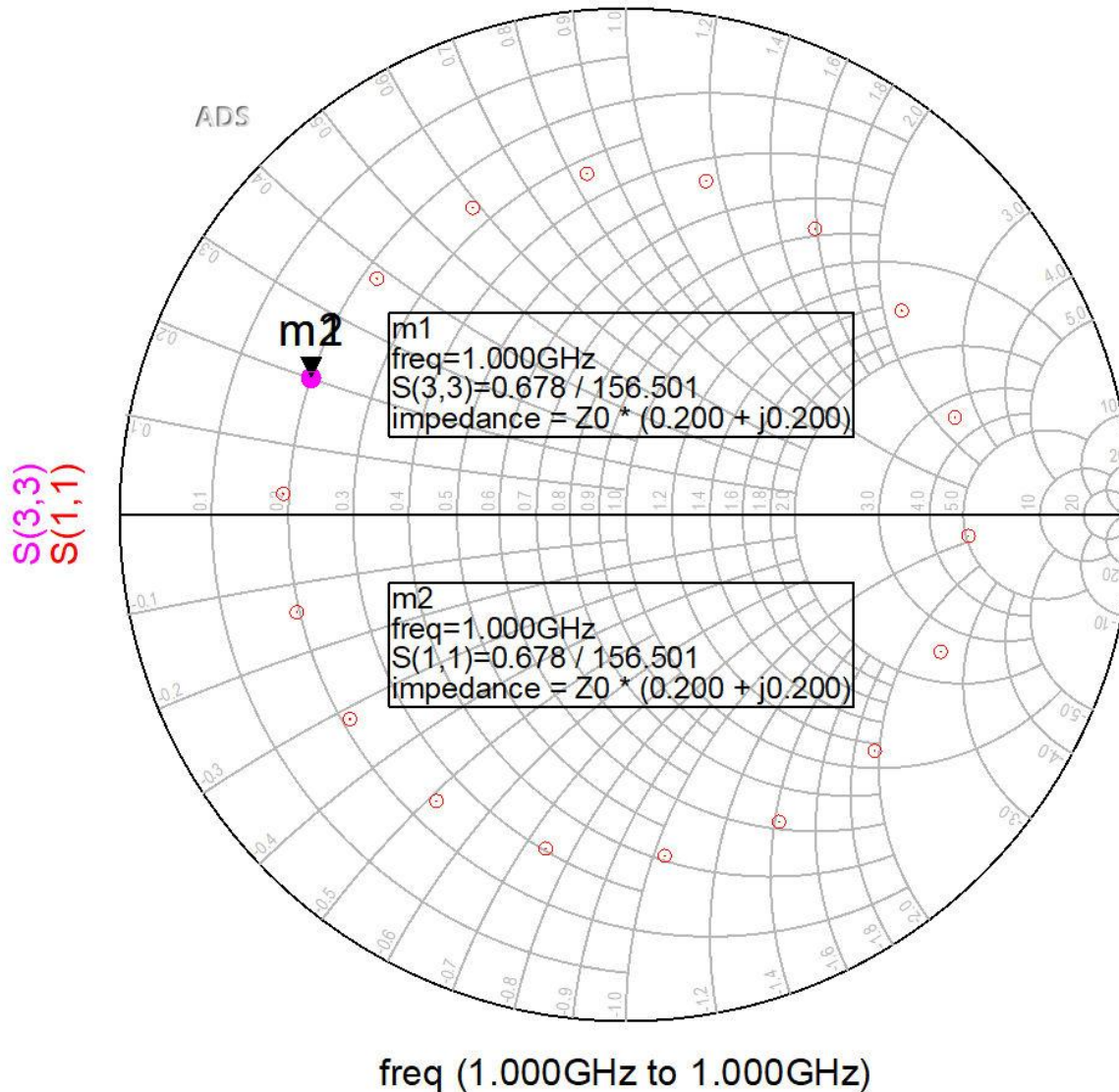
# ADS, Smith Chart, series transmission line, $E=180^\circ$


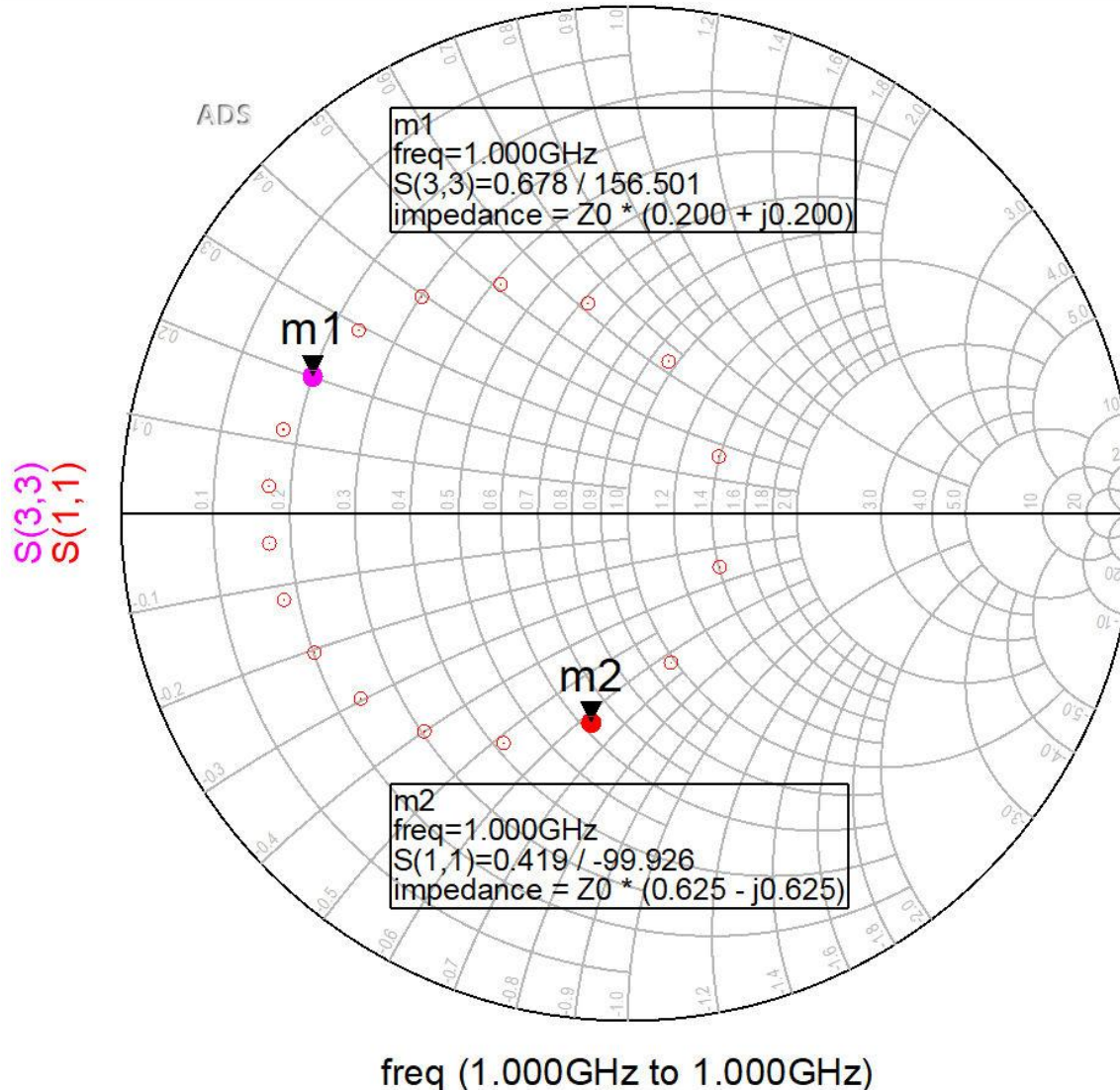
# ADS, Smith Chart, series transmission line, $Z=25\Omega \neq Z_0$



# The Admittance Smith Chart

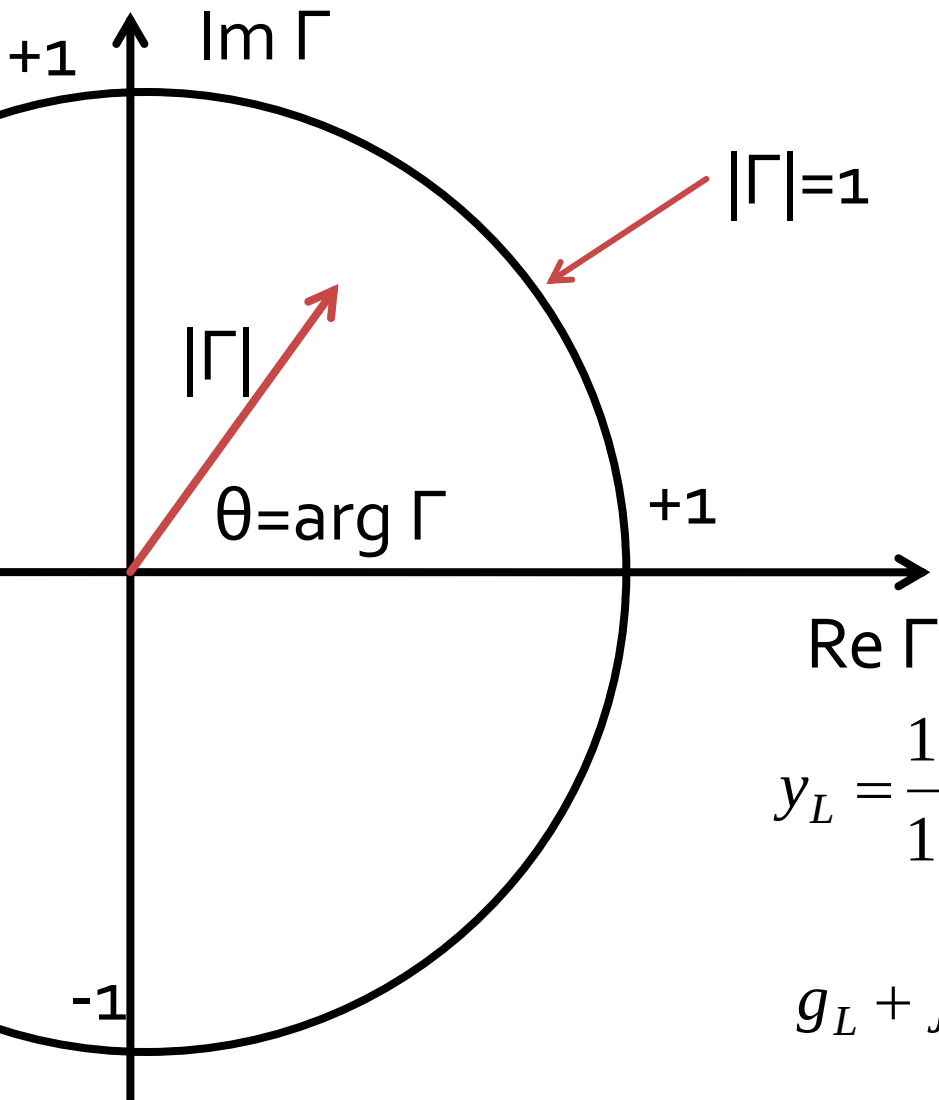

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1} = |\Gamma| \cdot e^{j\theta}$$


$$\Gamma = \Gamma_r + j \cdot \Gamma_i$$

$$z_L = \frac{1 + |\Gamma| \cdot e^{j\theta}}{1 - |\Gamma| \cdot e^{j\theta}} = r_L + j \cdot x_L$$

$$y_L = \frac{1 - |\Gamma| \cdot e^{j\theta}}{1 + |\Gamma| \cdot e^{j\theta}} = \frac{1}{r_L + j \cdot x_L} = g_L + j \cdot b_L$$

$$g_L + j \cdot b_L = \frac{(1 - \Gamma_r) - j \cdot \Gamma_i}{(1 + \Gamma_r) + j \cdot \Gamma_i}$$

# The Admittance Smith Chart

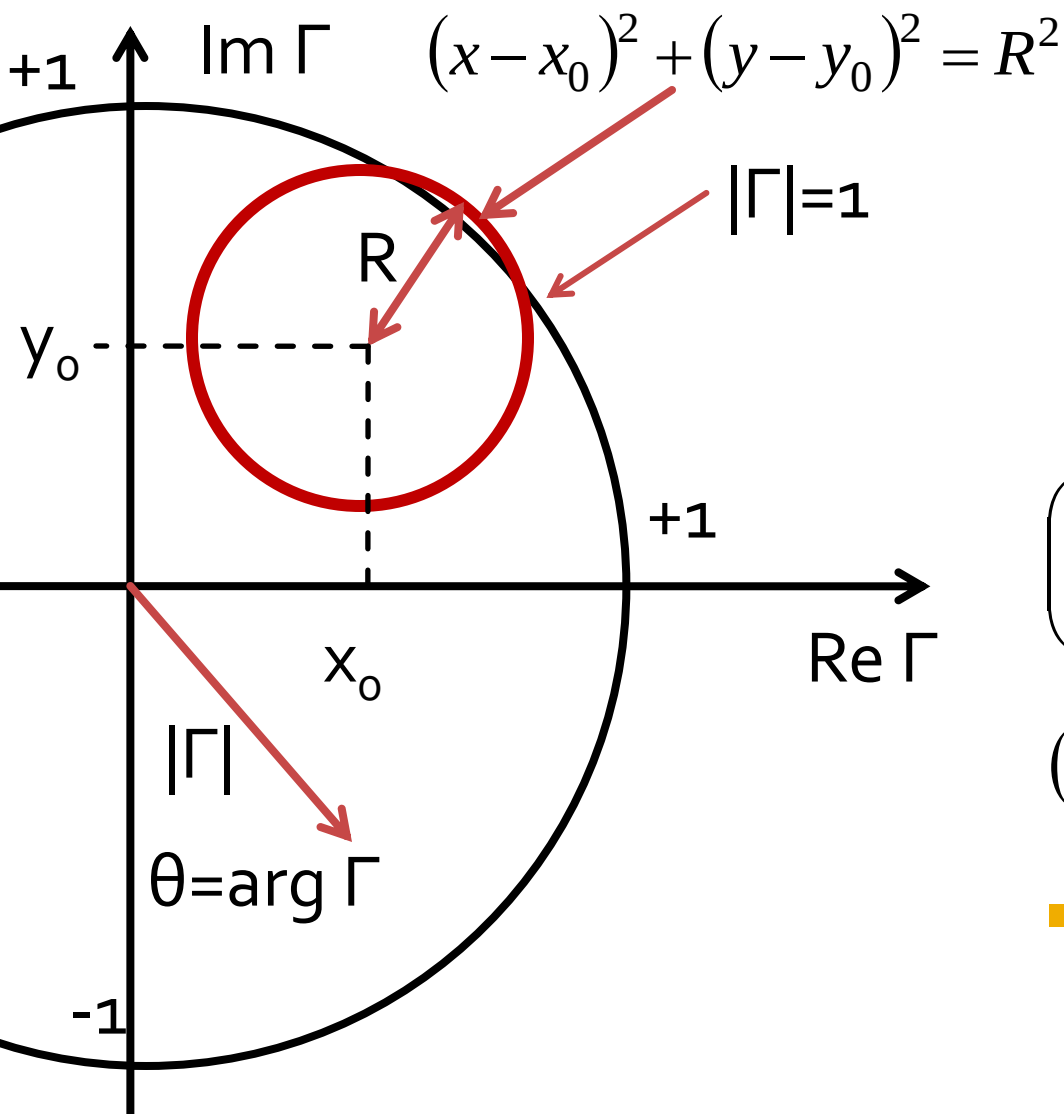

$$g_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 + \Gamma_r)^2 + \Gamma_i^2}$$

$$b_L = \frac{-2 \cdot \Gamma_i}{(1 + \Gamma_r)^2 + \Gamma_i^2}$$

## ■ Rearajate


$$\left( \Gamma_r + \frac{g_L}{1 + g_L} \right)^2 + \Gamma_i^2 = \left( \frac{1}{1 + g_L} \right)^2$$

$$(\Gamma_r + 1)^2 + \left( \Gamma_i + \frac{1}{b_L} \right)^2 = \left( \frac{1}{b_L} \right)^2$$


## ■ Cercuri in planul complex

$$(x - x_0)^2 + (y - y_0)^2 = R^2$$


# The Smith Chart, conductance

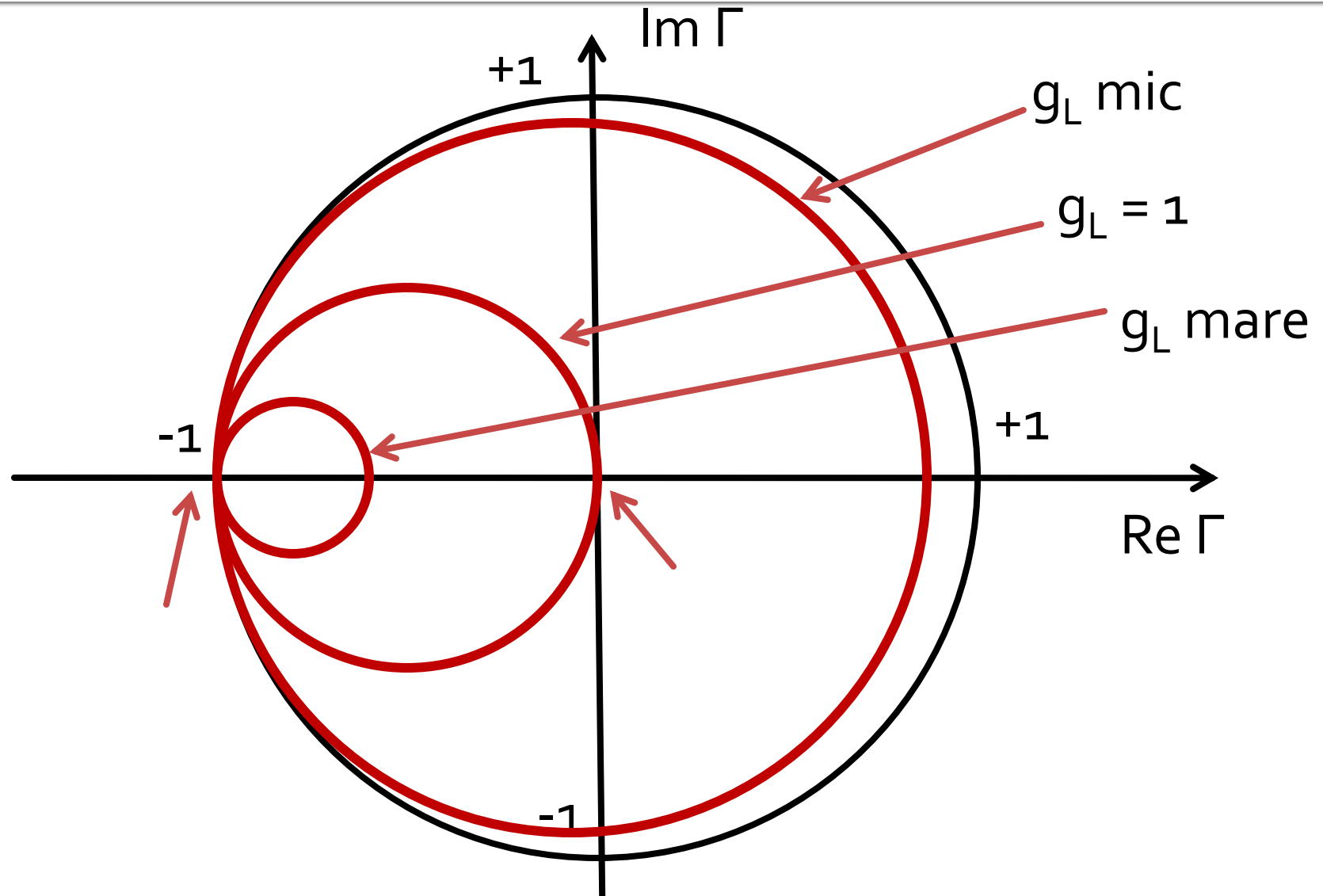



# The Smith Chart, susceptance

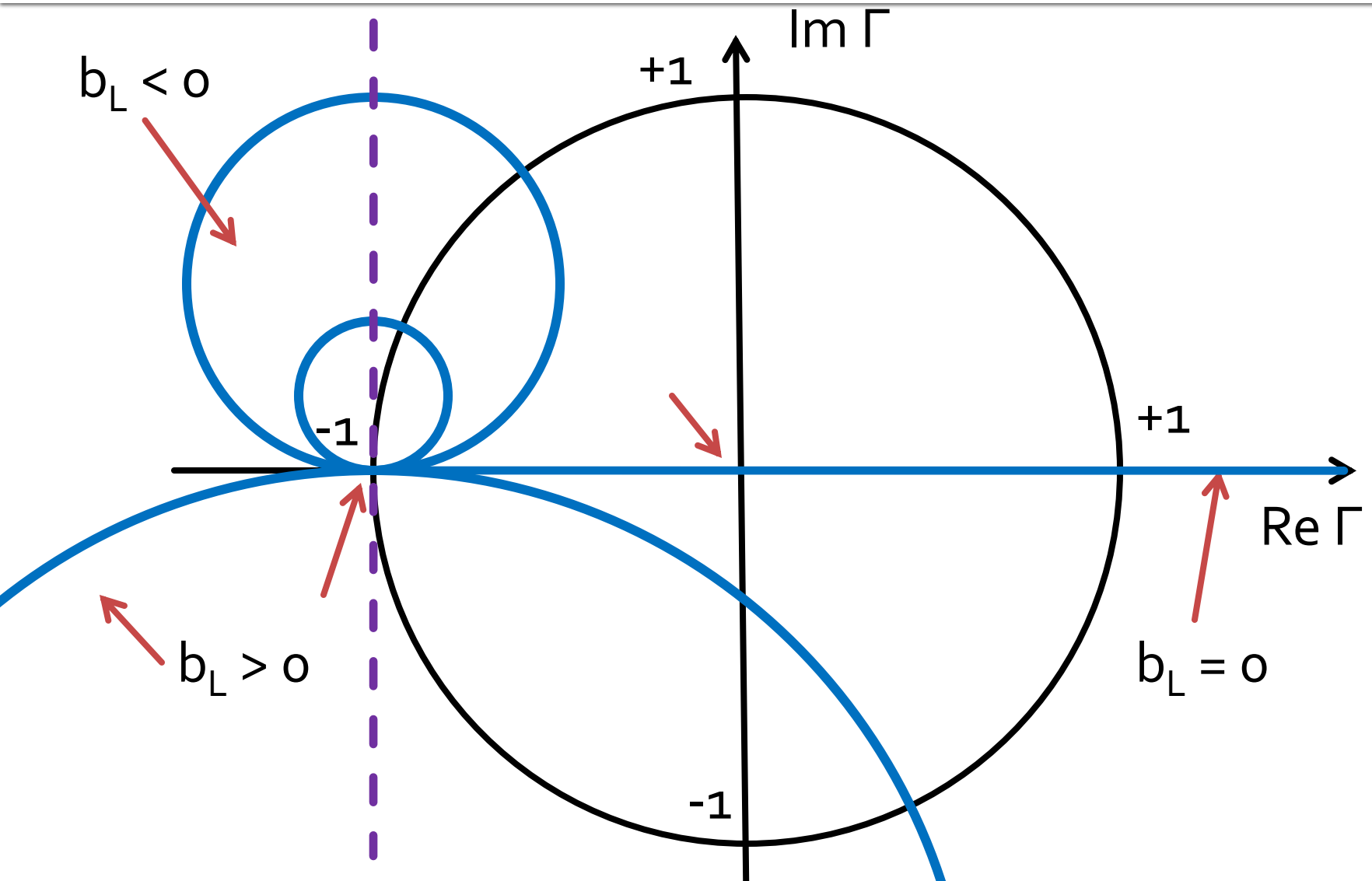
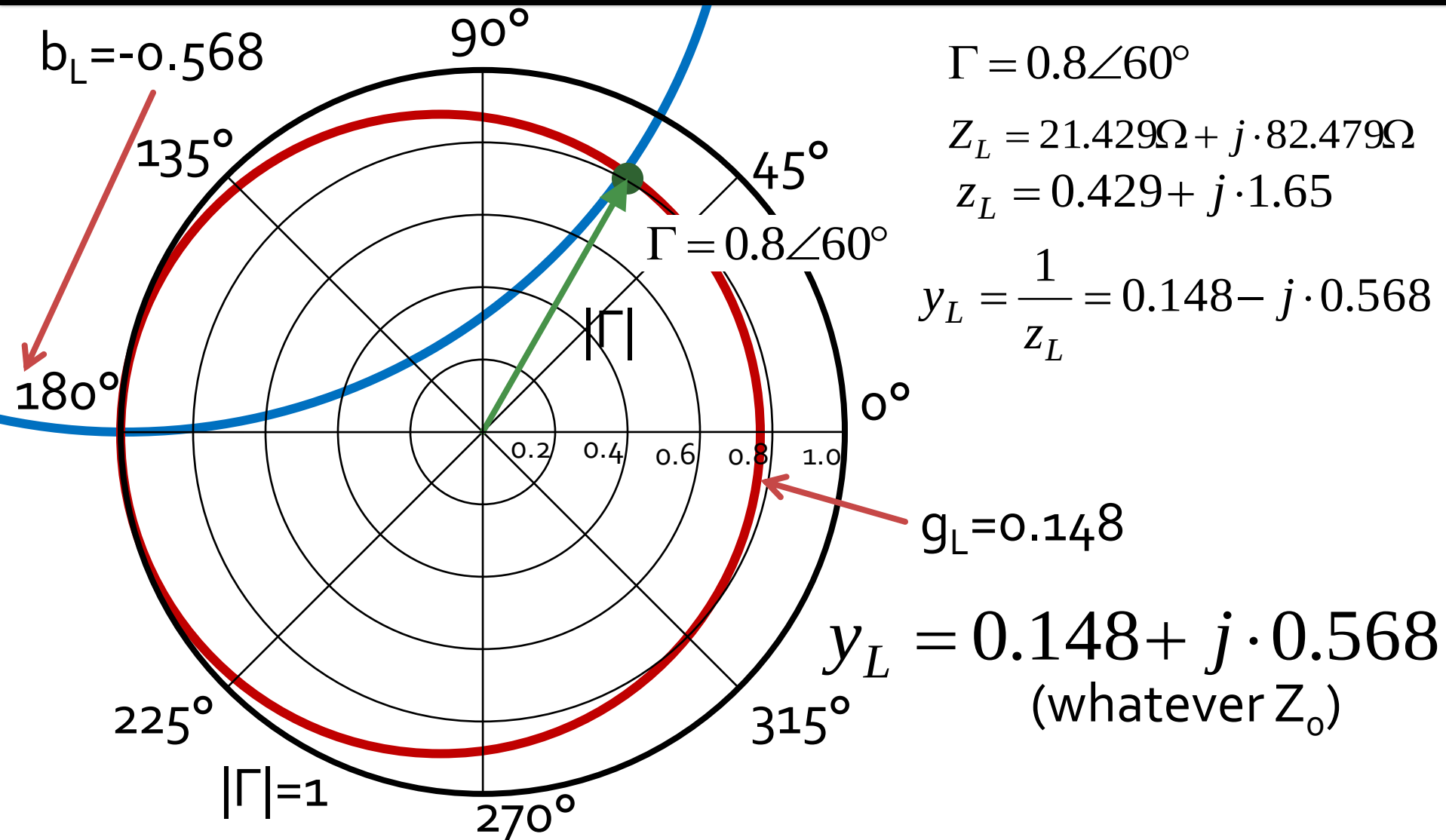
# The Smith Chart, reflection coefficient $\Leftrightarrow$ admittance


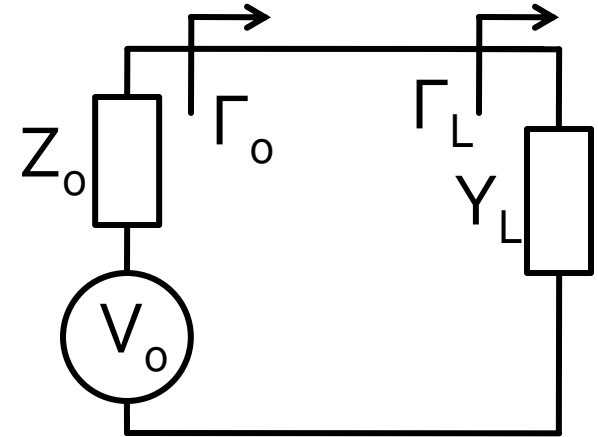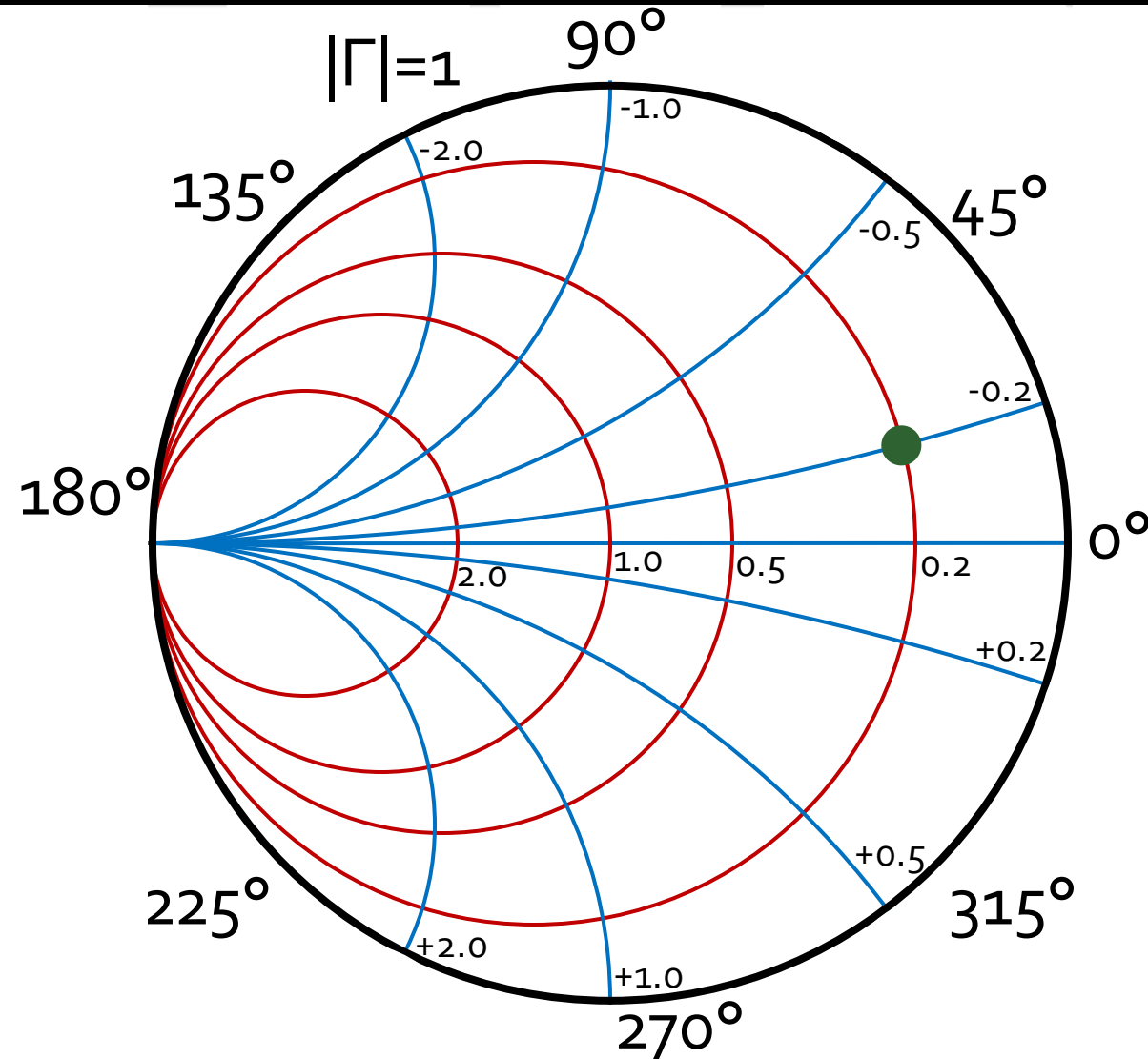
# The Smith Chart, reflection coefficient $\Leftrightarrow$ admittance



$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$Z_L = 125\Omega + j \cdot 125\Omega$$



$$z_L = 2.5 + j \cdot 2.5$$

$$\Gamma_L = \Gamma_0 = 0.678 \angle 23.5^\circ$$

$$Y_L = \frac{1}{Z_L} = 0.004S - j \cdot 0.004S$$

$$y_L = \frac{1}{z_L} = \frac{Y_L}{Y_0} = 0.2 - j \cdot 0.2$$

# The Smith Chart, shunt susceptance

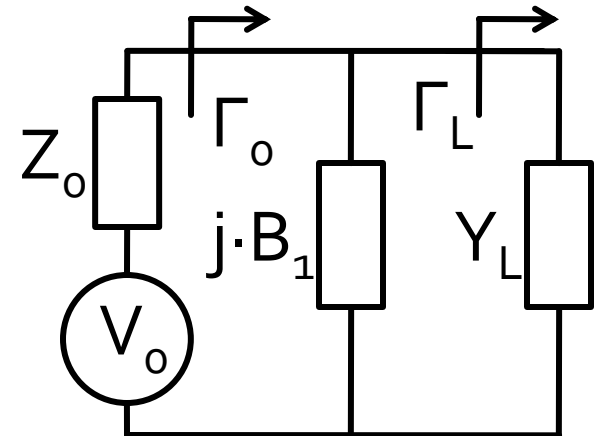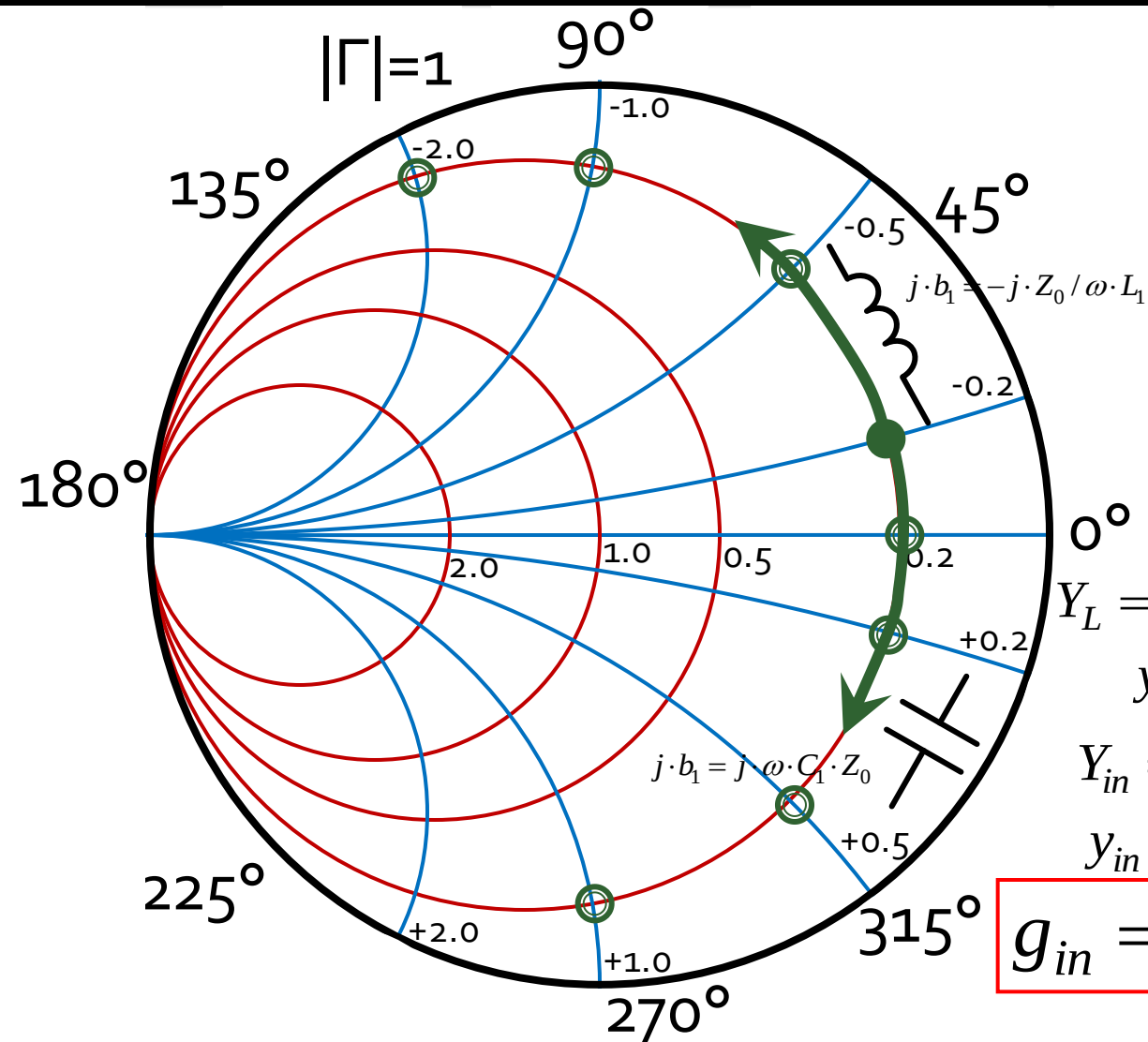

$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$\Gamma_L = 0.678 \angle 23.5^\circ$$

$$Y_L = G_L + j \cdot B_L = 0.004S + j \cdot 0.004$$

$$y_L = g_L + j \cdot b_L = 0.2 - j \cdot 0.2$$

$$Y_{in} = Y_L + j \cdot B_1 = G_L + j \cdot (B_L + B_1)$$



$$y_{in} = g_L + j \cdot (b_L + b_1)$$

$$g_{in} = g_L$$

$$j \cdot b_1 = j \cdot \omega \cdot C_1 \cdot Z_0 > 0$$

$$j \cdot b_1 = -j \cdot Z_0 / \omega \cdot L_1 < 0$$

# ADS, shunt susceptance

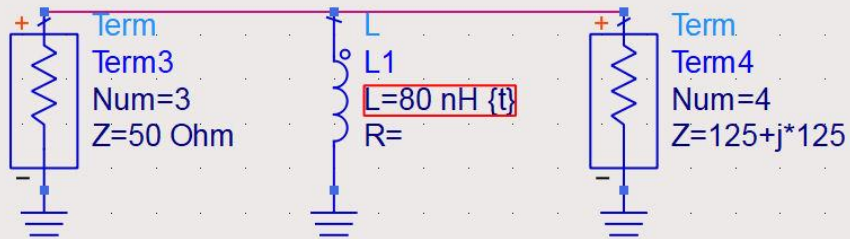
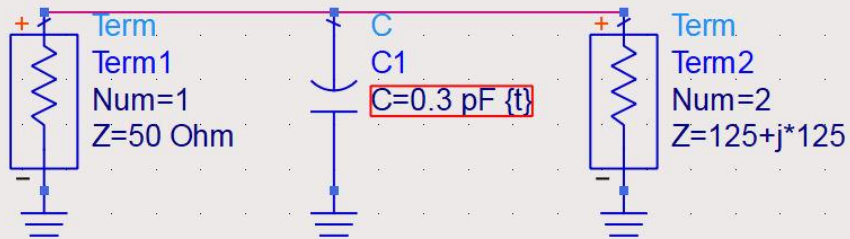


S-PARAMETERS


S\_Param

SP1



Freq=1.0 GHz

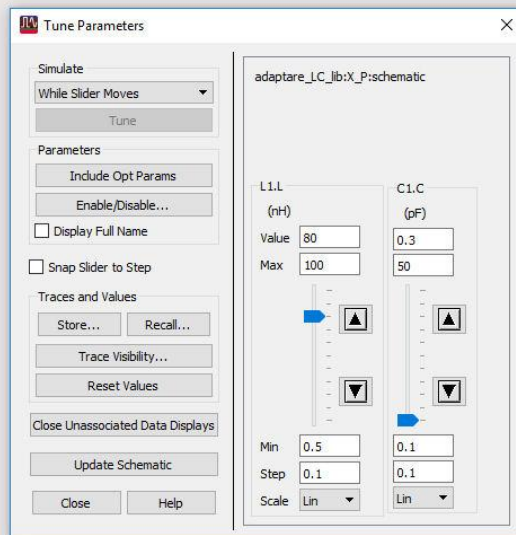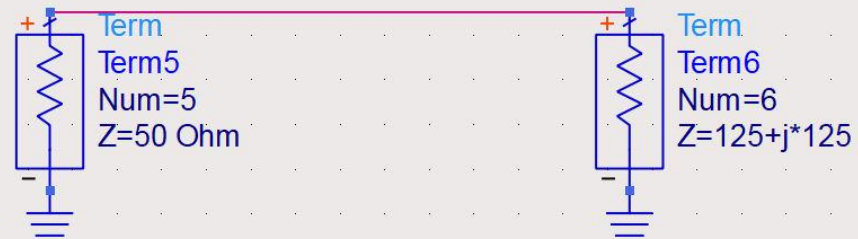

# ADS, shunt susceptance

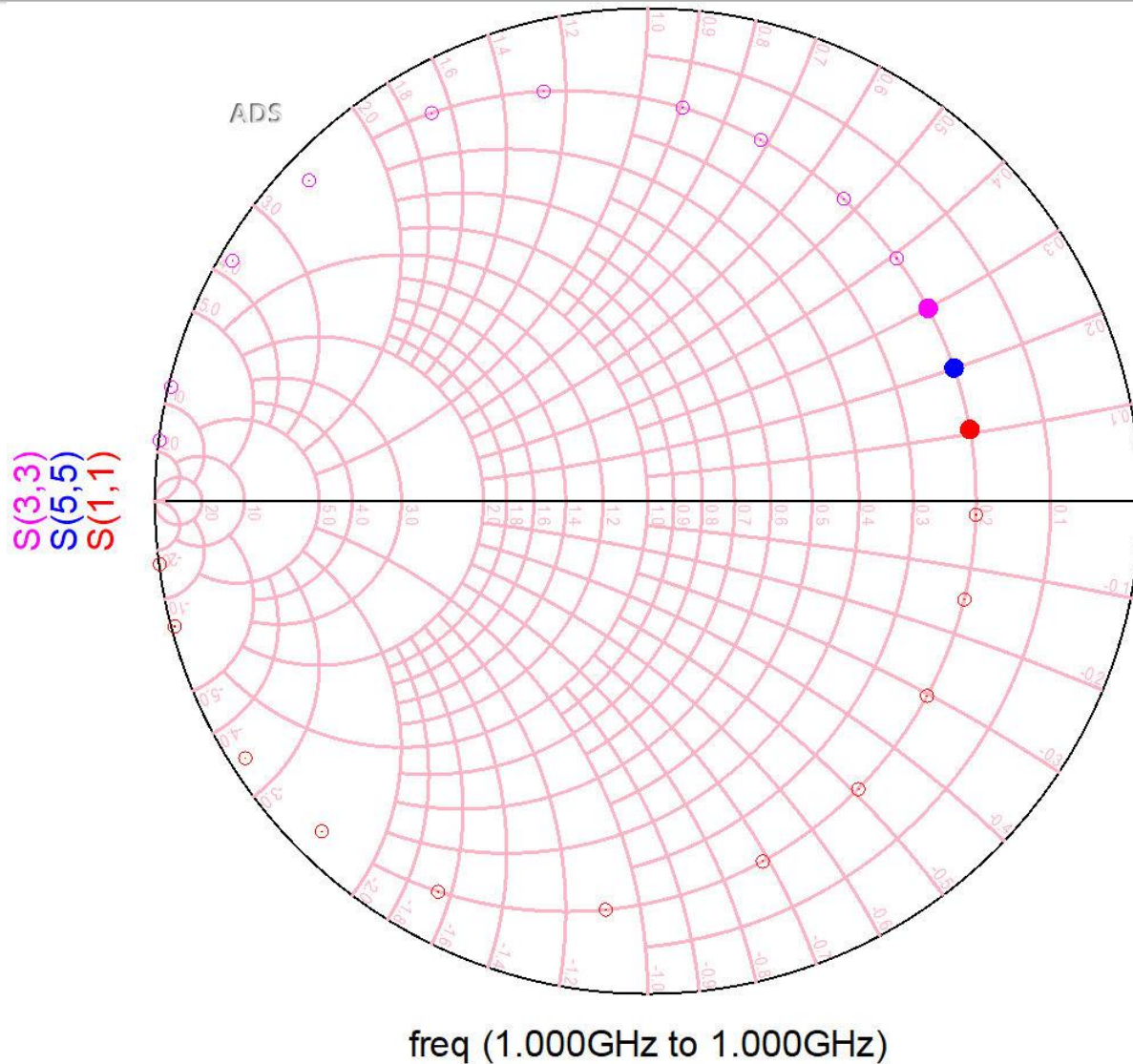

# The Smith Chart, shunt conductance

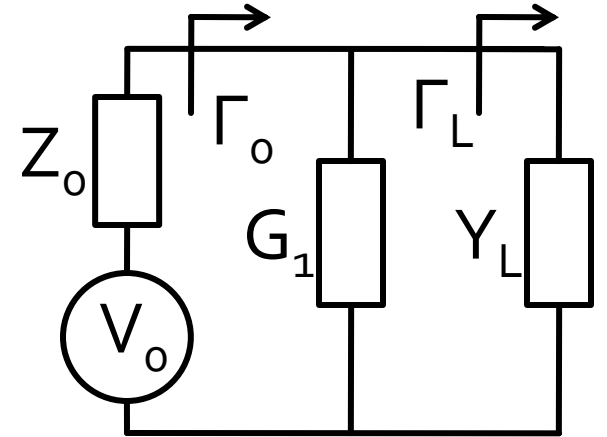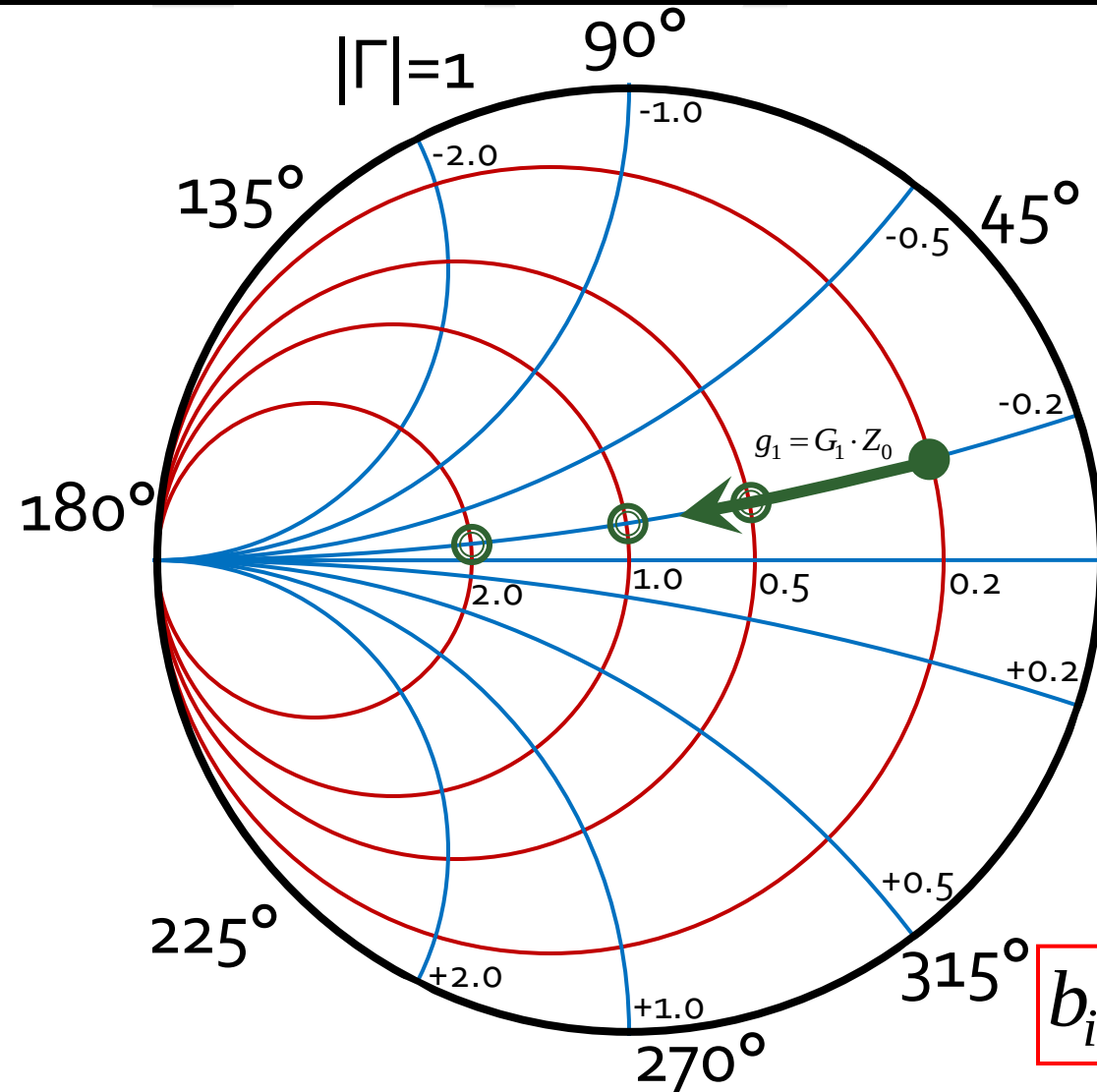

$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$\Gamma_L = 0.678 \angle 23.5^\circ$$

$$Y_L = G_L + j \cdot B_L = 0.004S + j \cdot 0.004S$$

$$y_L = g_L + j \cdot b_L = 0.2 - j \cdot 0.2$$


$$Y_{in} = Y_L + G_1 = (G_L + G_1) + j \cdot B_L$$

$$y_{in} = (g_L + g_1) + j \cdot b_L$$

$$b_{in} = b_L$$

$$g_{in} = g_L + G_1 \cdot Z_0$$


# ADS, shunt conductance

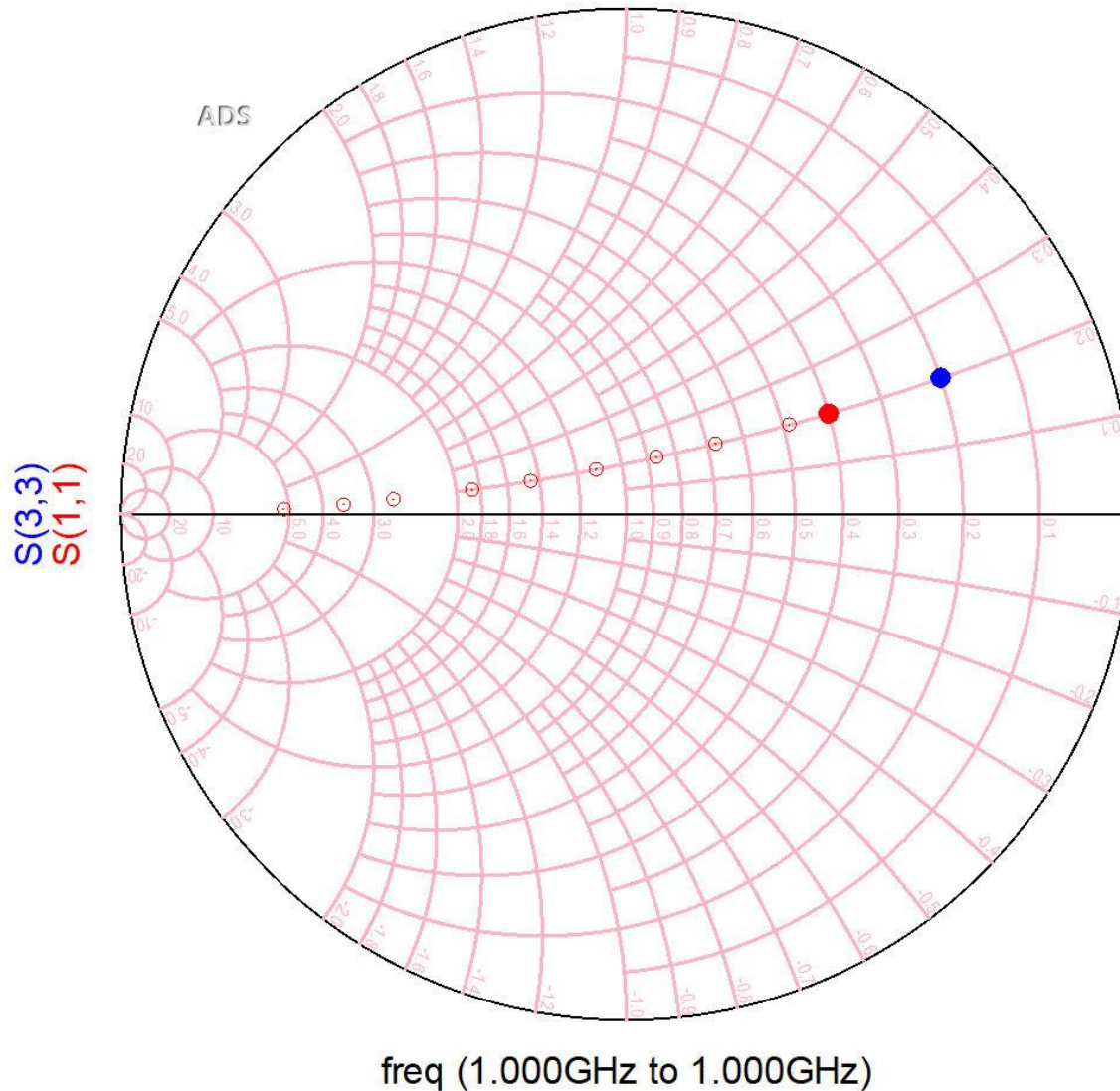

# Constant VSWR circles

- Certain applications may require a certain ratio between maximum / minimum line voltage
- $VSWR = \text{const} \rightarrow \Gamma = \text{const}$



$$VSWR = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

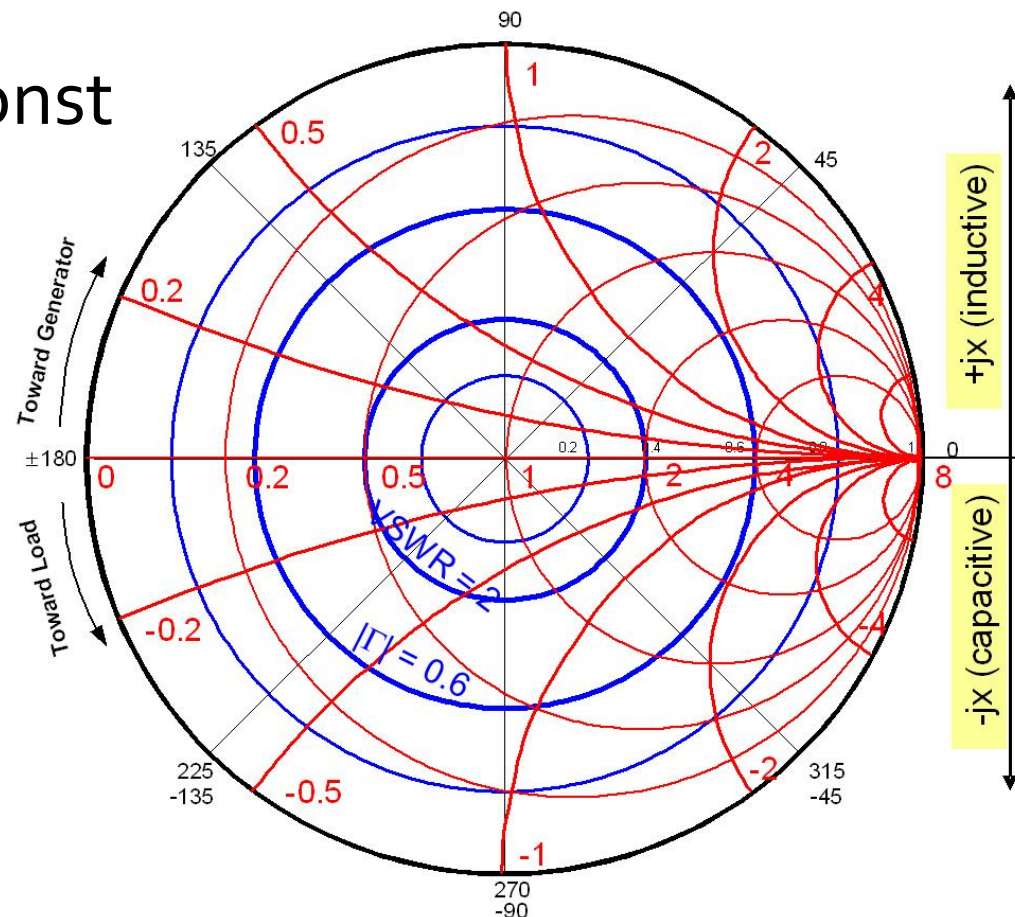
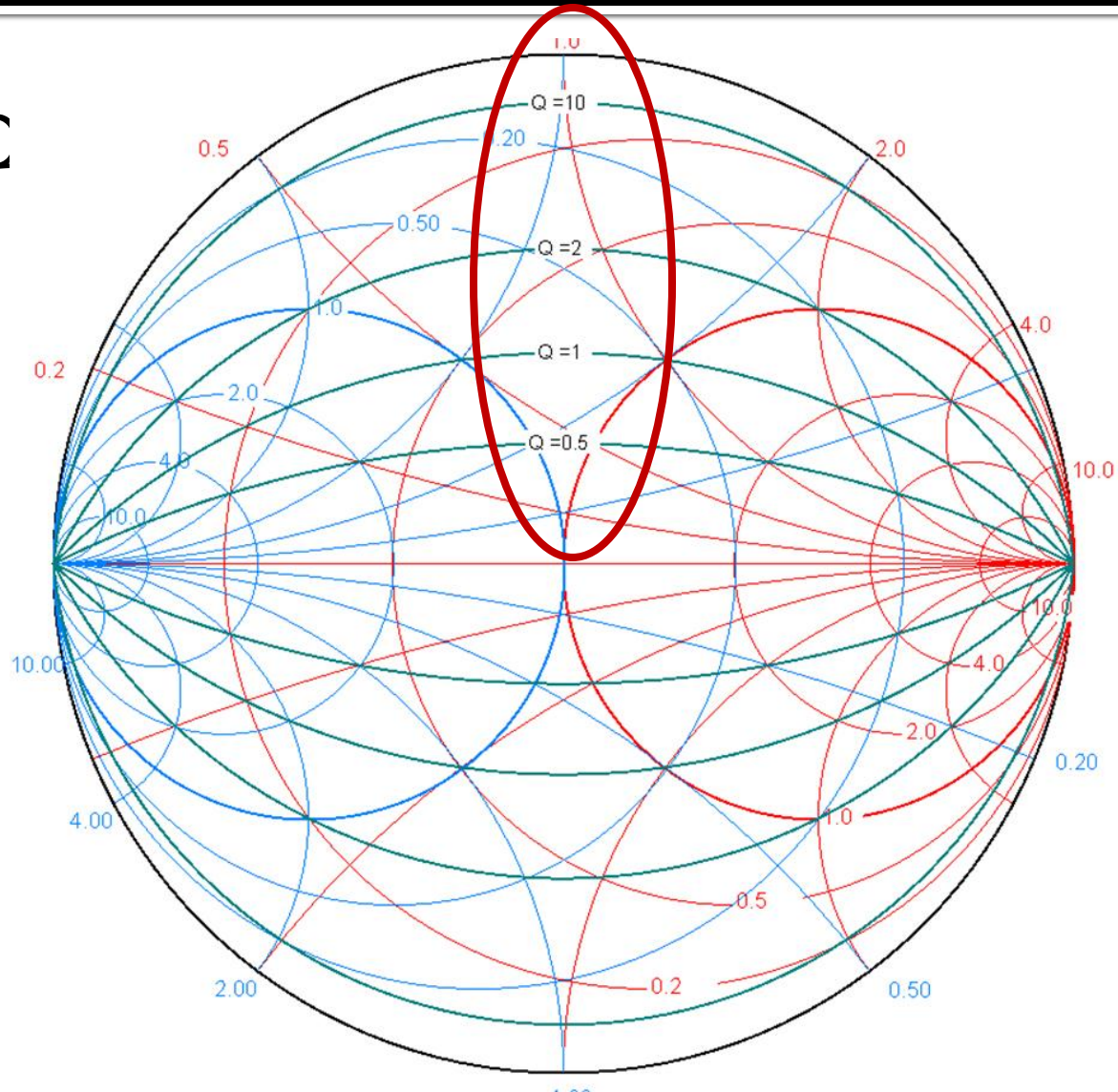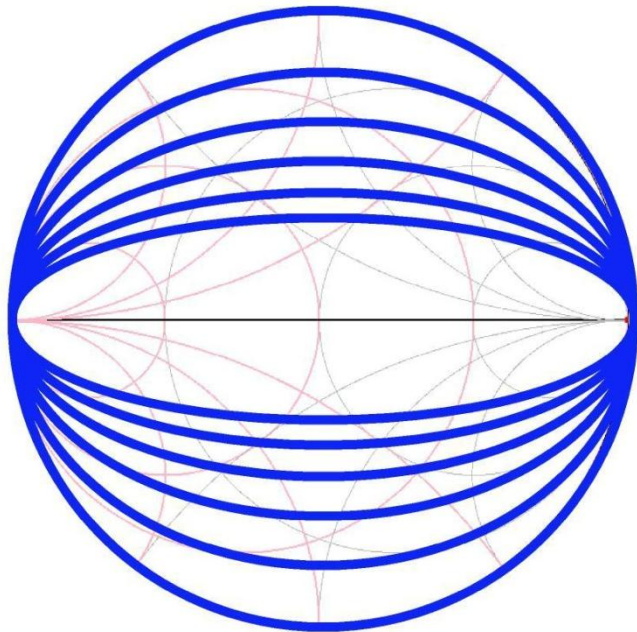
# Constant Q circles

- Quality factor C

$$Q = \frac{X}{R} = \frac{G}{B} = \text{const}$$



# Traditional usage


- transmission line
  - 100Ω impedance
  - 0.3λ length
  - $Z_L = 40\Omega + j \cdot 70\Omega$  load
- normalization with  $Z_0 = 100\Omega$

$$z_L = \frac{Z_L}{Z_0} = 0.4 + j \cdot 0.7$$

- movement with 0.3λ on a line with  $Z_0 = 100\Omega$  (circle)

- from  $z_L$  (0.105λ)
- to  $z_{in}$  (0.405λ)
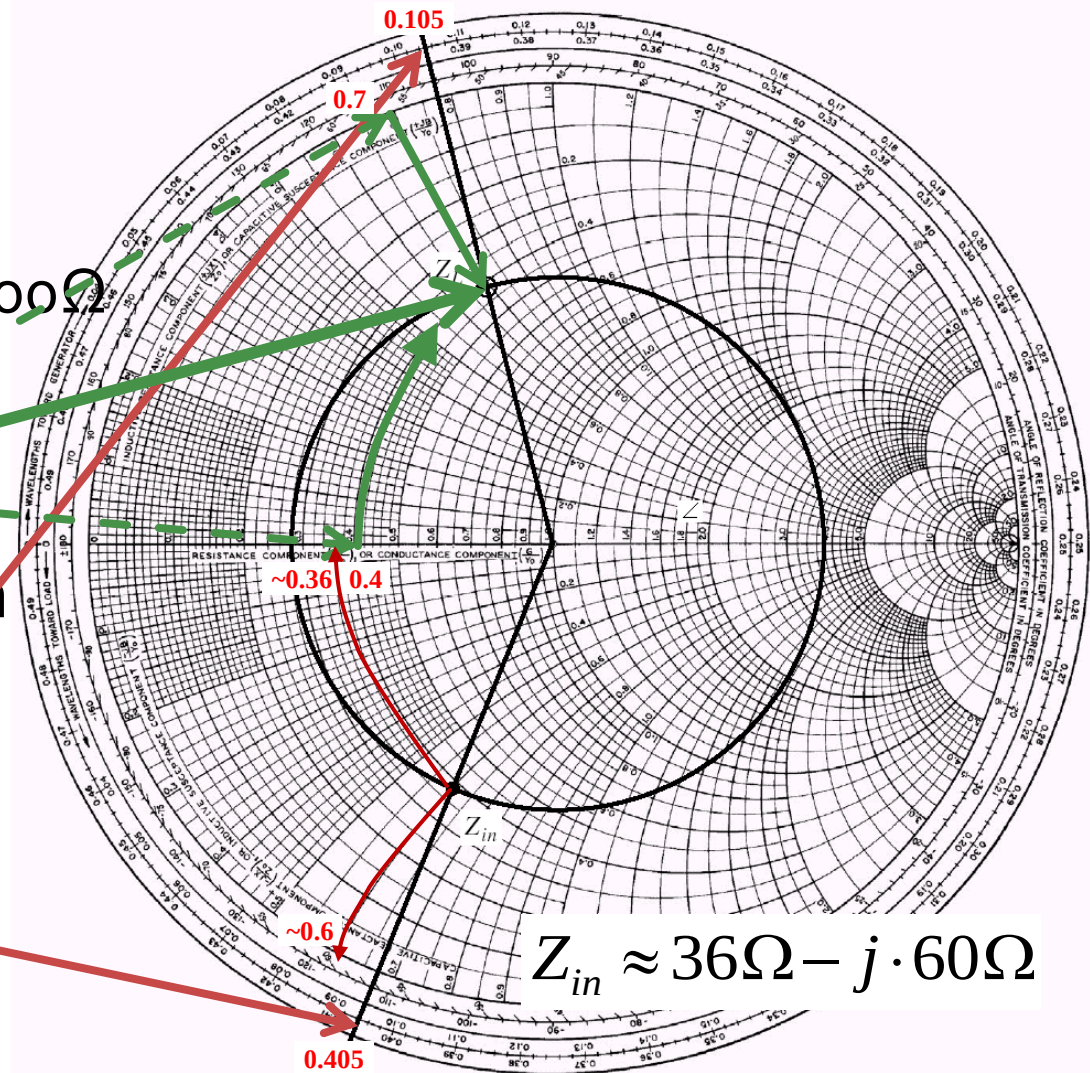
$$z_{in} \approx 0.36 - j \cdot 0.6 = \frac{Z_{in}}{Z_0}$$



# Reflection coefficients

- transmission line
  - 100Ω characteristic impedance
  - 0.3λ length
  - $Z_L = 40\Omega + j \cdot 70\Omega$  load
- $Z_{in} = ?$

$$z_L = \frac{Z_L}{Z_0} = 0.4 + j \cdot 0.7$$

$$\Gamma_L = \frac{z_L - 1}{z_L + 1} = -0.143 + j \cdot 0.571$$


$$\Gamma_{in} = \Gamma_L \cdot e^{-2j \cdot \beta \cdot l} = \Gamma_L \cdot e^{-2j \cdot \frac{2\pi}{\lambda} \cdot 0.3\lambda} = \Gamma_L \cdot e^{-1.2j \cdot \pi}$$

$$\theta = -1.2 \cdot \pi = -216^\circ$$


$$\Gamma_{in} = \Gamma_L \cdot (\cos 216^\circ - j \cdot \sin 216^\circ) = -0.22 - j \cdot 0.546$$

$$z_{in} = \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 0.365 - j \cdot 0.611$$

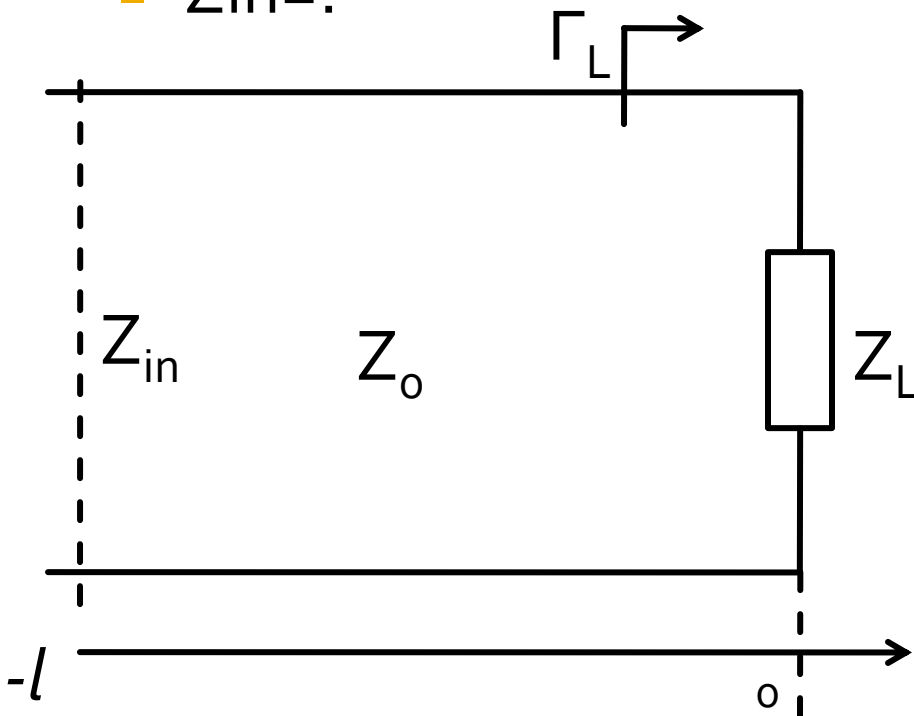
$$Z_{in} = z_{in} \cdot Z_0 = 36.534\Omega - j \cdot 61.119\Omega$$



# Reflection coefficients

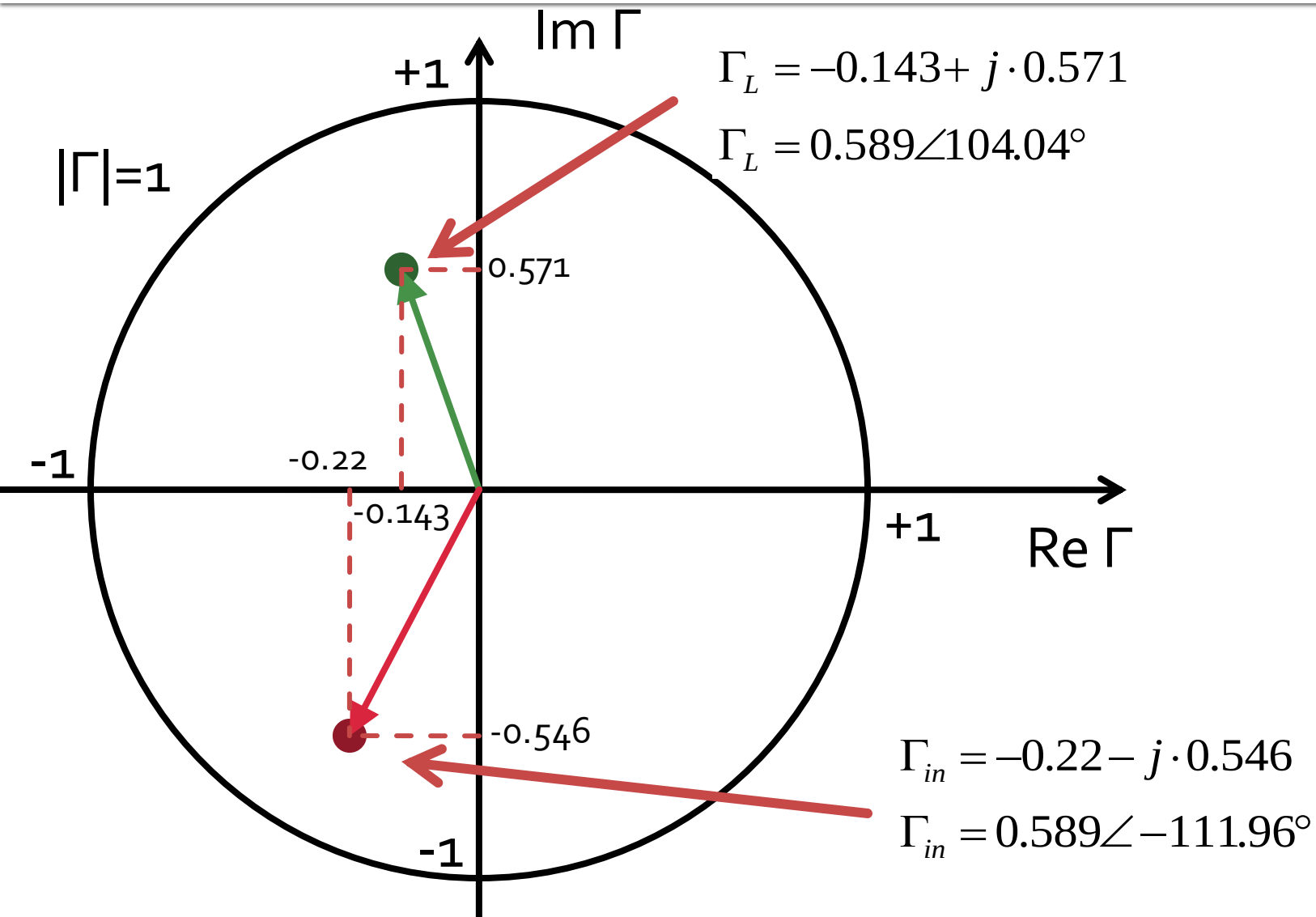

# ADS, simulation

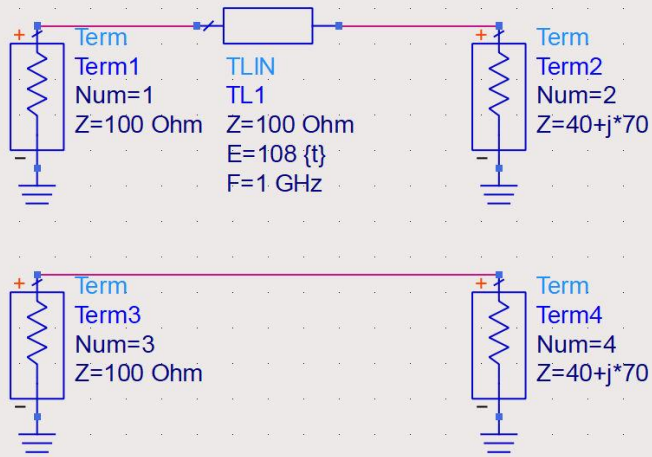


S-PARAMETERS

S\_Param

SP1

Freq=1.0 GHz

$S(3,3)$   
 $S(1,1)$

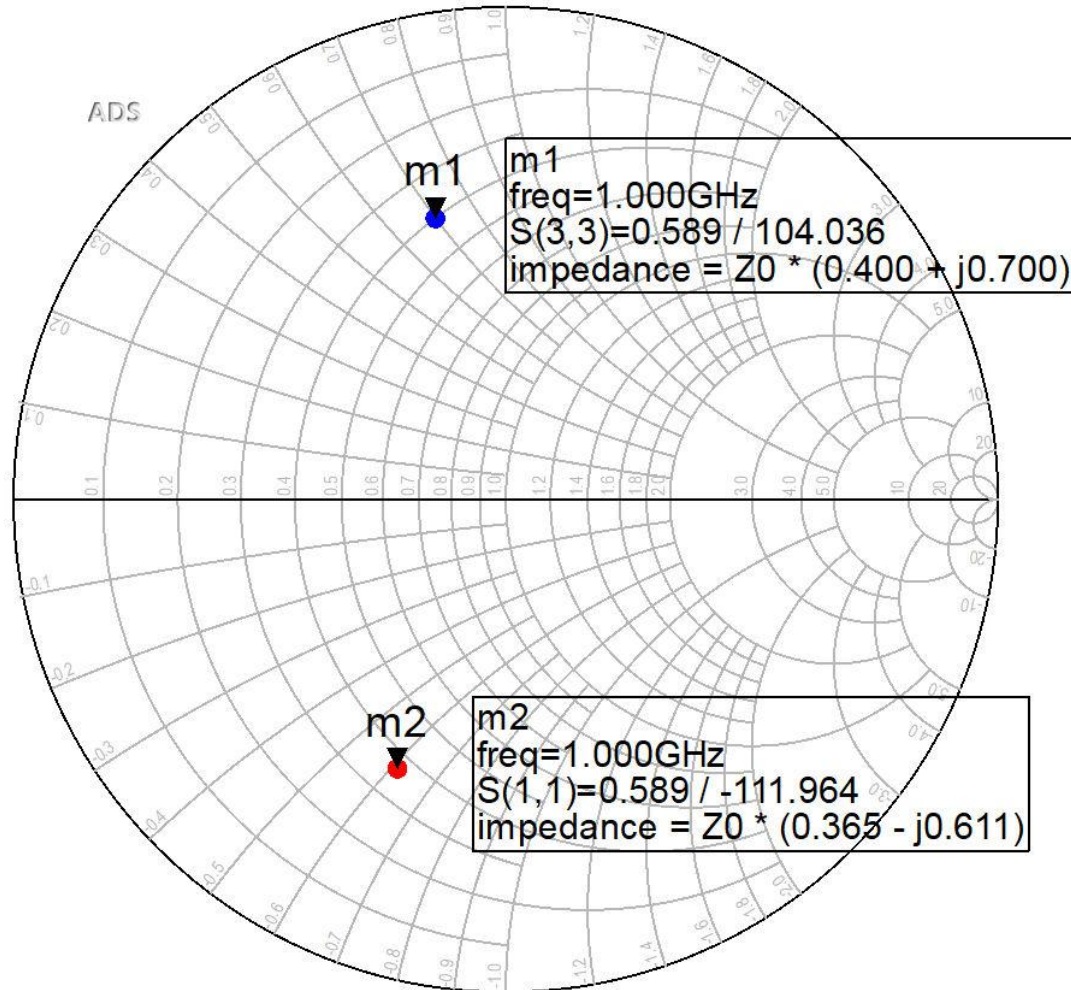

freq (1.000GHz to 1.000GHz)

# Contact

---

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.etti.tuiasi.ro>
- [rdamian@etti.tuiasi.ro](mailto:rdamian@etti.tuiasi.ro)