

Lecture 5
2018/2019

Microwave Devices and Circuits for Radiocommunications

2018/2019

- 2C/1L, **MDCR**
- Attendance at minimum 7 sessions (course + laboratory)
- Lectures- **associate professor Radu Damian**
 - Friday 09-11, II.13
 - E – 50% final grade
 - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
 - 3p=+0.5p
 - all materials/equipments authorized
- Laboratory – **associate professor Radu Damian**
 - Wednesday 12-14, II.12 odd weeks
 - L – 25% final grade
 - P – 25% final grade

Materials

■ <http://rf-opto.eti.tuiasi.ro>

Laboratorul de Microunde și Optică

Not secure | rf-opto.eti.tuiasi.ro/microwave_cd.php?chg_lang=0

Main Courses Master Staff Research Students Admin

Microwave CD Optical Communications Optoelectronics Internet Antennas Practica Networks Educational software

Microwave Devices and Circuits for Radiocommunications (English)

Course: MDCR (2017-2018)

Course Coordinator: Assoc.P. Dr. Radu-Florin Damian
Code: EDOS412T
Discipline Type: DOS; Alternative, Specialty
Credits: 4
Enrollment Year: 4, Sem. 7

Activities

Course: Instructor: Assoc.P. Dr. Radu-Florin Damian, 2 Hours/Week, Specialization Section, Timetable:
Laboratory: Instructor: Assoc.P. Dr. Radu-Florin Damian, 1 Hours/Week, Group, Timetable:

Evaluation

Type: Examen

A: 50%, (Test/Colloquium)
B: 25%, (Seminary/Laboratory/Project Activity)
D: 25%, (Homework/Specialty papers)

Grades

[Aggregate Results](#)

Attendance

[Course](#)
[Laboratory](#)

Lists

[Bonus-uri acumulate \(final\)](#)
[Studenti care nu pot intra in examen](#)

Materials

Course Slides

[MDCR Lecture_1 \(pdf, 5.43 MB, en,](#)
[MDCR Lecture_2 \(pdf, 3.67 MB, en,](#)
[MDCR Lecture_3 \(pdf, 4.76 MB, en,](#)
[MDCR Lecture_4 \(pdf, 5.58 MB, en,](#)

Photos

Grupa 5403											
Nr.	Student	Prezent		Nr.	Student	Prezent		Nr.	Student	Prezent	
1	ANGHELUS IONUT-MARCUS		<input type="checkbox"/> Prezent	2	ANTIGHIN FLORIN-RAZVAN		Fotografia nu există	3	ANTONICA BIANCA		Fotografia nu există
4	APOSTOL PAVEL-MANUEL		Fotografia nu există	5	BALASCA TUDIAN-PETRU		Fotografia nu există	6	BOSTAN ANDREI-PETRICA		Fotografia nu există
7	BOTEZAT EMANUEL		<input type="checkbox"/> Prezent	8	BUTUNOI GEORGE-MADALIN		Fotografia nu există	9	CHILEA SALUCA-MARIA		Fotografia nu există
10	CHRITOIU CATERINA		<input type="checkbox"/> Prezent	11	CODOC MARIUS		<input checked="" type="checkbox"/> Prezent	12	COJOCARU AURA-FLORINA		<input type="checkbox"/> Prezent

Nr. Student

2 ANTIGHIN
FLORIN-RAZVAN

Prezent

Prezent

Puncte:

0

Nota:

0

Obs:

Fotografia nu există

Access

- Not customized

A screenshot of a student profile page. On the left is a thumbnail photo of a student. Below it is a link "Acceseaza ca acest student". To the right is a table with student details:

Grupa	5304 (2015/2016)
Specializarea	Tehnologii si sisteme de telecomunicatii
Marca	5184

Below the table is a section titled "Note obtinute" with a table:

Disciplina	Tip	Data	Descriere	Nota	Puncte	Obs.
TW	Tehnologii Web					
	N	17/01/2014	Nota finala	10	-	
	A	17/01/2014	Colocviu Tehnologii Web 2013/2014	10	7.55	
	B	17/01/2014	Laborator Tehnologii Web 2013/2014	9	-	
	D	17/01/2014	Tema Tehnologii Web 2013/2014	9	-	

A screenshot of a contact form. It includes fields for "Nume" (Name) with a redacted value, "Email" (Email), and "Cod de verificare" (Verification code) with a redacted value. At the bottom is a large blue button containing the verification code "344bd9f".

Trimite

Examen: Logarithmic scales

$$\text{dB} = 10 \cdot \log_{10} (P_2 / P_1)$$

$$0 \text{ dB} = 1$$

$$+0.1 \text{ dB} = 1.023 (+2.3\%)$$

$$+3 \text{ dB} = 2$$

$$+5 \text{ dB} = 3$$

$$+10 \text{ dB} = 10$$

$$-3 \text{ dB} = 0.5$$

$$-10 \text{ dB} = 0.1$$

$$-20 \text{ dB} = 0.01$$

$$-30 \text{ dB} = 0.001$$

$$\text{dBm} = 10 \cdot \log_{10} (P / 1 \text{ mW})$$

$$0 \text{ dBm} = 1 \text{ mW}$$

$$3 \text{ dBm} = 2 \text{ mW}$$

$$5 \text{ dBm} = 3 \text{ mW}$$

$$10 \text{ dBm} = 10 \text{ mW}$$

$$20 \text{ dBm} = 100 \text{ mW}$$

$$-3 \text{ dBm} = 0.5 \text{ mW}$$

$$-10 \text{ dBm} = 100 \mu\text{W}$$

$$-20 \text{ dBm} = 1 \mu\text{W}$$

$$-30 \text{ dBm} = 1 \text{ nW}$$

$$[\text{dBm}] + [\text{dB}] = [\text{dBm}]$$

$$[\text{dBm}/\text{Hz}] + [\text{dB}] = [\text{dBm}/\text{Hz}]$$

$$[x] + [\text{dB}] = [x]$$


Examen

- Complex numbers arithmetic!!!!
- $z = a + j \cdot b ; j^2 = -1$

TEM transmission lines

Transmission line equivalent model

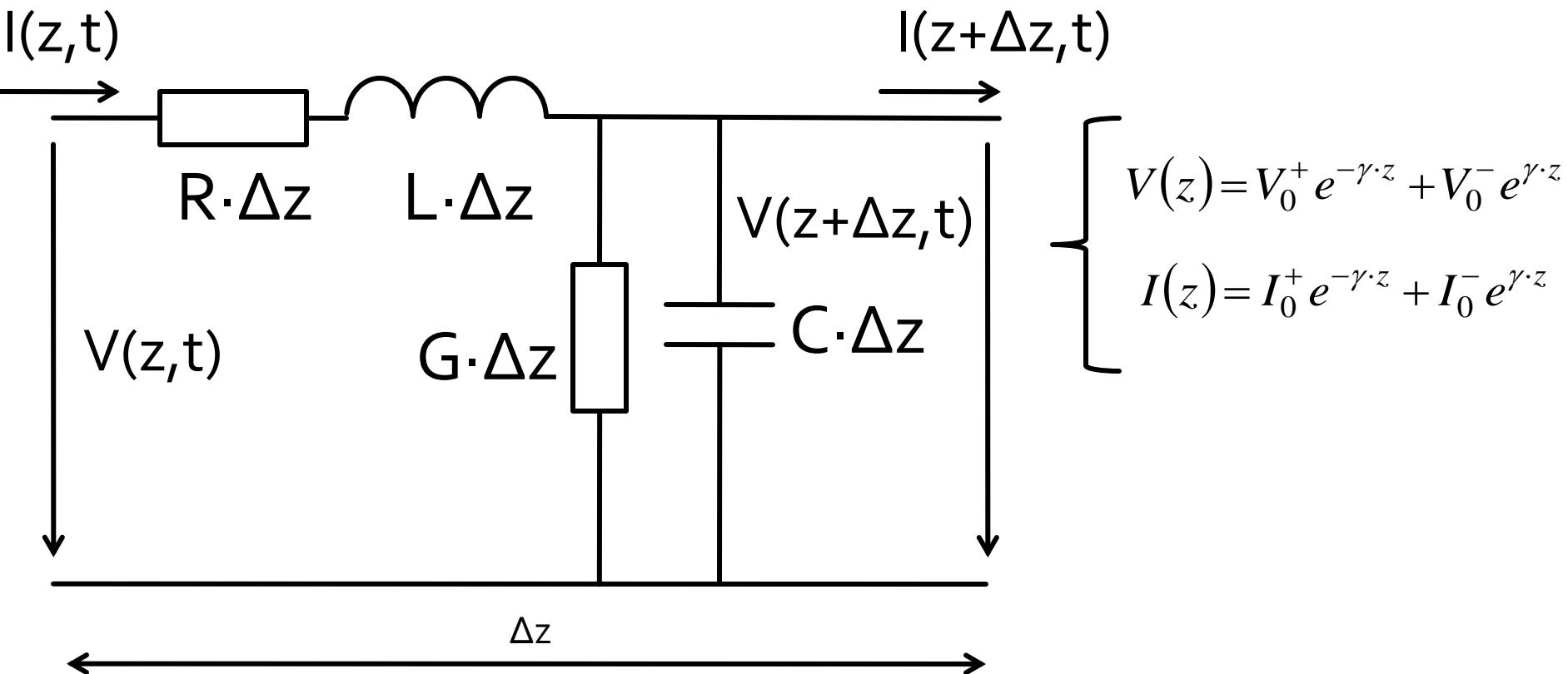- TEM wave propagation, at least two conductors



The lossless line

$$V(z) = V_0^+ \cdot (e^{-j\beta z} + \Gamma \cdot e^{j\beta z})$$

$$I(z) = \frac{V_0^+}{Z_0} \cdot (e^{-j\beta z} - \Gamma \cdot e^{j\beta z})$$

- time-average Power flow along the line


$$P_{avg} = \frac{1}{2} \cdot \text{Re}\{V(z) \cdot I(z)^*\} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot \text{Re}\left\{1 - \Gamma^* \cdot e^{-2j\beta z} + \Gamma \cdot e^{2j\beta z} - |\Gamma|^2\right\}$$
$$P_{avg} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot \left(1 - |\Gamma|^2\right)$$

$(z - z^*) = \text{Im}$

- Total power delivered to the load = Incident power – “Reflected” power
- Return “Loss” [dB]
$$\text{RL} = -20 \cdot \log|\Gamma| \quad [\text{dB}]$$

The lossless line

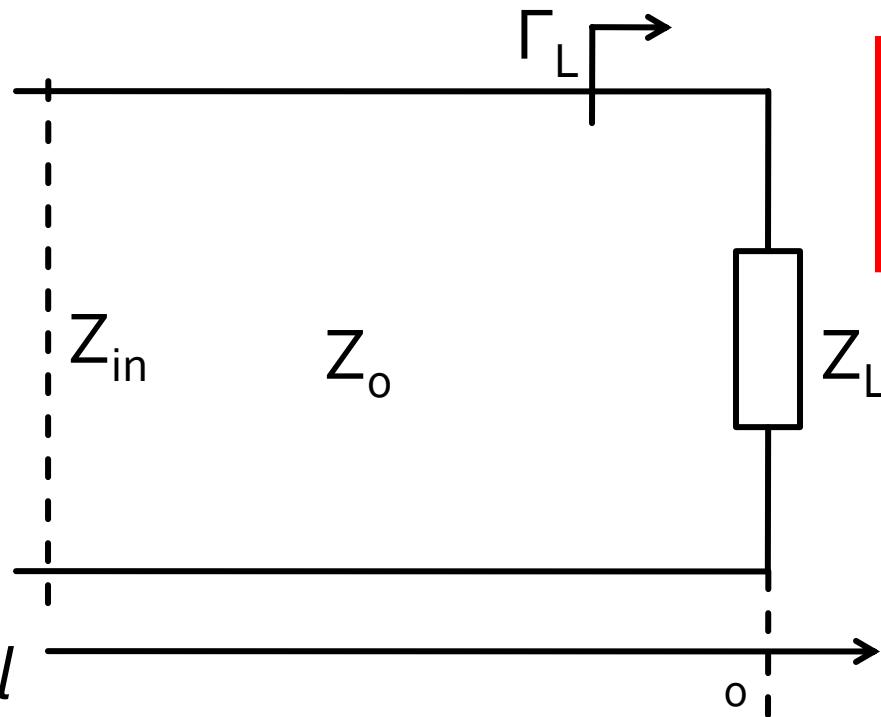
- input impedance of a length l of transmission line with characteristic impedance Z_0 , loaded with an arbitrary impedance Z_L



$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

The lossless line, special cases

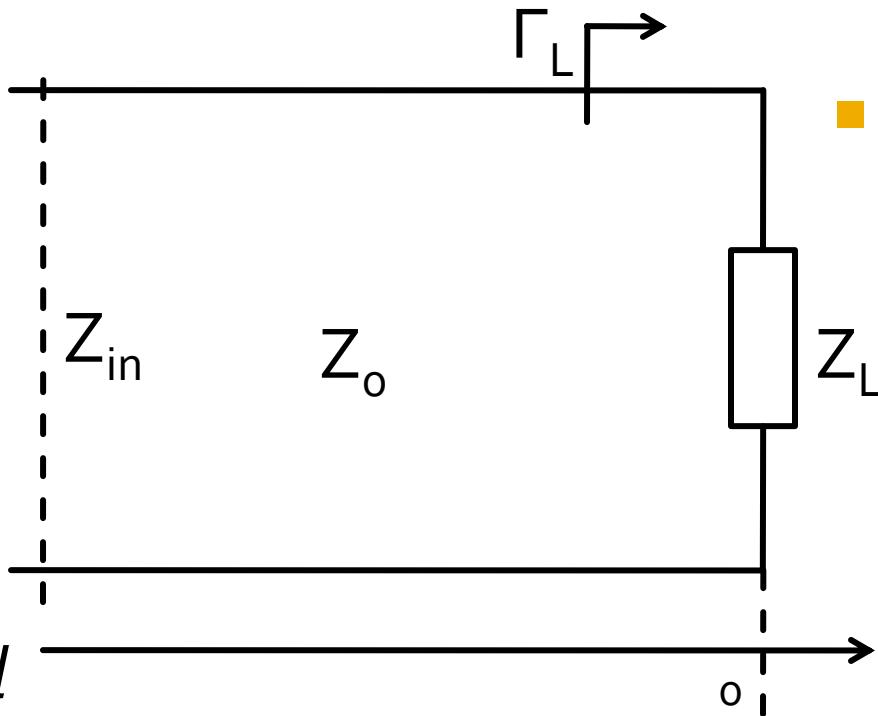- $l = k \cdot \lambda / 2$ $\beta \cdot l = \frac{2\pi}{\lambda} \cdot l = k \cdot \pi$ $\tan \beta \cdot l = 0$ $Z_{in} = Z_0$
- $l = \lambda / 4 + k \cdot \lambda / 2$ $\tan \beta \cdot l \rightarrow \infty$ $Z_{in} = \frac{Z_0^2}{Z_L}$




■ quarter-wave transformer

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

Impedance Matching with Impedance Transformers (Lab 1)

Impedance Matching

Matching, complex impedances

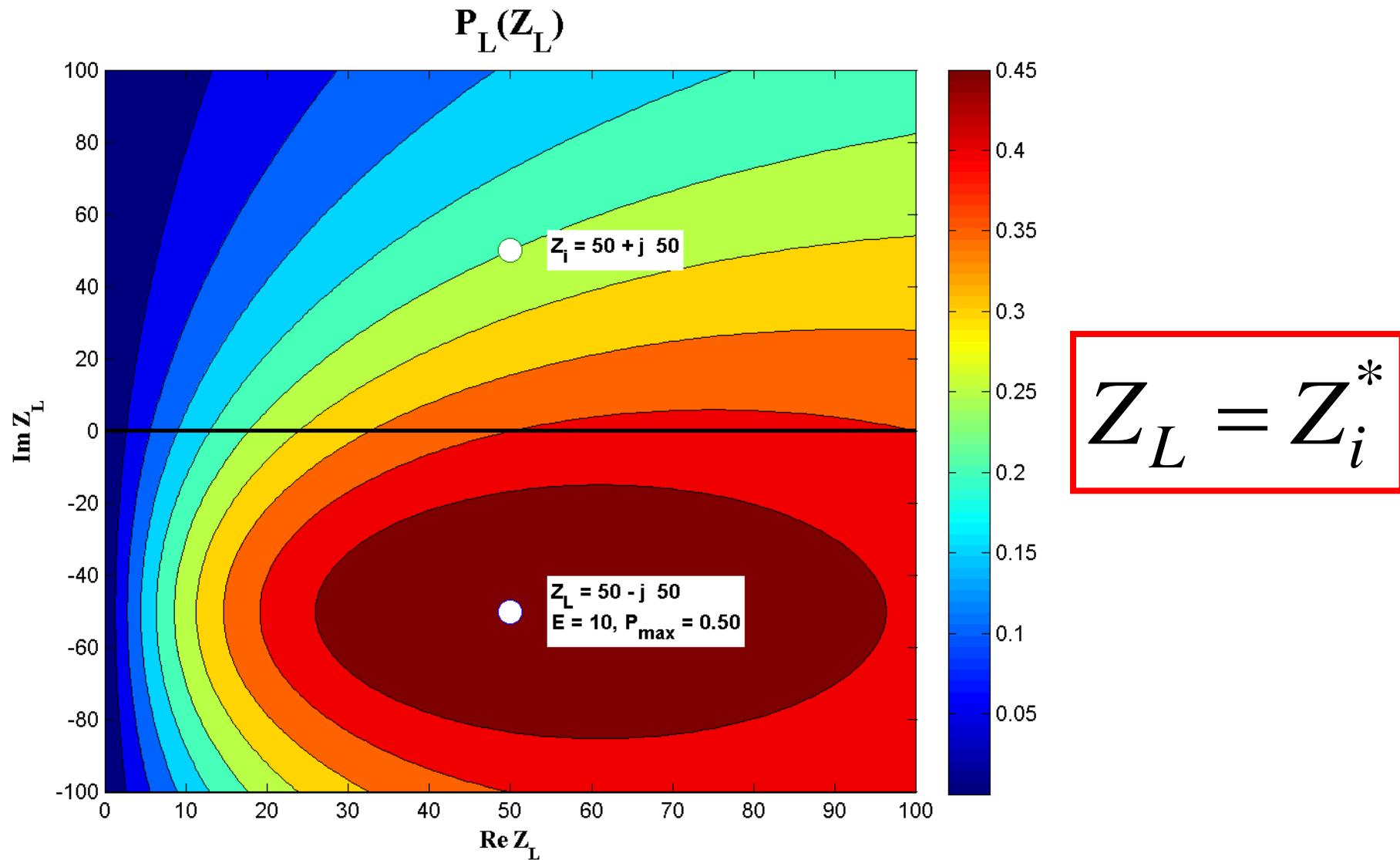

Matching , from the point of view of power transmission


$$Z_L = Z_i^*$$

If we choose a real Z_0


$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

$$\Gamma_L = \Gamma_i^*$$

- complex numbers
- in the complex plane

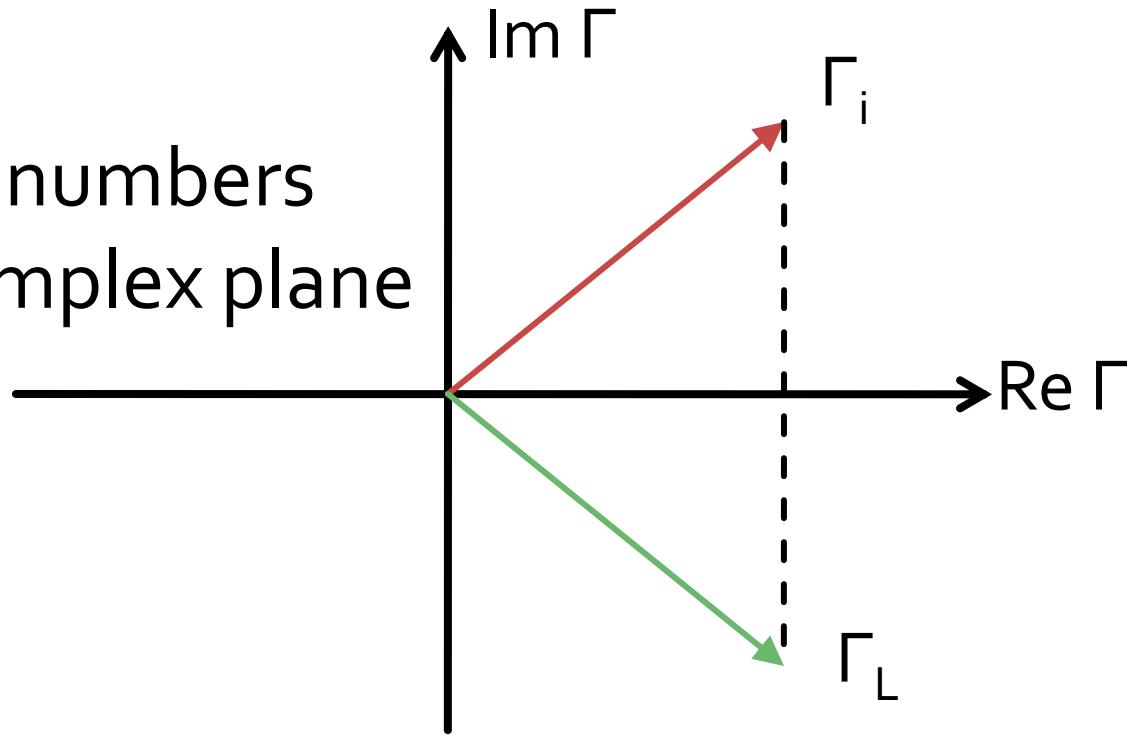


Reflection and power / Model

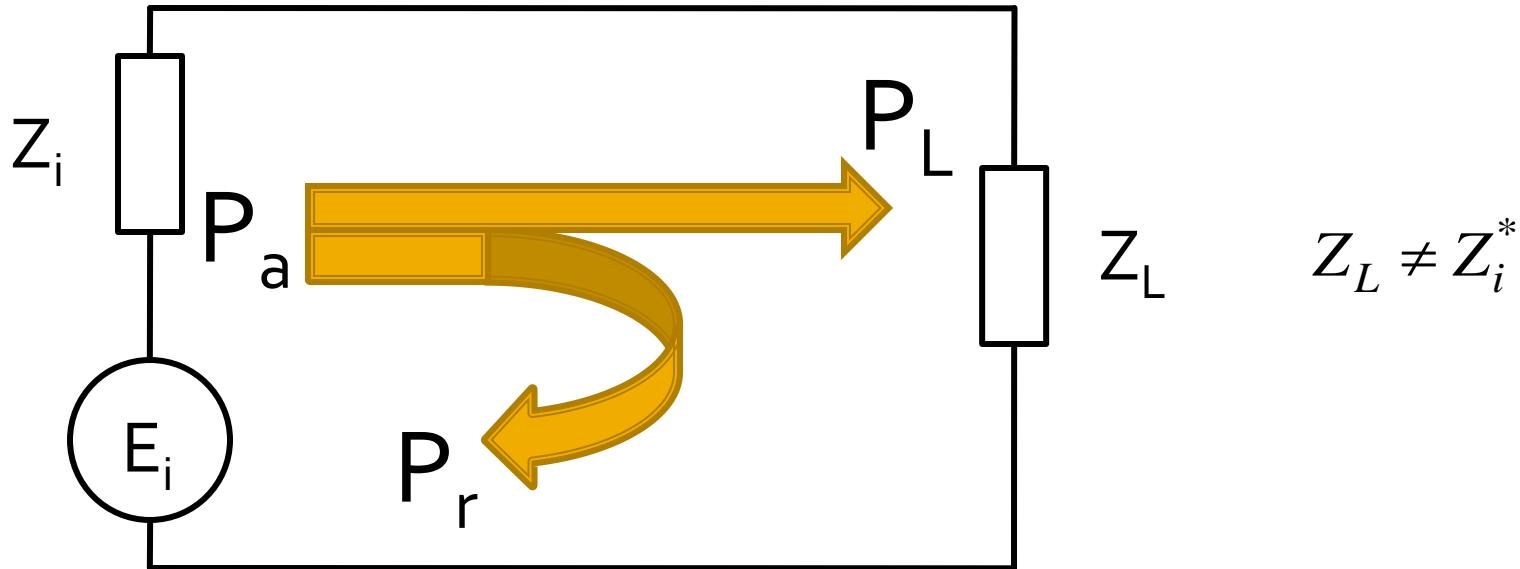

- Power reflection
- Power of the reflected wave

Reflection and power / Model

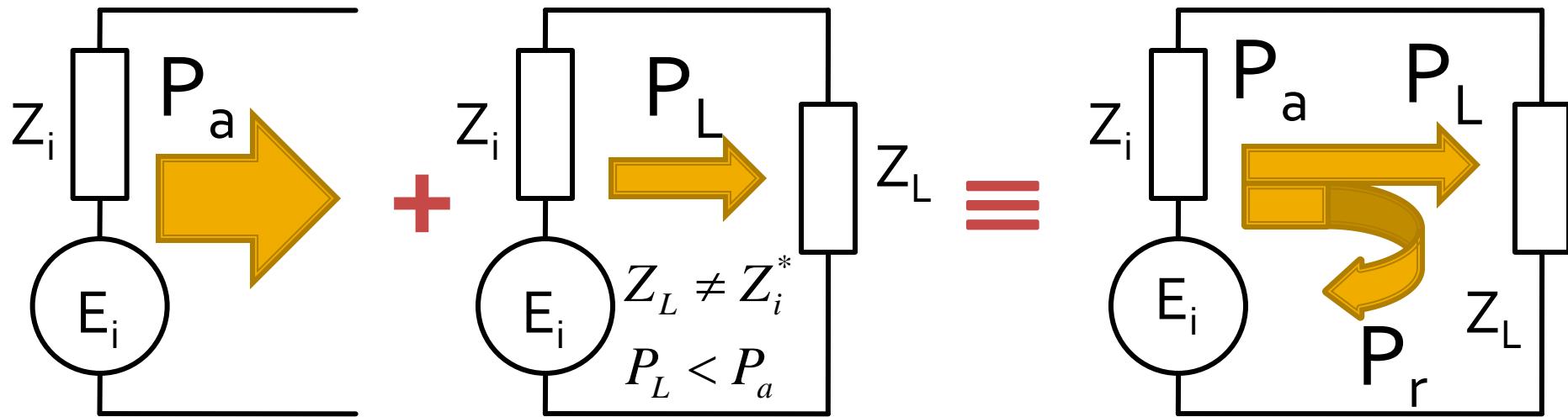


- The source has the ability to send to the load a certain maximum power (available power) P_a
- For a particular load the power sent to the load is less than the maximum (mismatch) $P_L < P_a$
- The phenomenon is “as if” (model) some of the power is reflected $P_r = P_a - P_L$
- The power is a **scalar**!

Lecture 3-4

Microwave Network Analysis


ABCD (transmission) matrix

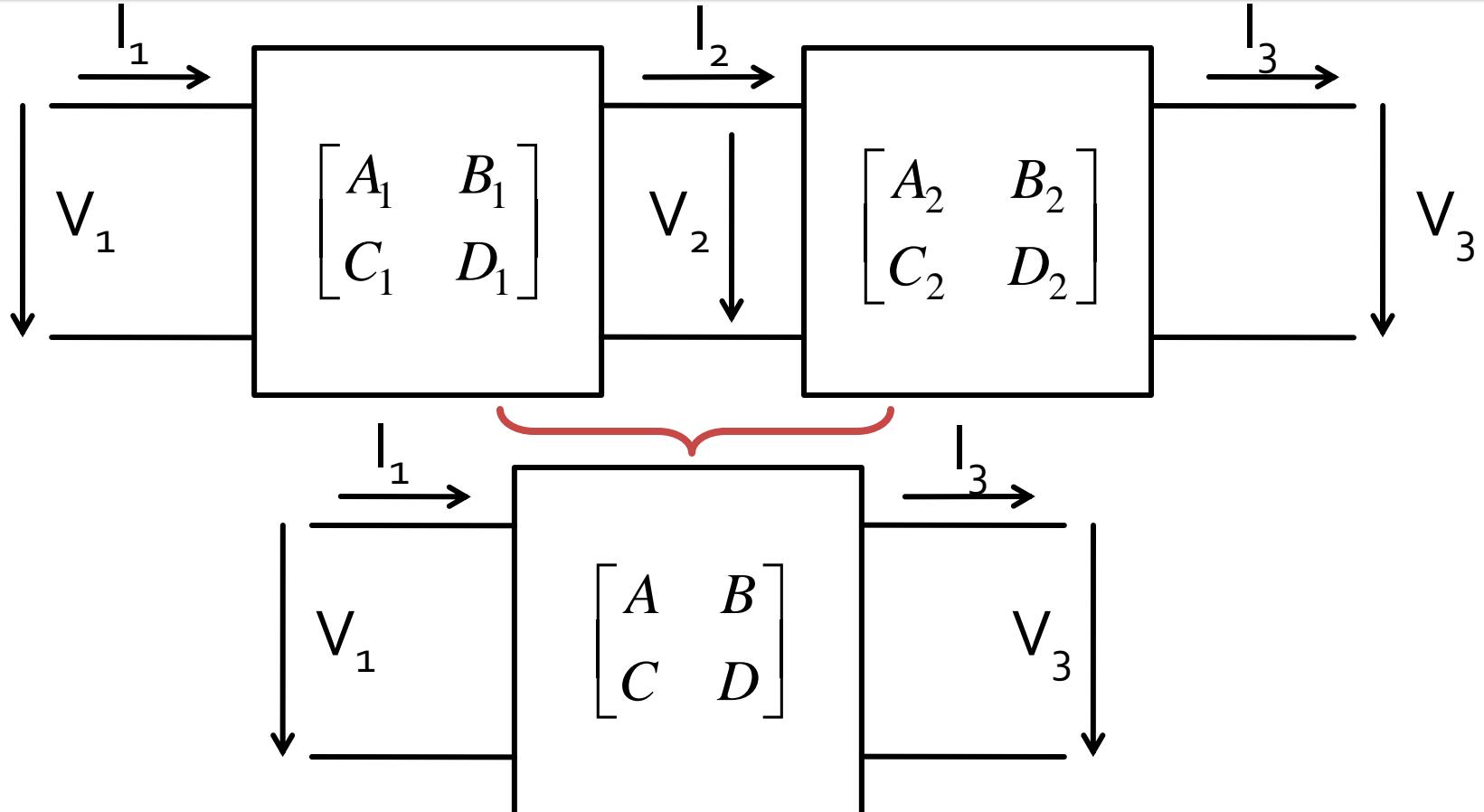

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \cdot \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

Scattering matrix – S

■ Scattering parameters

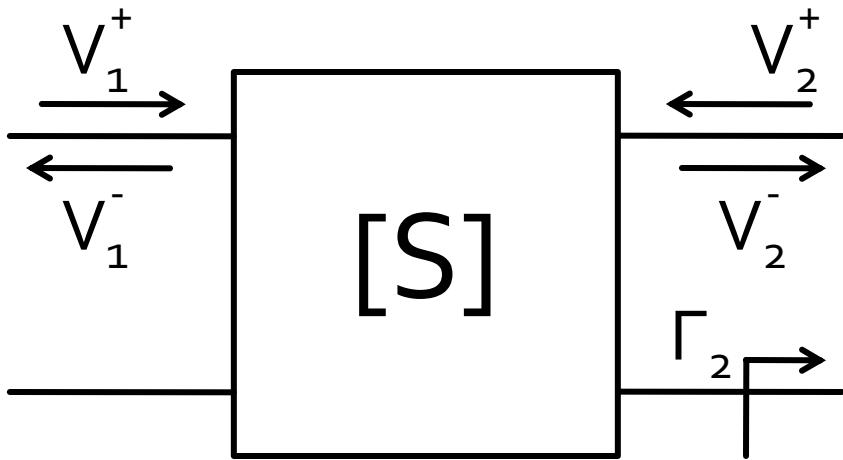


$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_1^+=0} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+=0}$$

- $V_2^+ = 0$ meaning: port 2 is terminated in matched load to avoid reflections towards the port

$$\Gamma_2 = 0 \rightarrow V_2^+ = 0$$

Scattering matrix – S

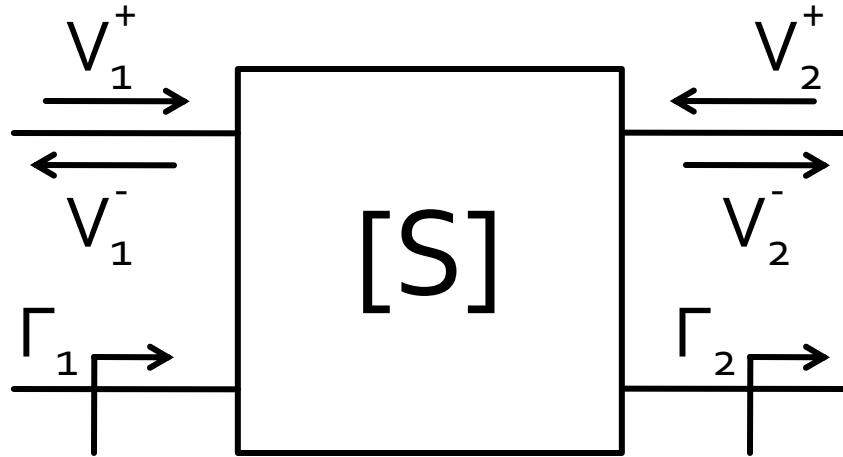

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$S_{11} = \frac{V_1^-}{V_1^+} \Bigg|_{V_2^+=0} = \Gamma_1 \Big|_{\Gamma_2=0}$$

$$S_{21} = \frac{V_2^-}{V_1^+} \Bigg|_{V_2^+=0} = T_{21} \Big|_{\Gamma_2=0}$$

- S_{11} is the reflection coefficient seen looking into port **1** when port **2** is terminated in matched load
- S_{21} is the transmission coefficient from port **1** (**second** index) to port **2** (**first** index) when port **2** is terminated in matched load

Scattering matrix – S

- S matrix can be extended to multiple ports

$$S_{ii} = \left. \frac{V_i^-}{V_i^+} \right|_{V_k^+=0, \forall k \neq i}$$

$$S_{ij} = \left. \frac{V_i^-}{V_j^+} \right|_{V_k^+=0, \forall k \neq j}$$

- S_{ii} is the reflection coefficient seen looking into port i when all other ports are terminated in matched loads
- S_{ij} is the transmission coefficient from port j (**second** index) to port i (**first** index) when all other ports are terminated in matched loads

Properties of S matrix

- If port i is connected to a transmission line with characteristic impedance Z_{oi}

$$[Z_0] = \begin{bmatrix} Z_{01} & \cdots & 0 \\ \vdots & \ddots & \vdots \\ 0 & \cdots & Z_{0n} \end{bmatrix}$$

- Lecture 2 $V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$ $I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$

In the port's reference plane, $z=0$

$$V_i = V_i^+ + V_i^- \quad I_i = \frac{V_i^+}{Z_{0i}} - \frac{V_i^-}{Z_{0i}}$$

- Relation to Z matrix $[Z] \cdot [I] = [V]$

$$[Z] \cdot [I] = [Z_0]^{-1} \cdot [Z] \cdot [V^+] - [Z_0]^{-1} \cdot [Z] \cdot [V^-] \quad [V] = [V^+] + [V^-]$$

$$[Z_0]^{-1} \cdot [Z] \cdot [V^+] - [Z_0]^{-1} \cdot [Z] \cdot [V^-] = [V^+] + [V^-] \quad ([Z] - [Z_0]) \cdot [V^+] = ([Z] + [Z_0]) \cdot [V^-]$$

$$[V^-] = [S] \cdot [V^+]$$

$$[S] = ([Z] - [Z_0]) \cdot ([Z] + [Z_0])^{-1}$$

Generalized Scattering Parameters

- We define the power wave amplitudes a and b

$$a = \frac{V + Z_R \cdot I}{2 \cdot \sqrt{R_R}} \text{ the incident power wave} \quad Z_R = R_R + j \cdot X_R$$

$$b = \frac{V - Z_R^* \cdot I}{2 \cdot \sqrt{R_R}} \text{ the reflected power wave}$$

Any complex impedance,
named reference impedance

- Total voltage and current in terms of the power wave amplitudes

$$V = \frac{Z_R^* \cdot a + Z_R \cdot b}{\sqrt{R_R}}$$

$$I = \frac{a - b}{\sqrt{R_R}}$$

Power waves for N ports

$$[b] = [F] \cdot ([Z] - [Z_R]^*) \cdot ([Z] + [Z_R])^{-1} \cdot [F]^{-1} \cdot [a]$$

- The scattering matrix for power waves, $[S_p]$

$$[b] = [S_p] \cdot [a]$$

$$[S_p] = [F] \cdot ([Z] - [Z_R]^*) \cdot ([Z] + [Z_R])^{-1} \cdot [F]^{-1}$$

- But: $[S] = ([Z] - [Z_0]) \cdot ([Z] + [Z_0])^{-1}$

- Typically


$$Z_{0i} = Z_{Ri} = R_0, \forall i$$

$$R_0 = 50\Omega$$

$$[S_p] \equiv [S]$$

- they coincide!!!

Scattering matrix – S

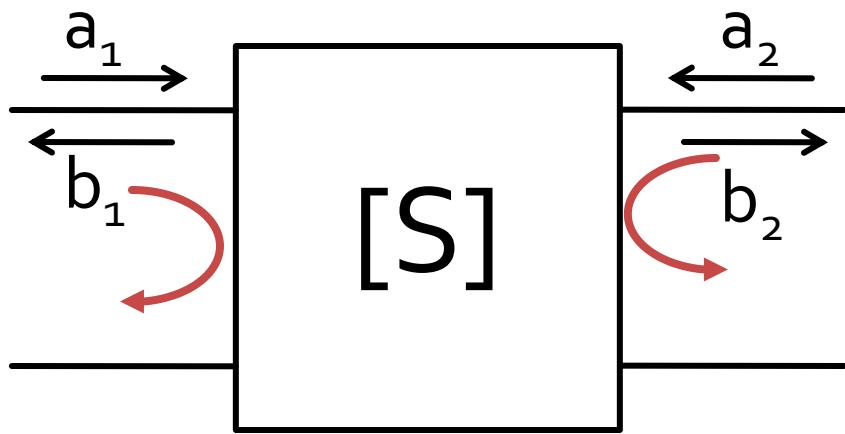


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

- S_{11} and S_{22} are reflection coefficients at ports 1 and 2 when the other port is matched

Scattering matrix – S

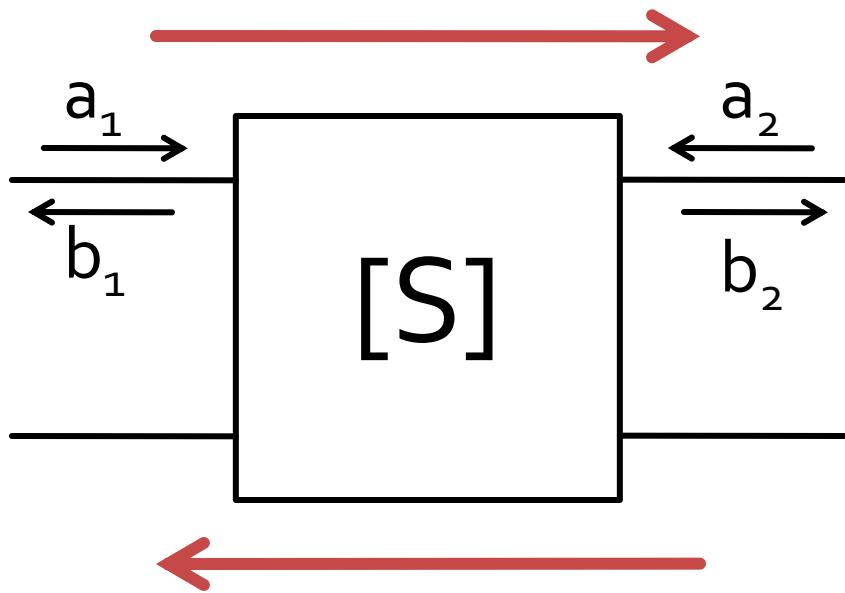


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0}$$

$$S_{12} = \frac{b_1}{a_2} \Big|_{a_1=0}$$

- S_{21} si S_{12} are signal amplitude gain when the other port is matched

Scattering matrix – S

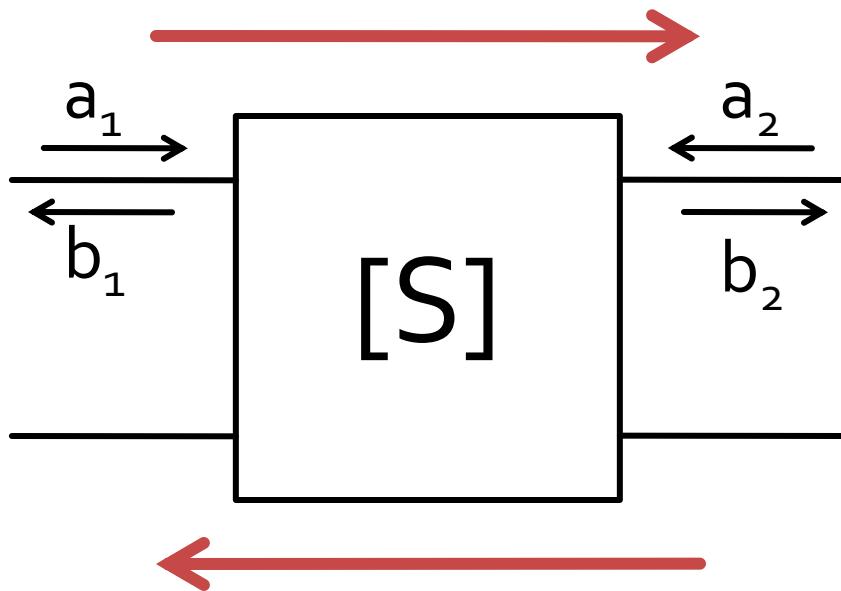

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- a, b
 - information about signal power **AND** signal phase
- S_{ij}
 - network effect (gain) over signal power **including** phase information

Measuring S parameters - VNA

■ Vector Network Analyzer


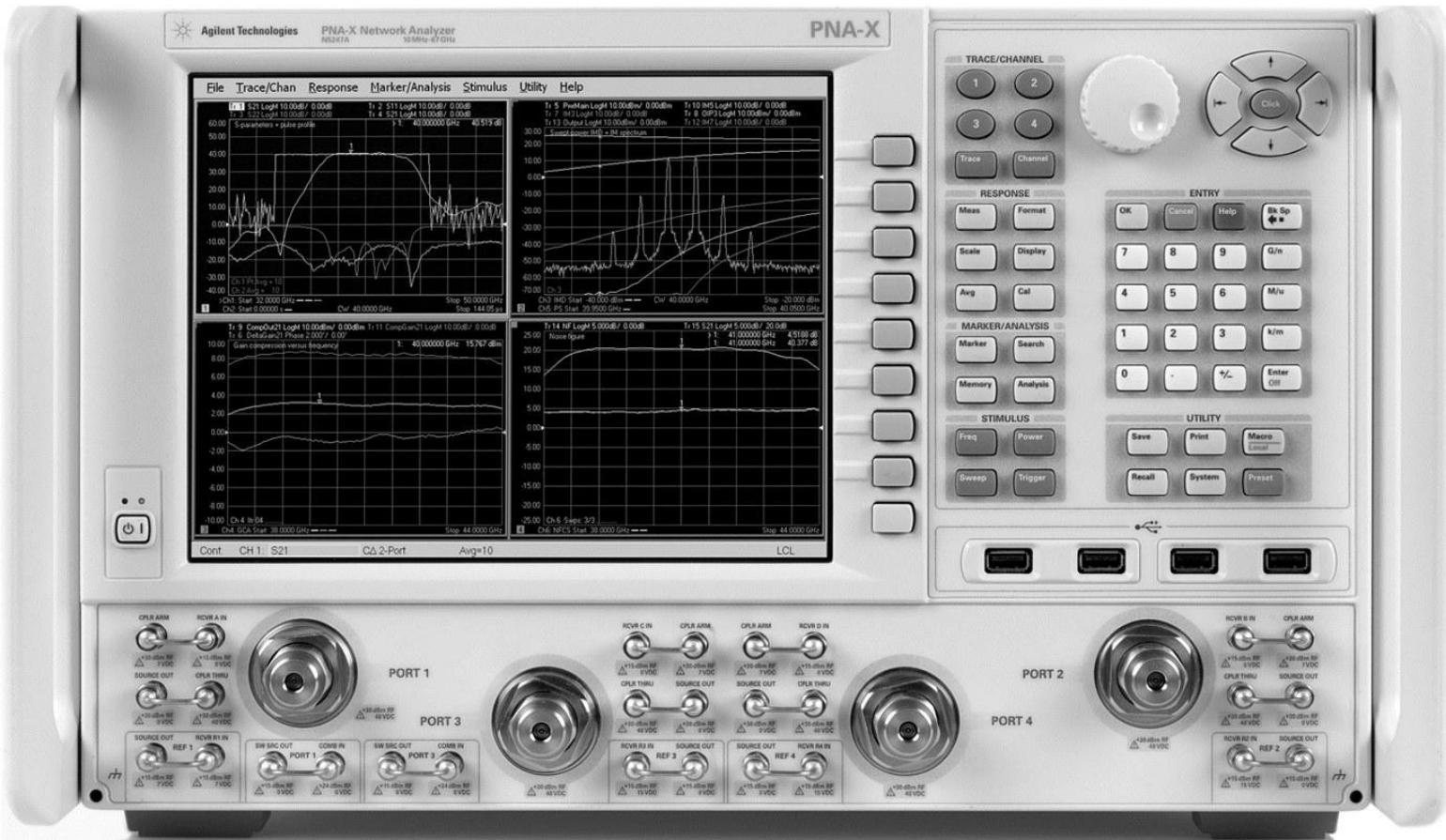


Figure 4.7
Courtesy of Agilent Technologies


Impedance Matching

The Smith Chart



The Smith Chart

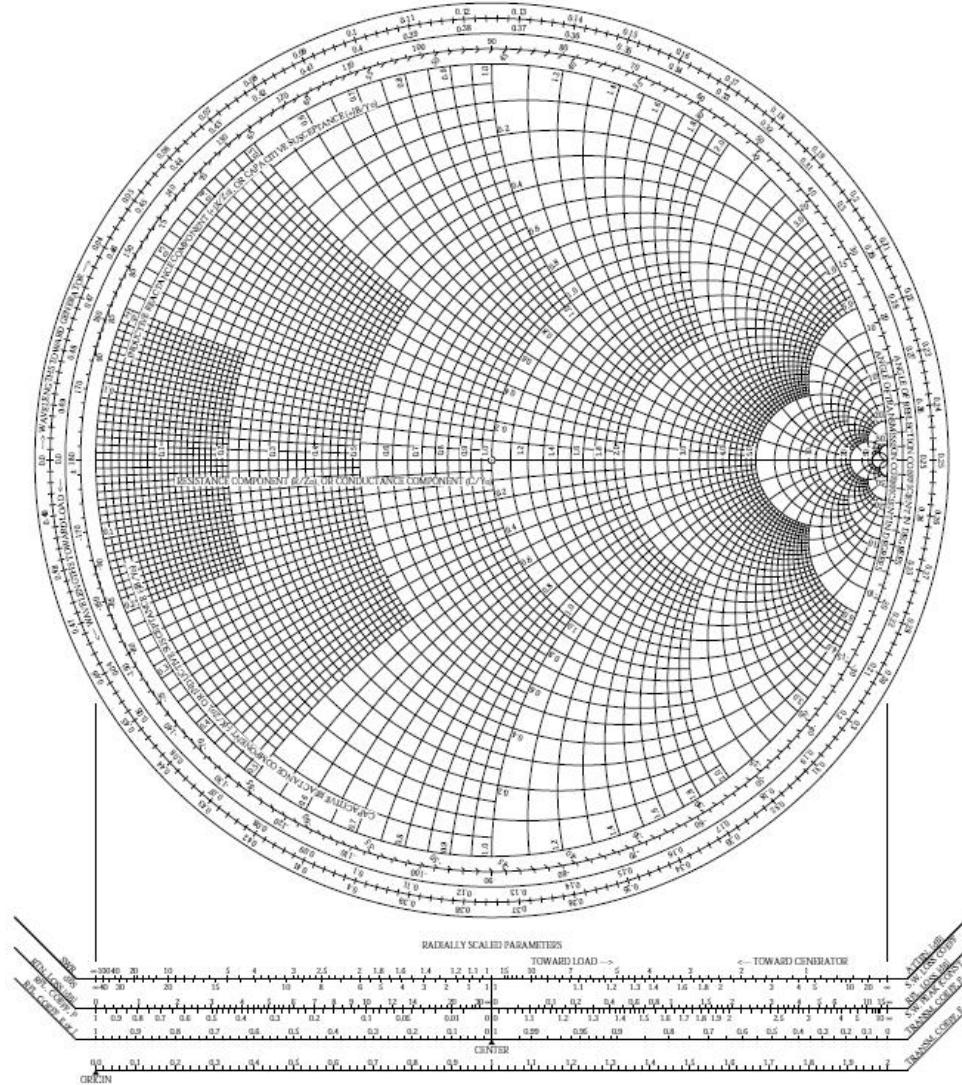


The Smith Chart

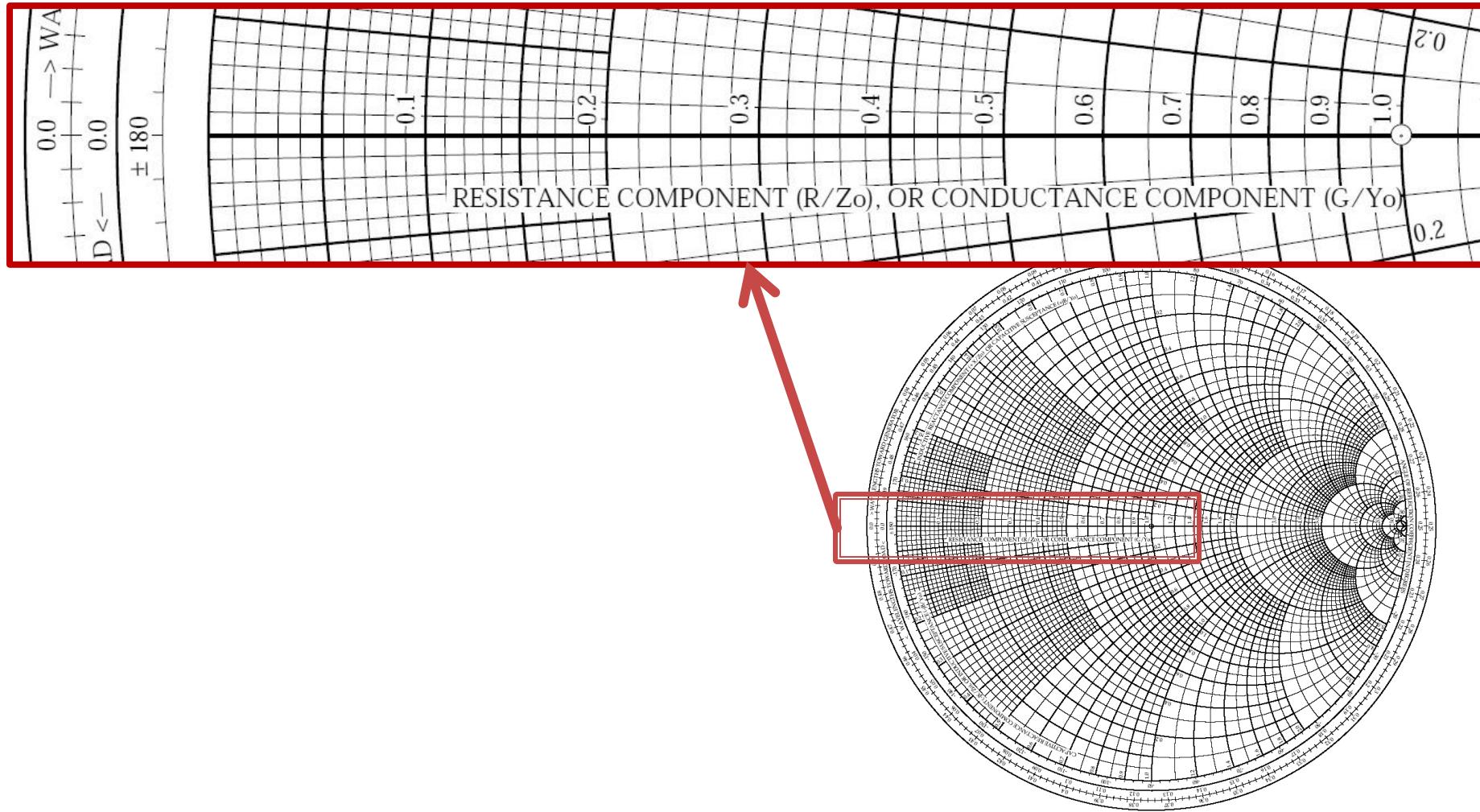


The Smith Chart

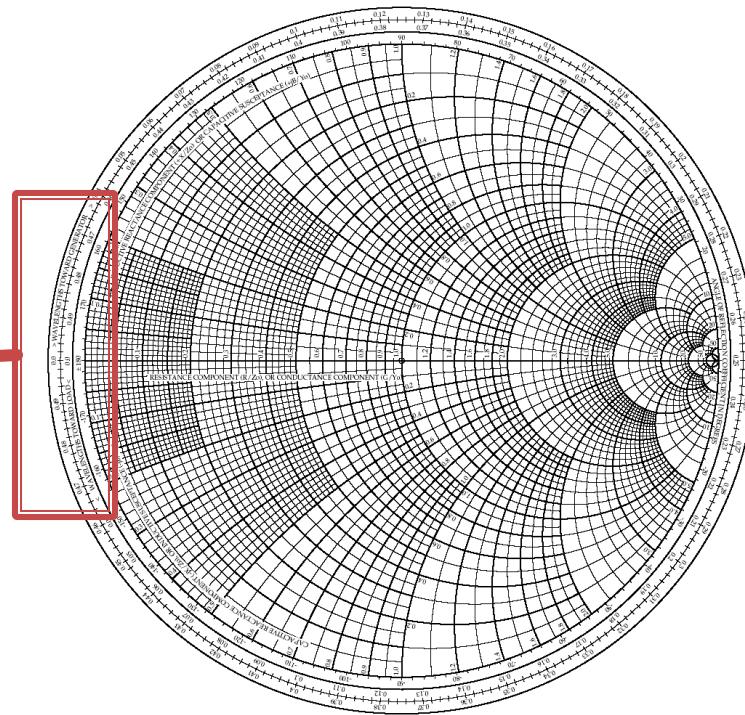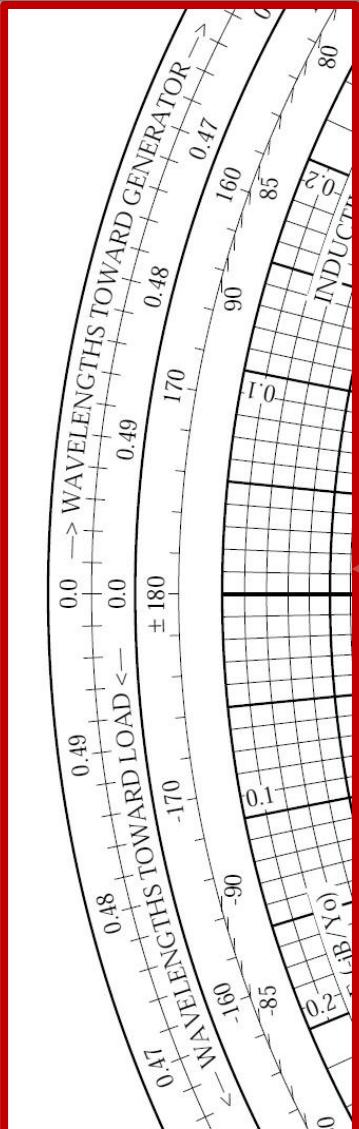


The Smith Chart

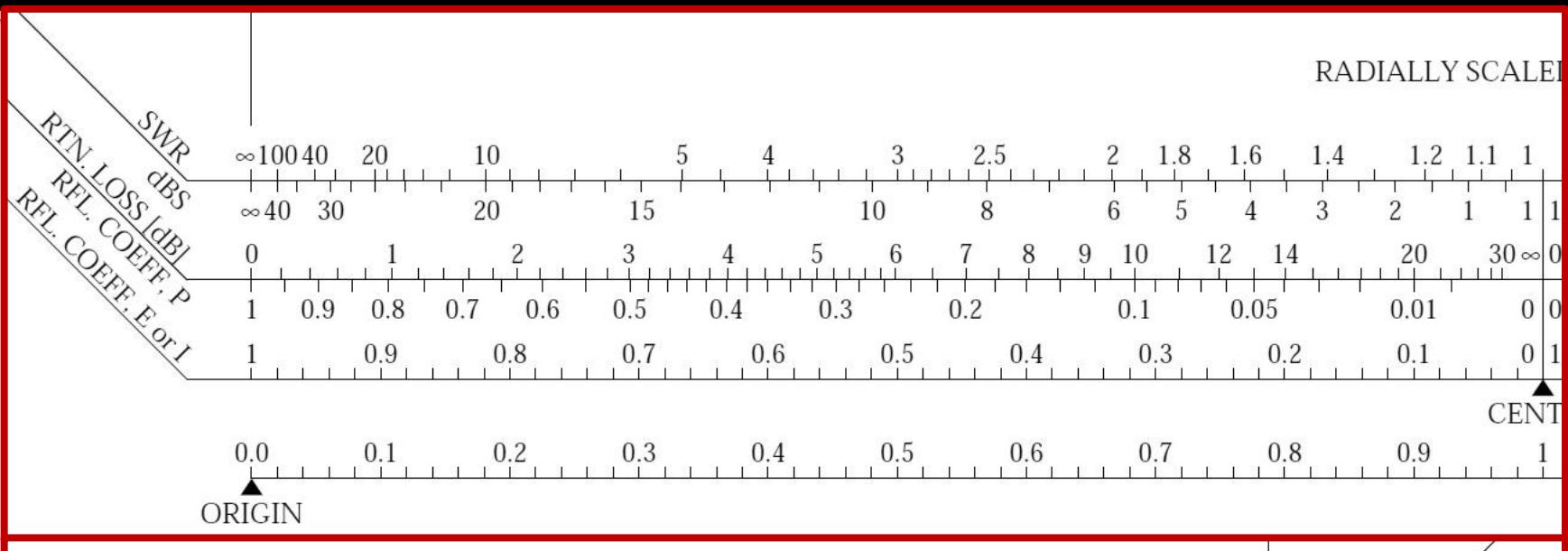


ALIGNED PARAMETERS

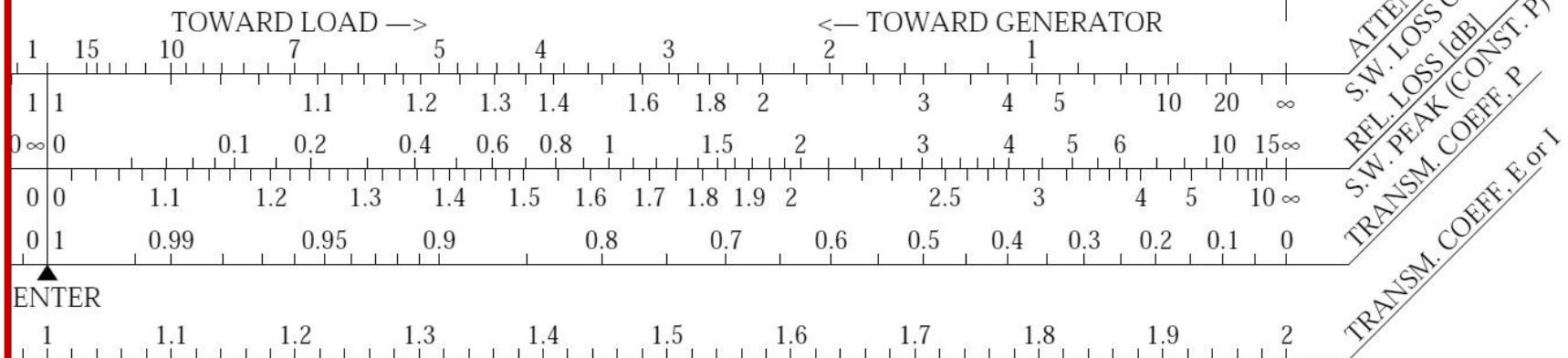


The Smith Chart

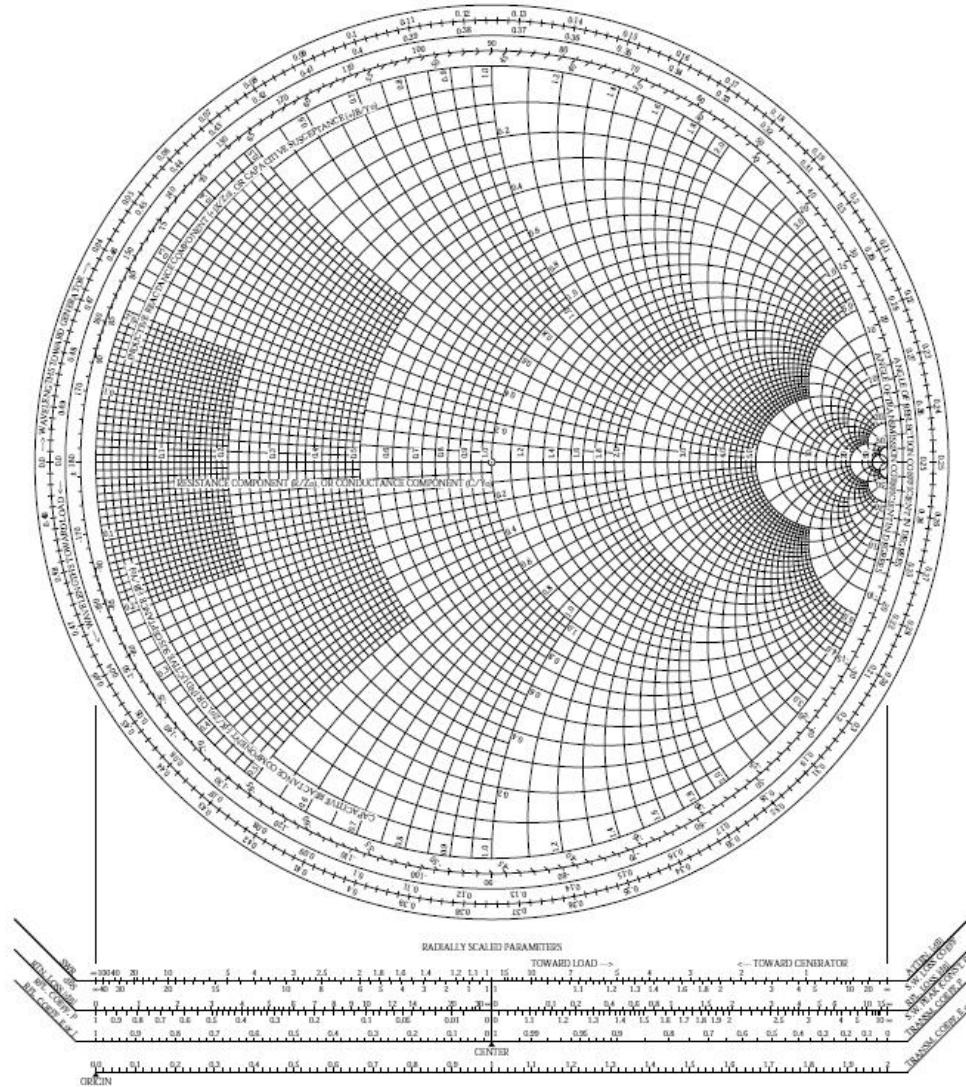


The Smith Chart

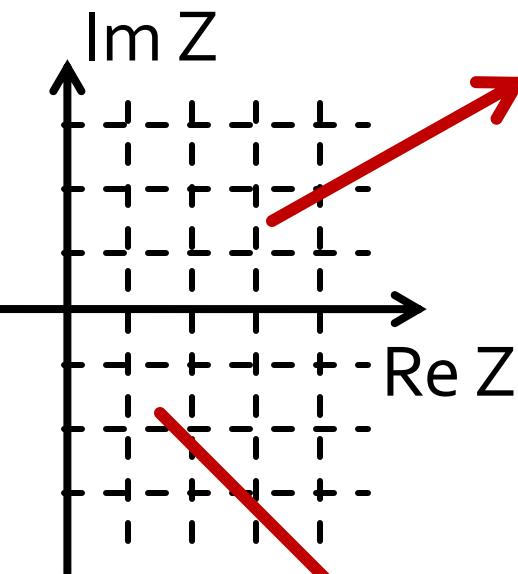
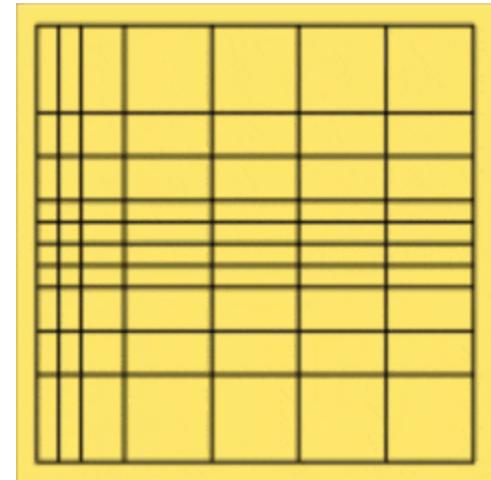
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$



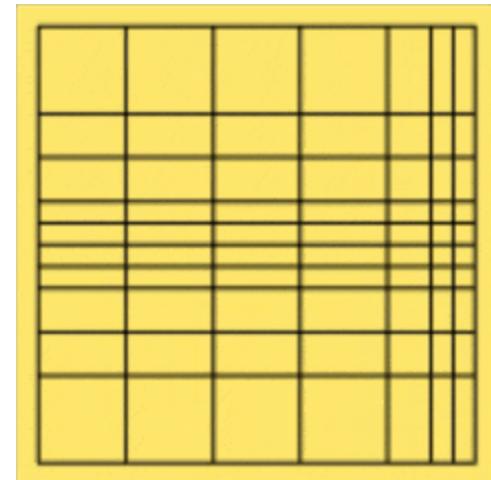
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Y_0 - Y_L}{Y_0 + Y_L} = \frac{1 - y_L}{1 + y_L}$$



Traditional usage

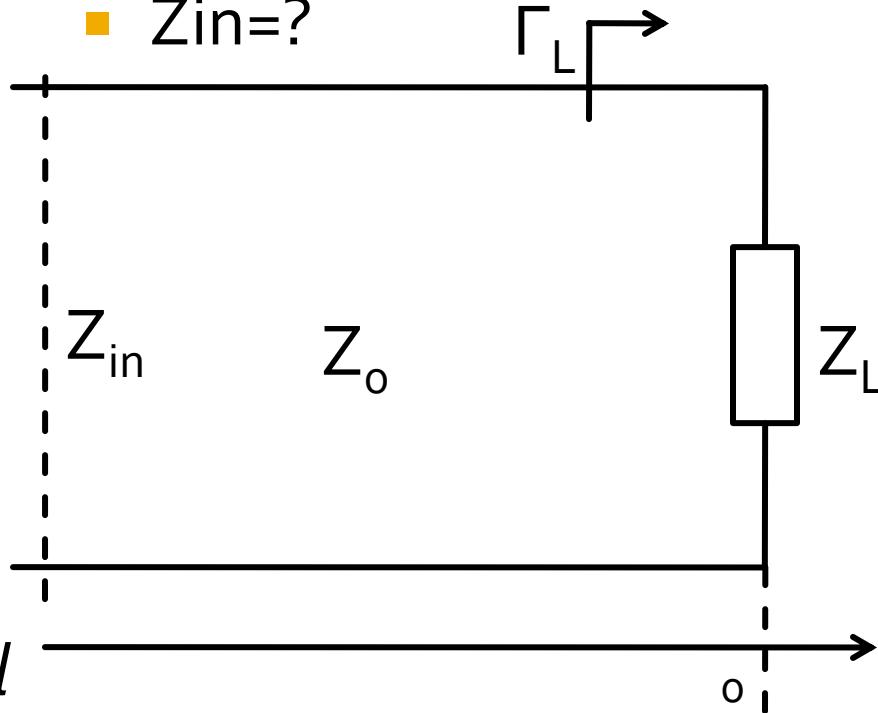- transmission line
 - 100Ω characteristic impedance
 - 0.3λ length
 - $Z_L = 40\Omega + j \cdot 70\Omega$ load
- $Z_{in}=?$



$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

$$Z_{in} = 36.5340\Omega - j \cdot 61.1190\Omega$$

Traditional usage


- transmission line
 - 100Ω impedance
 - 0.3λ length
 - $Z_L = 40\Omega + j \cdot 70\Omega$ load
- normalization with $Z_0 = 100\Omega$

$$z_L = \frac{Z_L}{Z_0} = 0.4 + j \cdot 0.7$$


- movement with 0.3λ on a line with $Z_0 = 100\Omega$ (circle)

- from z_L (0.105λ)
- to z_{in} (0.405λ)

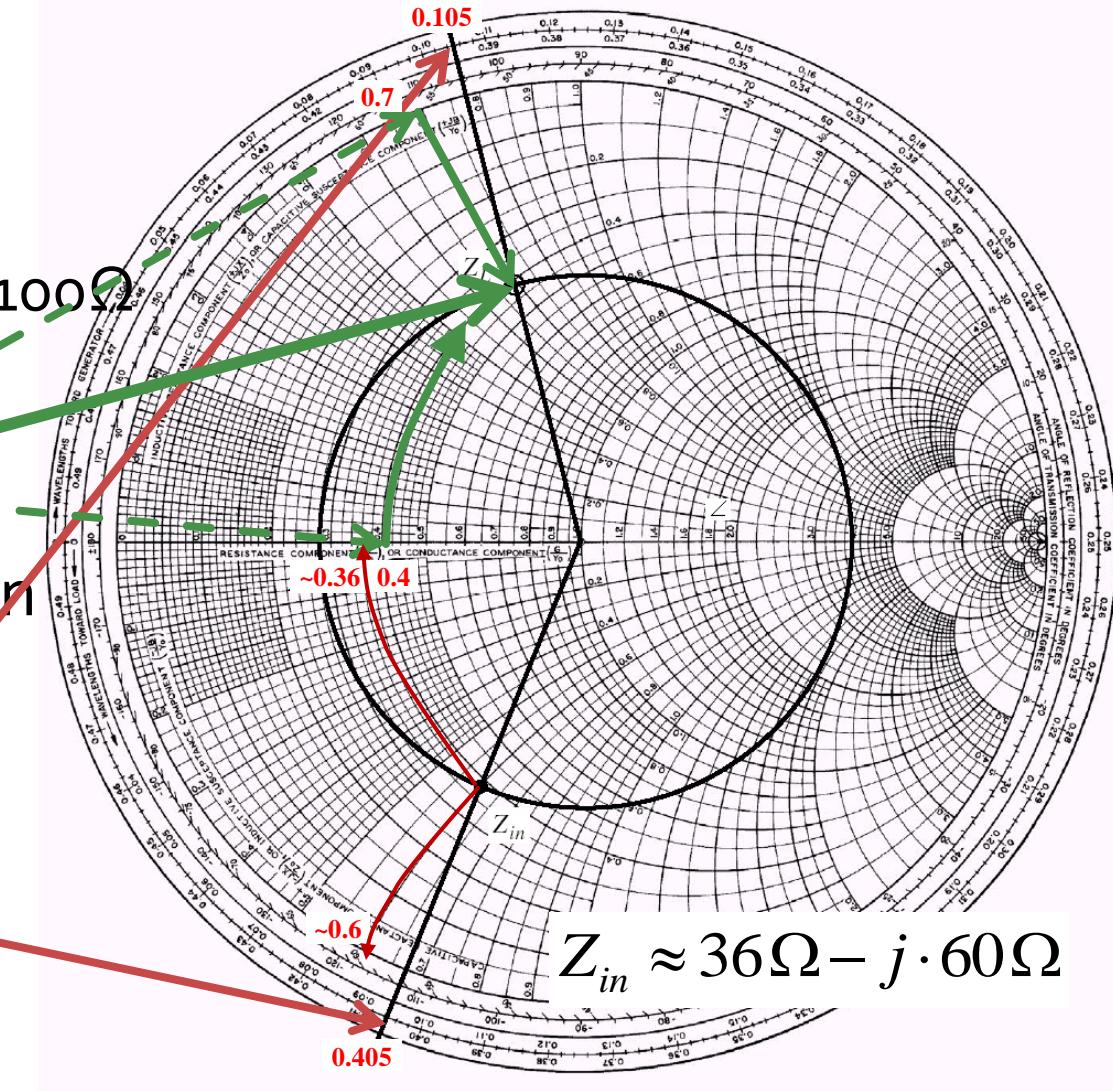
$$z_{in} \approx 0.36 - j \cdot 0.6 = \frac{Z_{in}}{Z_0}$$



The Smith Chart

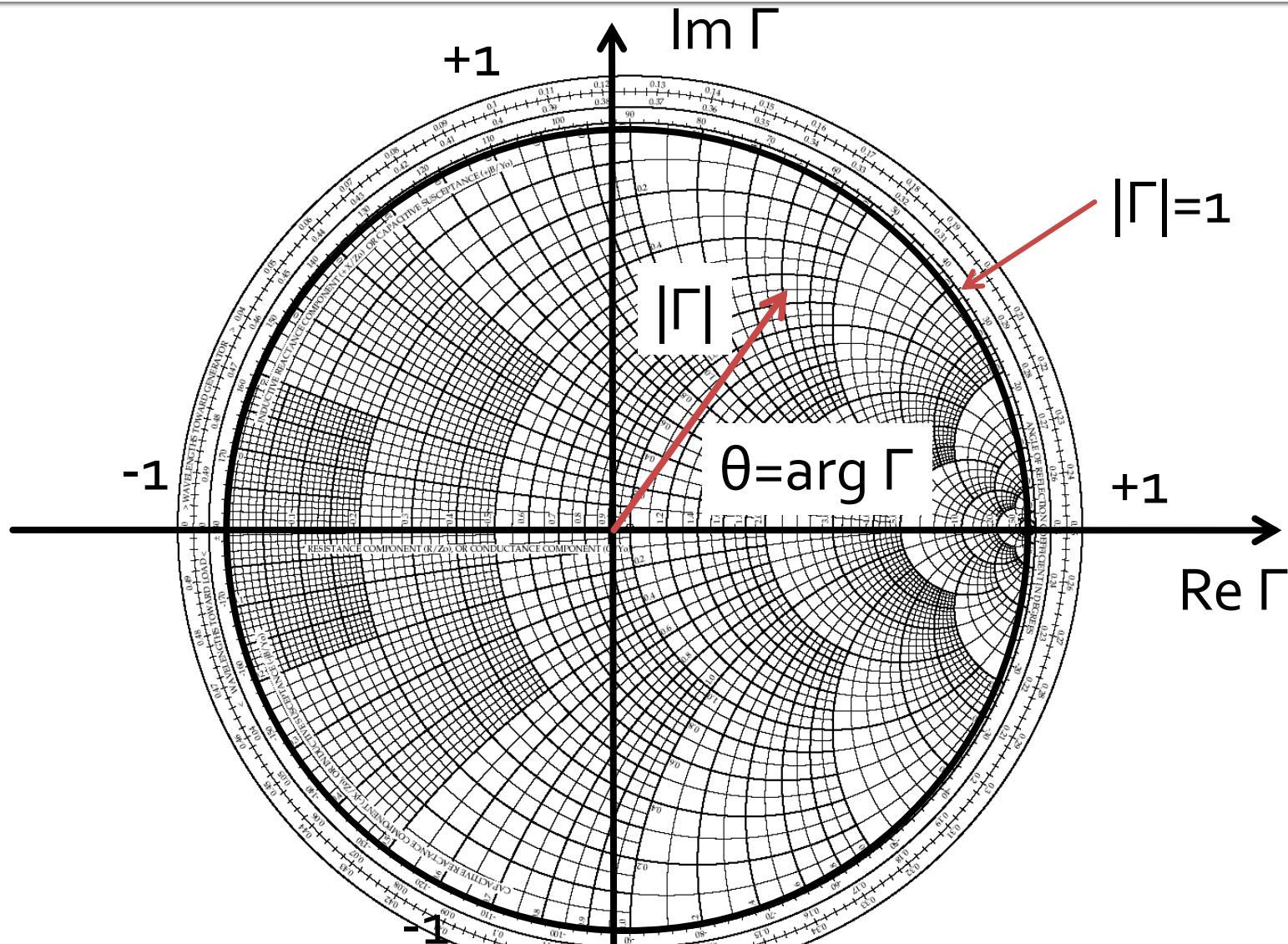


The Smith Chart



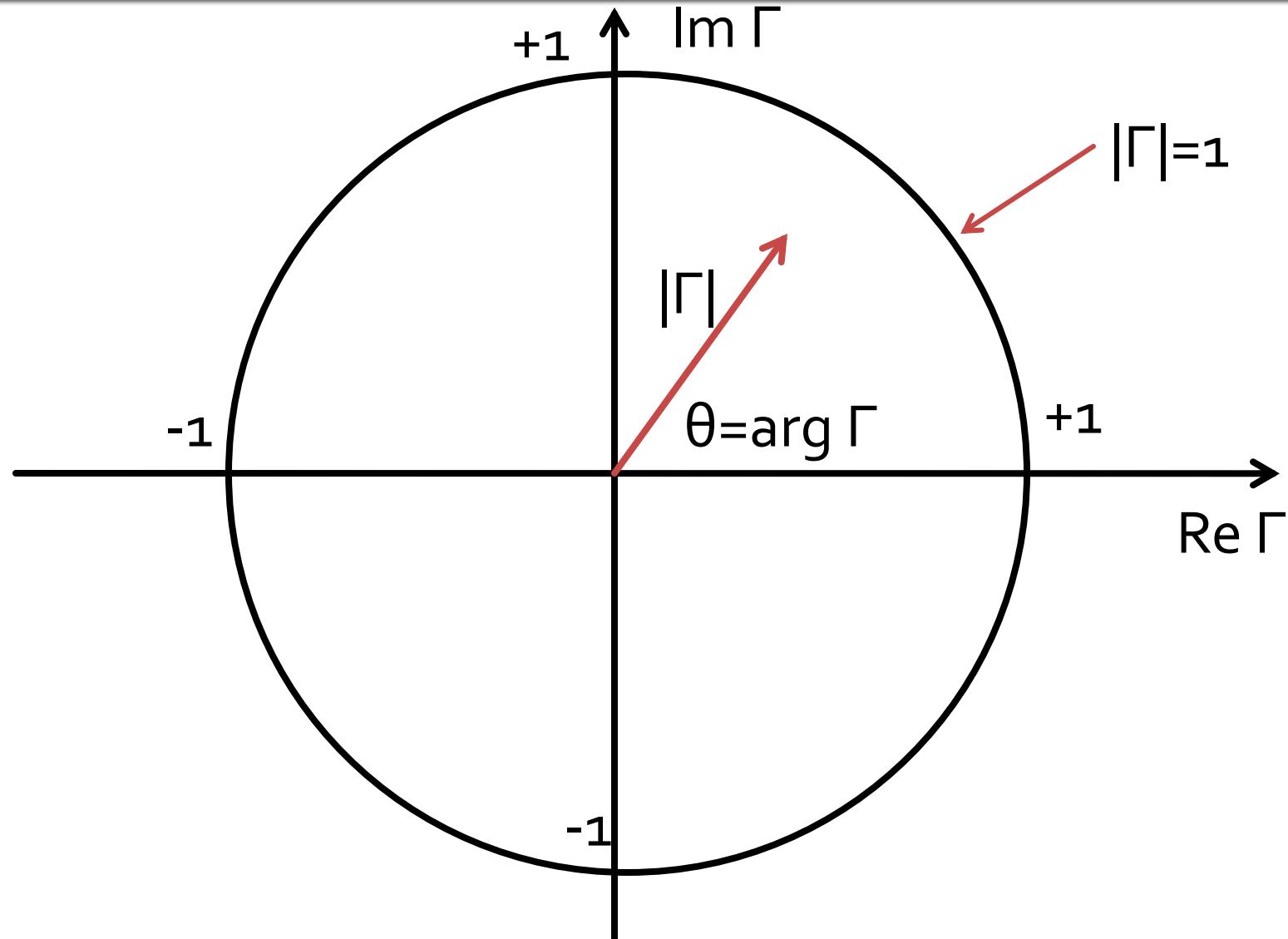


The Smith Chart

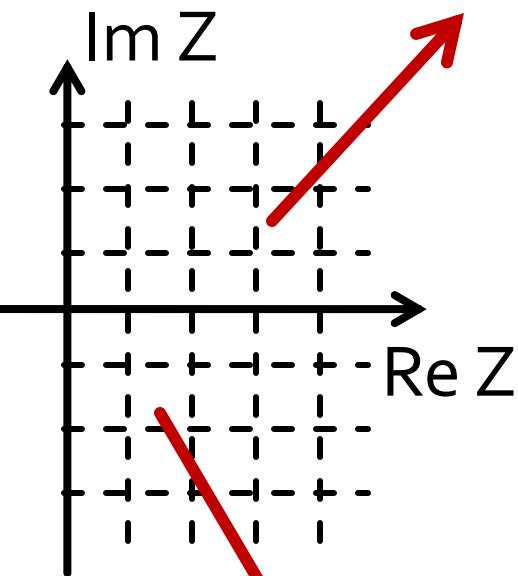
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$


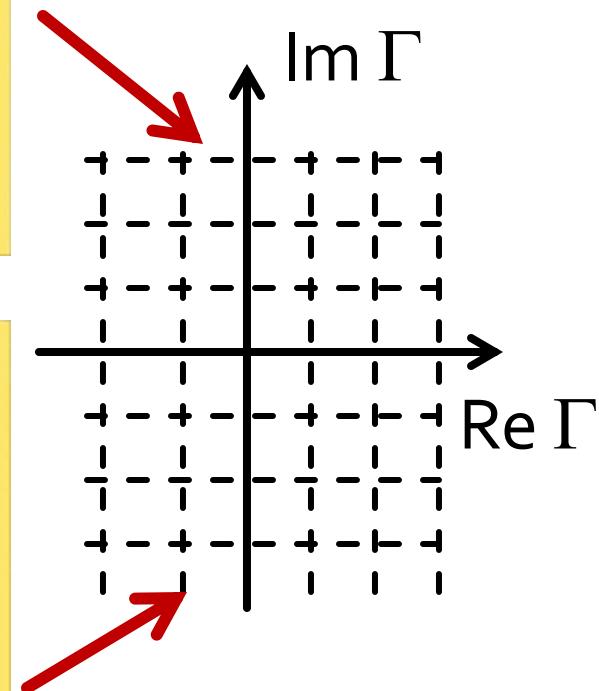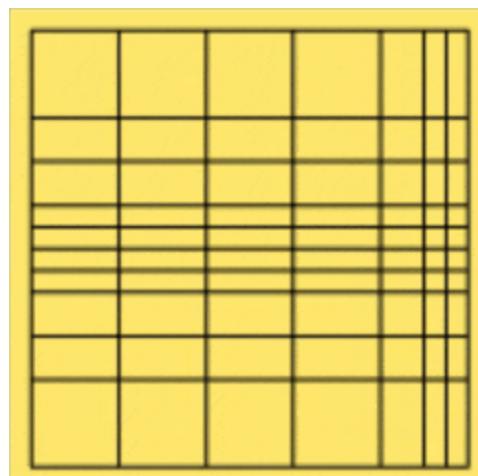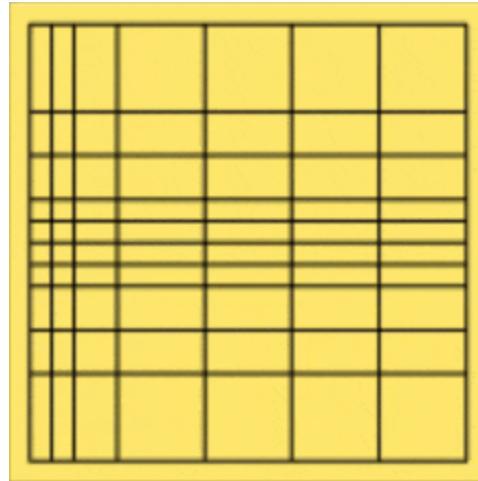
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Y_0 - Y_L}{Y_0 + Y_L} = \frac{1 - y_L}{1 + y_L}$$



The Smith Chart

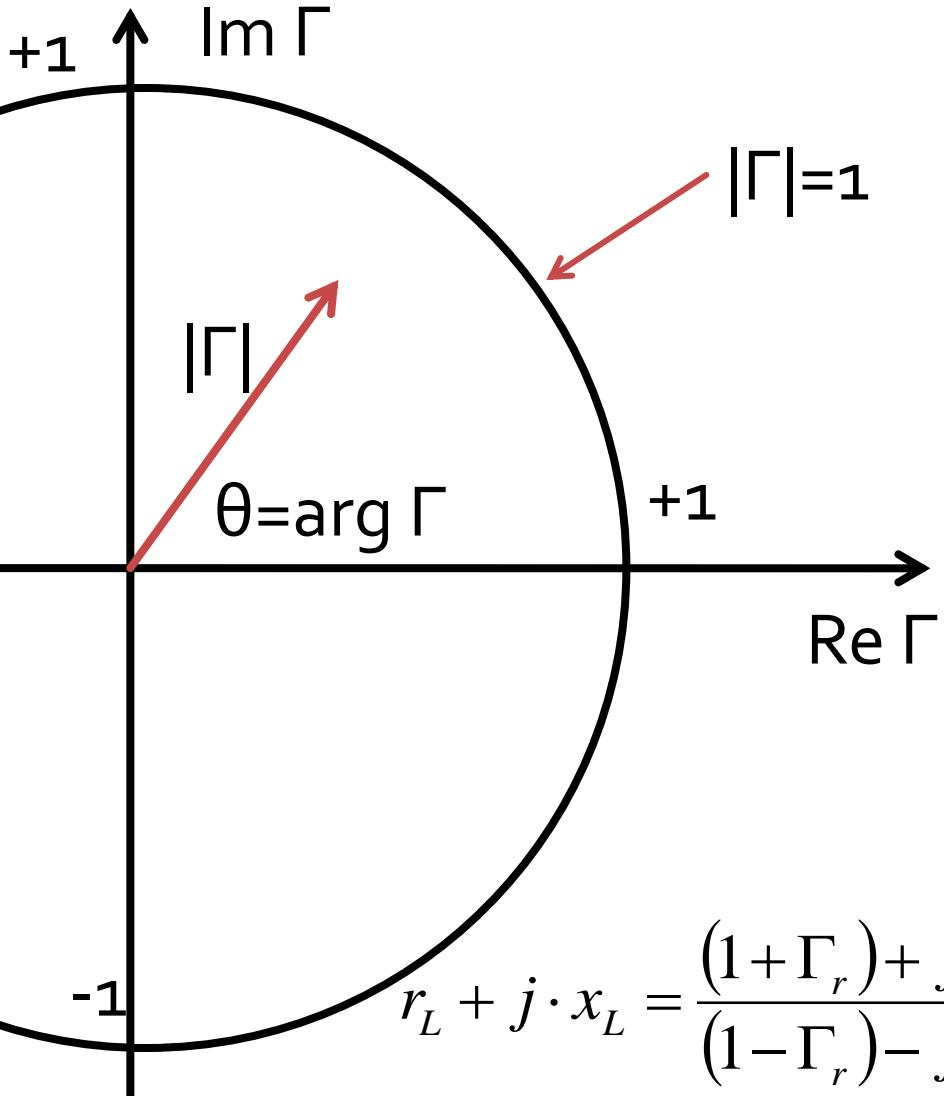

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1} = |\Gamma| \cdot e^{j\theta}$$

$$z_L = \frac{Z_L}{Z_0} \quad y_L = \frac{Y_L}{Y_0} = \frac{Z_0}{Z_L}$$


normalization $Z_L \rightarrow z_L$ allows using the same chart for any reference impedance Z_0 (the plot becomes independent of the chosen Z_0)

$$\Gamma = \Gamma_r + j \cdot \Gamma_i$$

$$z_L = \frac{1 + |\Gamma| \cdot e^{j\theta}}{1 - |\Gamma| \cdot e^{j\theta}} = r_L + j \cdot x_L$$

$$r_L + j \cdot x_L = \frac{(1 + \Gamma_r) + j \cdot \Gamma_i}{(1 - \Gamma_r) - j \cdot \Gamma_i} = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} + j \cdot \frac{2 \cdot \Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

The Smith Chart

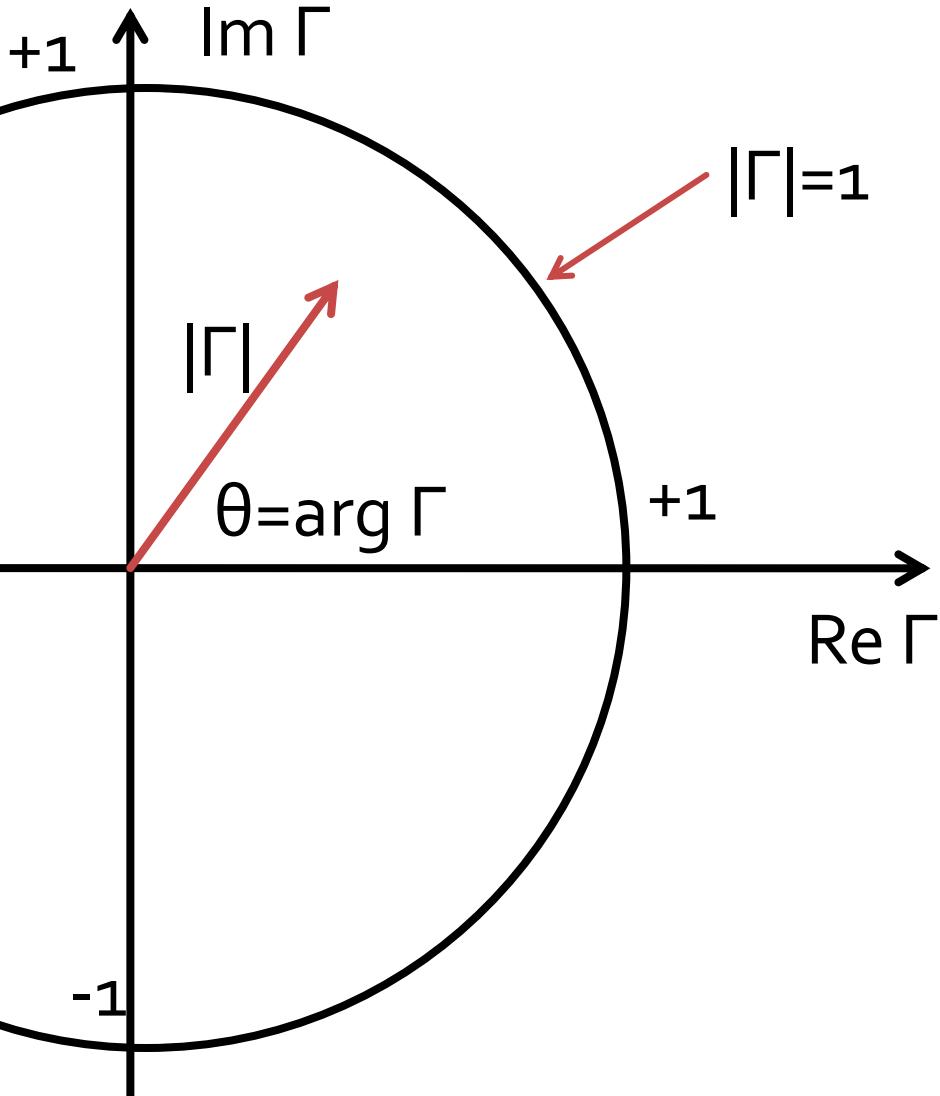

$$r_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$


$$x_L = \frac{2 \cdot \Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

■ Rearranged


$$\left(\Gamma_r - \frac{r_L}{1 + r_L} \right)^2 + \Gamma_i^2 = \left(\frac{1}{1 + r_L} \right)^2$$

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L} \right)^2 = \left(\frac{1}{x_L} \right)^2$$

The Smith Chart

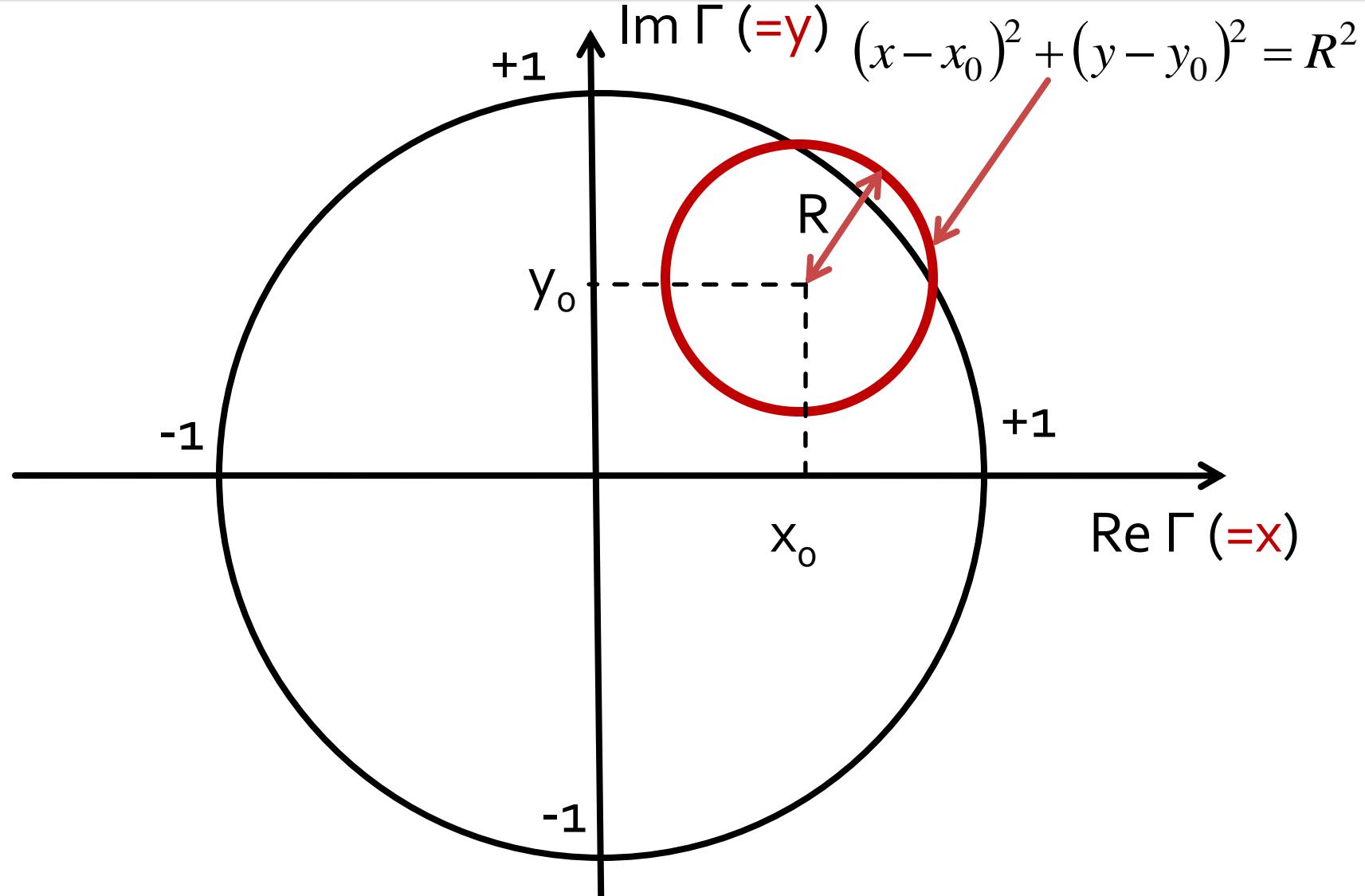

The Smith Chart

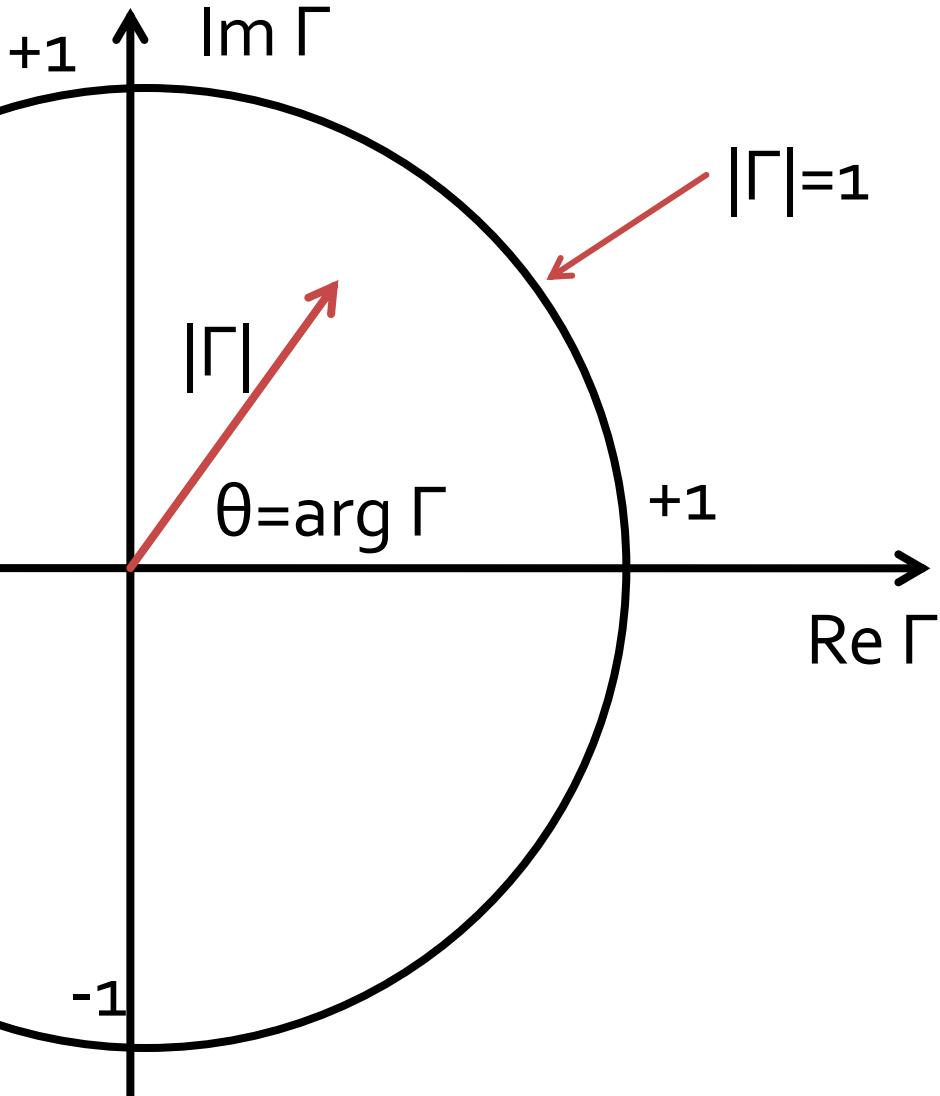

$$\left(\Gamma_r - \frac{r_L}{1+r_L} \right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r_L} \right)^2$$

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L} \right)^2 = \left(\frac{1}{x_L} \right)^2$$

- **Circles** in the (Γ_r, Γ_i) complex plane

$$(x - x_0)^2 + (y - y_0)^2 = R^2$$

The Smith Chart, resistance


$$\begin{aligned} & \left(\Gamma_r - \frac{r_L}{1+r_L} \right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r_L} \right)^2 \\ & (x-x_0)^2 + (y-y_0)^2 = R^2 \end{aligned}$$

$$\begin{cases} x_0 = \frac{r_L}{1+r_L} \\ y_0 = 0 \\ R = \frac{1}{1+r_L} \end{cases}$$

- The locus (the set of all points whose location satisfies one or more specified conditions) of the points generated by all impedances having normalized resistance r_L is a circle which:

- have its **center on the horizontal axis** ($y_0=0$) $\left(1 - \frac{r_L}{1+r_L}\right)^2 + 0 = \left(\frac{1}{1+r_L}\right)^2$
- passes through **$x=1, y=0$** point, whatever x_0, r_L $\left(0 - \frac{r_L}{1+r_L}\right)^2 = \left(\frac{1}{1+r_L}\right)^2 \leftrightarrow r_L = 1$
- have its radius between 0 and 1
 - tends to 0 for large r_L
 - tends to 1 for small r_L
- when r_L is 1 passes also through **origin**

The Smith Chart, resistance

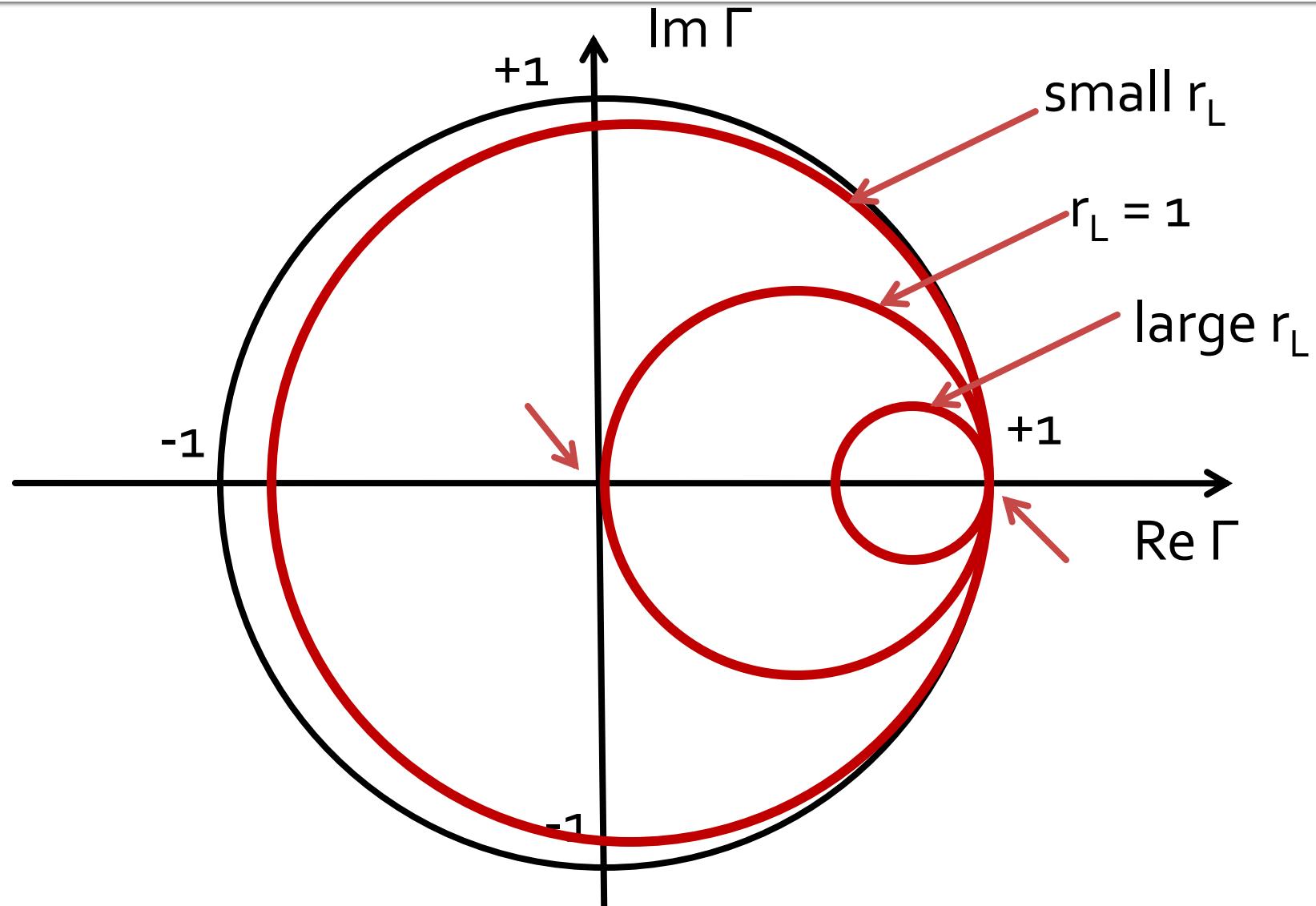

The Smith Chart, reactance


$$\begin{array}{l} \text{→ } (\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L} \right)^2 = \left(\frac{1}{x_L} \right)^2 \\ \text{→ } (x - x_0)^2 + (y - y_0)^2 = R^2 \end{array}$$

$$\left\{ \begin{array}{l} x_0 = 1 \\ y_0 = \frac{1}{x_L} \\ R = \frac{1}{x_L} \end{array} \right.$$


- The locus of the points generated by all impedances having normalized resistance x_L is a circle which:
 - have its **center on a line parallel with the vertical axis** ($x_0=1$)
 - passes through **$x=1, y=0$** point, whatever x_0, x_L
 - have its radius between 0 and ∞
 - tends to 0 for large $|x_L|$
 - tends to ∞ for small $|x_L|$
 - when x_L is **0** transforms itself in the **horizontal axis**
 - if $x_L > 0$ the circle is above the horizontal axis, otherwise is below it

$$0 + \left(0 - \frac{1}{x_L} \right)^2 = \left(\frac{1}{x_L} \right)^2$$


The Smith Chart, reactance

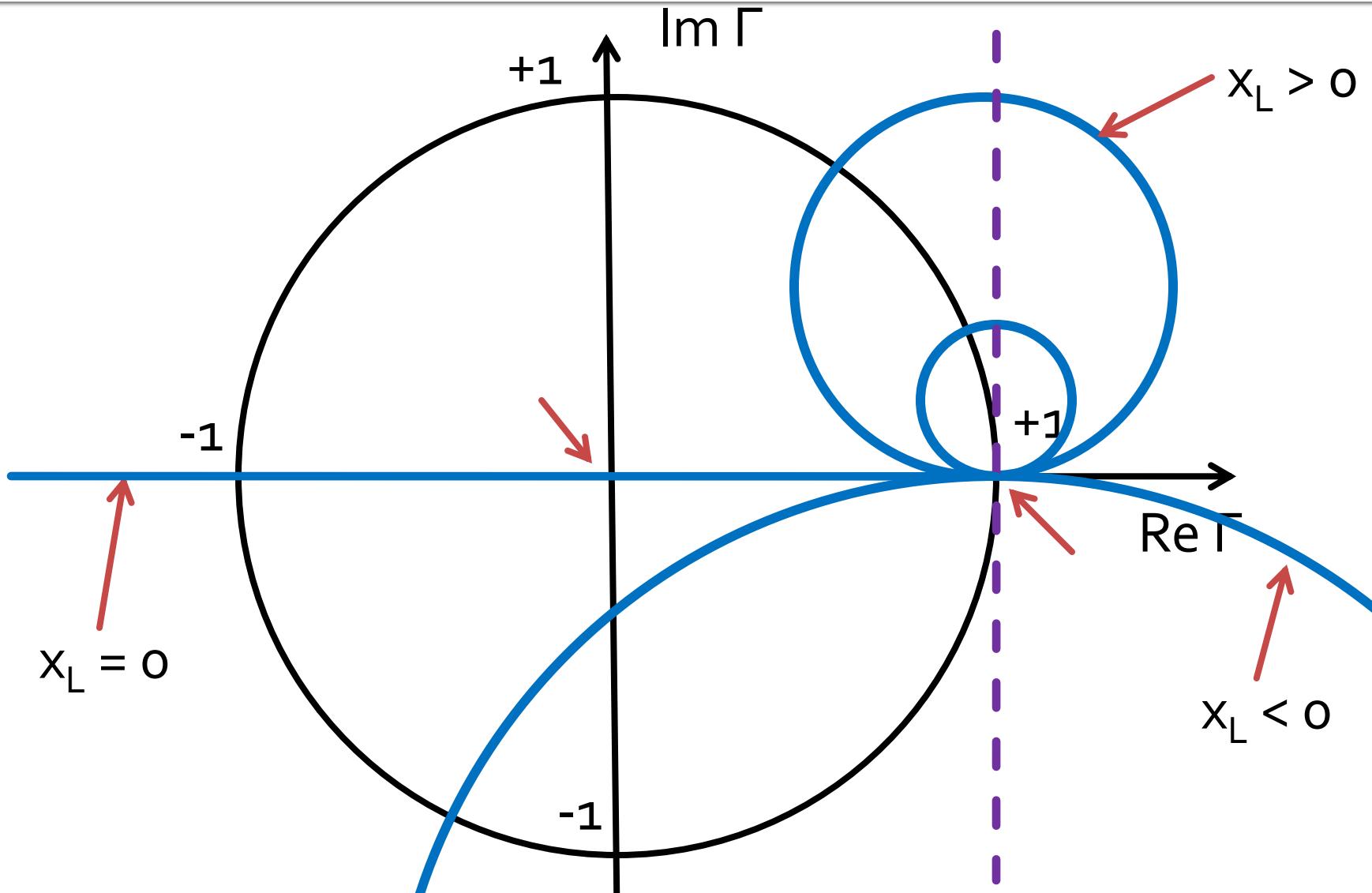

The Smith Chart, impedance

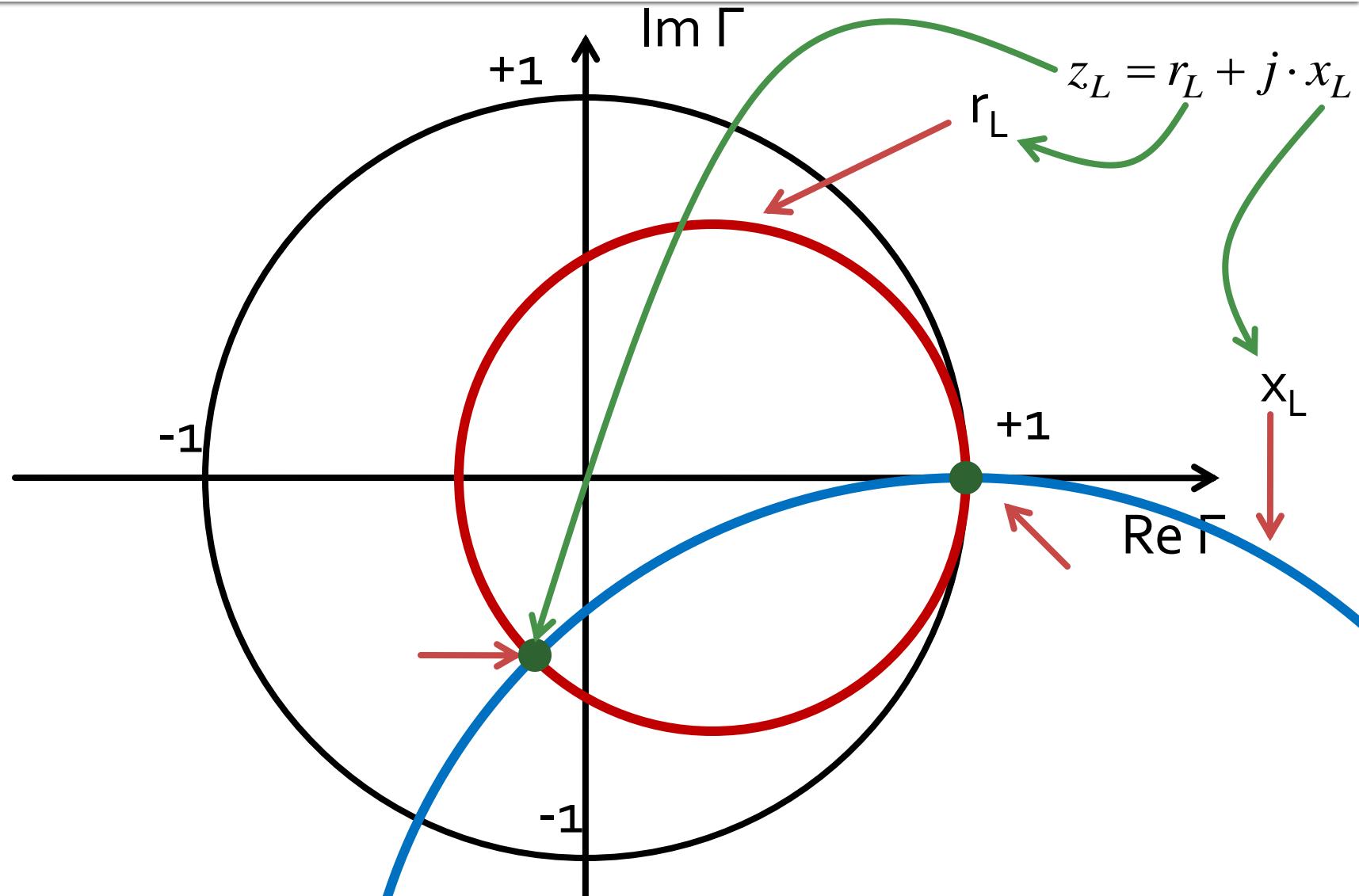

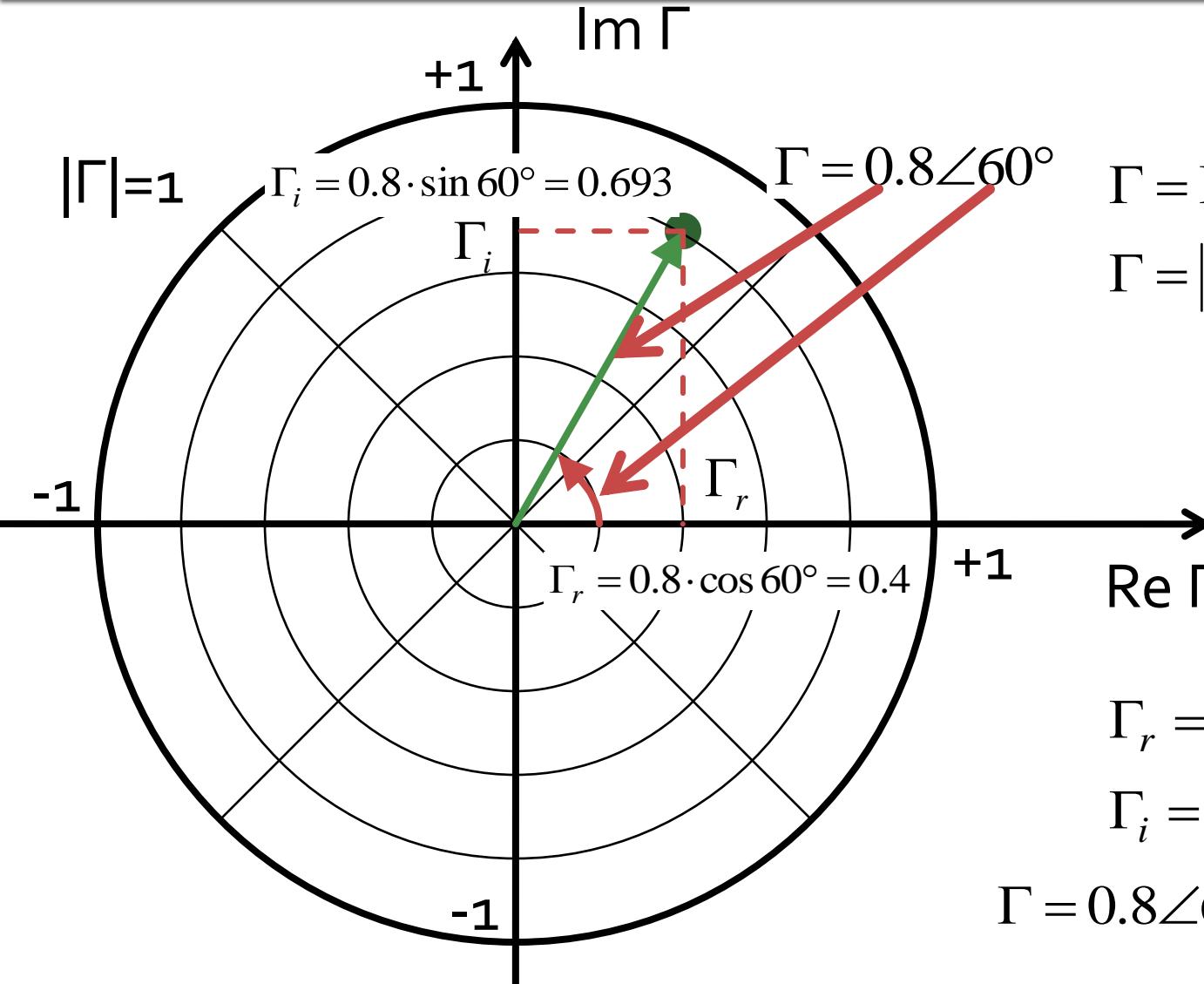The Smith Chart, reflection coefficient, Cartesian coordinate system



$$\Gamma = \Gamma_r + j \cdot \Gamma_i$$

$$\Gamma = |\Gamma| \cdot (\cos \theta + j \cdot \sin \theta)$$

$$\Gamma = |\Gamma| \cdot e^{j\theta}$$

$$\Gamma = |\Gamma| \angle \theta^\circ$$


$$\Gamma = 0.8 \angle 60^\circ$$

$$\Gamma_r = 0.8 \cdot \cos 60^\circ = 0.4$$

$$\Gamma_i = 0.8 \cdot \sin 60^\circ = 0.693$$

$$\Gamma = 0.8 \angle 60^\circ = 0.4 + j \cdot 0.693$$

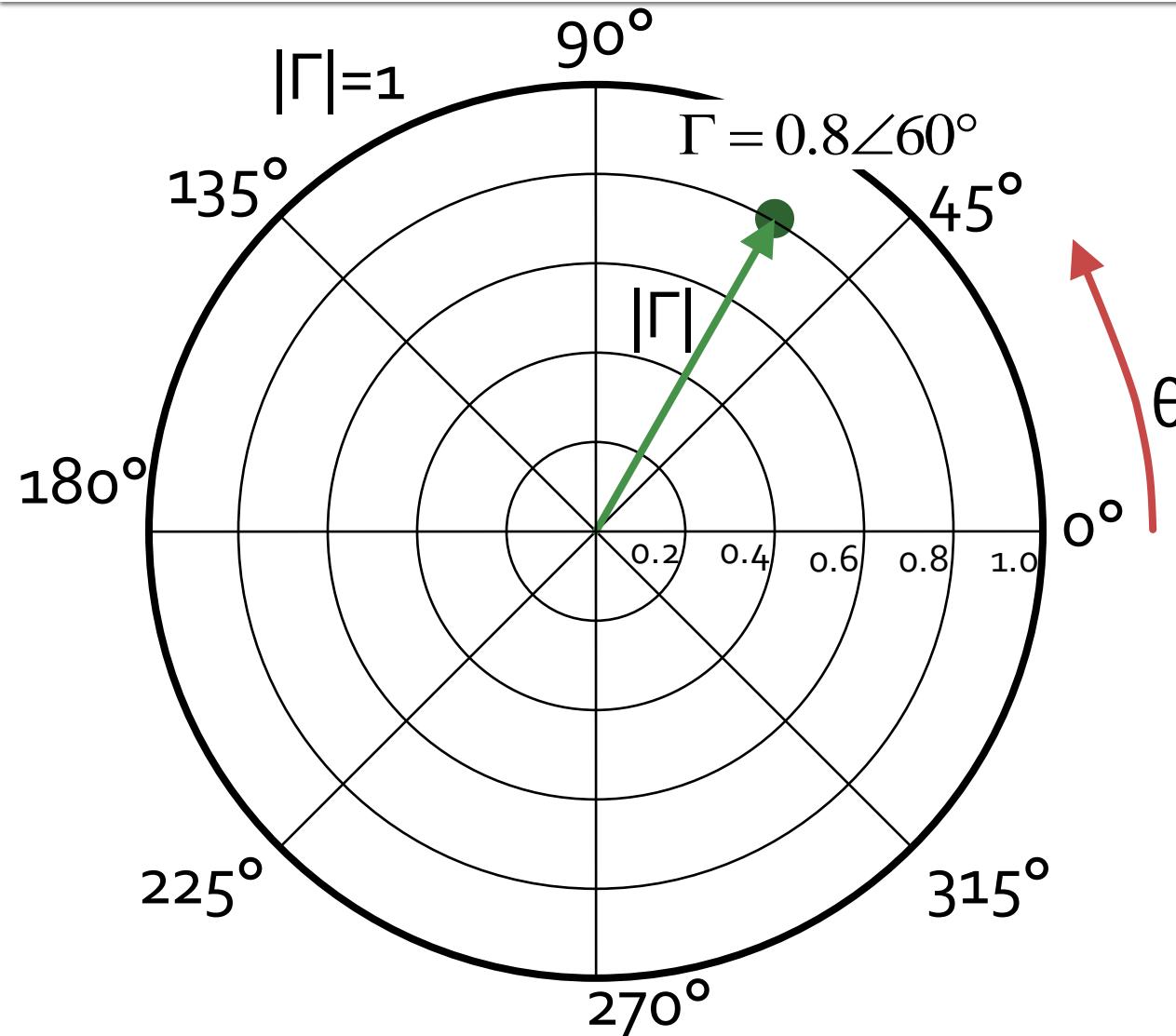The Smith Chart, reflection coefficient, Polar coordinate system



$$\Gamma = \Gamma_r + j \cdot \Gamma_i$$

$$\Gamma = |\Gamma| \cdot (\cos \theta + j \cdot \sin \theta)$$

$$\Gamma = |\Gamma| \cdot e^{j\theta}$$


$$\Gamma = |\Gamma| \angle \theta^\circ$$

$$\Gamma = 0.8 \angle 60^\circ$$

$$\Gamma_r = 0.8 \cdot \cos 60^\circ = 0.4$$

$$\Gamma_i = 0.8 \cdot \sin 60^\circ = 0.693$$

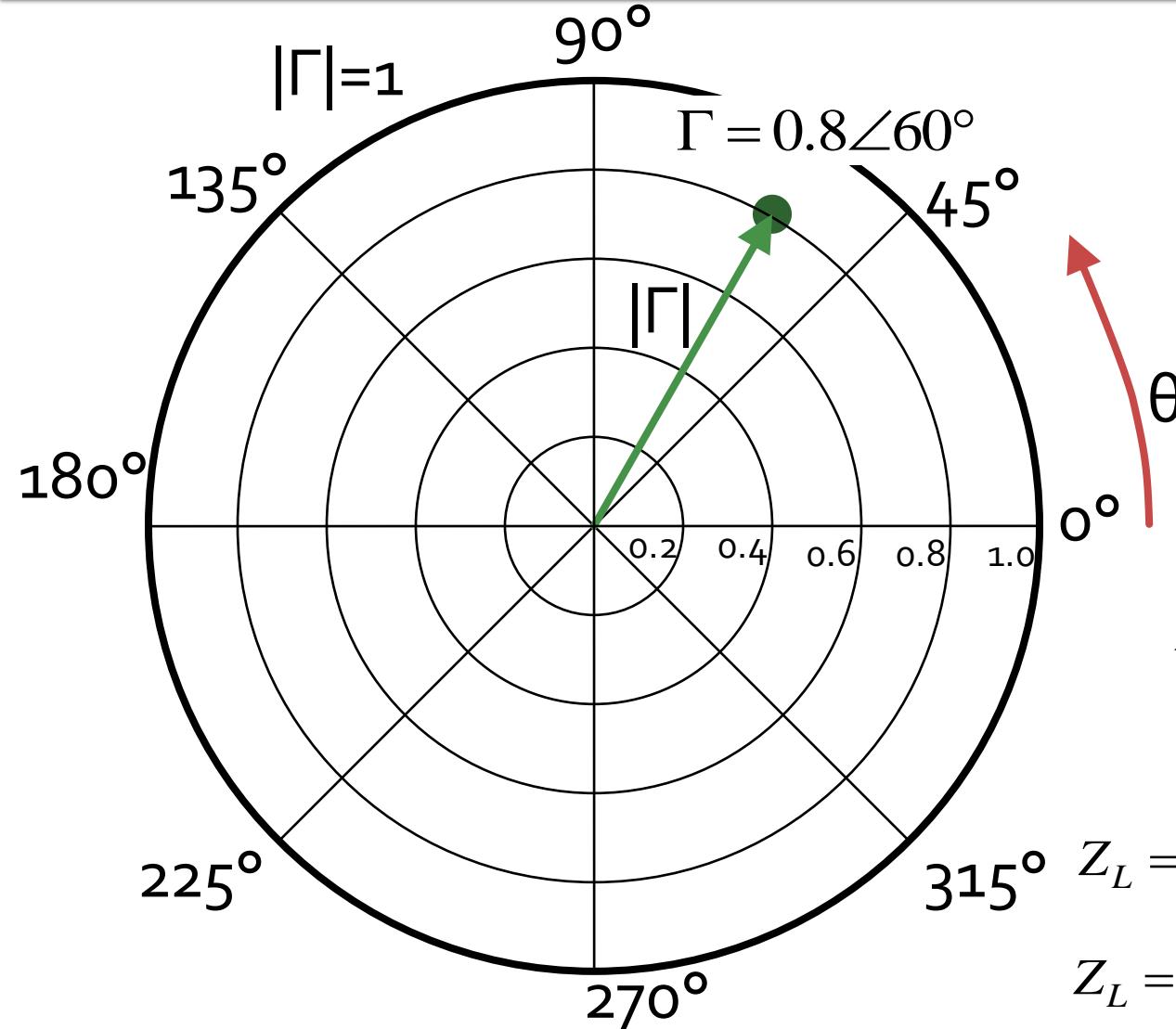The Smith Chart, reflection coefficient, impedance



$$\Gamma = |\Gamma| \cdot e^{j\theta}$$

$$\Gamma = |\Gamma| \angle \theta^\circ$$

$$\Gamma = 0.8 \angle 60^\circ$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$

$$z_L = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + 0.8 \angle 60^\circ}{1 - 0.8 \angle 60^\circ}$$


$$z_L = 0.429 + j \cdot 1.65$$

$$Z_L = Z_0 \cdot \frac{1 + \Gamma}{1 - \Gamma} = 50\Omega \cdot \frac{1 + 0.8 \angle 60^\circ}{1 - 0.8 \angle 60^\circ}$$


$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

Equivalence


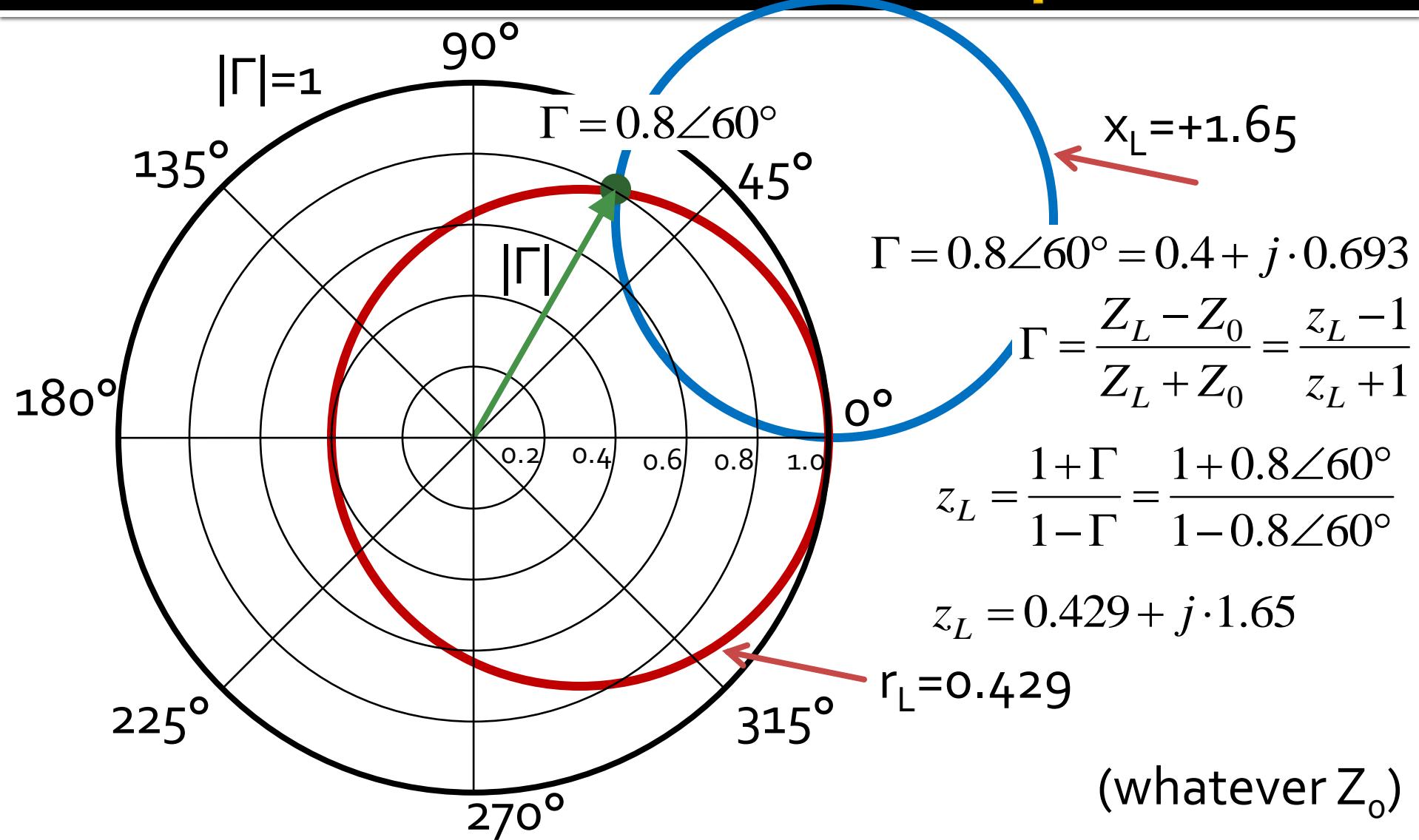
reflection coefficient \Leftrightarrow impedance



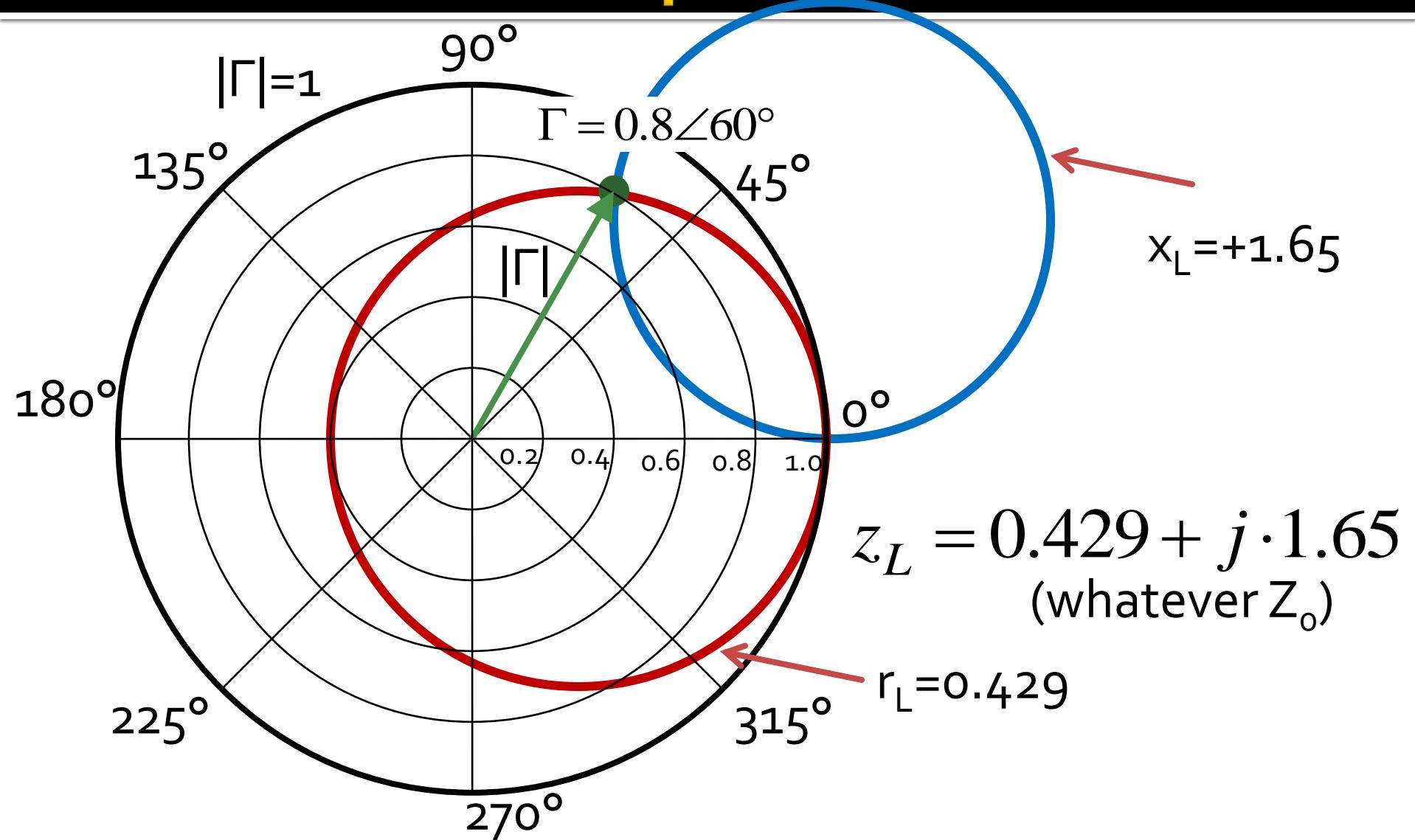The Smith Chart, reflection coefficient \Leftrightarrow impedance



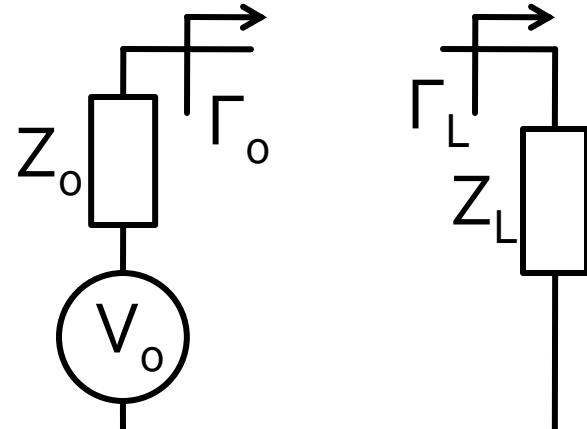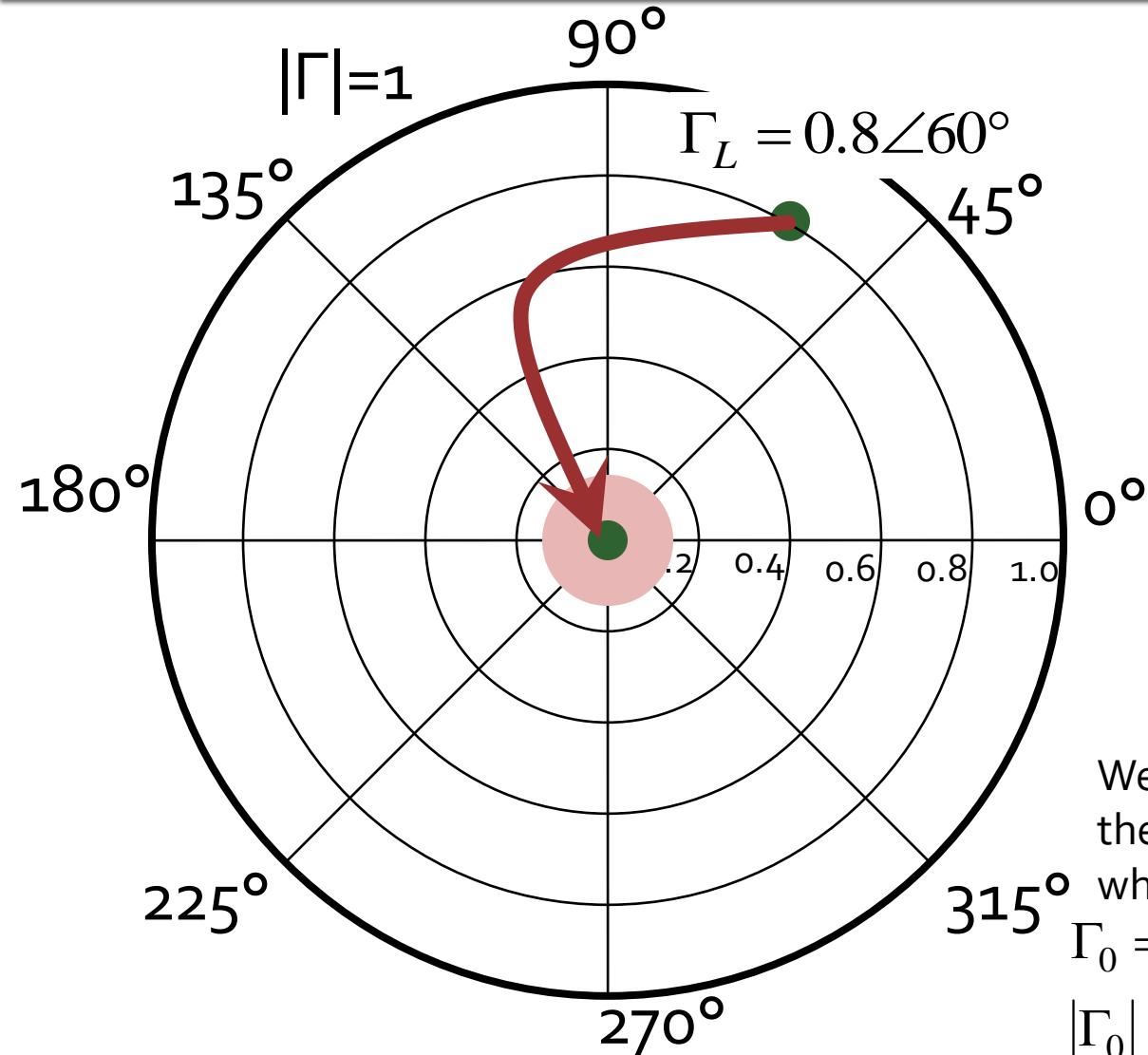The Smith Chart, reflection coefficient, matching



Matching Z_L load to Z_0 source.
We normalize Z_L over Z_0

$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

$$z_L = 0.429 + j \cdot 1.65$$

$$\Gamma_L = 0.8∠60^\circ$$



We must move the point denoting the reflection coefficient in the area where with a Z_0 source we have:
 $\Gamma_0 = 0$ perfect match

$|\Gamma_0| \leq \Gamma_m$ "good enough" match





Example

Laboratory 1

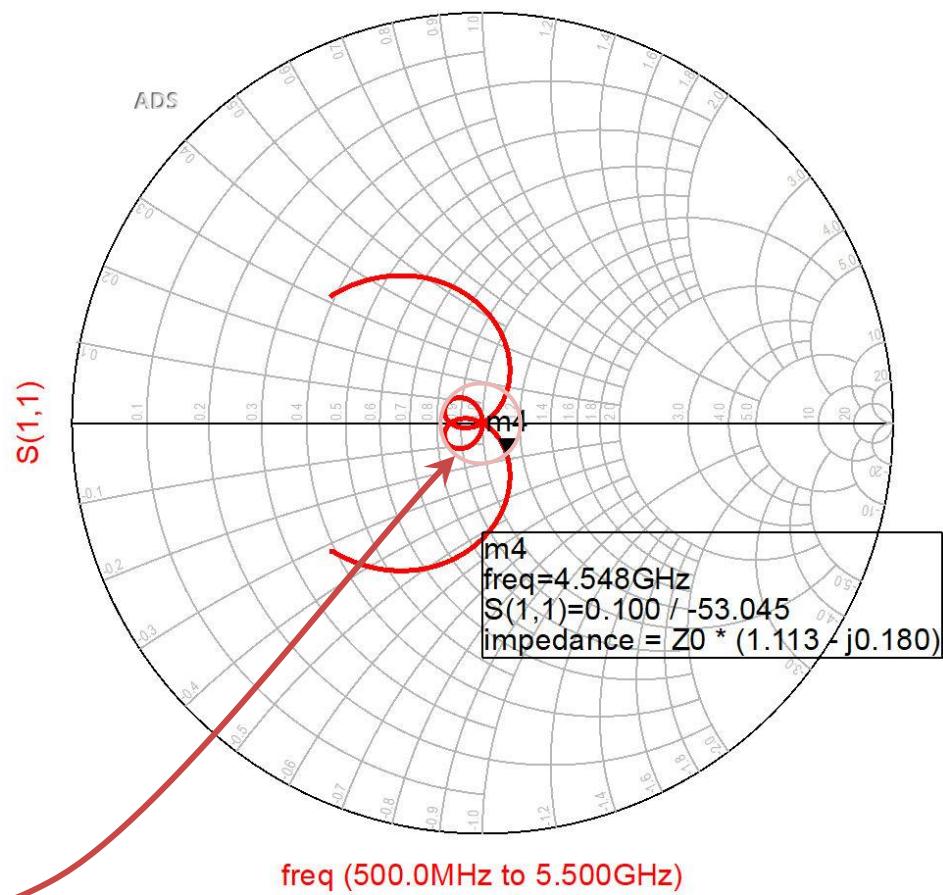
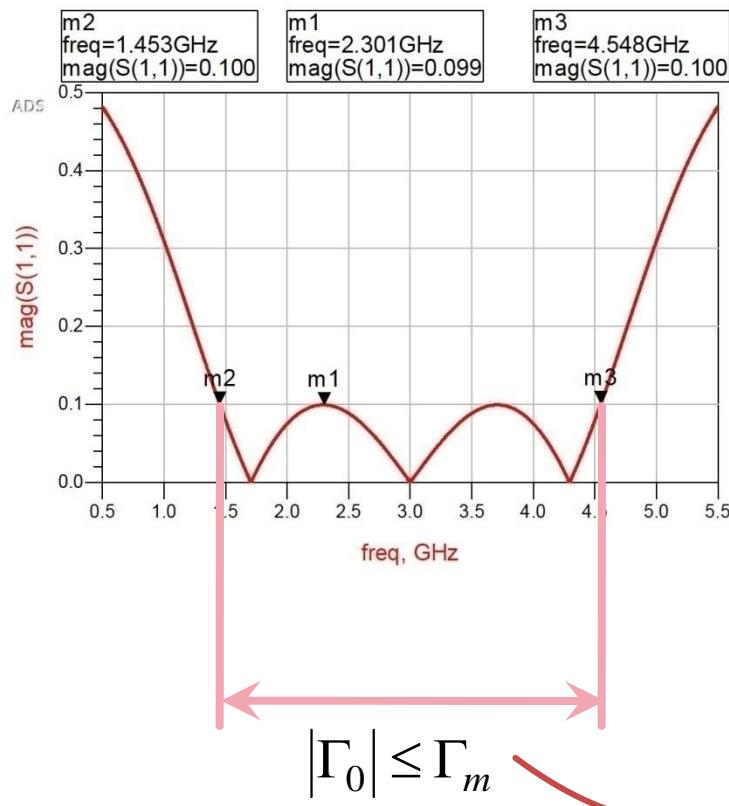


Example

Laboratory 1

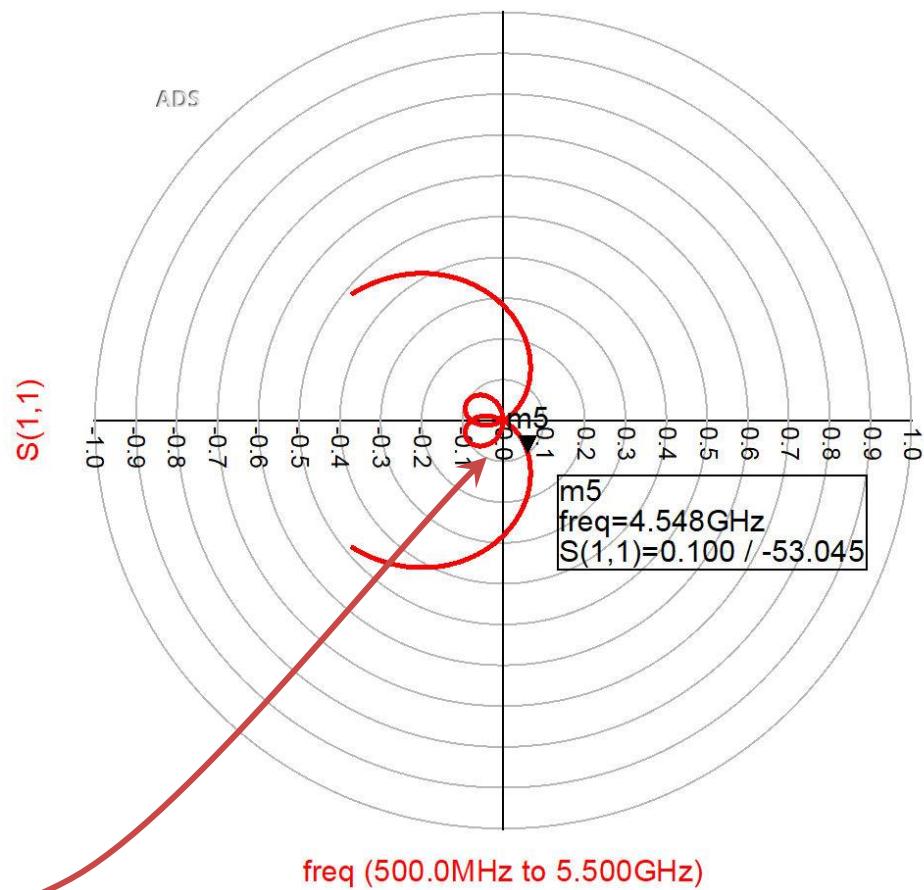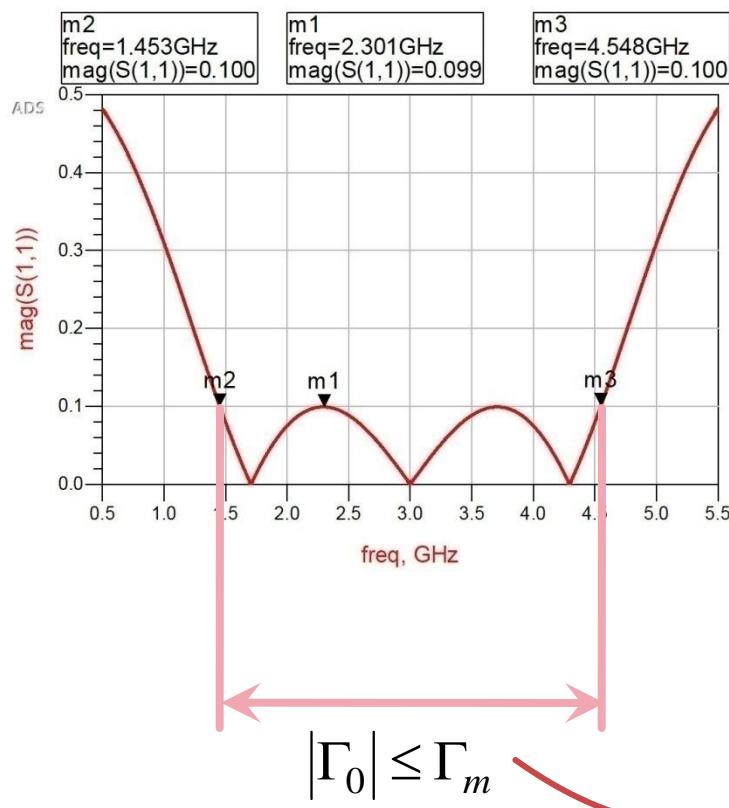

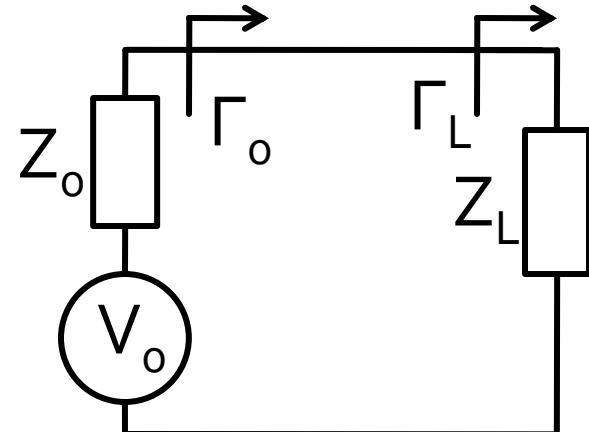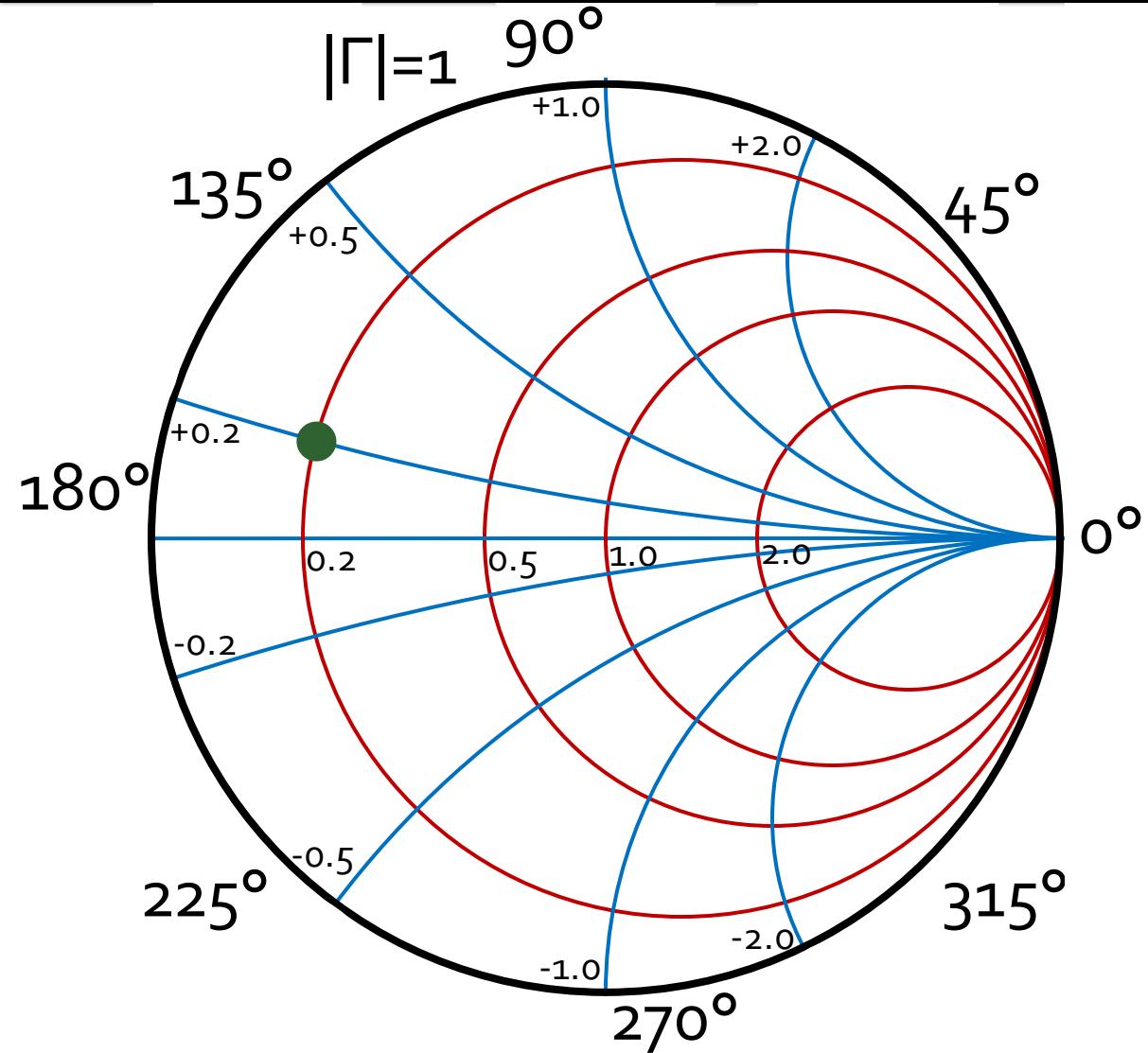The Smith Chart, impedance/reflection coefficient





$$Z_0 = 50\Omega$$

$$Z_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = 0.2 + j \cdot 0.2$$

$$\Gamma_L = \Gamma_0 = 0.678 \angle 156.5^\circ$$

The Smith Chart, series reactance

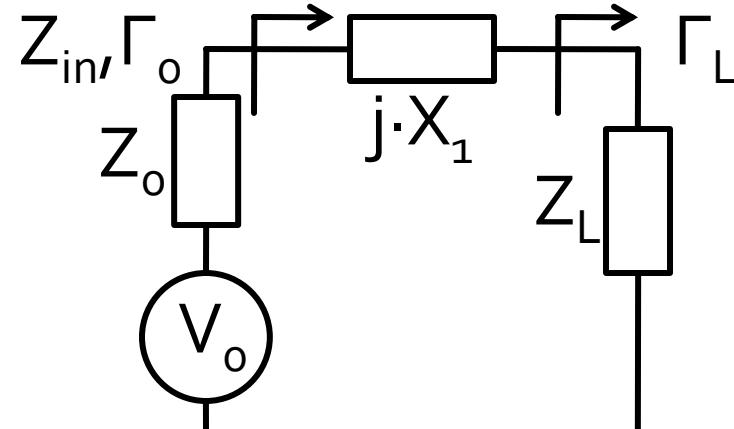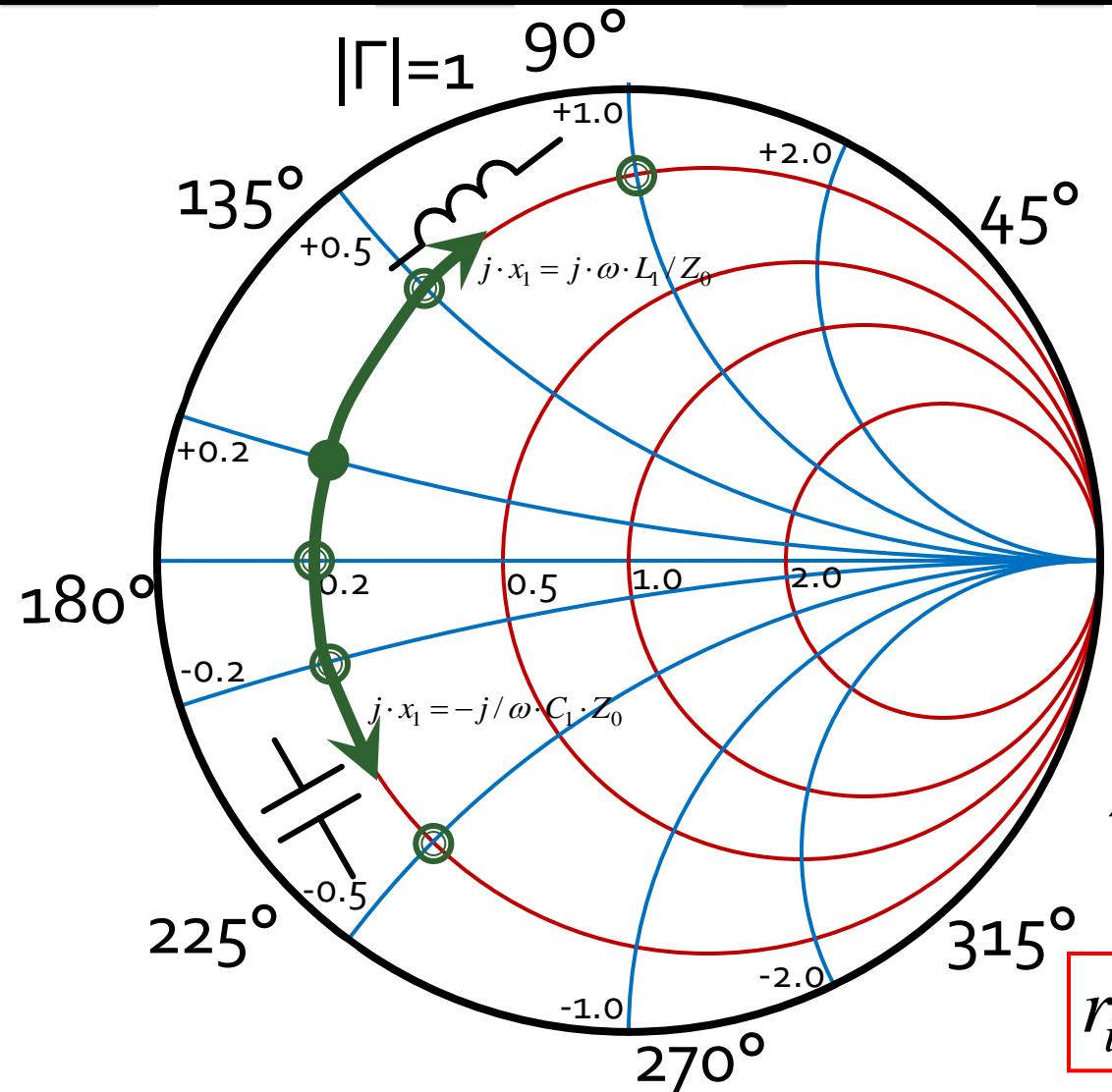

$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$

$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_L + j \cdot X_1 = R_L + j \cdot (X_L + X_1)$$



$$z_{in} = r_L + j \cdot (x_L + x_1)$$

$$r_{in} = r_L$$

$$j \cdot x_1 = j \cdot \omega \cdot L_1 / Z_0 > 0$$

$$j \cdot x_1 = -j / \omega \cdot C_1 \cdot Z_0 < 0$$

ADS, Smith Chart, series reactance

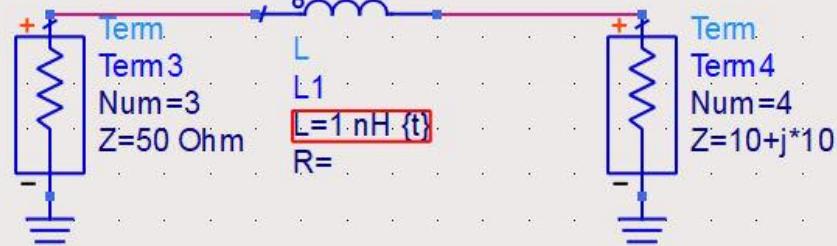
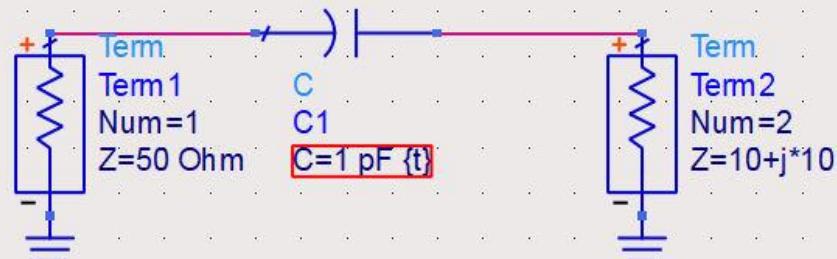


S-PARAMETERS


S_Param

SP1



Freq=1.0 GHz

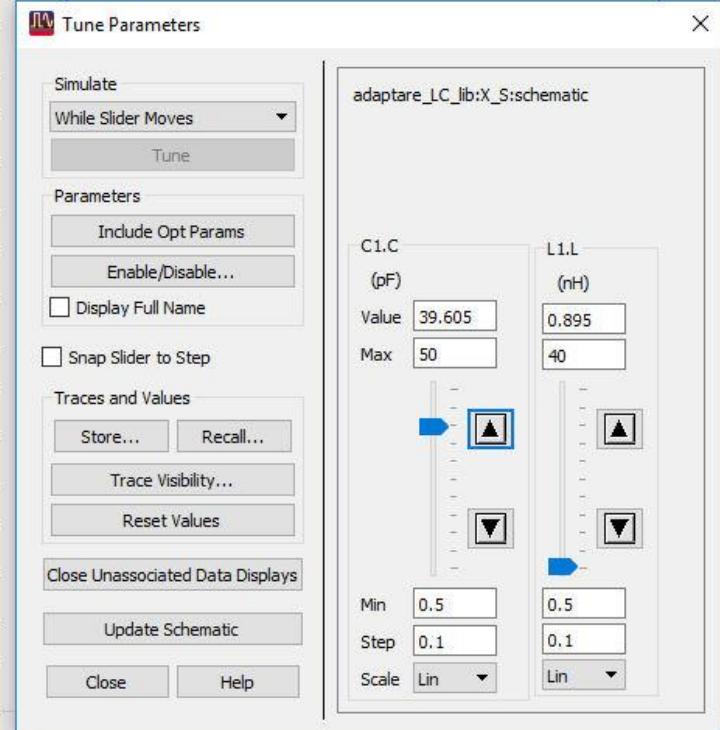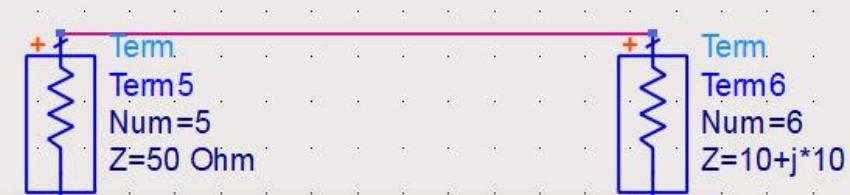

ADS, Smith Chart, series reactance

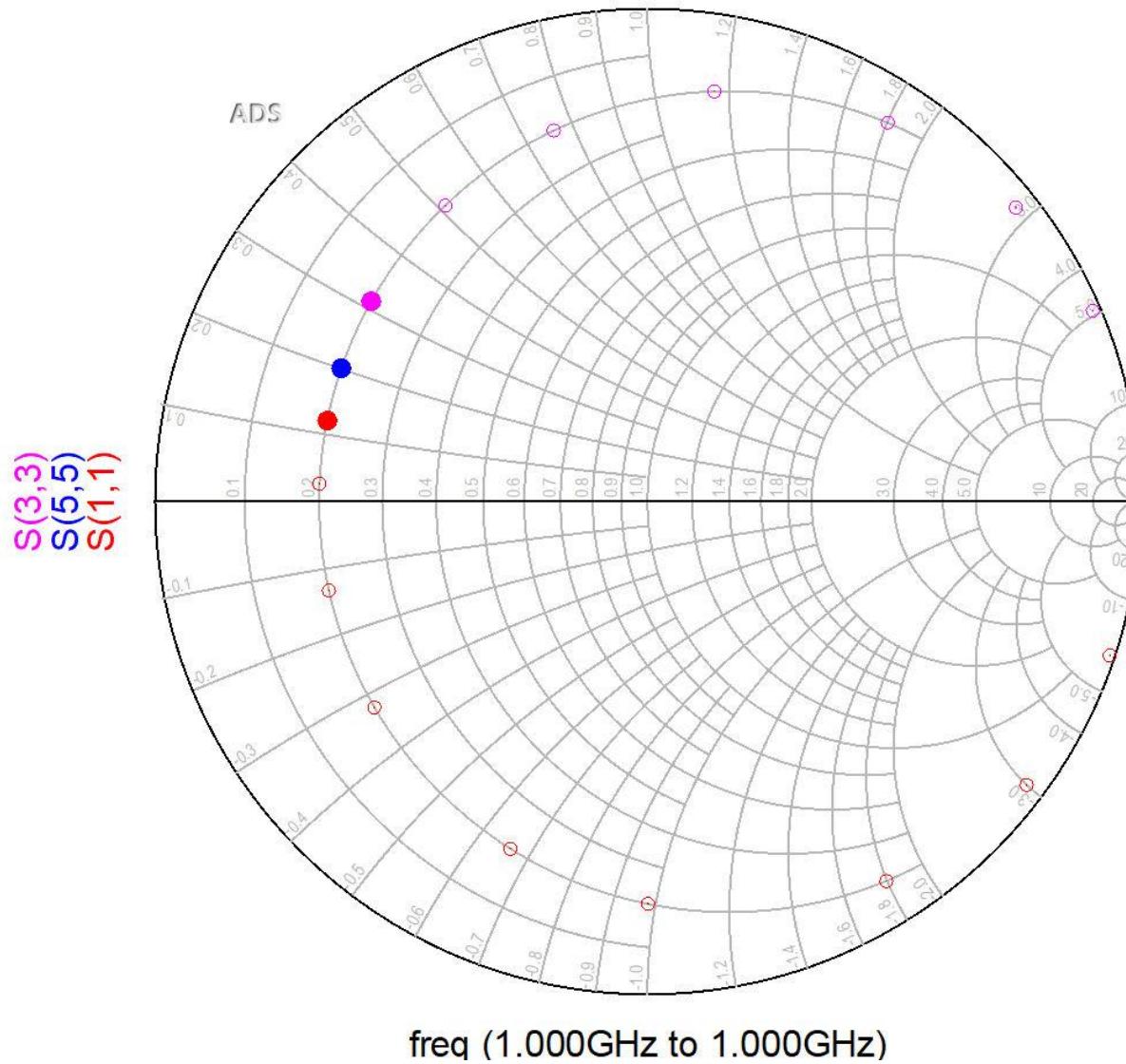

The Smith Chart, series resistance

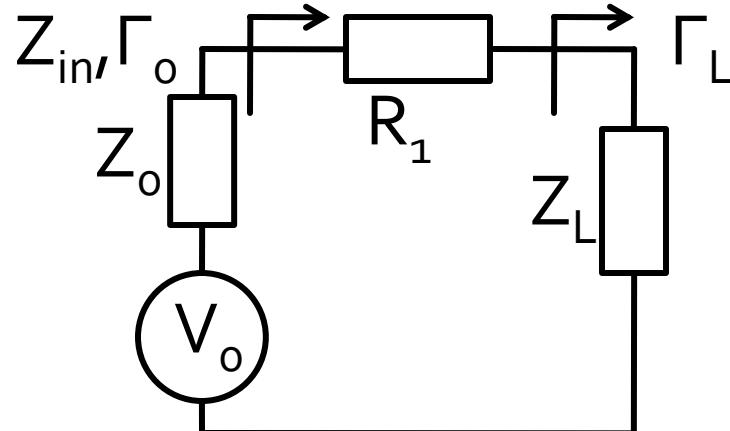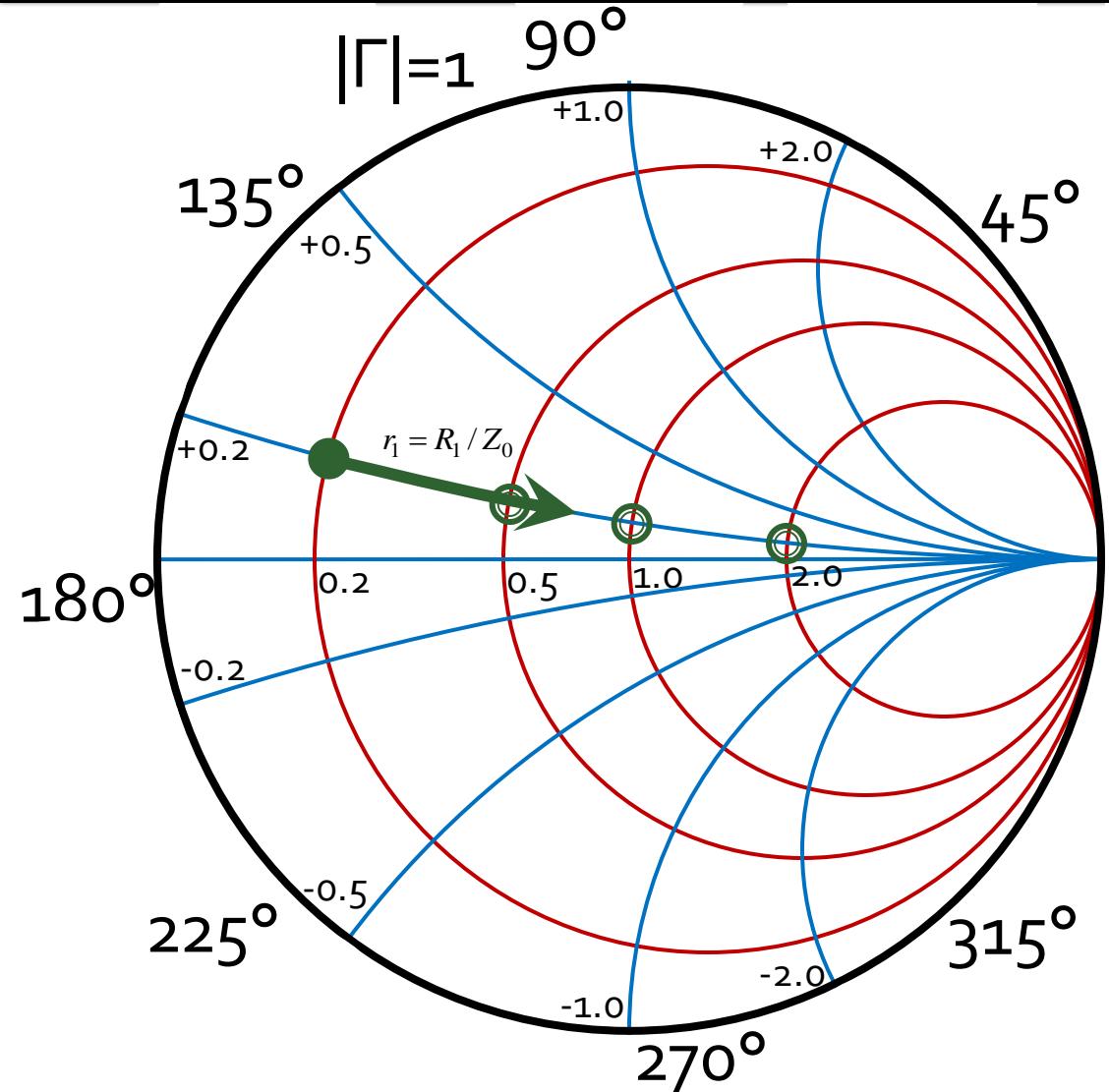

$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$

$$\Gamma_L = 0.678 \angle 156.5^\circ$$


$$Z_{in} = Z_L + R_1 = (R_L + R_1) + j \cdot X_L$$

$$z_{in} = z_L + r_1 = (r_L + r_1) + j \cdot x_L$$



$x_{in} = x_L$

$$r_{in} = r_L + R_1 / Z_0$$

ADS, Smith Chart, series resistance

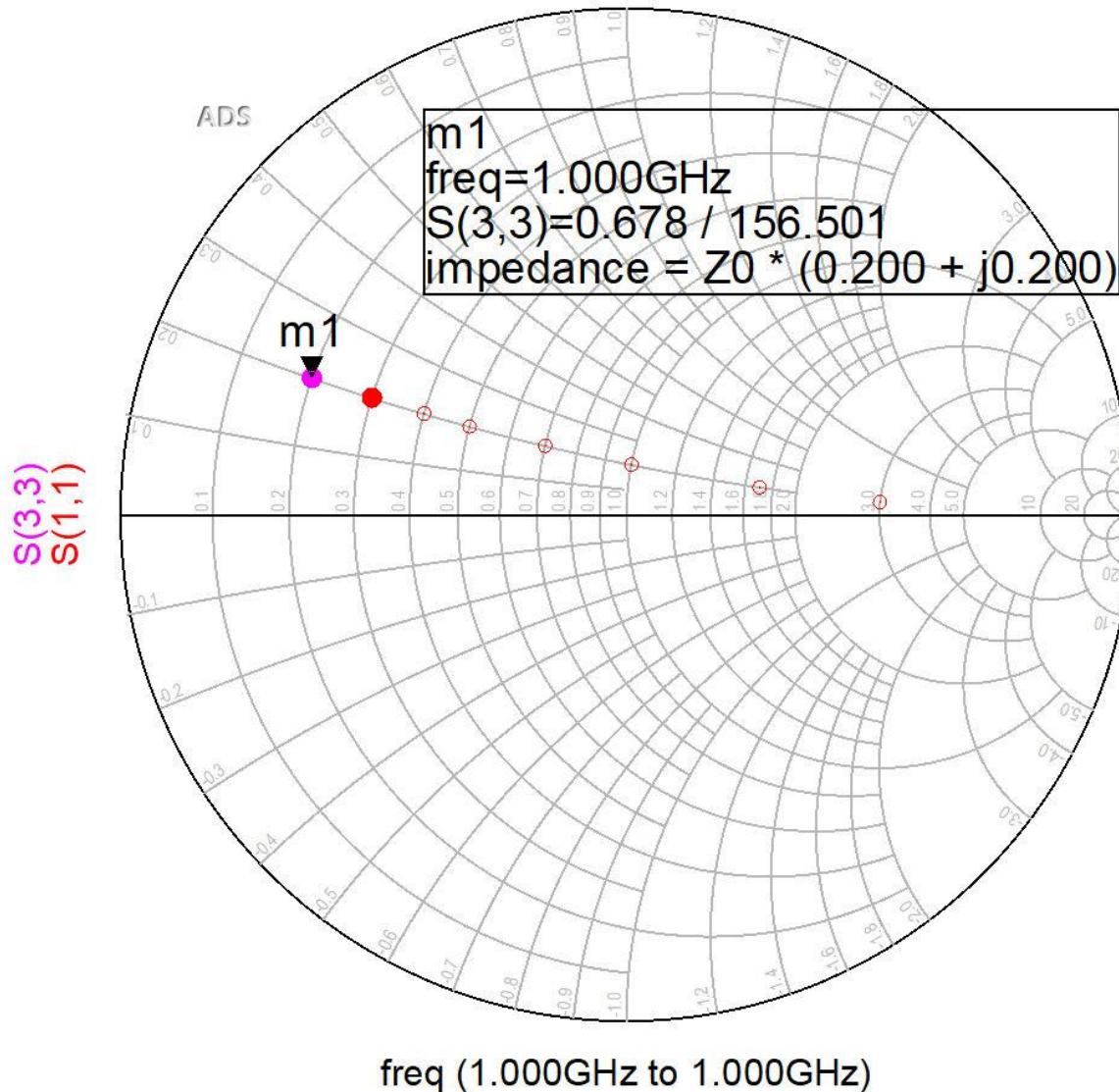

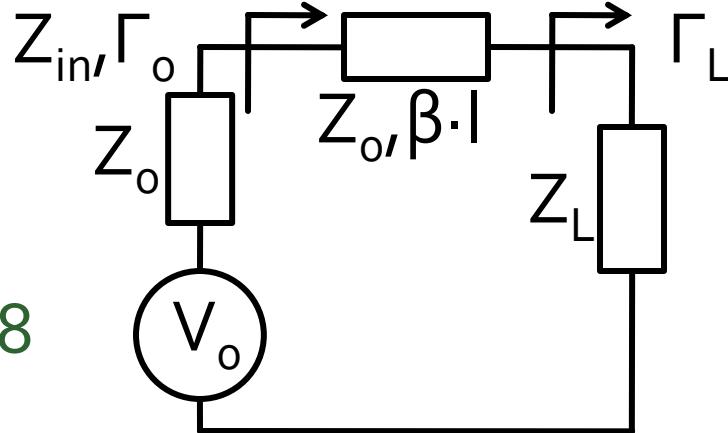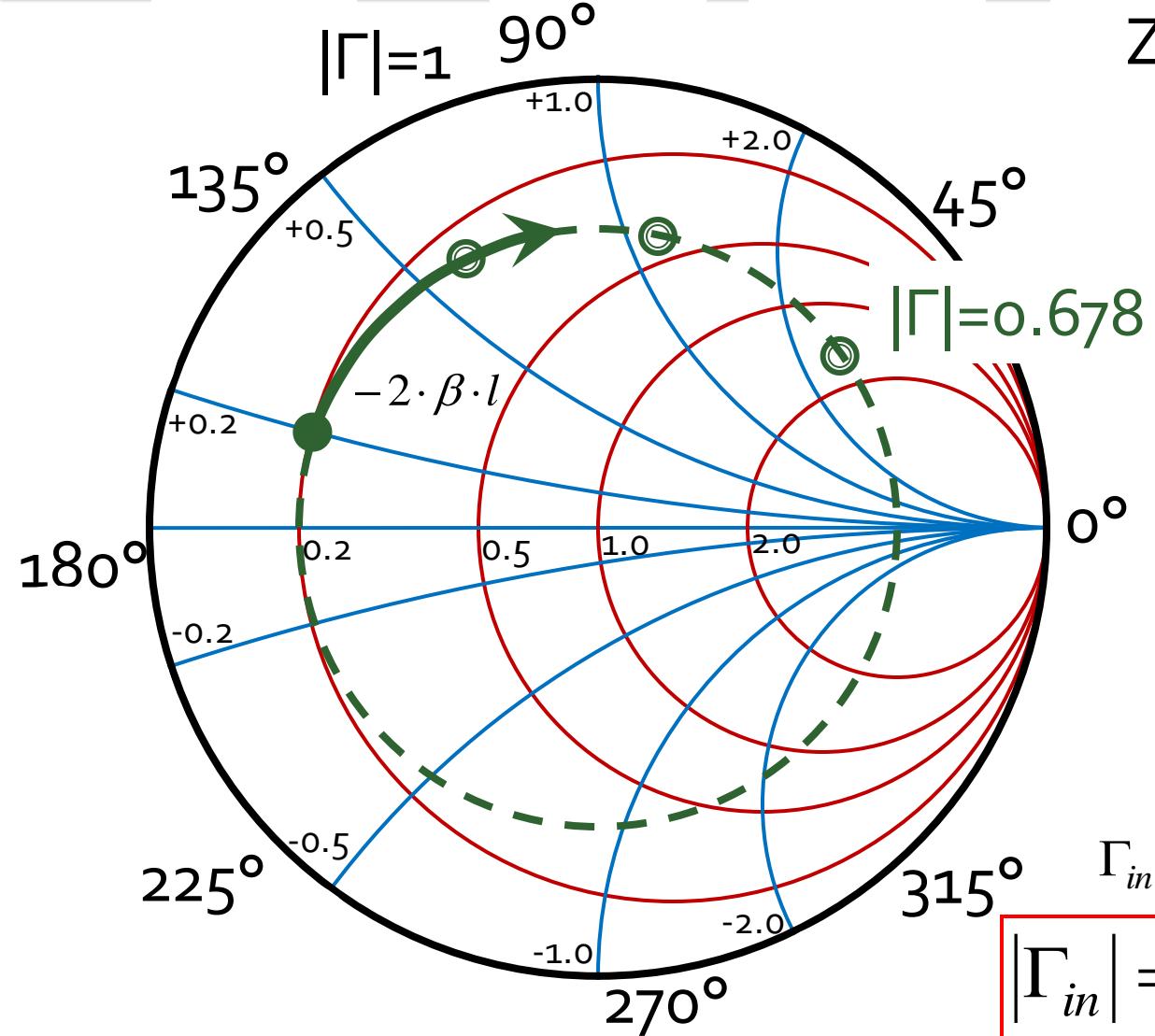The Smith Chart, series transmission line, Z_o



$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$

$$\Gamma_L = 0.678 \angle 156.5^\circ$$


$$Z_{in} = Z_0 \cdot \frac{1 + \Gamma_L \cdot e^{-2j\beta l}}{1 - \Gamma_L \cdot e^{-2j\beta l}}$$

$$\Gamma_{in} = \Gamma_L \cdot e^{-2j\beta l}$$


$$|\Gamma_{in}| = |\Gamma_L|$$

$$\arg(\Gamma_{in}) = \arg(\Gamma_L) - 2 \cdot \beta l$$

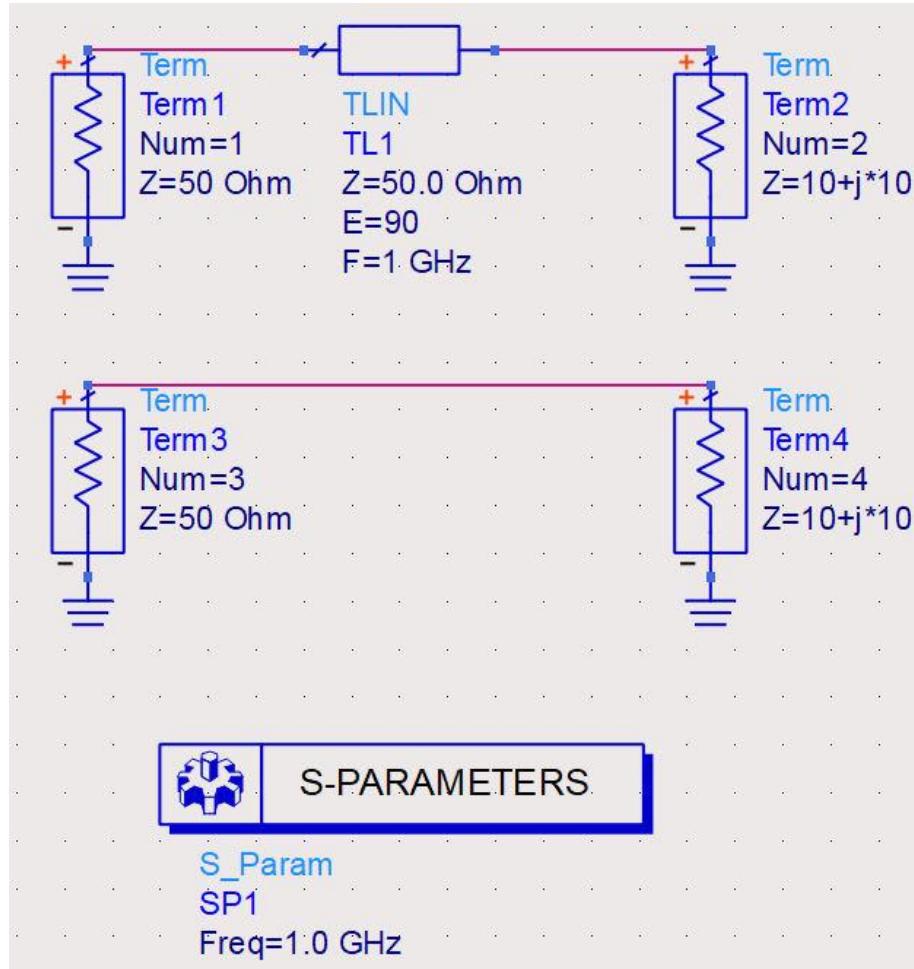
ADS, Smith Chart, series transmission line



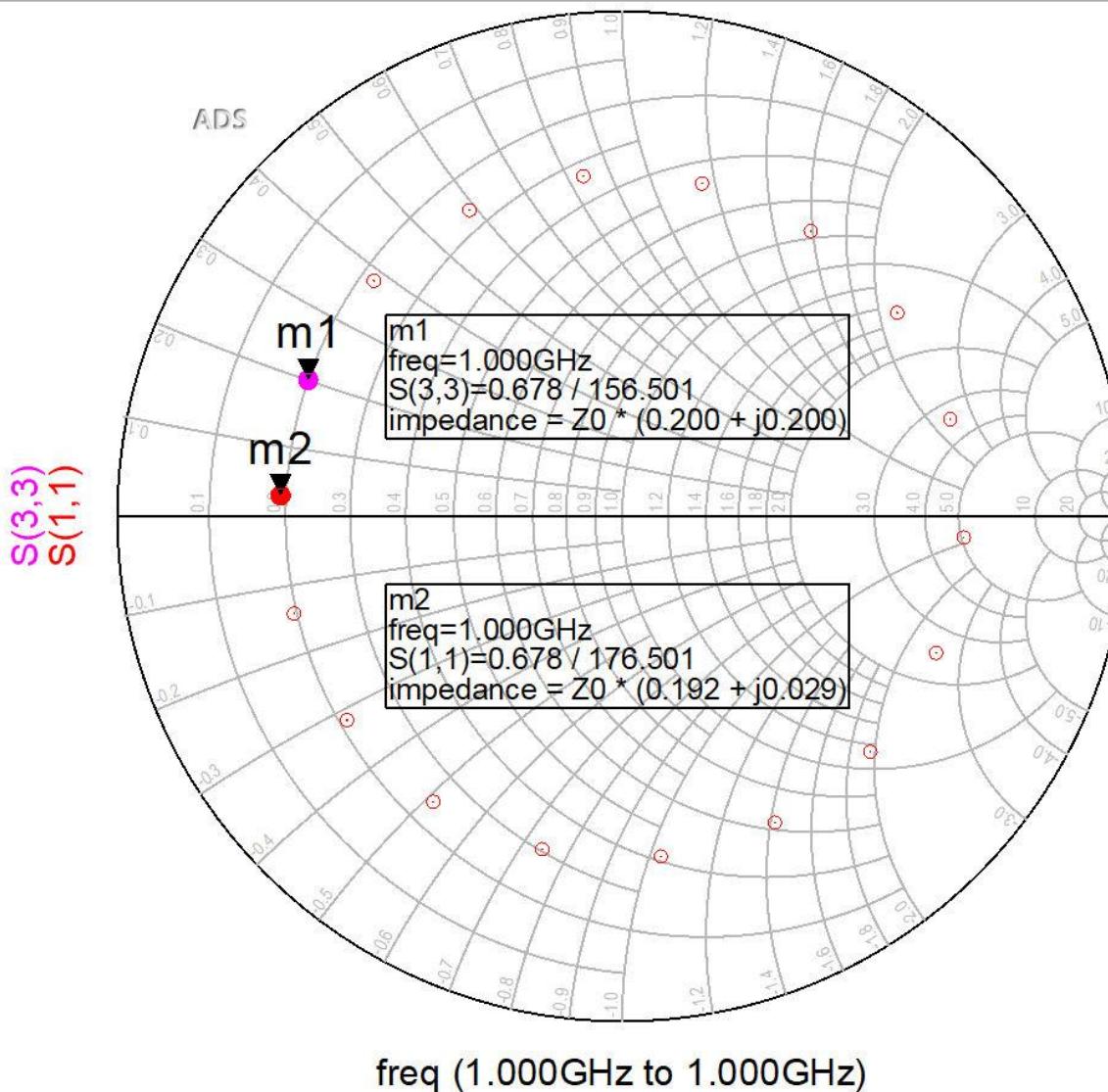
ADS, Smith Chart, series transmission line



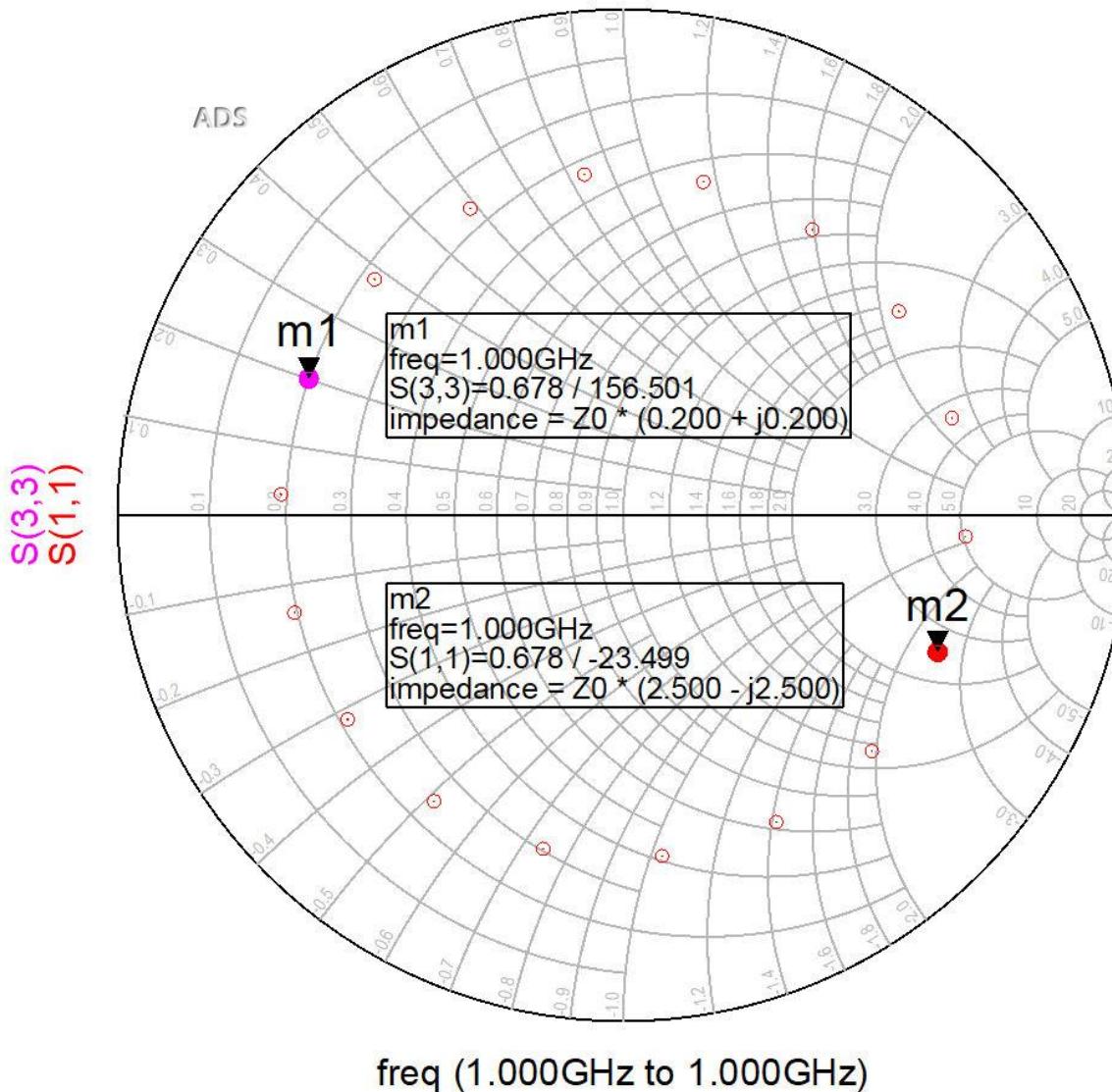
ADS, Smith Chart, series transmission line, E=90°



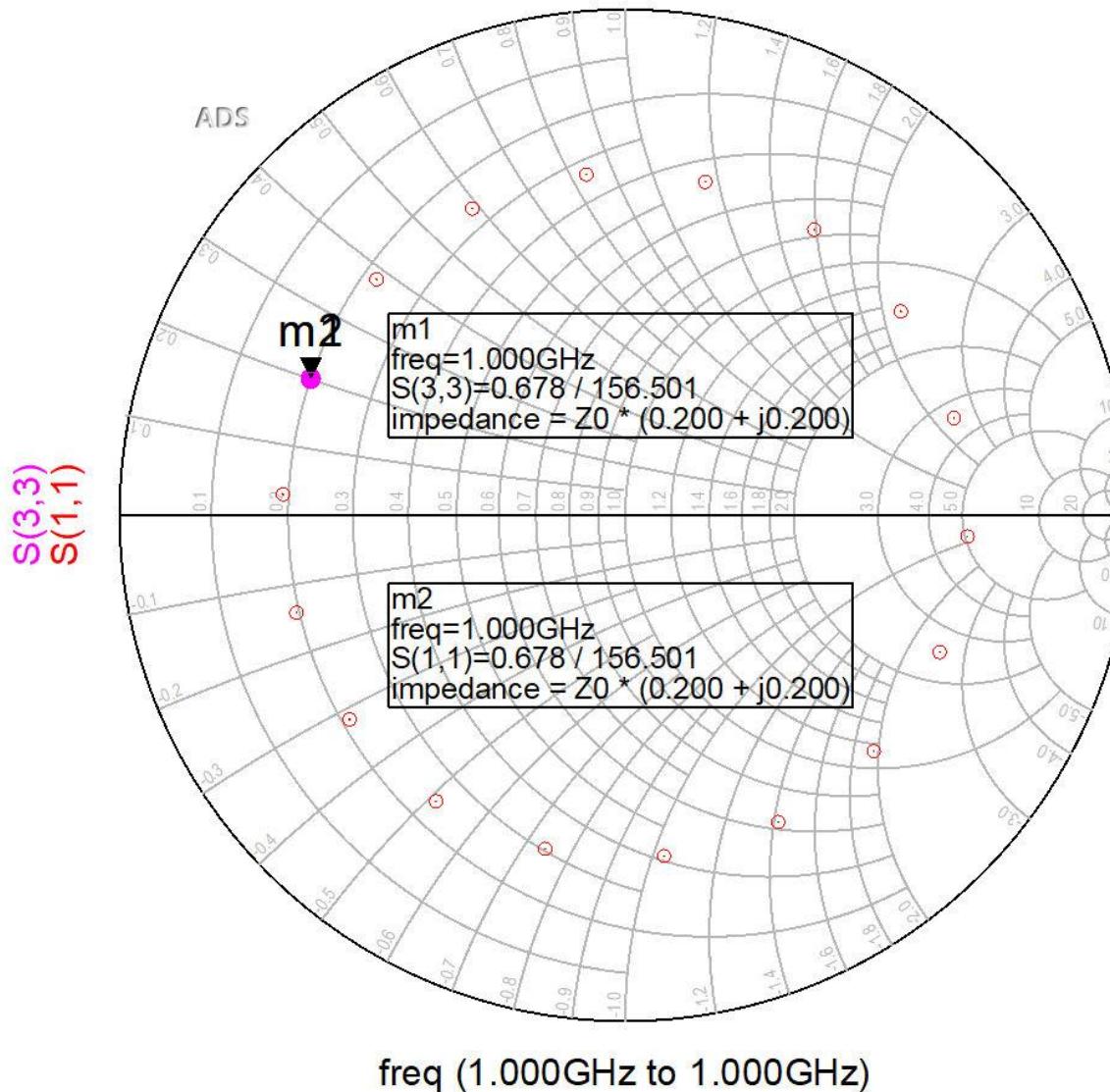
ADS, Smith Chart, series transmission line, E=180°



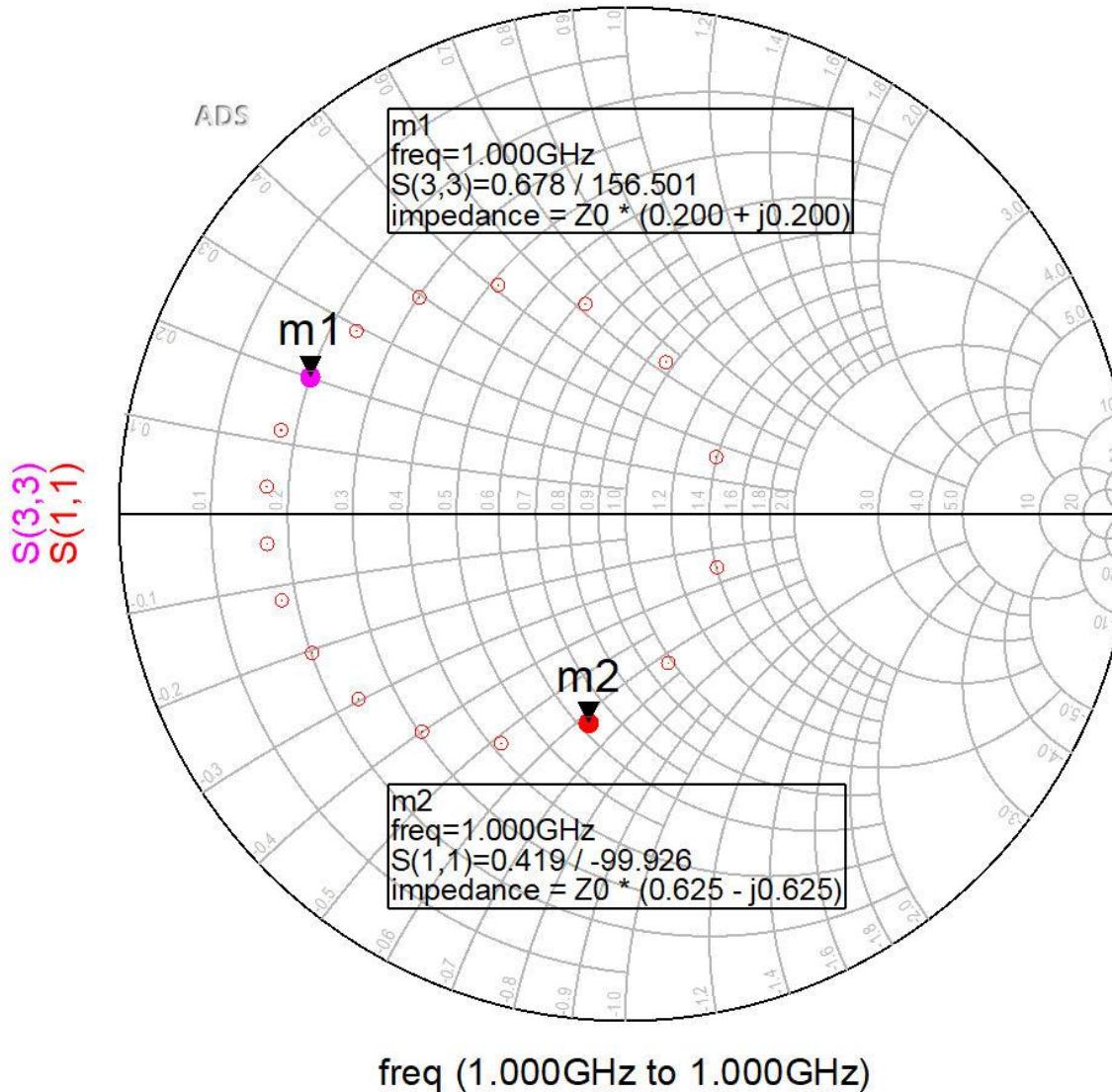ADS, Smith Chart, series transmission line, $Z=25\Omega \neq Z_0$



The Admittance Smith Chart

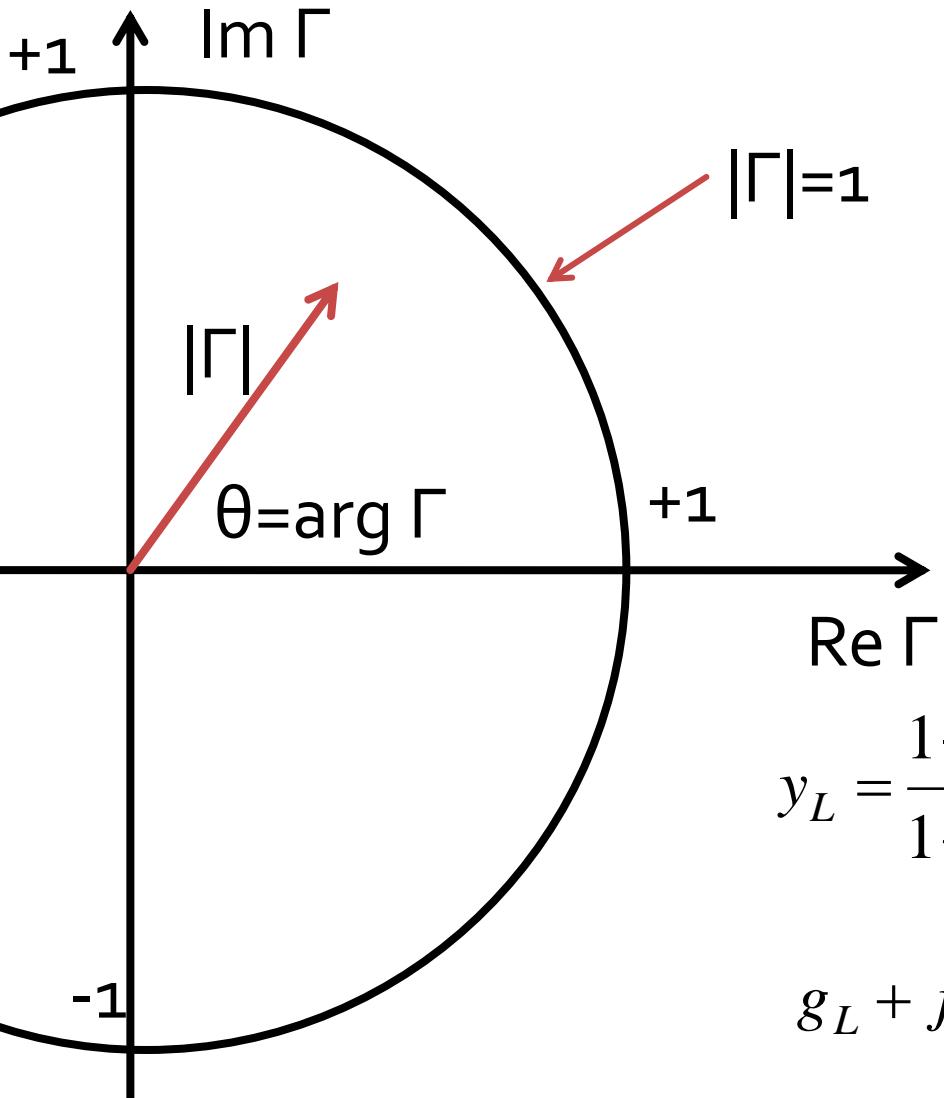

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1} = |\Gamma| \cdot e^{j\theta}$$


$$\Gamma = \Gamma_r + j \cdot \Gamma_i$$

$$z_L = \frac{1 + |\Gamma| \cdot e^{j\theta}}{1 - |\Gamma| \cdot e^{j\theta}} = r_L + j \cdot x_L$$

$$y_L = \frac{1 - |\Gamma| \cdot e^{j\theta}}{1 + |\Gamma| \cdot e^{j\theta}} = \frac{1}{r_L + j \cdot x_L} = g_L + j \cdot b_L$$

$$g_L + j \cdot b_L = \frac{(1 - \Gamma_r) - j \cdot \Gamma_i}{(1 + \Gamma_r) + j \cdot \Gamma_i}$$

The Admittance Smith Chart

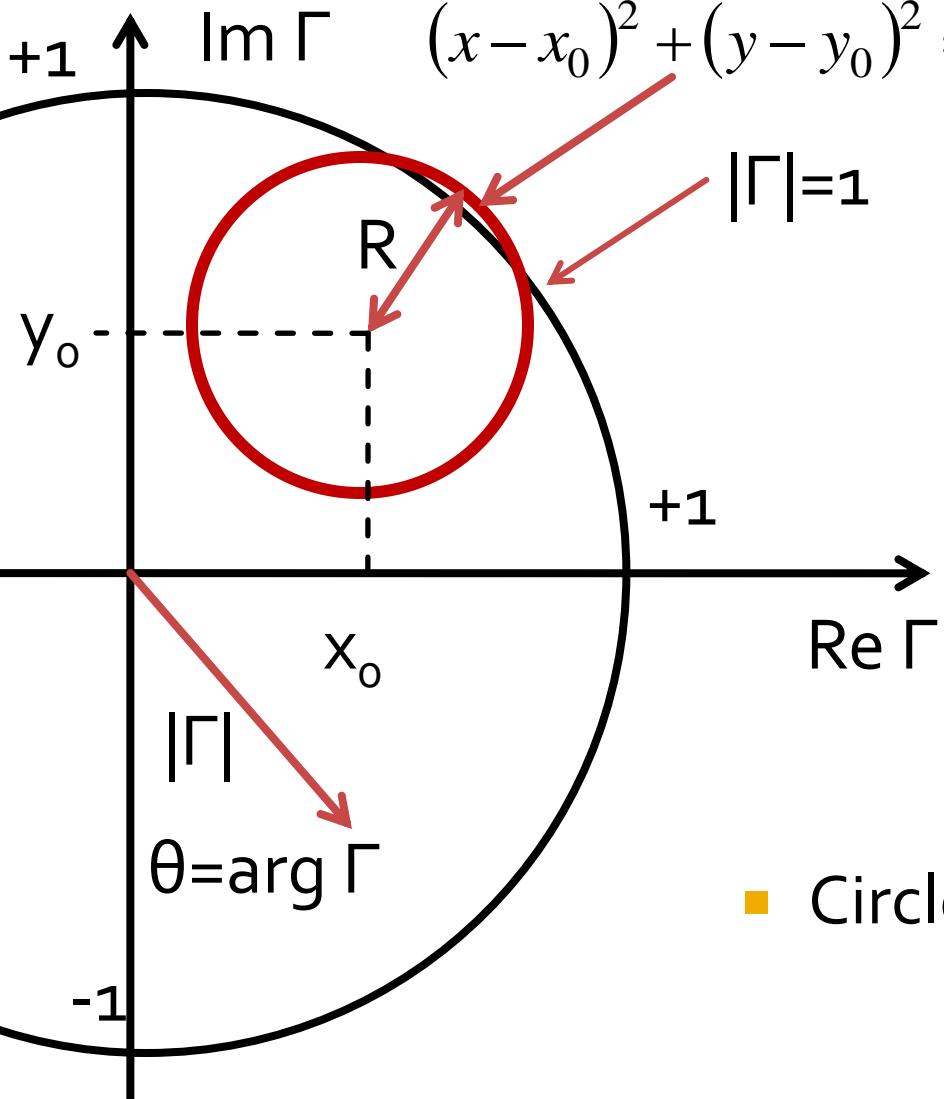

$$(x - x_0)^2 + (y - y_0)^2 = R^2$$

$$g_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 + \Gamma_r)^2 + \Gamma_i^2}$$

$$b_L = \frac{-2 \cdot \Gamma_i}{(1 + \Gamma_r)^2 + \Gamma_i^2}$$

- Rearranged


$$\left(\Gamma_r + \frac{g_L}{1 + g_L} \right)^2 + \Gamma_i^2 = \left(\frac{1}{1 + g_L} \right)^2$$

$$(\Gamma_r + 1)^2 + \left(\Gamma_i + \frac{1}{b_L} \right)^2 = \left(\frac{1}{b_L} \right)^2$$


- Circles in the (Γ_r, Γ_i) complex plane

$$(x - x_0)^2 + (y - y_0)^2 = R^2$$


The Smith Chart, conductance

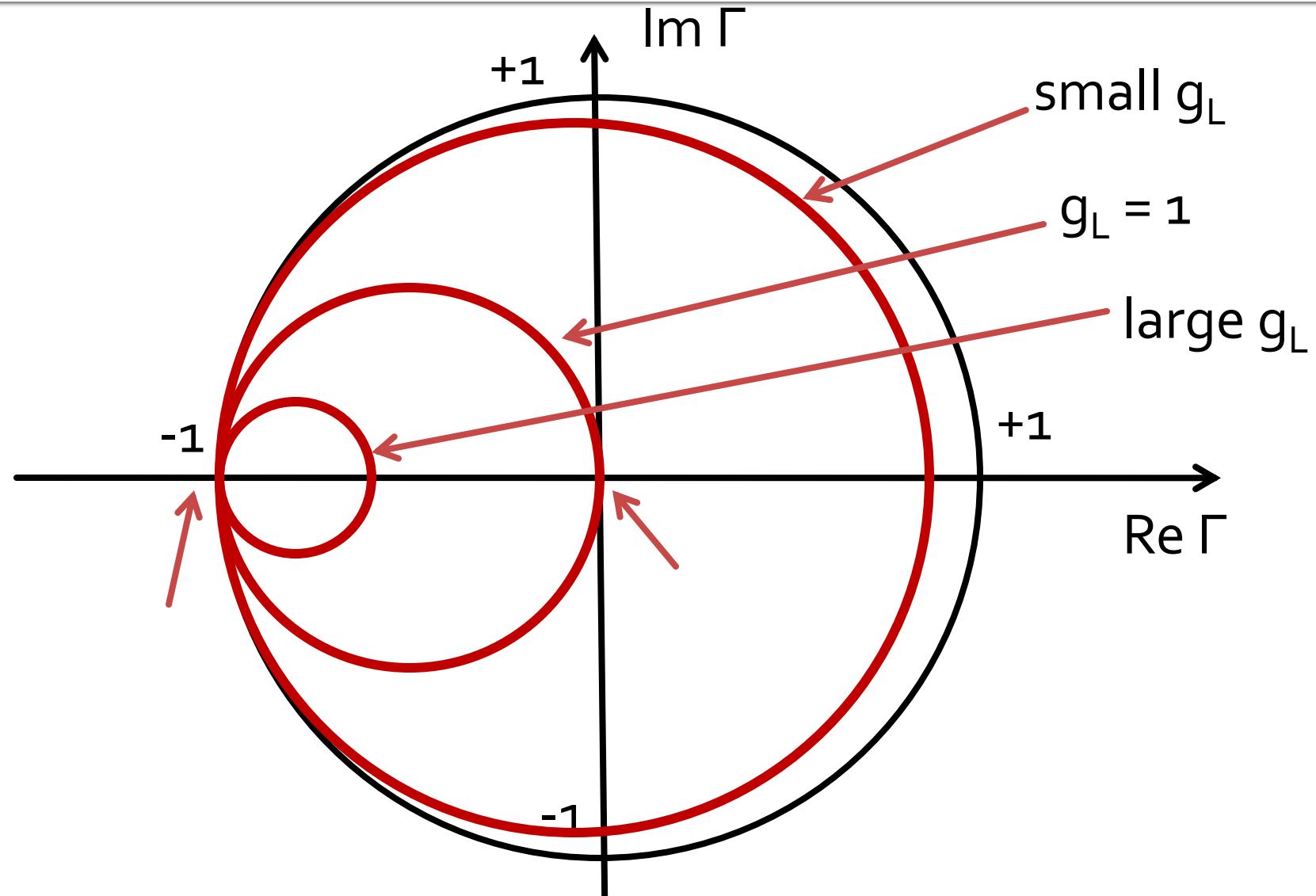

The Smith Chart, susceptance

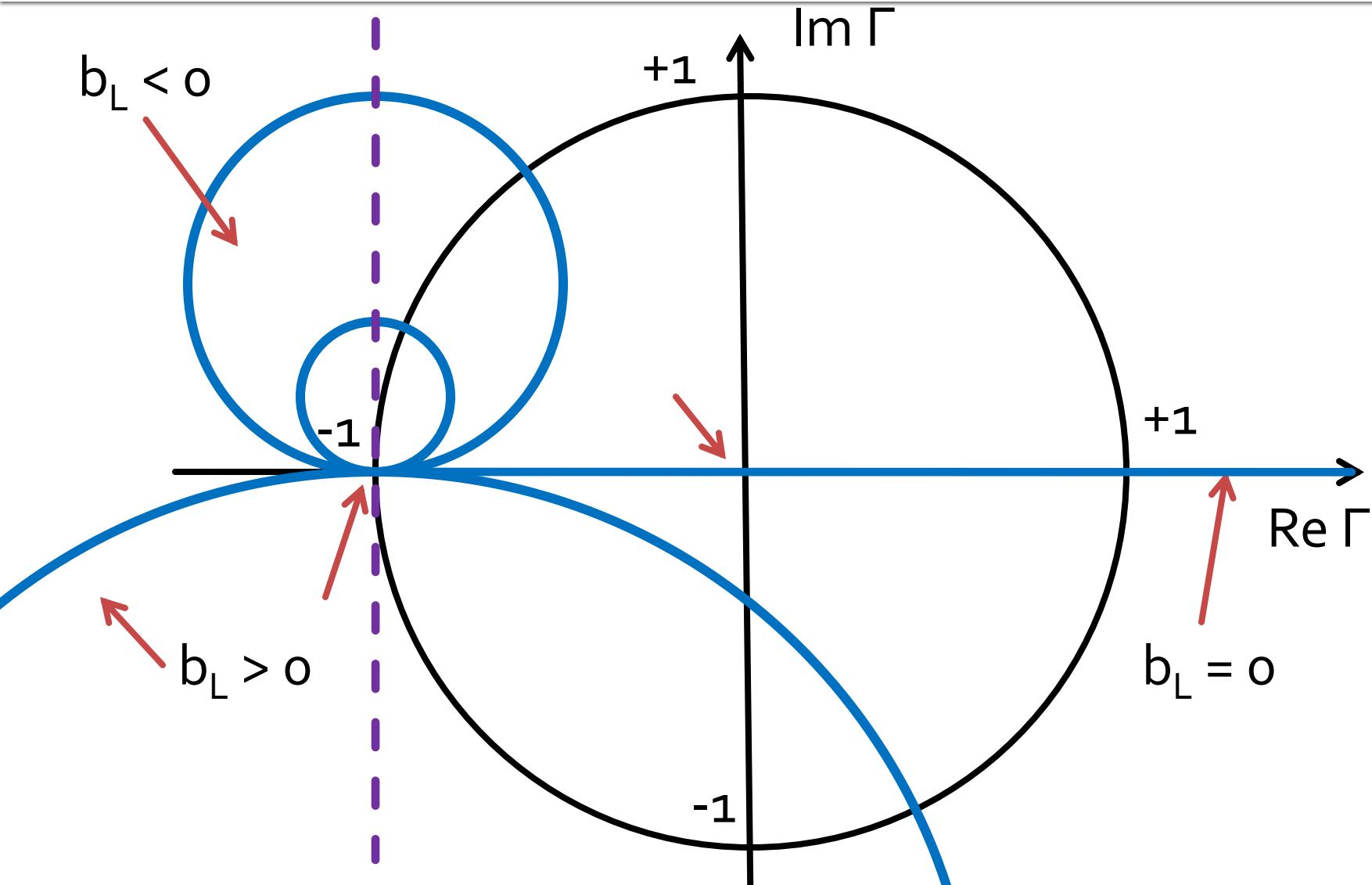

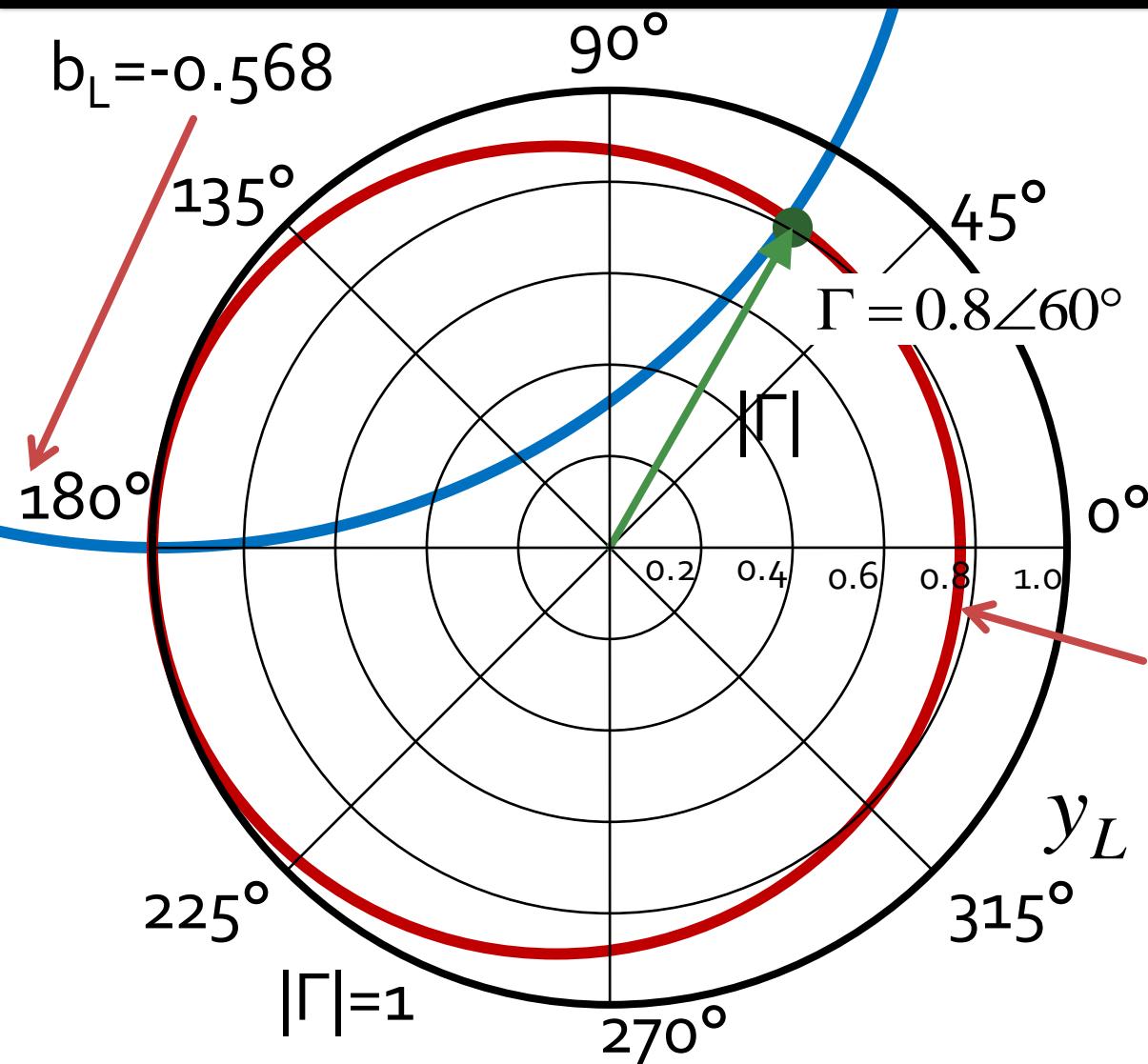The Smith Chart, reflection coefficient \Leftrightarrow admittance



$$\Gamma = 0.8 \angle 60^\circ$$

$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

$$z_L = 0.429 + j \cdot 1.65$$



$$y_L = \frac{1}{z_L} = 0.148 - j \cdot 0.568$$

$$g_L = 0.148$$

$$y_L = 0.148 + j \cdot 0.568$$

(whatever Z_0)

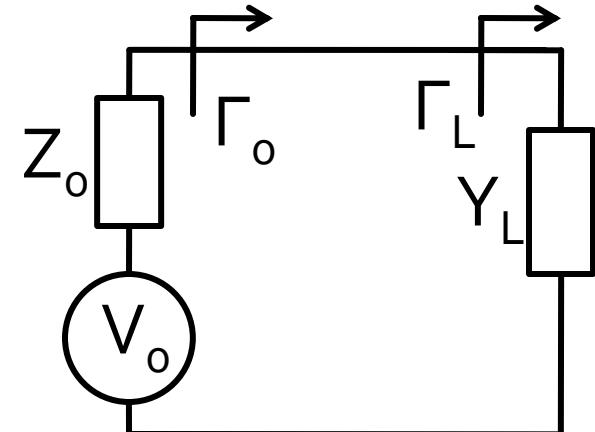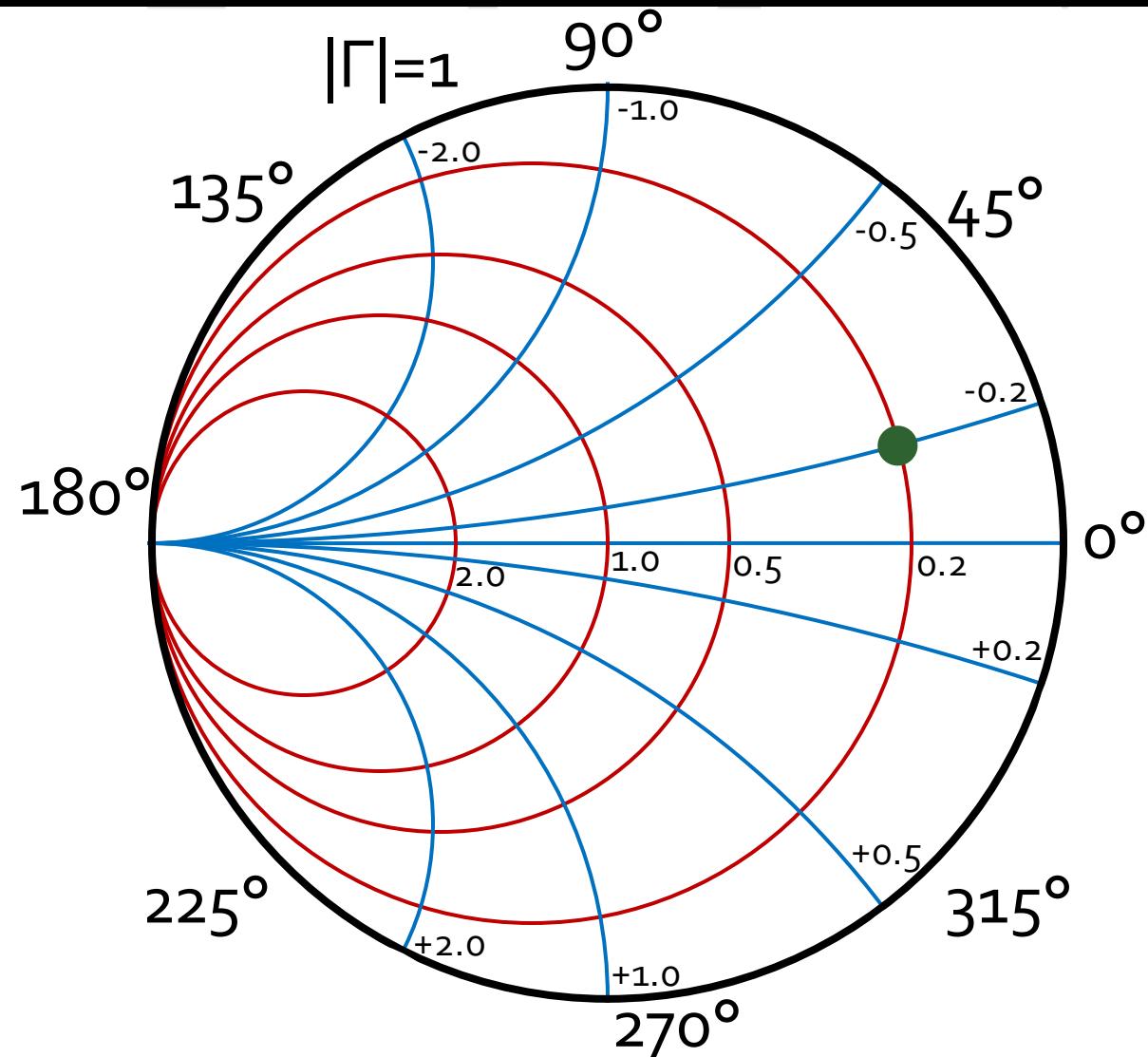The Smith Chart, reflection coefficient \Leftrightarrow admittance



$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$Z_L = 125\Omega + j \cdot 125\Omega$$



$$z_L = 2.5 + j \cdot 2.5$$

$$\Gamma_L = \Gamma_0 = 0.678 \angle 23.5^\circ$$

$$Y_L = \frac{1}{Z_L} = 0.004S - j \cdot 0.004S$$

$$y_L = \frac{1}{z_L} = \frac{Y_L}{Y_0} = 0.2 - j \cdot 0.2$$

The Smith Chart, shunt susceptance

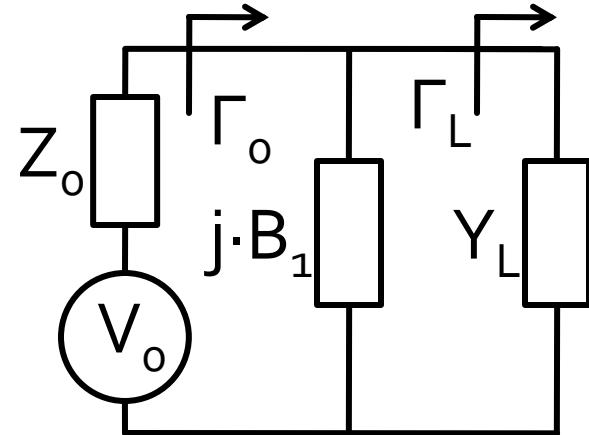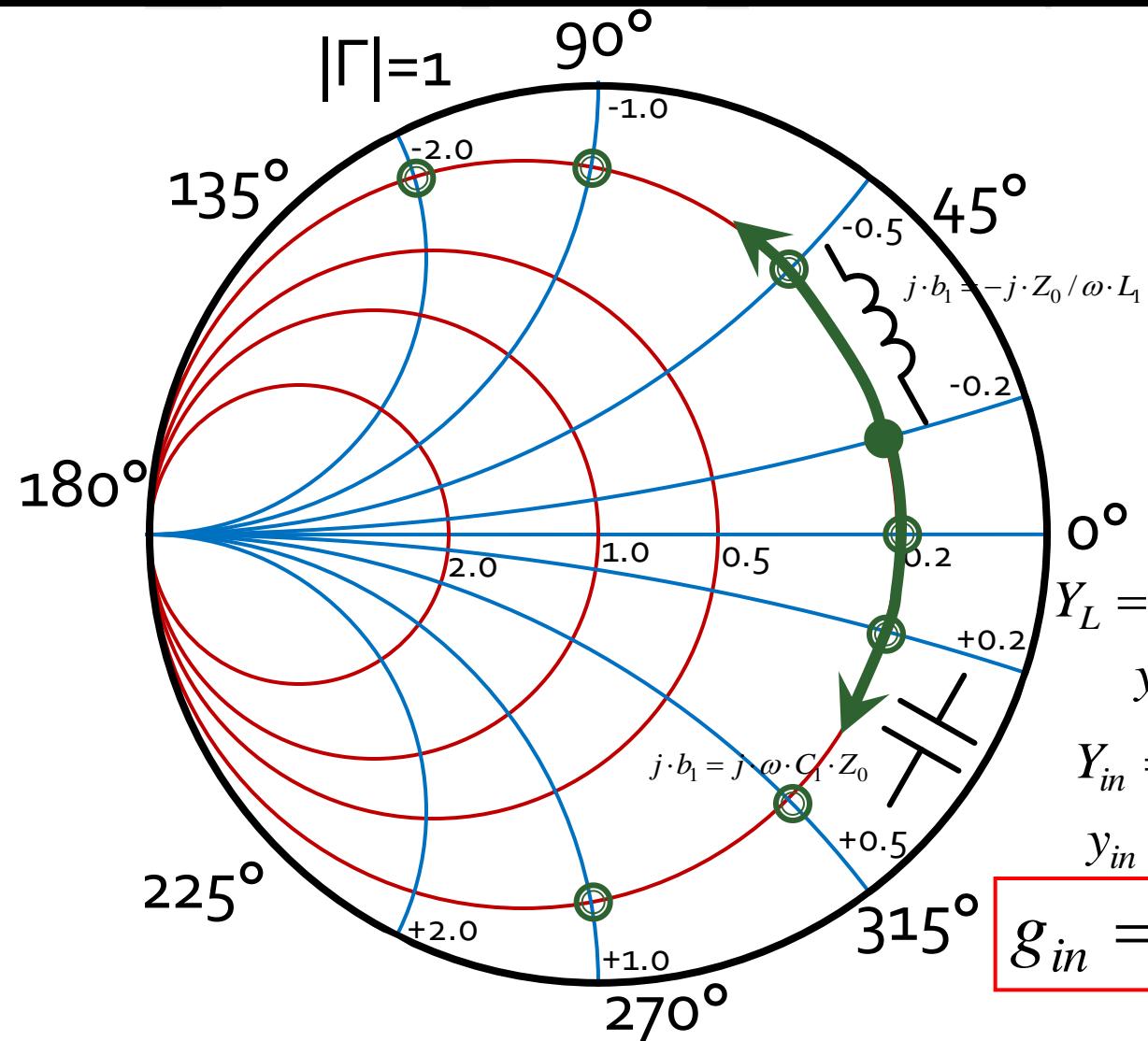

$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$\Gamma_L = 0.678 \angle 23.5^\circ$$

$$Y_L = G_L + j \cdot B_L = 0.004S + j \cdot 0.004$$

$$y_L = g_L + j \cdot b_L = 0.2 - j \cdot 0.2$$





$$Y_{in} = Y_L + j \cdot B_1 = G_L + j \cdot (B_L + B_1)$$

$$y_{in} = g_L + j \cdot (b_L + b_1)$$


$$g_{in} = g_L \quad j \cdot b_1 = j \cdot \omega \cdot C_1 \cdot Z_0 > 0$$

$$j \cdot b_1 = -j \cdot Z_0 / \omega \cdot L_1 < 0$$


ADS, shunt susceptance

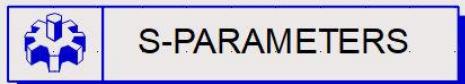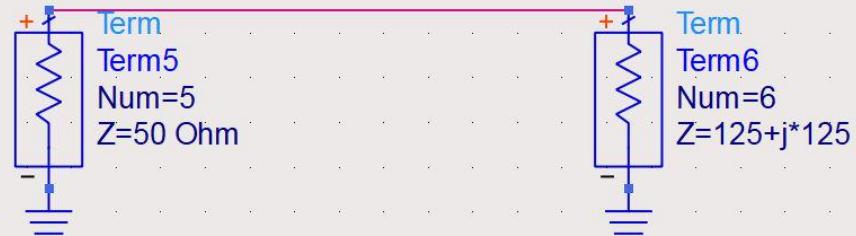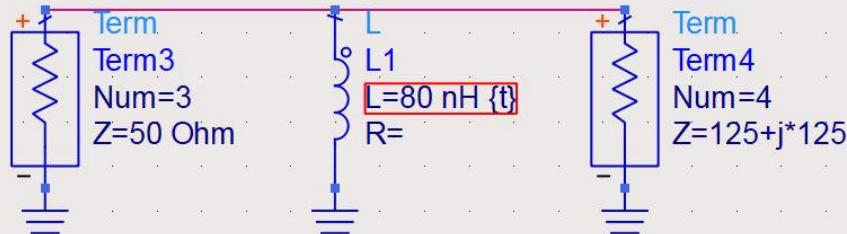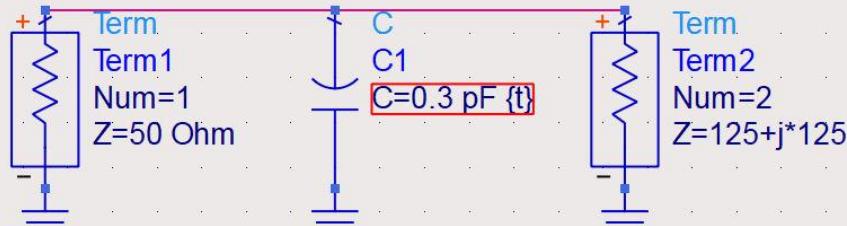



S_Param
SP1
Freq=1.0 GHz

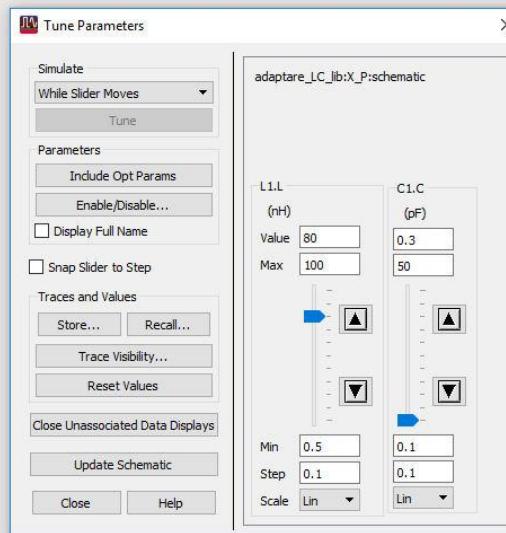

ADS, shunt susceptance

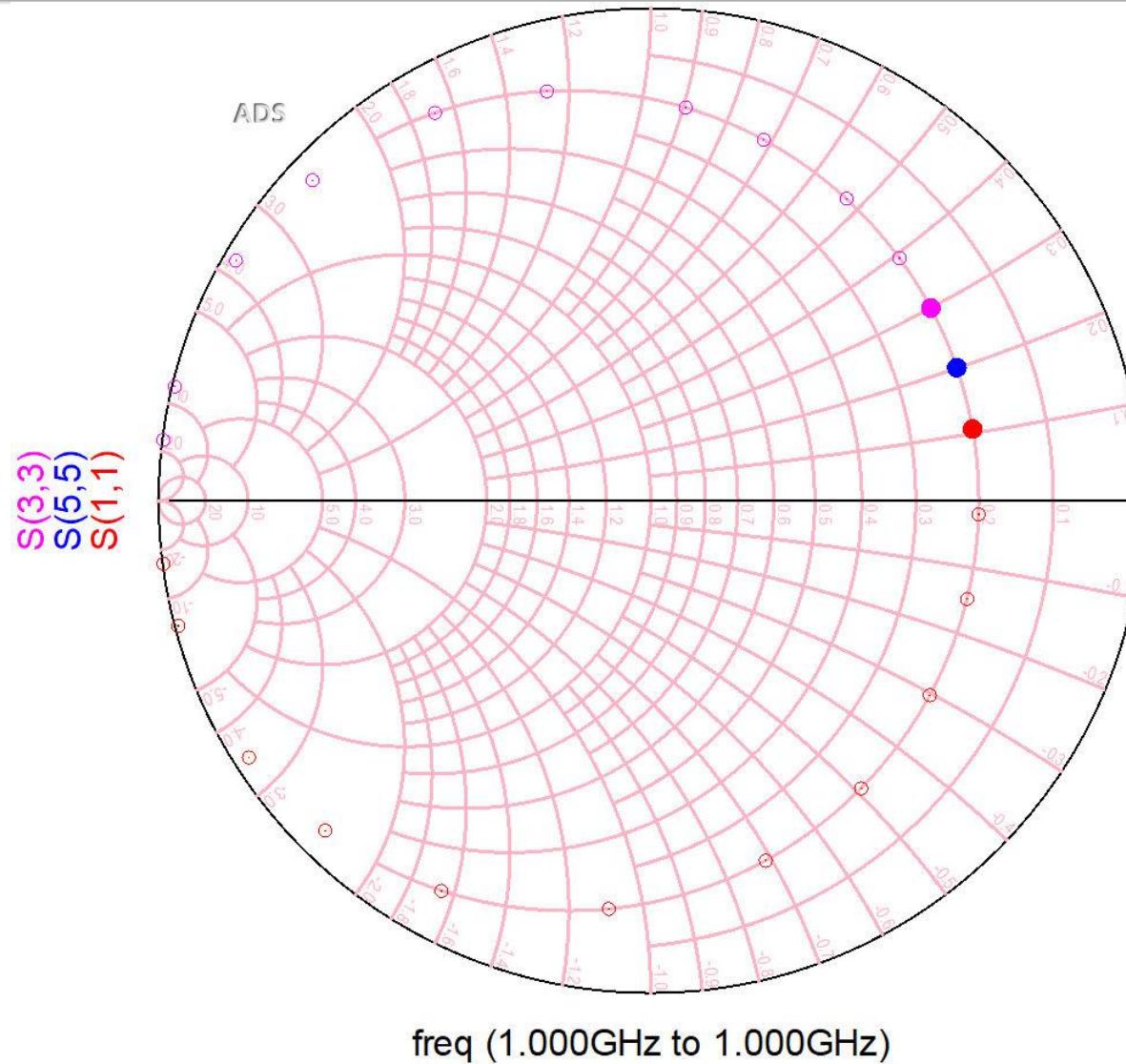

The Smith Chart, shunt conductance

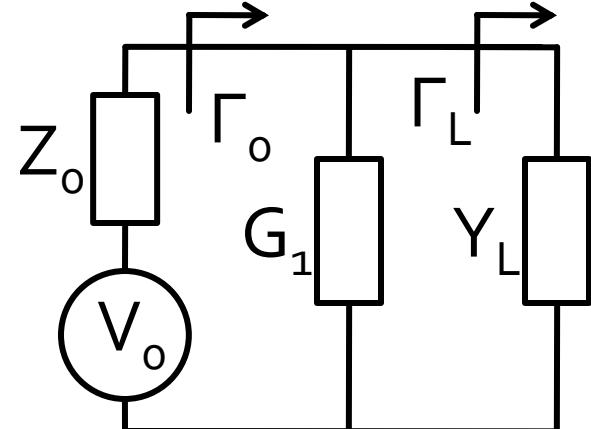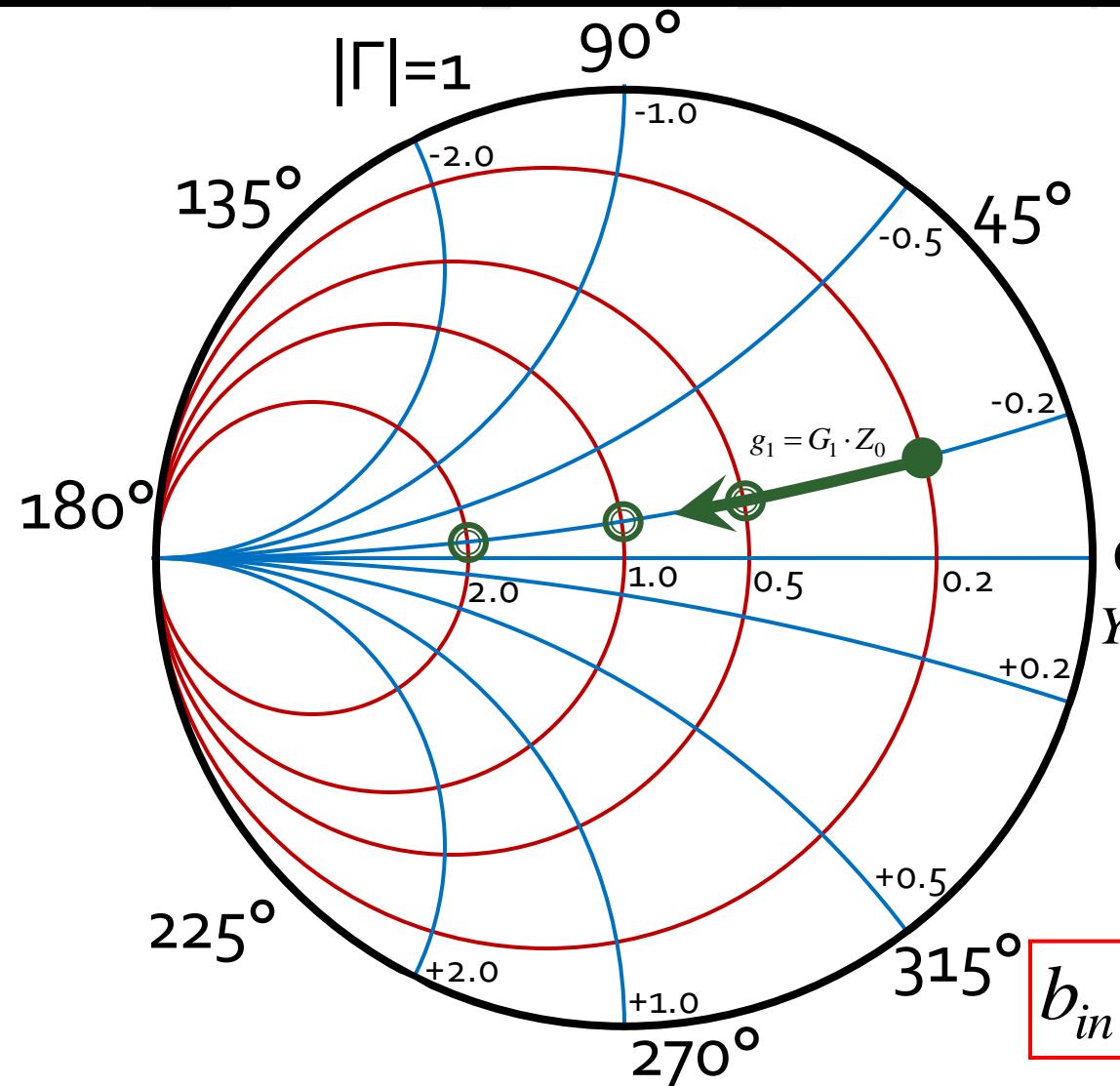

$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$\Gamma_L = 0.678 \angle 23.5^\circ$$

$$Y_L = G_L + j \cdot B_L = 0.004S + j \cdot 0.004$$

$$y_L = g_L + j \cdot b_L = 0.2 - j \cdot 0.2$$


$$Y_{in} = Y_L + G_1 = (G_L + G_1) + j \cdot B_L$$

$$y_{in} = (g_L + g_1) + j \cdot b_L$$

$$b_{in} = b_L$$

$$g_{in} = g_L + G_1 \cdot Z_0$$

ADS, shunt conductance

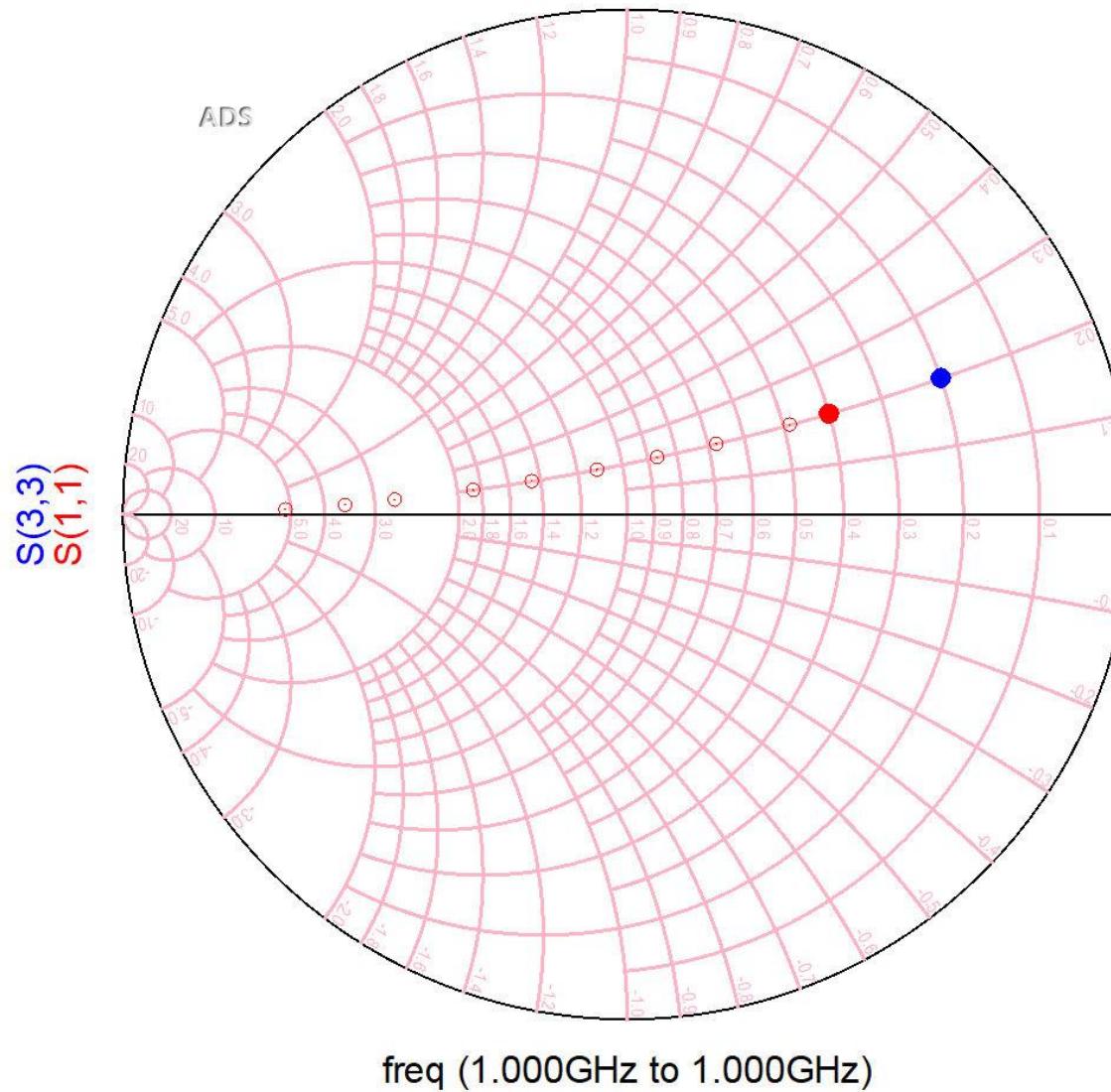

Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.eti.tuiasi.ro>
- rdamian@etti.tuiasi.ro