

Lecture 5  
2020/2021

# Microwave Devices and Circuits for Radiocommunications

# 2020/2021

- 2C/1L, MDCR
- Attendance at minimum 7 sessions (course + laboratory)
- Lectures- associate professor Radu Damian
  - Wednesday 15-17, Online, Microsoft Teams
  - E – 50% final grade
  - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
    - 3p=+0.5p
  - all materials/equipments authorized

# 2020/2021

- Laboratory – associate professor Radu Damian
  - Thursday **10-12**, II.13 / (**Online**)
  - L – 25% final grade
    - ADS, 4 sessions
    - Attendance + personal results
  - P – 25% final grade
    - ADS, 2 sessions (**-1~25.02.2021**)
    - personal homework

# Materials

- RF-OPTO
  - <http://rf-opto.eti.tuiasi.ro>
- **David Pozar, “Microwave Engineering”,**  
Wiley; 4th edition , 2011
  - 1 exam problem ← Pozar
- Photos
  - sent by ~~email~~/online exam
  - used at lectures/laboratory

# Profile photo

- Profile photo – online “exam”

**Examene online: 2020/2021**

**Disciplina: MDC (Microwave Devices and Circuits (Engleza))**

**Pas 3**

Nr.	Titlu	Start	Stop	Text
1	Profile photos	03/03/2021; 10:00	08/04/2021; 08:00	Online "exam" created f ..
2	Mini Test 1 (lecture 2)	03/03/2021; 15:35	03/03/2021; 15:50	The current test consis ..

# Online

- access to **online exams** requires the **password** received by email

English | Romana |

Main Courses Master Staff Research **Student List**

Grades Student List Exams Photos

## POPESCU GOPO ION

Fotografia nu există

Date:

Grupa	5700 (2019/2020)
Specializarea	Inginerie electronica si telecomunicatii
Marca	7000000

[Access the site as this student](#) | [Request access to software](#)

**Grades**

Inca nu a fost notat.

Main Courses Master Staff Research

Grades **Student List** Exams Photos

### Login

Use the last name and email stored in the database

Name  
POPESCU GOPO

Email/Password

Write the code below

828f26b

Send

# Online results submission

- many numerical values

i	<b>Z1</b>	<b>Z2</b>	<b>Z3</b>	<b>Z4</b>	<b>Z5</b>	<b>Z6</b>	<b>Z7</b>
	148.33	155.88	202.12	164.35	180.91	30.29	185.19
	25.97	153.5	34.64	35.79	55.56	26.212	10,693
	0	0	0	0	0	0	0
	50	50	50	50	50	50	50




# Online results submission

Grade = Quality of the work +  
+ Quality of the submission

**Important**

# The lossless line

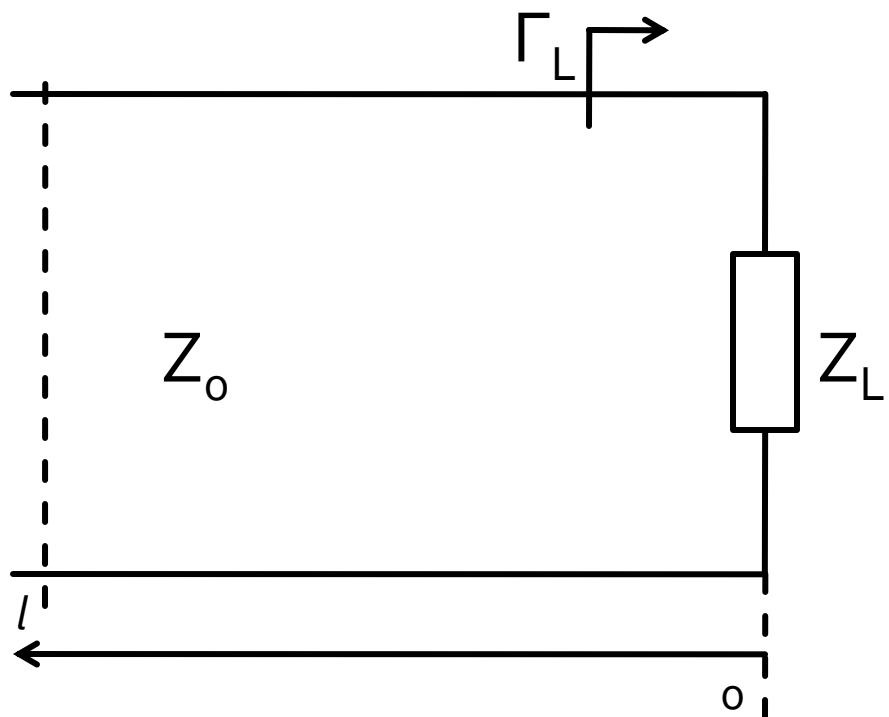

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$$

$$Z_L = \frac{V(0)}{I(0)} \quad Z_L = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \cdot Z_0$$

- voltage reflection coefficient

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

- $Z_0$  real

# The lossless line

$$V(z) = V_0^+ \cdot (e^{-j\beta z} + \Gamma \cdot e^{j\beta z}) \quad I(z) = \frac{V_0^+}{Z_0} \cdot (e^{-j\beta z} - \Gamma \cdot e^{j\beta z})$$


- time-average Power flow along the line

$$P_{avg} = \frac{1}{2} \cdot \text{Re}\{V(z) \cdot I(z)^*\} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot \text{Re}\left\{1 - \Gamma^* \cdot e^{-2j\beta z} + \Gamma \cdot e^{2j\beta z} - |\Gamma|^2\right\}$$
$$P_{avg} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot \left(1 - |\Gamma|^2\right)$$

$(z - z^*) = \text{Im}$

- Total power delivered to the load = Incident power – “Reflected” power
- Return “Loss” [dB] 
$$\text{RL} = -20 \cdot \log|\Gamma| \quad [\text{dB}]$$

# Reflection and power / Model

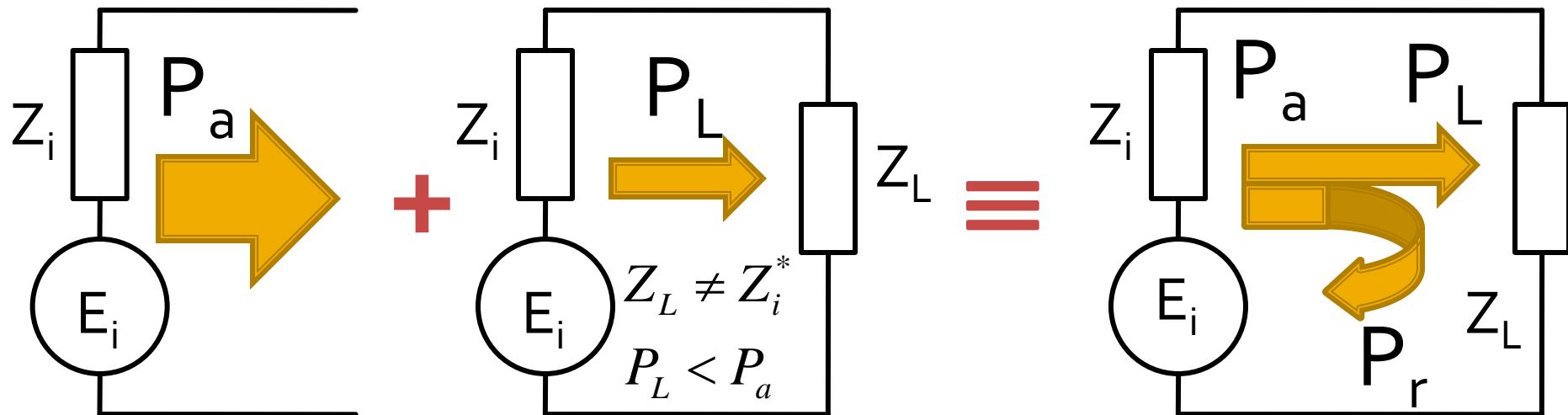

- The source has the ability to send to the load a certain maximum power (available power)  $P_a$
- For a particular load the power sent to the load is less than the maximum (mismatch)  $P_L < P_a$
- The phenomenon is “as if” (model) some of the power is reflected  $P_r = P_a - P_L$
- The power is a **scalar** !

# Matching , from the point of view of power transmission


$$Z_L = Z_i^*$$

If we choose a real  $Z_0$

$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

$$\Gamma_L = \Gamma_i^*$$

- complex numbers
- in the complex plane

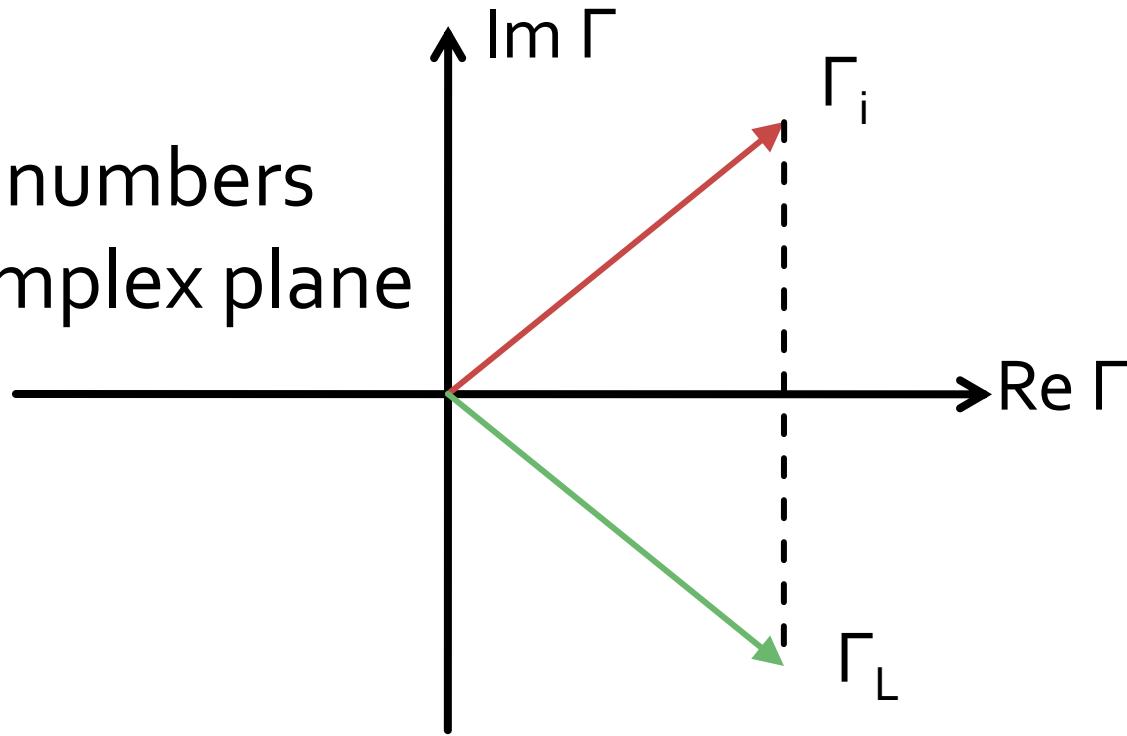

General theory

# Microwave Network Analysis


# Course Topics

- Transmission lines
- Impedance matching and tuning
- Directional couplers
- Power dividers
- Microwave amplifier design
- Microwave filters
- ~~Oscillators and mixers?~~



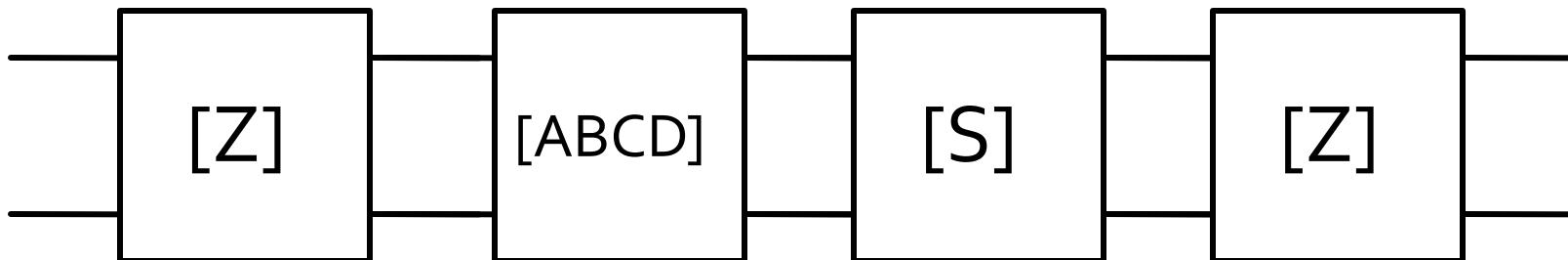
# Network Analysis


- We try to separate a complex circuit into individual blocks
- These are analyzed separately (decoupled from the rest of the circuit) and are characterized only by the port level signals (**black box**)
- Network-level analysis allows you to put together individual block results and get a total result for the entire circuit



# Impedance matrix – Z

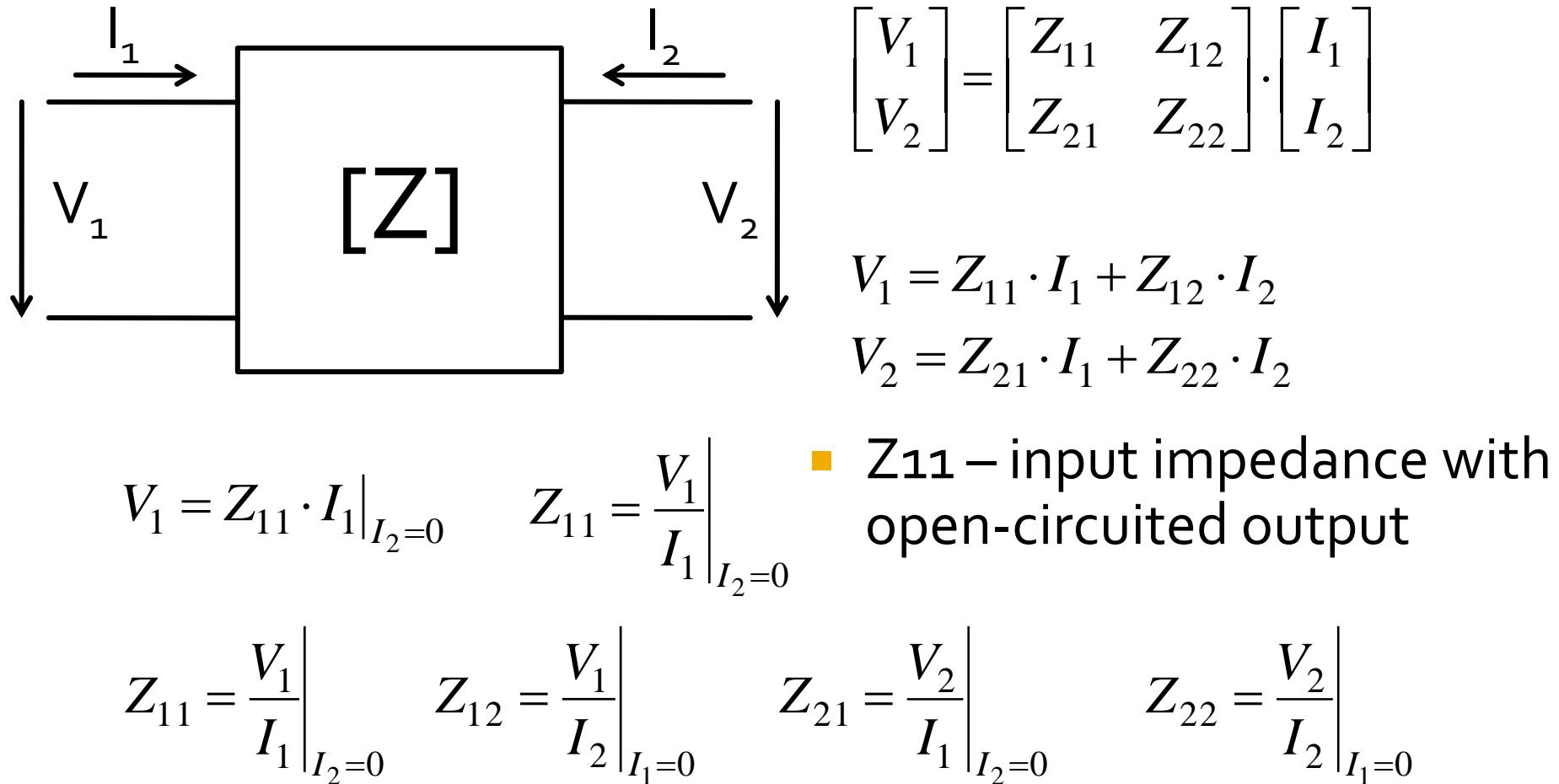

# Admittance matrix – Y

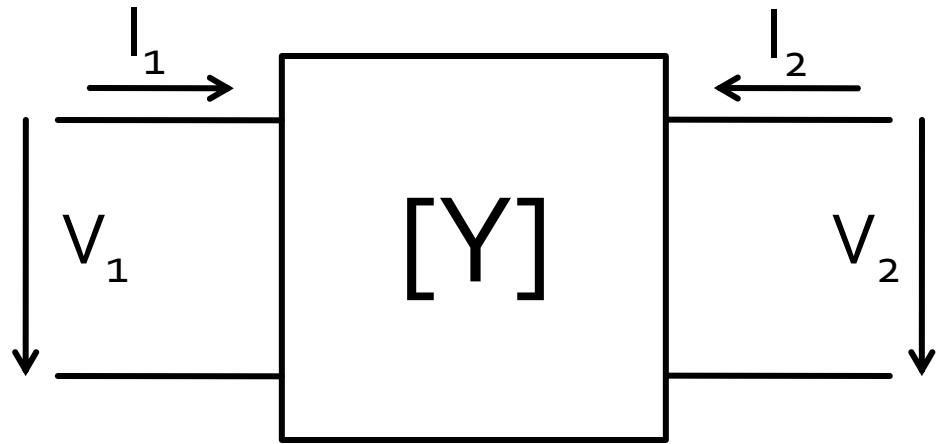

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = Y_{11} \cdot V_1 + Y_{12} \cdot V_2$$


$$I_2 = Y_{21} \cdot V_1 + Y_{22} \cdot V_2$$

$$I_1 = Y_{11} \cdot V_1 \Big|_{V_2=0} \quad Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} \quad Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \quad Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

- $Y_{11}$  – input admittance with short-circuited output

# Hybrid matrices – H and G

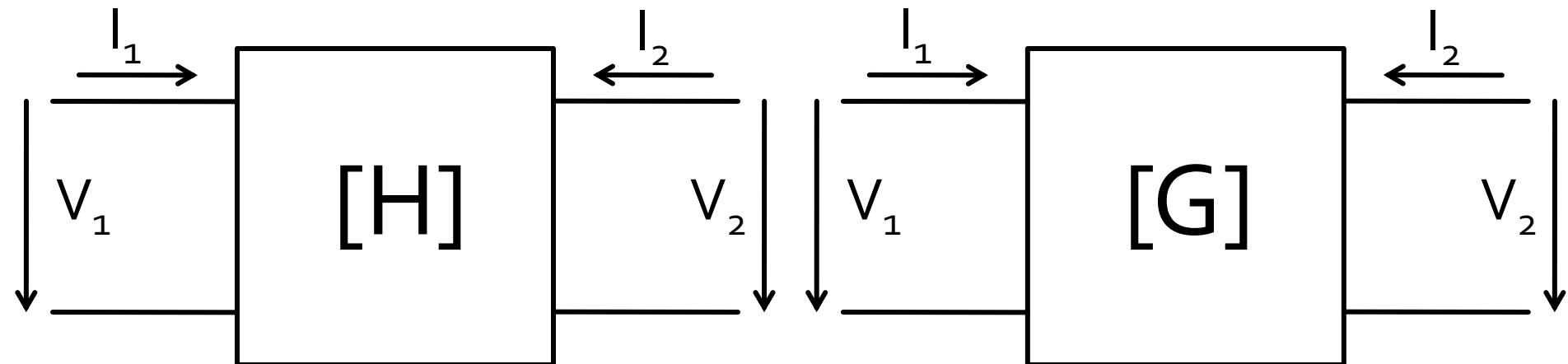

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} H_{11} & H_{12} \\ H_{21} & H_{22} \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$H_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0 \text{ or } H_{22} \rightarrow \infty}$$

- $h_{21E}$  widely used for Bipolar Transistors,  
common emitter topology (or  $\beta$ ,  $h_{22E} \gg$ )


# Network Analysis

- Each matrix is best suited for a particular mode of port excitation (V, I)
  - matrix H in common emitter connection for TB:  $I_B$ ,  $V_{CE}$
  - matrices provide the associated quantities depending on the “attack” ones
- Traditional notation of Z, Y, G, H parameters is in lowercase (z, y, g, h)
- In microwave analysis we prefer the notation in uppercase to avoid confusion with the **normalized parameters**

$$z = \frac{Z}{Z_0} \quad y = \frac{Y}{Y_0} = \frac{1/Z}{1/Z_0} = \frac{Z_0}{Z} = Z_0 \cdot Y$$

$$z_{11} = \frac{Z_{11}}{Z_0} \quad y_{11} = \frac{Y_{11}}{Y_0} = Z_0 \cdot Y_{11}$$

# ABCD (transmission) matrix

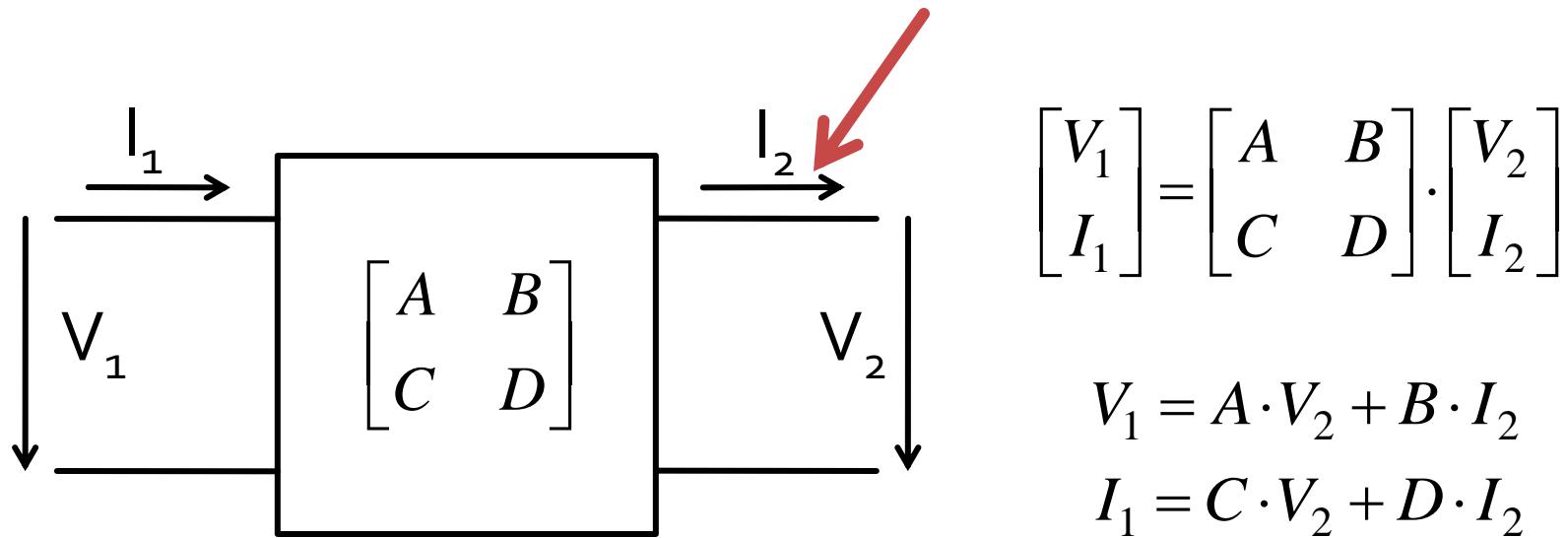

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \frac{1}{A \cdot D - B \cdot C} \cdot \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$


$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

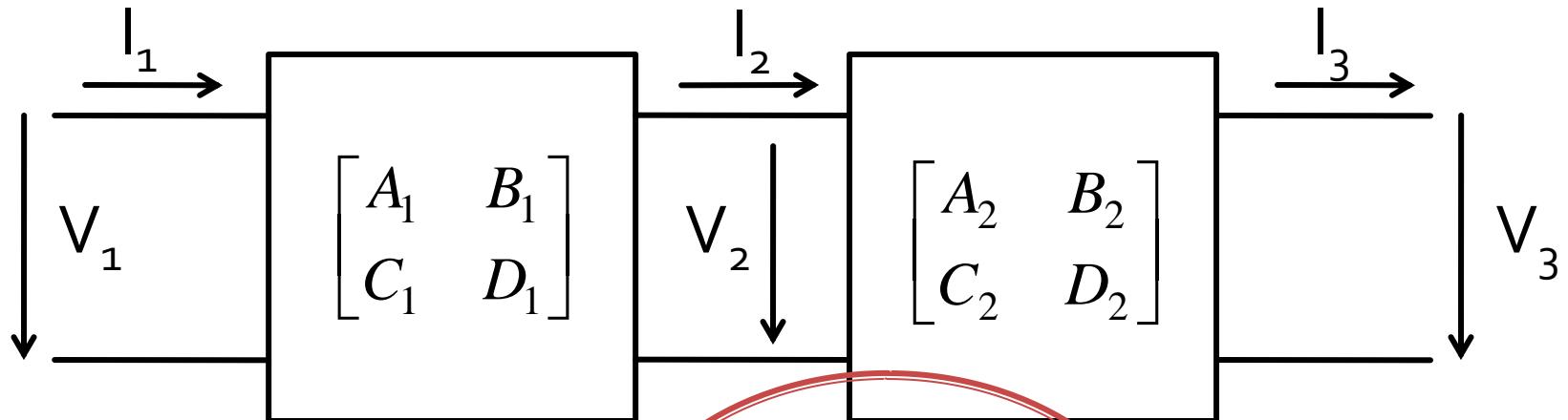
# ABCD (transmission) matrix

- This 2X2 matrix characterizes the “input”/“output” relation
- Allows easy chaining of multiple two-ports



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \cdot \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \cdot \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \cdot \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

# ABCD (transmission) matrix

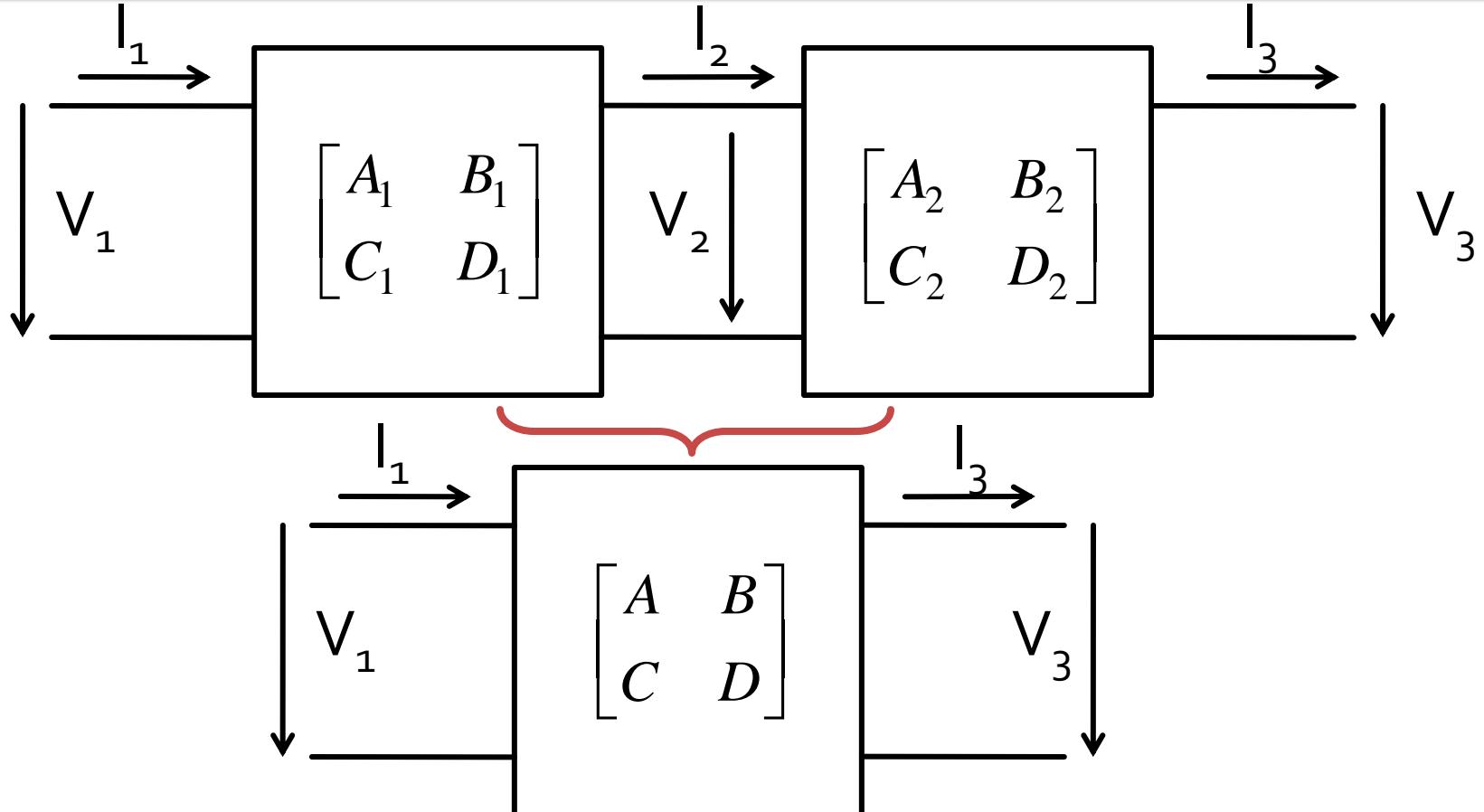


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \cdot \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

# ABCD (transmission) matrix

- suitable **only** for two-port networks ( $Z$ ,  $Y$  can be easily extended for multiport / n-ports)
- allows easy coupling of multiple elements
- allows the calculation of complex circuits with one input and one output by breaking them in individual component blocks
- a library of ABCD matrices for elementary two-port networks can be built up

# Library of ABCD matrices

- Series impedance

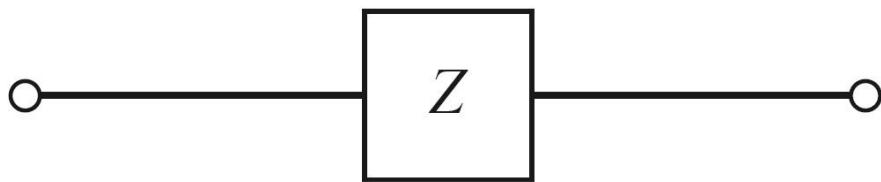

$$A = 1$$

$$C = 0$$

$$B = Z$$

$$D = 1$$




$$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = 1 \quad B = \frac{V_1}{I_2} \Big|_{V_2=0} = \frac{V_1}{V_1/Z} = Z$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = 0 \quad D = \frac{I_1}{I_2} \Big|_{V_2=0} = \frac{I_1}{I_1} = 1$$

# Library of ABCD matrices

- Shunt admittance

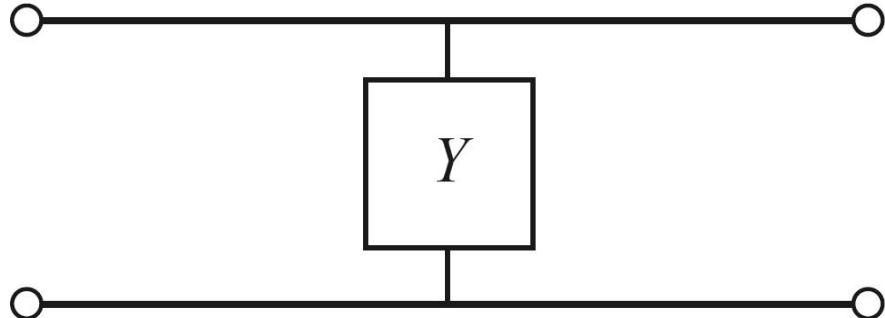

$$A = 1$$

$$C = Y$$

$$B = 0$$


$$D = 1$$

$$\begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

Homework!

# Library of ABCD matrices

- Transmission line

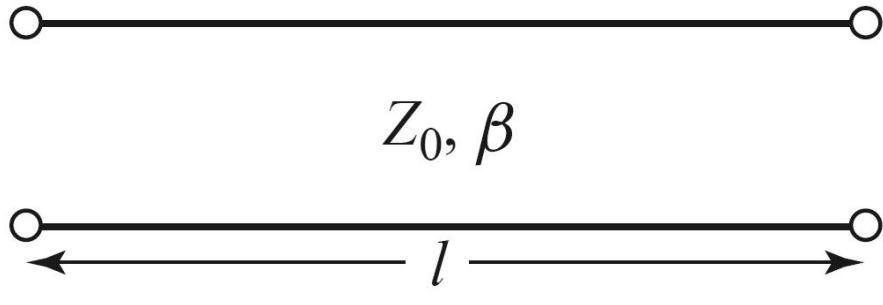

$$A = \cos \beta \cdot l$$

$$B = j \cdot Z_0 \cdot \sin \beta \cdot l$$

$$C = j \cdot Y_0 \cdot \sin \beta \cdot l$$

$$D = \cos \beta \cdot l$$


Homework!

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

$$\begin{bmatrix} \cos \beta \cdot l & j \cdot Z_0 \cdot \sin \beta \cdot l \\ j \cdot Y_0 \cdot \sin \beta \cdot l & \cos \beta \cdot l \end{bmatrix}$$

# Library of ABCD matrices

- Transformer

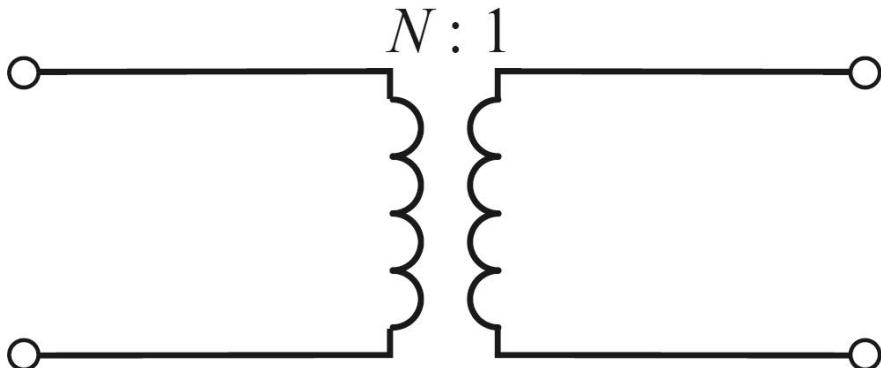

$$A = N$$

$$C = 0$$

$$B = 0$$


$$D = \frac{1}{N}$$

$$\begin{bmatrix} N & 0 \\ 0 & \frac{1}{N} \end{bmatrix}$$

Homework!

# Library of ABCD matrices

- $\pi$  network

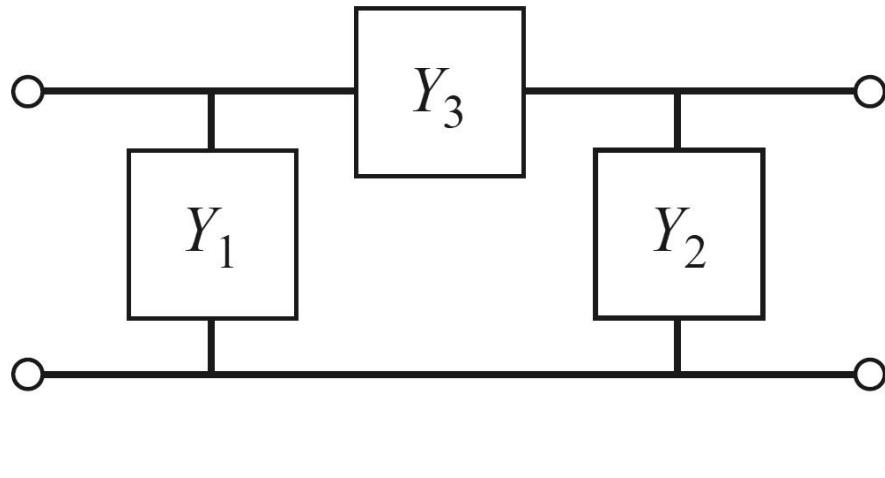

$$A = 1 + \frac{Y_2}{Y_3}$$

$$B = \frac{1}{Y_3}$$


$$C = Y_1 + Y_2 + \frac{Y_1 \cdot Y_2}{Y_3}$$

$$D = 1 + \frac{Y_1}{Y_3}$$

Homework!

# Library of ABCD matrices

- T network

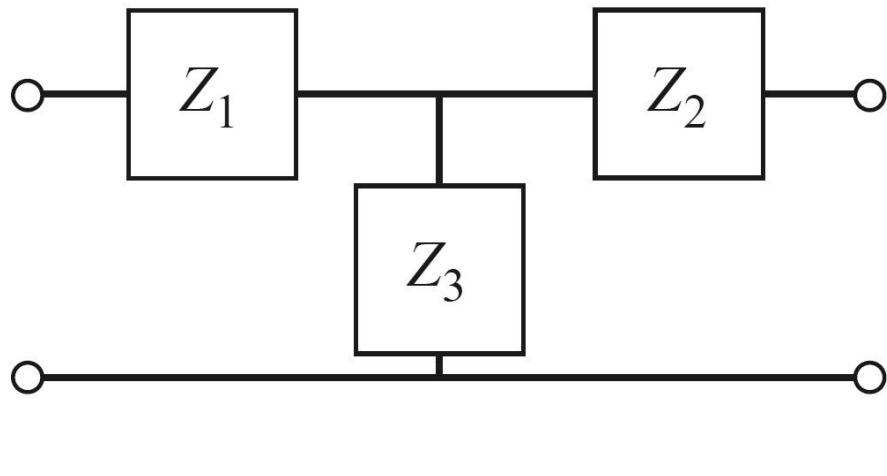

$$A = 1 + \frac{Z_1}{Z_3}$$

$$B = Z_1 + Z_2 + \frac{Z_1 \cdot Z_2}{Z_3}$$


$$C = \frac{1}{Z_3}$$

$$D = 1 + \frac{Z_2}{Z_3}$$

Homework!

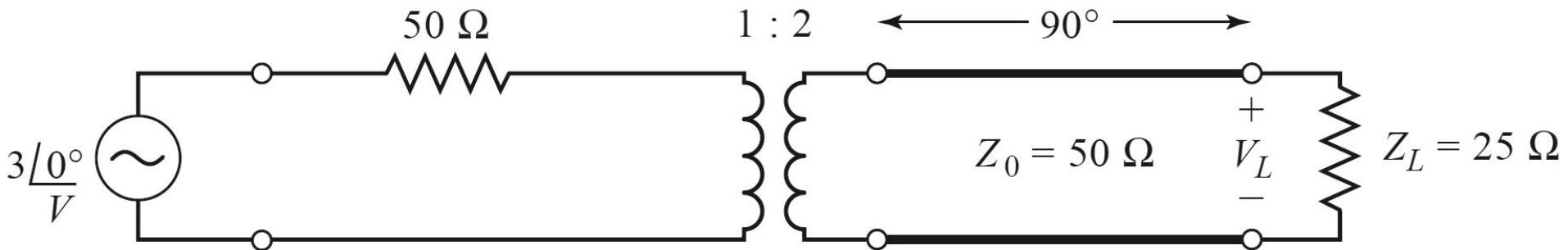
# Example for ABCD matrix

- Find the voltage  $V_L$  across the load resistor in the circuit shown below (Pozar/exam problem)


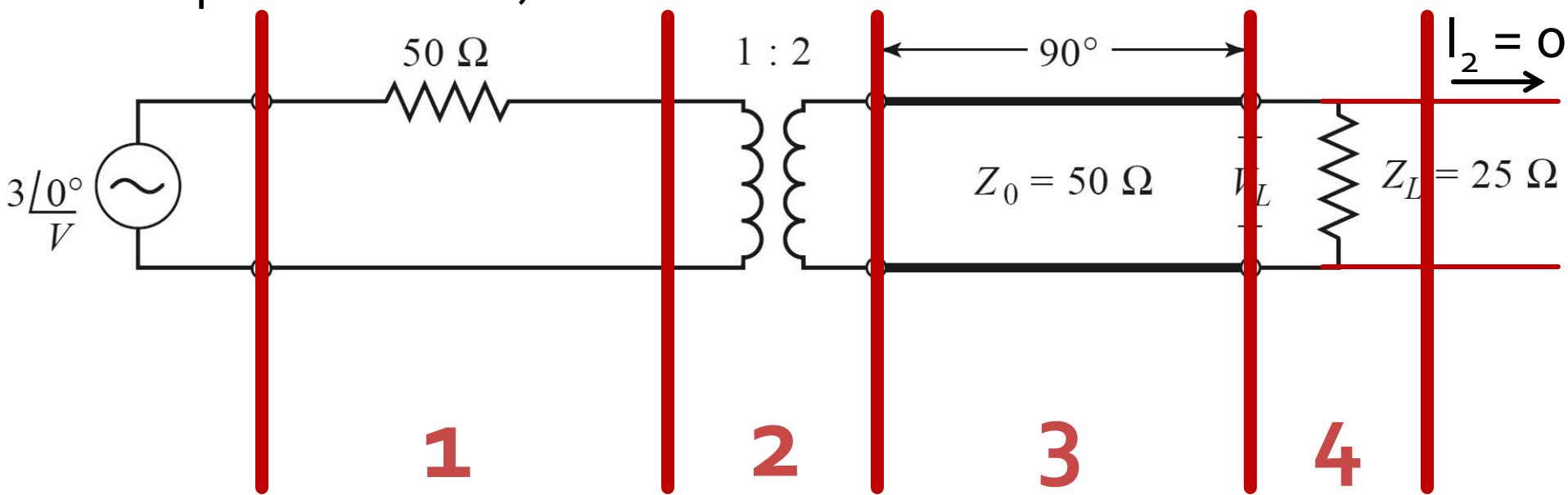
# Example for ABCD matrix


- We break the circuit in elementary sections
- Sources are left outside
- If necessary, input and output ports are created (and left open-circuited)



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = M_1 \cdot M_2 \cdot M_3 \cdot M_4 \quad V_1 = A \cdot V_2 + B \cdot I_2 \Big|_{I_2=0} \quad V = A \cdot V_L \rightarrow V_L = \frac{V}{A}$$

# Example for ABCD matrix


- $M_1$ , series impedance

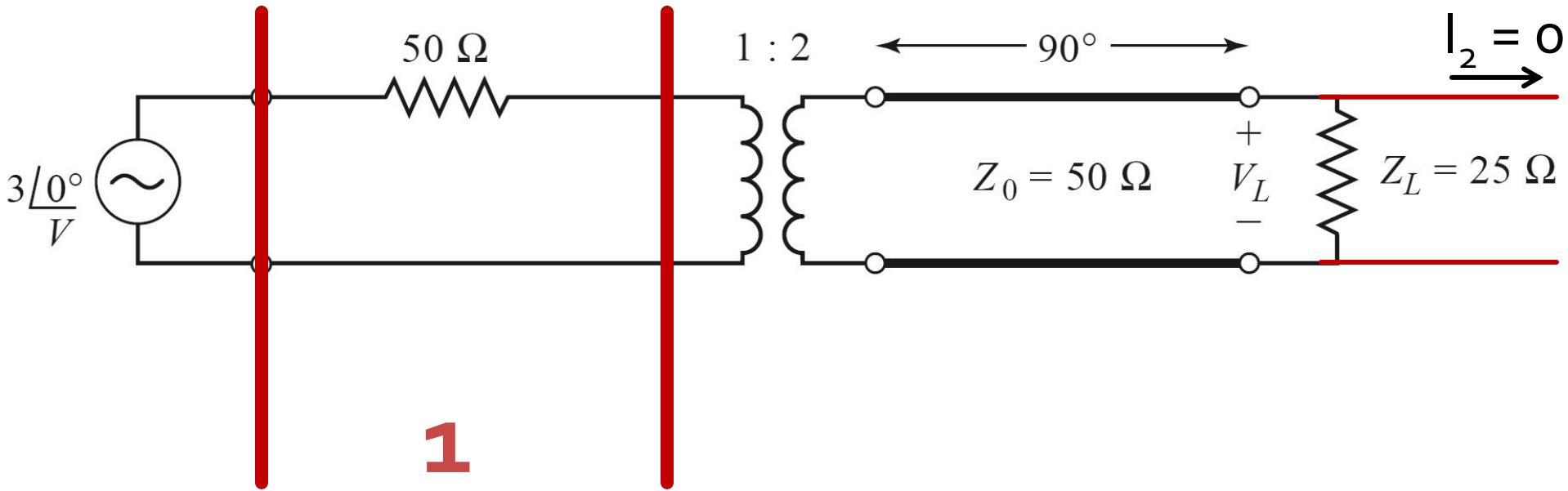

$$M_1 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 50 \\ 0 & 1 \end{bmatrix}$$

# Example for ABCD matrix


- $M_2$ , 1:2 transformer

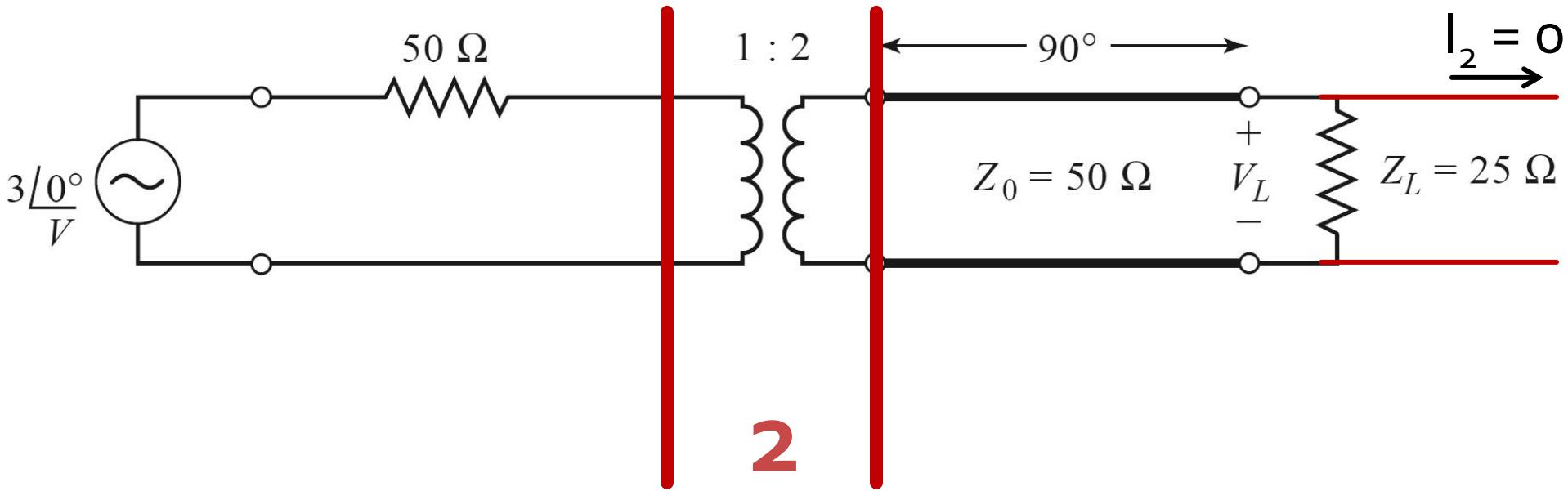

$$M_2 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{1}{2} & 0 \\ 0 & 2 \end{bmatrix}$$
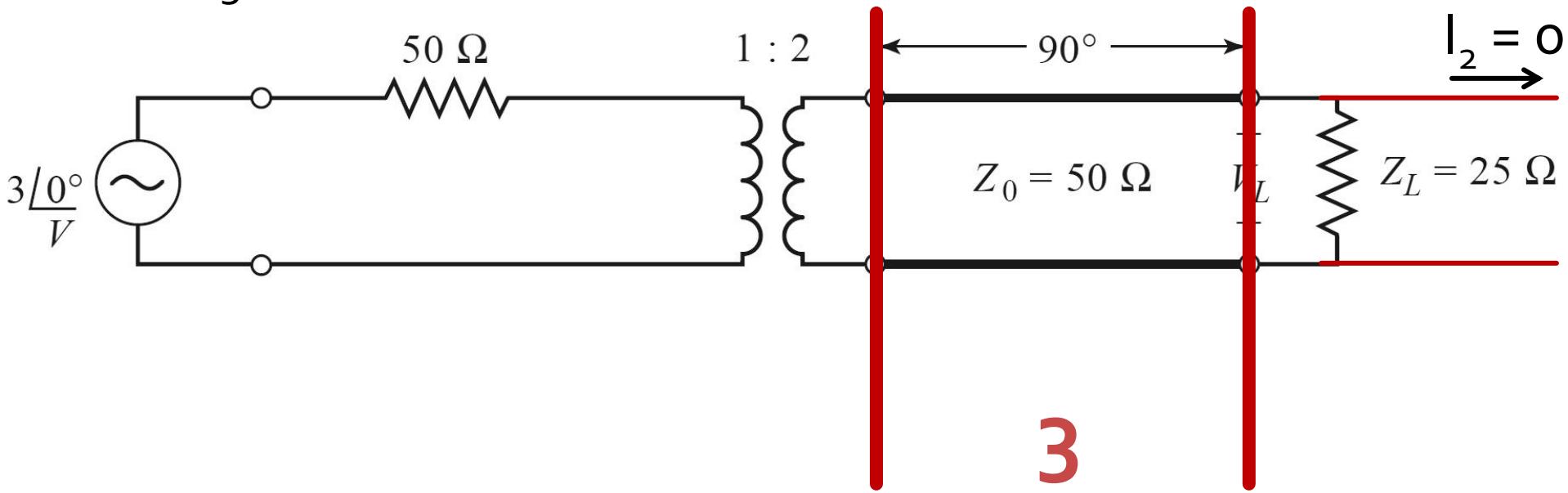
# Example for ABCD matrix


- M<sub>3</sub>, series transmission line, E = 90°



$$M_3 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0 & 50 \cdot j \\ \frac{j}{50} & 0 \end{bmatrix}$$


# Example for ABCD matrix

- $M_4$ , shunt impedance/admittance

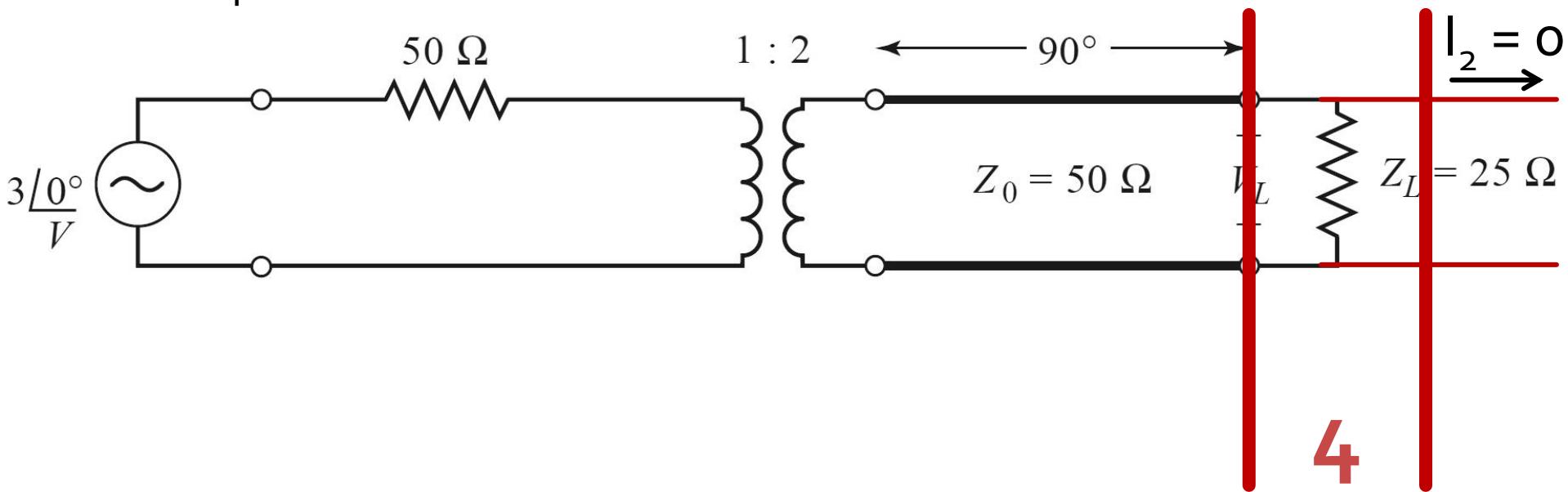

$$M_4 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{25} & 1 \end{bmatrix}$$

# Example for ABCD matrix

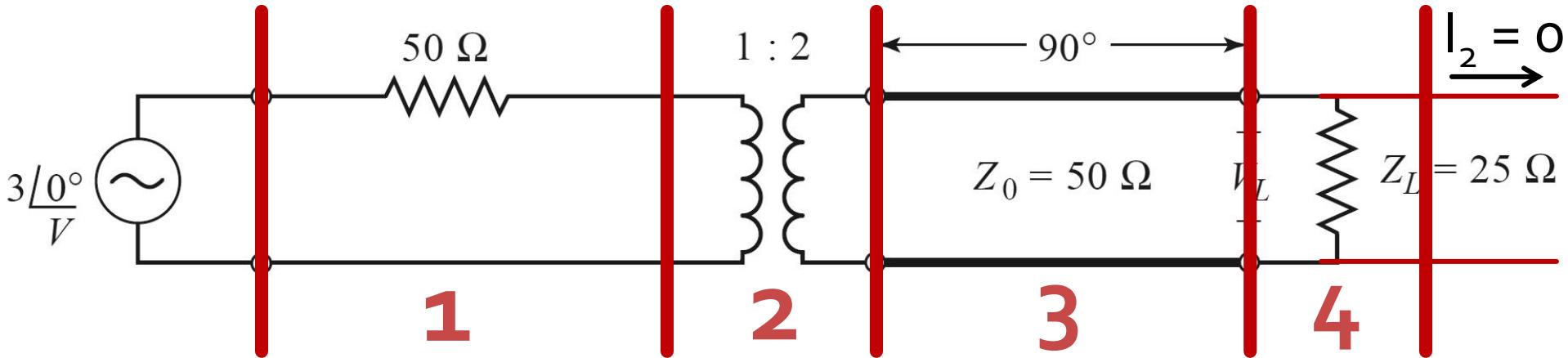

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 50 \\ 0 & 1 \end{bmatrix} \cdot \begin{bmatrix} \frac{1}{2} & 0 \\ 0 & 2 \end{bmatrix} \cdot \begin{bmatrix} 0 & 50 \cdot j \\ \frac{j}{50} & 0 \end{bmatrix} \cdot \begin{bmatrix} 1 & 0 \\ \frac{1}{25} & 1 \end{bmatrix} = \begin{bmatrix} 3 \cdot j & 25 \cdot j \\ \frac{j}{25} & 0 \end{bmatrix}$$


$$V_L = \frac{V}{A} = \frac{3\angle 0^\circ}{3 \cdot j} = 1\angle -90^\circ$$

(Somewhat!) Specific theory

# Microwave Network Analysis

# Scattering matrix – S

## ■ Scattering parameters

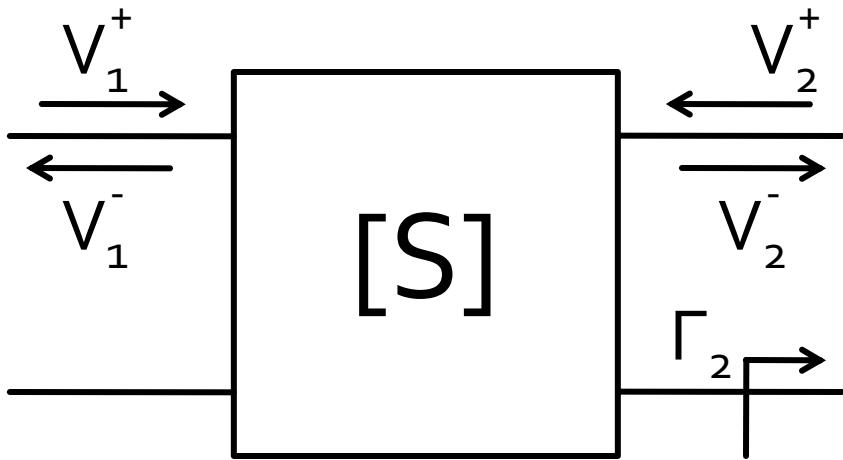


$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_1^+=0} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+=0}$$

- $V_2^+ = 0$  meaning: port 2 is terminated in matched load to avoid reflections towards the port

$$\Gamma_2 = 0 \rightarrow V_2^+ = 0$$

# Scattering matrix – $S$

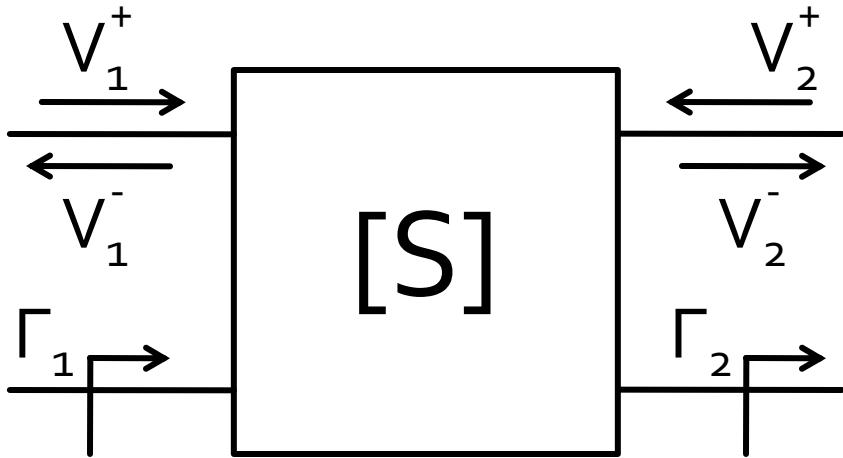

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$S_{11} = \frac{V_1^-}{V_1^+} \Bigg|_{V_2^+ = 0} = \Gamma_1 \Big|_{\Gamma_2 = 0}$$

$$S_{21} = \frac{V_2^-}{V_1^+} \Bigg|_{V_2^+ = 0} = T_{21} \Big|_{\Gamma_2 = 0}$$

- $S_{11}$  is the reflection coefficient seen looking into port **1** when port **2** is terminated in matched load
- $S_{21}$  is the transmission coefficient from port **1** (**second** index!) to port **2** (**first** index!) when port **2** is terminated in matched load

# Scattering matrix – S

- S matrix can be extended to multiple ports

$$S_{ii} = \left. \frac{V_i^-}{V_i^+} \right|_{V_k^+=0, \forall k \neq i}$$

$$S_{ij} = \left. \frac{V_i^-}{V_j^+} \right|_{V_k^+=0, \forall k \neq j}$$

- $S_{ii}$  is the reflection coefficient seen looking into port  $i$  when all other ports are terminated in matched loads
- $S_{ij}$  is the transmission coefficient from port  $j$  (**second** index!) to port  $i$  (**first** index!) when all other ports are terminated in matched loads

# Properties of S matrix

- If port  $i$  is connected to a transmission line with characteristic impedance  $Z_{oi}$

$$[Z_0] = \begin{bmatrix} Z_{01} & \cdots & 0 \\ \vdots & \ddots & \vdots \\ 0 & \cdots & Z_{0n} \end{bmatrix}$$

- Lecture 3  $V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$   $I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$

In the port's reference plane,  $z=0$

$$V_i = V_i^+ + V_i^- \quad I_i = \frac{V_i^+}{Z_{0i}} - \frac{V_i^-}{Z_{0i}}$$

- Relation to Z matrix  $[Z] \cdot [I] = [V]$


$$[Z] \cdot [I] = [Z_0]^{-1} \cdot [Z] \cdot [V^+] - [Z_0]^{-1} \cdot [Z] \cdot [V^-] \quad [V] = [V^+] + [V^-]$$

$$[Z_0]^{-1} \cdot [Z] \cdot [V^+] - [Z_0]^{-1} \cdot [Z] \cdot [V^-] = [V^+] + [V^-] \quad ([Z] - [Z_0]) \cdot [V^+] = ([Z] + [Z_0]) \cdot [V^-]$$

$$[V^-] = [S] \cdot [V^+]$$

$$[S] = ([Z] - [Z_0]) \cdot ([Z] + [Z_0])^{-1}$$

# A Shift in Reference Planes

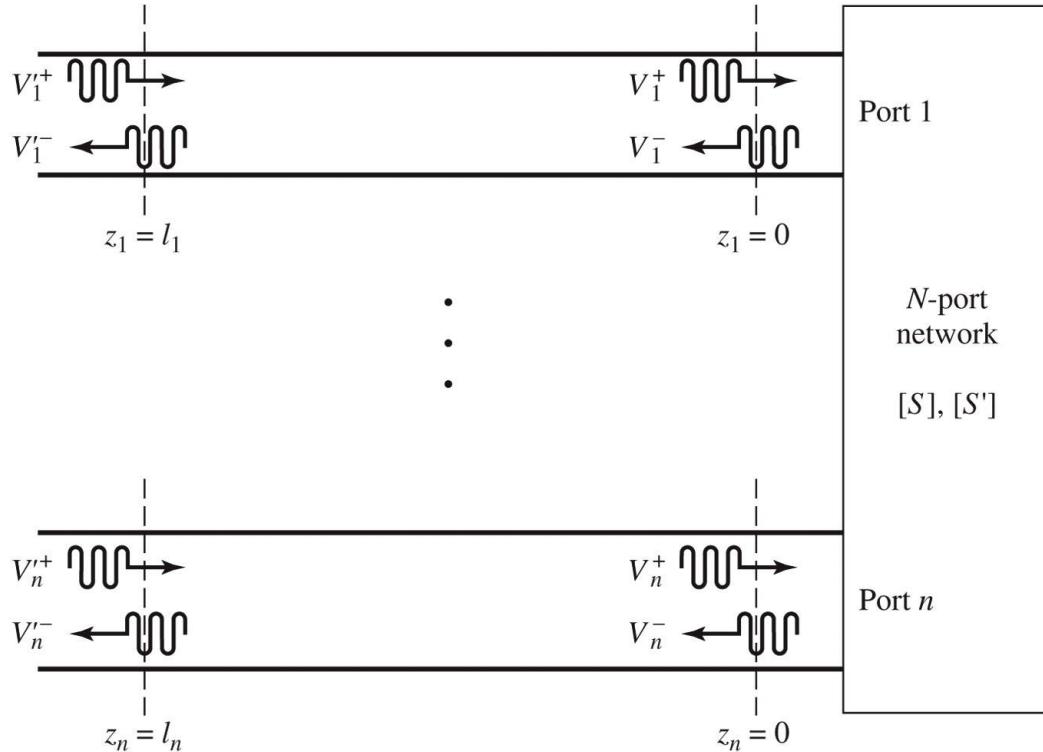

## ■ De-Embedding

Figure 4.9  
© John Wiley & Sons, Inc. All rights reserved.

$$[S'] = \begin{bmatrix} e^{-j\cdot\theta_1} & 0 & \dots & 0 \\ 0 & e^{-j\cdot\theta_2} & 0 & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & \dots & \dots & e^{-j\cdot\theta_N} \end{bmatrix} \cdot [S] \cdot \begin{bmatrix} e^{-j\cdot\theta_1} & 0 & \dots & 0 \\ 0 & e^{-j\cdot\theta_2} & 0 & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & \dots & \dots & e^{-j\cdot\theta_N} \end{bmatrix}$$

# Properties of S matrix (Z,Y)

- Reciprocal networks (no active circuits, no ferrites)

$$Z_{ij} = Z_{ji}, \forall j \neq i$$

$$Y_{ij} = Y_{ji}, \forall j \neq i$$

$$S_{ij} = S_{ji}, \forall j \neq i$$

$$[S] = [S]^t$$

- Lossless networks

$$\operatorname{Re}\{Z_{ij}\} = 0, \forall i, j$$

$$\operatorname{Re}\{Y_{ij}\} = 0, \forall i, j$$

$$\sum_{k=1}^N S_{ki} \cdot S_{kj}^* = \delta_{ij}, \forall i, j$$

$$[S]^* \cdot [S]^t = [1]$$

$$\sum_{k=1}^N S_{ki} \cdot S_{ki}^* = 1$$

$$\sum_{k=1}^N S_{ki} \cdot S_{kj}^* = 0, \forall i \neq j$$

# Generalized Scattering Parameters

- The total voltage and current on a transmission line in terms of the incident and reflected voltage wave amplitudes

$$V = V_0^+ + V_0^- \quad I = \frac{1}{Z_0} \cdot (V_0^+ - V_0^-) \quad \text{In the port's reference plane, } z=0$$

- We find the incident and reflected voltage wave amplitudes

$$V_0^+ = \frac{V + Z_0 \cdot I}{2} \quad V_0^- = \frac{V - Z_0 \cdot I}{2}$$

- The average power delivered to a load :

$$P_L = \frac{1}{2} \cdot \operatorname{Re}\{V \cdot I^*\} = \frac{1}{2 \cdot Z_0} \cdot \operatorname{Re}\left\{ |V_0^+|^2 - V_0^+ \cdot V_0^{-*} + V_0^{+*} \cdot V_0^- - |V_0^-|^2 \right\}$$

$$P_L = \frac{1}{2 \cdot Z_0} \cdot \left( |V_0^+|^2 - |V_0^-|^2 \right)$$

$$(z - z^*) = \operatorname{Im}$$

# Generalized Scattering Parameters

- The average power delivered to a load:

$$P_L = \frac{1}{2 \cdot Z_0} \cdot \left( |V_0^+|^2 - |V_0^-|^2 \right)$$

- Restrictions
  - Result valid for  $Z_0$  real
  - Requires the presence of a line with characteristic impedance  $Z_0$  between the source and the load

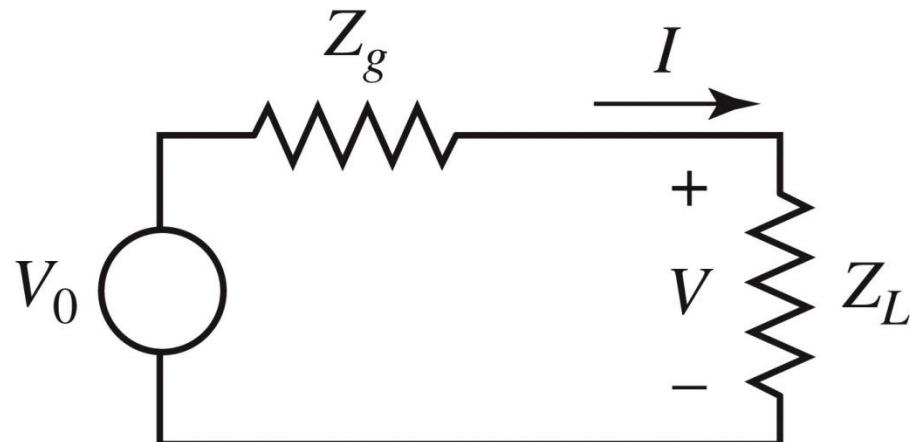


Figure 4.10  
© John Wiley & Sons, Inc. All rights reserved.

# Generalized Scattering Parameters

- We define the power wave amplitudes a and b

$$a = \frac{V + Z_R \cdot I}{2 \cdot \sqrt{R_R}} \text{ the incident power wave} \quad Z_R = R_R + j \cdot X_R$$

$$b = \frac{V - Z_R^* \cdot I}{2 \cdot \sqrt{R_R}} \text{ the reflected power wave}$$


Any complex impedance,  
named reference impedance

- Total voltage and current in terms of the power wave amplitudes

$$V = \frac{Z_R^* \cdot a + Z_R \cdot b}{\sqrt{R_R}}$$

$$I = \frac{a - b}{\sqrt{R_R}}$$

# Reflection and power / Model – L4

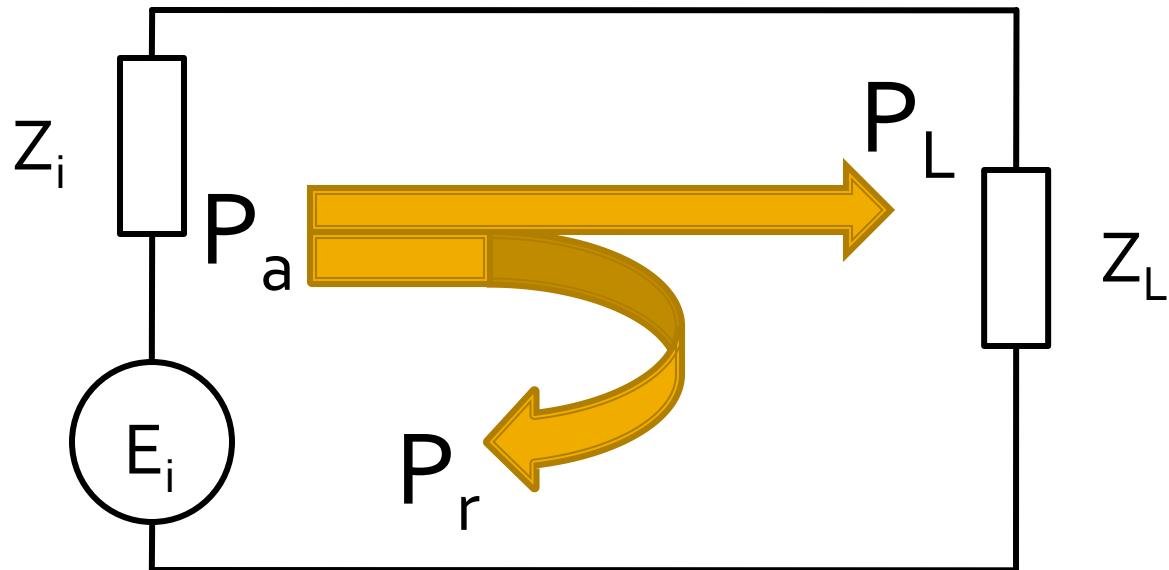

$$P_a = \frac{|E_i|^2}{4R_i}$$


$$P_L = \frac{R_L \cdot |E_i|^2}{(R_i + R_L)^2 + (X_i + X_L)^2}$$

$$\Gamma_L = \frac{Z_L - Z_0^*}{Z_L + Z_0}$$

$$P_r = \frac{|E_i|^2}{4R_i} \cdot \left[ \frac{(R_i - R_L)^2 + (X_i + X_L)^2}{(R_i + R_L)^2 + (X_i + X_L)^2} \right] = P_a \cdot |\Gamma|^2$$

- $\Gamma$ , power reflection coefficient

# Power waves

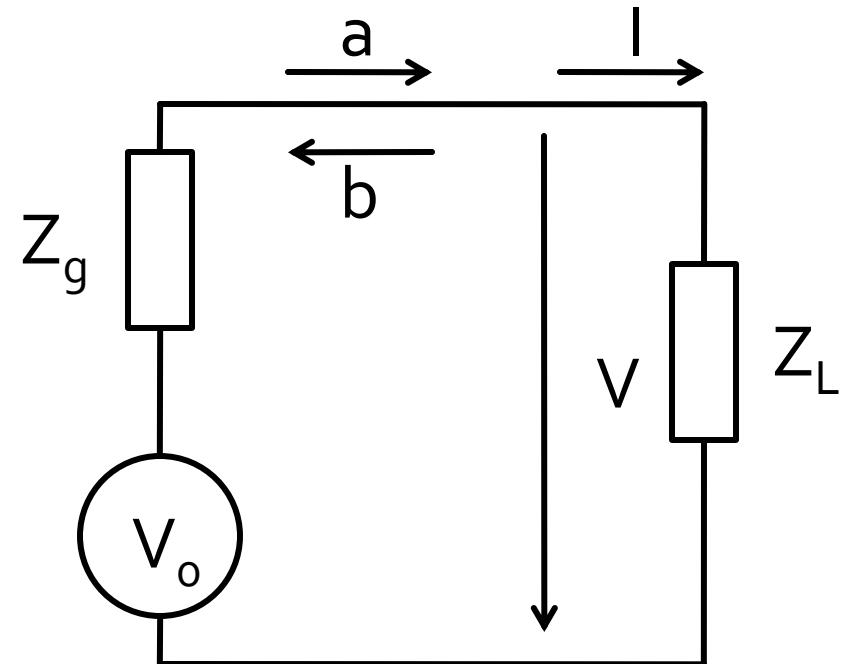

$$P_L = \frac{1}{2} \cdot \text{Re}\{V \cdot I^*\}$$

$$P_L = \frac{1}{2} \cdot \text{Re} \left\{ \frac{Z_R^* \cdot a + Z_R \cdot b}{\sqrt{R_R}} \cdot \left( \frac{a - b}{\sqrt{R_R}} \right)^* \right\}$$

$$P_L = \frac{1}{2R_R} \cdot \text{Re} \left\{ Z_R^* \cdot |a|^2 - Z_R^* \cdot a \cdot b^* + Z_R \cdot a^* \cdot b - Z_R \cdot |b|^2 \right\}$$

$$P_L = \frac{1}{2} \cdot |a|^2 - \frac{1}{2} \cdot |b|^2 \quad (z - z^*) = \text{Im} \quad \forall Z_R \in C$$

$$\Gamma_p = \frac{b}{a} = \frac{V - Z_R^* \cdot I}{V + Z_R \cdot I} = \frac{Z_L - Z_R^*}{Z_L + Z_R}$$

# Power waves

$$V = \frac{V_0 \cdot Z_L}{Z_g + Z_L}$$

$$I = \frac{V_0}{Z_g + Z_L}$$

$$P_L = \frac{V_0^2}{2} \cdot \frac{R_L}{|Z_g + Z_L|^2}$$

■ If we choose

$$Z_R = Z_L^*$$

$$a = \frac{V + Z_R \cdot I}{2 \cdot \sqrt{R_R}} = V_0 \cdot \frac{\frac{Z_L}{Z_g + Z_L} + \frac{Z_L^*}{Z_g + Z_L}}{2 \cdot \sqrt{R_L}} = V_0 \cdot \frac{\sqrt{R_L}}{Z_g + Z_L}$$

$$b = \frac{V - Z_R^* \cdot I}{2 \cdot \sqrt{R_R}} = V_0 \cdot \frac{\frac{Z_L}{Z_g + Z_L} - \frac{Z_L^*}{Z_g + Z_L}}{2 \cdot \sqrt{R_L}} = 0$$

$$P_L = \frac{1}{2} \cdot |a|^2 = \frac{V_0^2}{2} \cdot \frac{R_L}{|Z_g + Z_L|^2}$$

# Power waves

- When the load is conjugately matched to the generator

$$Z_g = Z_L^* \quad P_{L\max} = \frac{1}{2} \cdot |a|^2 = \frac{V_0^2}{8 \cdot R_L}$$

- Power reflection: L4

$$Z_L = Z_i^* \quad P_{L\max} \equiv P_a$$

$$\Gamma = \frac{Z - Z_0^*}{Z + Z_0}$$


$$Z_L \neq Z_i^* \quad P_r = P_a \cdot |\Gamma|^2 \quad P_L = P_a - P_r = P_a - P_a \cdot |\Gamma|^2 = P_a \cdot (1 - |\Gamma|^2)$$

- Power reflection: L5

$$P_{L\max} \equiv P_a = \frac{1}{2} \cdot |a|^2 \quad P_L = \frac{1}{2} \cdot |a|^2 - \frac{1}{2} \cdot |b|^2 \quad \Gamma_p = \frac{b}{a} = \frac{V - Z_R^* \cdot I}{V + Z_R \cdot I} = \frac{Z_L - Z_R^*}{Z_L + Z_R}$$

$$P_L = \frac{1}{2} \cdot |a|^2 - \frac{1}{2} \cdot |a|^2 \cdot |\Gamma_p|^2 \quad P_L = P_a \cdot (1 - |\Gamma_p|^2) \quad P_r = P_a \cdot |\Gamma_p|^2 = \frac{1}{2} \cdot |b|^2$$

# Scattering matrix for power waves

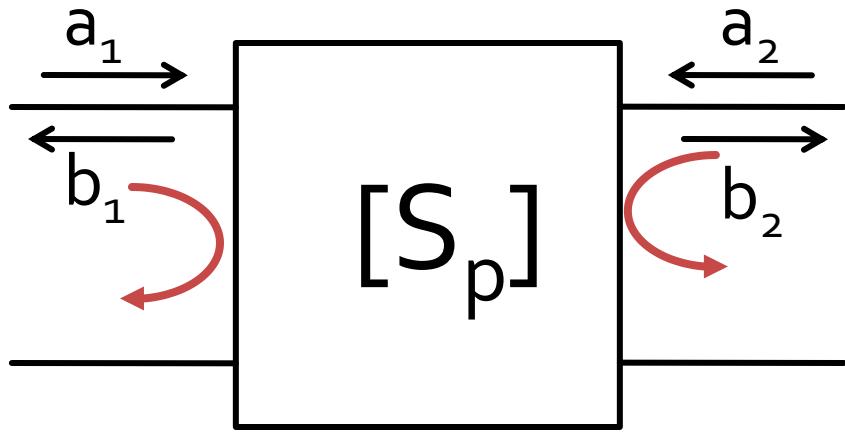

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S'_{11} & S'_{12} \\ S'_{21} & S'_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S'_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0}$$

$$S'_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

# Power waves

- To define the scattering matrix for power waves for an N-port network

$$[Z_R] = \begin{bmatrix} Z_{R1} & \cdots & 0 \\ \vdots & \ddots & \vdots \\ 0 & \cdots & Z_{Rn} \end{bmatrix} \quad [F] = \begin{bmatrix} 1/2\sqrt{R_{R1}} & \cdots & 0 \\ \vdots & \ddots & \vdots \\ 0 & \cdots & 1/2\sqrt{R_{Rn}} \end{bmatrix}$$

$$[a] = [F] \cdot ([V] + [Z_R] \cdot [I])$$

$$[b] = [F] \cdot ([V] - [Z_R]^* \cdot [I])$$

$$[Z] \cdot [I] = [V]$$

# Power waves for N ports

$$[b] = [F] \cdot ([Z] - [Z_R]^*) \cdot ([Z] + [Z_R])^{-1} \cdot [F]^{-1} \cdot [a]$$

- The scattering matrix for power waves,  $[S_p]$

$$[b] = [S_p] \cdot [a]$$

$$[S_p] = [F] \cdot ([Z] - [Z_R]^*) \cdot ([Z] + [Z_R])^{-1} \cdot [F]^{-1}$$

- But:  $[S] = ([Z] - [Z_0]) \cdot ([Z] + [Z_0])^{-1}$

- Typically


$$Z_{0i} = Z_{Ri} = R_0, \forall i$$

$$R_0 = 50\Omega$$

$$[S_p] \equiv [S]$$

- they coincide!!!

# Scattering matrix – $S$

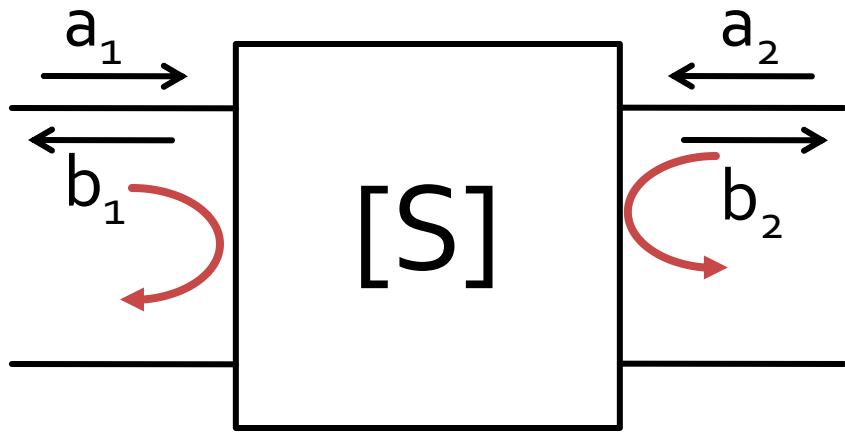


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{11} = \frac{b_1}{a_1} \Big|_{a_2=0}$$

$$S_{22} = \frac{b_2}{a_2} \Big|_{a_1=0}$$

- $S_{11}$  and  $S_{22}$  are reflection coefficients at ports 1 and 2 when the other port is matched

# Scattering matrix – $S$

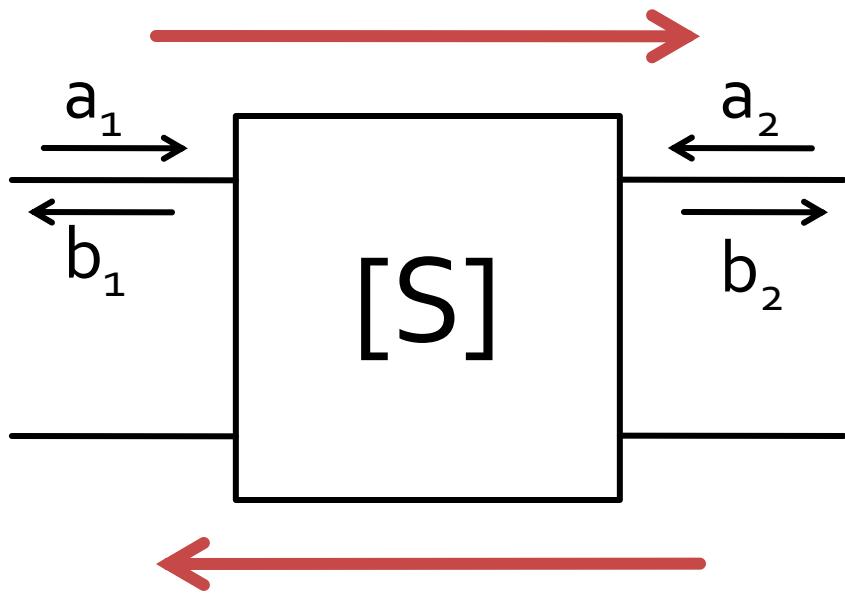


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0}$$

$$S_{12} = \frac{b_1}{a_2} \Big|_{a_1=0}$$

- $S_{21}$  si  $S_{12}$  are signal amplitude gain when the other port is matched

# Scattering matrix – S

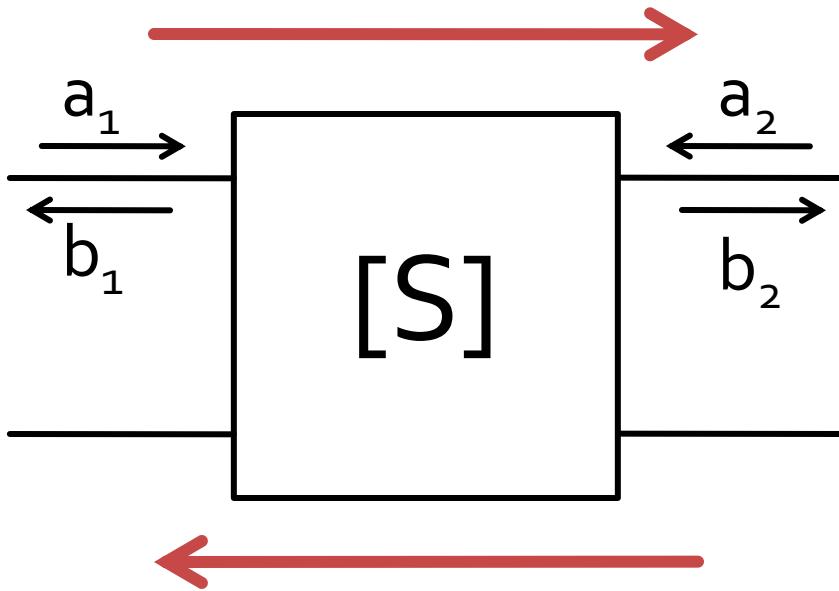

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- a,b
  - information about signal power **AND** signal phase
- $S_{ij}$ 
  - network effect (gain) over signal power **including** phase information

# Measuring S parameters - VNA

## ■ Vector Network Analyzer

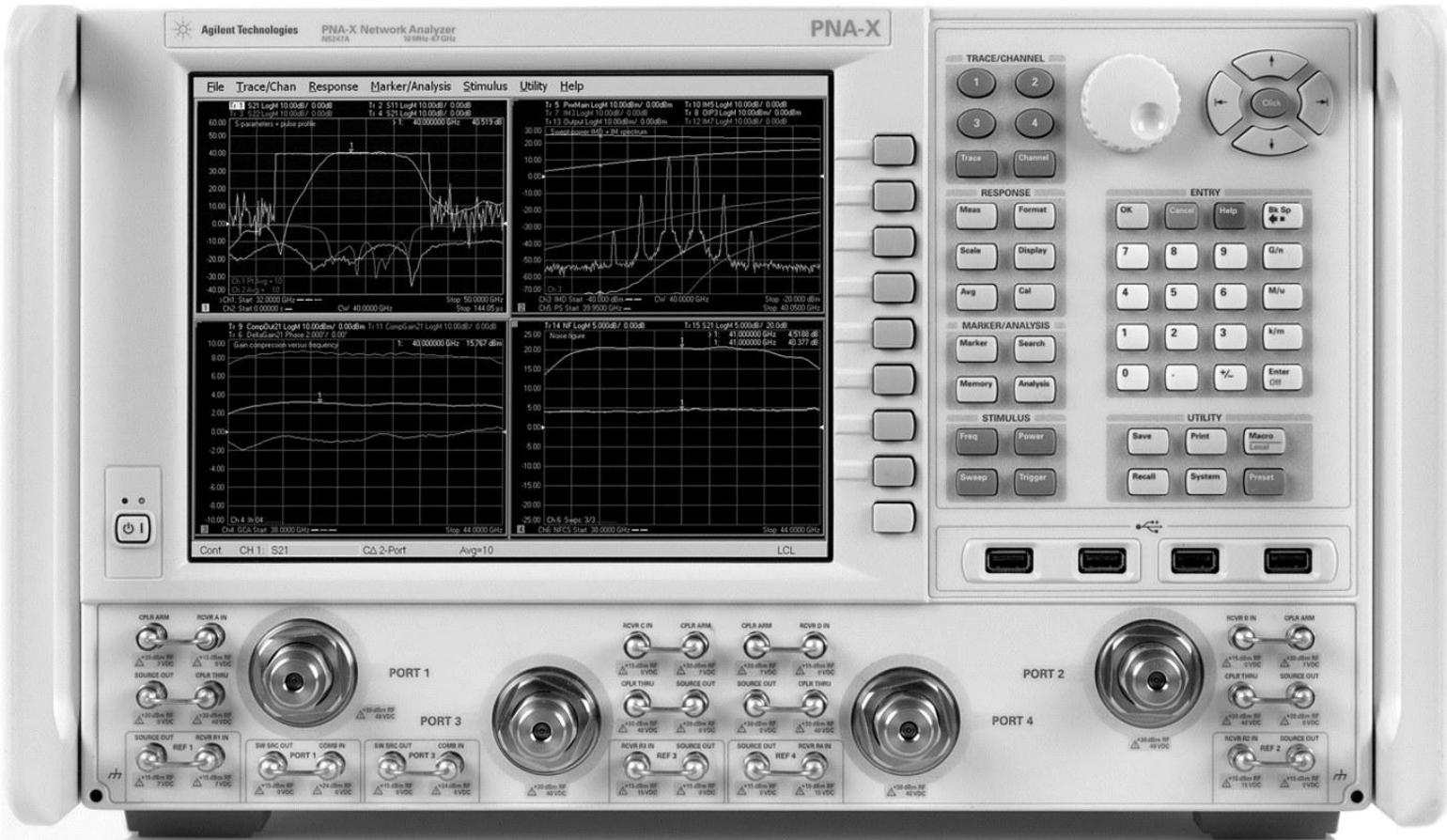


Figure 4.7  
Courtesy of Agilent Technologies

# Relation between two port S parameters and ABCD parameters

$$A = \sqrt{\frac{Z_{01}}{Z_{02}}} \frac{(1 + S_{11} - S_{22} - \Delta S)}{2S_{21}}$$

$$B = \sqrt{Z_{01}Z_{02}} \frac{(1 + S_{11} + S_{22} + \Delta S)}{2S_{21}}$$

$$C = \frac{1}{\sqrt{Z_{01}Z_{02}}} \frac{1 - S_{11} - S_{22} + \Delta S}{2S_{21}}$$

$$D = \sqrt{\frac{Z_{02}}{Z_{01}}} \frac{1 - S_{11} + S_{22} - \Delta S}{2S_{21}}$$

$$\Delta S = S_{11}S_{22} - S_{12}S_{21}$$

$$S_{11} = \frac{AZ_{02} + B - CZ_{01}Z_{02} - DZ_{01}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

$$S_{12} = \frac{2(AD - BC)\sqrt{Z_{01}Z_{02}}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$


$$S_{21} = \frac{2\sqrt{Z_{01}Z_{02}}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

$$S_{22} = \frac{-AZ_{02} + B - CZ_{01}Z_{02} + DZ_{01}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

# Even/Odd Mode Analysis
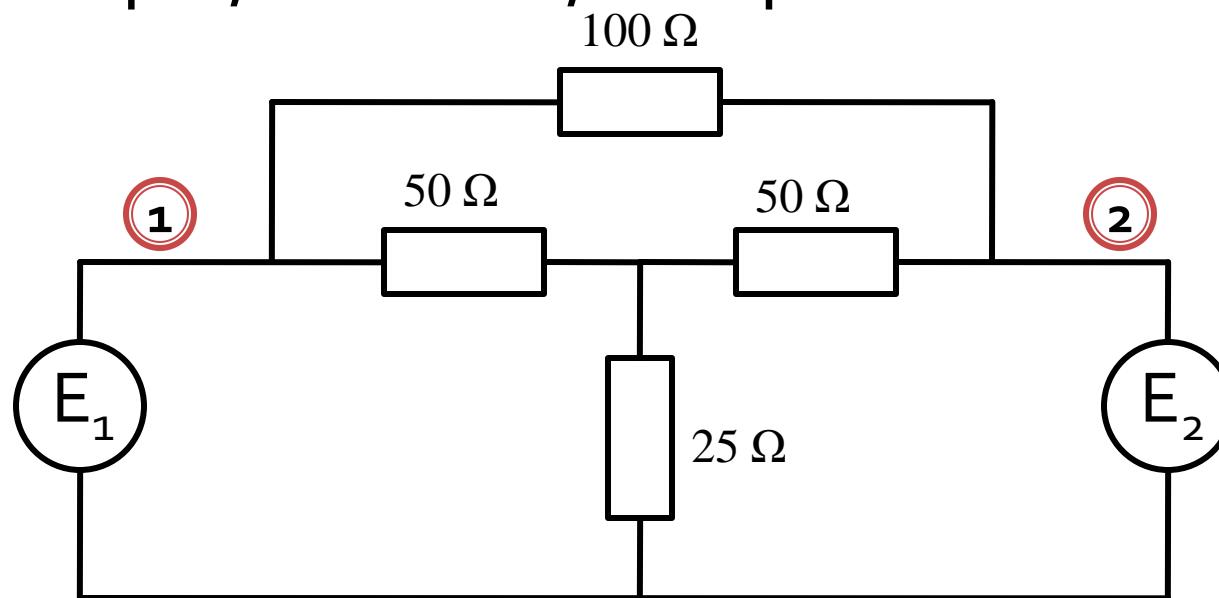
# Even/Odd Mode Analysis



- useful method, necessary even for multiple ports
- example, resistors, two port circuit



# Even/Odd Mode Analysis

- assume we want to compute  $Y_{11}$
- $E_2 = 0$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

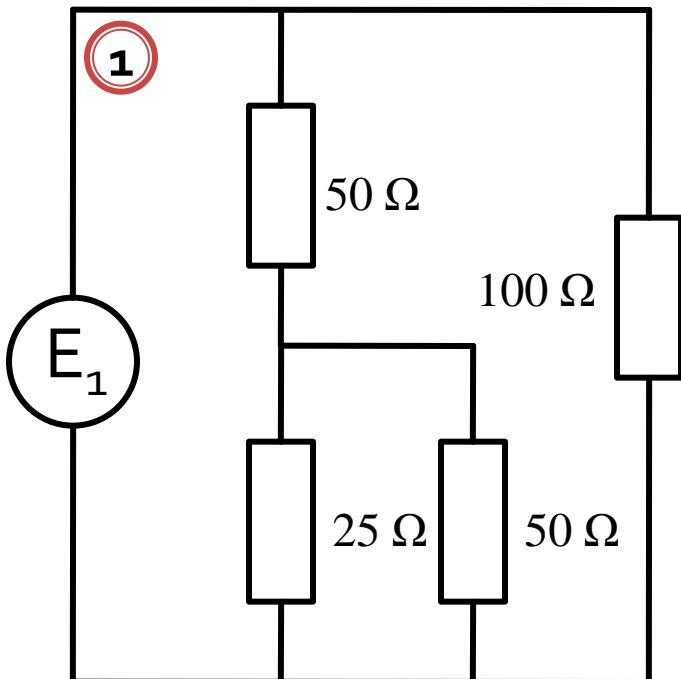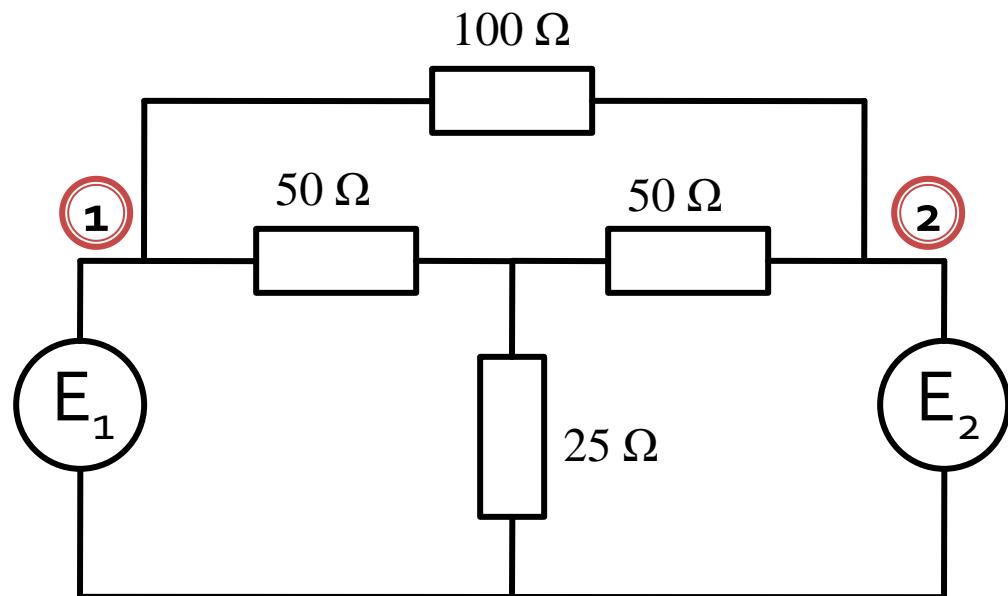


$$\begin{aligned} R_{ech} &= 100\Omega \parallel (50\Omega + 25\Omega \parallel 50\Omega) = \\ &= 100\Omega \parallel (50\Omega + 16.67\Omega) = 100\Omega \parallel 66.67\Omega = 40\Omega \end{aligned}$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = 0.025S$$


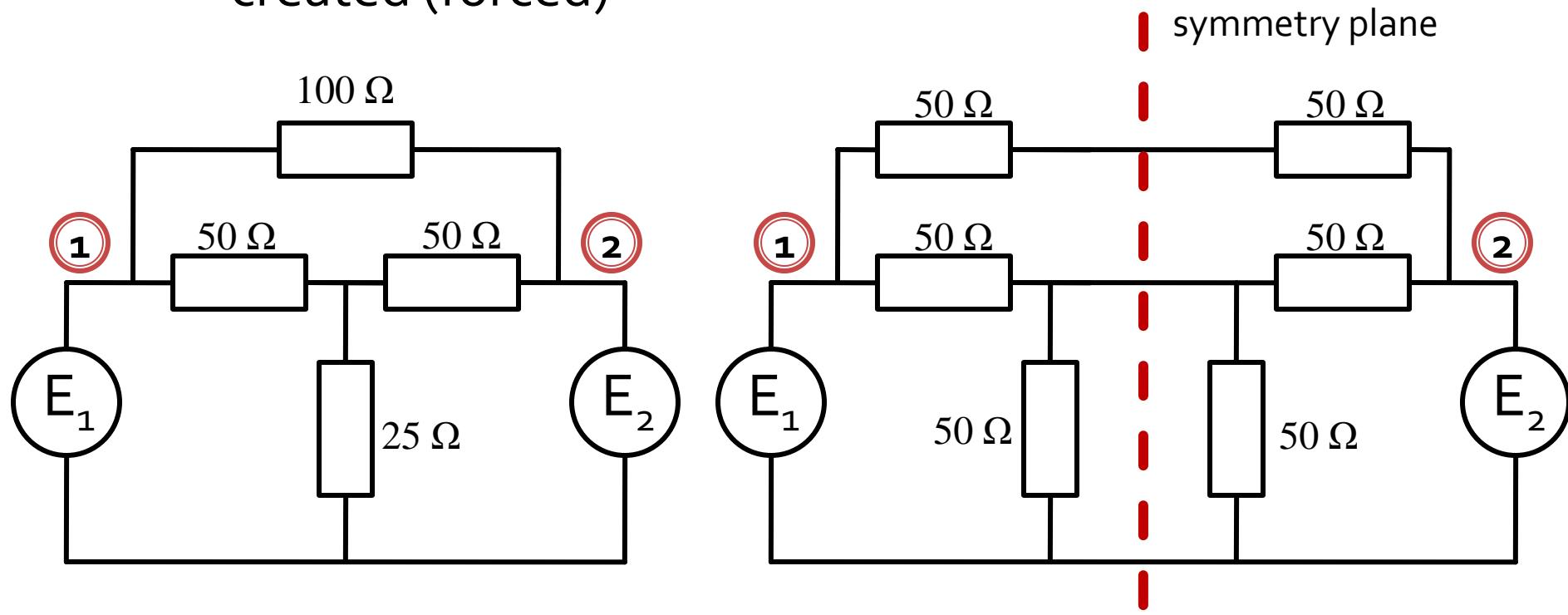
# Even/Odd Mode Analysis

- Even/Odd mode analysis benefit from the existence of symmetry planes in the circuit
  - existing or
  - created (forced)



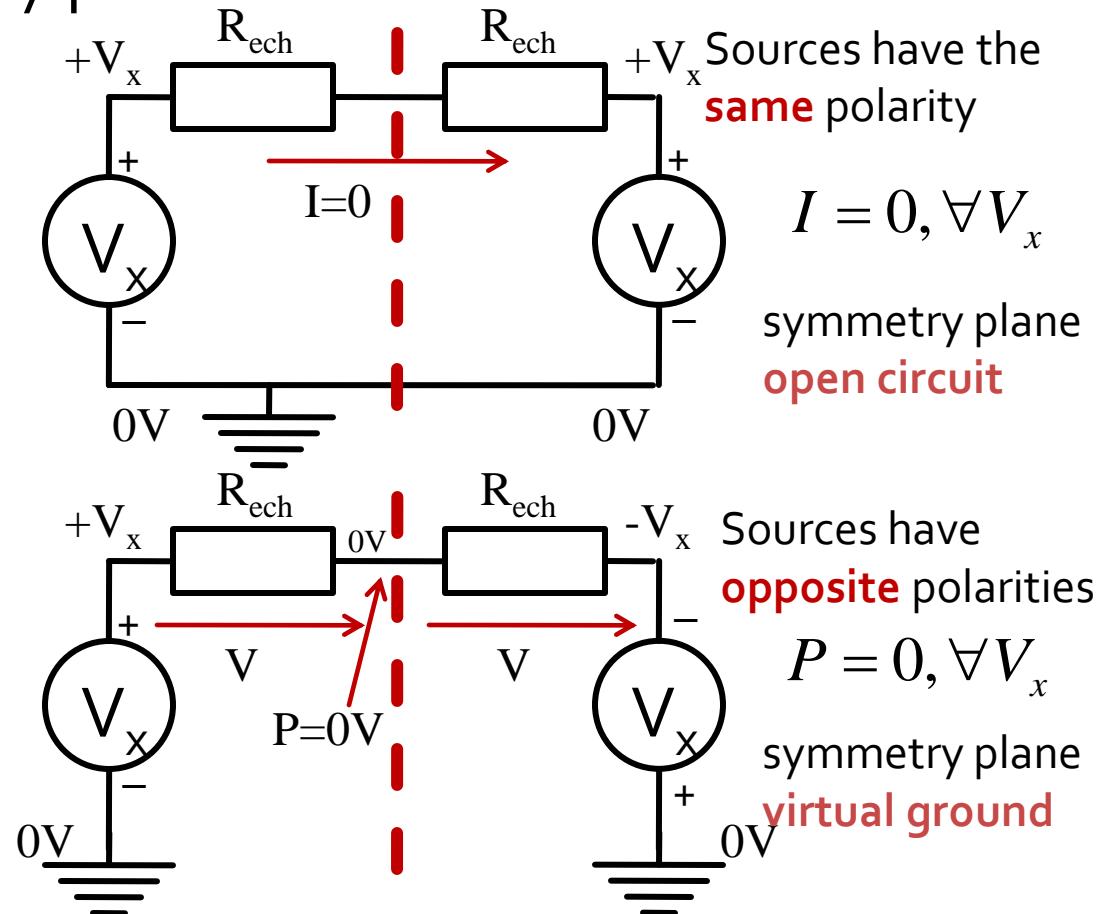
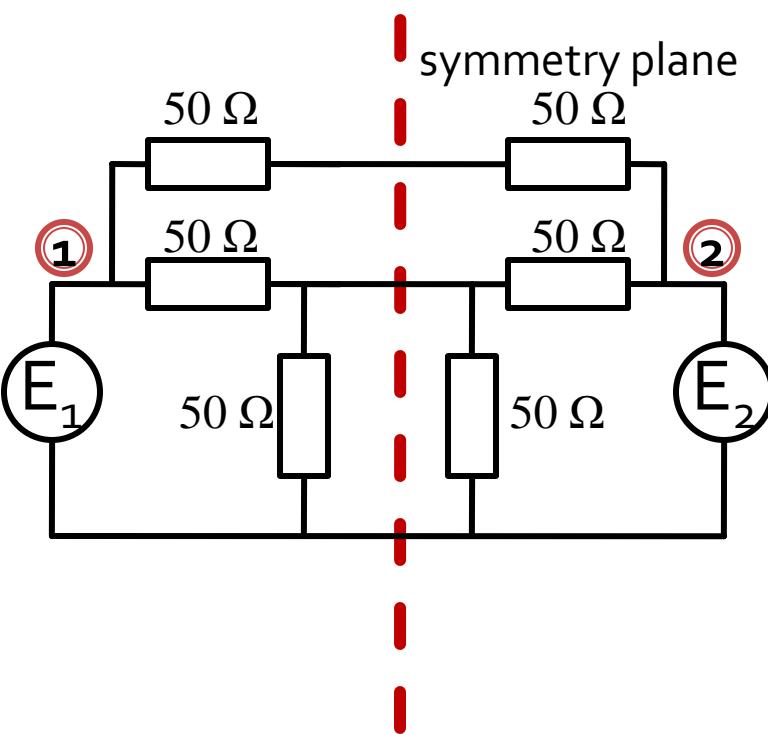
# Even/Odd Mode Analysis

- when exciting the ports with symmetric/anti-symmetric sources the symmetry planes are transformed into:
  - open circuit
  - virtual ground


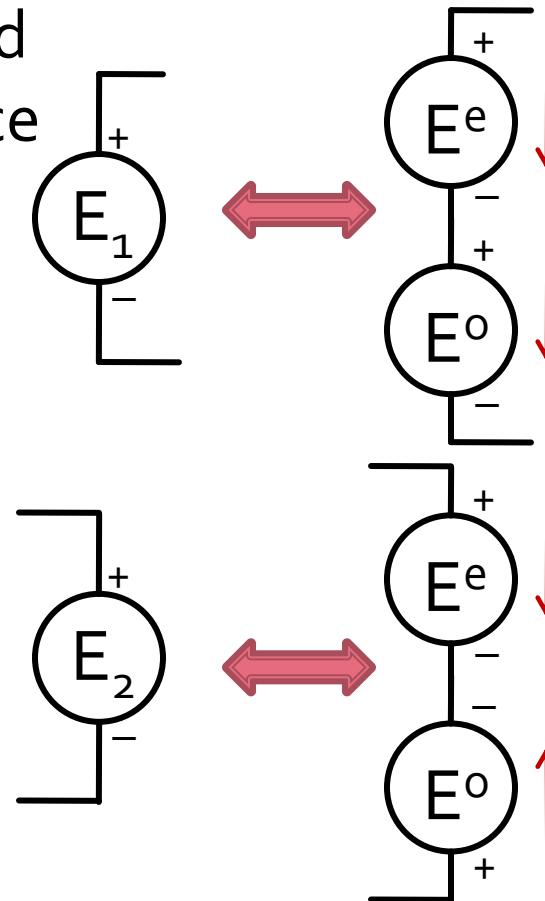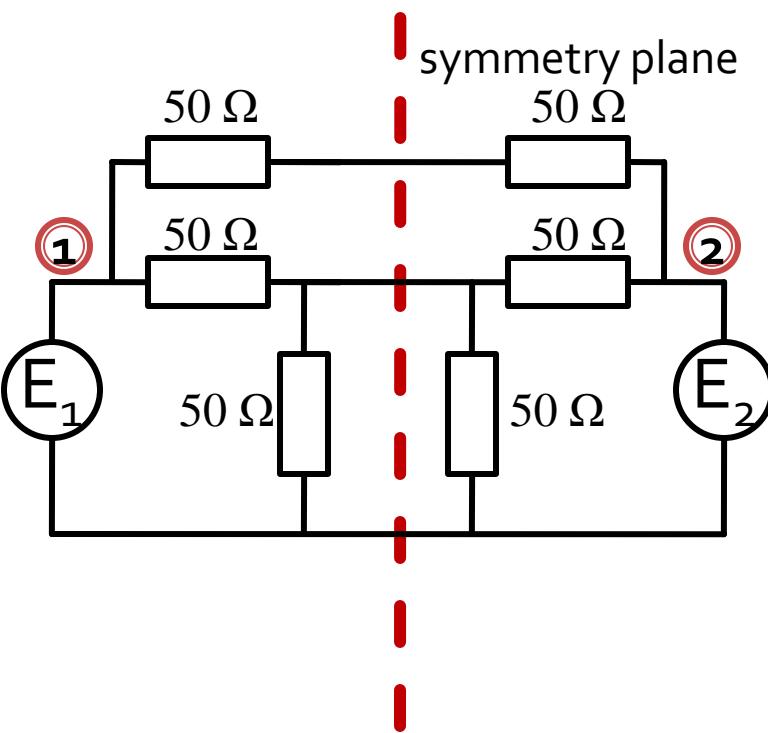
# Even/Odd Mode Analysis

- the combination of any two sources is equivalent for linear circuits with the superposition of:
  - a symmetric source and
  - a anti-symmetric source



$$E_1 = E^e + E^o$$

$$E_2 = E^e - E^o$$

$$E^e = \frac{E_1 + E_2}{2}$$

$$E^o = \frac{E_1 - E_2}{2}$$


# Even/Odd Mode Analysis

- In linear circuits the **superposition principle** is always true
  - the response caused by two or more stimuli is the sum of the responses that would have been caused by each stimulus individually

**Response ( Source1 + Source2 ) =**

$$= \text{Response (Source1)} + \text{Response (Source2)}$$

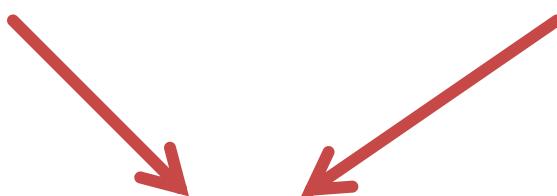
**Response( ODD + EVEN ) = Response ( ODD ) + Response ( EVEN )**



We can benefit from existing symmetries !!

# Even/Odd Mode Analysis

- example

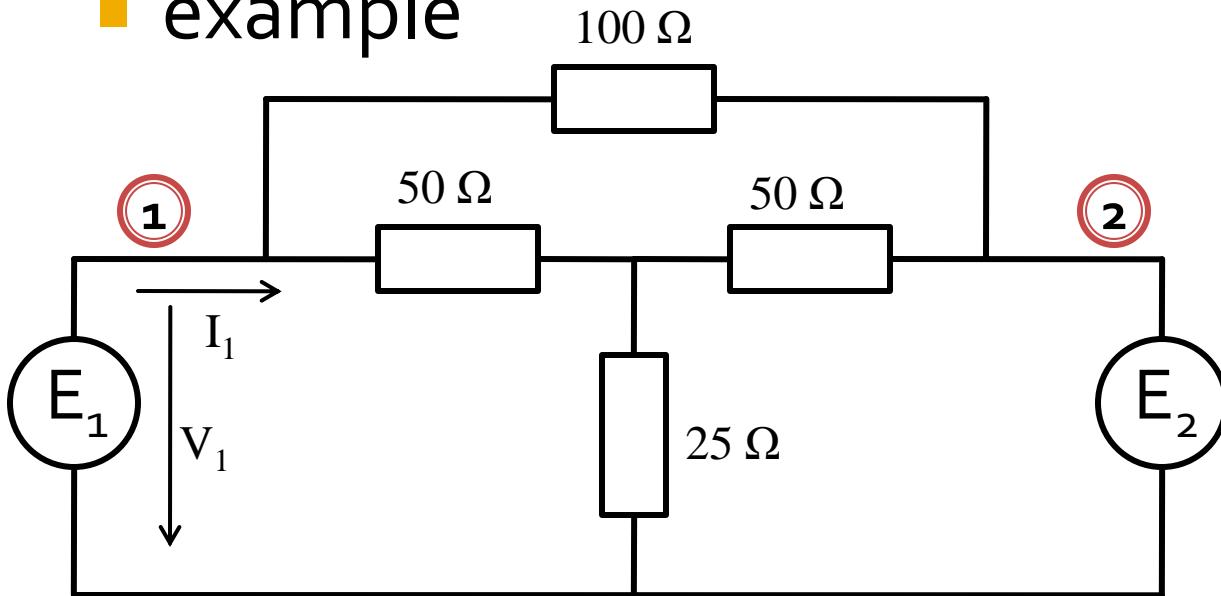


$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$V_2 \equiv E_2 = 0 \Rightarrow$$


$$E^e = \frac{E_1}{2}$$

$$E^o = \frac{E_1}{2}$$

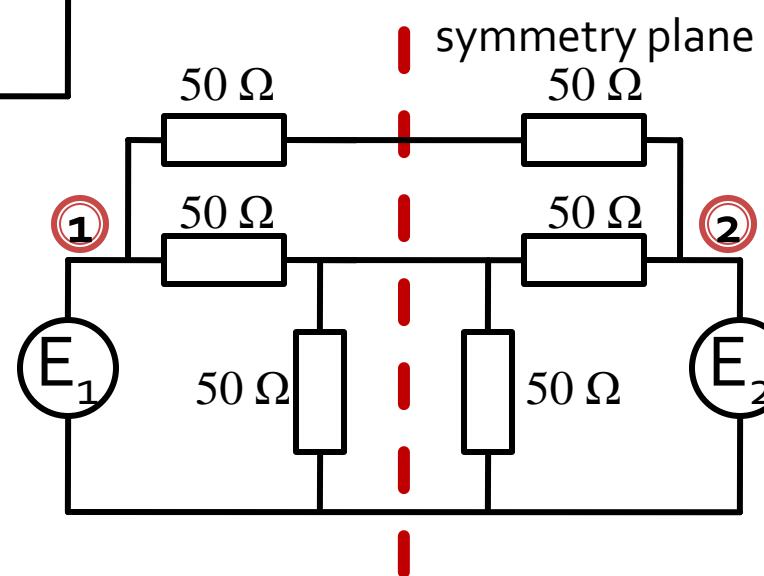

# Even/Odd Mode Analysis


- Even/Odd mode analysis

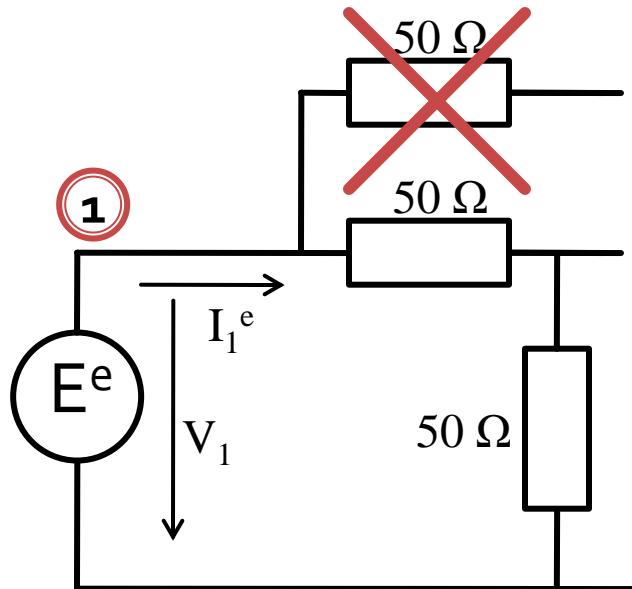

$$R_{ech}^e = 50\Omega + 50\Omega = 100\Omega$$

$$I_1^e = \frac{E^e}{R_{ech}^e} = \frac{E_1/2}{100\Omega} = \frac{E_1}{200\Omega}$$

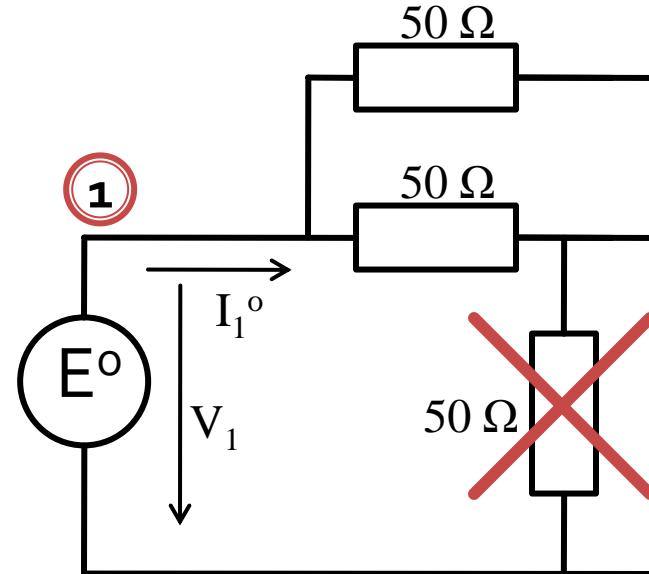**EVEN** → symmetry plane **open circuit**




$$R_{ech}^o = 50\Omega || 50\Omega = 25\Omega$$

$$I_1^o = \frac{E^o}{R_{ech}^o} = \frac{E_1/2}{25\Omega} = \frac{E_1}{50\Omega}$$

**ODD** → symmetry plane **virtual ground**

# Even/Odd Mode Analysis

- superposition principle

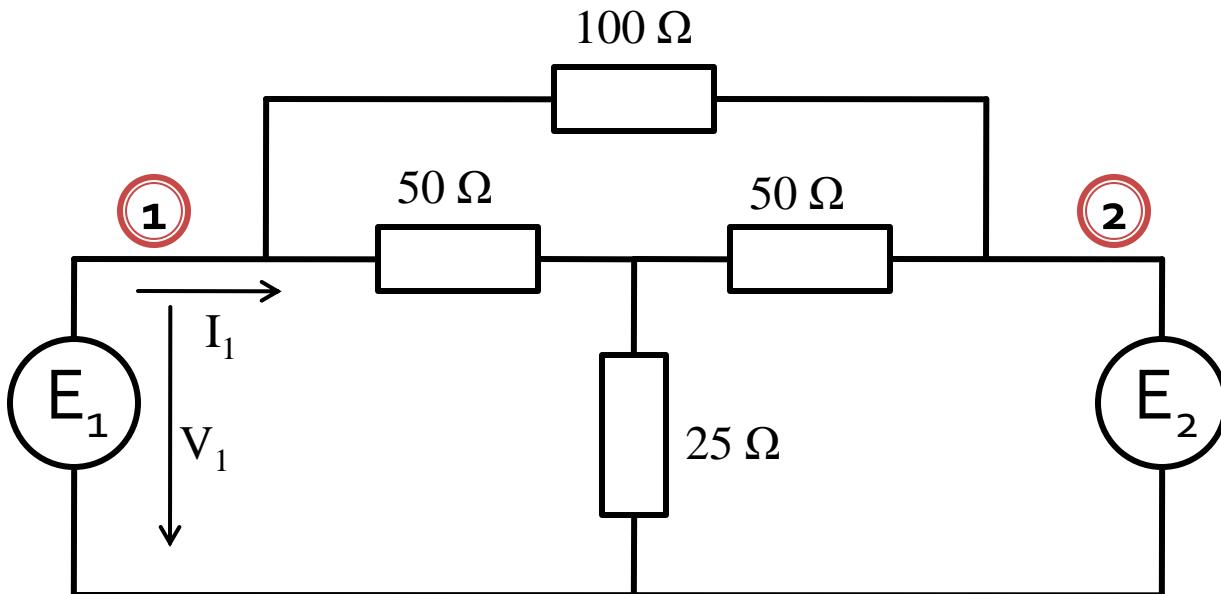

$$I_1 = I_1^e + I_1^o$$

$$V_1 = V_1^e + V_1^o$$

$$I_1 = I_1^e + I_1^o = \frac{E_1}{200\Omega} + \frac{E_1}{50\Omega} = \frac{E_1}{40\Omega}$$


$$V_1 = V_1^e + V_1^o = E_1$$

$$Y_{11} = \frac{I_1}{V_1} = \frac{1}{40\Omega} = 0.025S$$
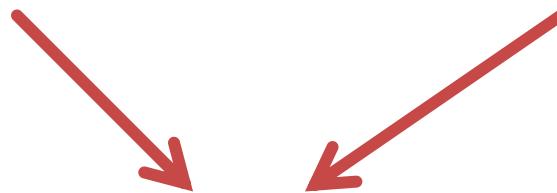
# Even/Odd Mode Analysis

- In linear circuits we can use the superposition principle
- advantages
  - reduction of the circuit complexity
  - decrease of the number of ports (**main** advantage)

$$\text{Response (ODD + EVEN)} = \text{Response (ODD)} + \text{Response (EVEN)}$$



We can benefit from existing symmetries !!

# Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.eti.tuiasi.ro>
- [rdamian@etti.tuiasi.ro](mailto:rdamian@etti.tuiasi.ro)