

Lecture 6

2020/2021

Microwave Devices and Circuits for Radiocommunications

2020/2021

- 2C/1L, **MDCR**
- Attendance at minimum 7 sessions (course + laboratory)
- Lectures- **associate professor Radu Damian**
 - Wednesday 15-17, Online, Microsoft Teams
 - E – 50% final grade
 - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
 - 3p=+0.5p
 - all materials/equipments authorized

Materials

- RF-OPTO
 - <http://rf-opto.etti.tuiasi.ro>
- **David Pozar, “Microwave Engineering”,**
Wiley; 4th edition , 2011
 - 1 exam problem ← Pozar
- Photos
 - sent by email/online exam
 - used at lectures/laboratory

Profile photo

- Profile photo – online “exam”

Examene online: 2020/2021

Disciplina: MDC (Microwave Devices and Circuits (Engleza))

Pas 3

Nr.	Titlu	Start	Stop	Text
1	Profile photos	03/03/2021; 10:00	08/04/2021; 08:00	Online "exam" created f ..
2	Mini Test 1 (lecture 2)	03/03/2021; 15:35	03/03/2021; 15:50	The current test consis ..

Online

- access to **online exams** requires the **password** received by email

English | Romana |

Main Courses Master Staff Research **Student**

Grades Student List Exams Photos

POPESCU GOPO ION

Fotografia nu exista

Date:

Grupa	5700 (2019/2020)
Specializarea	Inginerie electronica si telecomunicatii
Marca	7000000

[Access the site as this student](#) | [request access to software](#)

Grades

Inca nu a fost notat.

Main Courses Master Staff Research

Grades **Student List** Exams Photos

Login

Use the last name and email stored in the database

Name

POPESCU GOPO

Email/Password

Write the code below



828f26b

Send

Online results submission

- many numerical values

	Z1	Z2	Z3	Z4	Z5	Z6	Z7
	148.33	155.88	202.12	164.35	180.91	30.29	185.19
	25.97	153.5	34.64	35.79	55.56	26.212	10.693
	0	0	0	0	0	0	0
	50	50	50	50	50	50	50

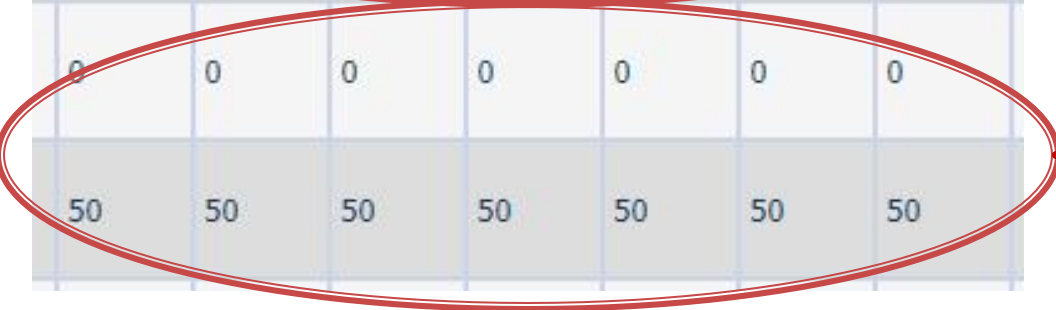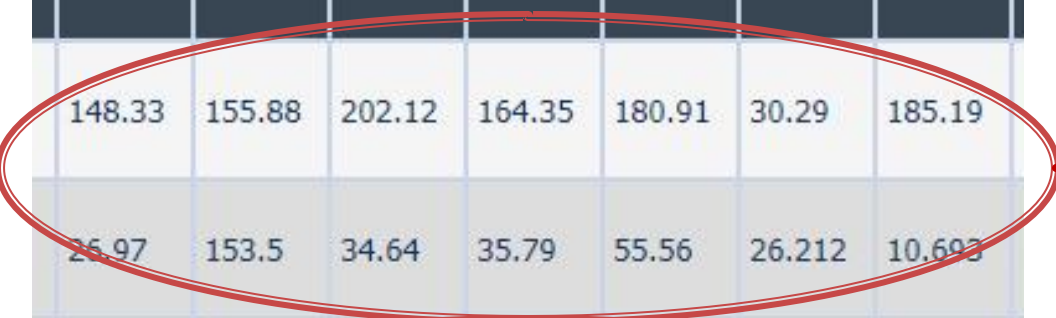


Online results submission

Grade = Quality of the work +
+ Quality of the submission

Important


The lossless line

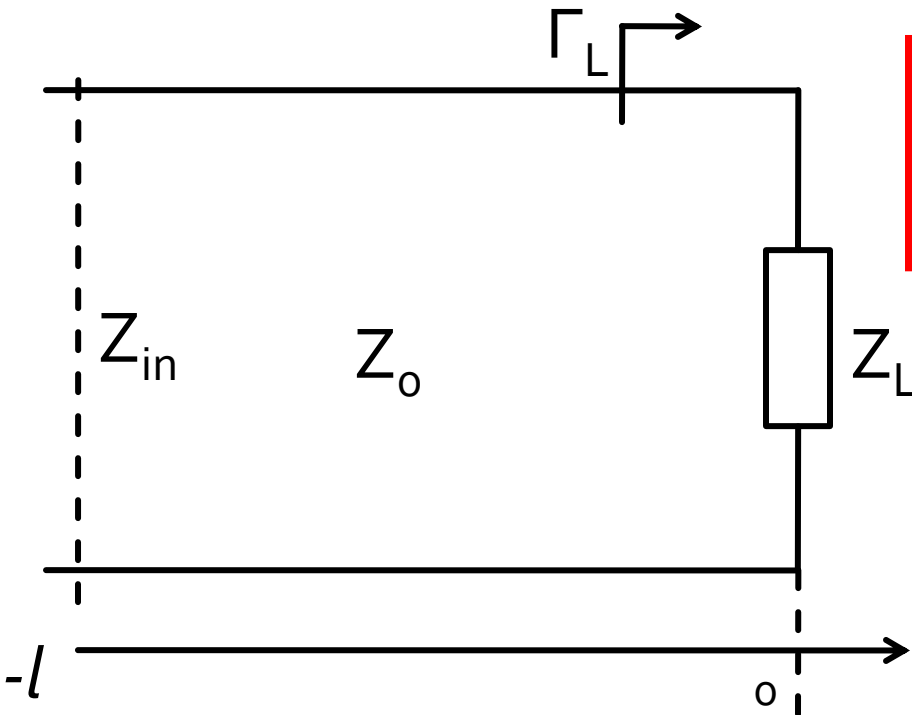- input impedance of a length l of transmission line with characteristic impedance Z_0 , loaded with an arbitrary impedance Z_L



$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

The lossless line

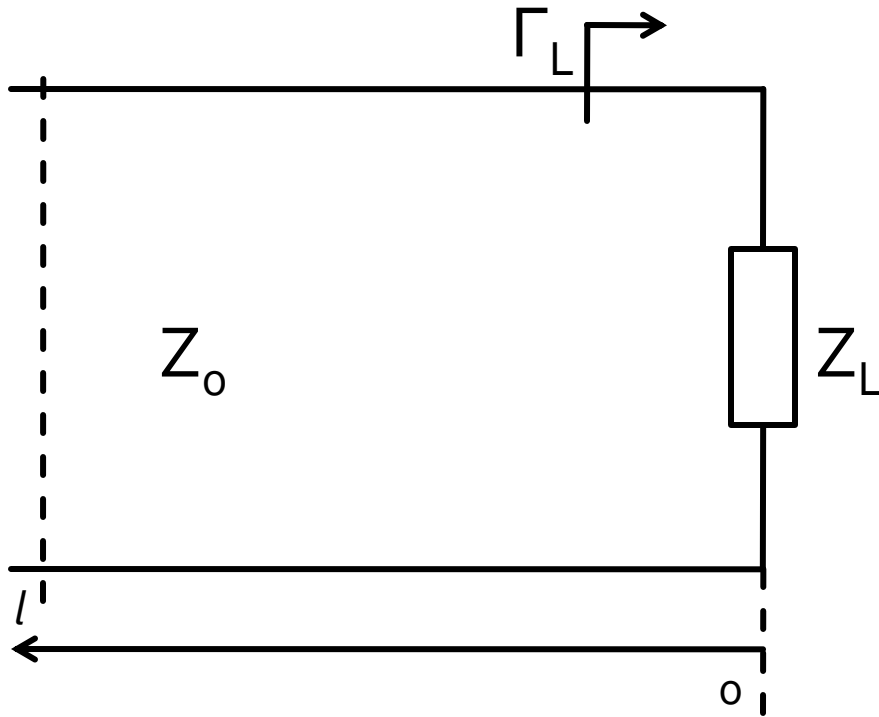

$$V(z) = V_0^+ e^{-j\beta \cdot z} + V_0^- e^{j\beta \cdot z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta \cdot z} - \frac{V_0^-}{Z_0} e^{j\beta \cdot z}$$

$$Z_L = \frac{V(0)}{I(0)} \quad Z_L = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \cdot Z_0$$

- voltage reflection coefficient

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

- Z_0 real

The lossless line


$$V(z) = V_0^+ \cdot (e^{-j\beta \cdot z} + \Gamma \cdot e^{j\beta \cdot z}) \quad I(z) = \frac{V_0^+}{Z_0} \cdot (e^{-j\beta \cdot z} - \Gamma \cdot e^{j\beta \cdot z})$$

- time-average Power flow along the line

$$P_{avg} = \frac{1}{2} \cdot \text{Re}\{V(z) \cdot I(z)^*\} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot \text{Re}\left\{1 - \Gamma^* \cdot \underbrace{e^{-2j\beta \cdot z} + \Gamma \cdot e^{2j\beta \cdot z}}_{(z - z^*) = \text{Im}} - |\Gamma|^2\right\}$$
$$P_{avg} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot (1 - |\Gamma|^2)$$

- Total power delivered to the load = Incident power – “Reflected” power
- Return “Loss” [dB] $RL = -20 \cdot \log|\Gamma| \quad [\text{dB}]$

Reflection and power / Model

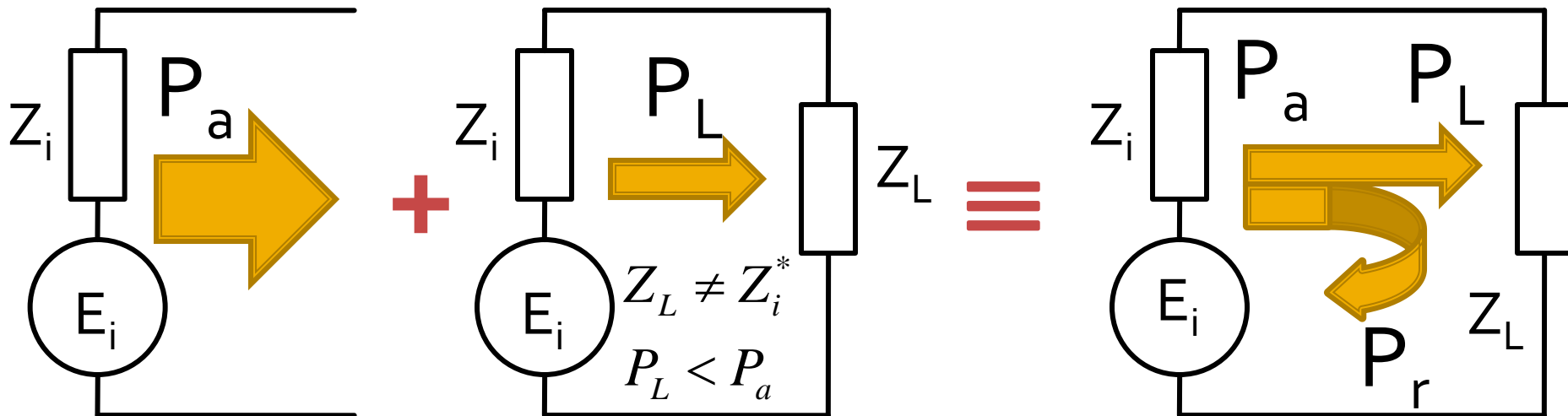

- The source has the ability to send to the load a certain maximum power (available power) P_a
- For a particular load the power sent to the load is less than the maximum (mismatch) $P_L < P_a$
- The phenomenon is **"as if"** (model) some of the power is reflected $P_r = P_a - P_L$
- The power is a **scalar** !

Matching , from the point of view of power transmission


$$Z_L = Z_i^*$$

If we choose a real Z_0


$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

$$\Gamma_L = \Gamma_i^*$$

- complex numbers
- in the complex plane

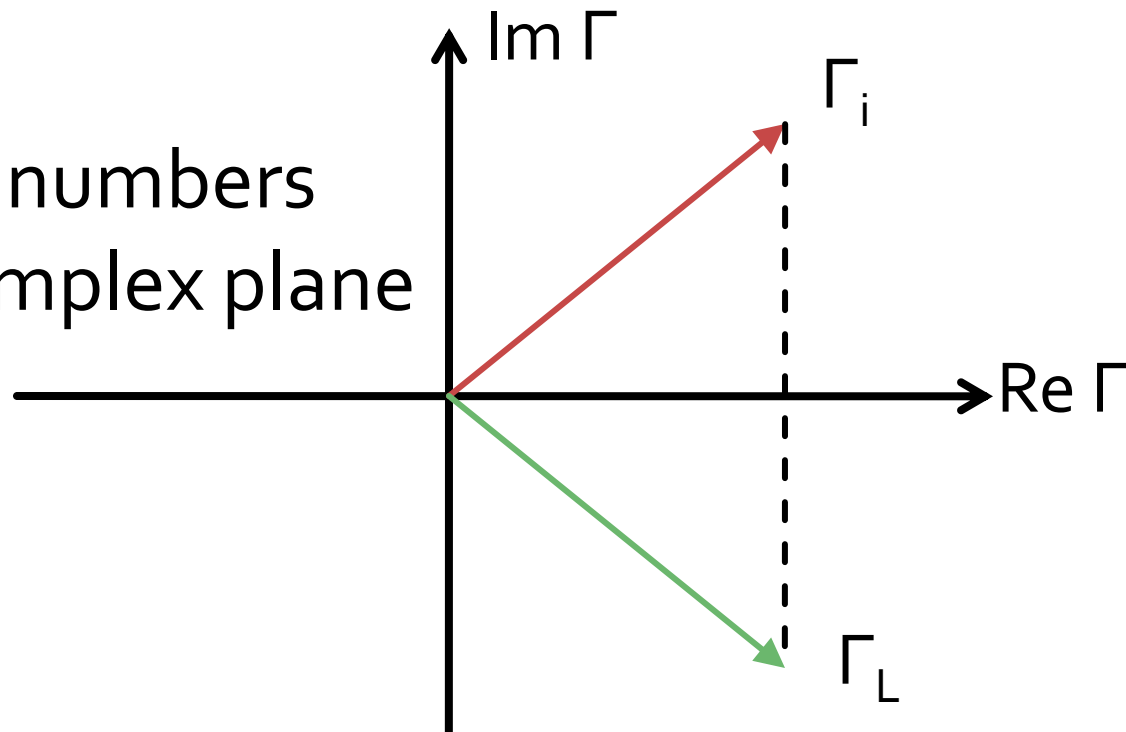

Scattering matrix – S

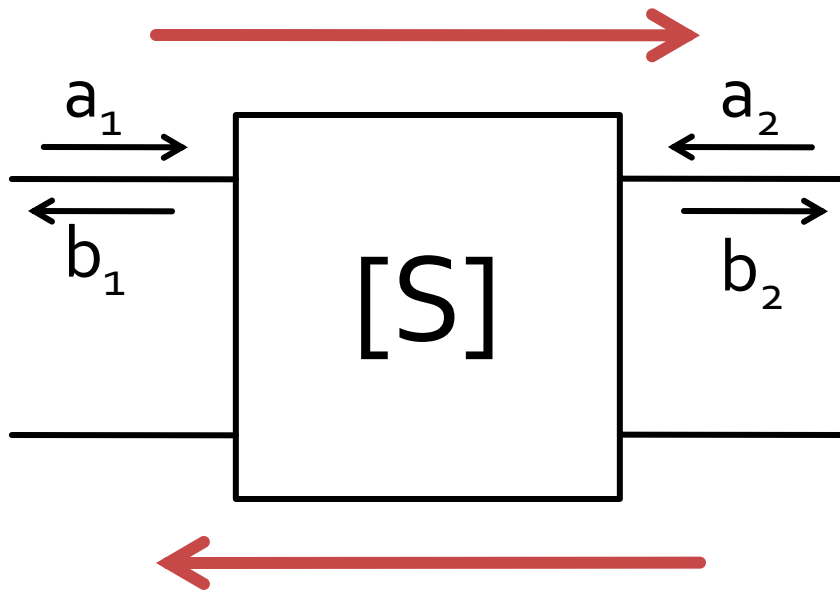

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- a, b
 - information about signal power **AND** signal phase
- S_{ij}
 - network effect (gain) over signal power **including** phase information

Power dividers and directional couplers

Course Topics

- Transmission lines
- Impedance matching and tuning
- **Directional couplers**
- **Power dividers**
- Microwave amplifier design
- Microwave filters
- ~~Oscillators and mixers~~

Introduction

Power dividers and couplers

- Desired functionality:
 - division
 - combining
- of signal power


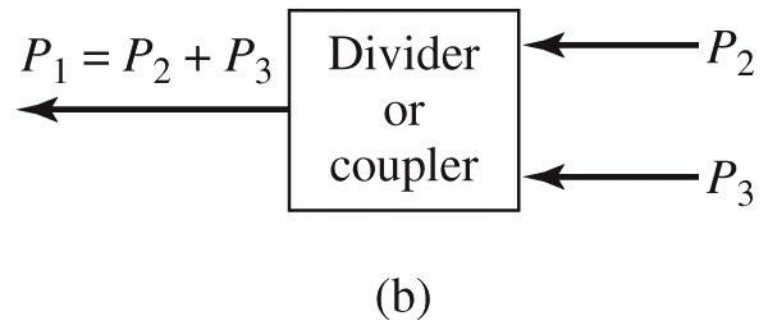
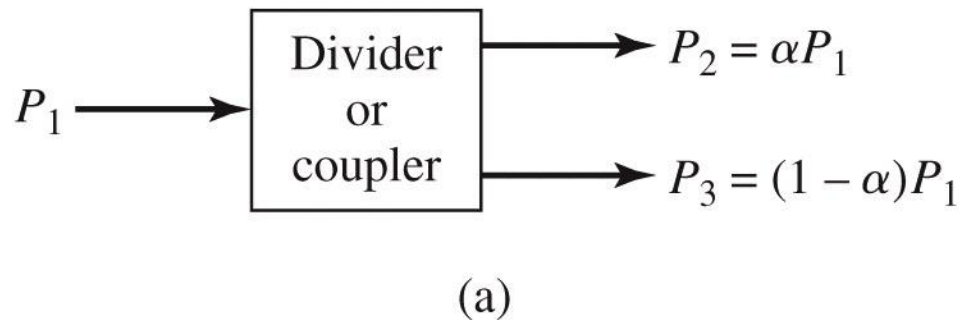



Figure 7.1
© John Wiley & Sons, Inc. All rights reserved.

Balanced amplifiers

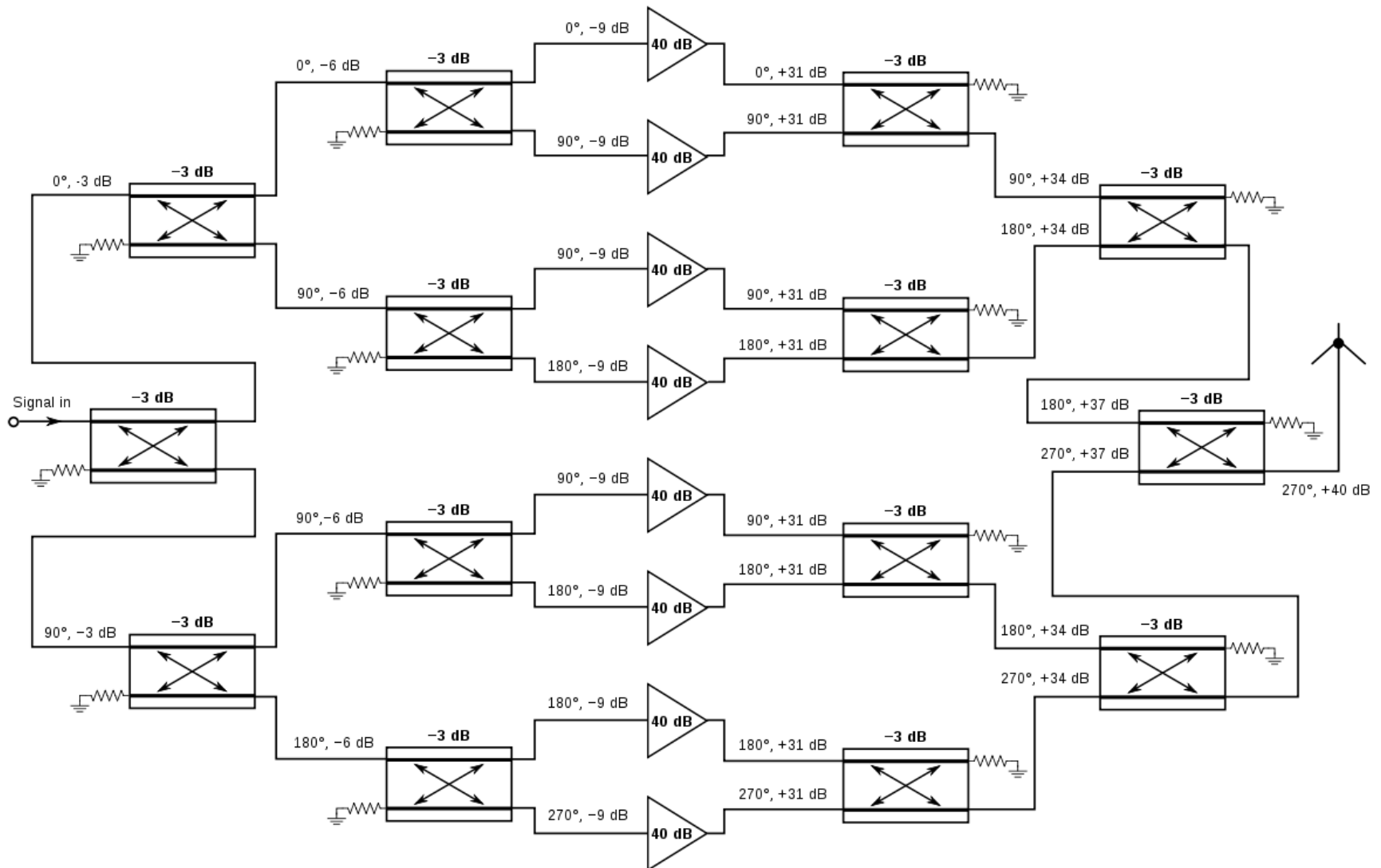

Matching

- feedback amplifier

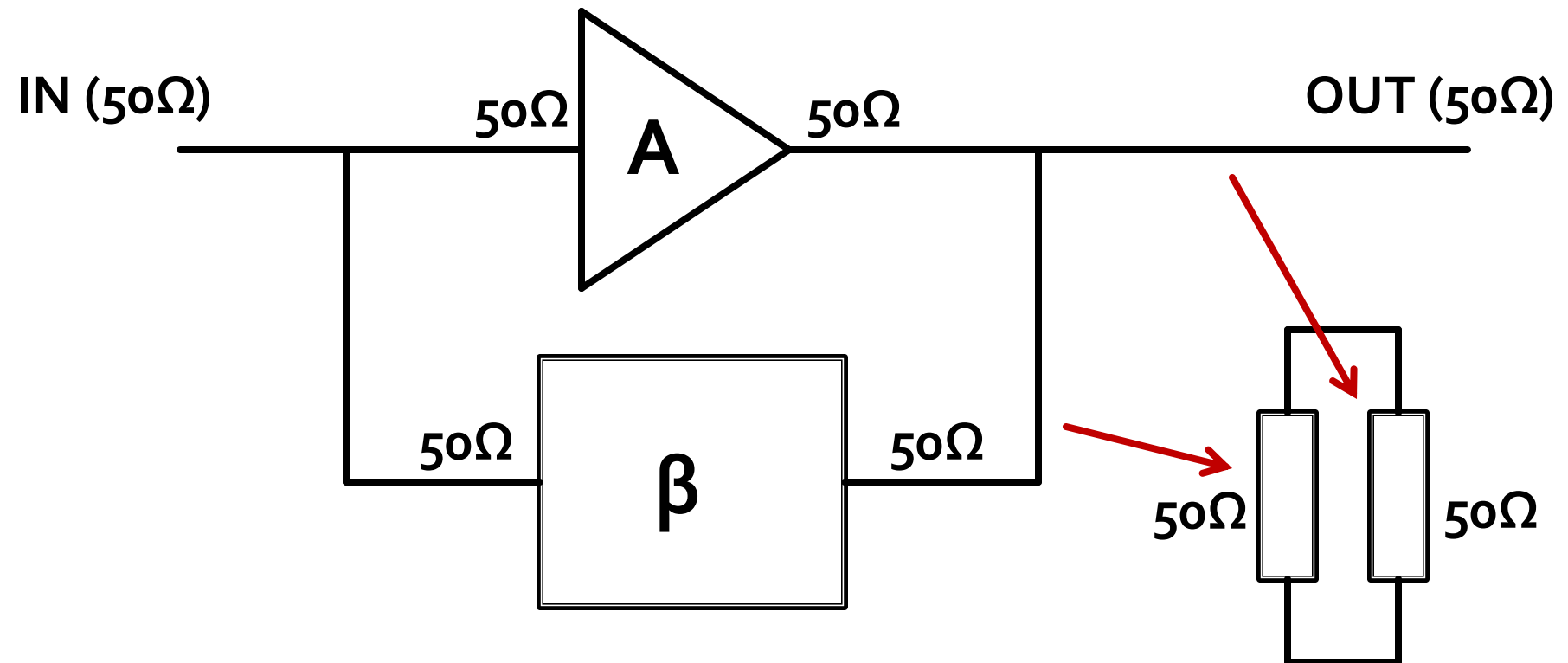

Three-Port Networks

- also known as T-Junctions
- characterized by a 3x3 **S** matrix

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

- the device is **reciprocal** if it does **not** contain:
 - anisotropic materials (usually ferrites)
 - active circuits
- to avoid power loss, we would like to have a network that is:
 - **lossless**, and
 - **matched at all ports**
 - to avoid reflection power “loss”

Three-Port Networks

- reciprocal

$$[S] = [S]^t \quad S_{ij} = S_{ji}, \forall j \neq i$$

$$S_{12} = S_{21}, S_{13} = S_{31}, S_{23} = S_{32}$$

- matched at all ports

$$S_{ii} = 0, \forall i \quad S_{11} = 0, S_{22} = 0, S_{33} = 0$$

- then the S matrix is:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$


Three-Port Networks

- reciprocal, matched at all ports, S matrix:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

- lossless network

- all the power injected in one port will be found exiting the network on all ports

$$[S]^* \cdot [S]^t = [1] \quad \sum_{k=1}^N S_{ki} \cdot S_{kj}^* = \delta_{ij}, \forall i, j$$


The diagram shows a red line branching from the general equation above into two specific equations below. The left branch points to the equation for i=j, and the right branch points to the equation for i≠j.

$$\sum_{k=1}^N S_{ki} \cdot S_{ki}^* = 1 \quad \sum_{k=1}^N S_{ki} \cdot S_{kj}^* = 0, \forall i \neq j$$

Three-Port Networks

- lossless network

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

$$\sum_{k=1}^N S_{ki} \cdot S_{ki}^* = 1$$

$$\sum_{k=1}^N S_{ki} \cdot S_{kj}^* = 0, \forall i \neq j$$

- 6 equations / 3 unknowns

$$|S_{12}|^2 + |S_{13}|^2 = 1 \quad S_{13}^* S_{23} = 0$$

$$|S_{12}|^2 + |S_{23}|^2 = 1 \quad S_{12}^* S_{13} = 0$$

$$|S_{13}|^2 + |S_{23}|^2 = 1 \quad S_{23}^* S_{12} = 0$$

- no solution is possible

Three-Port Networks

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

- 6 equations / 3 unknowns
 - no solution is possible
- A three-port network **cannot** be simultaneously:
 - reciprocal
 - lossless
 - matched at all ports
- If any one of these three conditions is relaxed, then a physically realizable device is possible

Nonreciprocal Three-Port Networks

- usually containing anisotropic materials, ferrites
- **nonreciprocal**, but matched at all ports and lossless $S_{ij} \neq S_{ji}$

- S matrix

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{21} & 0 & S_{23} \\ S_{31} & S_{32} & 0 \end{bmatrix}$$

- 6 equations / 3 unknowns

$$|S_{12}|^2 + |S_{13}|^2 = 1 \quad S_{31}^* S_{32} = 0$$

$$|S_{21}|^2 + |S_{23}|^2 = 1 \quad S_{21}^* S_{23} = 0$$

$$|S_{31}|^2 + |S_{32}|^2 = 1 \quad S_{12}^* S_{13} = 0$$

Nonreciprocal Three-Port Networks


- two possible solutions
- circulators

- clockwise circulation

$$S_{12} = S_{23} = S_{31} = 0$$

$$|S_{21}| = |S_{32}| = |S_{13}| = 1$$
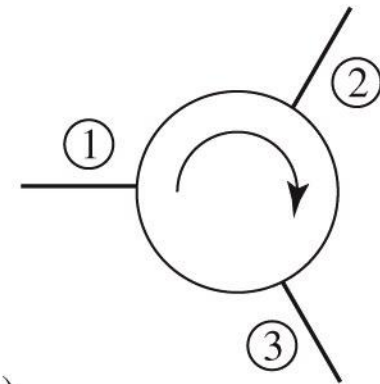
$$[S] = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$




(a)

- counterclockwise circulation

$$S_{21} = S_{32} = S_{13} = 0$$

$$|S_{12}| = |S_{23}| = |S_{31}| = 1$$


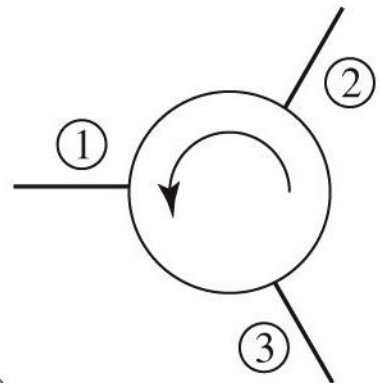
$$[S] = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix}$$



(b)

Nonreciprocal Three-Port Networks

- circulator often found in duplexer

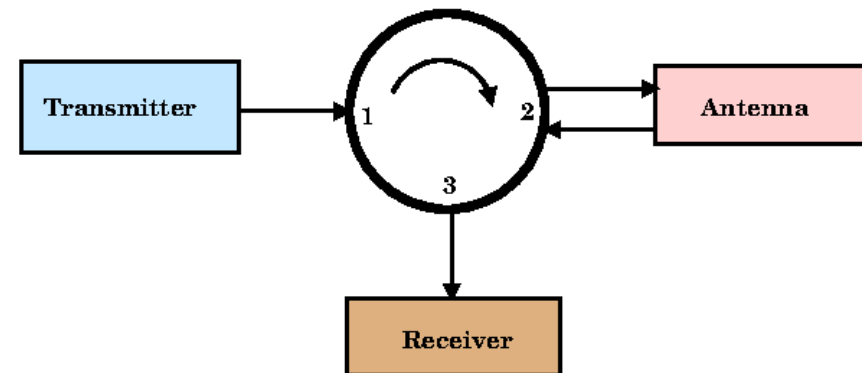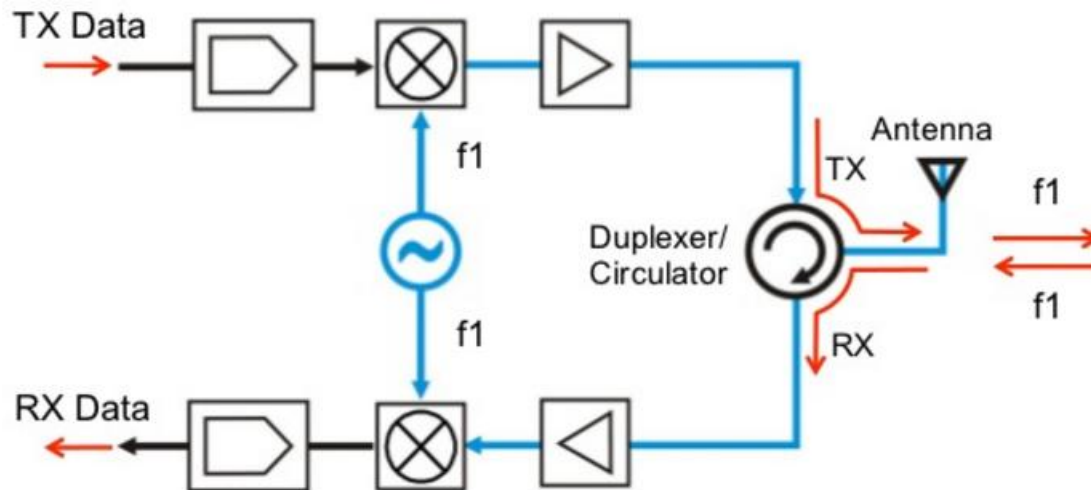

Mismatched Three-Port Networks

- A lossless and reciprocal three-port network can be matched only on two ports, eg. 1 and 2:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & S_{33} \end{bmatrix}$$

$$S_{13}^* S_{23} = 0$$

$$S_{12}^* S_{13} + S_{23}^* S_{33} = 0$$

$$S_{23}^* S_{12} + S_{33}^* S_{13} = 0$$

$$S_{13} = S_{23} = 0$$

$$|S_{13}| = |S_{23}|$$

$$|S_{12}|^2 + |S_{13}|^2 = 1$$

$$|S_{12}|^2 + |S_{23}|^2 = 1$$

$$|S_{13}|^2 + |S_{23}|^2 + |S_{33}|^2 = 1$$

$$|S_{12}| = |S_{33}| = 1$$

Mismatched Three-Port Networks

- A lossless and reciprocal three-port network


$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & S_{33} \end{bmatrix}$$

$$S_{13} = S_{23} = 0 \quad |S_{12}| = |S_{33}| = 1$$

$$S_{12} = e^{j\theta}$$

$$S_{33} = e^{j\phi}$$
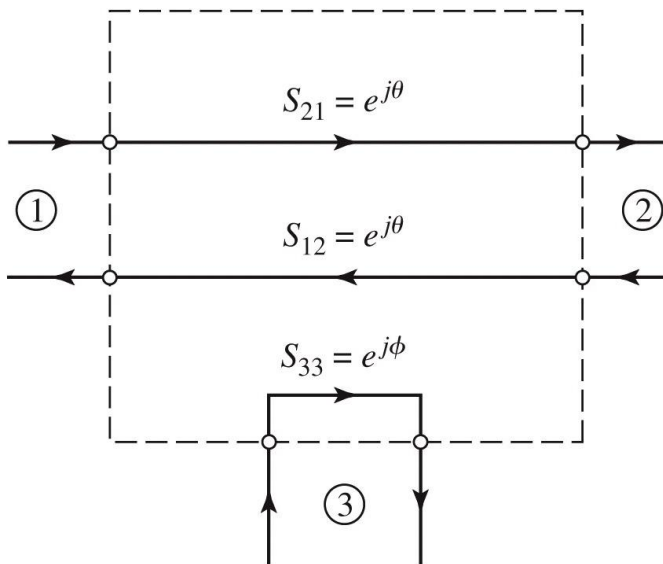
$$[S] = \begin{bmatrix} 0 & e^{j\theta} & 0 \\ e^{j\theta} & 0 & 0 \\ 0 & 0 & e^{j\phi} \end{bmatrix}$$



- A lossless and reciprocal three-port network **degenerates** into two separate components:

- a matched two-port **line**
- a totally **mismatched one-port**:

Four-Port Networks

- characterized by a 4x4 **S** matrix

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix}$$

- the device is **reciprocal** if it does **not** contain:
 - anisotropic materials (usually ferrites)
 - active circuits
- to avoid power loss, we would like to have a network that is:
 - **lossless**, and
 - **matched at all ports**
 - to avoid reflection power “loss”

Four-Port Networks

- reciprocal

$$[S] = [S]^t \quad S_{ij} = S_{ji}, \forall j \neq i$$

$$S_{12} = S_{21}, S_{13} = S_{31}, S_{23} = S_{32}$$

- matched at all ports

$$S_{ii} = 0, \forall i \quad S_{11} = 0, S_{22} = 0, S_{33} = 0, S_{44} = 0$$

- then the S matrix is:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & S_{14} \\ S_{12} & 0 & S_{23} & S_{24} \\ S_{13} & S_{23} & 0 & S_{34} \\ S_{14} & S_{24} & S_{34} & 0 \end{bmatrix}$$


Four-Port Networks

- reciprocal, matched at all ports, S matrix:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & S_{14} \\ S_{12} & 0 & S_{23} & S_{24} \\ S_{13} & S_{23} & 0 & S_{34} \\ S_{14} & S_{24} & S_{34} & 0 \end{bmatrix}$$

- lossless network

- all the power injected in one port will be found exiting the network on all ports

$$[S]^* \cdot [S]^t = [1] \quad \sum_{k=1}^N S_{ki} \cdot S_{kj}^* = \delta_{ij}, \forall i, j$$

$$\sum_{k=1}^N S_{ki} \cdot S_{ki}^* = 1 \quad \sum_{k=1}^N S_{ki} \cdot S_{kj}^* = 0, \forall i \neq j$$

Four-Port Networks

$$S_{13}^* \cdot S_{23} + S_{14}^* \cdot S_{24} = 0 \quad / \cdot S_{24}^*$$

$$S_{14}^* \cdot S_{13} + S_{24}^* \cdot S_{23} = 0 \quad / \cdot S_{13}^*$$

$$S_{14}^* \cdot (|S_{13}|^2 - |S_{24}|^2) = 0$$

$$S_{12}^* \cdot S_{23} + S_{14}^* \cdot S_{34} = 0 \quad / \cdot S_{12}^*$$

$$S_{14}^* \cdot S_{12} + S_{34}^* \cdot S_{23} = 0 \quad / \cdot S_{34}^*$$

$$S_{23} \cdot (|S_{12}|^2 - |S_{34}|^2) = 0$$

- one solution: $S_{14} = S_{23} = 0$
- resulting coupler is **directional**

$$|S_{12}|^2 + |S_{13}|^2 = 1$$

$$|S_{12}|^2 + |S_{24}|^2 = 1$$

$$|S_{13}|^2 + |S_{34}|^2 = 1$$

$$|S_{24}|^2 + |S_{34}|^2 = 1$$

$$|S_{13}| = |S_{24}|$$

$$|S_{12}| = |S_{34}|$$

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & 0 \\ S_{12} & 0 & 0 & S_{24} \\ S_{13} & 0 & 0 & S_{34} \\ 0 & S_{24} & S_{34} & 0 \end{bmatrix}$$

Four-Port Networks

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & 0 \\ S_{12} & 0 & 0 & S_{24} \\ S_{13} & 0 & 0 & S_{34} \\ 0 & S_{24} & S_{34} & 0 \end{bmatrix} \quad \begin{aligned} |S_{12}| &= |S_{34}| = \alpha & |S_{13}| &= |S_{24}| = \beta \\ \beta &\text{ – voltage coupling coefficient} \end{aligned}$$

- We can choose the phase reference

$$S_{12} = S_{34} = \alpha \quad S_{13} = \beta \cdot e^{j\theta} \quad S_{24} = \beta \cdot e^{j\phi}$$

$$S_{12}^* \cdot S_{13} + S_{24}^* \cdot S_{34} = 0 \quad \rightarrow \quad \theta + \phi = \pi \pm 2 \cdot n \cdot \pi$$

$$|S_{12}|^2 + |S_{24}|^2 = 1 \quad \rightarrow \quad \alpha^2 + \beta^2 = 1$$

- The other possible solution for previous equations offer either essentially the same result (with a different phase reference) or the degenerate case (2 separate two port networks side by side)

$$S_{14}^* \cdot (|S_{13}|^2 - |S_{24}|^2) = 0 \quad S_{23} \cdot (|S_{12}|^2 - |S_{34}|^2) = 0$$

Four-Port Networks

- A four-port network simultaneously:
 - matched at all ports
 - reciprocal
 - lossless
- is **always directional**
 - the signal power injected into one port is transmitted **only towards two** of the other three ports

$$[S] = \begin{bmatrix} 0 & \alpha & \beta \cdot e^{j\theta} & 0 \\ \alpha & 0 & 0 & \beta \cdot e^{j\phi} \\ \beta \cdot e^{j\theta} & 0 & 0 & \alpha \\ 0 & \beta \cdot e^{j\phi} & \alpha & 0 \end{bmatrix}$$

Four-Port Networks

- two particular choices commonly occur in practice


- A Symmetric Coupler $\theta = \phi = \pi/2$

$$[S] = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$

- An Antisymmetric Coupler $\theta = 0, \phi = \pi$

$$[S] = \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$

Directional Coupler

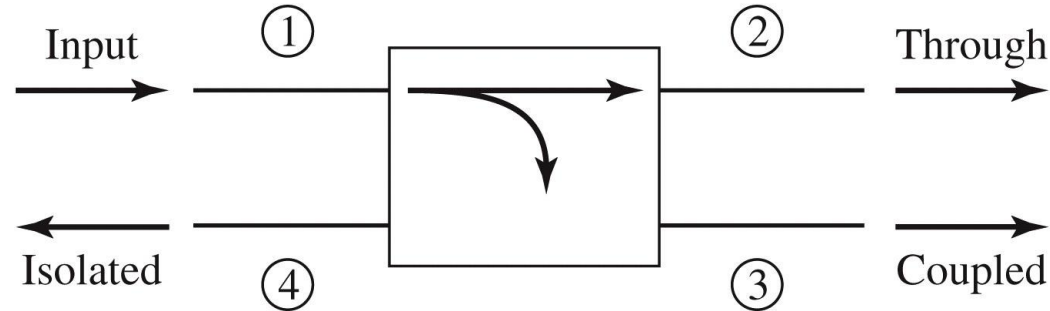

$$|S_{12}|^2 = \alpha^2 = 1 - \beta^2$$

$$|S_{13}|^2 = \beta^2$$

Coupling

$$C = 10 \log \frac{P_1}{P_3} = -20 \cdot \log(\beta) [\text{dB}]$$

Directivity

$$D = 10 \log \frac{P_3}{P_4} = 20 \cdot \log \left(\frac{\beta}{|S_{14}|} \right) [\text{dB}]$$

Isolation

$$I = 10 \log \frac{P_1}{P_4} = -20 \cdot \log |S_{14}| [\text{dB}]$$

$$I = D + C, \quad [\text{dB}]$$

Figure 7.4
© John Wiley & Sons, Inc. All rights reserved.

Power dividers


Three-Port Networks

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

- 6 equations / 3 unknowns
 - no solution is possible
- A three-port network **cannot** be simultaneously:
 - reciprocal
 - **lossless**
 - matched at all ports
- If any one of these three conditions is relaxed, then a physically realizable device is possible


Power division of the T-junction

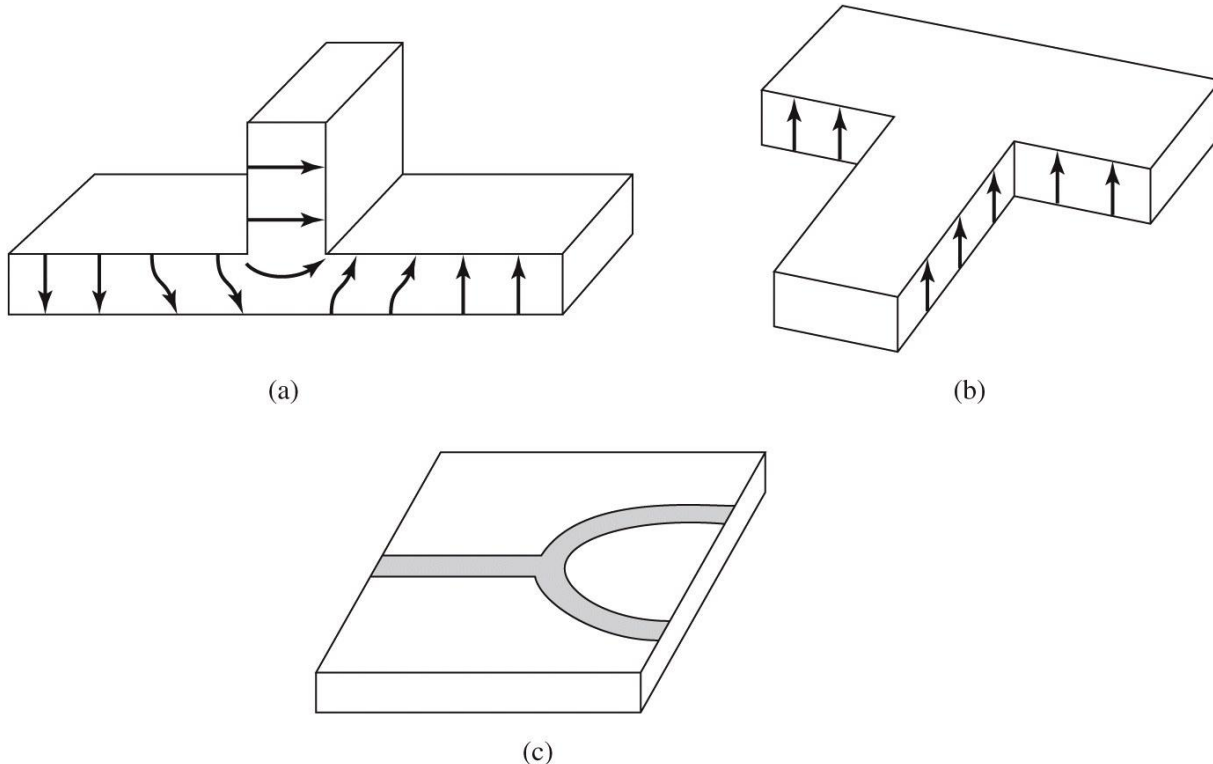- consists in splitting an input line into two separate output lines
- available in various technologies for the lines




Power division of the T-junction

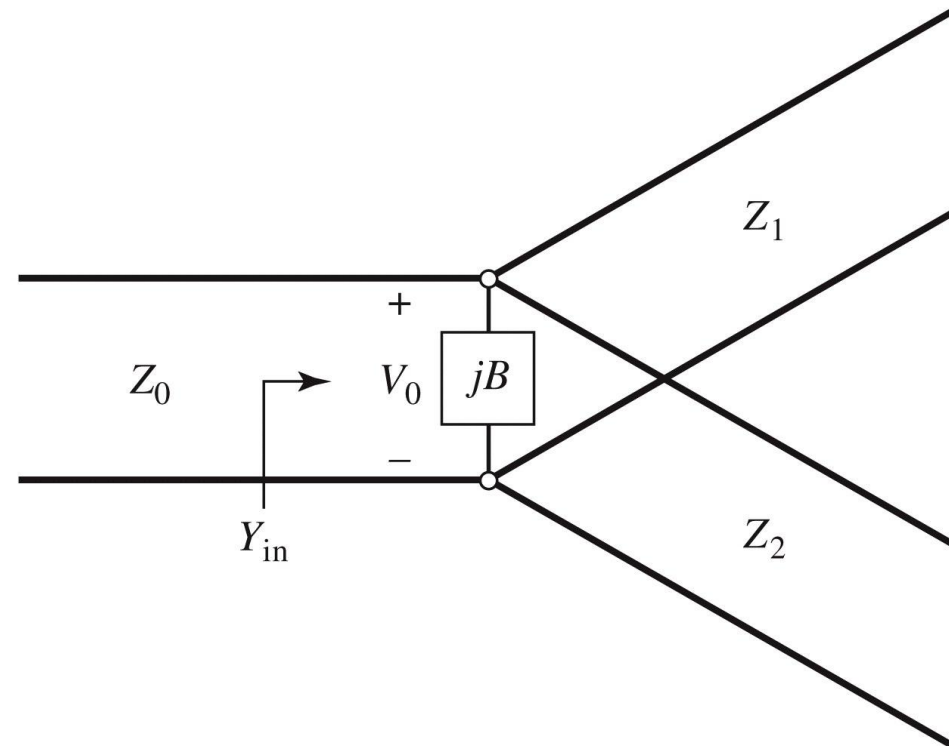- if the lines are lossless, the network is reciprocal, so it cannot be matched at all ports simultaneously



- there may be fringing fields and higher order modes associated with the discontinuity at such a junction
- the stored energy can be accounted for by a lumped susceptance: **B**
- Designing the power divider targets matching to the input line Z_0
 - outputs (unmatched, Z_1 and Z_2) can be, if needed, matched to Z_0 ($\lambda/4$, binomial, Chebyshev)

Power division of the T-junction

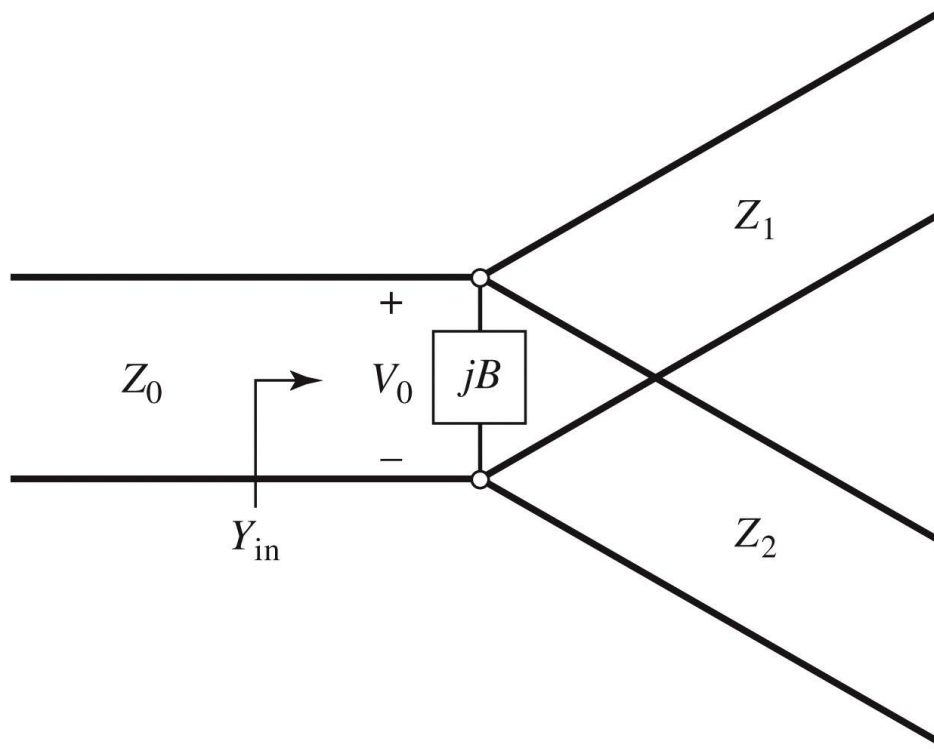

$$Y_{in} = j \cdot B + \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$$

- If the transmission lines are assumed to be lossless, then the characteristic impedances are real
- the matching condition can be met only if $B \cong 0$ thus the matching condition is:

$$\frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$$

Figure 7.6
© John Wiley & Sons, Inc. All rights reserved.

In practice, if B is not negligible, some type of discontinuity compensation or a reactive tuning element can usually be used to cancel this susceptance, at least over a narrow frequency range.

Power division of the T-junction

- if V_0 is the voltage at the junction, we can compute how the input power is divided between the two output lines

$$P_{in} = \frac{1}{2} \cdot \frac{V_0^2}{Z_0} \quad P_1 = \frac{1}{2} \cdot \frac{V_0^2}{Z_1}$$

$$\text{then:} \quad P_2 = \frac{1}{2} \cdot \frac{V_0^2}{Z_2}$$


$$P_{in} = P_1 + P_2 \quad (\text{lossless/input matching})$$

$$\frac{P_1}{P_2} = \frac{Z_2}{Z_1} = \alpha \quad (\text{power division between the two output lines})$$

$$P_1 = P_{in} \cdot \frac{Z_2}{Z_1 + Z_2} \quad P_2 = P_{in} \cdot \frac{Z_1}{Z_1 + Z_2}$$


$$P_1 = P_{in} \cdot \frac{\alpha}{1 + \alpha} \quad P_2 = P_{in} \cdot \frac{1}{1 + \alpha}$$
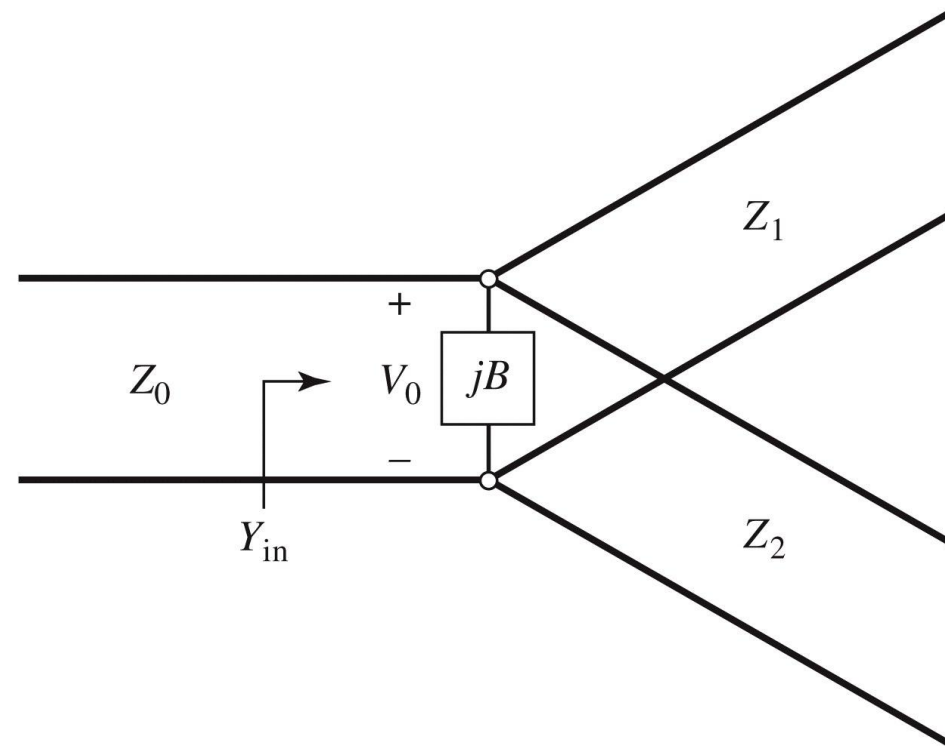
$$Z_1 = Z_0 \cdot \left(1 + \frac{1}{\alpha}\right) \quad Z_2 = Z_0 \cdot (1 + \alpha)$$



Power division of the T-junction

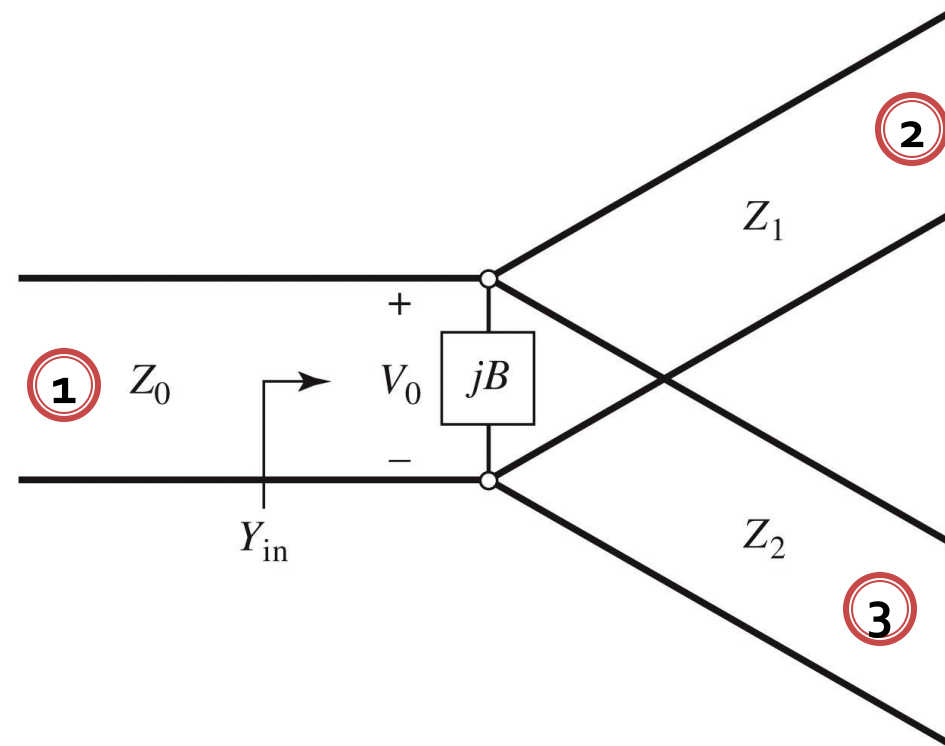- S matrix
 - lossless (unitary matrix)
 - reciprocal (symmetrical matrix)
 - input port is matched $S_{11} = 0$



$$P_2 = P_1 \cdot \frac{\alpha}{1 + \alpha} \quad S_{21} = S_{12} = \sqrt{\frac{\alpha}{1 + \alpha}}$$

$$P_3 = P_1 \cdot \frac{1}{1 + \alpha} \quad S_{31} = S_{13} = \sqrt{\frac{1}{1 + \alpha}}$$


the reflection coefficients seen looking into the output ports

$$S_{22} = \Gamma_1 = \frac{Z_0 \parallel Z_2 - Z_1}{Z_0 \parallel Z_2 + Z_1} = -\frac{1}{1 + \alpha}$$

$$S_{33} = \Gamma_2 = \frac{Z_0 \parallel Z_1 - Z_2}{Z_0 \parallel Z_1 + Z_2} = -\frac{\alpha}{1 + \alpha}$$

Power division of the T-junction
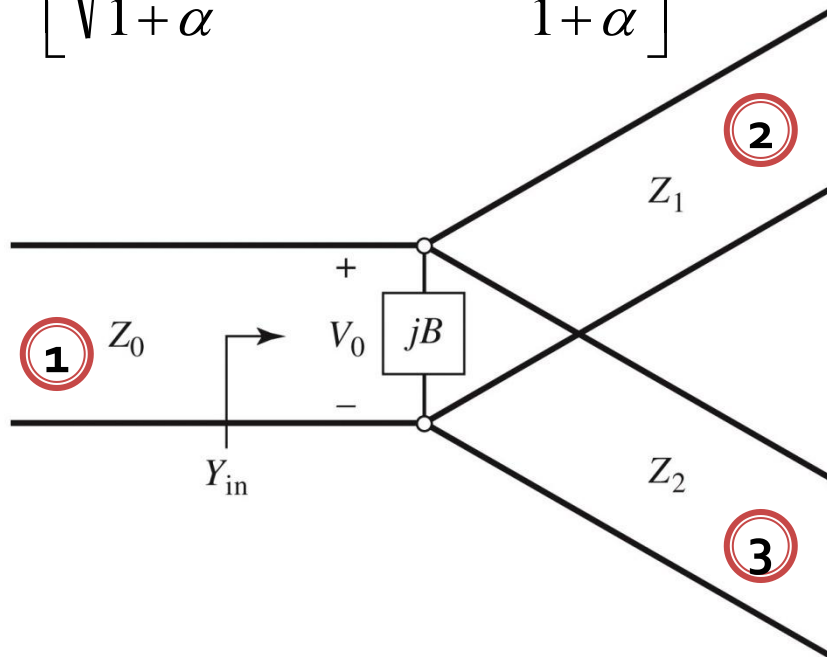
$$[S] = \begin{bmatrix} 0 & \sqrt{\frac{\alpha}{1+\alpha}} & \sqrt{\frac{1}{1+\alpha}} \\ \sqrt{\frac{\alpha}{1+\alpha}} & -\frac{1}{1+\alpha} & x \\ \sqrt{\frac{1}{1+\alpha}} & x & -\frac{\alpha}{1+\alpha} \end{bmatrix}$$



Unitary matrix, columns 1 and 2

$$0 - \frac{1}{1+\alpha} \cdot \sqrt{\frac{\alpha}{1+\alpha}} + x \cdot \sqrt{\frac{1}{1+\alpha}} = 0$$

$$S_{23} = S_{32} = \frac{\sqrt{\alpha}}{1+\alpha}$$

$$[S] = \begin{bmatrix} 0 & \sqrt{\frac{\alpha}{1+\alpha}} & \sqrt{\frac{1}{1+\alpha}} \\ \sqrt{\frac{\alpha}{1+\alpha}} & -\frac{1}{1+\alpha} & \frac{\sqrt{\alpha}}{1+\alpha} \\ \sqrt{\frac{1}{1+\alpha}} & \frac{\sqrt{\alpha}}{1+\alpha} & -\frac{\alpha}{1+\alpha} \end{bmatrix}$$


Power division of the T-junction

- 3dB divider
 - equal splitting of the power between the two outputs
 - $Z_1 = Z_2 = 2 \cdot Z_0$, $\alpha = 1$

$$[S] = \begin{bmatrix} 0 & \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & -\frac{1}{2} & \frac{1}{2} \\ \frac{1}{\sqrt{2}} & \frac{1}{2} & -\frac{1}{2} \end{bmatrix}$$

If we add $\lambda/4$ transformers to match outputs to Z_0 S matrix:
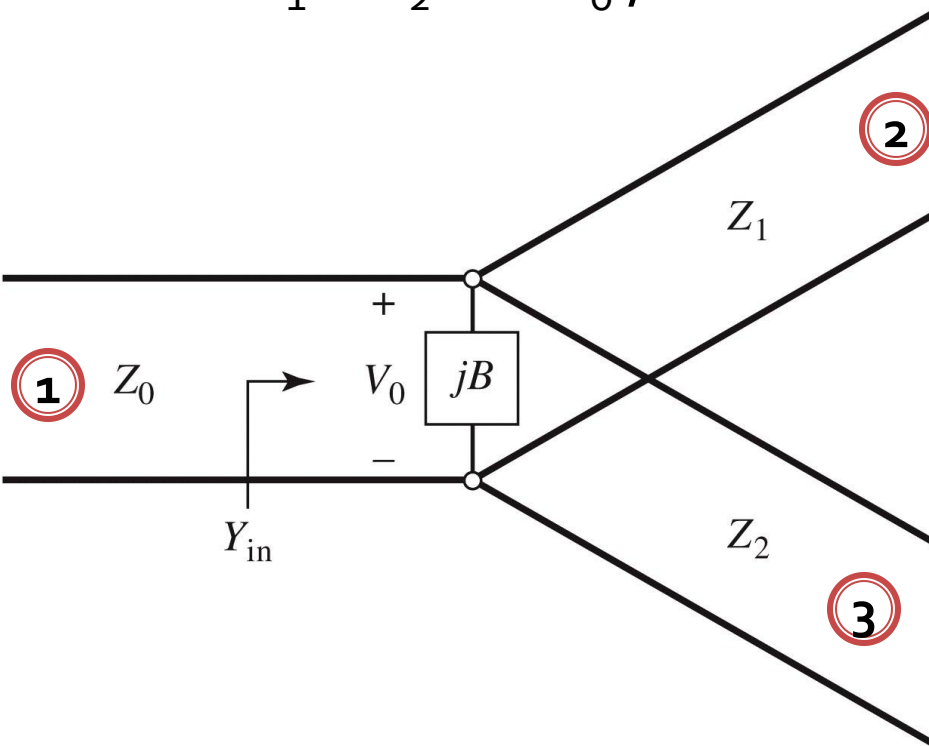
$$[S] = \begin{bmatrix} 0 & -\frac{j}{\sqrt{2}} & -\frac{j}{\sqrt{2}} \\ -\frac{j}{\sqrt{2}} & \frac{1}{2} & \frac{1}{2} \\ -\frac{j}{\sqrt{2}} & -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$



Example

- Design a lossless T-junction divider with a 30Ω source impedance to give a 3:1 power split. Design quarter-wave matching transformers to convert the impedances of the output lines to 30Ω . (**Pozar** problem)

$$P_{in} = \frac{1}{2} \cdot \frac{V_0^2}{Z_0} \quad \begin{cases} P_1 + P_2 = P_{in} \\ P_1 : P_2 = 3:1 \end{cases} \Rightarrow \begin{cases} P_1 = \frac{1}{4} \cdot P_{in} \\ P_2 = \frac{3}{4} \cdot P_{in} \end{cases}$$

$$P_1 = \frac{1}{2} \cdot \frac{V_0^2}{Z_1} = \frac{1}{4} \cdot P_{in} \quad Z_1 = 4 \cdot Z_0 = 120 \Omega$$

$$P_2 = \frac{1}{2} \cdot \frac{V_0^2}{Z_2} = \frac{3}{4} \cdot P_{in} \quad Z_2 = 4 \cdot Z_0 / 3 = 40 \Omega$$

Input match check


$$Z_{in} = 40 \Omega \parallel 120 \Omega = 30 \Omega$$

quarter-wave transformers $Z_c^i = \sqrt{Z_i \cdot Z_L}$

$$Z_c^1 = \sqrt{Z_1 \cdot Z_L} = \sqrt{120\Omega \cdot 30\Omega} = 60\Omega \quad Z_c^2 = \sqrt{Z_2 \cdot Z_L} = \sqrt{40\Omega \cdot 30\Omega} = 34.64\Omega$$

Resistive Divider

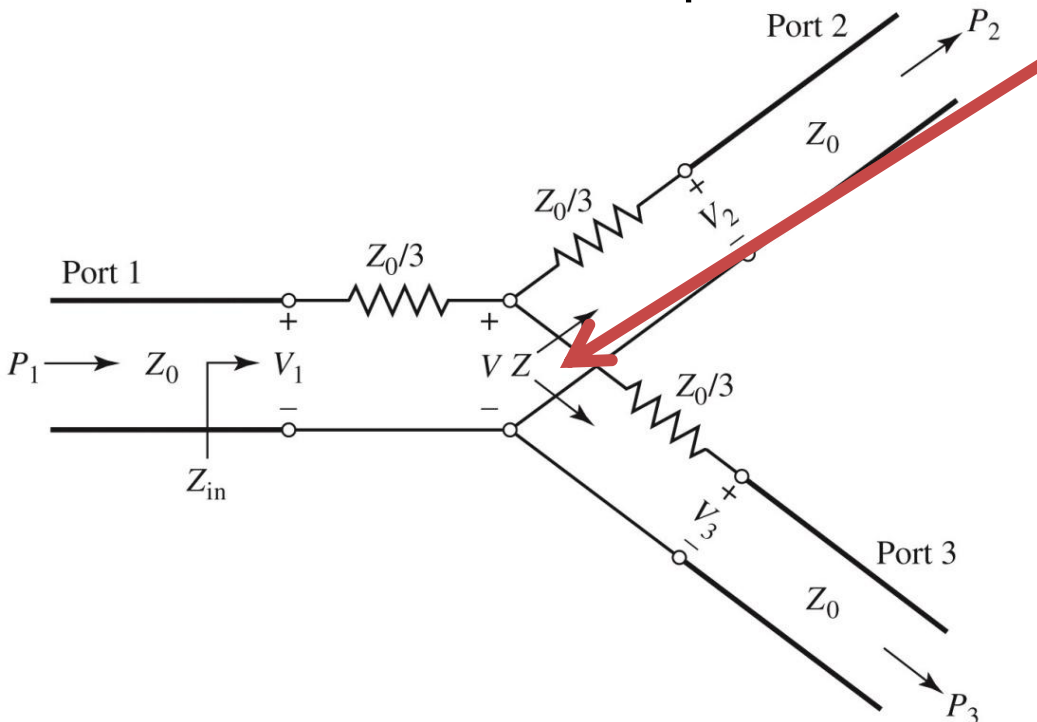- If a three-port divider contains lossy components, it can be made to be :
 - reciprocal
 - matched at all ports



The impedance Z , seen looking into the $Z_0/3$ resistor followed by a terminated output line:

$$Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$$

The input line will be terminated with a $Z_0/3$ resistor in series with two such lines Z in parallel


$$Z_{in} = \frac{Z_0}{3} + \frac{1}{2} \cdot \frac{4Z_0}{3} = Z_0$$

so it will be matched: $S_{11} = 0$

from symmetry: $S_{11} = S_{22} = S_{33} = 0$

Resistive Divider

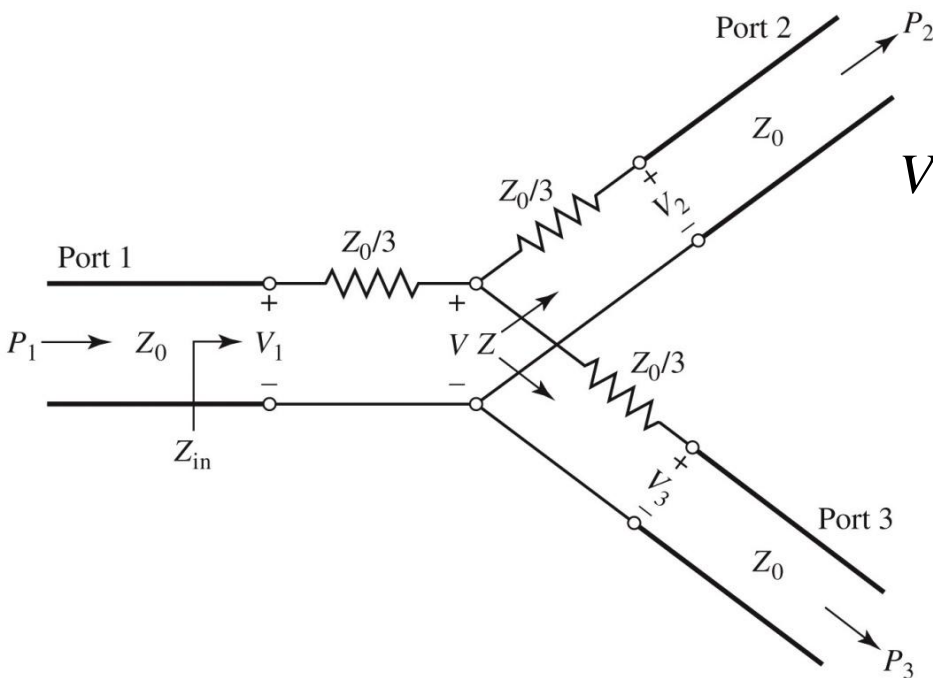- If a three-port divider contains lossy components, it can be made to be :
 - reciprocal
 - matched at all ports $S_{11} = S_{22} = S_{33} = 0$



If the voltage at port 1 is V_1 , then by voltage division the voltage V at the junction is:

$$V = V_1 \cdot \frac{Z/2}{Z/2 + Z_0/3} = V_1 \cdot \frac{2Z_0/3}{2Z_0/3 + Z_0/3} = \frac{2}{3} \cdot V_1$$

The output voltages are, again by voltage division :


$$V_2 = V_3 = V \cdot \frac{Z_0}{Z_0 + Z_0/3} = \frac{3}{4} \cdot V = \frac{1}{2} \cdot V_1$$

$$S_{21} = S_{31} = \frac{1}{2}$$

from symmetry: $S_{21} = S_{31} = S_{23} = \frac{1}{2}$

Resistive Divider

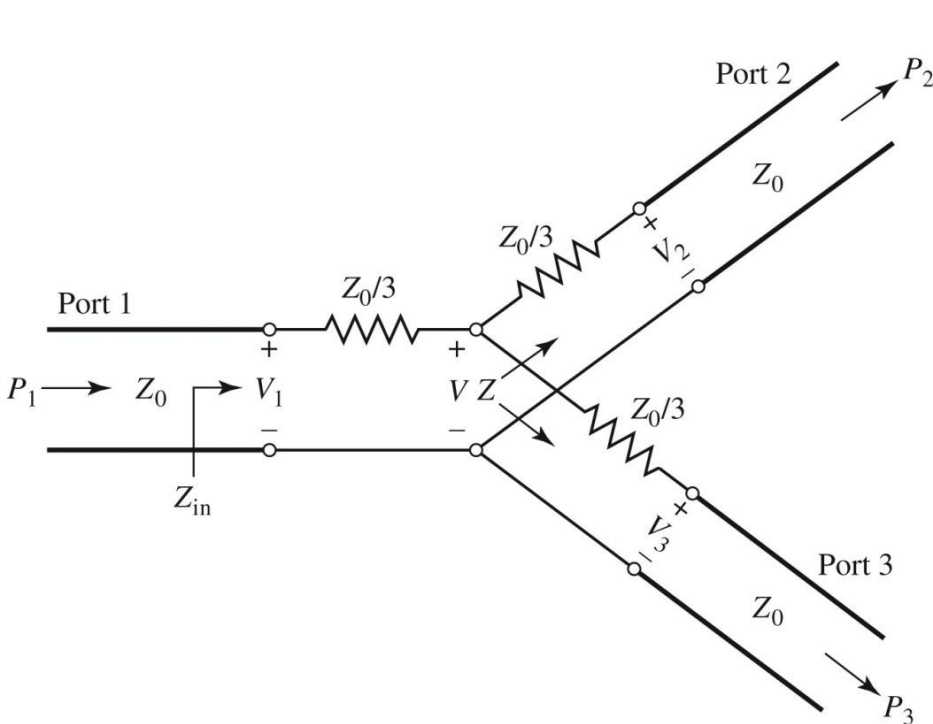- If a three-port divider contains lossy components, it can be made to be :
 - reciprocal (S matrix is symmetrical) $S_{21} = S_{31} = S_{23} = \frac{1}{2}$
 - matched at all ports $S_{11} = S_{22} = S_{33} = 0$



S matrix: $[S] = \frac{1}{2} \cdot \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$


Powers: $P_{in} = \frac{1}{2} \cdot \frac{V_1^2}{Z_0}$

$$P_2 = P_3 = \frac{1}{2} \cdot \frac{(1/2 V_1)^2}{Z_0} = \frac{1}{8} \cdot \frac{V_1^2}{Z_0} = \frac{1}{4} \cdot P_{in}$$

Half of the supplied power is dissipated in the 3 resistors. The output powers are 6 dB below the input power level


The Wilkinson power divider

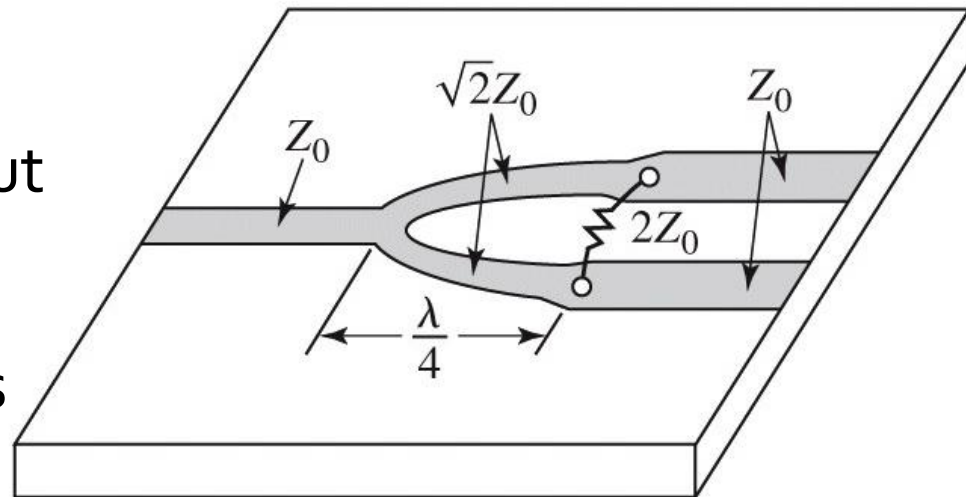- Previous power dividers suffer from a major drawback, there is not isolation between the two output ports $S_{23} = S_{32} \neq 0$
 - this requirement is important in some applications
- The Wilkinson power divider solves this problem
 - it also has the useful property of appearing **lossless** when the output ports are matched
 - only reflected power from the output ports is dissipated




The Wilkinson power divider

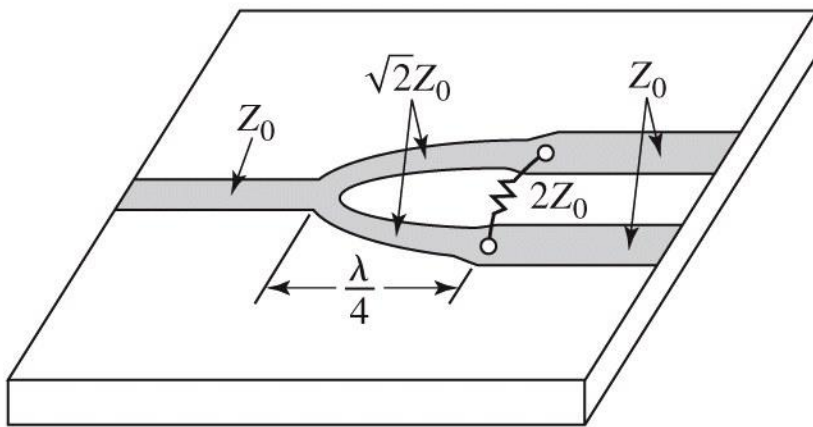- one input line
- two $\lambda/4$ transformers
- one resistor between the output lines



(a)

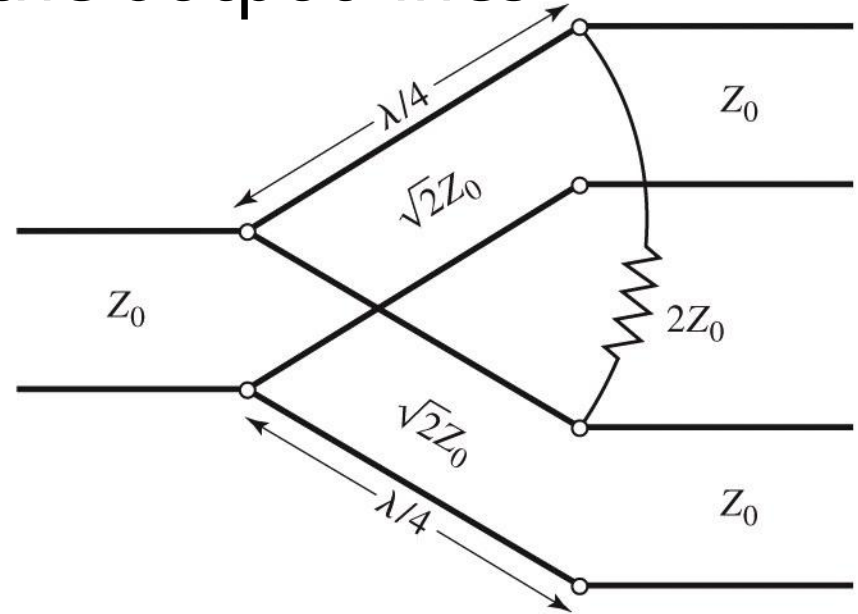

(b)

Even/Odd Mode Analysis

- In linear circuits we can use the superposition principle
- advantages
 - reduction of the circuit complexity
 - decrease of the number of ports (**main** advantage)

$$\text{Response (ODD + EVEN)} = \text{Response (ODD)} + \text{Response (EVEN)}$$



We can benefit from existing symmetries !!

The Wilkinson power divider

- the circuit in normalized and symmetric form


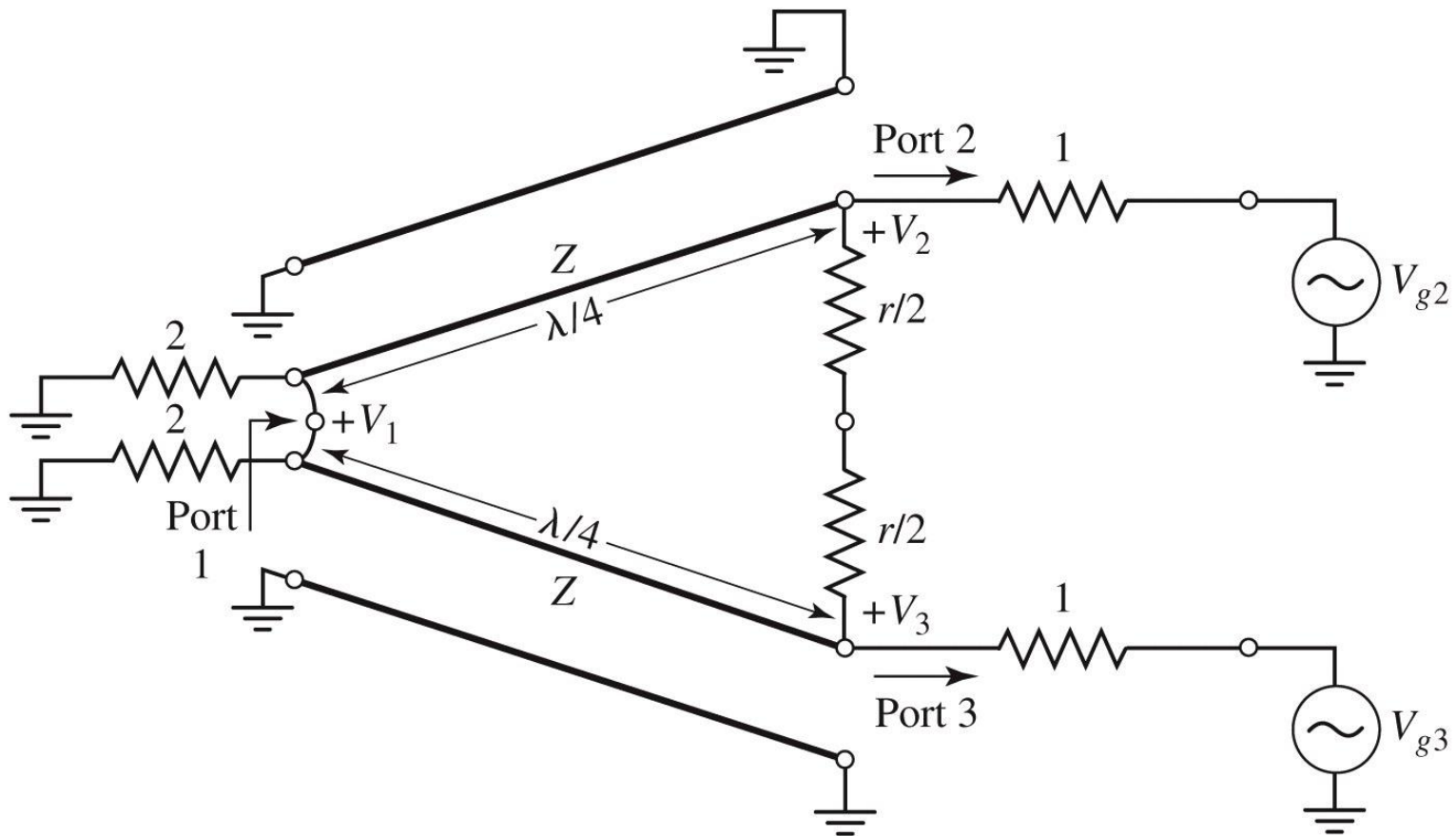
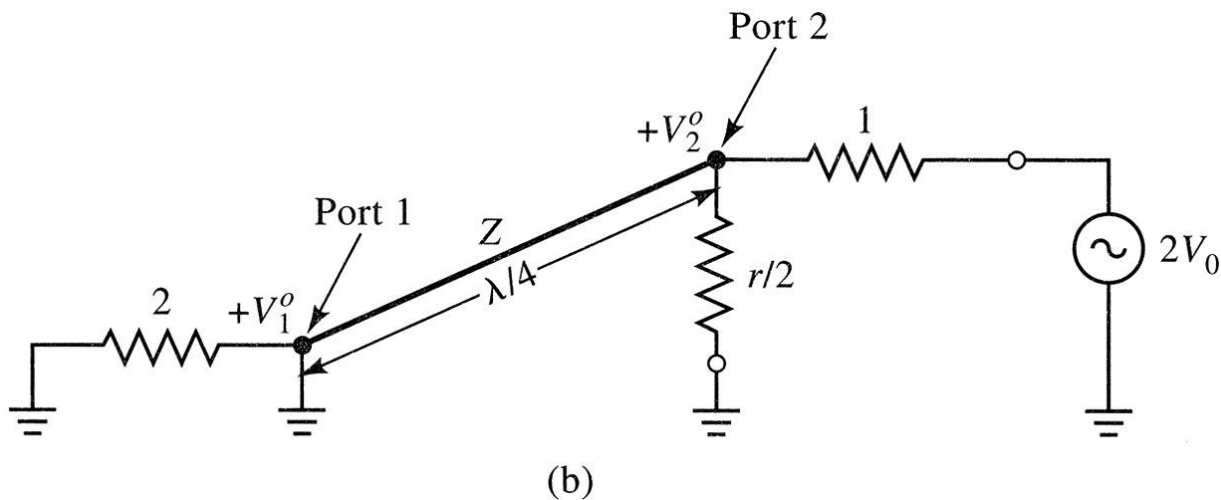


Figure 7.9


The Wilkinson power divider

- Even/Odd Mode Analysis

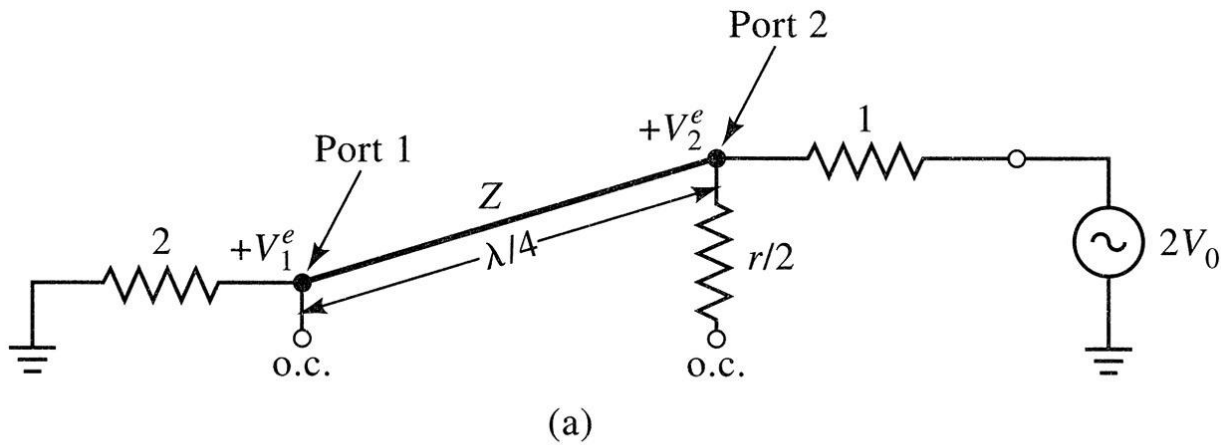

The Wilkinson power divider

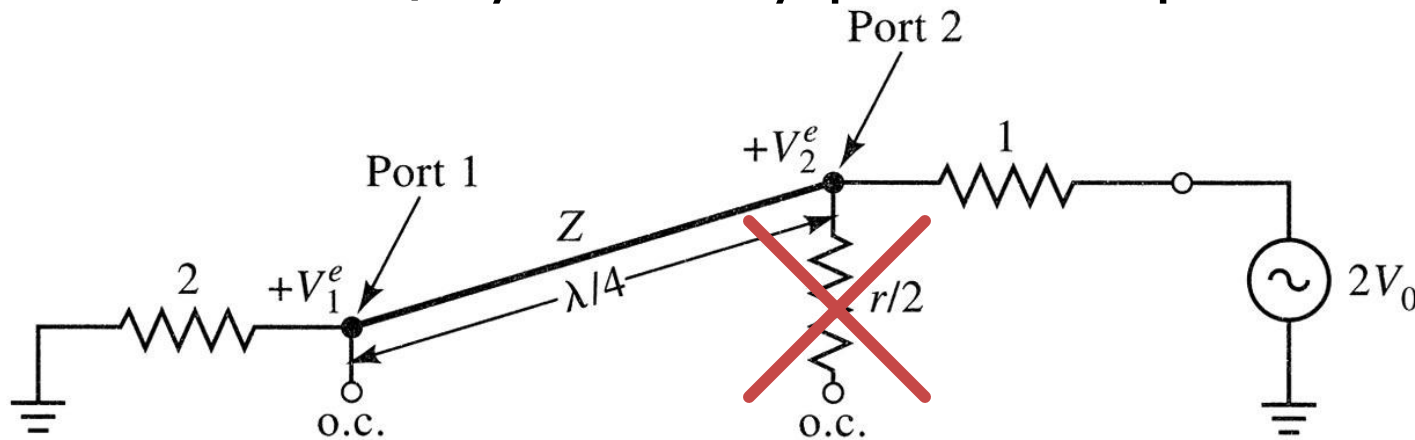- even mode, symmetry plane is open circuit



looking into port 2, $\lambda/4$ transformer with 2 load $Z_{in2}^e = \frac{Z^2}{2}$ if $Z = \sqrt{2}$ port 2 is matched $Z_{in2}^e = 1$

$$V(x) = V^+ \cdot (e^{-j\beta \cdot x} + \Gamma \cdot e^{j\beta \cdot x}) \quad \begin{array}{l} x=0 \text{ at port 1} \\ x=-\lambda/4 \text{ at port 2} \end{array}$$

$$V_2^e = V(-\lambda/4) = jV^+ \cdot (1 - \Gamma) = V_0 \quad V_1^e = V(0) = V^+ \cdot (1 + \Gamma) = jV_0 \cdot \frac{\Gamma + 1}{\Gamma - 1}$$


$Z_{in2}^e = 1$

Γ : reflection coefficient seen at port 1 looking toward the resistor of normalized value 2 from the transformer $Z = \sqrt{2}$

$$\Gamma = \frac{2 - \sqrt{2}}{2 + \sqrt{2}} \quad V_1^e = -jV_0\sqrt{2}$$

The Wilkinson power divider

- odd mode, symmetry plane is grounded

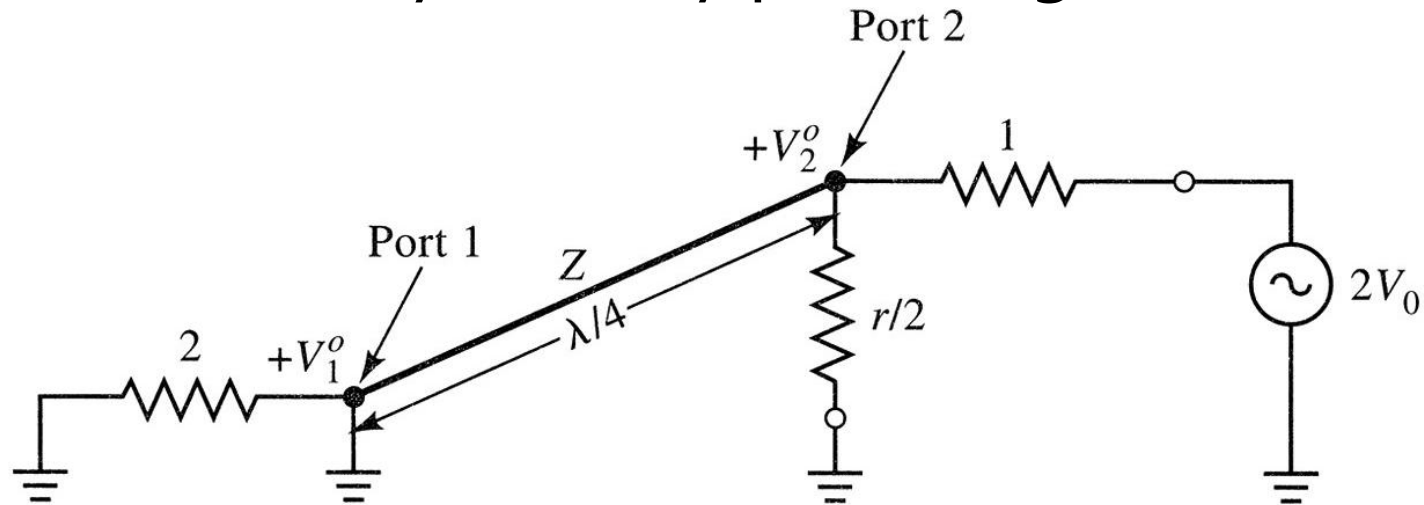


looking from port 2 the $\lambda/4$ line is short-circuited, impedance seen from port 2 is ∞ $Z_{in2}^o = r/2$ if $r = 2$ port 2 is matched

$$Z_{in2}^o = 1 \rightarrow V_2^o = V_0$$

$V_1^o = 0$ in the odd mode all the power is dissipated in the $r/2$ resistor


The Wilkinson power divider

- input impedance in port 1

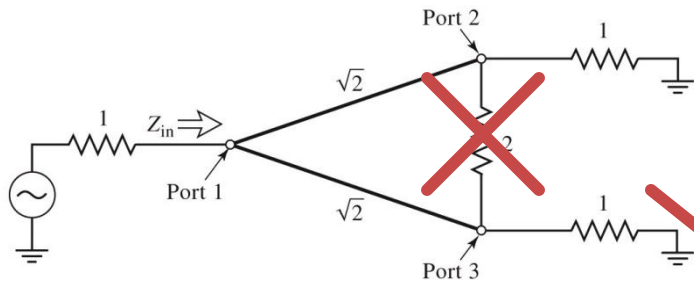

two $\lambda/4$ transformers with load 1 in parallel
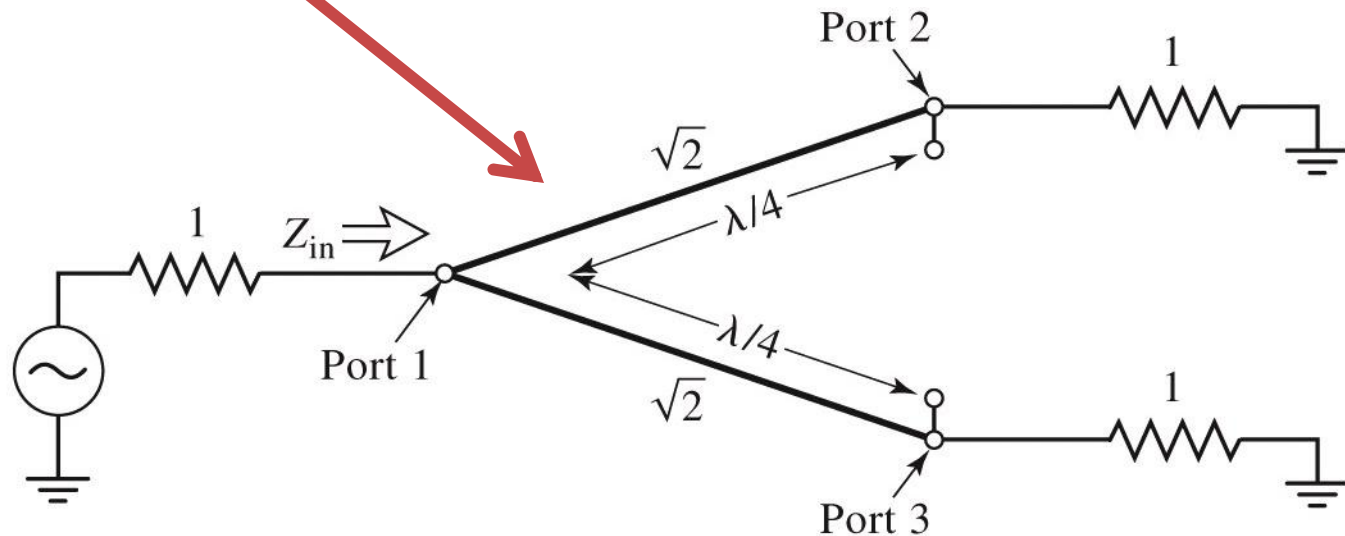
$$Z_{in1} = \frac{1}{2} (\sqrt{2})^2 = 1$$



The Wilkinson power divider

- S parameters

$$Z_{in1} = \frac{1}{2}(\sqrt{2})^2 = 1 \quad S_{11} = 0$$

$$Z_{in2}^e = 1 \quad Z_{in2}^o = 1 \quad \text{and} \quad Z_{in3}^e = 1 \quad Z_{in3}^o = 1 \quad S_{22} = S_{33} = 0$$

$$S_{12} = S_{21} = \frac{V_1^e + V_1^o}{V_2^e + V_2^o} = -\frac{j}{\sqrt{2}}$$

$$\text{and} \quad S_{13} = S_{31} = -\frac{j}{\sqrt{2}}$$

$$S_{23} = S_{32} = 0 \quad \text{due to short or open at bisection, both eliminate transfer between the ports + reciprocal circuit}$$

The Wilkinson power divider

- at design frequency (length of the transformer equal to $\lambda_0/4$) we have **isolation** between the two output ports

$$[S] = \begin{bmatrix} 0 & -\frac{j}{\sqrt{2}} & -\frac{j}{\sqrt{2}} \\ -\frac{j}{\sqrt{2}} & 0 & 0 \\ -\frac{j}{\sqrt{2}} & 0 & 0 \end{bmatrix}$$


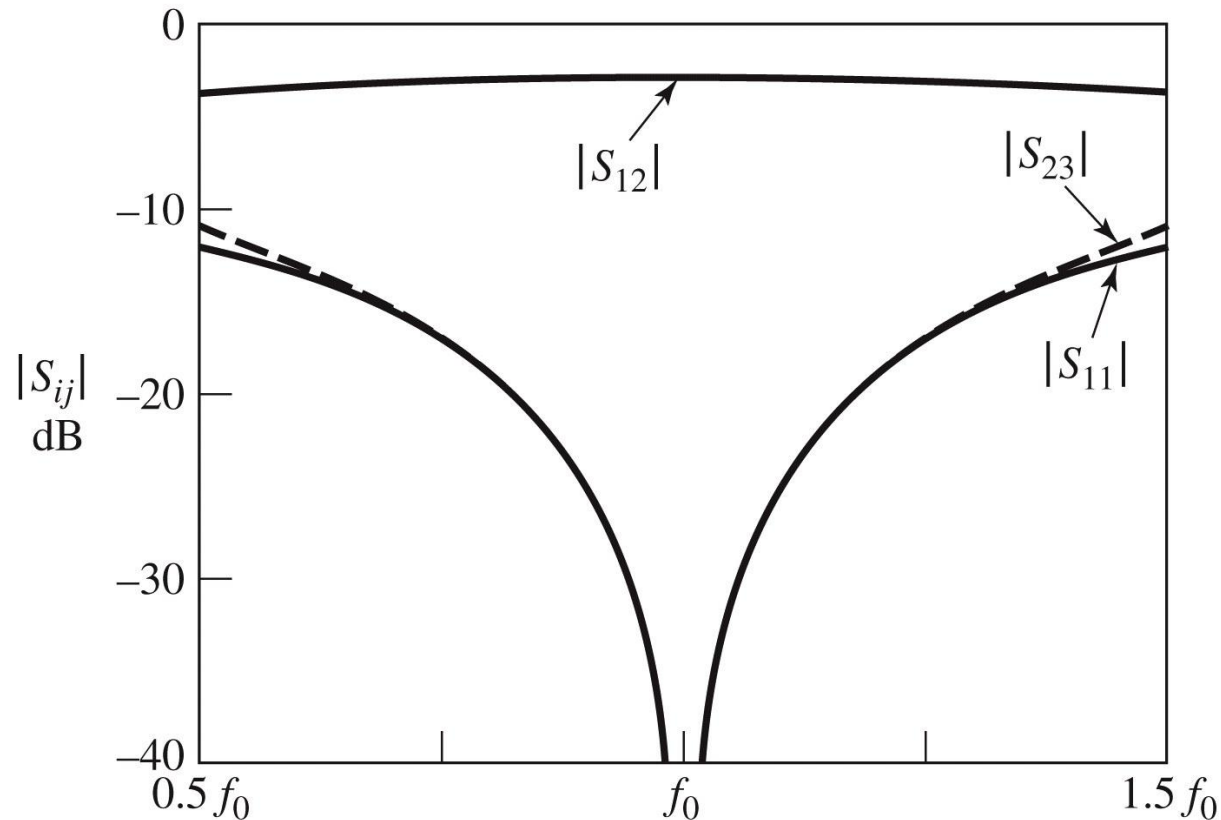


Figure 7.12
© John Wiley & Sons, Inc. All rights reserved.


The Wilkinson power divider

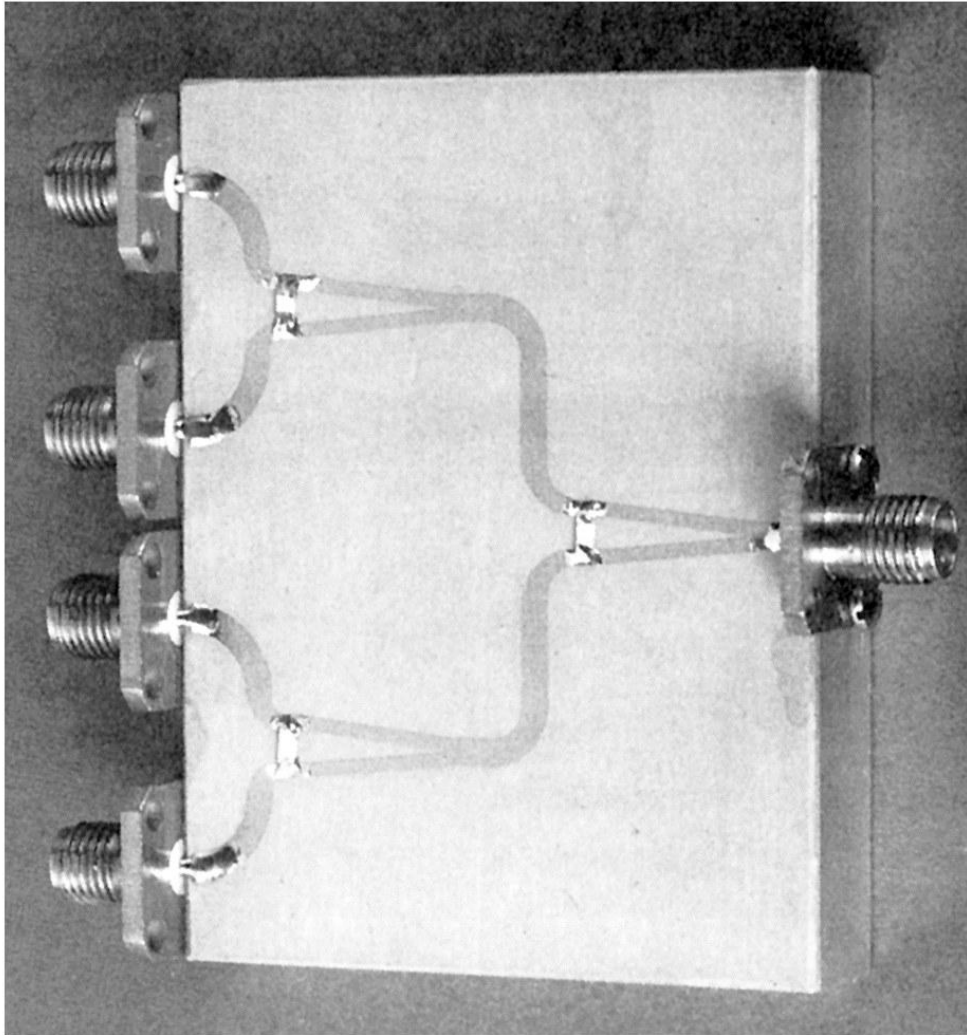

- 3 X Wilkinson = 4-way power divider

Figure 7.15
Courtesy of M. D. Abouzahra, MIT Lincoln Laboratory, Lexington, Mass.

The Wilkinson power divider

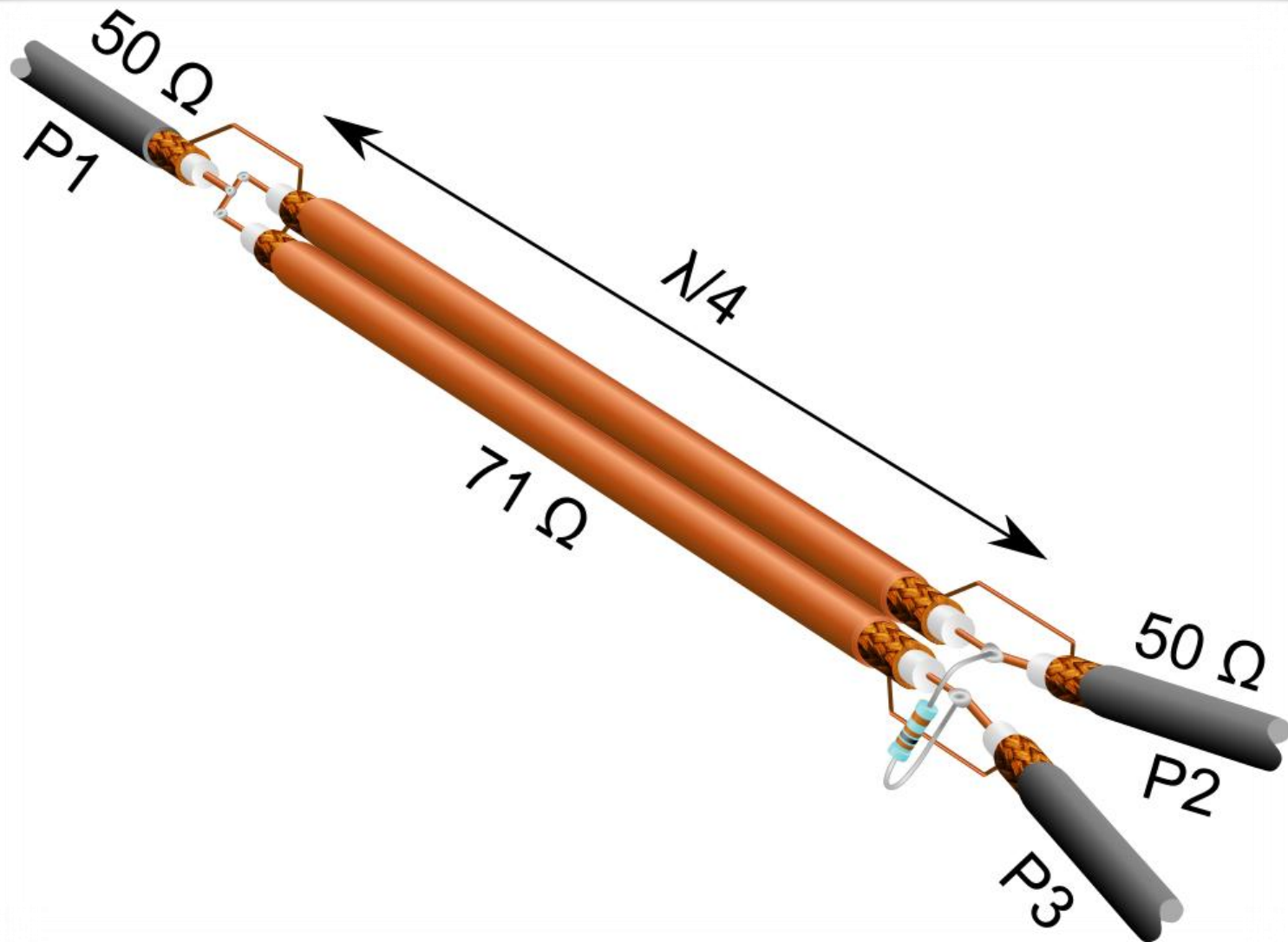


Directional couplers

Four-Port Networks

- A four-port network simultaneously:
 - matched at all ports
 - reciprocal
 - lossless
- is **always directional**
 - the signal power injected into one port is transmitted **only towards two** of the other three ports

$$[S] = \begin{bmatrix} 0 & \alpha & \beta \cdot e^{j\theta} & 0 \\ \alpha & 0 & 0 & \beta \cdot e^{j\phi} \\ \beta \cdot e^{j\theta} & 0 & 0 & \alpha \\ 0 & \beta \cdot e^{j\phi} & \alpha & 0 \end{bmatrix}$$

Directional Coupler

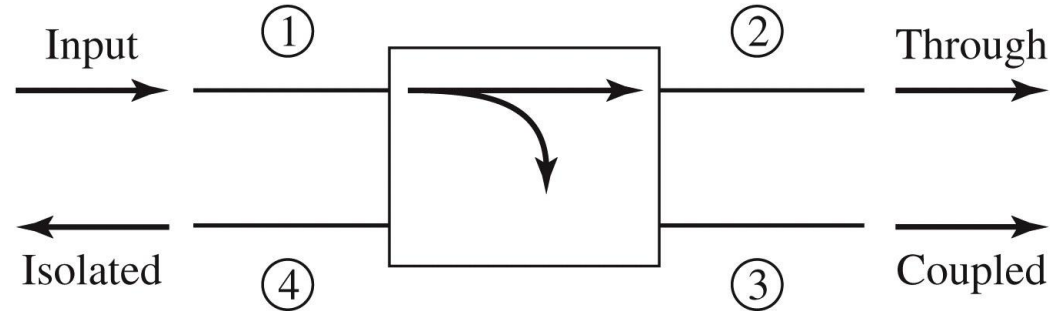

$$|S_{12}|^2 = \alpha^2 = 1 - \beta^2$$

$$|S_{13}|^2 = \beta^2$$

Coupling

$$C = 10 \log \frac{P_1}{P_3} = -20 \cdot \log(\beta) [\text{dB}]$$

Directivity

$$D = 10 \log \frac{P_3}{P_4} = 20 \cdot \log \left(\frac{\beta}{|S_{14}|} \right) [\text{dB}]$$

Isolation

$$I = 10 \log \frac{P_1}{P_4} = -20 \cdot \log |S_{14}| [\text{dB}]$$

$$I = D + C, [dB]$$

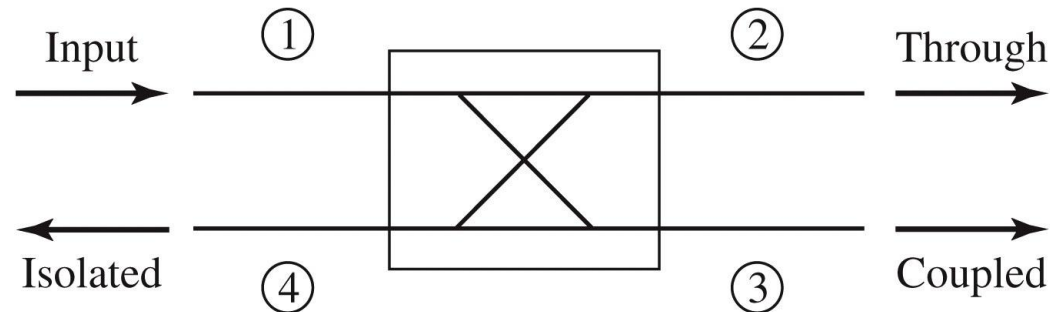


Figure 7.4
© John Wiley & Sons, Inc. All rights reserved.

Four-Port Networks

- two particular choices commonly occur in practice

- A Symmetric Coupler $\theta = \phi = \pi/2$

$$[S] = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$

- An Antisymmetric Coupler $\theta = 0, \phi = \pi$

$$[S] = \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$

Hybrid Couplers

Hybrid Couplers are directional couplers with 3 dB coupling factor

$$\alpha = \beta = 1/\sqrt{2}$$

The quadrature (90°) hybrid

$$(\theta = \phi = \pi/2)$$

$$[S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & j & 0 \\ 1 & 0 & 0 & j \\ j & 0 & 0 & 1 \\ 0 & j & 1 & 0 \end{bmatrix}$$

The 180° ring hybrid (rat-race)

$$(\theta = 0, \phi = \pi)$$

$$[S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$

The quadrature (90°) hybrid


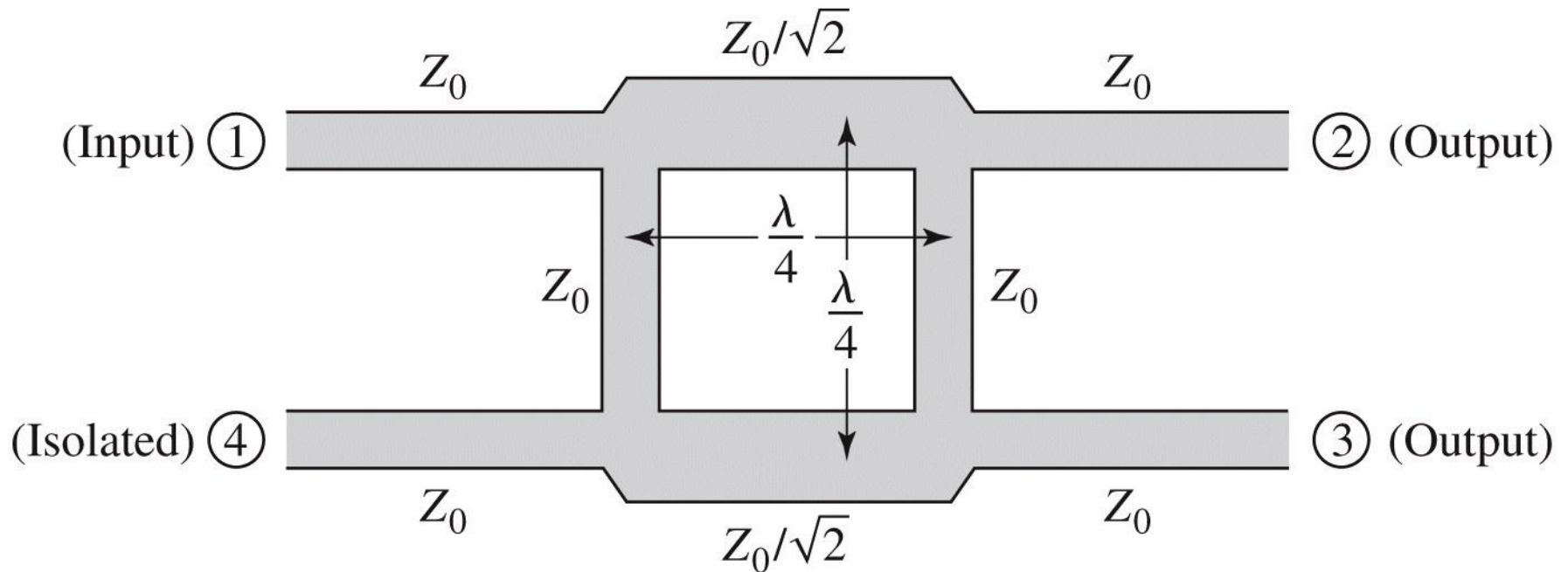



Figure 7.21
© John Wiley & Sons, Inc. All rights reserved.

$$[S] = \frac{-1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$$


Even/Odd Mode Analysis

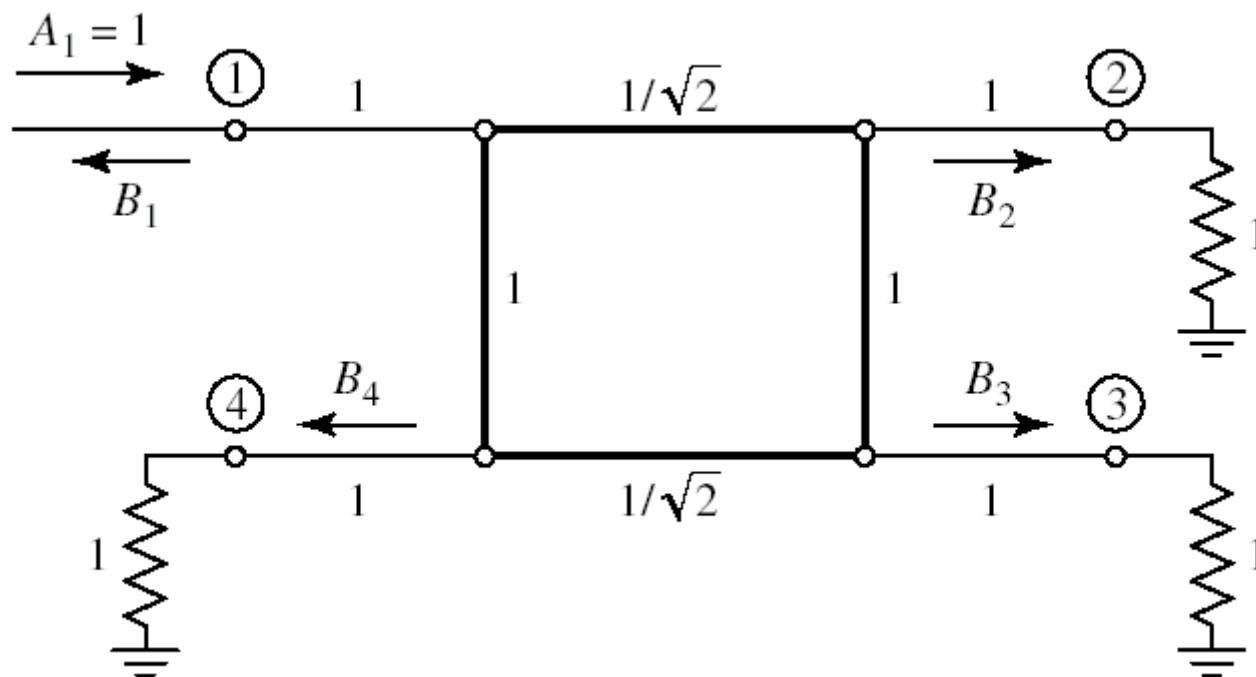

Even/Odd Mode Analysis

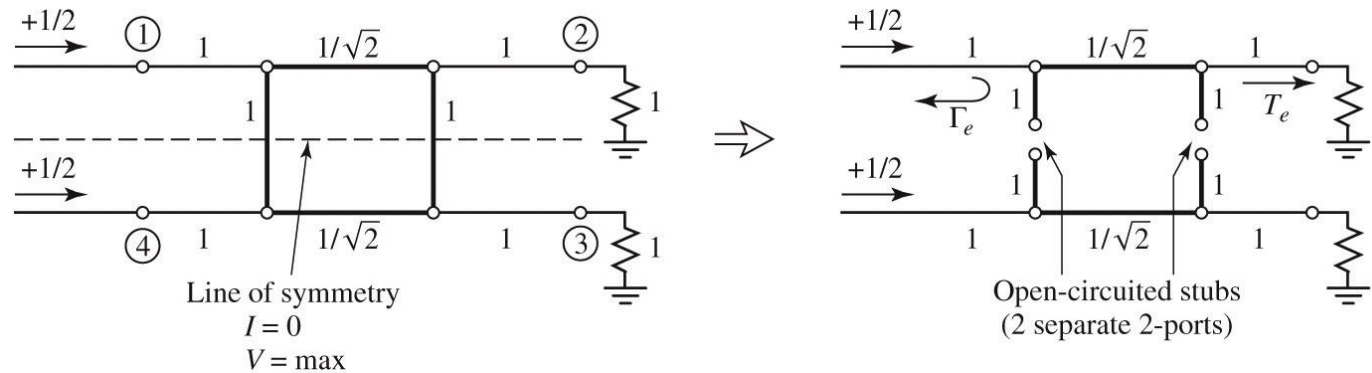

(a)

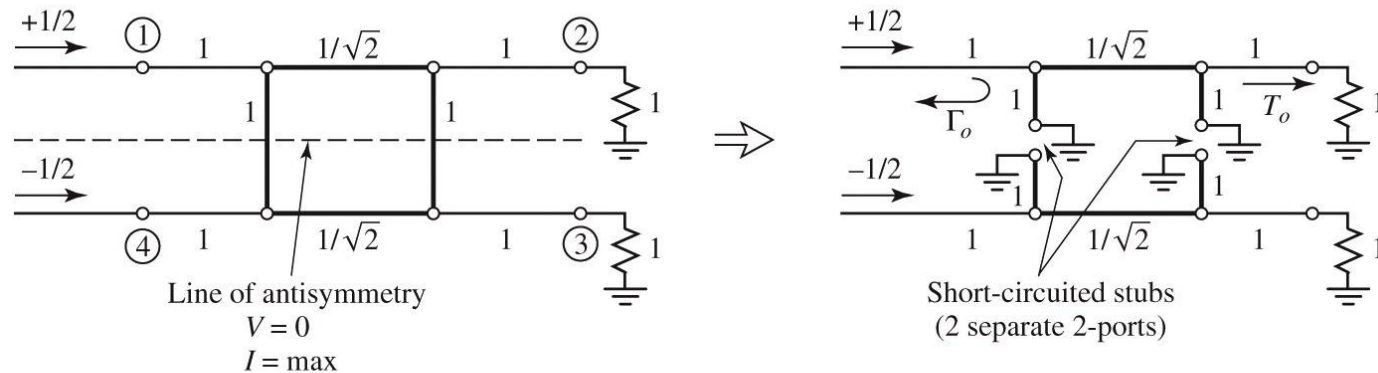

(b)

Figure 7.23
 © John Wiley & Sons, Inc. All rights reserved.

$$b_1 = \frac{1}{2}\Gamma_e + \frac{1}{2}\Gamma_o$$




$$b_2 = \frac{1}{2}T_e + \frac{1}{2}T_o$$

$$b_3 = \frac{1}{2}T_e - \frac{1}{2}T_o$$



$$b_4 = \frac{1}{2}\Gamma_e - \frac{1}{2}\Gamma_o$$

Library of ABCD matrices

TABLE 4.1 *ABCD* Parameters of Some Useful Two-Port Circuits

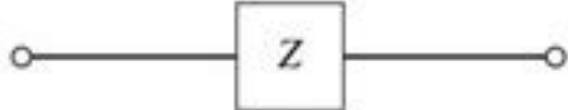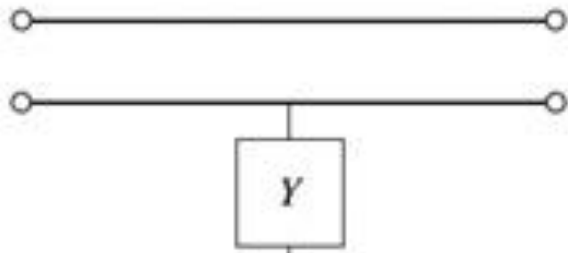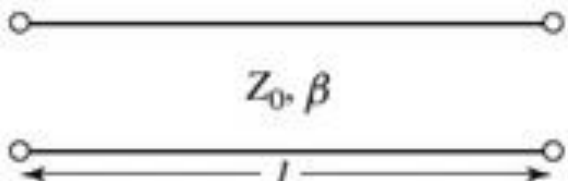Circuit	<i>ABCD</i> Parameters	
	$A = 1$ $C = 0$	$B = Z$ $D = 1$
	$A = 1$ $C = Y$	$B = 0$ $D = 1$
	$A = \cos \beta \ell$ $C = jY_0 \sin \beta \ell$	$B = jZ_0 \sin \beta \ell$ $D = \cos \beta \ell$

S parameters (from ABCD)

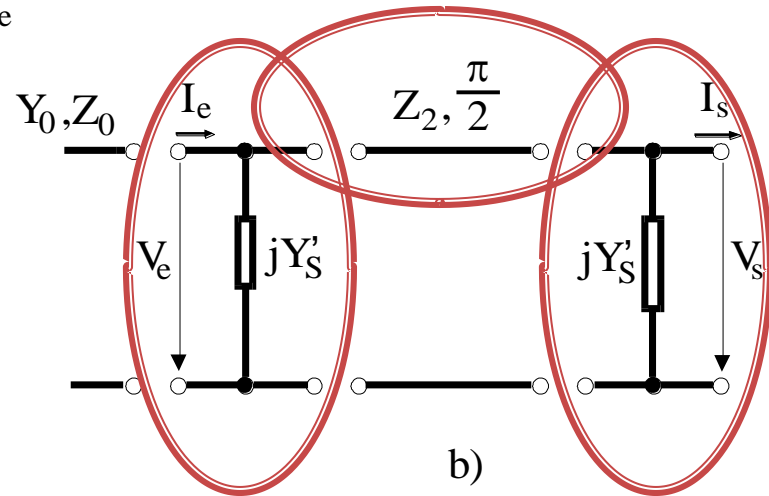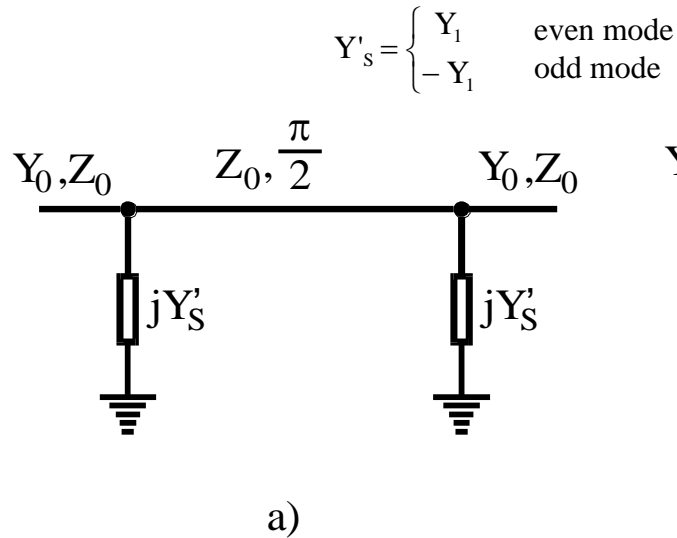

$$\begin{bmatrix} V_e \\ I_e \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ jY'_s & 1 \end{bmatrix} \cdot \begin{bmatrix} 0 & jZ_2 \\ jY_2 & 0 \end{bmatrix} \cdot \begin{bmatrix} 1 & 0 \\ jY'_s & 1 \end{bmatrix} \cdot \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$\begin{bmatrix} V_e \\ I_e \end{bmatrix} = \begin{bmatrix} -Y'_s Z_2 & jZ_2 \\ -jY'^2_s Z_2 + jY_2 & -Y'_s Z_2 \end{bmatrix} \cdot \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$S_{11} = \frac{j\frac{Z_2}{Z_0} - Z_0(-jY'^2_s Z_2 + jY_2)}{-2Y'_s Z_2 + j\frac{Z_2}{Z_0} + Z_0(-jY'^2_s Z_2 + jY_2)}$$

$$S_{12} = \frac{2|(-Y'_s Z_2)^2 - jZ_2(-jY'^2_s Z_2 + jY_2)|}{-2Y'_s Z_2 + j\frac{Z_2}{Z_0} + Z_0(-jY'^2_s Z_2 + jY_2)}$$

$$\Gamma = S_{11} = \frac{j(z_2 - y_2 + y'^2_s z_2)}{-2y'_s z_2 + j(z_2 + y_2 - y'^2_s z_2)} = S_{22}$$

$$S_{21} = \frac{2}{-2Y'_s Z_2 + j\frac{Z_2}{Z_0} + Z_0(-jY'^2_s Z_2 + jY_2)} \quad S_{22} = \frac{j\frac{Z_2}{Z_0} - Z_0(-jY'^2_s Z_2 + jY_2)}{-2Y'_s Z_2 + j\frac{Z_2}{Z_0} + Z_0(-jY'^2_s Z_2 + jY_2)}$$

$$T = S_{21} = \frac{2}{-2y'_s z_2 + j(z_2 + y_2 - y'^2_s z_2)} = S_{12}$$

Relation between two port S parameters and ABCD parameters

$$A = \sqrt{\frac{Z_{01}}{Z_{02}}} \frac{(1 + S_{11} - S_{22} - \Delta S)}{2S_{21}}$$

$$B = \sqrt{Z_{01}Z_{02}} \frac{(1 + S_{11} + S_{22} + \Delta S)}{2S_{21}}$$

$$C = \frac{1}{\sqrt{Z_{01}Z_{02}}} \frac{1 - S_{11} - S_{22} + \Delta S}{2S_{21}}$$

$$D = \sqrt{\frac{Z_{02}}{Z_{01}}} \frac{1 - S_{11} + S_{22} - \Delta S}{2S_{21}}$$

$$\Delta S = S_{11}S_{22} - S_{12}S_{21}$$

$$S_{11} = \frac{AZ_{02} + B - CZ_{01}Z_{02} - DZ_{01}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

$$S_{12} = \frac{2(AD - BC)\sqrt{Z_{01}Z_{02}}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

$$S_{21} = \frac{2\sqrt{Z_{01}Z_{02}}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

$$S_{22} = \frac{-AZ_{02} + B - CZ_{01}Z_{02} + DZ_{01}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

Matching and coupling factor

$$\Gamma_e = \frac{j(z_2 - y_2 + y_1^2 z_2)}{-2y_1 z_2 + j(z_2 + y_2 - y_1^2 z_2)}$$

$$\Gamma_o = \frac{j(z_2 - y_2 + y_1^2 z_2)}{2y_1 z_2 + j(z_2 + y_2 - y_1^2 z_2)}$$

$$T_e = \frac{2}{-2y_1 z_2 + j(z_2 + y_2 - y_1^2 z_2)}$$

$$T_o = \frac{2}{2y_1 z_2 + j(z_2 + y_2 - y_1^2 z_2)}$$

$$b_1 = 0 \Rightarrow z_2 - y_2 + y_1^2 z_2 = 0 \Rightarrow z_2^2 = \frac{1}{1 + y_1^2}$$

$$y_2^2 = 1 + y_1^2$$

$$b_1 = 0 \quad b_4 = 0 \quad b_3 = -y_1 z_2 \quad b_2 = -j z_2$$

$$b_3 = -\frac{\sqrt{y_2^2 - 1}}{y_2}, \quad b_2 = -\frac{j}{y_2}$$

$$b_3 = -C$$

$$b_2 = -j\sqrt{1 - C^2}$$

$$[S] = \begin{bmatrix} 0 & -j\sqrt{1 - C^2} & -C & 0 \\ -j\sqrt{1 - C^2} & 0 & 0 & -C \\ -C & 0 & 0 & -j\sqrt{1 - C^2} \\ 0 & -C & -j\sqrt{1 - C^2} & 0 \end{bmatrix}$$

$$b_1 = \frac{\Gamma_e + \Gamma_o}{2} = \frac{z_2^2 - (y_2 - y_1^2 z_2)^2}{(2y_1 z_2)^2 + (z_2 + y_2 - y_1^2 z_2)^2}$$

$$b_2 = \frac{T_e + T_o}{2} = \frac{-2j(z_2 + y_2 - y_1^2 z_2)}{(2y_1 z_2)^2 + (z_2 + y_2 - y_1^2 z_2)^2}$$

$$b_3 = \frac{T_e - T_o}{2} = \frac{-4y_1 z_2}{(2y_1 z_2)^2 + (z_2 + y_2 - y_1^2 z_2)^2}$$

$$b_4 = \frac{\Gamma_e - \Gamma_o}{2} = \frac{-2jy_1 z_2(z_2 - y_2 + y_1^2 z_2)}{(2y_1 z_2)^2 + (z_2 + y_2 - y_1^2 z_2)^2}$$

$$C = 10 \log \frac{P_1}{P_3} = -20 \log |b_3|, dB$$

$$\beta = \frac{\sqrt{y_2^2 - 1}}{y_2}$$

The quadrature (90°) hybrid

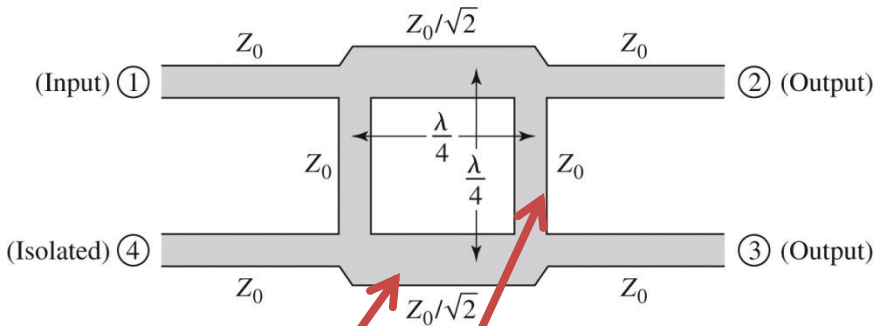


Figure 7.21
© John Wiley & Sons, Inc. All rights reserved.

$$y_2^2 = 1 + y_1^2$$

$$|\beta| = \frac{\sqrt{y_2^2 - 1}}{y_2}$$

$$C[\text{dB}] = -20 \cdot \log_{10} \frac{\sqrt{y_2^2 - 1}}{y_2}$$

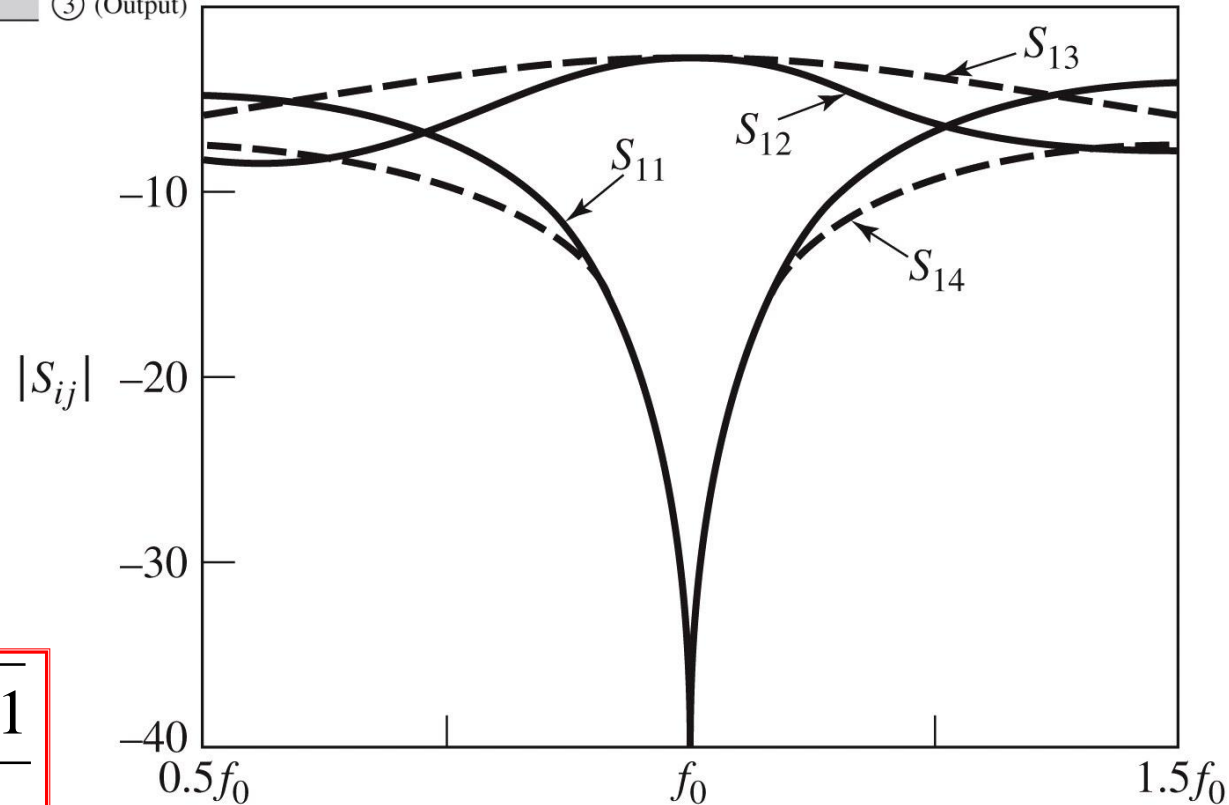


Figure 7.25
© John Wiley & Sons, Inc. All rights reserved.

Example

Design a quadrature (90°) hybrid working on $50\ \Omega$, and plot the S parameters between

$0.5f_0$ and $1.5f_0$, where f_0

is the frequency at which the length of the branches is $\lambda/4$



Solution

A quadrature (90°) hybrid has $C = 3\text{dB}$, then $\beta = 1/\sqrt{2}$


$$y_2 = \sqrt{2} \quad \text{and} \quad y_1 = 1$$

$Z_0 = 50\Omega$ the characteristic impedances will be:
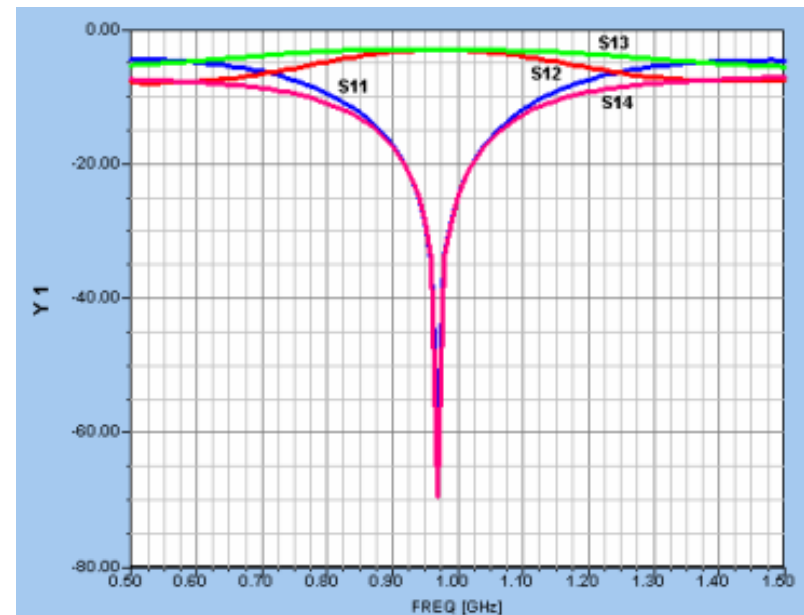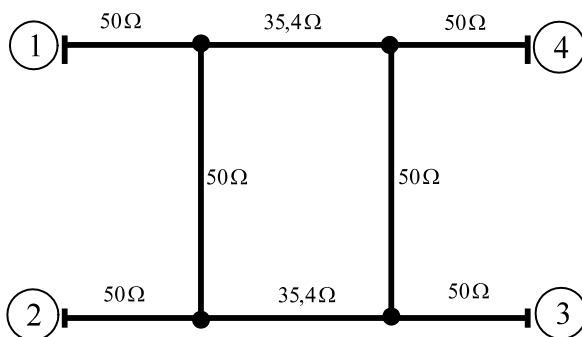
$$Z_1 = Z_0 = 50\Omega \quad Z_2 = \frac{Z_0}{\sqrt{2}} = 35.4\Omega$$



The cuadrature (90°) hybrid

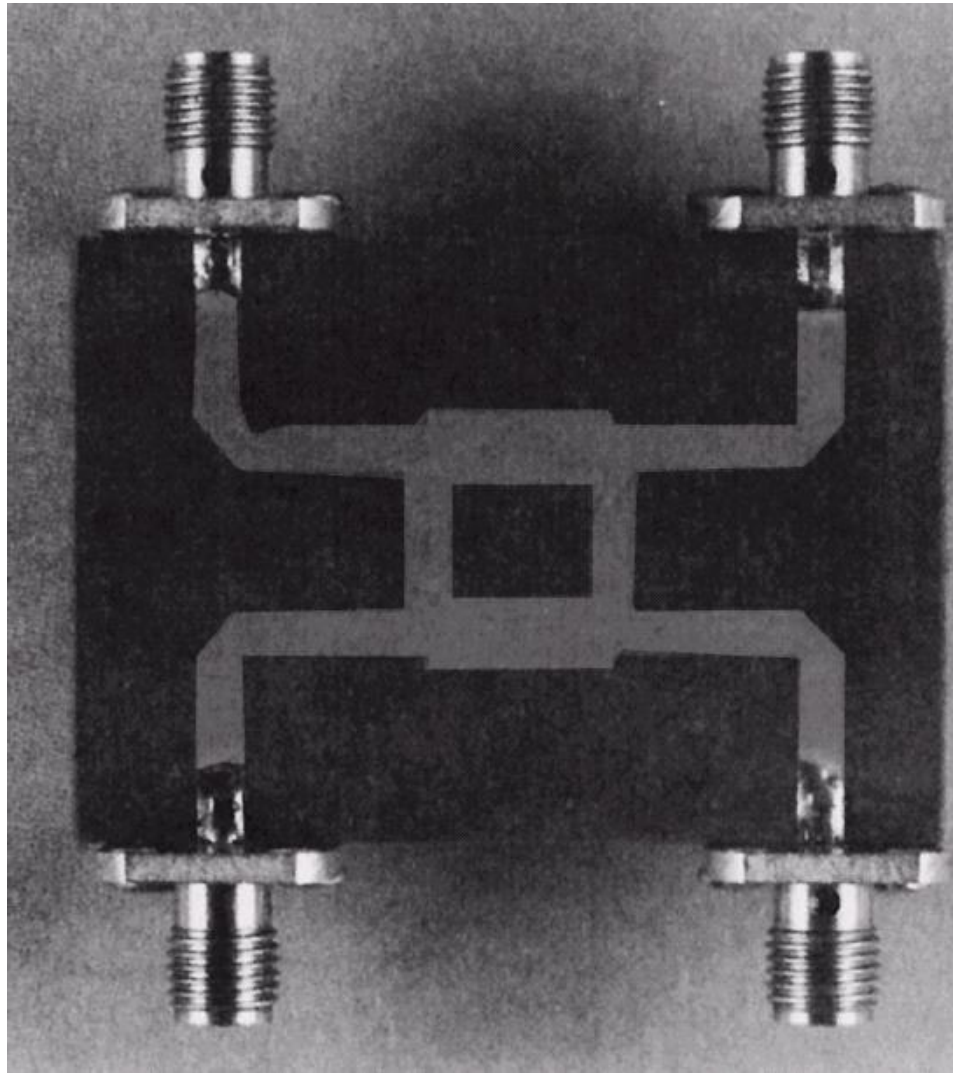

The quadrature (90°) hybrid

- eight-way microstrip power divider with six quadrature hybrids in a Bailey configuration


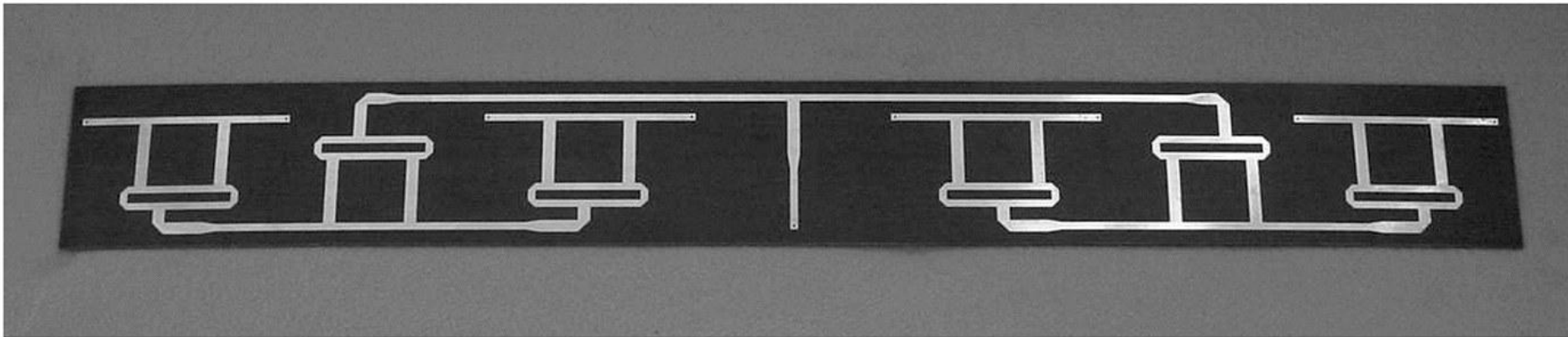



Figure 7.24
Courtesy of ProSensing, Inc., Amherst, Mass.

Datasheet

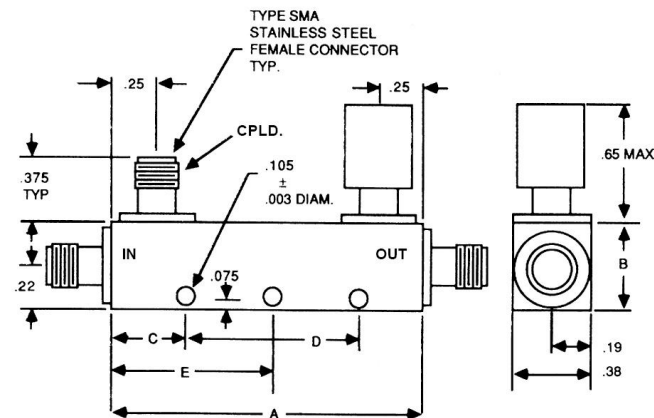

Model No.	Frequency Range (Ghz)	Coupling † (dB)	Freq. Sens. (dB)	Insertion Loss (dB)		Directivity (dB min.)	VSWR max.	
				Excl. Cpld Pwr	True		Primary Line	Secondary Line
MDC6223-6	0.5-1.0	6 ±1.00	±0.60	0.20	1.80	25	1.15	1.15
MDC6223-10	0.5-1.0	10 ±1.25	±0.75	0.20	0.80	25	1.10	1.10
MDC6223-20	0.5-1.0	20 ±1.25	±0.75	0.15	0.20	25	1.10	1.10
MDC6223-30	0.5-1.0	30 ±1.25	±0.75	0.15	0.20	25	1.10	1.10
MDC6224-6	1.0-2.0	6 ±1.00	±0.60	0.20	1.80	25	1.15	1.15
MDC6224-10	1.0-2.0	10 ±1.25	±0.75	0.20	0.80	25	1.10	1.10
MDC6224-20	1.0-2.0	20 ±1.25	±0.75	0.15	0.20	25	1.10	1.10
MDC6224-30	1.0-2.0	30 ±1.25	±0.75	0.15	0.20	25	1.10	1.10
MDC6225-6	2.0-4.0	6 ±1.00	±0.60	0.20	1.80	22	1.15	1.15
MDC6225-10	2.0-4.0	10 ±1.25	±0.75	0.20	0.80	22	1.15	1.15
MDC6225-20	2.0-4.0	20 ±1.25	±0.75	0.15	0.20	22	1.15	1.15
MDC6225-30	2.0-4.0	30 ±1.25	±0.75	0.15	0.20	22	1.15	1.15
MDC6266-6	2.6-5.2	6 ±1.00	±0.60	0.20	1.80	20	1.25	1.25
MDC6266-10	2.6-5.2	10 ±1.25	±0.75	0.20	0.80	20	1.25	1.25
MDC6266-20	2.6-5.2	20 ±1.25	±0.75	0.20	0.25	20	1.25	1.25
MDC6266-30	2.6-5.2	30 ±1.25	±0.75	0.20	0.20	20	1.25	1.25
MDC6226-6	4.0-8.0	6 ±1.00	±0.60	0.25	1.90	20	1.25	1.25
MDC6226-10	4.0-8.0	10 ±1.25	±0.75	0.25	0.90	20	1.25	1.25
MDC6226-20	4.0-8.0	20 ±1.25	±0.75	0.25	0.30	20	1.25	1.25
MDC6226-30	4.0-8.0	30 ±1.25	±0.75	0.25	0.25	20	1.25	1.25
MDC6227-6	7.0-12.4	6 ±1.00	±0.50	0.30	2.00	17	1.30	1.30
MDC6227-10	7.0-12.4	10 ±1.00	±0.50	0.30	1.00	17	1.30	1.30
MDC6227-20	7.0-12.4	20 ±1.00	±0.50	0.30	0.35	17	1.30	1.30

The 180° ring hybrid (rat-race)

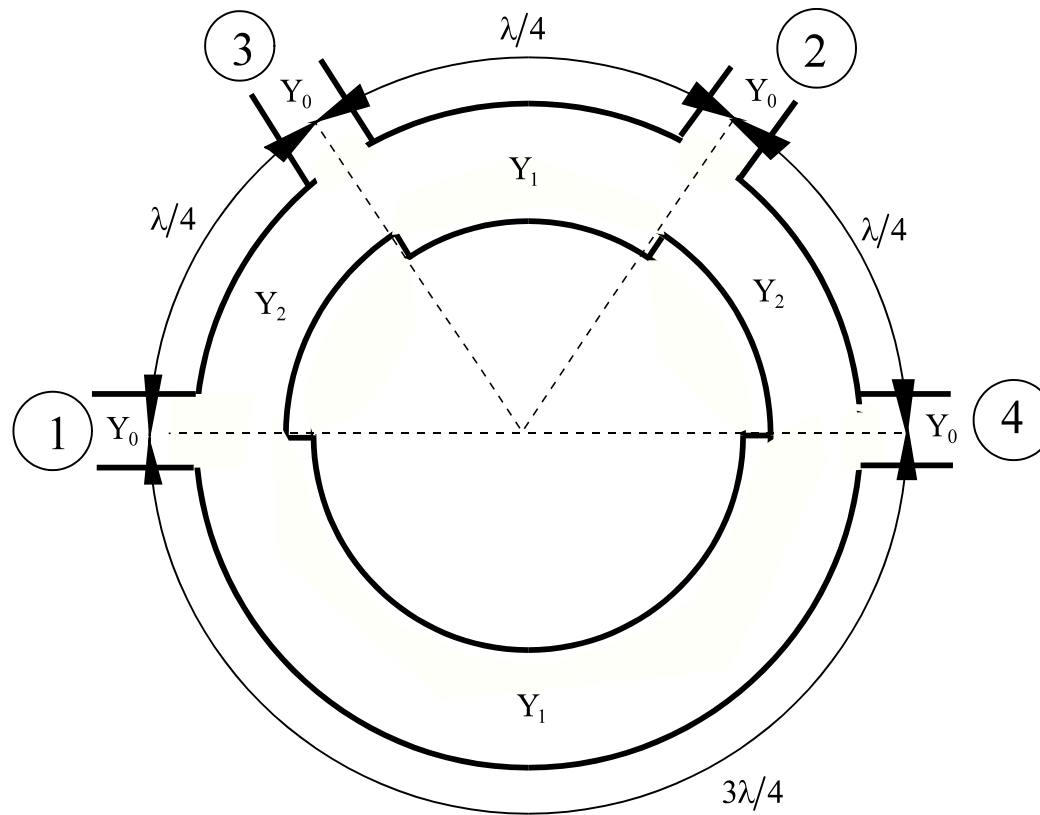

The 180° ring hybrid


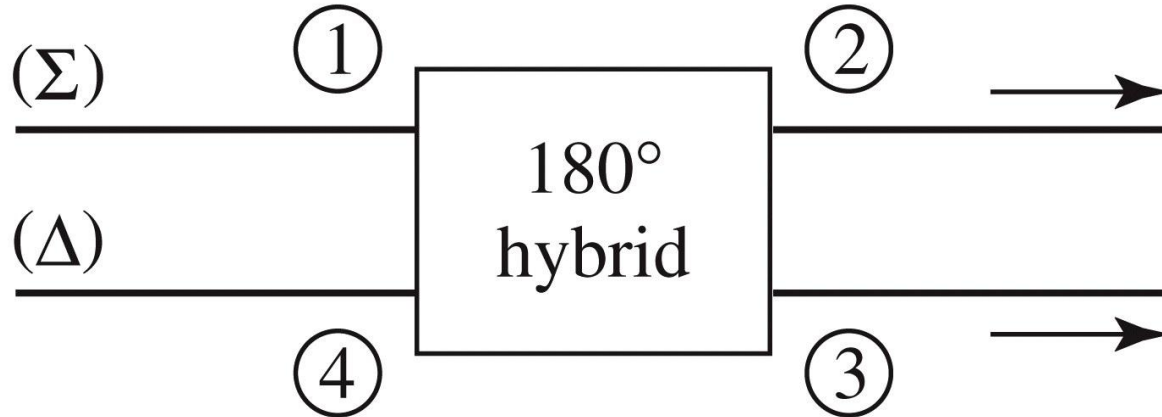



Figure 7.41
© John Wiley & Sons, Inc. All rights reserved.

- The 180° ring hybrid can be operated in different modes:
 - a signal applied to port 1 will be evenly split into two in-phase components at ports 2 and 3
 - input applied to port 4 it will be equally split into two components with a 180° phase difference at ports 2 and 3
 - input signals applied at ports 2 and 3, the sum of the inputs will be formed at port 1, while the difference will be formed at port 4 (power combiner)

Even/Odd Mode Analysis

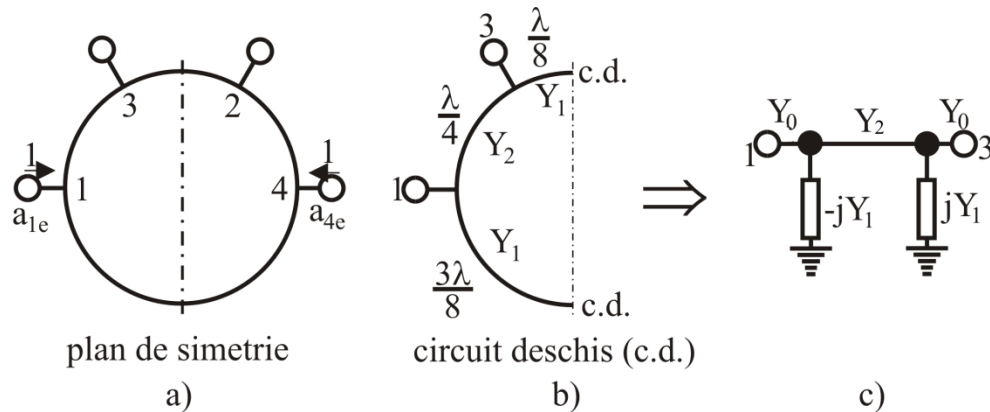

Even Mode

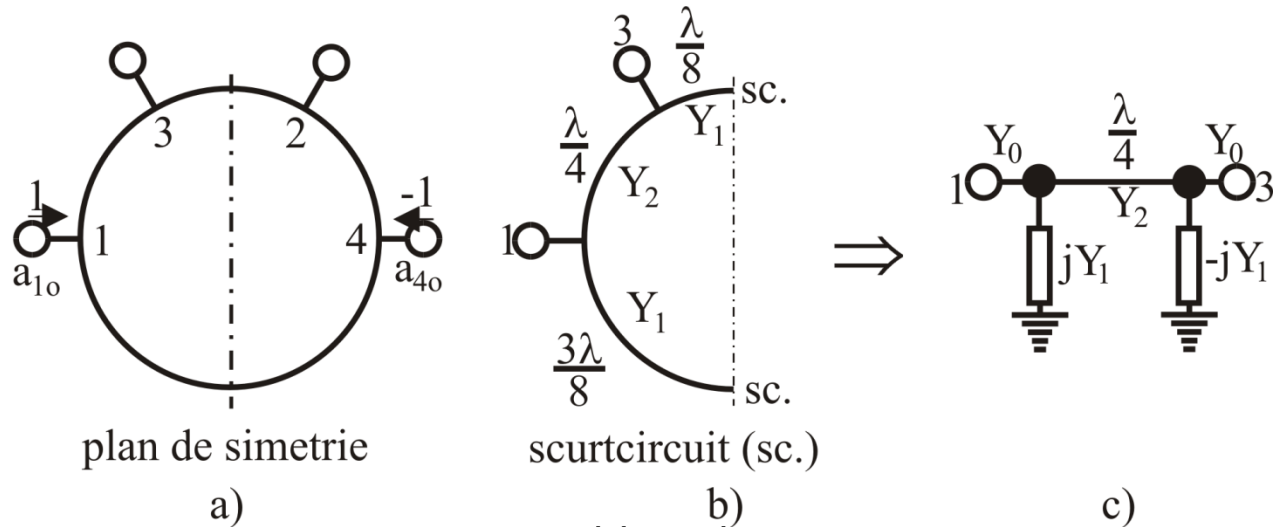

Odd Mode

Even/Odd Mode Analysis

$$S_{11} = \frac{jz_2 y_s + jz_2 - j(y_2 + y_e y_s z_2) - jy_e z_2}{jz_2 y_s + jz_2 + j(y_2 + y_e y_s z_2) + jy_e z_2}$$

$$S_{12} = \frac{2}{jz_2 y_s + jz_2 + j(y_2 + y_e y_s z_2) + jy_e z_2}$$

Even mode:


$$y_e = -jy_1$$

$$y_s = jy_1$$

$$S_{11e} = \frac{z_2 - y_2 - y_1^2 z_2 + 2jz_2 y_1}{z_2 + y_2 + y_1^2 z_2}$$

$$S_{12e} = S_{21e} = \frac{-2j}{z_2 + y_2 + y_1^2 z_2}$$
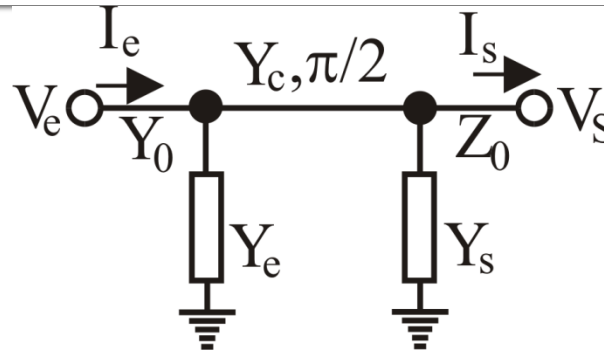
$$S_{22e} = \frac{z_2 - y_2 - y_1^2 z_2 - 2jz_2 y_1}{z_2 + y_2 + y_1^2 z_2}$$



Matching condition

$$y_1^2 + y_2^2 = 1$$

$$[S] = \begin{bmatrix} 0 & 0 & -jy_2 & jy_1 \\ 0 & 0 & -jy_1 & -jy_2 \\ -jy_2 & -jy_1 & 0 & 0 \\ jy_1 & -jy_2 & 0 & 0 \end{bmatrix}$$

$$S_{21} = \frac{2}{jz_2 y_s + jz_2 + j(y_2 + y_e y_s z_2) + jy_e z_2}$$

$$S_{22} = \frac{-jz_2 y_s + jz_2 - j(y_2 + y_e y_s z_2) + jy_e z_2}{jz_2 y_s + jz_2 + j(y_2 + y_e y_s z_2) + jy_e z_2}$$

Odd mode:

$$y_e = jy_1$$


$$y_s = -jy_1$$

$$S_{11o} = \frac{z_2 - y_2 - y_1^2 z_2 - 2jz_2 y_1}{z_2 + y_2 + y_1^2 z_2}$$

$$S_{12o} = S_{21o} = \frac{-2j}{z_2 + y_2 + y_1^2 z_2}$$

$$S_{22o} = \frac{z_2 - y_2 - y_1^2 z_2 + 2jz_2 y_1}{z_2 + y_2 + y_1^2 z_2}$$

The 180° ring hybrid

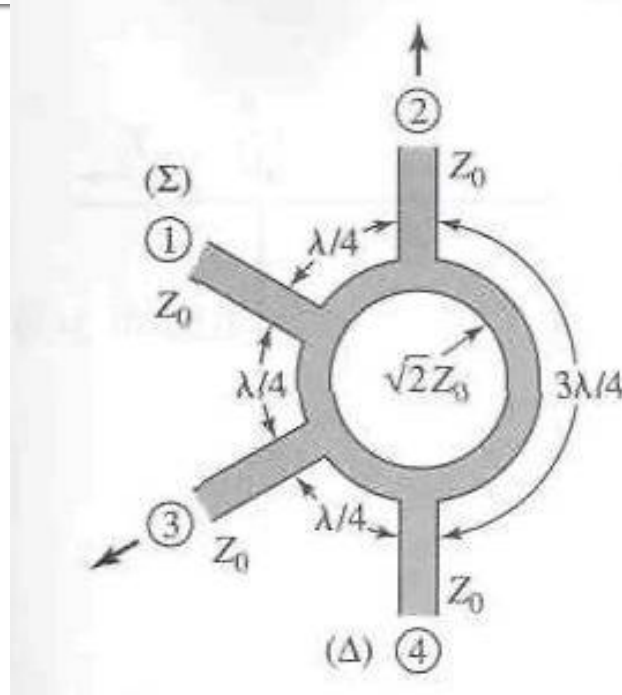

$$[S] = \begin{bmatrix} 0 & -jy_2 & -jy_1 & 0 \\ -jy_2 & 0 & 0 & jy_1 \\ -jy_1 & 0 & 0 & -jy_2 \\ 0 & jy_1 & -jy_2 & 0 \end{bmatrix} = -j \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$

$$C(dB) = -20 \log(\beta) = -20 \log(y_1)$$

Example

Design a ring (180°) hybrid working on $50\ \Omega$, and plot the S parameters between 0.5 and 1.5 of the design frequency.

$$C\ [\text{dB}] = -20 \log(y_1)$$

$$\sqrt{2}Z_0 = 70.7\ \Omega$$


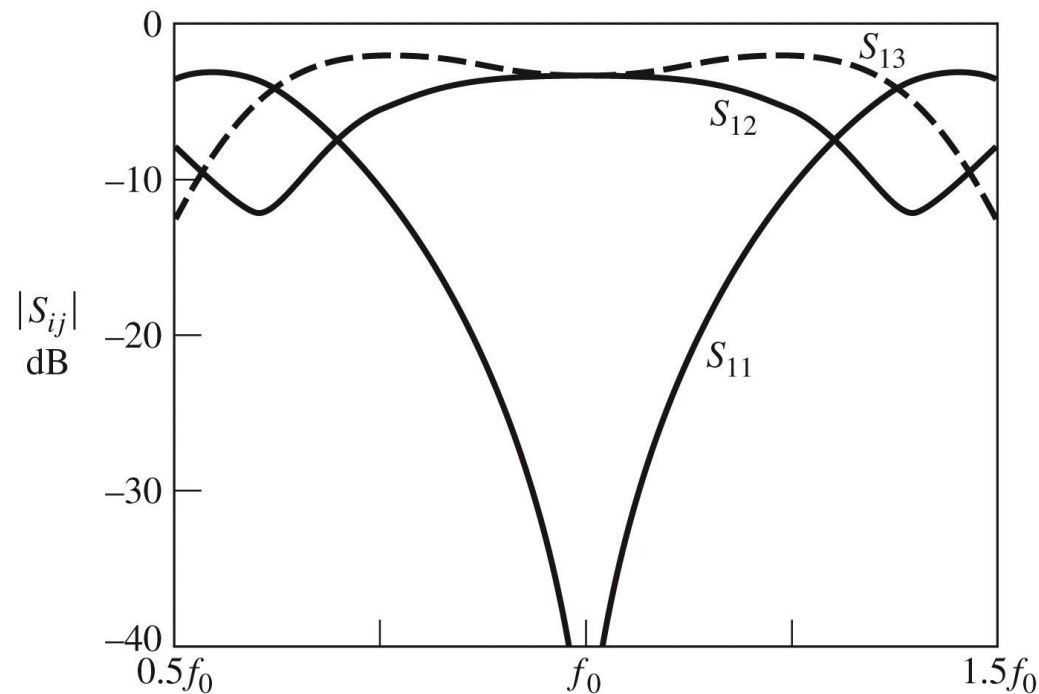


Figure 7.46
© John Wiley & Sons, Inc. All rights reserved.

The 180° ring hybrid

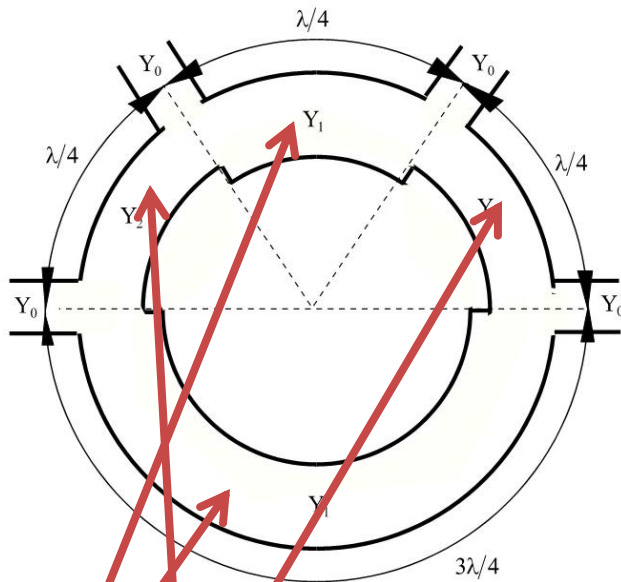

$$y_1^2 + y_2^2 = 1$$

$$|\beta| = y_1$$

$$C \text{ [dB]} = -20 \cdot \log_{10}(y_1)$$

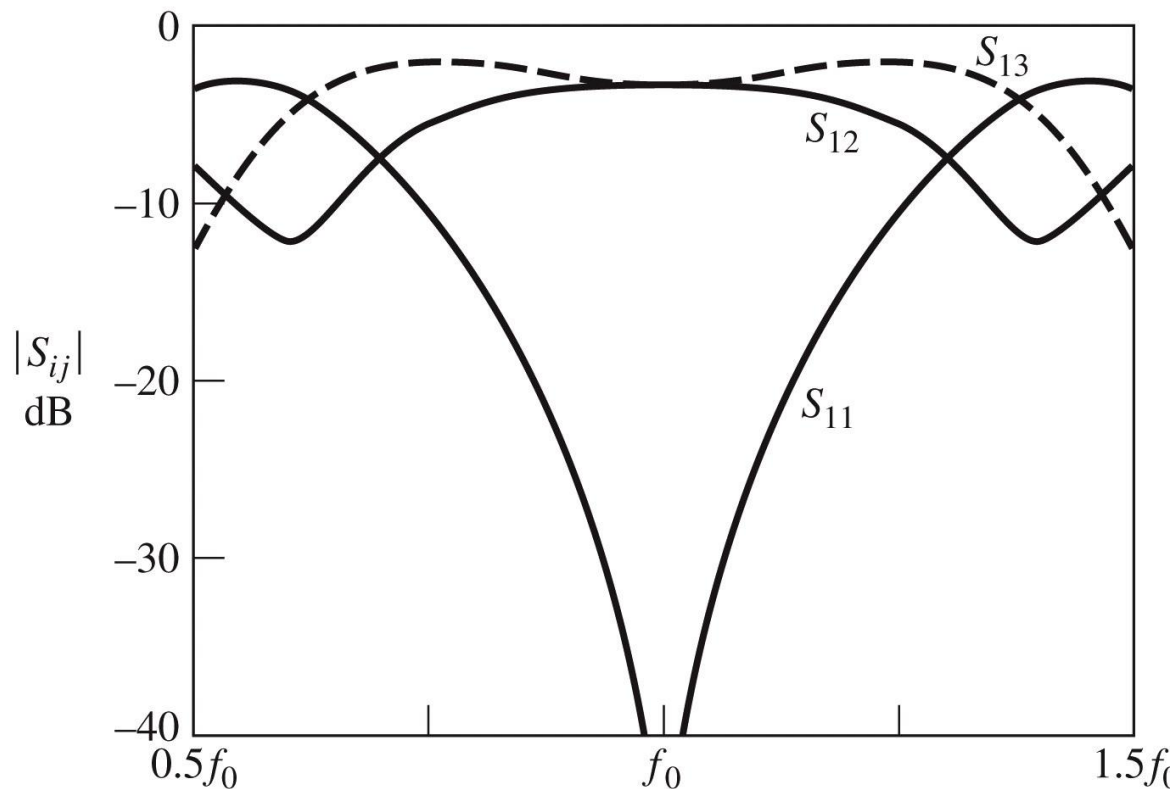


Figure 7.46
© John Wiley & Sons, Inc. All rights reserved.

The 180° ring hybrid


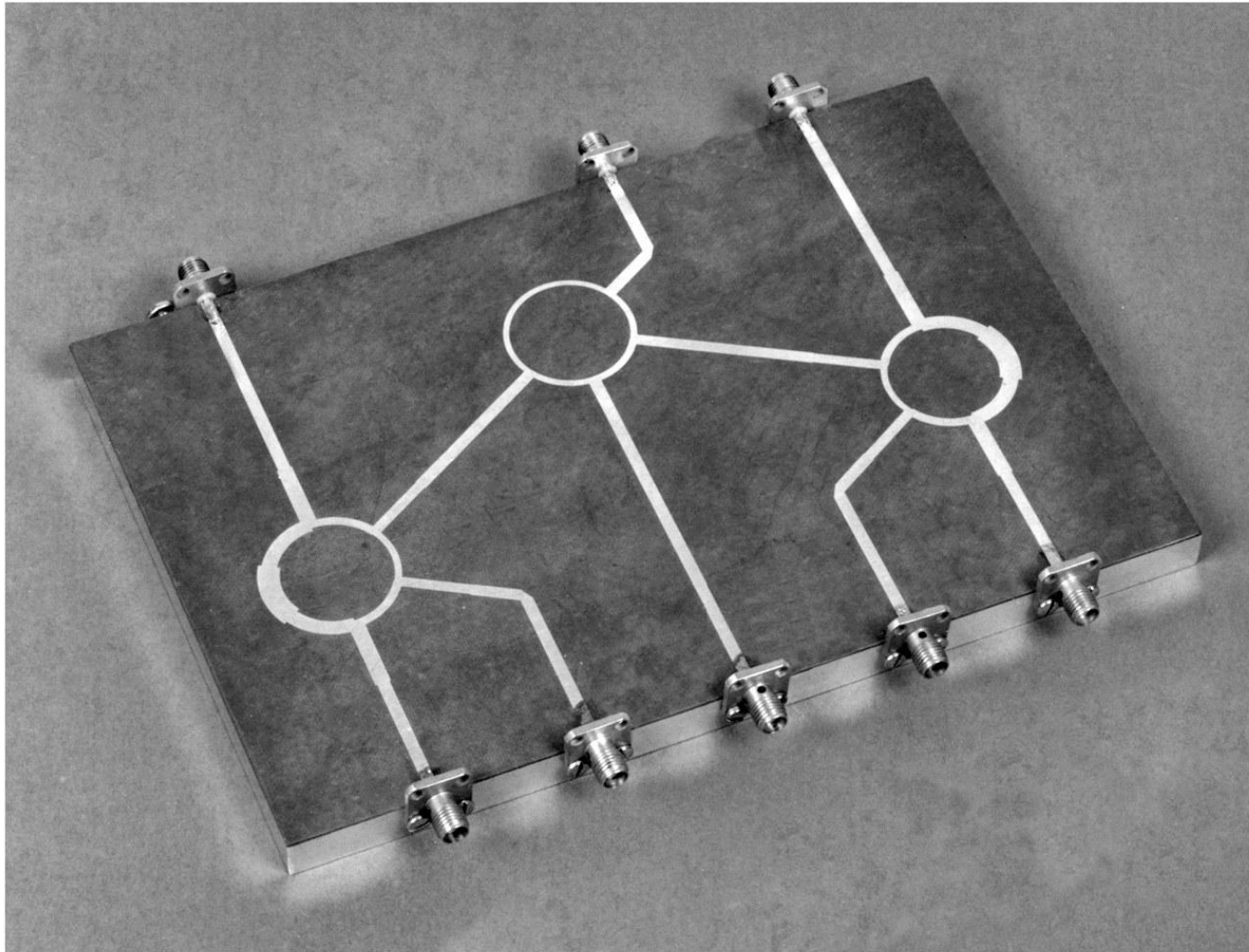


Figure 7.43
Courtesy of M. D. Abouzahra, MIT Lincoln Laboratory, Lexington, Mass.

Coupled Line Coupler

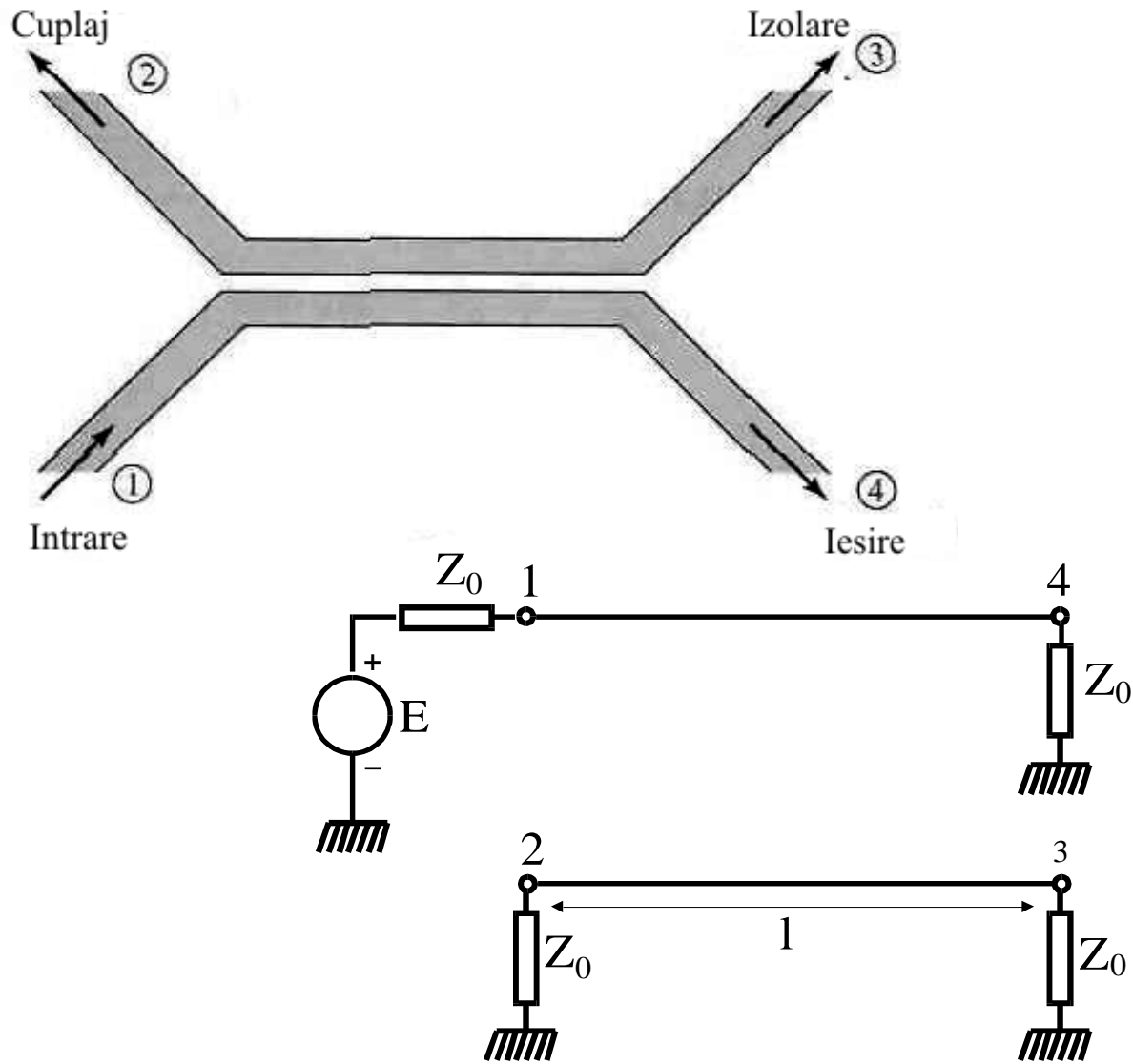

Coupled Lines



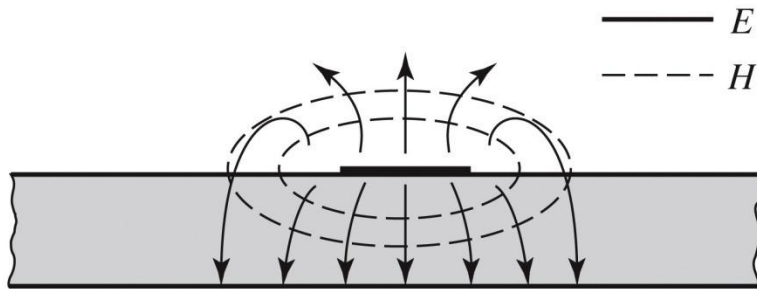


Figure 3.25b
© John Wiley & Sons, Inc. All rights reserved.

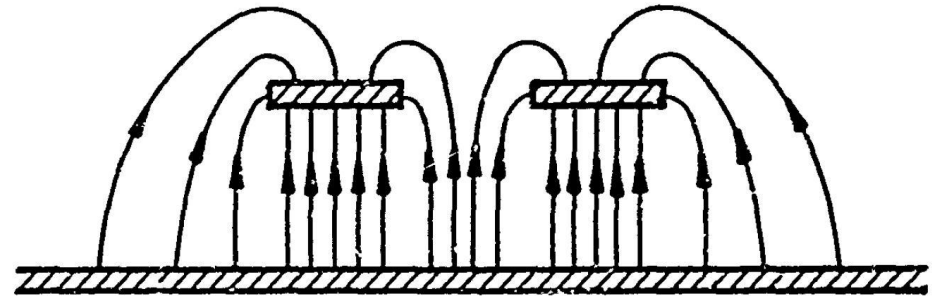

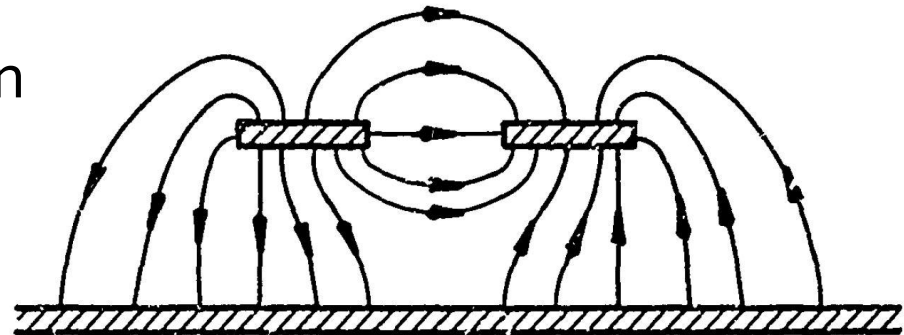b) EVEN MODE ELECTRIC FIELD PATTERN (SCHEMATIC)



c) ODD MODE ELECTRIC FIELD PATTERN (SCHEMATIC)

- Even mode - characterizes the common mode signal on the two lines
- Odd mode - characterizes the differential mode signal between the two lines
- Each of the two modes is characterized by **different** characteristic impedances

Coupled Lines

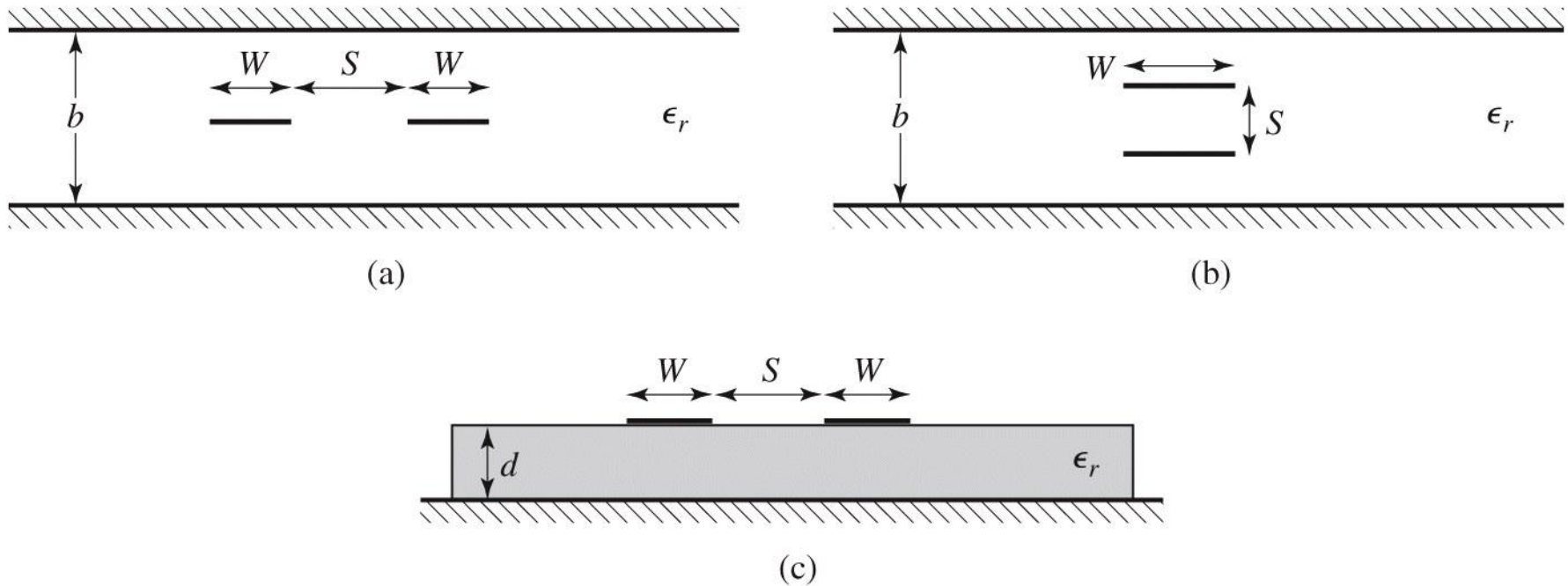


Figure 7.26
© John Wiley & Sons, Inc. All rights reserved.

Coupled Lines



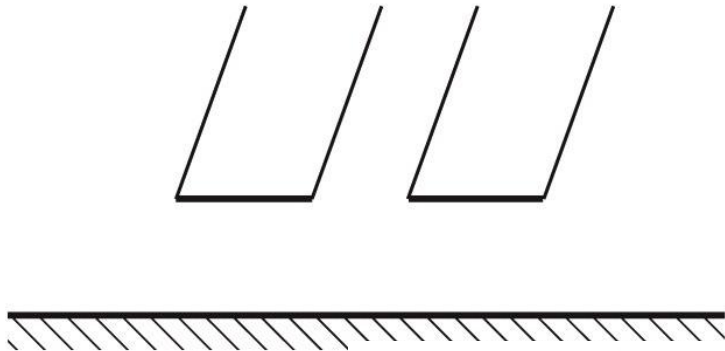


Figure 7.27

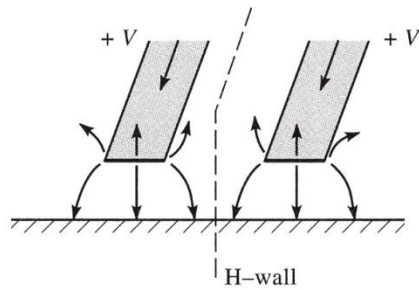
© John Wiley & Sons, Inc. All rights reserved.




⇒

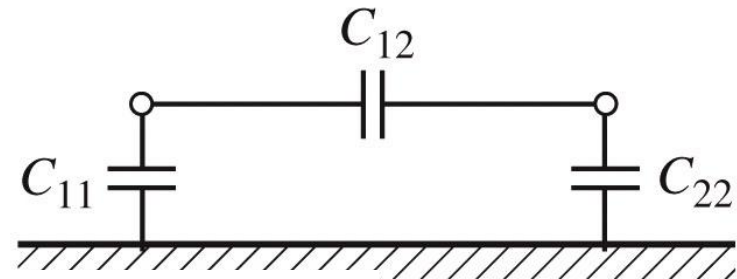

(a)

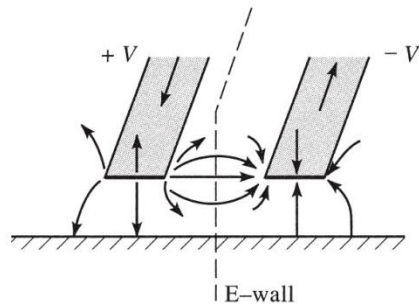

⇒

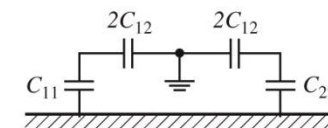


(b)

Figure 7.28


© John Wiley & Sons, Inc. All rights reserved.

Matching in Coupled Line Coupler

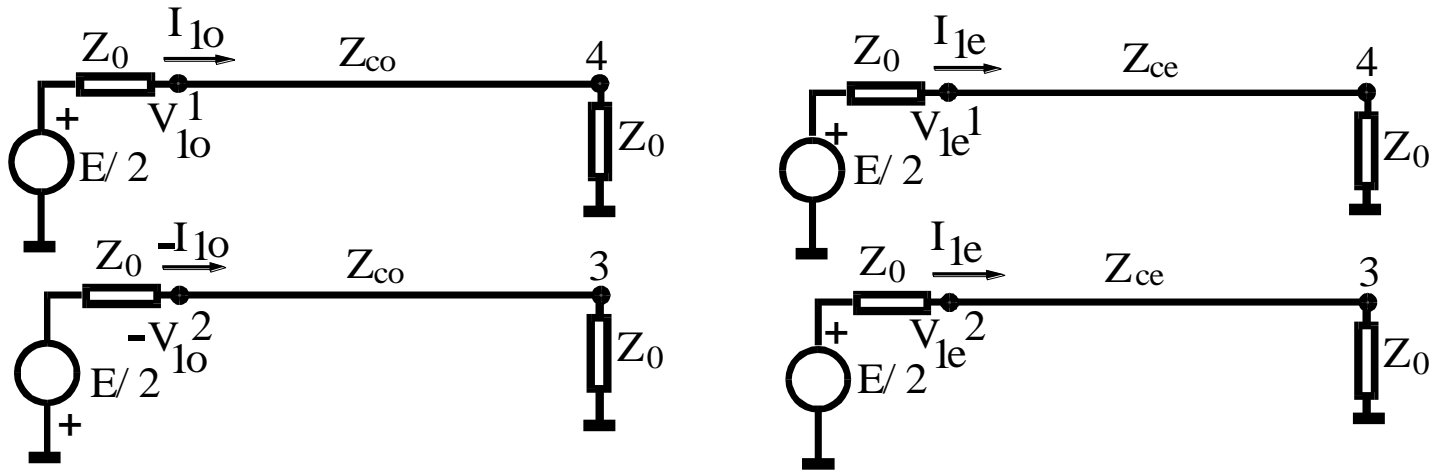


$$\begin{cases} Z_{ce}Z_{co} = Z_0^2 \\ \theta_e = \theta_o \end{cases}$$

Directivity and Coupling factor

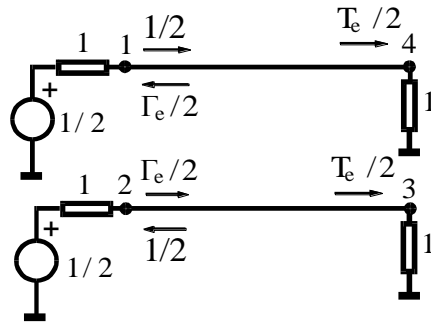

modul par

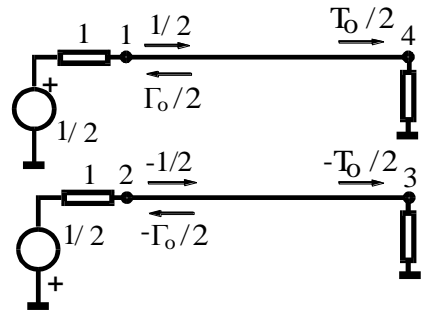

modul impar

$$a_1 = a_{1e} + a_{1o} = 1, a_2 = a_3 = a_4 = 0$$

$$b_1 = \frac{1}{2}(\Gamma_e + \Gamma_o) = 0 \Leftrightarrow$$

$$b_2 = \frac{1}{2}(\Gamma_e - \Gamma_o) = \frac{jC \sin(\theta)}{\cos(\theta)\sqrt{1-C^2} + j\sin(\theta)}$$

$$b_3 = \frac{1}{2}(T_e - T_o) = 0$$

$$b_4 = \frac{1}{2}(T_e + T_o) = \frac{\sqrt{1-C^2}}{\cos(\theta)\sqrt{1-C^2} + j\sin(\theta)}$$

$$C = \frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}}$$

$$\theta = \pi/2$$

$$[S] = \begin{bmatrix} 0 & C & 0 & -j\sqrt{1-C^2} \\ C & 0 & -j\sqrt{1-C^2} & 0 \\ 0 & -j\sqrt{1-C^2} & 0 & C \\ -j\sqrt{1-C^2} & 0 & C & 0 \end{bmatrix}$$

Coupled Line Coupler


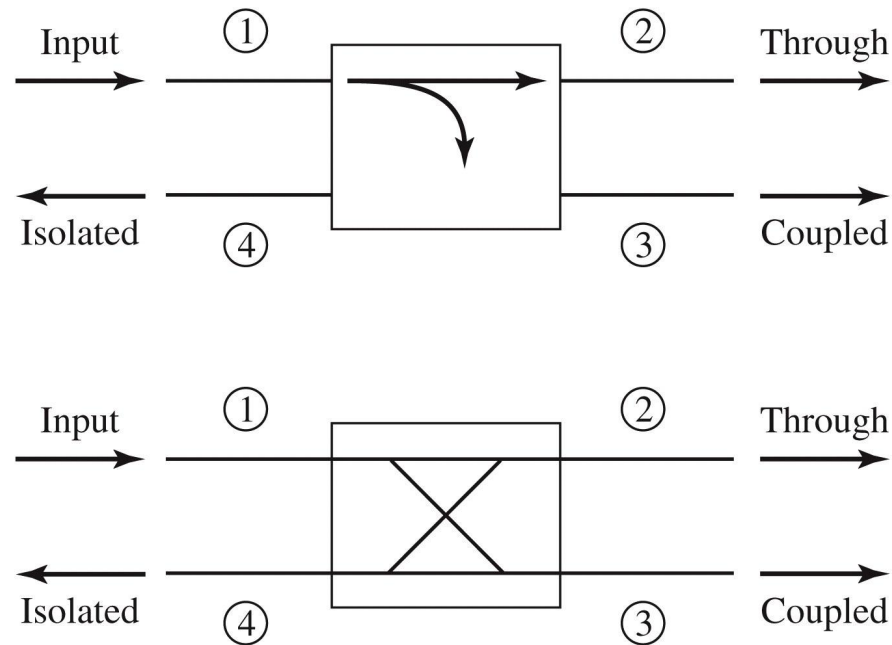


Figure 7.4
© John Wiley & Sons, Inc. All rights reserved.


$$[S] = -j \cdot \begin{bmatrix} 0 & \sqrt{1-C^2} & jC & 0 \\ \sqrt{1-C^2} & 0 & 0 & jC \\ jC & 0 & 0 & \sqrt{1-C^2} \\ 0 & jC & \sqrt{1-C^2} & 0 \end{bmatrix}$$

$$[S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & j & 0 \\ 1 & 0 & 0 & j \\ j & 0 & 0 & 1 \\ 0 & j & 1 & 0 \end{bmatrix}$$

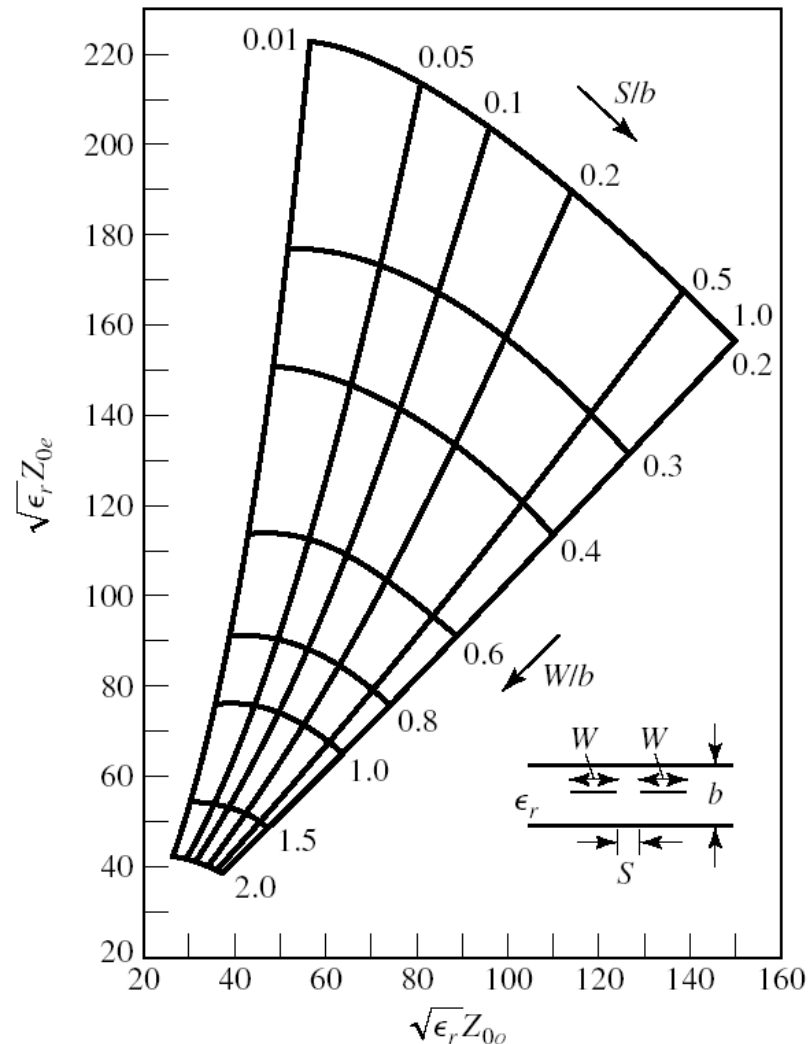
Normalized even- and odd-mode characteristic impedance design data for edge-coupled striplines.



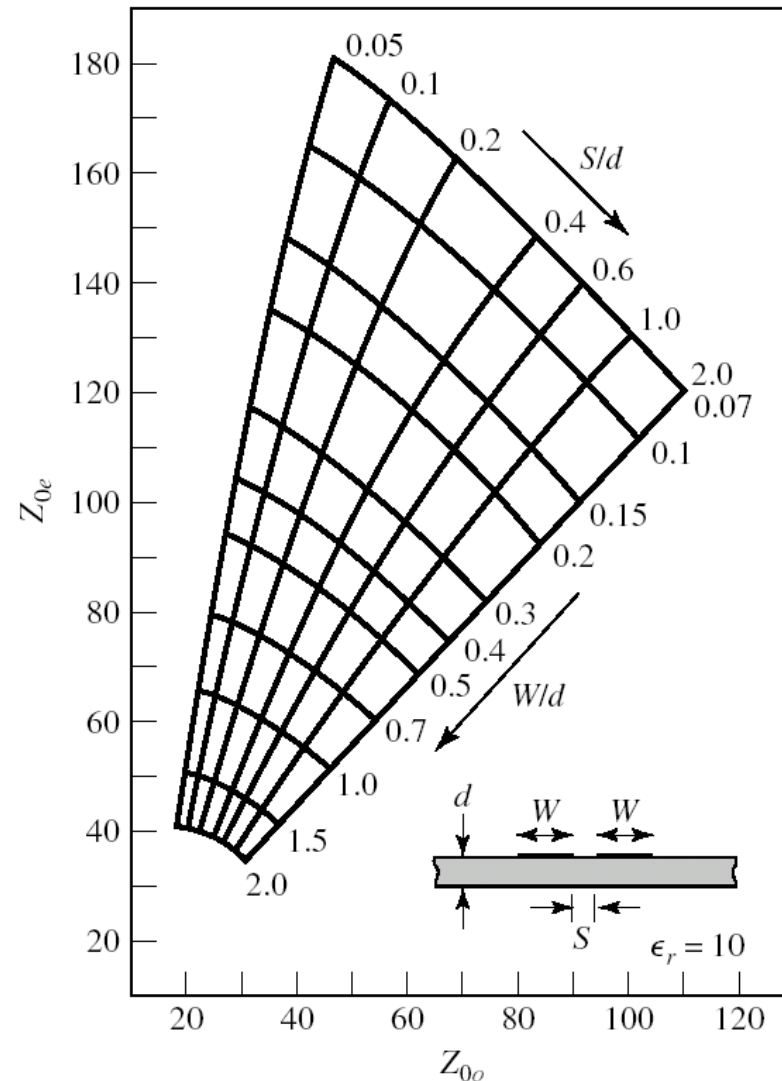
Even- and odd-mode characteristic impedance design data for coupled microstrip lines on a substrate with $\epsilon_r = 10$.



Coupled Line Coupler

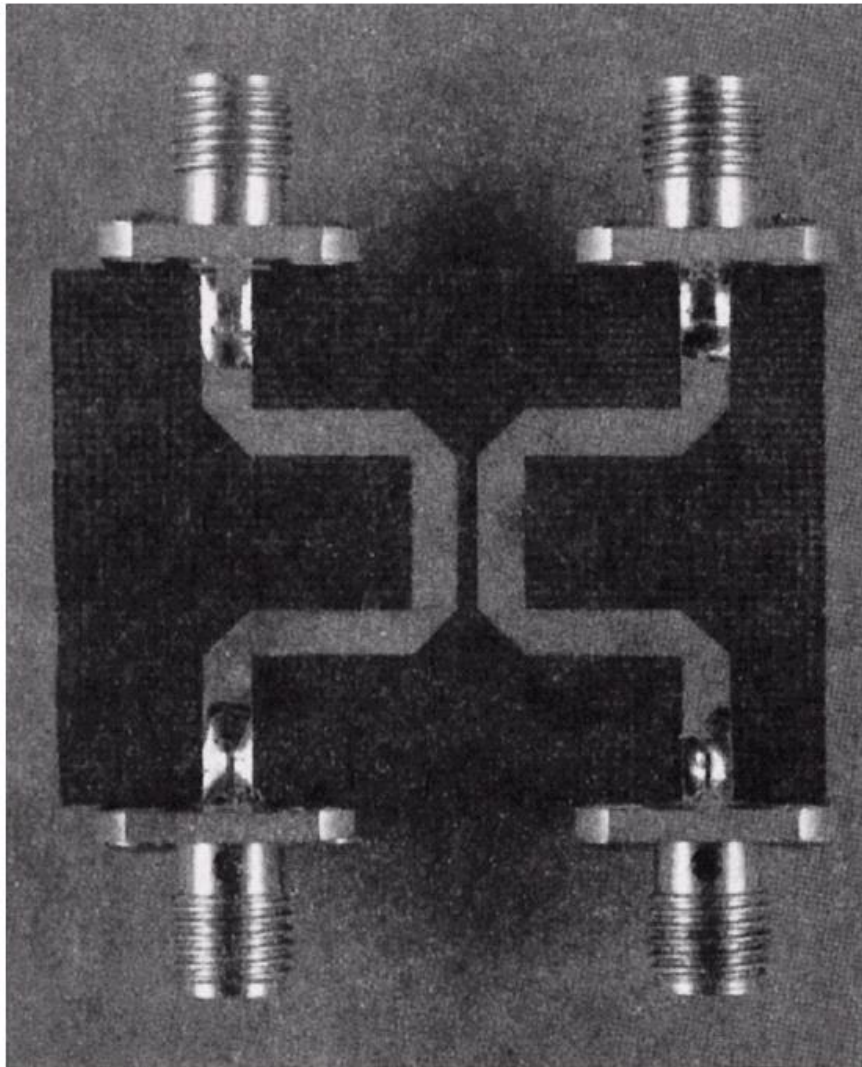

Coupled Line Coupler

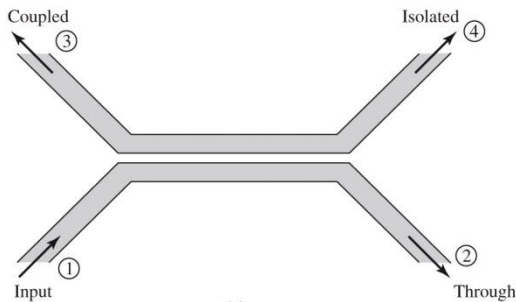

Coupling, Directivity (dB)

$$Z_{ce}Z_{co} = Z_0^2$$

$$|\beta| = \frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}}$$

$$C \text{ [dB]} = -20 \cdot \log_{10} \left(\frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}} \right)$$

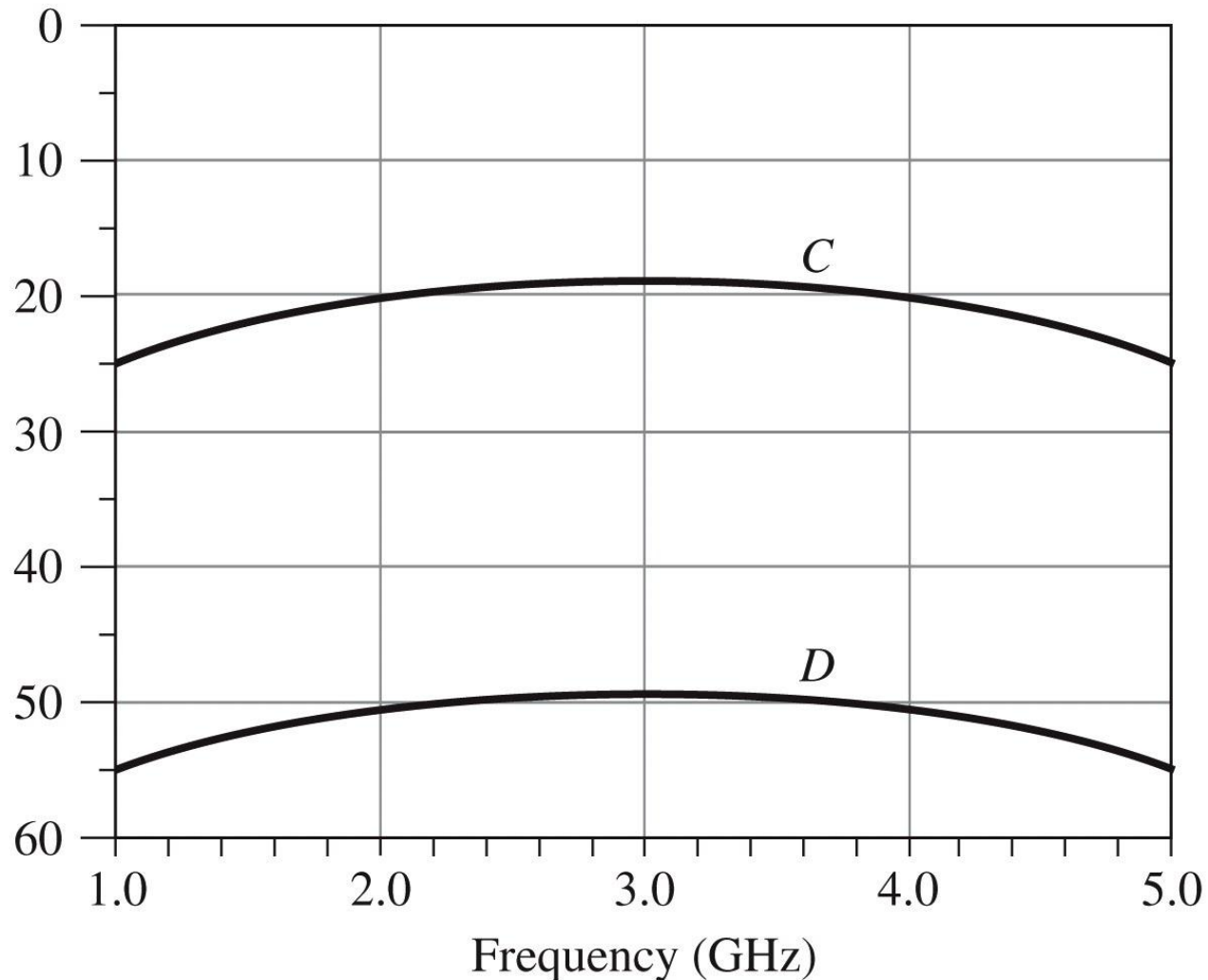


Figure 7.34

Example

Design a coupled line coupler with 20 dB coupling factor, using stripline technology, with a distance between ground planes of 0.158 cm and an electrical permittivity of 2.56, working on 50Ω , at the design frequency of 3 GHz. Plot the coupling and directivity between 1 and 5 GHz.

Solution

$$C = 10^{-20/20} = 0.1$$

$$Z_{co} = 50 \sqrt{\frac{0.9}{1.1}} = 45.23 \Omega$$

$$Z_{ce} = 50 \sqrt{\frac{1.1}{0.9}} = 55.28 \Omega$$

TRL - Edge-coupled Symmetric Stripline (CPL)1

File Edit View Structure Window Help

Edge-coupled Symmetric Stripline (CPL)1

Dimensions

W 1.14072

S 0.51747

P 15.6142

Electrical

Z0 50

K 20

E 90

Zo 45.2267

Ze 55.2771

Units

Dimension mm

Frequency GHz

Impedance Ohm

Electrical Length Deg

Resistivity uOhm*cm

Frequency 3 Analysis Auto Calculate Off ! Reset All ! Synthesis 3

Substrate

Required

B 1.58 ER 2.56

Optional

TAND 0


Metallization

Layers	Metal Name	Code	Resistivity	Thickness	
Bottom	*None*				Reset
Middle	*None*				Reset
Top	*None*				Reset

RGH 0 Add new metal



For Help, press F1

NUM

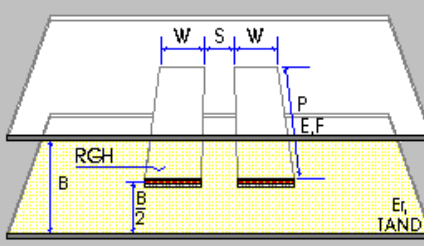

$$Z_{ce} = Z_0 \sqrt{\frac{1+C}{1-C}}, Z_{co} = Z_0 \sqrt{\frac{1-C}{1+C}}$$

Simulation

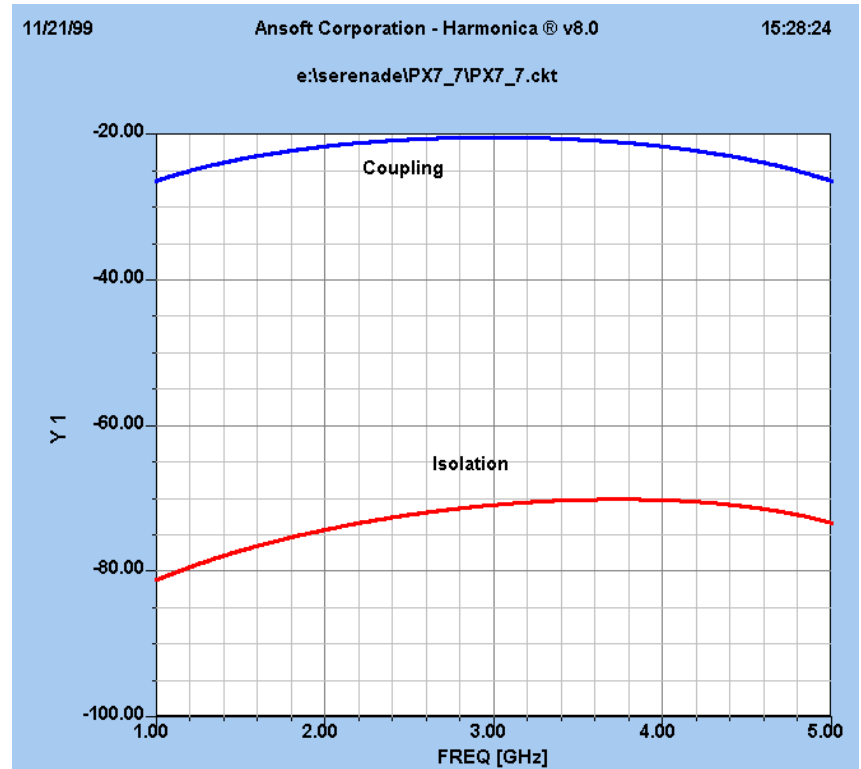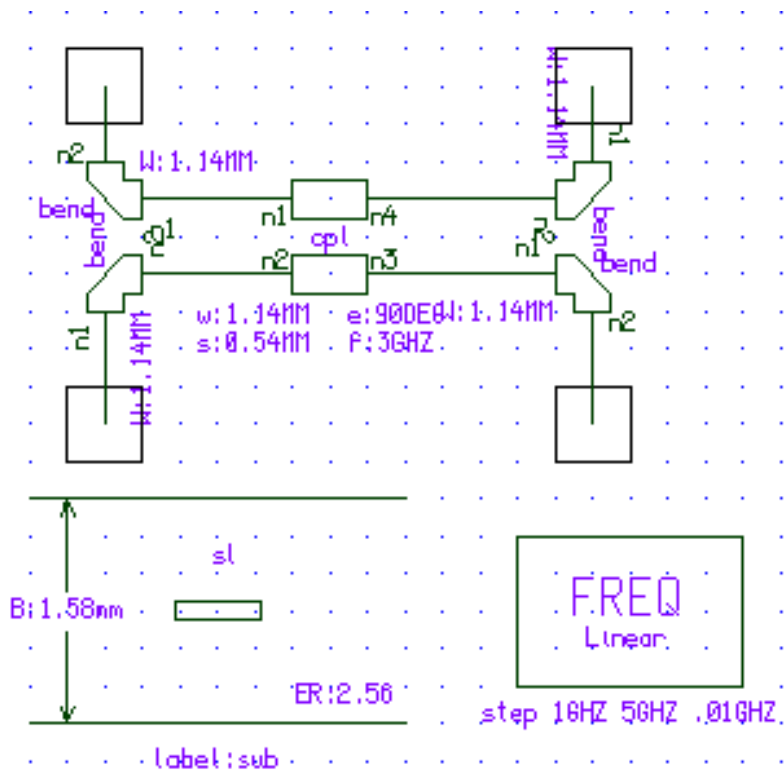

Multisection Coupled Line Couplers

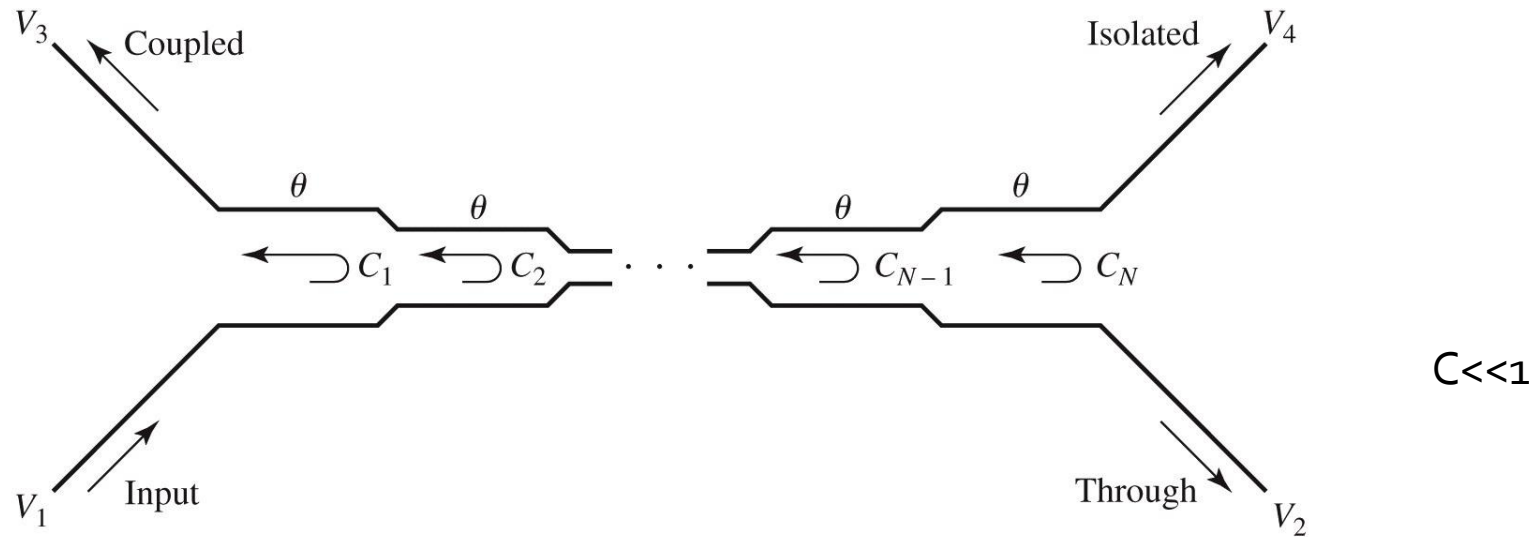


Figure 7.35

© John Wiley & Sons, Inc. All rights reserved.

$$\frac{V_3}{V_1} = b_3 = \frac{jC \sin \theta}{\cos \theta \sqrt{1-C^2} + j \sin \theta} = \frac{jC \tan \theta}{\sqrt{1-C^2} + j \tan \theta} \approx \frac{jC \tan \theta}{1 + j \tan \theta} = jC \sin \theta e^{-j\theta}$$

$$\frac{V_2}{V_1} = b_2 = \frac{\sqrt{1-C^2}}{\cos \theta \sqrt{1-C^2} + j \sin \theta} \approx \frac{1}{\cos \theta + j \sin \theta} = e^{-j\theta}$$

$$C = \frac{V_3}{V_1} = 2j \sin \theta e^{-j\theta} e^{-j(N-1)\theta} \left[C_1 \cos(N-1)\theta + C_2 \cos(N-3)\theta + \dots + \frac{1}{2} C_{\frac{N+1}{2}} \right]$$

Example

Design a three sections coupled line coupler with 20 dB coupling factor, binomial characteristic (maximum flat), working on 50Ω , at the design frequency of 3 GHz. Plot the coupling and directivity between 1 and 5 GHz

Solution

$$\left. \frac{d^n}{d\theta^n} C(\theta) \right|_{\theta=\pi/2} = 0, n=1,2$$

$$C = \left| \frac{V_3}{V_1} \right| = 2 \sin \theta \left[C_1 \cos 2\theta + \frac{1}{2} C_2 \right] = C_1 (\sin 3\theta - \sin \theta) + C_2 \sin \theta$$

$$\left. \frac{dC}{d\theta} \right|_{\theta=\pi/2} = [3C_1 \cos 3\theta + (C_2 - C_1) \cos \theta] \big|_{\theta=\pi/2} = 0$$

$$\left. \frac{d^2 C}{d\theta^2} \right|_{\theta=\pi/2} = [-9C_1 \sin 3\theta - (C_2 - C_1) \sin \theta] \big|_{\theta=\pi/2} = 10C_1 - C_2 = 0$$

$$\begin{cases} C_2 - 2C_1 = 0.1 \\ 10C_1 - C_2 = 0 \end{cases}$$

$$\begin{cases} C_1 = C_3 = 0.0125 \\ C_2 = 0.125 \end{cases}$$


$$Z_{0e}^1 = Z_{0e}^3 = 50 \sqrt{\frac{1.0125}{0.9875}} = 50.63 \Omega$$

$$Z_{0o}^1 = Z_{0o}^3 = 50 \sqrt{\frac{0.9875}{1.0125}} = 49.38 \Omega$$

$$Z_{0e}^2 = 50 \sqrt{\frac{1.125}{0.875}} = 56.69 \Omega$$

$$Z_{0o}^2 = 50 \sqrt{\frac{0.875}{1.125}} = 44.10 \Omega$$

Simulare

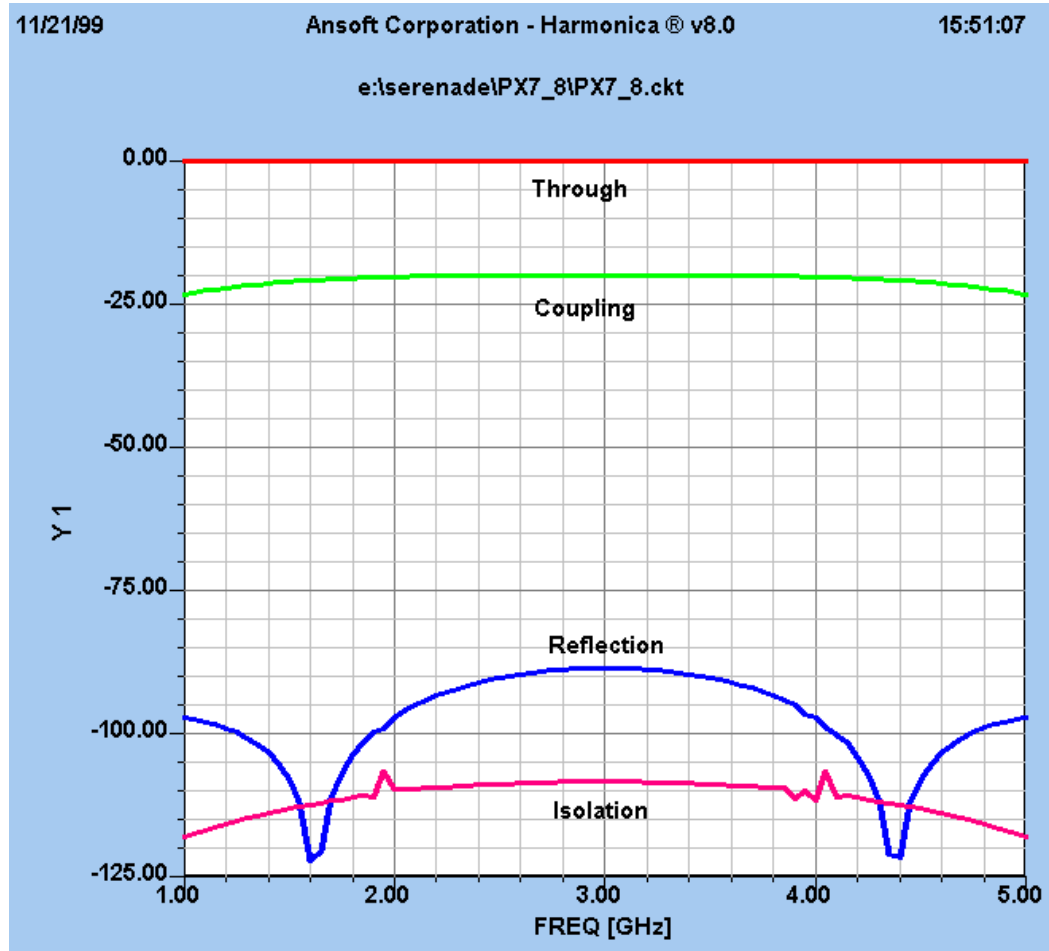

The Lange Coupler

- allows achieving coupling factors of 3 or 6 dB


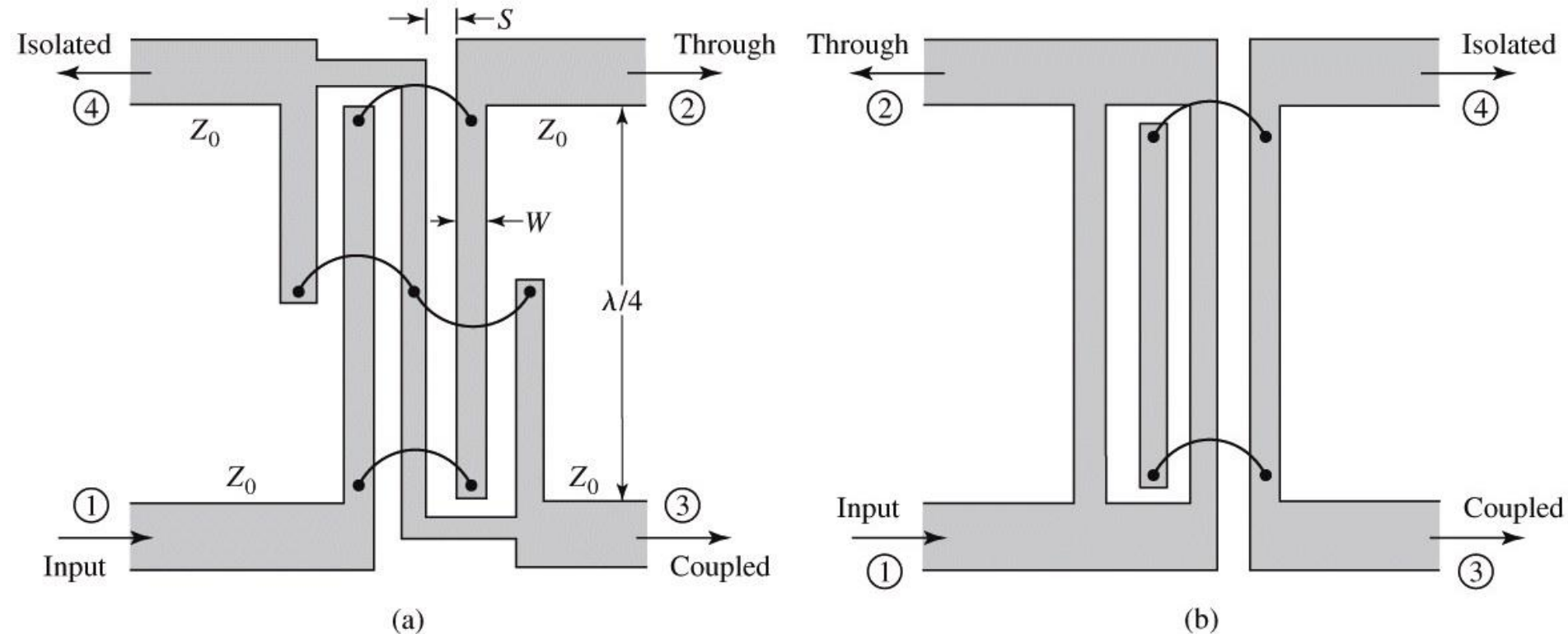



Figure 7.38

© John Wiley & Sons, Inc. All rights reserved.

The Lange Coupler

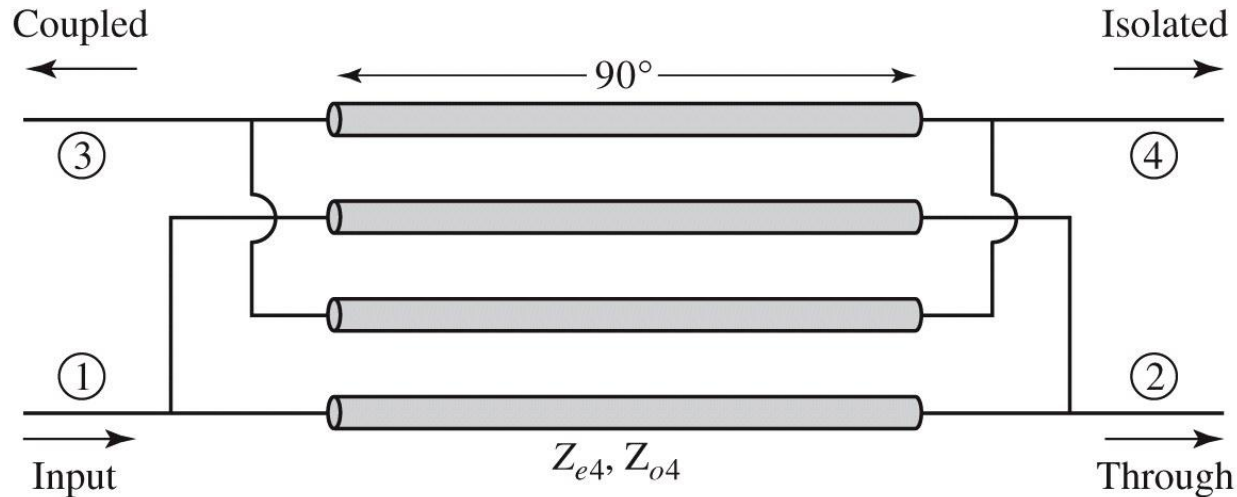


(a)

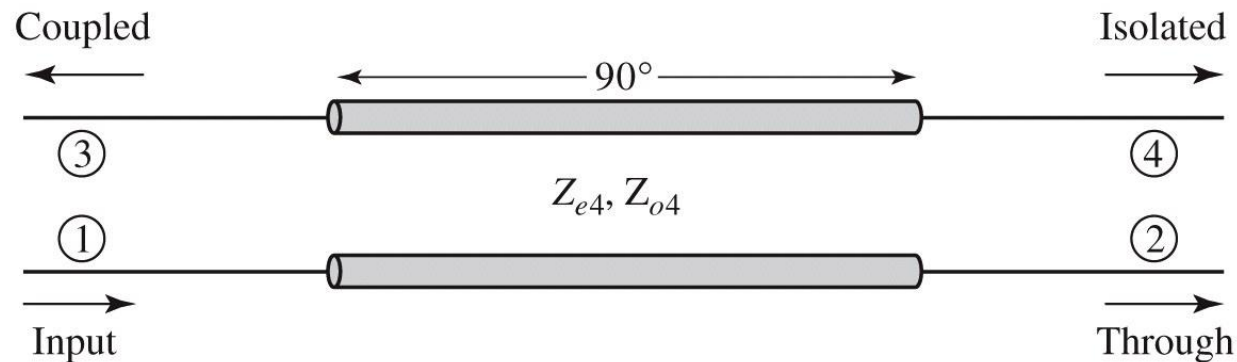

(b)


Circuit model

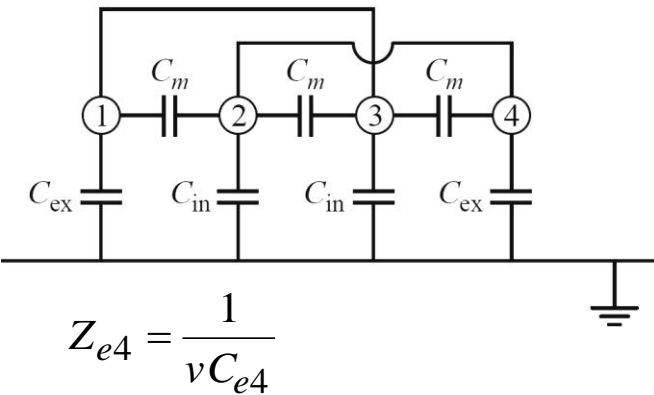

$$C_{in} = C_{ex} - \frac{C_{ex}C_m}{C_{ex} + C_m}$$

$$C_{e4} = C_{ex} + C_{in}$$

$$C_{o4} = C_{ex} + C_{in} + 6C_m$$

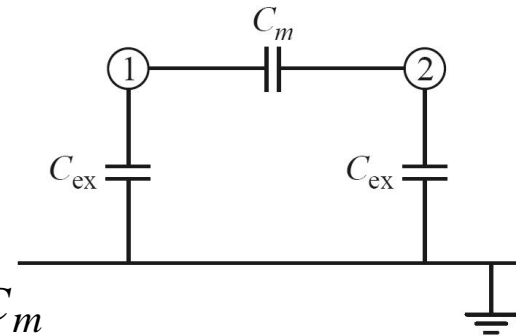

$$C_e = C_{ex}$$

$$C_o = C_{ex} + 2C_m$$

$$Z_{o4} = \frac{1}{vC_{o4}}$$

$$Z_0 = \sqrt{Z_{e4}Z_{o4}} = \sqrt{\frac{Z_{0e}Z_{0o}(Z_{0o} + Z_{0e})^2}{(3Z_{0o} + Z_{0e})(3Z_{0e} + Z_{0o})}}$$

$$C_{e4} = \frac{C_e(3C_e + C_o)}{C_e + C_o}$$

$$Z_{e4} = Z_{0e} \frac{Z_{0e} + Z_{0o}}{3Z_{0o} + Z_{0e}}$$

$$C = \frac{Z_{e4} - Z_{o4}}{Z_{e4} + Z_{o4}} = \frac{3(Z_{0e}^2 - Z_{0o}^2)}{3(Z_{0e}^2 + Z_{0o}^2) + 2Z_{0e}Z_{0o}}$$


$$C_{o4} = \frac{C_o(3C_o + C_e)}{C_e + C_o}$$

$$Z_{o4} = Z_{0o} \frac{Z_{0e} + Z_{0o}}{3Z_{0e} + Z_{0o}}$$

$$Z_{0e} = \frac{4C - 3 + \sqrt{9 - 8C^2}}{2C\sqrt{(1-C)/(1+C)}} Z_0$$

$$Z_{0o} = \frac{4C + 3 - \sqrt{9 - 8C^2}}{2C\sqrt{(1+C)/(1-C)}} Z_0$$


The Lange Coupler

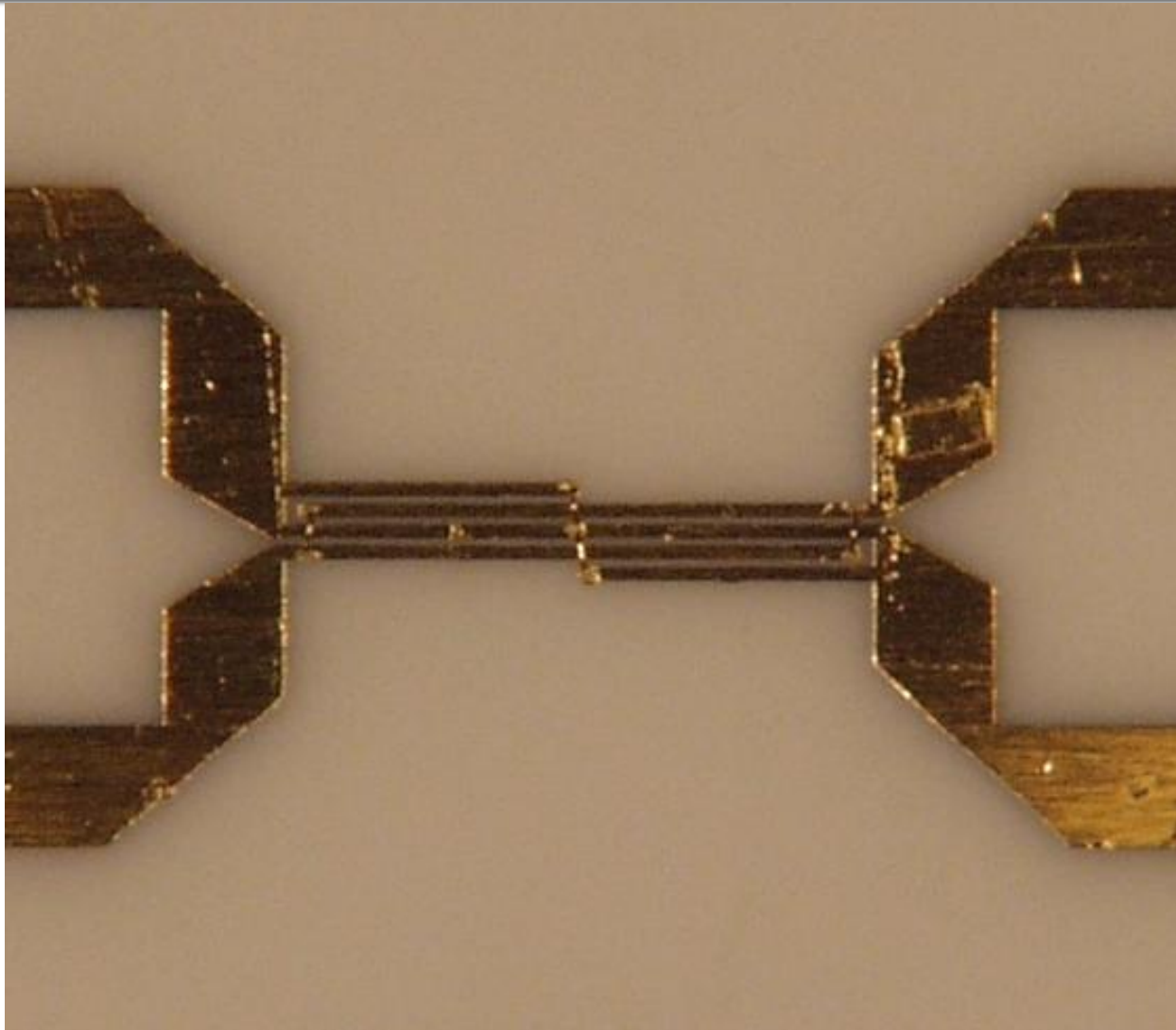

Directional Couplers

Laboratory no. 2

Directional Coupler

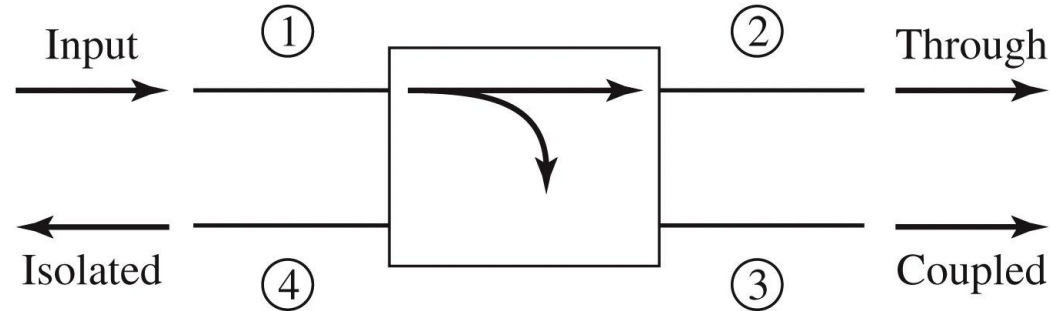

$$|S_{12}|^2 = \alpha^2 = 1 - \beta^2$$

$$|S_{13}|^2 = \beta^2$$

Cuplaj

$$C = 10 \log \frac{P_1}{P_3} = -20 \cdot \log(\beta) [\text{dB}]$$

Directivitate

$$D = 10 \log \frac{P_3}{P_4} = 20 \cdot \log \left(\frac{\beta}{|S_{14}|} \right) [\text{dB}]$$

Izolare

$$I = 10 \log \frac{P_1}{P_4} = -20 \cdot \log |S_{14}| [\text{dB}]$$

$$I = D + C, \text{ dB}$$

Figure 7.4
© John Wiley & Sons, Inc. All rights reserved.

The quadrature (90°) hybrid

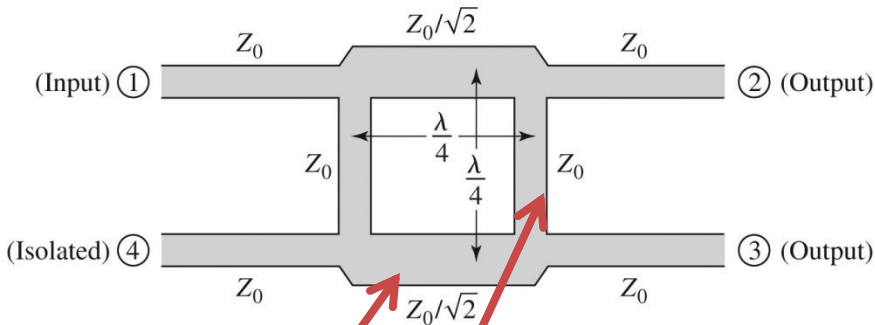


Figure 7.21
© John Wiley & Sons, Inc. All rights reserved.

$$y_2^2 = 1 + y_1^2$$

$$|\beta| = \frac{\sqrt{y_2^2 - 1}}{y_2}$$

$$C[\text{dB}] = -20 \cdot \log_{10} \frac{\sqrt{y_2^2 - 1}}{y_2}$$



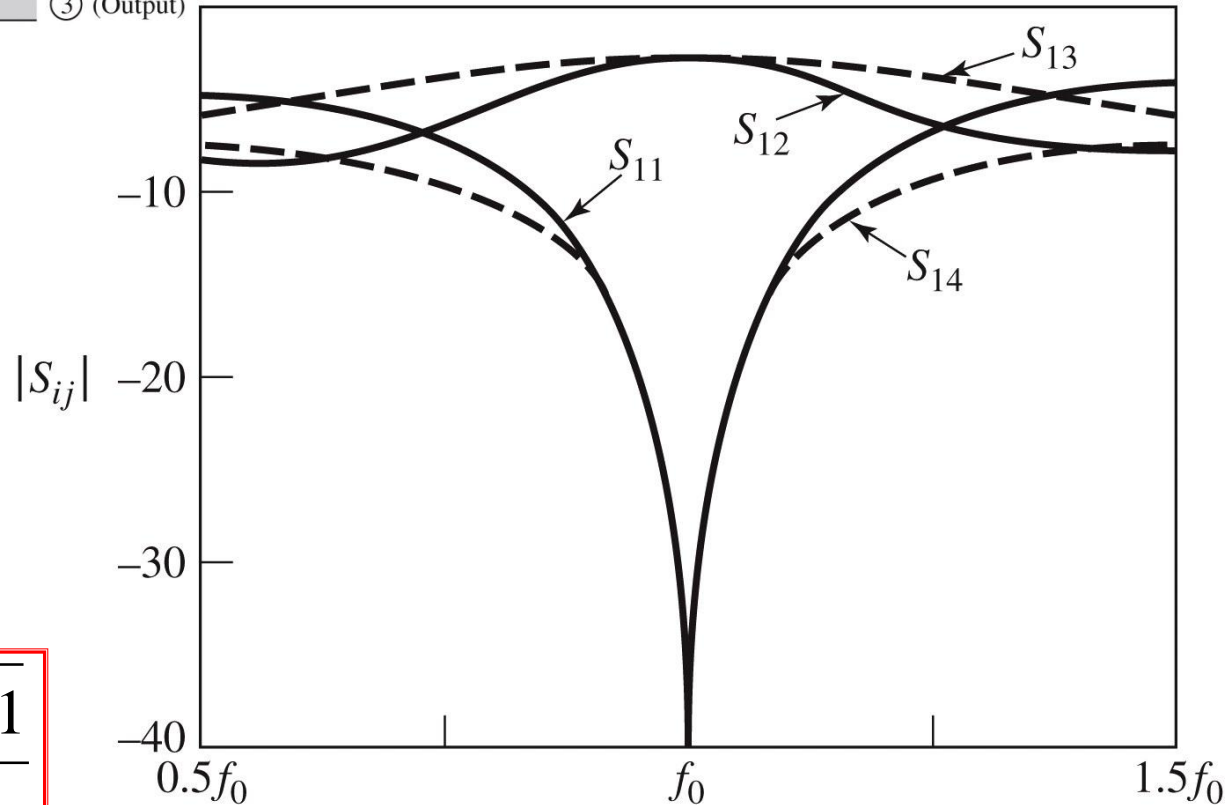


Figure 7.25
© John Wiley & Sons, Inc. All rights reserved.

Quadrature coupler

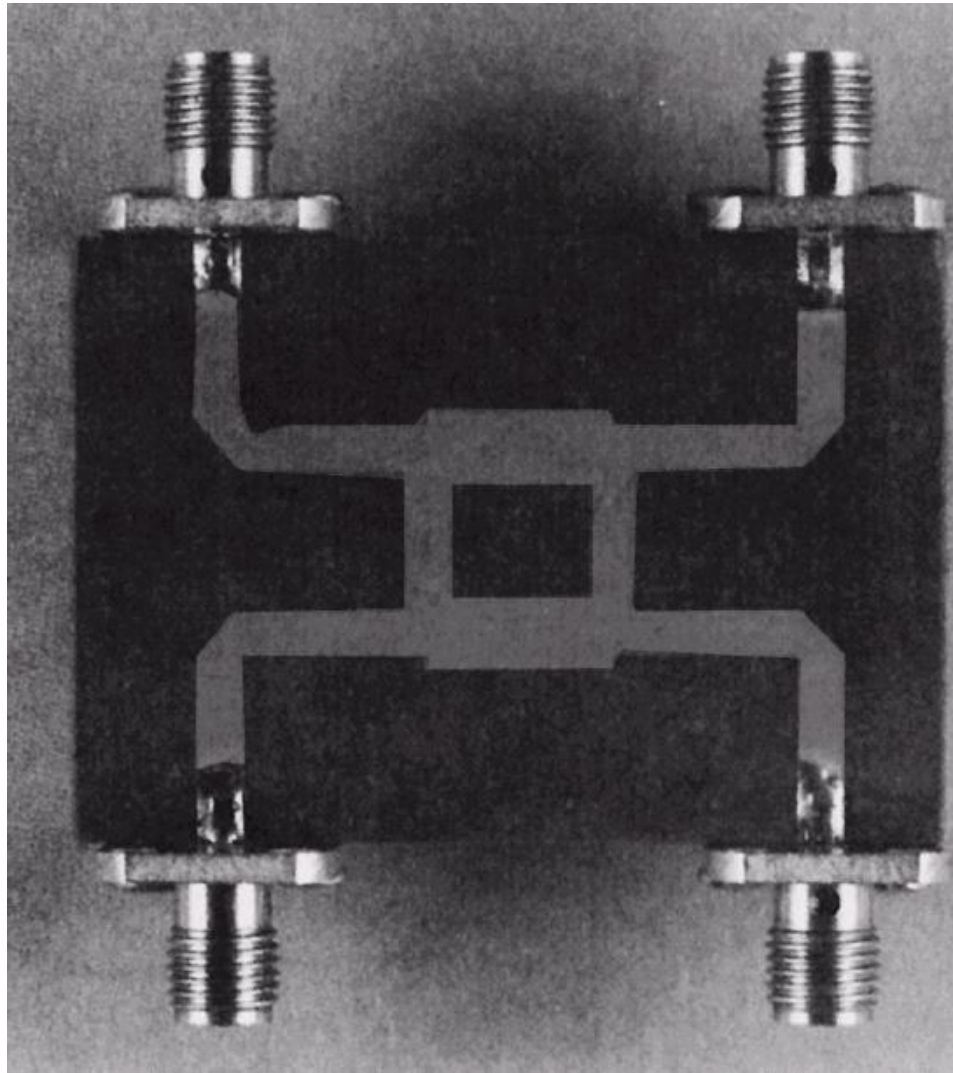

The 180° ring hybrid (rat-race)

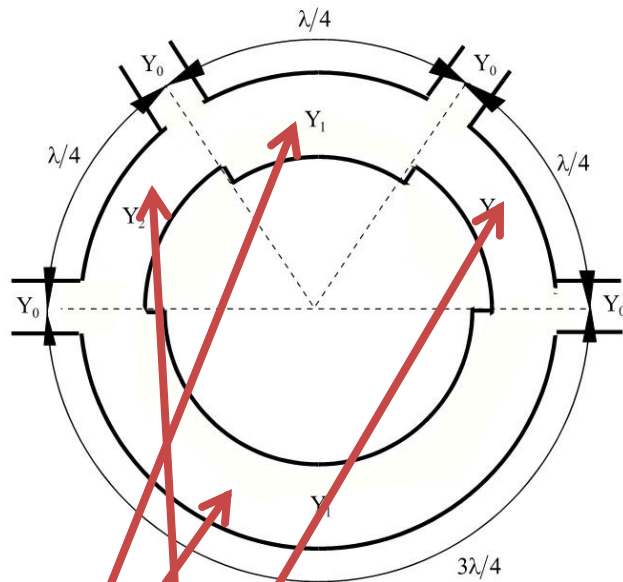

$$y_1^2 + y_2^2 = 1$$

$$|\beta| = y_1$$

$$C \text{ [dB]} = -20 \cdot \log_{10}(y_1)$$

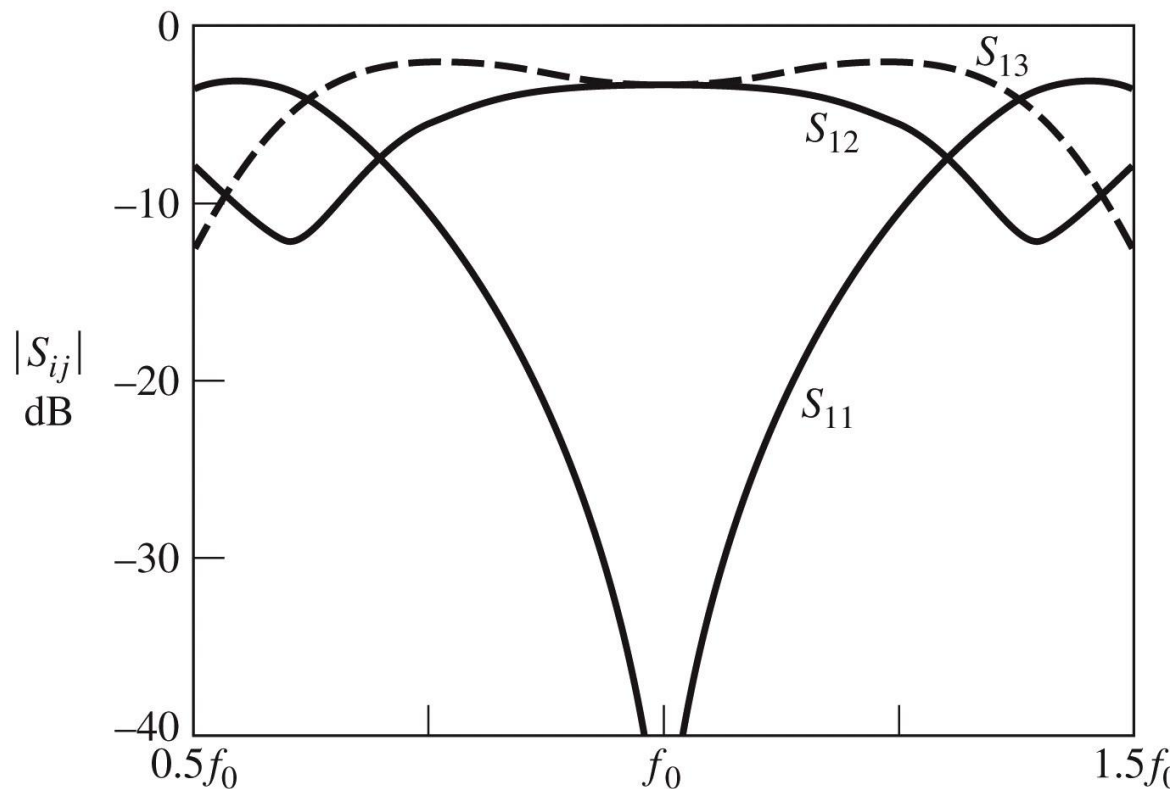


Figure 7.46
© John Wiley & Sons, Inc. All rights reserved.

Ring coupler


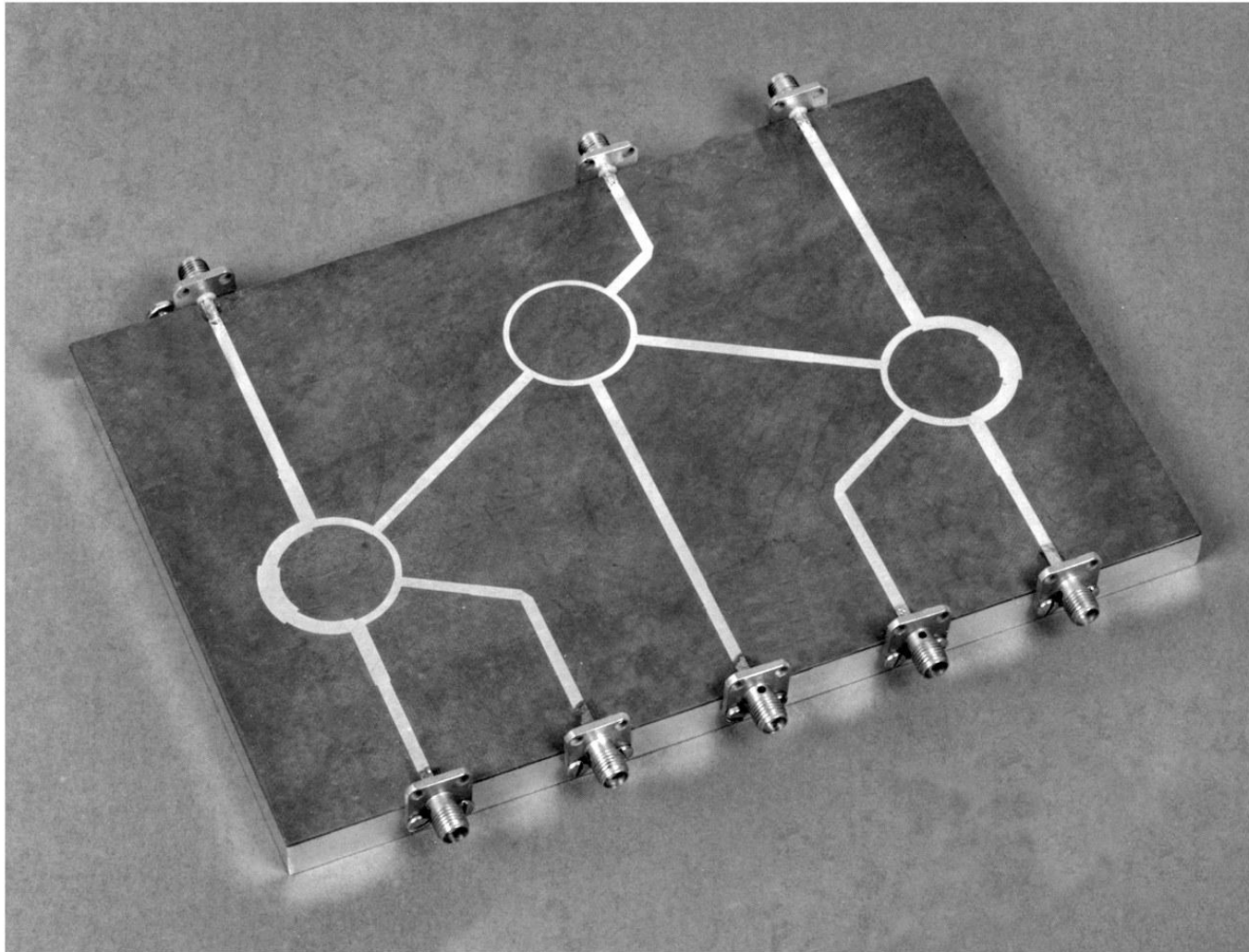


Figure 7.43
Courtesy of M. D. Abouzahra, MIT Lincoln Laboratory, Lexington, Mass.

Coupled Line Coupler

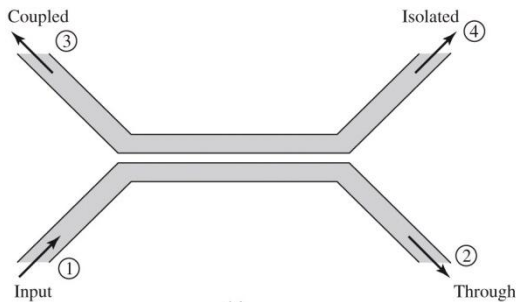

Coupling, Directivity (dB)

$$Z_{ce}Z_{co} = Z_0^2$$

$$|\beta| = \frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}}$$

$$C \text{ [dB]} = -20 \cdot \log_{10} \left(\frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}} \right)$$


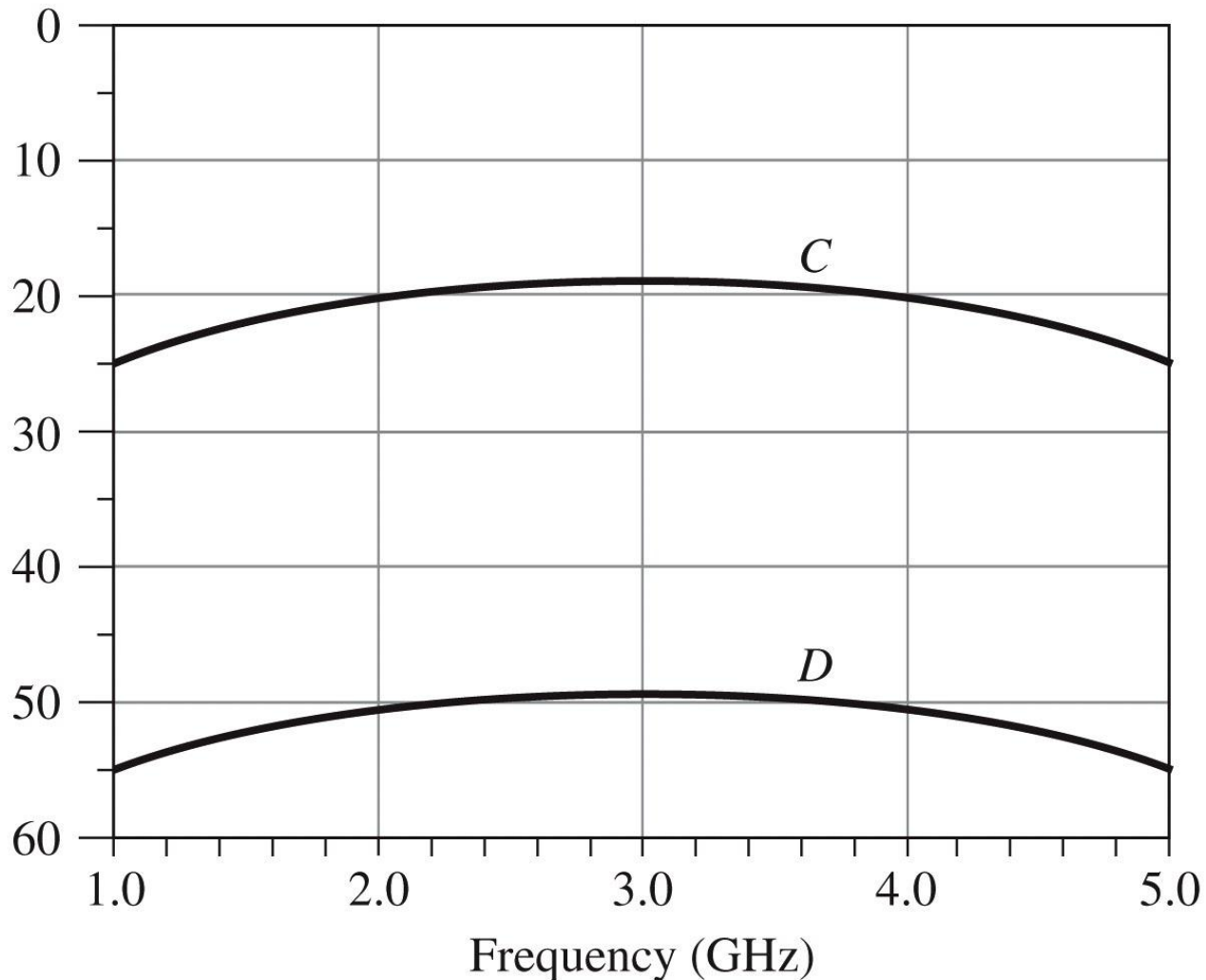


Figure 7.34

Coupled line coupler

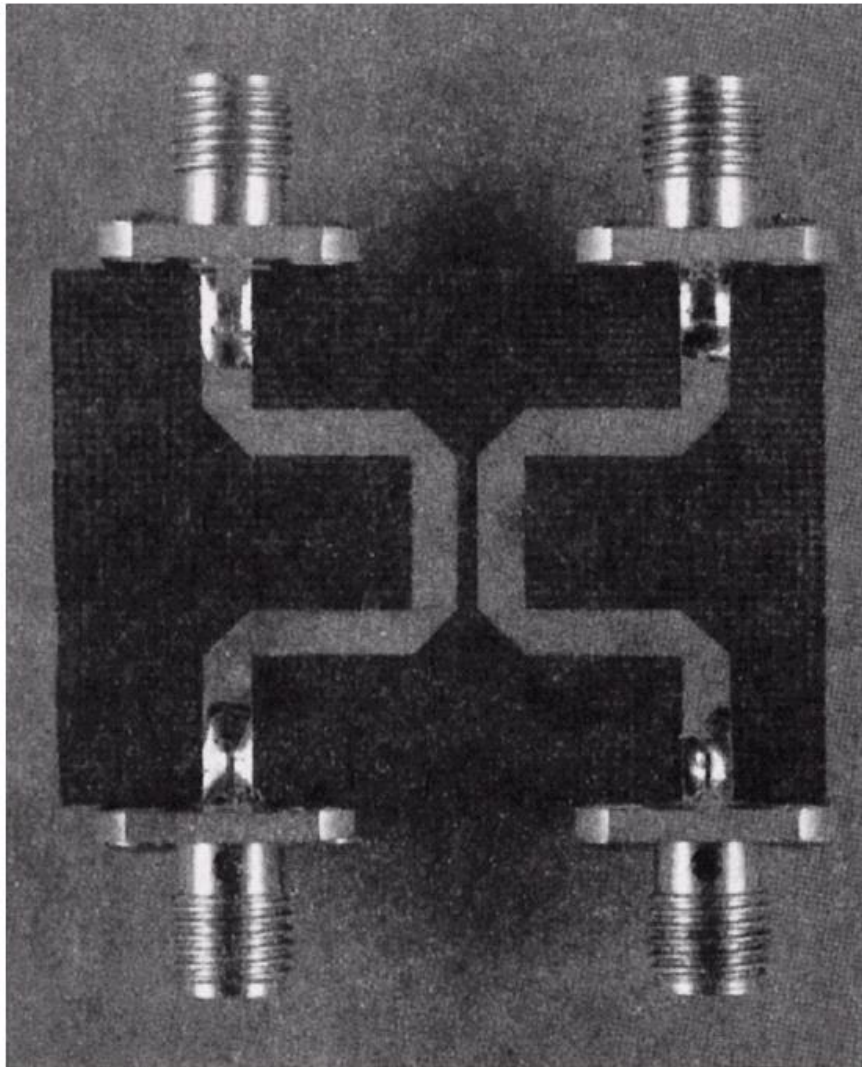

Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.etti.tuiasi.ro>
- rdamian@etti.tuiasi.ro