

Lecture 6

2023/2024

# Microwave Devices and Circuits for Radiocommunications

# 2023/2024

- 2C/1L, **MDCR**
- Attendance at minimum 7 sessions (course or laboratory)
- Lectures- **associate professor Radu Damian**
  - Tuesday 16-18, ~~Online~~, P8
  - E – 50% final grade
  - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
    - first test L1: 20-27.02.2024 (t2 and t3 not announced, lecture)
    - 3att.=+0.5p
  - all materials/equipments authorized

# 2023/2024

- Laboratory – **associate professor Radu Damian**
  - Tuesday 08-12, 11.13 / (08:10)
  - L – 25% final grade
    - ADS, 4 sessions
    - Attendance + **personal results**
  - P – 25% final grade
    - ADS, 3 sessions (-1? 20.02.2024)
    - personal homework

# Materials

■ <http://rf-opto.etti.tuiasi.ro>

The screenshot shows a web browser window with the URL [http://rf-opto.etti.tuiasi.ro/microwave\\_cd.php?chg\\_lang=0](http://rf-opto.etti.tuiasi.ro/microwave_cd.php?chg_lang=0). The page features a dark blue navigation bar with links for Main, Courses, Master, Staff, Research, Students, and Admin. Below this is a secondary navigation bar with links for Microwave CD, Optical Communications, Optoelectronics, Internet, Antennas, Practica, Networks, and Educational software. The main content area is titled "Microwave Devices and Circuits for Radiocommunications (English)" and includes the following information:

- Course: MDCR (2017-2018)**
- Course Coordinator:** Assoc.P. Dr. Radu-Florin Damian
- Code:** EDOS412T
- Discipline Type:** DOS; Alternative, Specialty
- Credits:** 4
- Enrollment Year:** 4, Sem. 7

**Activities**

**Course:** Instructor: Assoc.P. Dr. Radu-Florin Damian, 2 Hours/Week, Specialization Section, Timetable:  
**Laboratory:** Instructor: Assoc.P. Dr. Radu-Florin Damian, 1 Hours/Week, Group, Timetable:

**Evaluation**

Type: Examen

**A:** 50%, (Test/Colloquium)  
**B:** 25%, (Seminary/Laboratory/Project Activity)  
**D:** 25%, (Homework/Specialty papers)

**Grades**

[Aggregate Results](#)

**Attendance**

[Course](#)  
[Laboratory](#)

**Lists**

[Bonus-uri acumulate \(final\)](#)  
[Studenti care nu pot intra in examen](#)

**Materials**

**Course Slides**

- [MDCR Lecture 1](#) (pdf, 5.43 MB, en, [↗](#))
- [MDCR Lecture 2](#) (pdf, 3.67 MB, en, [↗](#))
- [MDCR Lecture 3](#) (pdf, 4.76 MB, en, [↗](#))
- [MDCR Lecture 4](#) (pdf, 5.58 MB, en, [↗](#))

On the right side of the screenshot, there is a banner for "RF-OPTO" with the ETTI logo and the University of Technical Sciences (UTS) logo. The banner includes a language selection menu with "English" (highlighted with a red circle) and "Romana". Below the banner is another navigation bar with links for Main, Courses, Master, Staff, Research, Grades, Student List, Exams, and Photos. The page also features a section for "Online Exams" with the text: "In order to participate at online exams you must get ready following..."



# Site



## Microwave and Optoelectronics Laboratory



We are enlisted in the Telecommunications Department of the Electronics, Telecommunication and Information Technology Faculty (ETTI) from the "Gh. Asachi" Technical University (TUIASI) in Iasi, Romania

We currently cover inside ETTI the fields related to:

- Microwave Circuits and Devices
- Optoelectronics
- Information Technology

### Courses

Nr.	Course	Shortcut	Code	Type	Semester	Credits	Weekly	Examination	Link
1	Microwave Devices and Circuits for Radiocommunications	DCMR	DOS412T	DOS	7	4	0P,1L,0S,2C	Exam	<a href="#">details</a>
2	Monolithic Microwave Integrated Circuits	CIMM	RD.IA.207	DOMS	11	6	1.5L,0S,2C,0P	Exam	<a href="#">details</a>
3	Advanced Techniques in the Design of the Radio-communications Systems	TAPSR	RD.IA.103	DIMS	9	6	1.5P,0L,0S,2C	Exam	<a href="#">details</a>
4	Optical Communications	CO	DOS409T	DOS	7	5	0P,1L,0S,3C	Colloquium	<a href="#">details</a>
5	Optical Communications	OC	EDOS409T	DOS	7	5	0P,1L,0S,3C	Exam	<a href="#">details</a>
6	Satellite Communications	CS	RC.IA.104	DIMS	9	6	0L,0S,2C,1.5P	Exam	<a href="#">details</a>
7	Applied Informatics 1	IA1	DOF135	DOF	1	4	0P,1L,0S,2C	Verification	<a href="#">details</a>
8	Applied Informatics 1	AI1	EDOF135	DOF	1	4	0P,1L,0S,2C	Verification	<a href="#">details</a>
9	Databases, Web Programming and Interfacing	DWPI	ITT.IA.601	DIS	11	5	1P,1L,0.25S,1C	Verification	<a href="#">details</a>
10	Web Applications Design	PAW	RC.IA.108	DIMS	10	5	1L,0S,1.5C,1P	Exam	<a href="#">details</a>
11	Optoelectronics	OPTO	DID405M	DID	8	4	0P,1L,0S,2C	Colloquium	<a href="#">details</a>
12	Microwave Devices and Circuits for Radiocommunications (English)	MDCR	EDOS412T	DOS	8	4	0P,1L,0S,2C	Exam	<a href="#">details</a>



# Site

- New online exams
  - Supplemental points for lectures 3, 4, 5

**Disciplina: MDCR (Microwave Devices and Circuits for Radiocommunications (Engleza))**

**Pas 3**

Nr.	Titlu	Start	Stop	Text	Subiecte
1	Profile photos	05/03/2024; 08:00	01/06/2024; 08:00	Online "exam" created f ...	<a href="#">fotografii_en.pdf</a>
2	Laboratory 2	19/03/2024; 08:00	10/04/2024; 18:00	Individual subjects for ...	<a href="#">Subjects_lab2_2024.pdf</a>
3	Lecture 5 Network Analysis - supplemental points	19/03/2024; 14:00	10/04/2024; 11:00	Supplemental points for ...	<a href="#">Supliment_c5_2024.pdf</a>
4	Lecture 3 Impedance Matching - supplemental points	19/03/2024; 08:00	03/04/2024; 11:00	Supplemental points for ...	<a href="#">Supliment_c3_2024.pdf</a>
5	Lecture 4 Impedance Transformers - supplemental points	19/03/2024; 08:00	03/04/2024; 11:00	Supplemental points for ...	<a href="#">Supliment_c4_2024.pdf</a>
6	Laboratory 1	05/03/2024; 08:00	27/03/2024; 14:00	Individual subjects for ...	<a href="#">Subjects_lab1_2024.pdf</a>

# Materials

- RF-OPTO
  - <http://rf-opto.etti.tuiasi.ro>
- **David Pozar, “Microwave Engineering”,**  
Wiley; 4th edition , 2011
  - 1 exam problem ← Pozar
- Photos
  - sent by email/**online exam > Week4-Week6**
  - used at lectures/laboratory

# Online – Registration no.

- access to **online exams** requires the **password** received by email

The password is communicated during the lectures. It is necessary to

**Password**


**Registration no.**

**Name of the student**

**Proposed email 1**

**Proposed email 2**

**Write the code below**

 **RF-OPTO** 

English | Romana |

[Main](#) [Courses](#) [Master](#) [Staff](#) [Research](#) [Students](#)

[Login](#) [Tutoring](#)

**Login**

Use the Registration no. and your email or the password received by email

**Registration no.**

**Email/Password**

**Write the code below**

# Password

## ■ received by email

Important message from RF-OPTO

Inbox x



Radu-Florin Damian

to me, POPESCU

Romanian > English Translate message



Laboratorul de Microunde si Optoelectronica  
Facultatea de Electronica, Telecomunicatii si Tehnologia Informatiei  
Universitatea Tehnica "Gh. Asachi" Iasi

In atentie: POPESCU GOPO ION

Parola pentru a accesa examenele pe server-ul rf-opto este  
Parola: [REDACTED]

Identificati-va pe [server](#), cu parola, cat mai rapid, pentru confirmare.

Memorati acest mesaj intr-un loc sigur, pentru utilizare ulterioara

Attention: POPESCU GOPO ION

The password to access the exams on the rf-opto server is  
Password: [REDACTED]

Login to the [server](#), with this password, as soon as possible, for confirmation.

Save this message in a safe place for later use

Reply

Reply all

Forward

Subject	Correspondents
Important message from RF-OPTO	POPESCU GOPO ION
Validation of MDCR exam from 02/05/2020	[REDACTED]
[REDACTED]	[REDACTED]

From Me <rdamian@etti.tuiasi.ro>  
Subject Important message from RF-OPTO  
To [REDACTED]  
Cc Me <rdamian@etti.tuiasi.ro>



Laboratorul de Microunde si Optoelectronica  
Facultatea de Electronica, Telecomunicatii si Tehnologia Informatiei  
Universitatea Tehnica "Gh. Asachi" Iasi

In atentie: POPESCU GOPO ION

Parola pentru a accesa examenele pe server-ul rf-opto este  
Parola: [REDACTED]

Identificati-va pe [server](#), cu parola, cat mai rapid, pentru confirmare.

Memorati acest mesaj intr-un loc sigur, pentru utilizare ulterioara

Attention: POPESCU GOPO ION

The password to access the exams on the rf-opto server is  
Password: [REDACTED]

Login to the [server](#), with this password, as soon as possible, for confirmation.

Save this message in a safe place for later use

# Online exam manual

- The online exam app used for:
  - ~~lectures (attendance)~~
  - laboratory
  - project
  - ~~examinations~~

## Materials

### Other data

[Manual examen on-line](#) (pdf, 2.65 MB, ro, 🇷🇴)

[Simulare Examen](#) (video) (mp4, 65.12 MB, ro, 🇷🇴)

## Microwave Devices and Circuits (Englis



# Examen online

- always against a **timetable**
  - long period (lecture attendance/laboratory results)
  - ~~short period (tests: 15min, exam: 2h)~~

<b>Announcement</b> 23:59 (10/05/2020)	<b>Support material</b> 00:05 (11/05/2020)	<b>Exam Topics</b> 00:07 (11/05/2020)	<b>Results</b> 00:10 (11/05/2020)	<b>End</b> 00:20 (15/05/2020)	<b>Confirmation</b> 00:20 (16/05/2020)	Next timeframe in: 05 m 43 s <a href="#">Refresh now</a>
---	---	--	--------------------------------------	----------------------------------	---	--

**Announcement**

This is a "fake" exam, introduced to familiarize you with the server interface and to perform the necessary actions during an exam: thesis scan, selfie, use email for co

**Server Time**

All exams are based on the server's time zone (it may be different from local time). For reference time on the server is now:

10/05/2020 23:59:16

# Online results submission

- many numerical values/files

Schema finala	Rezultate - castig	Rezultate - zgomot	Fisier justificare calcul (factor andrei)	Fisier zap (optional)	T1, fisier parametri S	T2, fisier parametri S	Z1	Z2	Z3	Z4	Z5	Z6	Z7	Ze1	Zo1	Ze2	Zo2	Ze3	Zo3	Ze4	Zo4	Ze5	Zo5	Ze6
86 - 5428 - 259 ...	86 - 5428 - 260 ...	86 - 5428 - 261 ...	86 - 5428 - 316 ...	-	86 - 5428 - 314 ...	86 - 5428 - 315 ...	148.33	155.88	202.12	164.35	180.91	30.29	185.19	79.9	37	68.89	45.14	61.83	45.05	57.97	46.02	61.85	45.05	68.8
86 - 5622 - 259 ...	86 - 5622 - 260 ...	86 - 5622 - 261 ...	86 - 5622 - 316 ...	86 - 5622 - 262 ...	86 - 5622 - 314 ...	86 - 5622 - 315 ...	26.97	153.5	34.64	35.79	55.56	26.212	10.693	0	0	0	0	0	0	0	0	0	0	0
86 - 5488 - 259 ...	86 - 5488 - 260 ...	86 - 5488 - 261 ...	86 - 5488 - 316 ...	86 - 5488 - 262 ...	86 - 5488 - 314 ...	86 - 5488 - 315 ...	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
86 - 5391 - 259 ...	86 - 5391 - 260 ...	86 - 5391 - 261 ...	86 - 5391 - 316 ...	-	-	-	50	50	50	50	50	50	50	70.14	40.39	61.85	44.59	55.7	45.2	54.89	45.38	58.65	45.8	70.0
86 - 5664 - 259 ...	86 - 5664 - 260 ...	86 - 5664 - 261 ...	86 - 5664 - 316 ...	-	86 - 5664 - 314 ...	86 - 5664 - 315 ...	168.02	150.5	178.28	133.75	92.12	121.67	144.48	94.36	36.19	70.77	42.56	65.69	42.05	55.17	42.29	65.59	42.05	70.7
86 - 5665 - 259 ...	86 - 5665 - 260 ...	86 - 5665 - 261 ...	86 - 5665 - 316 ...	-	86 - 5665 - 314 ...	86 - 5665 - 315 ...	162.2	80.8	209.2	140.85	135.1	183.7	167.6	94.58	36.15	78.16	39.77	65.57	45.05	65.57	45.05	78.16	39.77	94.5
86 - 5433 - 259 ...	86 - 5433 - 260 ...	86 - 5433 - 261 ...	86 - 5433 - 316 ...	-	86 - 5433 - 314 ...	86 - 5433 - 315 ...	165.138	106.228	226.157	130.134	72.71	180.177	164.616	101.36	36.11	77.22	42.49	68.02	45.62	60	45.42	68.02	45.62	77.2
86 - 5608 - 259 ...	86 - 5608 - 260 ...	86 - 5608 - 261 ...	86 - 5608 - 316 ...	-	86 - 5608 - 314 ...	86 - 5608 - 315 ...	150.84	152.5	30.94	32.37	54.36	19.837	29.85	64.14	40.145	54.32	46.32	53.8	46.7	53.8	46.7	54.32	46.32	54.9
86 - 5555 - 259 ...	86 - 5555 - 260 ...	86 - 5555 - 261 ...	86 - 5555 - 316 ...	-	86 - 5555 - 314 ...	86 - 5555 - 315 ...	168.001	150.288	178.399	133.115	92.491	121.257	144.126	97.05	36.16	71.13	43.09	65.45	42.12	55.66	42.18	65.45	42.12	71.1



# Online results submission

- many numerical values

	Z1	Z2	Z3	Z4	Z5	Z6	Z7
	148.33	155.88	202.12	164.35	180.91	30.29	185.19
	25.97	153.5	34.64	35.79	55.56	26.212	10.692
	0	0	0	0	0	0	0
	50	50	50	50	50	50	50




# Online results submission

Grade = Quality of the work +  
+ Quality of the submission

General theory


# Microwave Network Analysis

# Course Topics


- Transmission lines
  - Impedance matching and tuning
  - Directional couplers
  - Power dividers
  - Microwave amplifier design
  - Microwave filters
  - ~~Oscillators and mixers?~~
- 
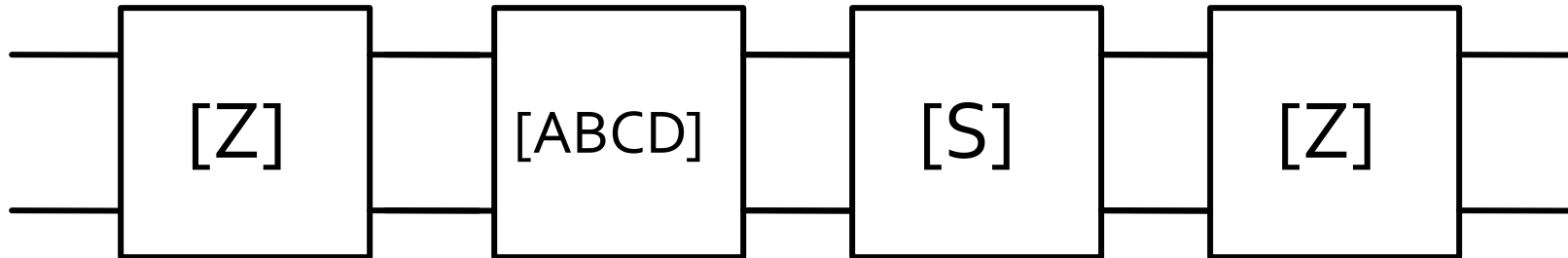
# Network Analysis

- We try to separate a complex circuit into individual blocks
- These are analyzed separately (decoupled from the rest of the circuit) and are characterized only by the port level signals (**black box**)
- Network-level analysis allows you to put together individual block results and get a total result for the entire circuit



# Impedance matrix – Z

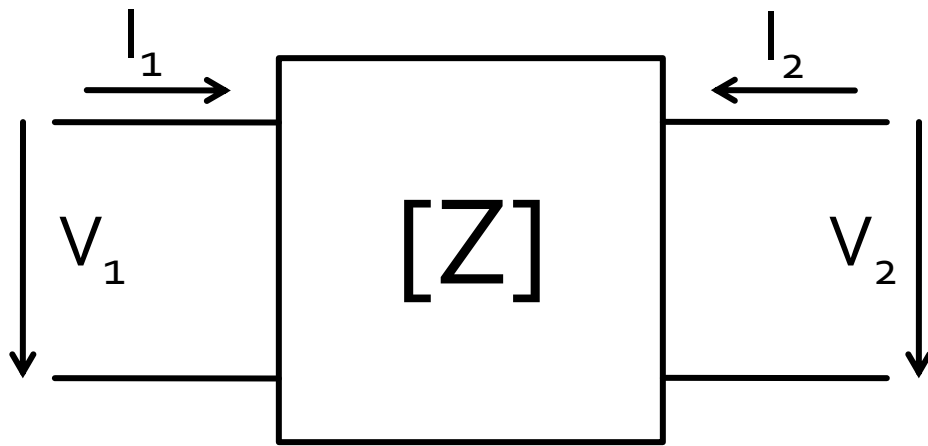

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_1 = Z_{11} \cdot I_1 + Z_{12} \cdot I_2$$


$$V_2 = Z_{21} \cdot I_1 + Z_{22} \cdot I_2$$

$$V_1 = Z_{11} \cdot I_1 \Big|_{I_2=0} \quad Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

- $Z_{11}$  – input impedance with open-circuited output

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \quad Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

# Admittance matrix – Y

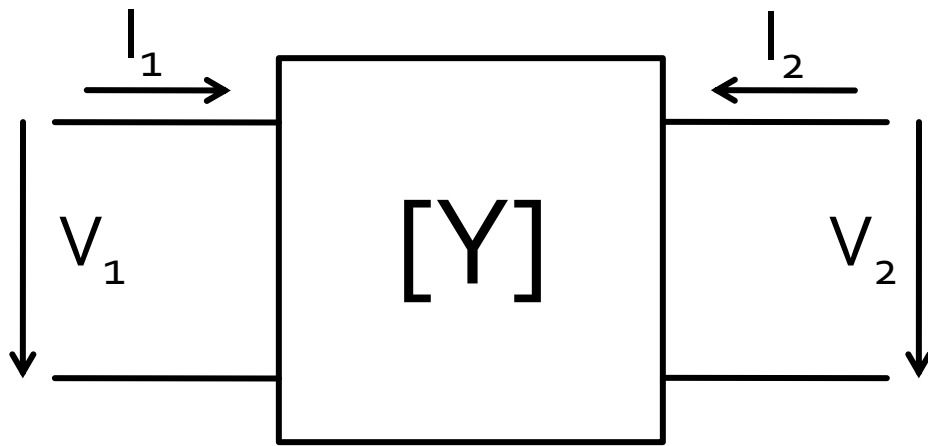

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = Y_{11} \cdot V_1 + Y_{12} \cdot V_2$$

$$I_2 = Y_{21} \cdot V_1 + Y_{22} \cdot V_2$$

$$I_1 = Y_{11} \cdot V_1 \Big|_{V_2=0} \quad Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

- $Y_{11}$  – input admittance with short-circuited output

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} \quad Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \quad Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

# Network Analysis


- Each matrix is best suited for a particular mode of port excitation (V, I)
  - matrix H in common emitter connection for TB:  $I_B, V_{CE}$
  - matrices provide the associated quantities depending on the “attack” ones
- Traditional notation of Z, Y, G, H parameters is in lowercase (z, y, g, h)
- In microwave analysis we prefer the notation in uppercase to avoid confusion with the **normalized parameters**

$$z = \frac{Z}{Z_0} \quad y = \frac{Y}{Y_0} = \frac{1/Z}{1/Z_0} = \frac{Z_0}{Z} = Z_0 \cdot Y$$

$$z_{11} = \frac{Z_{11}}{Z_0} \quad y_{11} = \frac{Y_{11}}{Y_0} = Z_0 \cdot Y_{11}$$



# ABCD (transmission) matrix

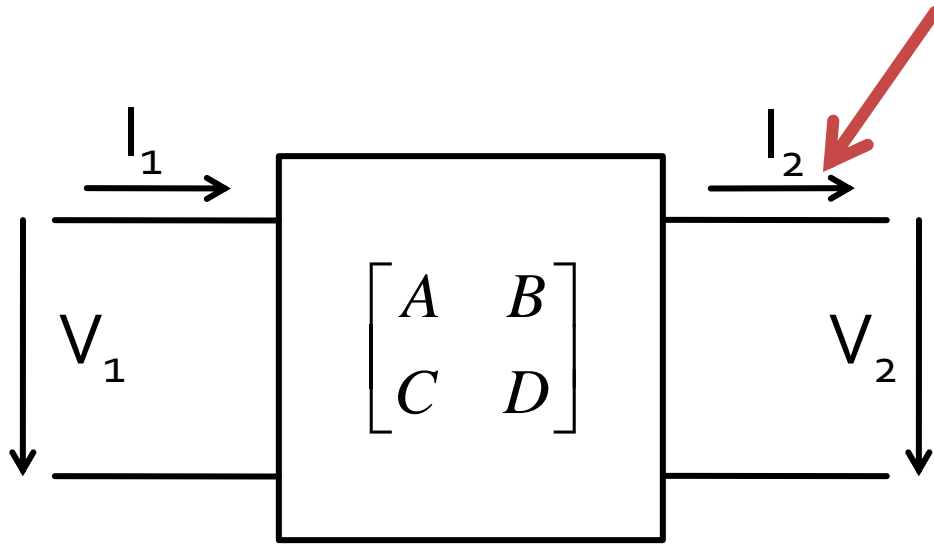

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \cdot \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$V_1 = A \cdot V_2 + B \cdot I_2$$

$$I_1 = C \cdot V_2 + D \cdot I_2$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \frac{1}{A \cdot D - B \cdot C} \cdot \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$


$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$D = \left. \frac{I_1}{I_2} \right|_{V_2=0}$$


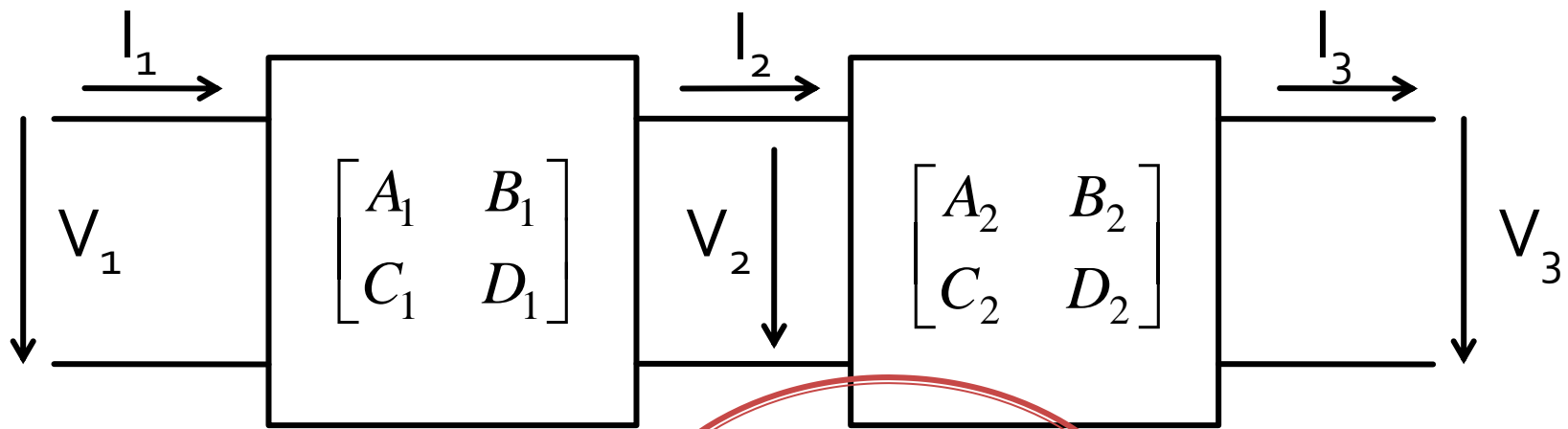
# ABCD (transmission) matrix

- This 2X2 matrix characterizes the “input”/“output” relation
- Allows easy chaining of multiple two-ports




$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \cdot \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \cdot \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \cdot \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

# ABCD (transmission) matrix

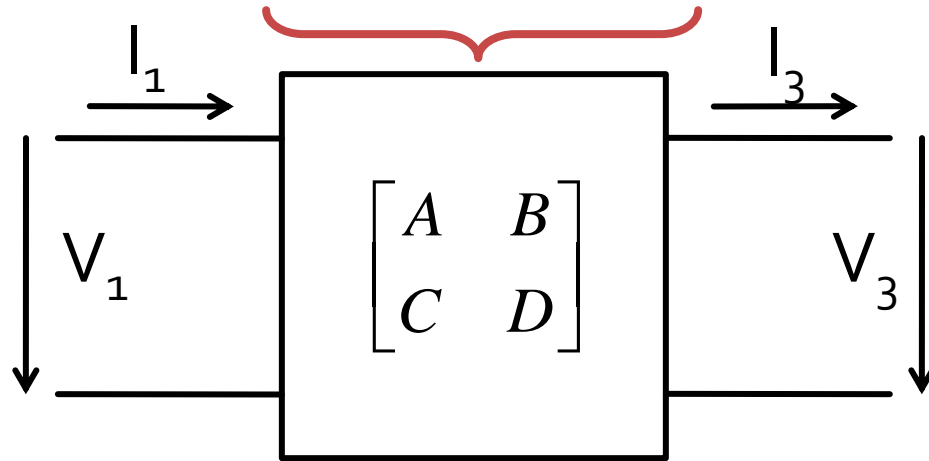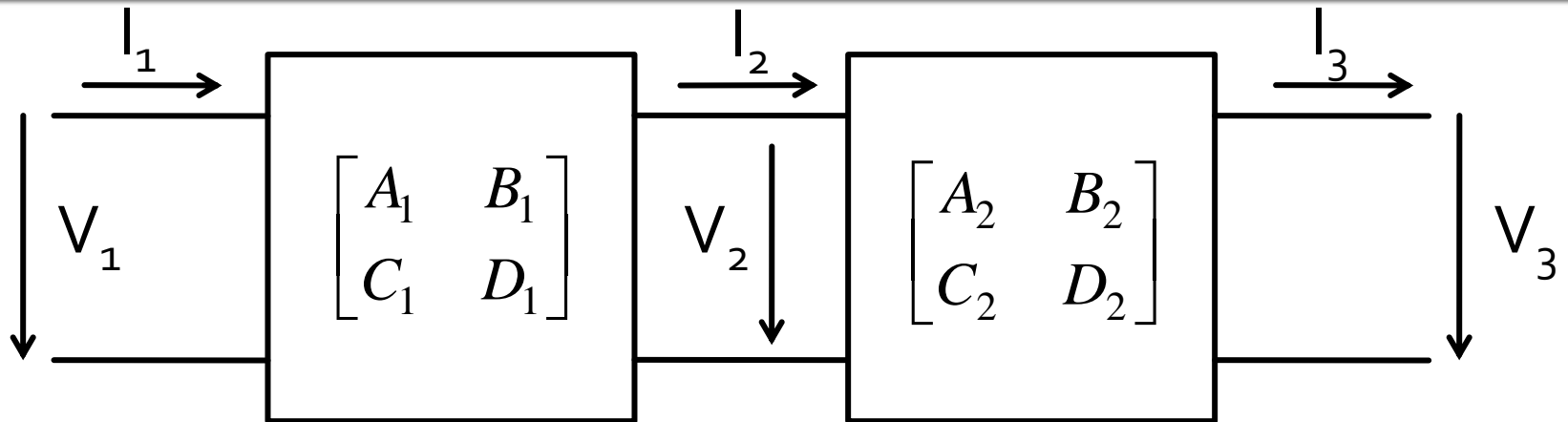

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \cdot \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

# Example for ABCD matrix

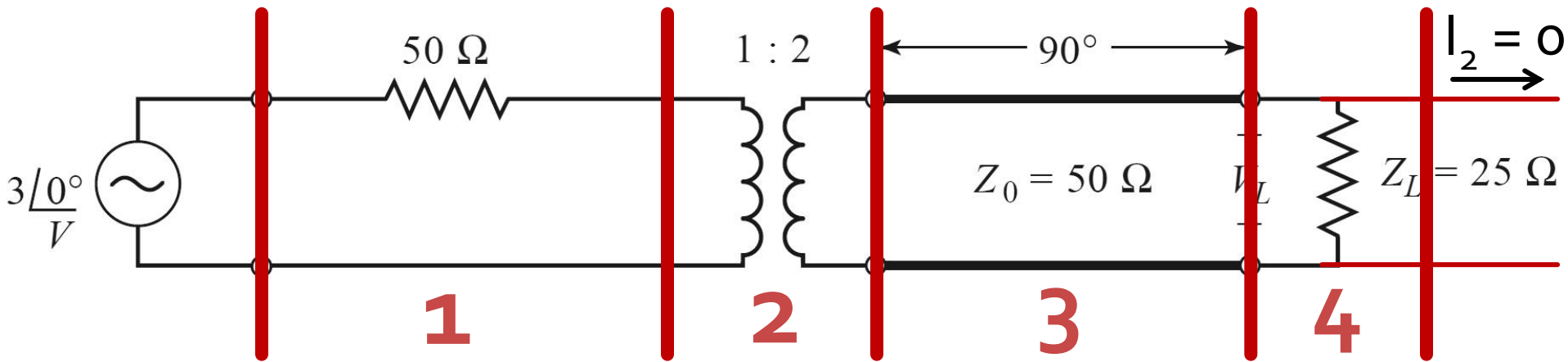

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 50 \\ 0 & 1 \end{bmatrix} \cdot \begin{bmatrix} \frac{1}{2} & 0 \\ 0 & 2 \end{bmatrix} \cdot \begin{bmatrix} 0 & 50 \cdot j \\ \frac{j}{50} & 0 \end{bmatrix} \cdot \begin{bmatrix} 1 & 0 \\ \frac{1}{25} & 1 \end{bmatrix} = \begin{bmatrix} 3 \cdot j & 25 \cdot j \\ \frac{j}{25} & 0 \end{bmatrix}$$

$$V_L = \frac{V}{A} = \frac{3\angle 0^\circ}{3 \cdot j} = 1\angle -90^\circ$$

(Somewhat!) Specific theory

# Microwave Network Analysis


# The lossless line

$$P_{avg} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot (1 - |\Gamma|^2)$$

- Average power flow is constant along the line
  - ( **no**  $P_{avg}(\mathbf{z})$  )
  - can be measured
- We can use the power to characterize the amplitude of a signal
  - a very “energetic” (basic physics) point of view
  - more power = “more” signal

# Scattering matrix – S

- Scattering parameters

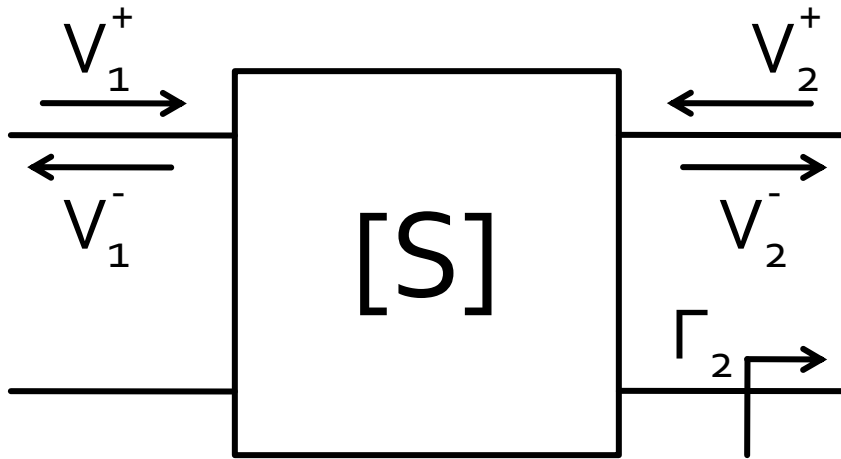


$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0}$$

- $V_2^+ = 0$  meaning: port 2 is terminated in matched load to avoid reflections towards the port

$$\Gamma_2 = 0 \rightarrow V_2^+ = 0$$

# Scattering matrix – S

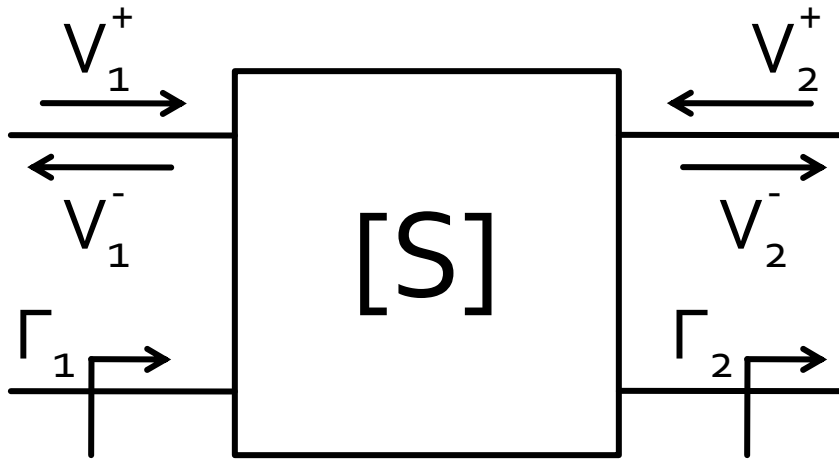

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} = \Gamma_1 \Big|_{\Gamma_2 = 0}$$
$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0} = T_{21} \Big|_{\Gamma_2 = 0}$$

- $S_{11}$  is the reflection coefficient seen looking into port **1** when port **2** is terminated in matched load
- $S_{21}$  is the transmission coefficient from port **1** (**second** index!) to port **2** (**first** index!) when port **2** is terminated in matched load



# Generalized Scattering Parameters

- We define the power wave amplitudes  $a$  and  $b$

$$a = \frac{V + Z_R \cdot I}{2 \cdot \sqrt{R_R}} \quad \text{the incident power wave} \quad Z_R = R_R + j \cdot X_R$$

$$b = \frac{V - Z_R^* \cdot I}{2 \cdot \sqrt{R_R}} \quad \text{the reflected power wave}$$

Any complex impedance,  
named reference impedance

- Total voltage and current in terms of the power wave amplitudes

$$V = \frac{Z_R^* \cdot a + Z_R \cdot b}{\sqrt{R_R}}$$

$$I = \frac{a - b}{\sqrt{R_R}}$$

# Power waves

- When the load is conjugately matched to the generator

$$Z_g = Z_L^* \quad P_{L_{\max}} = \frac{1}{2} \cdot |a|^2 = \frac{V_0^2}{8 \cdot R_L}$$

- Power reflection: L4

$$Z_L = Z_i^* \quad P_{L_{\max}} \equiv P_a \quad \Gamma = \frac{Z - Z_0^*}{Z + Z_0^*}$$


$$Z_L \neq Z_i^* \quad P_r = P_a \cdot |\Gamma|^2 \quad P_L = P_a - P_r = P_a - P_a \cdot |\Gamma|^2 = P_a \cdot (1 - |\Gamma|^2)$$

- Power reflection: L5

$$P_{L_{\max}} \equiv P_a = \frac{1}{2} \cdot |a|^2 \quad P_L = \frac{1}{2} \cdot |a|^2 - \frac{1}{2} \cdot |b|^2 \quad \Gamma_p = \frac{b}{a} = \frac{V - Z_R^* \cdot I}{V + Z_R \cdot I} = \frac{Z_L - Z_R^*}{Z_L + Z_R}$$

$$P_L = \frac{1}{2} \cdot |a|^2 - \frac{1}{2} \cdot |a|^2 \cdot |\Gamma_p|^2 \quad P_L = P_a \cdot (1 - |\Gamma_p|^2) \quad P_r = P_a \cdot |\Gamma_p|^2 = \frac{1}{2} \cdot |b|^2$$

# Scattering matrix – S

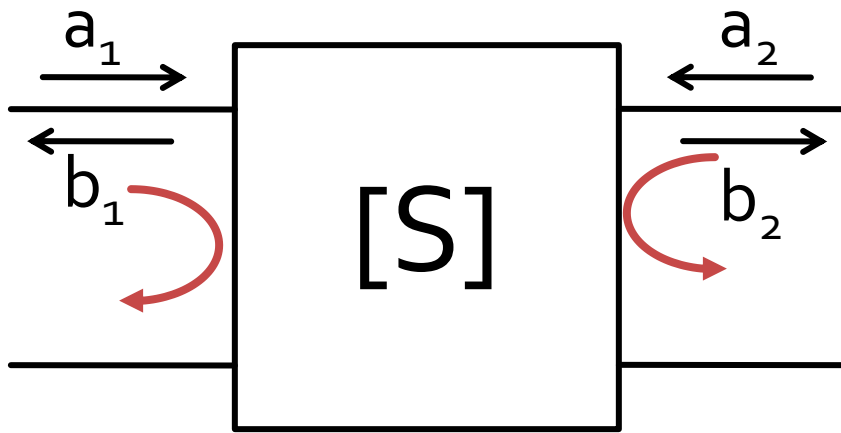


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

- $S_{11}$  and  $S_{22}$  are reflection coefficients at ports 1 and 2 when the other port is matched

# Scattering matrix – S

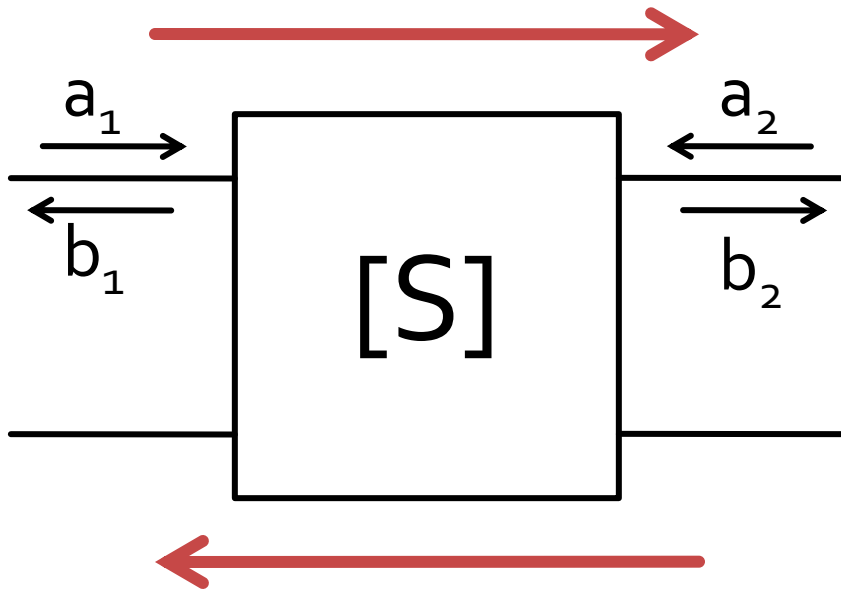


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$$

- $S_{21}$  si  $S_{12}$  are signal amplitude gain when the other port is matched

# Scattering matrix – S

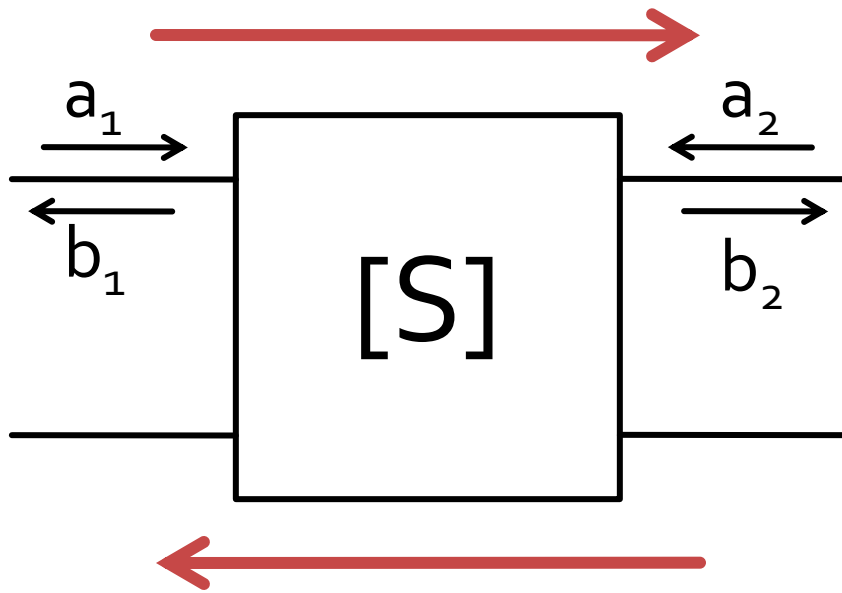

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- $a, b$ 
  - information about signal power **AND** signal phase
- $S_{ij}$ 
  - network effect (gain) over signal power **including** phase information

# Measuring S parameters - VNA

- Vector Network Analyzer


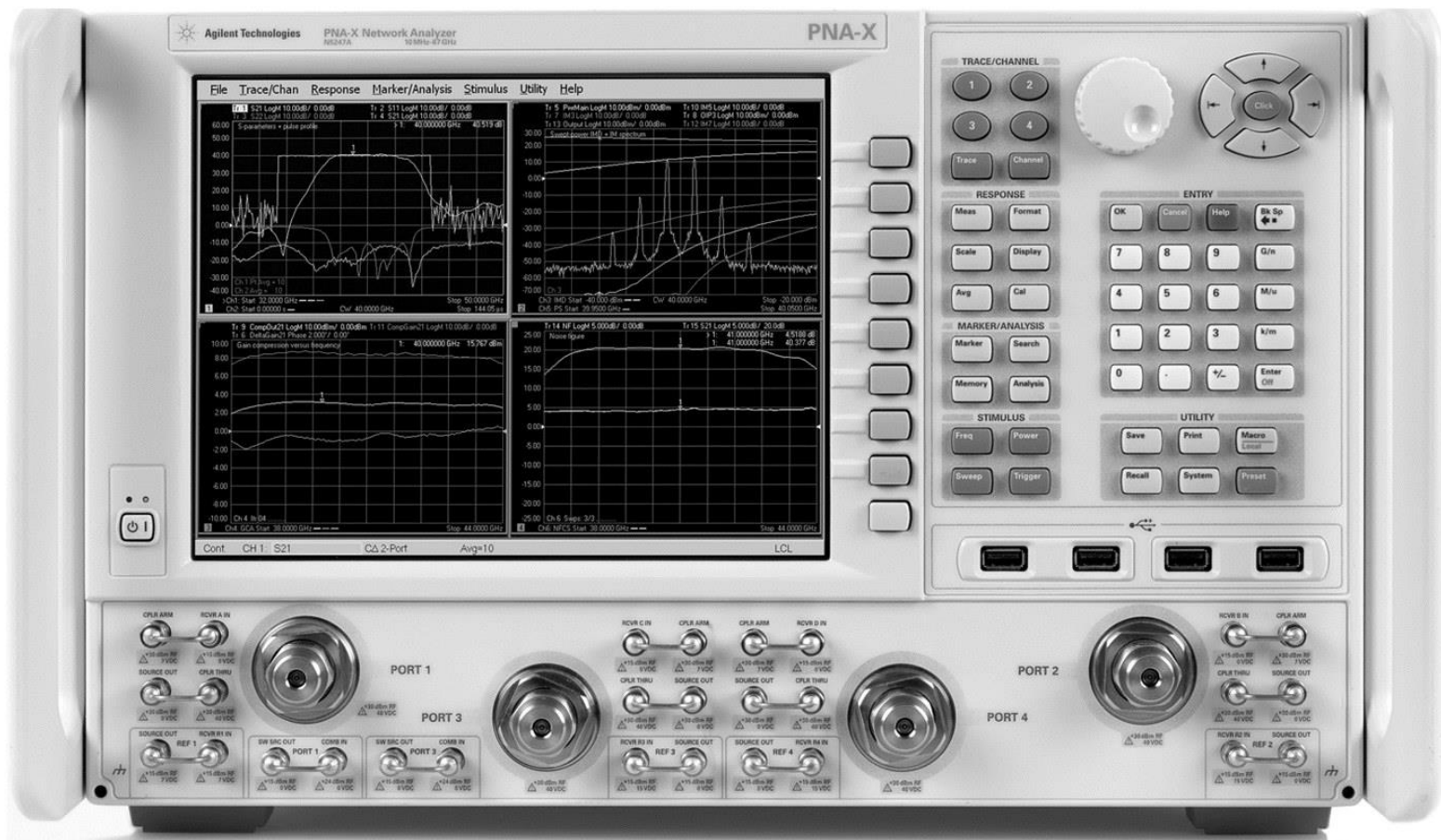


Figure 4.7  
Courtesy of Agilent Technologies

# Even/Odd Mode Analysis
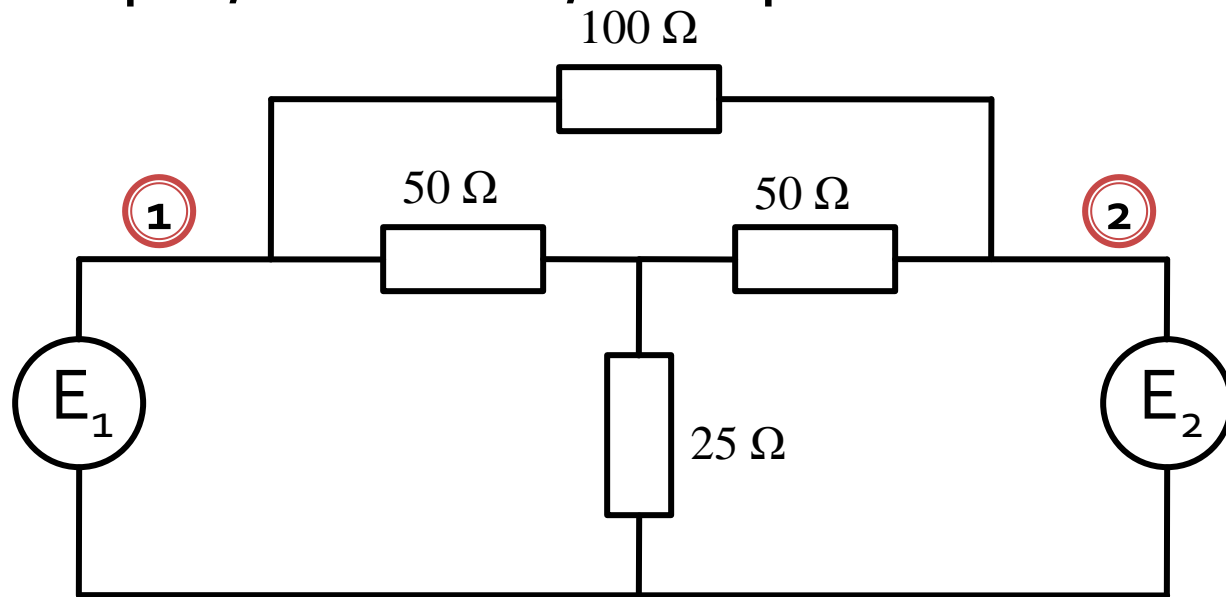
# Even/Odd Mode Analysis

- useful method, necessary even for multiple ports
- example, resistors, two port circuit






# Even/Odd Mode Analysis


- assume we want to compute  $Y_{11}$
- $E_2 = 0$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

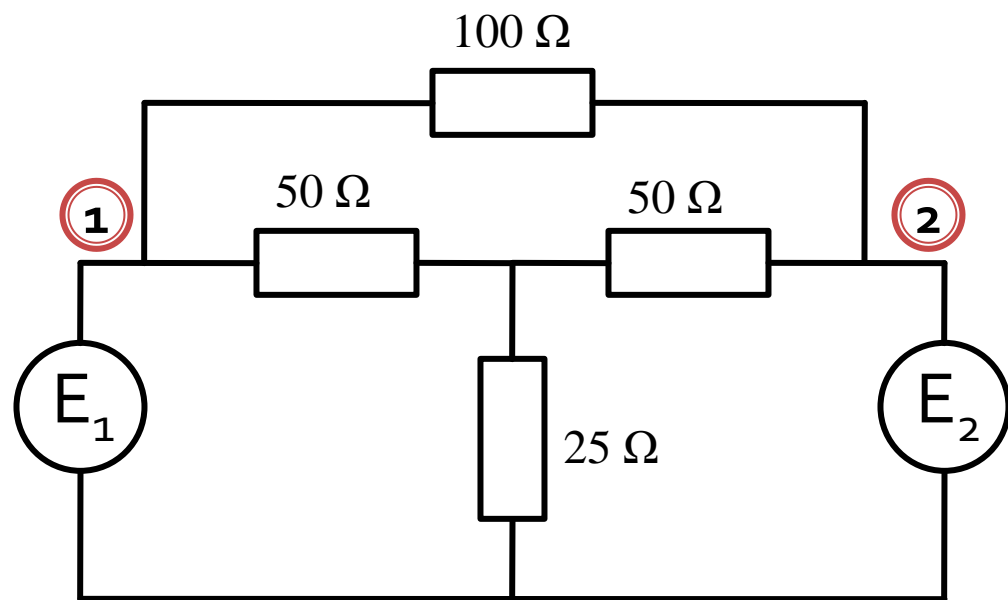

$$R_{ech} = 100\Omega \parallel (50\Omega + 25\Omega \parallel 50\Omega) =$$

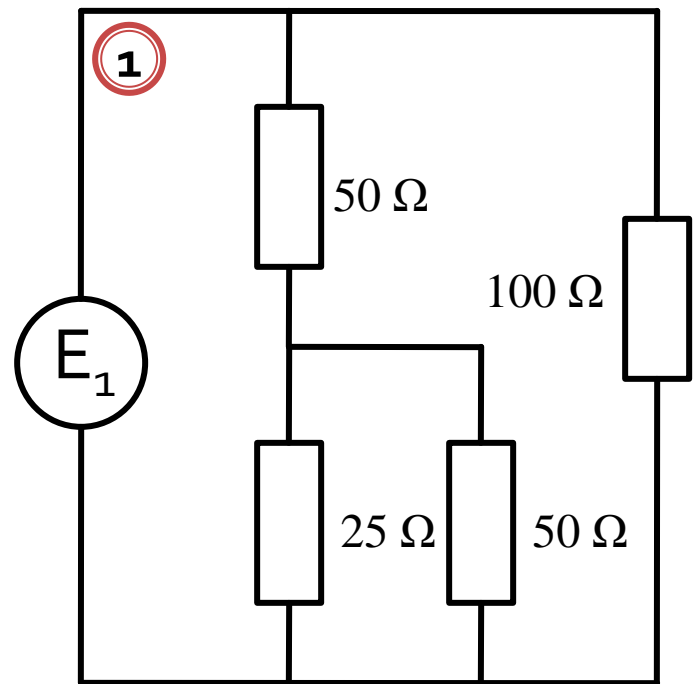
$$= 100\Omega \parallel (50\Omega + 16.67\Omega) = 100\Omega \parallel 66.67\Omega = 40\Omega$$



$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = 0.025S$$



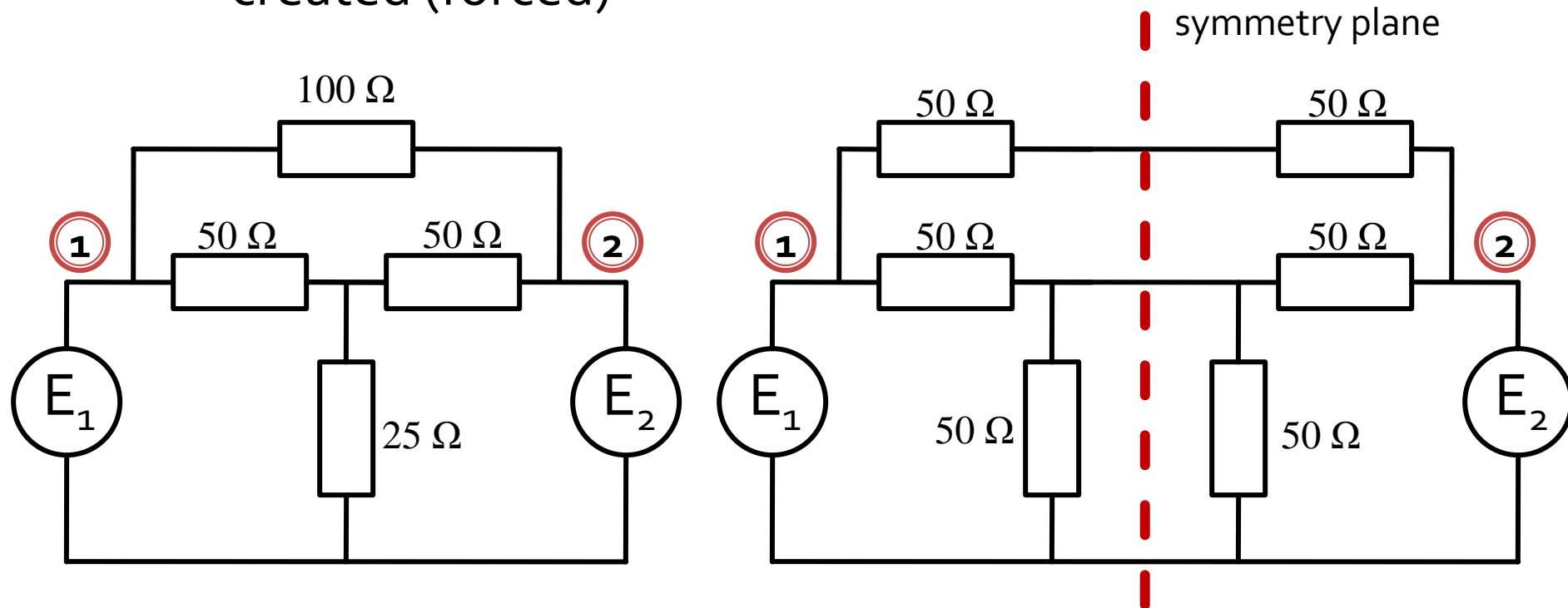
# Even/Odd Mode Analysis

- Even/Odd mode analysis benefit from the existence of symmetry planes in the circuit
  - existing or
  - created (forced)



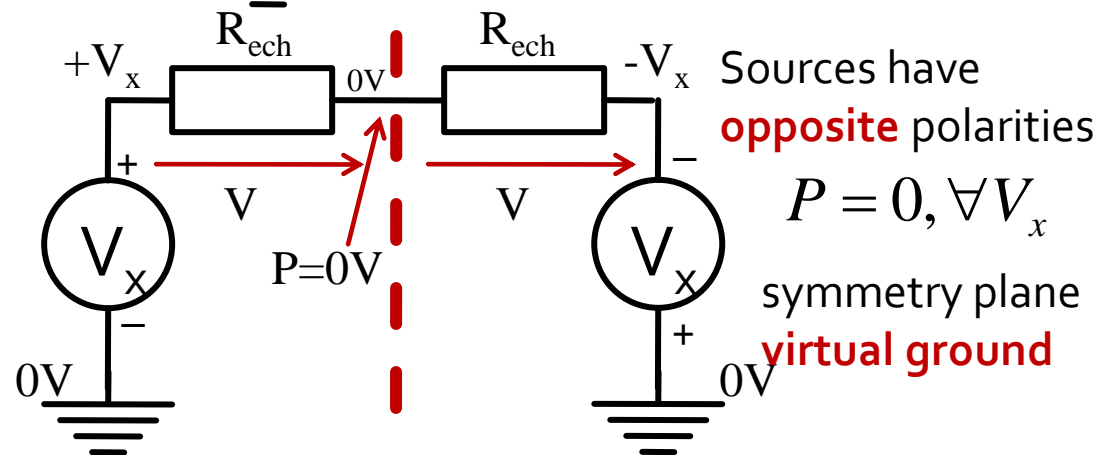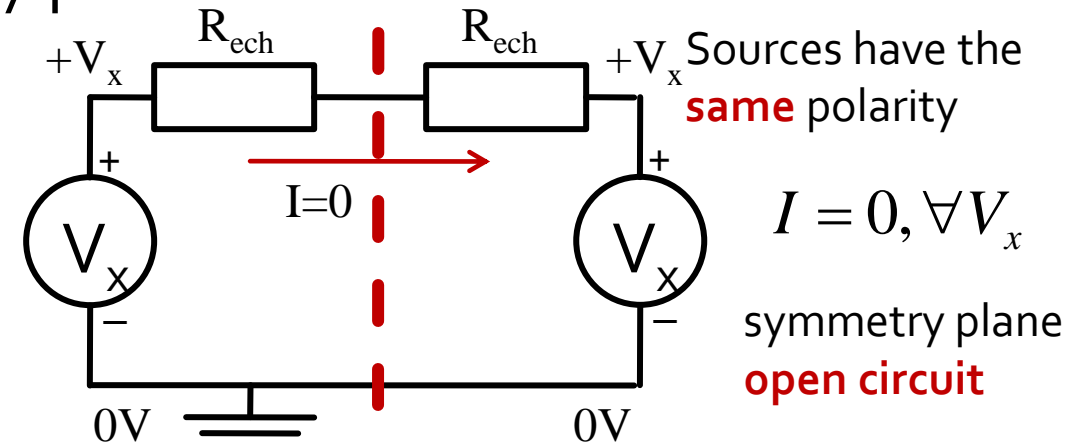
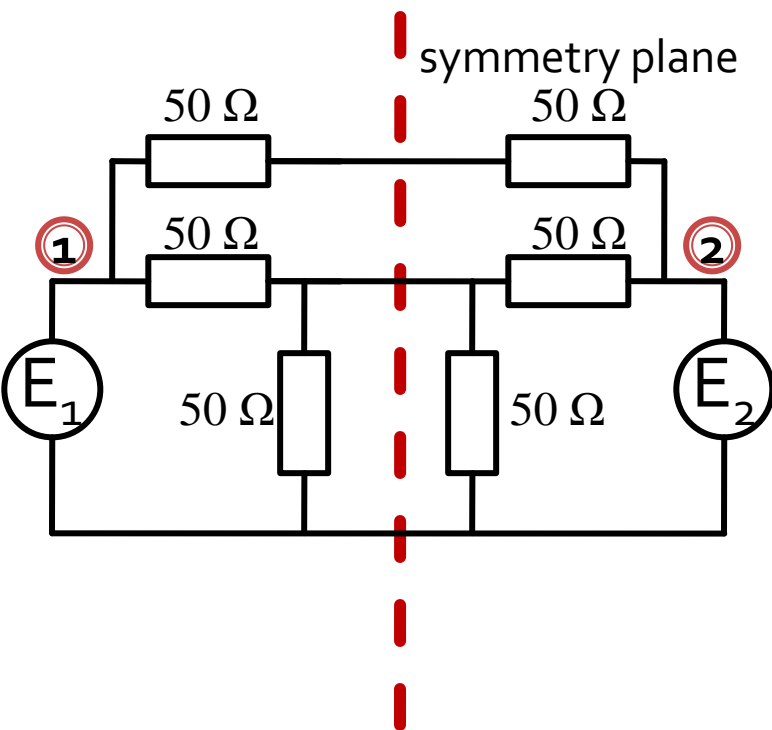
# Even/Odd Mode Analysis

- when exciting the ports with symmetric/anti-symmetric sources the symmetry planes are transformed into:
  - open circuit
  - virtual ground


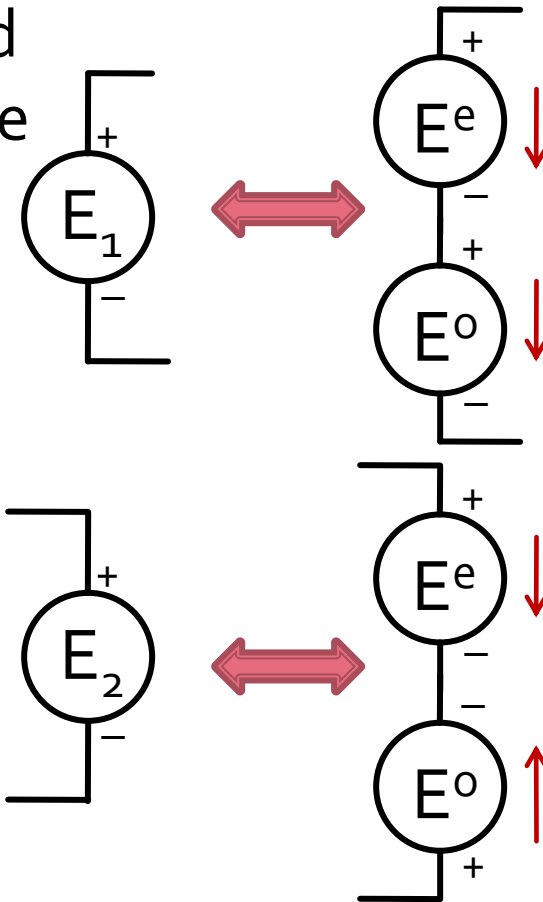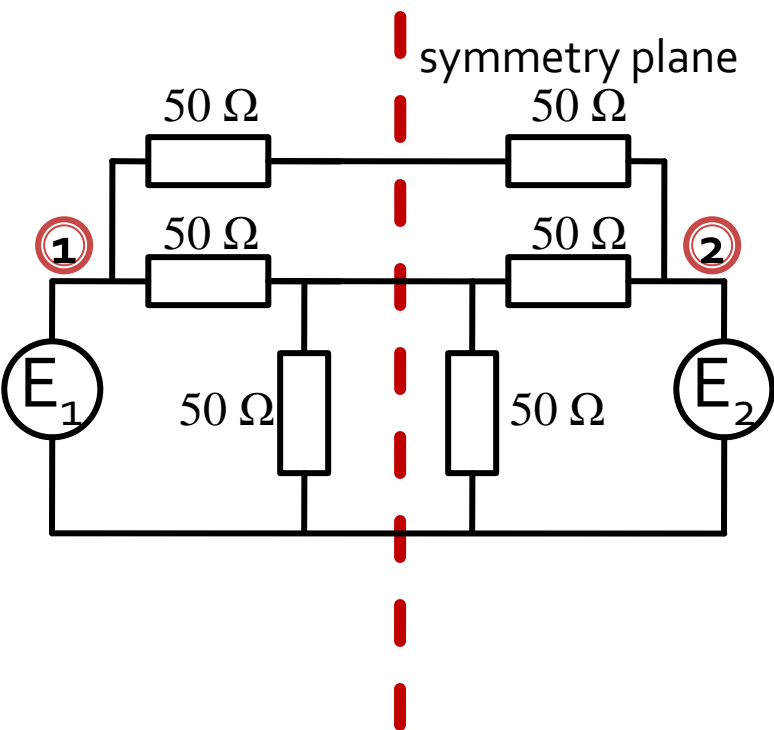
# Even/Odd Mode Analysis

- the combination of any two sources is equivalent for linear circuits with the superposition of:
  - a symmetric source and
  - a anti-symmetric source



$$E_1 = E^e + E^o$$

$$E_2 = E^e - E^o$$

$$E^e = \frac{E_1 + E_2}{2}$$

$$E^o = \frac{E_1 - E_2}{2}$$

# Even/Odd Mode Analysis

- In linear circuits the **superposition principle** is always true
  - the response caused by two or more stimuli is the sum of the responses that would have been caused by each stimulus individually

$$\begin{aligned} \text{Response ( Source1 + Source2 )} &= \\ &= \text{Response (Source1 )} + \text{Response ( Source2 )} \end{aligned}$$


$$\text{Response ( ODD + EVEN )} = \text{Response ( ODD )} + \text{Response ( EVEN )}$$



We can benefit from existing symmetries !!


# Even/Odd Mode Analysis

## ■ example

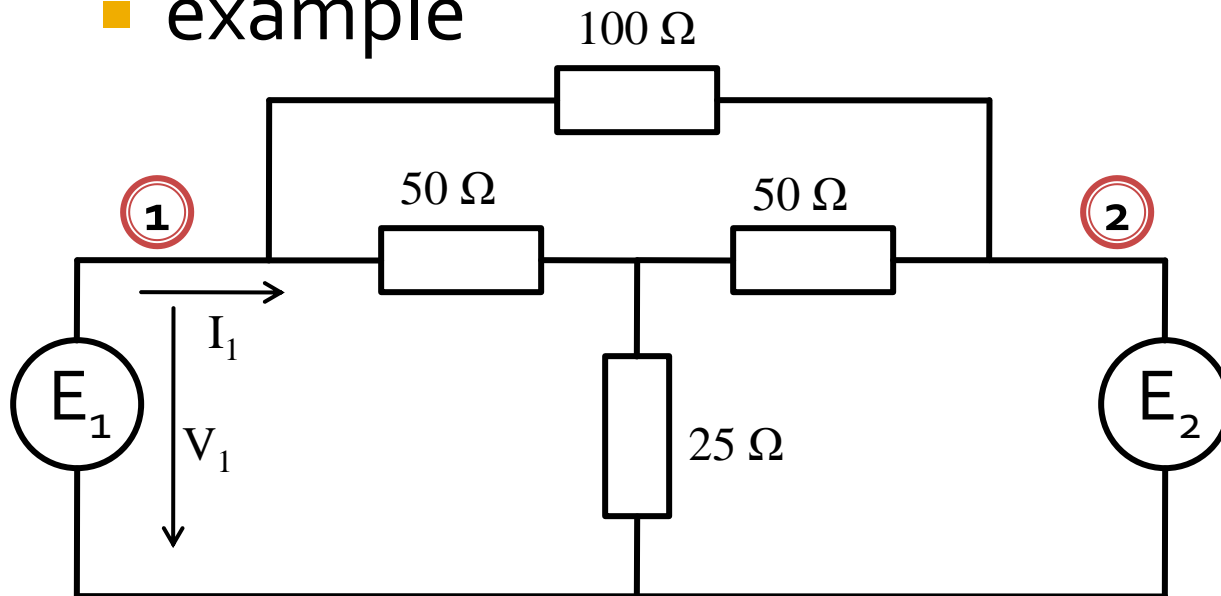


$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$
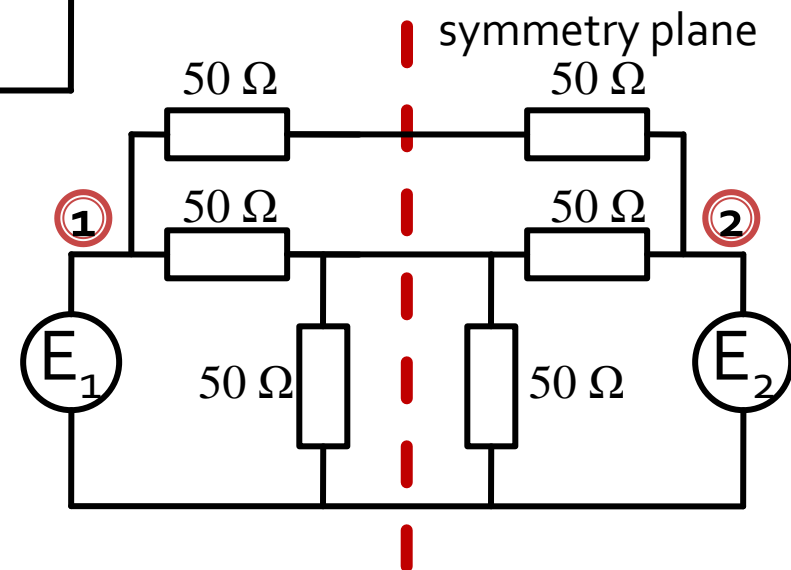
$$V_2 \equiv E_2 = 0 \Rightarrow \begin{aligned} E^e &= \frac{E_1}{2} \\ E^o &= \frac{E_1}{2} \end{aligned}$$



# Even/Odd Mode Analysis


- Even/Odd mode analysis

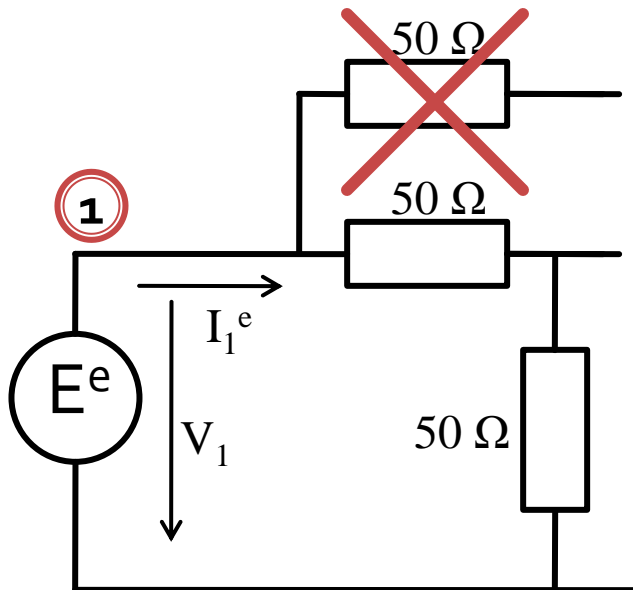

$$R_{ech}^e = 50\Omega + 50\Omega = 100\Omega$$

$$I_1^e = \frac{E^e}{R_{ech}^e} = \frac{E_1/2}{100\Omega} = \frac{E_1}{200\Omega}$$

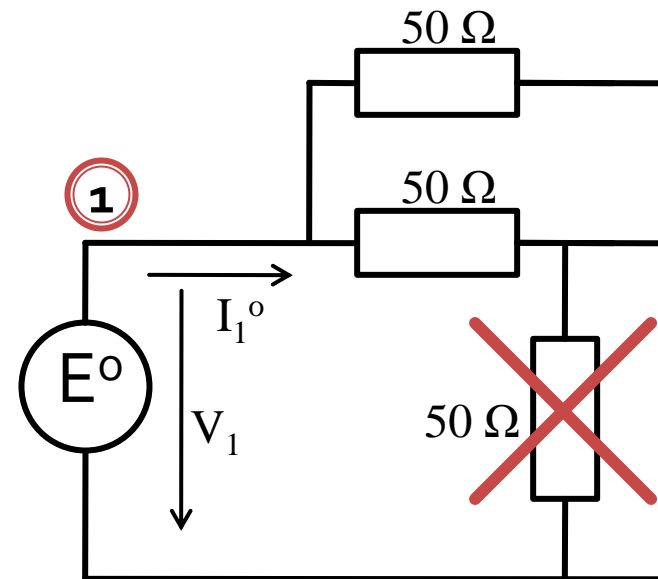**EVEN** → symmetry plane **open circuit**




$$R_{ech}^o = 50\Omega || 50\Omega = 25\Omega$$

$$I_1^o = \frac{E^o}{R_{ech}^o} = \frac{E_1/2}{25\Omega} = \frac{E_1}{50\Omega}$$

**ODD** → symmetry plane **virtual ground**

# Even/Odd Mode Analysis

- superposition principle

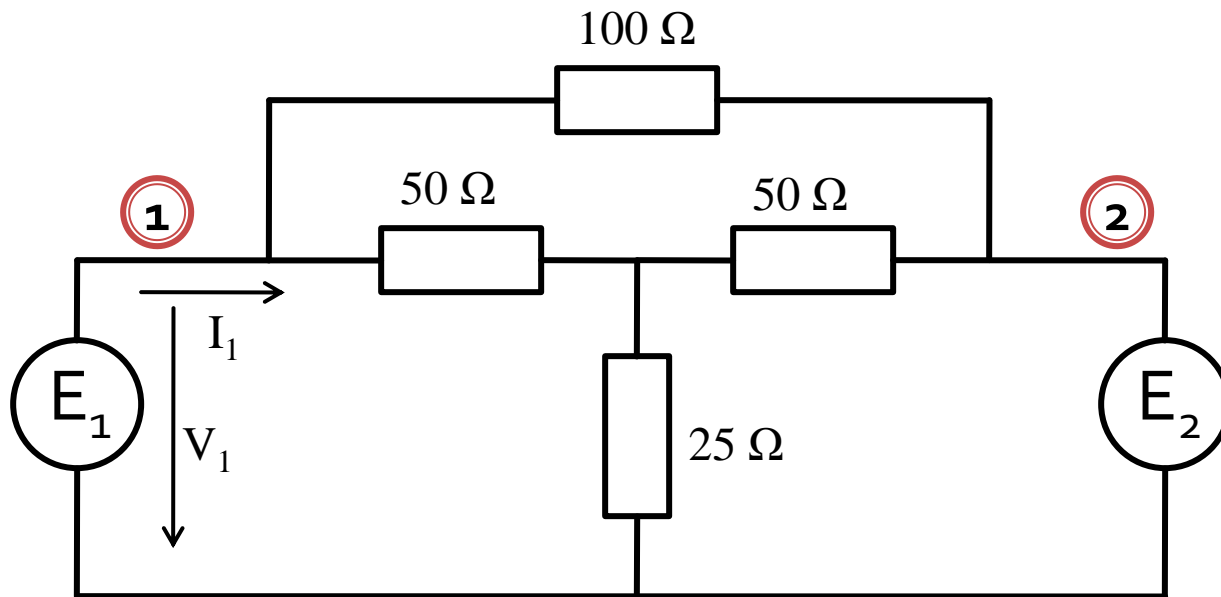

$$I_1 = I_1^e + I_1^o$$

$$V_1 = V_1^e + V_1^o$$

$$I_1 = I_1^e + I_1^o = \frac{E_1}{200\ \Omega} + \frac{E_1}{50\ \Omega} = \frac{E_1}{40\ \Omega}$$

$$V_1 = V_1^e + V_1^o = E_1$$

$$Y_{11} = \frac{I_1}{V_1} = \frac{1}{40\ \Omega} = 0.025\text{S}$$



# Even/Odd Mode Analysis

- In linear circuits we can use the superposition principle
- advantages
  - reduction of the circuit complexity
  - decrease of the **number of ports** (**main** advantage)

$$\text{Response ( ODD + EVEN )} = \text{Response ( ODD )} + \text{Response ( EVEN )}$$



We can benefit from existing symmetries !!

# Power dividers and directional couplers

# Course Topics


- Transmission lines
- Impedance matching and tuning
- **Directional couplers**
- **Power dividers**
- Microwave amplifier design
- Microwave filters
- ~~Oscillators and mixers~~

# Introduction


---
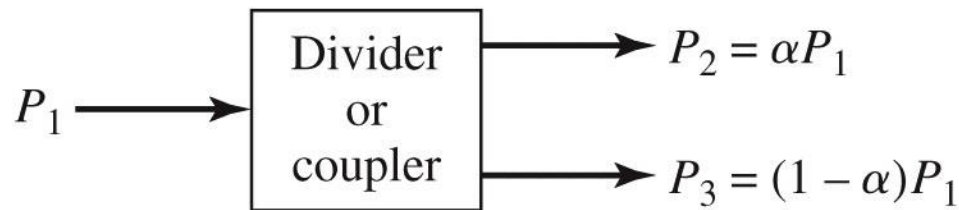
# Power dividers and couplers

- Desired functionality:
  - division
  - combining
- of signal power




(a)

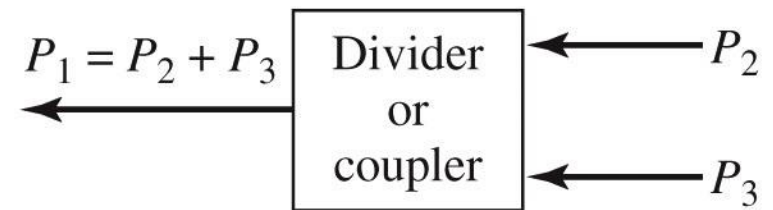


(b)

# Balanced amplifiers

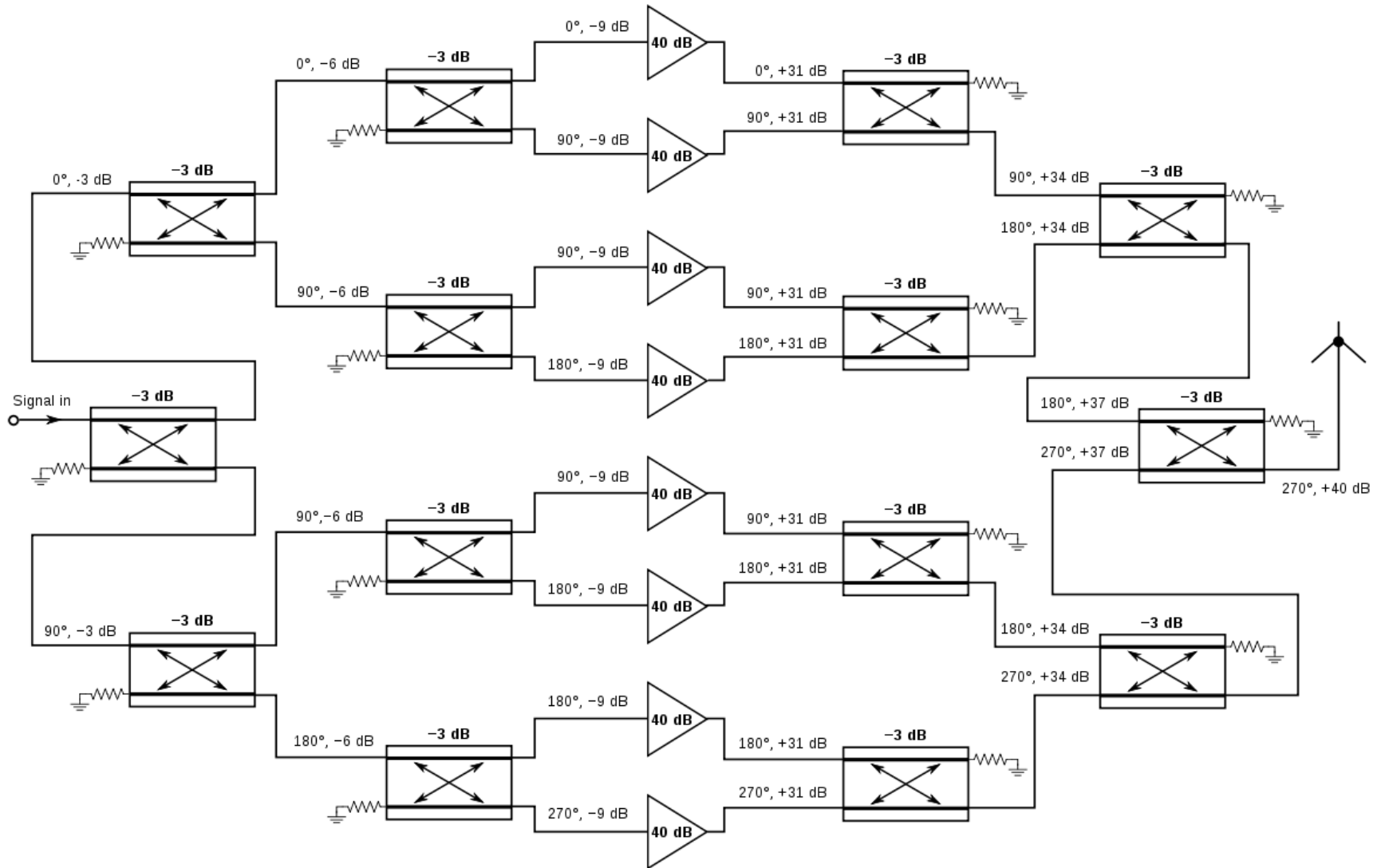

# Matching

- feedback amplifier

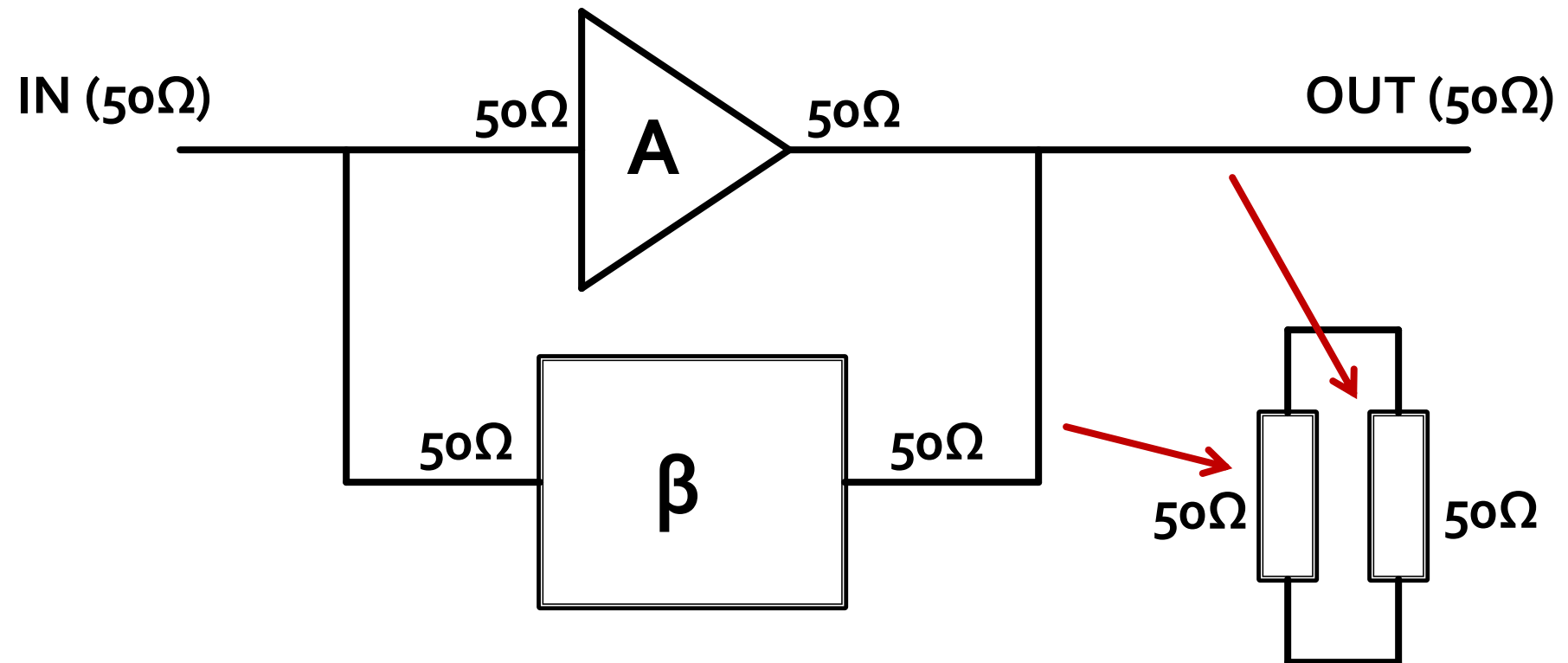

# Three-Port Networks

- also known as T-Junctions
- characterized by a  $3 \times 3$  **S** matrix

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

- the device is **reciprocal** if it does **not** contain:
  - anisotropic materials (usually ferrites)
  - active circuits
- to avoid power loss, we would like to have a network that is:
  - **lossless**, and
  - **matched at all ports**
    - to avoid reflection power “loss”



# Three-Port Networks

- reciprocal

$$[S] = [S]^t \quad S_{ij} = S_{ji}, \forall j \neq i$$

$$S_{12} = S_{21}, S_{13} = S_{31}, S_{23} = S_{32}$$

- matched at all ports

$$S_{ii} = 0, \forall i \quad S_{11} = 0, S_{22} = 0, S_{33} = 0$$

- then the S matrix is:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$


# Three-Port Networks

- reciprocal, matched at all ports, S matrix:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

- lossless network

- all the power injected in one port will be found exiting the network on all ports

$$[S]^* \cdot [S]^t = [1] \quad \sum_{k=1}^N S_{ki} \cdot S_{kj}^* = \delta_{ij}, \forall i, j$$

$$\sum_{k=1}^N S_{ki} \cdot S_{ki}^* = 1 \quad \sum_{k=1}^N S_{ki} \cdot S_{kj}^* = 0, \forall i \neq j$$

# Three-Port Networks

- lossless network

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

$$\sum_{k=1}^N S_{ki} \cdot S_{ki}^* = 1$$

$$\sum_{k=1}^N S_{ki} \cdot S_{kj}^* = 0, \forall i \neq j$$

- 6 equations / 3 unknowns

$$|S_{12}|^2 + |S_{13}|^2 = 1 \quad S_{13}^* S_{23} = 0$$

$$|S_{12}|^2 + |S_{23}|^2 = 1 \quad S_{12}^* S_{13} = 0$$

$$|S_{13}|^2 + |S_{23}|^2 = 1 \quad S_{23}^* S_{12} = 0$$

- no solution is possible

# Three-Port Networks

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

- 6 equations / 3 unknowns
  - no solution is possible
- A three-port network **cannot** be simultaneously:
  - reciprocal
  - lossless
  - matched at all ports
- If any one of these three conditions is relaxed, then a physically realizable device is possible

# Nonreciprocal Three-Port Networks

- usually containing anisotropic materials, ferrites
- **nonreciprocal**, but matched at all ports and lossless  $S_{ij} \neq S_{ji}$

- S matrix

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{21} & 0 & S_{23} \\ S_{31} & S_{32} & 0 \end{bmatrix}$$

- 6 equations / 6 unknowns

$$|S_{12}|^2 + |S_{13}|^2 = 1 \quad S_{31}^* S_{32} = 0$$

$$|S_{21}|^2 + |S_{23}|^2 = 1 \quad S_{21}^* S_{23} = 0$$

$$|S_{31}|^2 + |S_{32}|^2 = 1 \quad S_{12}^* S_{13} = 0$$

# Nonreciprocal Three-Port Networks

- two possible solutions
- circulators
  - clockwise circulation

$$S_{12} = S_{23} = S_{31} = 0$$

$$|S_{21}| = |S_{32}| = |S_{13}| = 1$$


$$[S] = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

- counterclockwise circulation


$$S_{21} = S_{32} = S_{13} = 0$$

$$|S_{12}| = |S_{23}| = |S_{31}| = 1$$
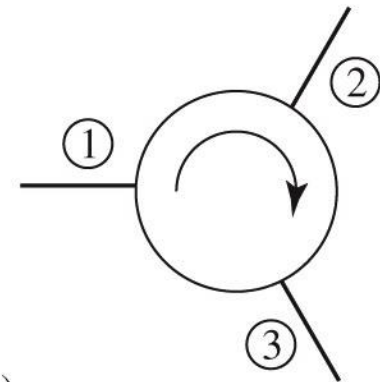
$$[S] = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix}$$





(a)

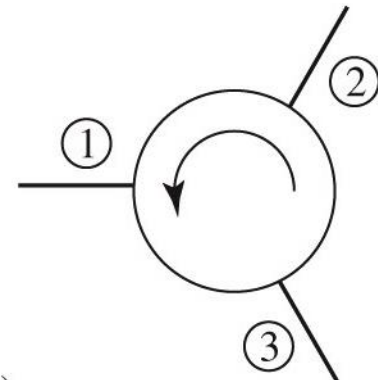

(b)

# Nonreciprocal Three-Port Networks

- circulator often found in duplexer

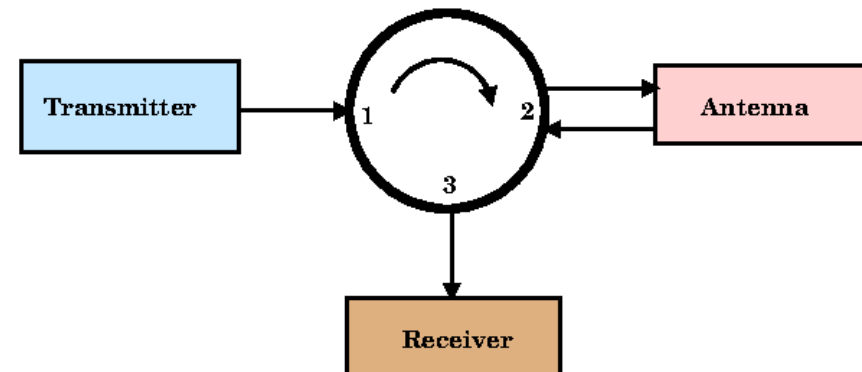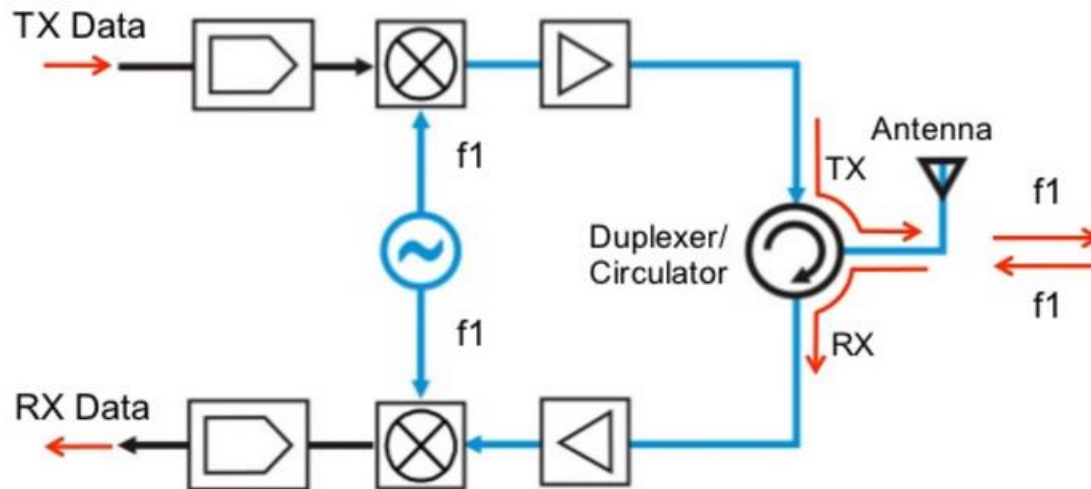

# Mismatched Three-Port Networks

- A lossless and reciprocal three-port network can be matched only on two ports, eg. 1 and 2:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & S_{33} \end{bmatrix}$$

$$S_{13}^* S_{23} = 0$$

$$S_{12}^* S_{13} + S_{23}^* S_{33} = 0$$

$$S_{23}^* S_{12} + S_{33}^* S_{13} = 0$$

$$S_{13} = S_{23} = 0$$

$$|S_{13}| = |S_{23}|$$

$$|S_{12}|^2 + |S_{13}|^2 = 1$$

$$|S_{12}|^2 + |S_{23}|^2 = 1$$

$$|S_{13}|^2 + |S_{23}|^2 + |S_{33}|^2 = 1$$

$$|S_{12}| = |S_{33}| = 1$$



# Mismatched Three-Port Networks

- A lossless and reciprocal three-port network


$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & S_{33} \end{bmatrix}$$

$$S_{13} = S_{23} = 0 \quad |S_{12}| = |S_{33}| = 1$$

$$S_{12} = e^{j\theta}$$

$$S_{33} = e^{j\phi}$$
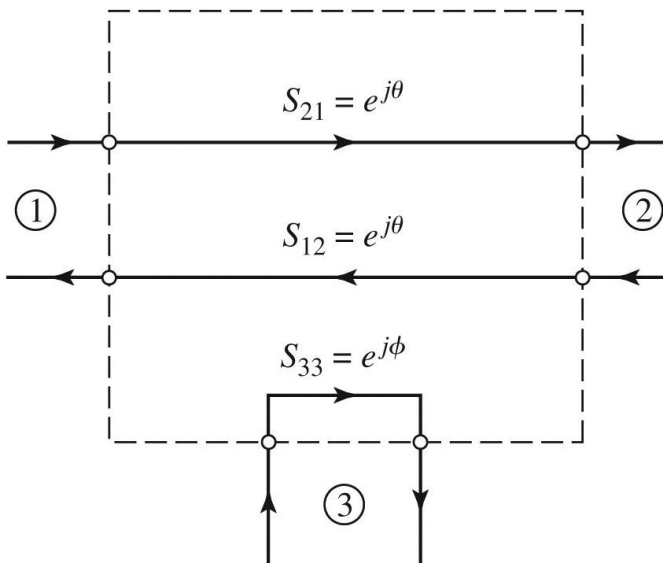
$$[S] = \begin{bmatrix} 0 & e^{j\theta} & 0 \\ e^{j\theta} & 0 & 0 \\ 0 & 0 & e^{j\phi} \end{bmatrix}$$



- A lossless and reciprocal three-port network **degenerates** into two separate components:
  - a matched two-port **line**
  - a totally **mismatched one-port**:

# Four-Port Networks

- characterized by a  $4 \times 4$  **S** matrix

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix}$$

- the device is **reciprocal** if it does **not** contain:
  - anisotropic materials (usually ferrites)
  - active circuits
- to avoid power loss, we would like to have a network that is:
  - **lossless**, and
  - **matched at all ports**
    - to avoid reflection power “loss”

# Four-Port Networks

- reciprocal

$$[S] = [S]^t \quad S_{ij} = S_{ji}, \forall j \neq i$$

$$S_{12} = S_{21}, S_{13} = S_{31}, S_{23} = S_{32}$$

- matched at all ports

$$S_{ii} = 0, \forall i \quad S_{11} = 0, S_{22} = 0, S_{33} = 0, S_{44} = 0$$

- then the S matrix is:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & S_{14} \\ S_{12} & 0 & S_{23} & S_{24} \\ S_{13} & S_{23} & 0 & S_{34} \\ S_{14} & S_{24} & S_{34} & 0 \end{bmatrix}$$


# Four-Port Networks

- reciprocal, matched at all ports, S matrix:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & S_{14} \\ S_{12} & 0 & S_{23} & S_{24} \\ S_{13} & S_{23} & 0 & S_{34} \\ S_{14} & S_{24} & S_{34} & 0 \end{bmatrix}$$

- lossless network

- all the power injected in one port will be found exiting the network on all ports

$$[S]^* \cdot [S]^t = [1] \quad \sum_{k=1}^N S_{ki} \cdot S_{kj}^* = \delta_{ij}, \forall i, j$$

$$\sum_{k=1}^N S_{ki} \cdot S_{ki}^* = 1 \quad \sum_{k=1}^N S_{ki} \cdot S_{kj}^* = 0, \forall i \neq j$$

# Four-Port Networks

$$S_{13}^* \cdot S_{23} + S_{14}^* \cdot S_{24} = 0 \quad / \cdot S_{24}^*$$

$$S_{14}^* \cdot S_{13} + S_{24}^* \cdot S_{23} = 0 \quad / \cdot S_{13}^*$$

---


$$S_{14}^* \cdot (|S_{13}|^2 - |S_{24}|^2) = 0$$

$$S_{12}^* \cdot S_{23} + S_{14}^* \cdot S_{34} = 0 \quad / \cdot S_{12}^*$$

$$S_{14}^* \cdot S_{12} + S_{34}^* \cdot S_{23} = 0 \quad / \cdot S_{34}^*$$

---


$$S_{23} \cdot (|S_{12}|^2 - |S_{34}|^2) = 0$$

- one solution:  $S_{14} = S_{23} = 0$
- resulting coupler is **directional**

$$|S_{12}|^2 + |S_{13}|^2 = 1$$

$$|S_{12}|^2 + |S_{24}|^2 = 1$$

$$|S_{13}|^2 + |S_{34}|^2 = 1$$

$$|S_{24}|^2 + |S_{34}|^2 = 1$$

$$|S_{13}| = |S_{24}|$$

$$|S_{12}| = |S_{34}|$$

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & 0 \\ S_{12} & 0 & 0 & S_{24} \\ S_{13} & 0 & 0 & S_{34} \\ 0 & S_{24} & S_{34} & 0 \end{bmatrix}$$

# Four-Port Networks

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & 0 \\ S_{12} & 0 & 0 & S_{24} \\ S_{13} & 0 & 0 & S_{34} \\ 0 & S_{24} & S_{34} & 0 \end{bmatrix} \quad |S_{12}| = |S_{34}| = \alpha \quad |S_{13}| = |S_{24}| = \beta$$

$\beta$  – voltage coupling coefficient

- We can choose the phase reference

$$S_{12} = S_{34} = \alpha \quad S_{13} = \beta \cdot e^{j\theta} \quad S_{24} = \beta \cdot e^{j\phi}$$

$$S_{12}^* \cdot S_{13} + S_{24}^* \cdot S_{34} = 0 \quad \rightarrow \quad \theta + \phi = \pi \pm 2 \cdot n \cdot \pi$$

$$|S_{12}|^2 + |S_{24}|^2 = 1 \quad \rightarrow \quad \alpha^2 + \beta^2 = 1$$

- The other possible solution for previous equations offer either essentially the same result (with a different phase reference) or the degenerate case (2 separate two port networks side by side)

$$S_{14}^* \cdot (|S_{13}|^2 - |S_{24}|^2) = 0 \quad S_{23} \cdot (|S_{12}|^2 - |S_{34}|^2) = 0$$

# Four-Port Networks

- A four-port network simultaneously:
  - matched at all ports
  - reciprocal
  - lossless
- is **always directional**
  - the signal power injected into one port is transmitted **only towards two** of the other three ports

$$[S] = \begin{bmatrix} 0 & \alpha & \beta \cdot e^{j\theta} & 0 \\ \alpha & 0 & 0 & \beta \cdot e^{j\phi} \\ \beta \cdot e^{j\theta} & 0 & 0 & \alpha \\ 0 & \beta \cdot e^{j\phi} & \alpha & 0 \end{bmatrix}$$

# Four-Port Networks

- two particular choices commonly occur in practice
  - A Symmetric Coupler ( $90^\circ$ )  $\theta = \phi = \pi/2$


$$[S] = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$

- An Antisymmetric Coupler ( $180^\circ$ )  $\theta = 0, \phi = \pi$

$$[S] = \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$



# Directional Coupler

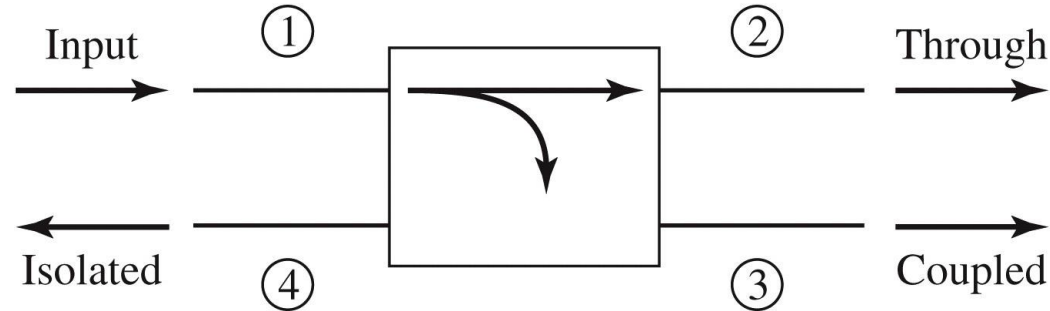

$$|S_{12}|^2 = \alpha^2 = 1 - \beta^2$$

$$|S_{13}|^2 = \beta^2$$

**Coupling**

$$C = 10 \log \frac{P_1}{P_3} = -20 \cdot \log(\beta) [\text{dB}]$$

**Directivity**


$$D = 10 \log \frac{P_3}{P_4} = 20 \cdot \log \left( \frac{\beta}{|S_{14}|} \right) [\text{dB}]$$

**Isolation**


$$I = 10 \log \frac{P_1}{P_4} = -20 \cdot \log |S_{14}| [\text{dB}]$$

$$I = D + C, \quad [\text{dB}]$$

Figure 7.4  
© John Wiley & Sons, Inc. All rights reserved.

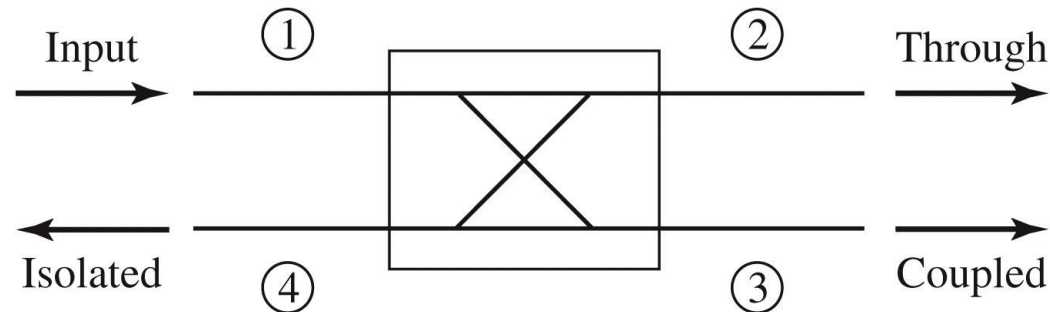

# Balanced amplifiers

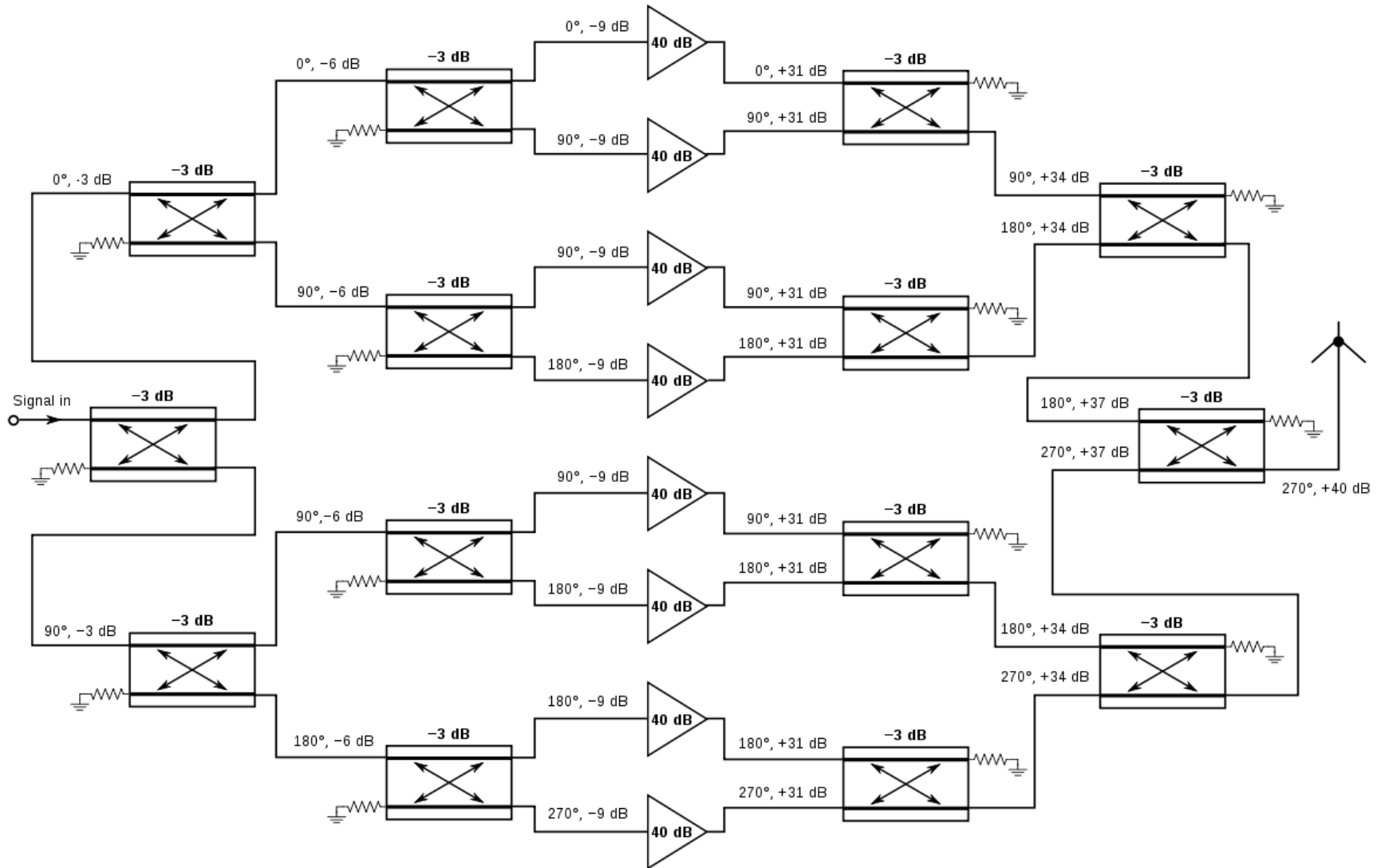

# Power dividers


# Three-Port Networks

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

- 6 equations / 3 unknowns
  - no solution is possible
- A three-port network **cannot** be simultaneously:
  - reciprocal
  - **lossless**
  - matched at all ports
- If any one of these three conditions is relaxed, then a physically realizable device is possible
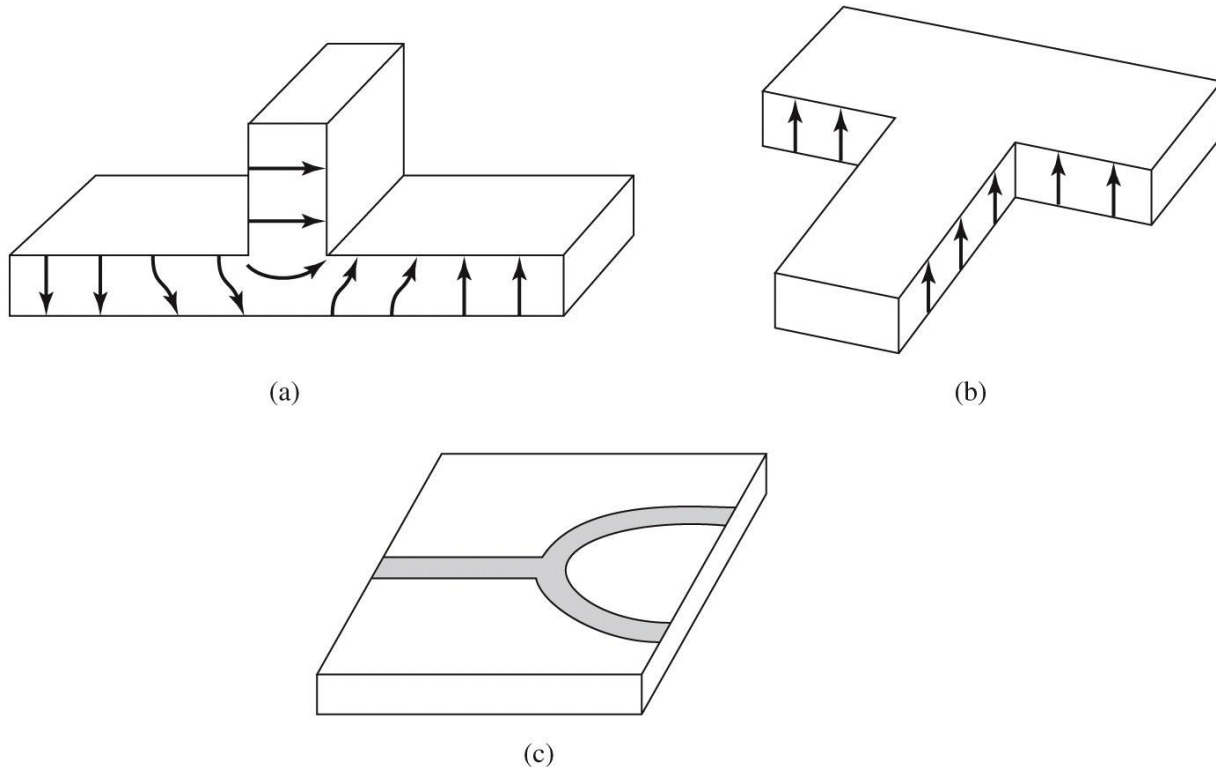
# Power division of the T-junction


- consists in splitting an input line into two separate output lines
- available in various technologies for the lines



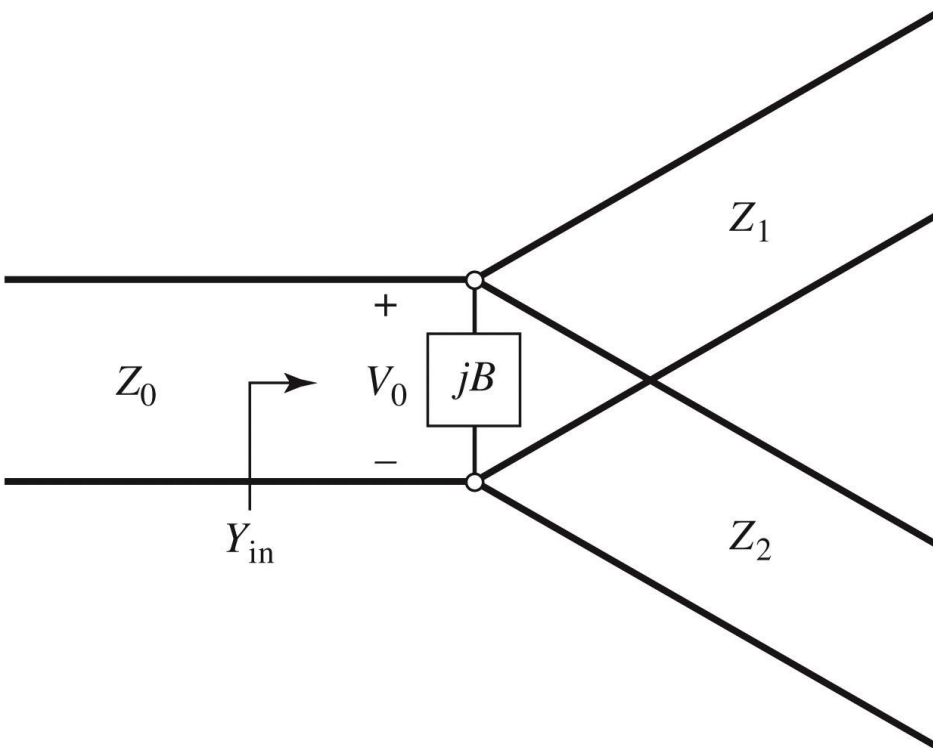
# Power division of the T-junction

- if the lines are lossless, the network is reciprocal, so it cannot be matched at all ports simultaneously

- there may be fringing fields and higher order modes associated with the discontinuity at such a junction
- the stored energy can be accounted for by a lumped susceptance: **B**
- Designing the power divider targets matching to the input line  $Z_0$ 
  - outputs (unmatched,  $Z_1$  and  $Z_2$ ) can be, if needed, matched to  $Z_0$  ( $\lambda/4$ , binomial, Chebyshev)



# Power division of the T-junction

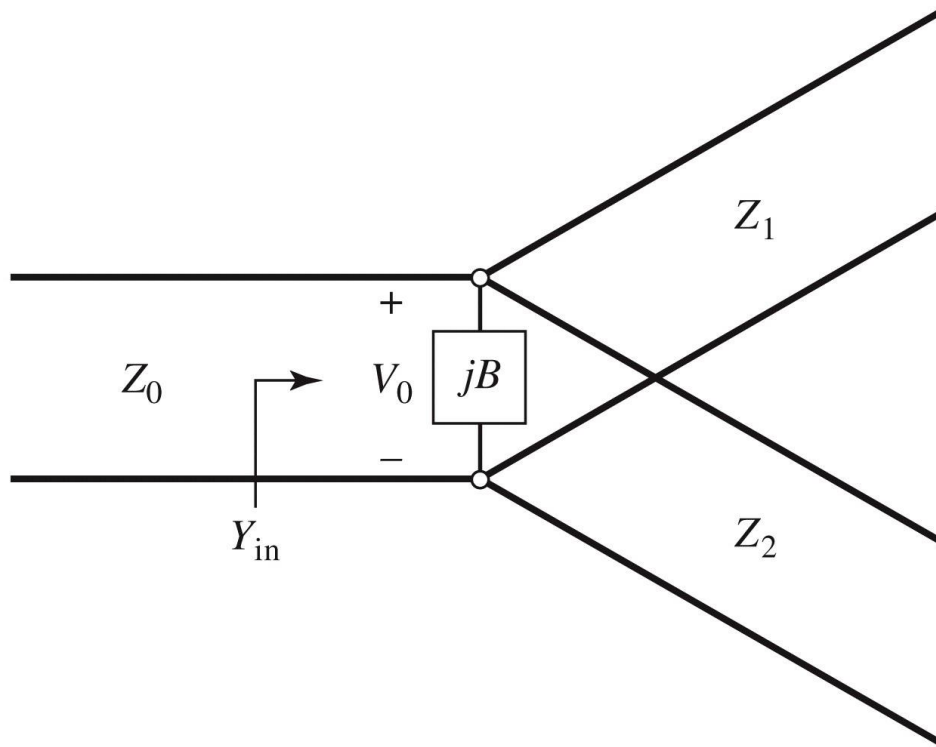

$$Y_{in} = j \cdot B + \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$$

- If the transmission lines are assumed to be lossless, then the characteristic impedances are real
- the matching condition can be met only if  $B \cong 0$  thus the matching condition is:

$$\frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$$

Figure 7.6  
© John Wiley & Sons, Inc. All rights reserved.

In practice, if  $B$  is not negligible, some type of discontinuity compensation or a reactive tuning element can usually be used to cancel this susceptance, at least over a narrow frequency range.

# Power division of the T-junction

- if  $V_0$  is the voltage at the junction, we can compute how the input power is divided between the two output lines

$$P_{in} = \frac{1}{2} \cdot \frac{V_0^2}{Z_0} \quad P_1 = \frac{1}{2} \cdot \frac{V_0^2}{Z_1}$$

then:

$$P_{in} = P_1 + P_2 \quad (\text{lossless/input matching})$$


$$P_2 = \frac{1}{2} \cdot \frac{V_0^2}{Z_2}$$

$$\frac{P_1}{P_2} = \frac{Z_2}{Z_1} = \alpha \quad (\text{power division between the two output lines})$$

$$P_1 = P_{in} \cdot \frac{Z_2}{Z_1 + Z_2} \quad P_2 = P_{in} \cdot \frac{Z_1}{Z_1 + Z_2}$$

$$P_1 = P_{in} \cdot \frac{\alpha}{1 + \alpha} \quad P_2 = P_{in} \cdot \frac{1}{1 + \alpha}$$

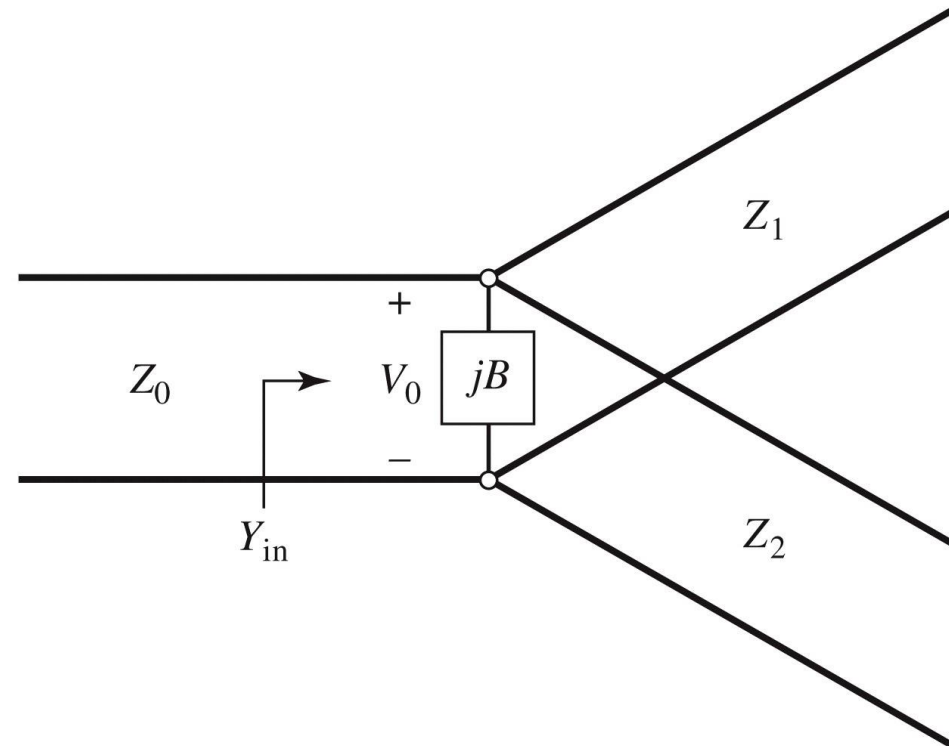
$$Z_1 = Z_0 \cdot \left(1 + \frac{1}{\alpha}\right) \quad Z_2 = Z_0 \cdot (1 + \alpha)$$




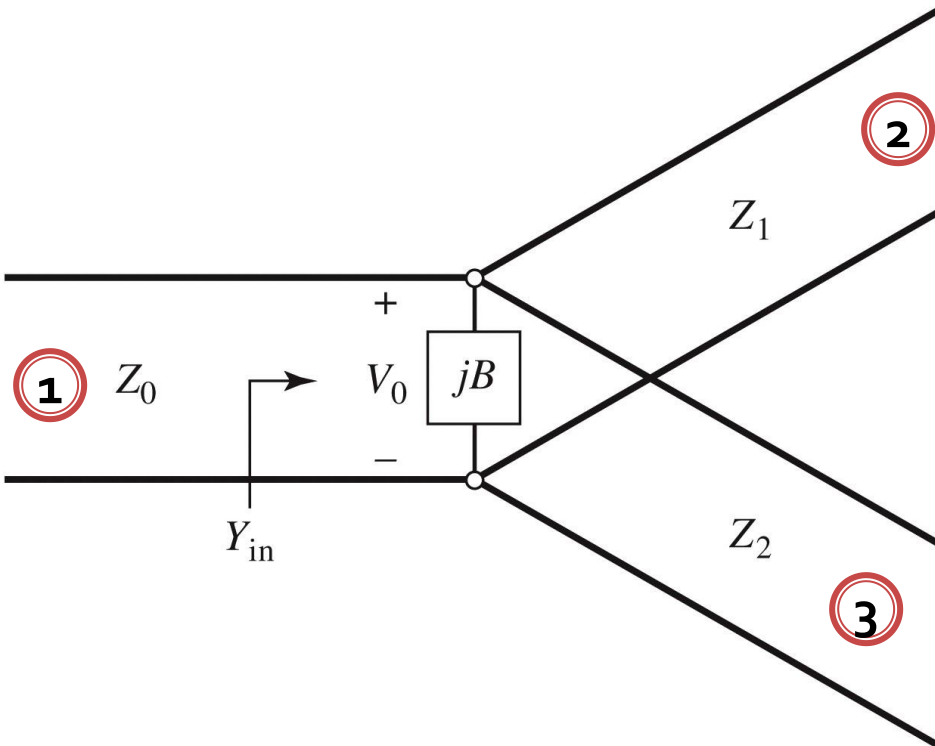
# Power division of the T-junction

- S matrix
  - lossless (unitary matrix)
  - reciprocal (symmetrical matrix)
  - input port is matched  $S_{11} = 0$



$$P_2 = P_1 \cdot \frac{\alpha}{1 + \alpha} \quad S_{21} = S_{12} = \sqrt{\frac{\alpha}{1 + \alpha}}$$

$$P_3 = P_1 \cdot \frac{1}{1 + \alpha} \quad S_{31} = S_{13} = \sqrt{\frac{1}{1 + \alpha}}$$


the reflection coefficients seen looking into the output ports

$$S_{22} = \Gamma_1 = \frac{Z_0 \parallel Z_2 - Z_1}{Z_0 \parallel Z_2 + Z_1} = -\frac{1}{1 + \alpha}$$

$$S_{33} = \Gamma_2 = \frac{Z_0 \parallel Z_1 - Z_2}{Z_0 \parallel Z_1 + Z_2} = -\frac{\alpha}{1 + \alpha}$$
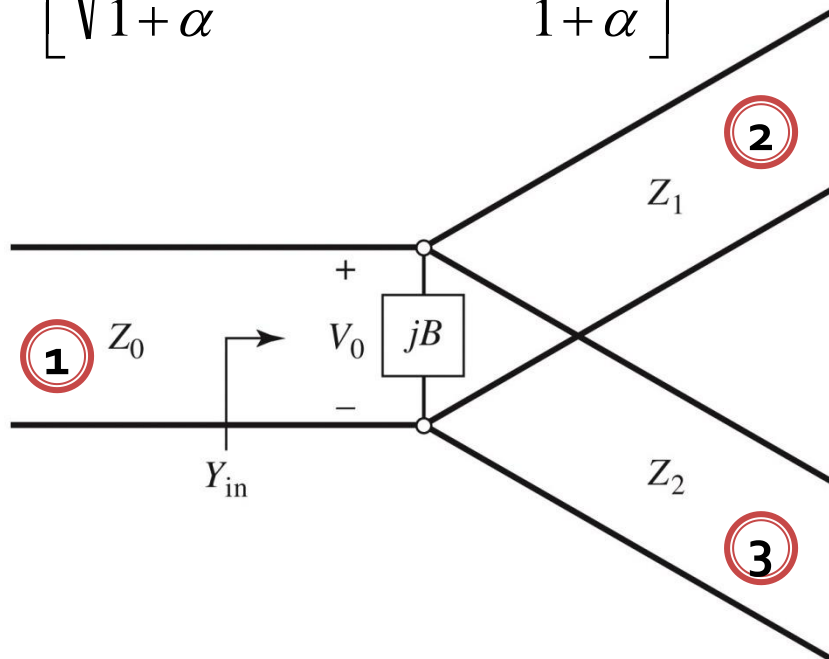
# Power division of the T-junction

$$[S] = \begin{bmatrix} 0 & \sqrt{\frac{\alpha}{1+\alpha}} & \sqrt{\frac{1}{1+\alpha}} \\ \sqrt{\frac{\alpha}{1+\alpha}} & -\frac{1}{1+\alpha} & x \\ \sqrt{\frac{1}{1+\alpha}} & x & -\frac{\alpha}{1+\alpha} \end{bmatrix}$$



Unitary matrix, columns 1 and 2

$$0 - \frac{1}{1+\alpha} \cdot \sqrt{\frac{\alpha}{1+\alpha}} + x \cdot \sqrt{\frac{1}{1+\alpha}} = 0$$

$$S_{23} = S_{32} = \frac{\sqrt{\alpha}}{1+\alpha}$$

$$[S] = \begin{bmatrix} 0 & \sqrt{\frac{\alpha}{1+\alpha}} & \sqrt{\frac{1}{1+\alpha}} \\ \sqrt{\frac{\alpha}{1+\alpha}} & -\frac{1}{1+\alpha} & \frac{\sqrt{\alpha}}{1+\alpha} \\ \sqrt{\frac{1}{1+\alpha}} & \frac{\sqrt{\alpha}}{1+\alpha} & -\frac{\alpha}{1+\alpha} \end{bmatrix}$$


# Power division of the T-junction

- 3dB divider
  - equal splitting of the power between the two outputs
  - $Z_1 = Z_2 = 2 \cdot Z_0, \alpha = 1$

$$[S] = \begin{bmatrix} 0 & \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & -\frac{1}{2} & \frac{1}{2} \\ \frac{1}{\sqrt{2}} & \frac{1}{2} & -\frac{1}{2} \end{bmatrix}$$

If we add  $\lambda/4$  transformers to match outputs to  $Z_0$  S matrix:
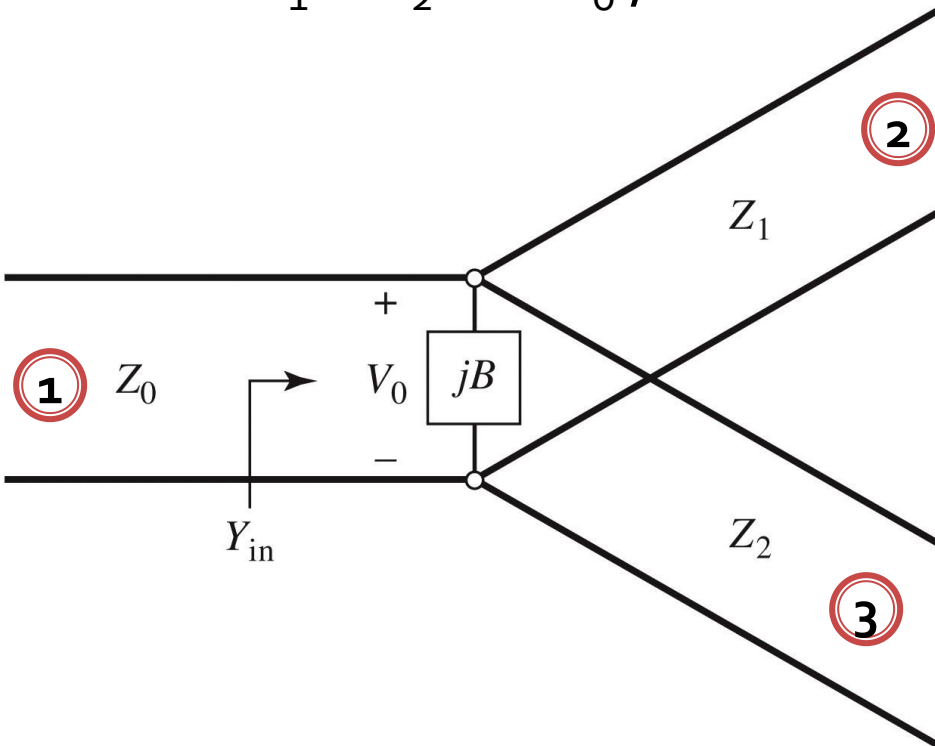
$$[S] = \begin{bmatrix} 0 & -\frac{j}{\sqrt{2}} & -\frac{j}{\sqrt{2}} \\ -\frac{j}{\sqrt{2}} & \frac{1}{2} & \frac{1}{2} \\ -\frac{j}{\sqrt{2}} & -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$



# Example

- Design a lossless T-junction divider with a  $30\Omega$  source impedance to give a 3:1 power split. Design quarter-wave matching transformers to convert the impedances of the output lines to  $30\Omega$ . (**Pozar** problem)

$$P_{in} = \frac{1}{2} \cdot \frac{V_0^2}{Z_0} \quad \begin{cases} P_1 + P_2 = P_{in} \\ P_1 : P_2 = 3 : 1 \end{cases} \Rightarrow \begin{cases} P_1 = \frac{1}{4} \cdot P_{in} \\ P_2 = \frac{3}{4} \cdot P_{in} \end{cases}$$

$$P_1 = \frac{1}{2} \cdot \frac{V_0^2}{Z_1} = \frac{1}{4} \cdot P_{in} \quad Z_1 = 4 \cdot Z_0 = 120\Omega$$

$$P_2 = \frac{1}{2} \cdot \frac{V_0^2}{Z_2} = \frac{3}{4} \cdot P_{in} \quad Z_2 = 4 \cdot Z_0 / 3 = 40\Omega$$

Input match check


$$Z_{in} = 40\Omega \parallel 120\Omega = 30\Omega$$

quarter-wave transformers  $Z_c^i = \sqrt{Z_i \cdot Z_L}$

$$Z_c^1 = \sqrt{Z_1 \cdot Z_L} = \sqrt{120\Omega \cdot 30\Omega} = 60\Omega \quad Z_c^2 = \sqrt{Z_2 \cdot Z_L} = \sqrt{40\Omega \cdot 30\Omega} = 34.64\Omega$$
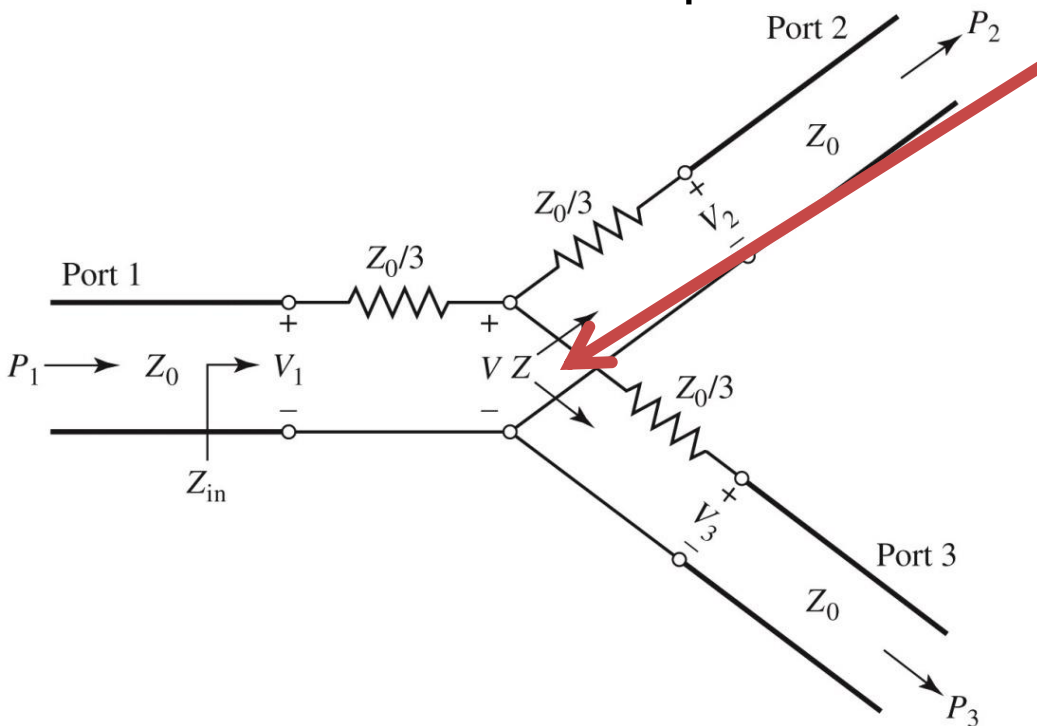
# Resistive Divider

- If a three-port divider contains lossy components, it can be made to be :
  - reciprocal
  - matched at all ports



The impedance  $Z$ , seen looking into the  $Z_0/3$  resistor followed by a terminated output line:

$$Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$$

The input line will be terminated with a  $Z_0/3$  resistor in series with two such lines  $Z$  in parallel


$$Z_{in} = \frac{Z_0}{3} + \frac{1}{2} \cdot \frac{4Z_0}{3} = Z_0$$

so it will be matched:  $S_{11} = 0$

from symmetry:  $S_{11} = S_{22} = S_{33} = 0$
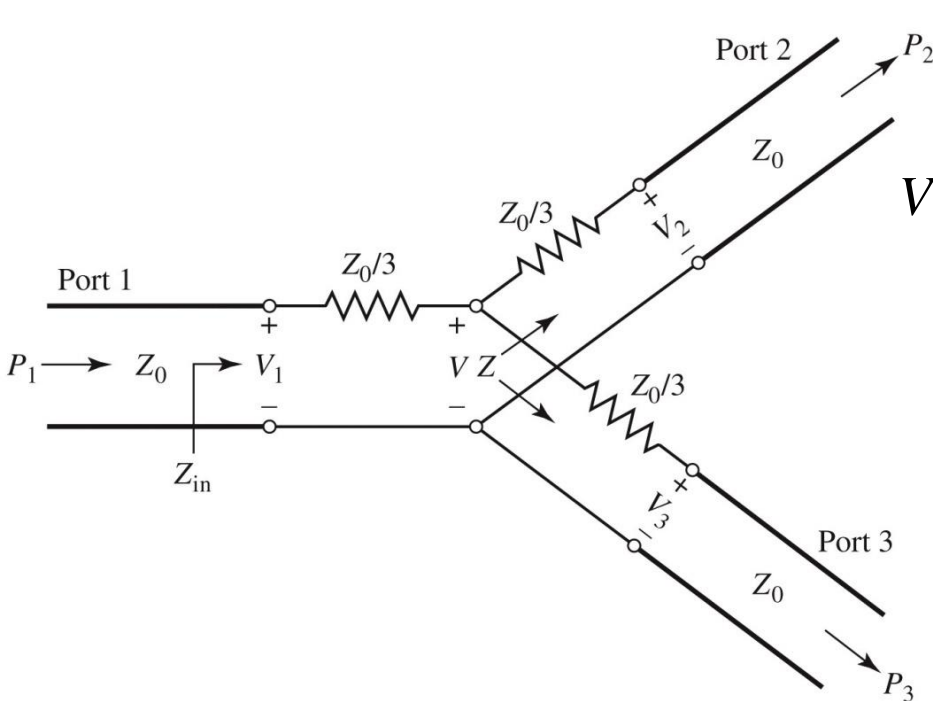
# Resistive Divider

- If a three-port divider contains lossy components, it can be made to be :
  - reciprocal
  - matched at all ports  $S_{11} = S_{22} = S_{33} = 0$



If the voltage at port 1 is  $V_1$ , then by voltage division the voltage  $V$  at the junction is:

$$V = V_1 \cdot \frac{Z/2}{Z/2 + Z_0/3} = V_1 \cdot \frac{2Z_0/3}{2Z_0/3 + Z_0/3} = \frac{2}{3} \cdot V_1$$

The output voltages are, again by voltage division :


$$V_2 = V_3 = V \cdot \frac{Z_0}{Z_0 + Z_0/3} = \frac{3}{4} \cdot V = \frac{1}{2} \cdot V_1$$

$$S_{21} = S_{31} = \frac{1}{2}$$

from symmetry:  $S_{21} = S_{31} = S_{23} = \frac{1}{2}$
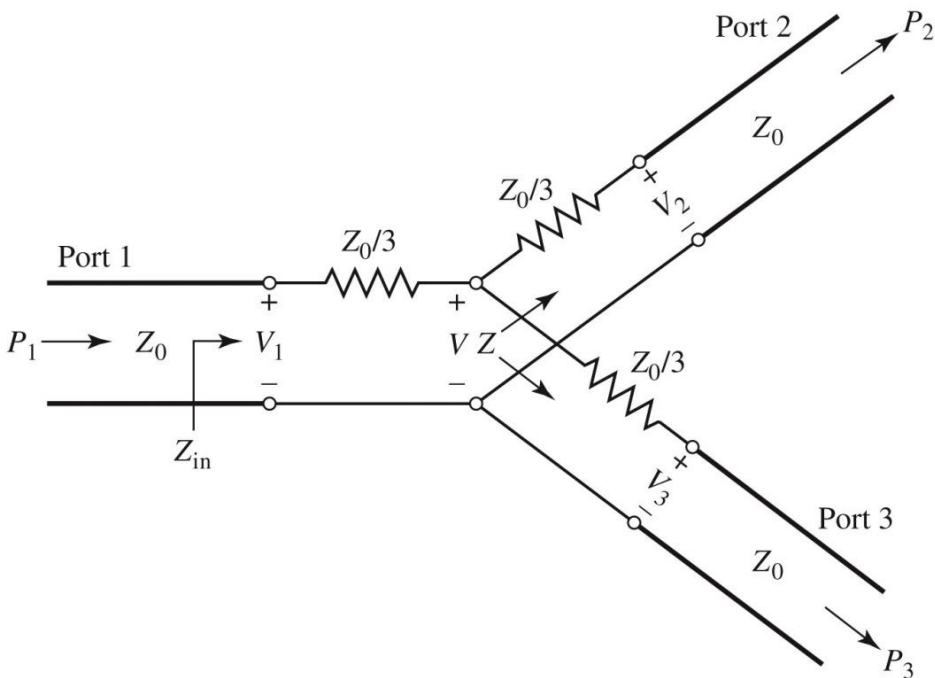
# Resistive Divider

- If a three-port divider contains lossy components, it can be made to be :
  - reciprocal (S matrix is symmetrical)  $S_{21} = S_{31} = S_{23} = \frac{1}{2}$
  - matched at all ports  $S_{11} = S_{22} = S_{33} = 0$



S matrix: 
$$[S] = \frac{1}{2} \cdot \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$


Powers: 
$$P_{in} = \frac{1}{2} \cdot \frac{V_1^2}{Z_0}$$

$$P_2 = P_3 = \frac{1}{2} \cdot \frac{(1/2 V_1)^2}{Z_0} = \frac{1}{8} \cdot \frac{V_1^2}{Z_0} = \frac{1}{4} \cdot P_{in}$$

**Half** of the supplied power is dissipated in the 3 resistors. The output powers are 6 dB below the input power level
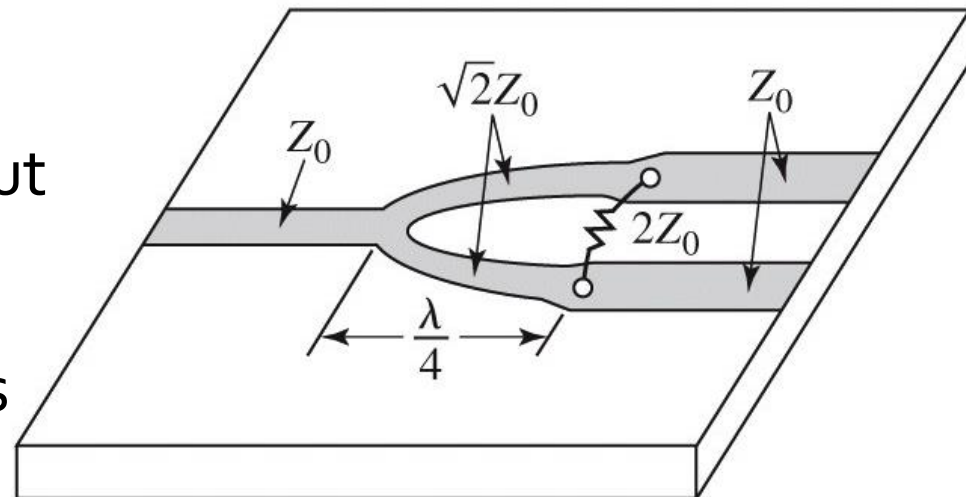
# The Wilkinson power divider


- Previous power dividers suffer from a major drawback, there is not isolation between the two output ports  $S_{23} = S_{32} \neq 0$ 
  - this requirement is important in some applications
- The Wilkinson power divider solves this problem
  - it also has the useful property of appearing **lossless** when the output ports are matched
  - only reflected power from the output ports is dissipated





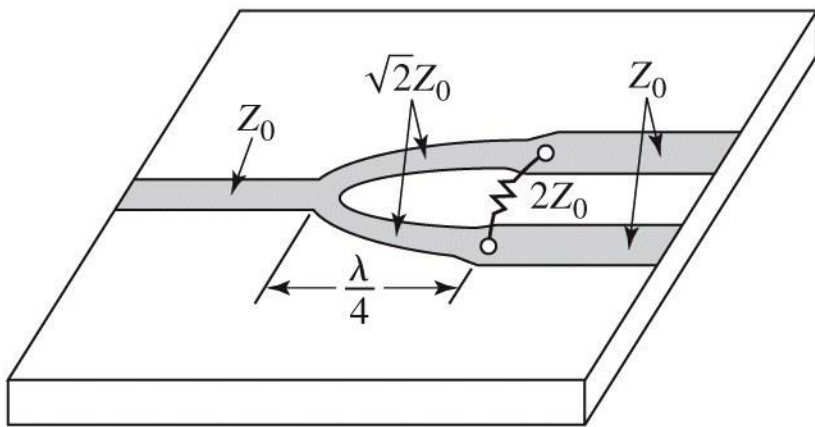
# The Wilkinson power divider

- one input line
- two  $\lambda/4$  transformers
- one resistor between the output lines



(a)

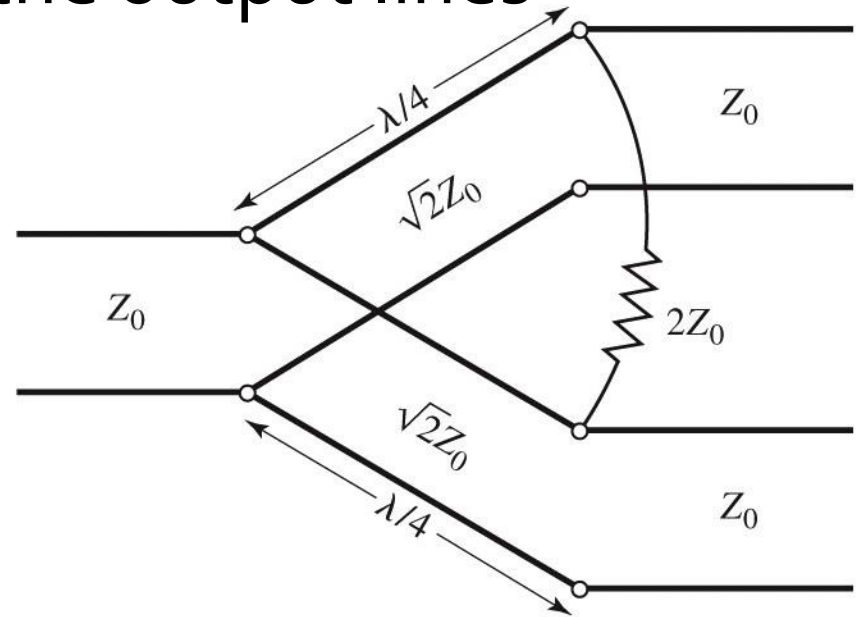

(b)

# Even/Odd Mode Analysis

- In linear circuits we can use the superposition principle
- advantages
  - reduction of the circuit complexity
  - decrease of the number of ports (**main** advantage)

$$\text{Response ( ODD + EVEN )} = \text{Response ( ODD )} + \text{Response ( EVEN )}$$



We can benefit from existing symmetries !!

# The Wilkinson power divider

- the circuit in normalized and symmetric form


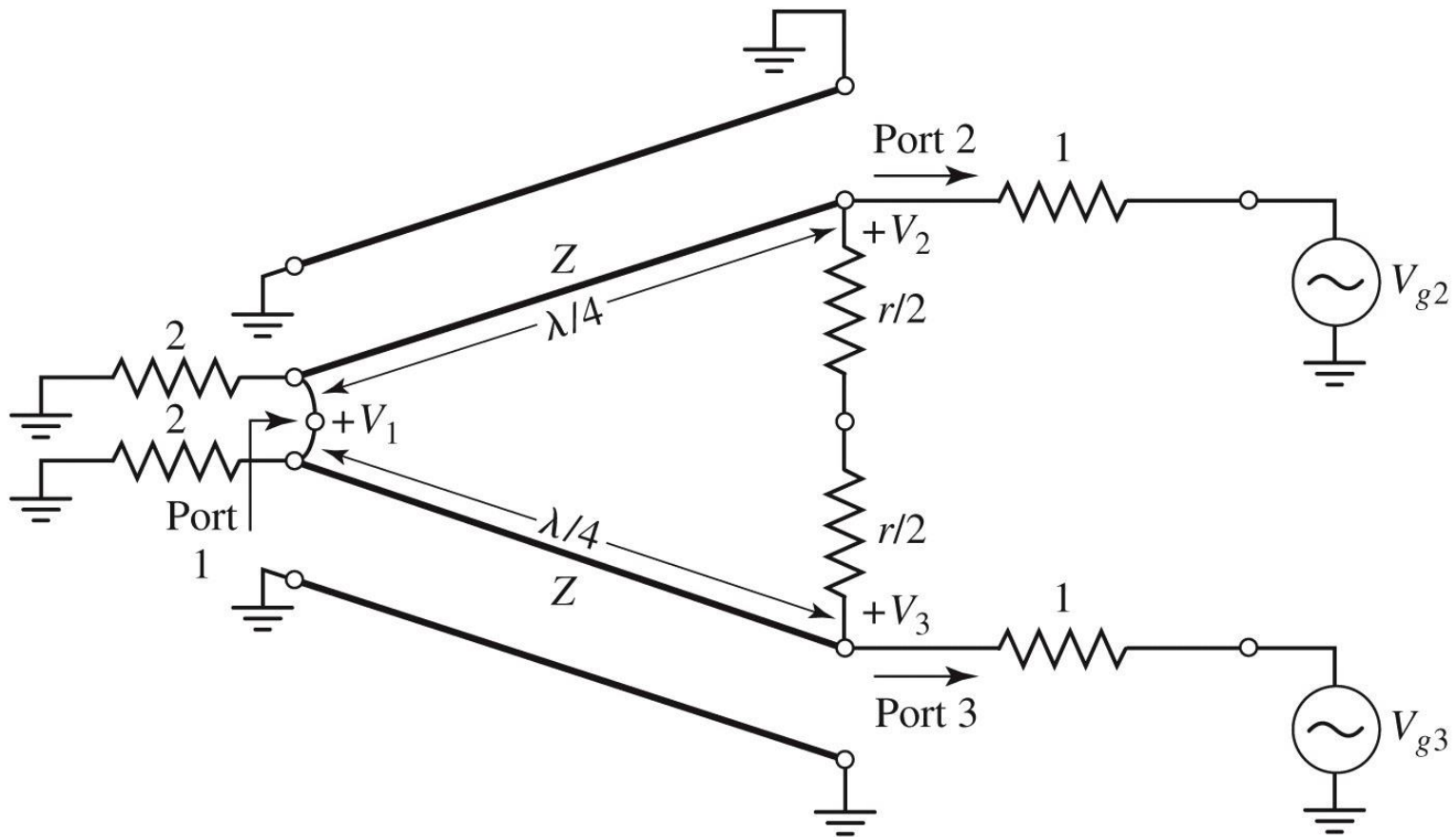
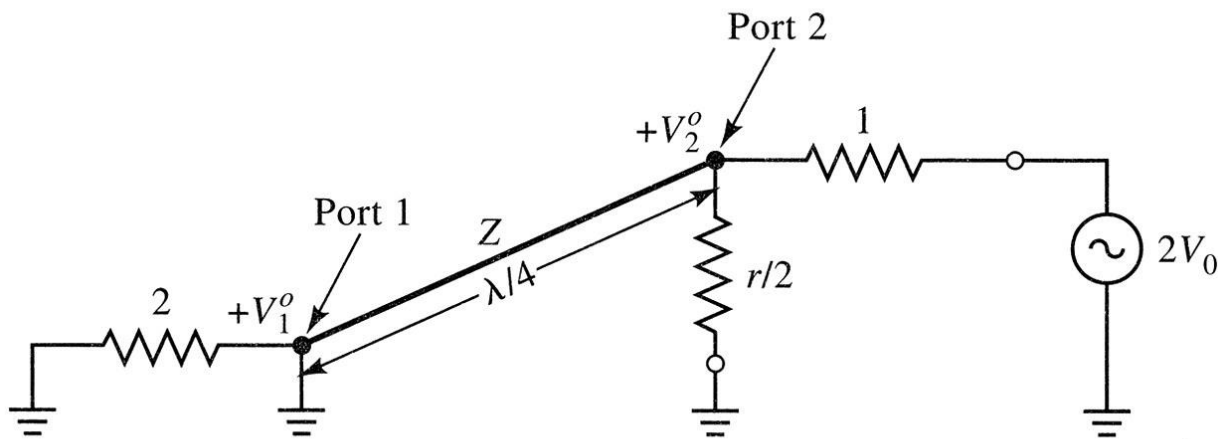


Figure 7.9  
© John Wiley & Sons, Inc. All rights reserved.


# The Wilkinson power divider

- Even/Odd Mode Analysis

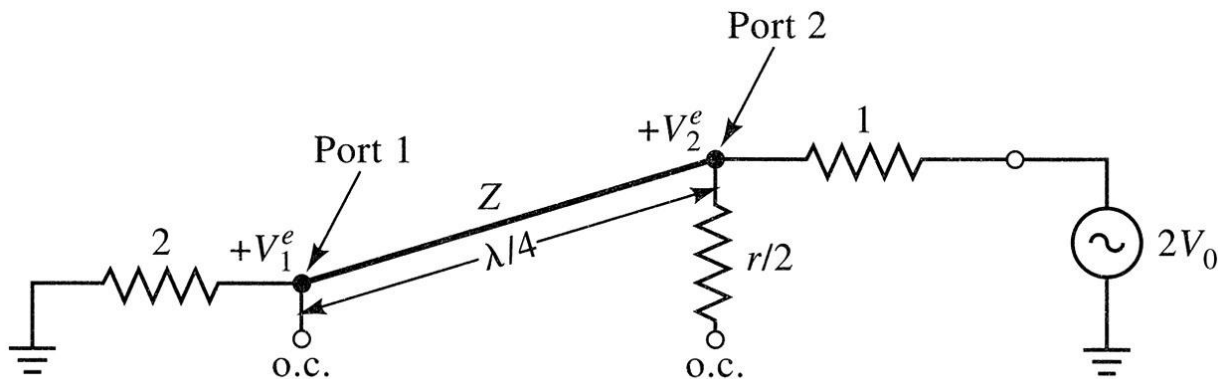
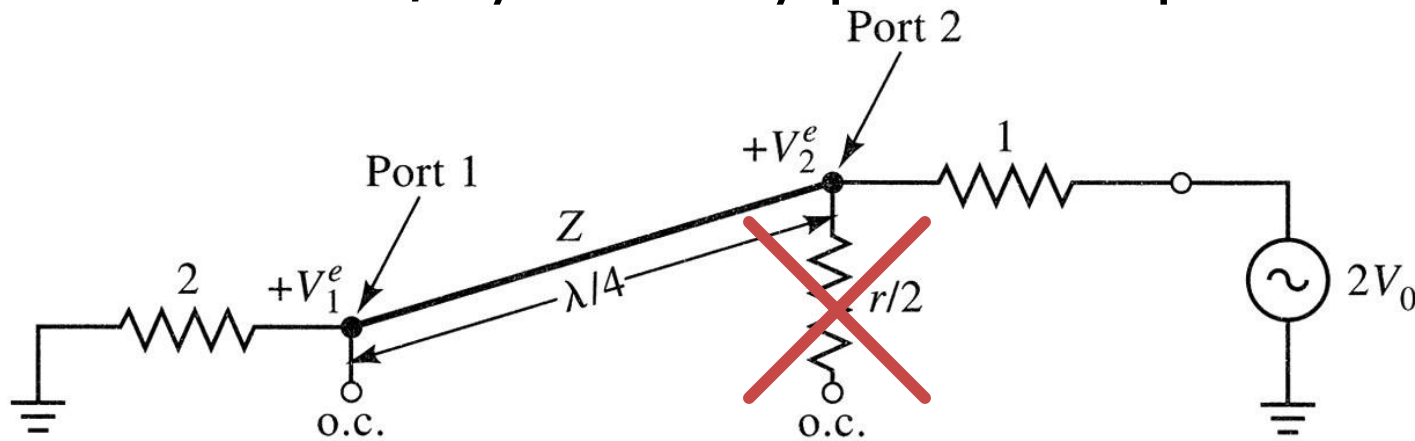
# The Wilkinson power divider

- even mode, symmetry plane is open circuit



looking into port 2,  $\lambda/4$  transformer with 2 load  $Z_{in2}^e = \frac{Z^2}{2}$  if  $Z = \sqrt{2}$  port 2 is matched  $Z_{in2}^e = 1$

$$V(x) = V^+ \cdot (e^{-j\beta \cdot x} + \Gamma \cdot e^{j\beta \cdot x}) \quad \begin{array}{l} x=0 \text{ at port 1} \\ x=-\lambda/4 \text{ at port 2} \end{array}$$

$$V_2^e = V(-\lambda/4) = jV^+ \cdot (1 - \Gamma) = V_0 \quad V_1^e = V(0) = V^+ \cdot (1 + \Gamma) = jV_0 \cdot \frac{\Gamma + 1}{\Gamma - 1}$$


$Z_{in2}^e = 1$

$\Gamma$ : reflection coefficient seen at port 1 looking toward the resistor of normalized value 2 from the transformer  $Z = \sqrt{2}$

$$\Gamma = \frac{2 - \sqrt{2}}{2 + \sqrt{2}} \quad V_1^e = -jV_0 \sqrt{2}$$

# The Wilkinson power divider

- odd mode, symmetry plane is grounded

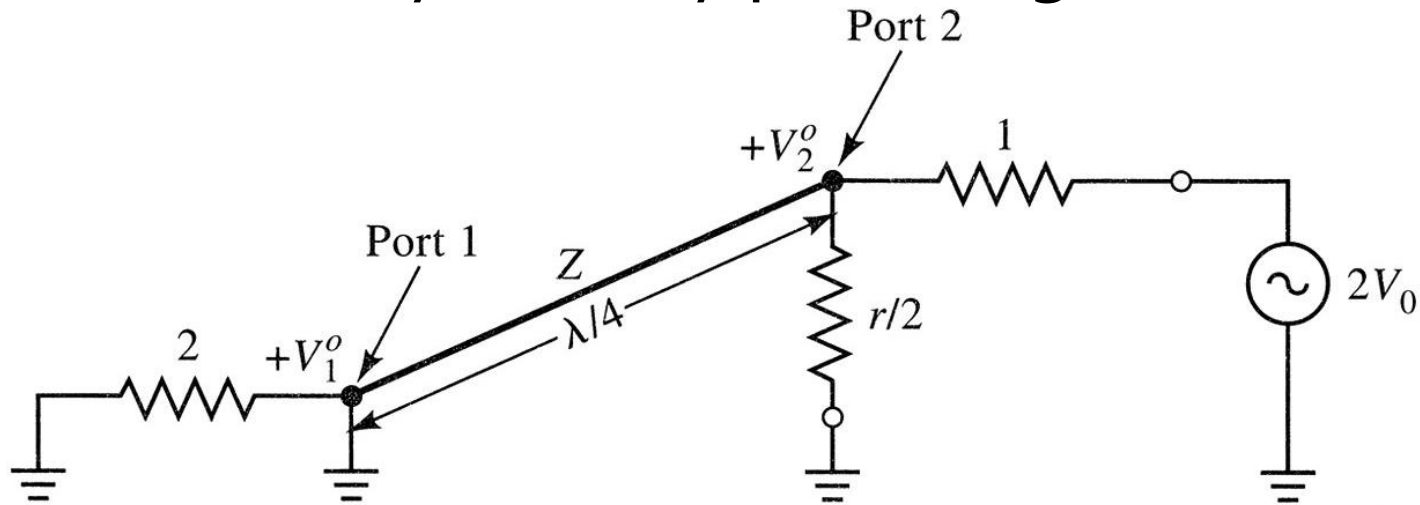


looking from port 2 the  $\lambda/4$  line is short-circuited, impedance seen from port 2 is  $\infty$   $Z_{in2}^o = r/2$  if  $r = 2$  port 2 is matched

$$Z_{in2}^o = 1 \rightarrow V_2^o = V_0$$

$V_1^o = 0$  in the odd mode all the power is dissipated in the  $r/2$  resistor


# The Wilkinson power divider

- input impedance in port 1

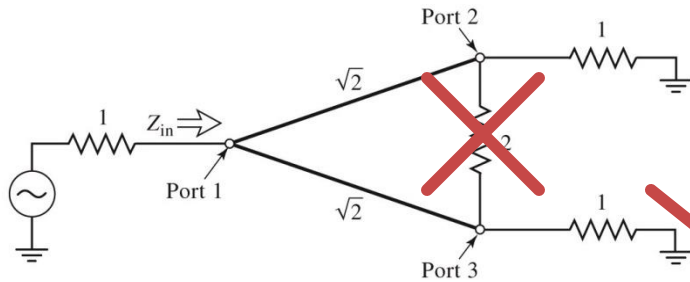

two  $\lambda/4$  transformers with load 1 in parallel
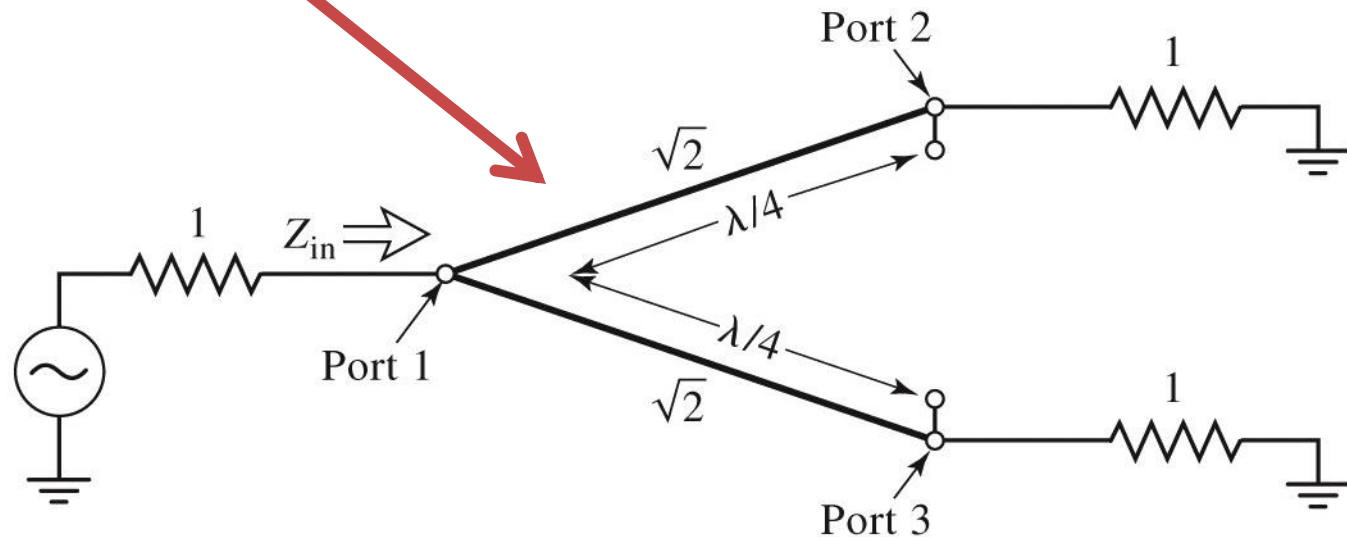
$$Z_{in1} = \frac{1}{2} (\sqrt{2})^2 = 1$$



# The Wilkinson power divider

- S parameters

$$Z_{in1} = \frac{1}{2}(\sqrt{2})^2 = 1 \quad S_{11} = 0$$

$$Z_{in2}^e = 1 \quad Z_{in2}^o = 1 \quad \text{and} \quad Z_{in3}^e = 1 \quad Z_{in3}^o = 1 \quad S_{22} = S_{33} = 0$$

$$S_{12} = S_{21} = \frac{V_1^e + V_1^o}{V_2^e + V_2^o} = -\frac{j}{\sqrt{2}}$$

$$\text{and} \quad S_{13} = S_{31} = -\frac{j}{\sqrt{2}}$$

$$S_{23} = S_{32} = 0 \quad \text{due to short or open at bisection, both eliminate transfer between the ports + reciprocal circuit}$$



# The Wilkinson power divider

- at design frequency (length of the transformer equal to  $\lambda_0/4$ ) we have **isolation** between the two output ports

$$[S] = \begin{bmatrix} 0 & -\frac{j}{\sqrt{2}} & -\frac{j}{\sqrt{2}} \\ -\frac{j}{\sqrt{2}} & 0 & 0 \\ -\frac{j}{\sqrt{2}} & 0 & 0 \end{bmatrix}$$


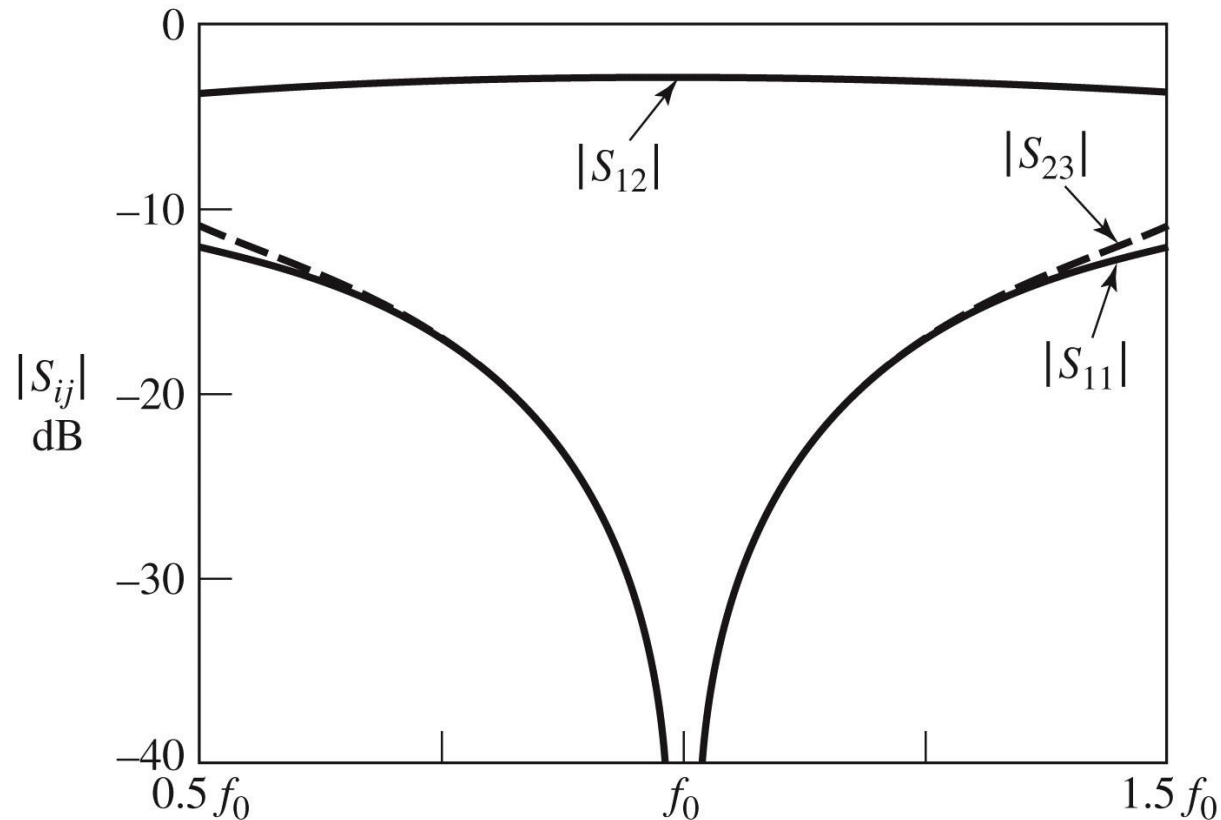


Figure 7.12  
© John Wiley & Sons, Inc. All rights reserved.


# The Wilkinson power divider

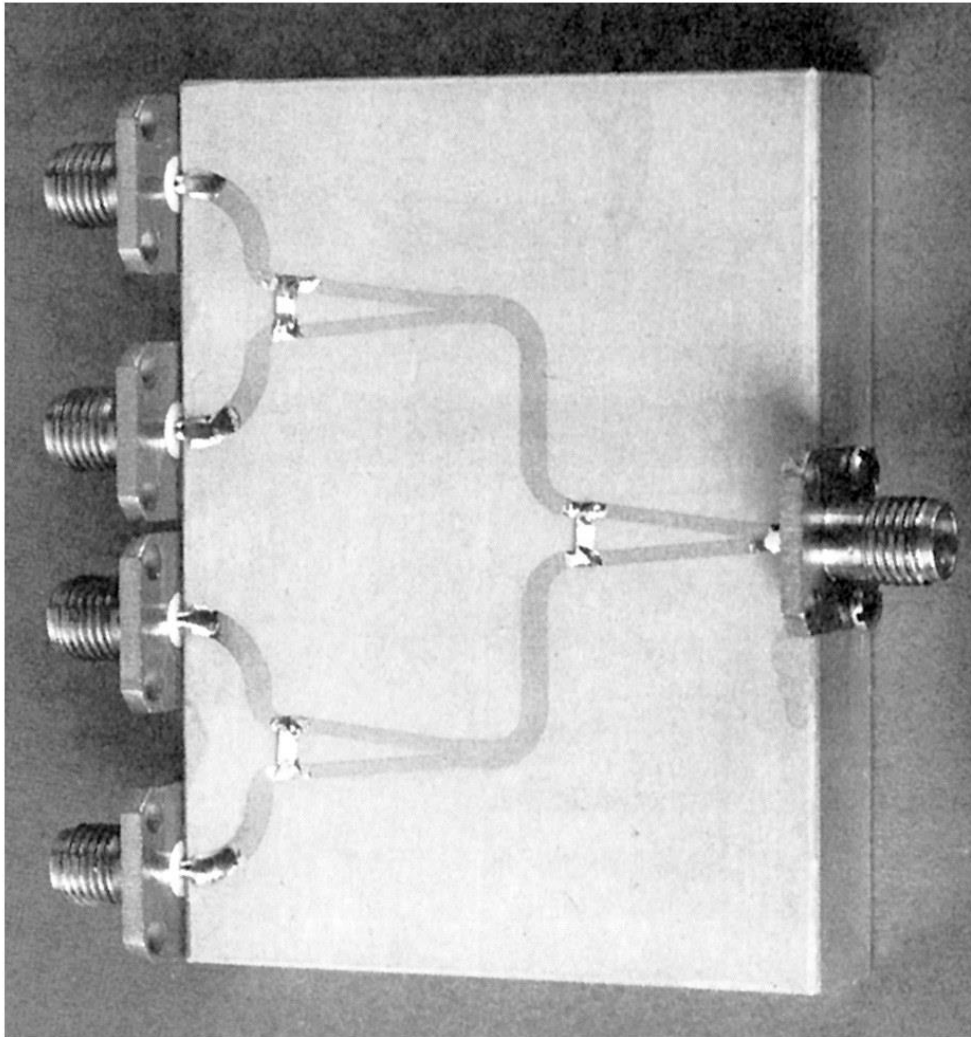

- 3 X Wilkinson = 4-way power divider

Figure 7.15  
Courtesy of M. D. Abouzahra, MIT Lincoln Laboratory, Lexington, Mass.

# The Wilkinson power divider

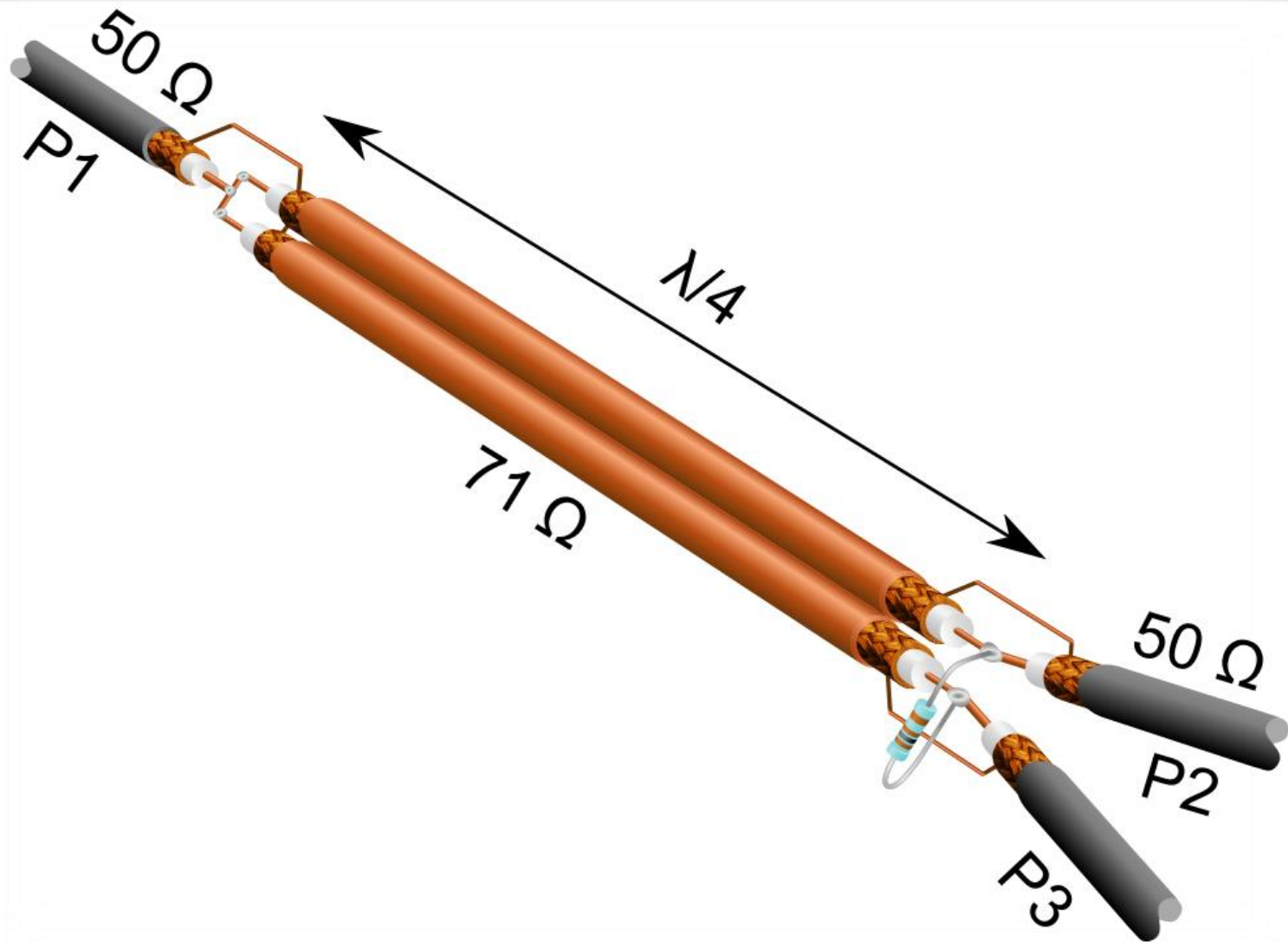


# Directional couplers

# Four-Port Networks

- A four-port network simultaneously:
  - matched at all ports
  - reciprocal
  - lossless
- is **always directional**
  - the signal power injected into one port is transmitted **only towards two** of the other three ports

$$[S] = \begin{bmatrix} 0 & \alpha & \beta \cdot e^{j\theta} & 0 \\ \alpha & 0 & 0 & \beta \cdot e^{j\phi} \\ \beta \cdot e^{j\theta} & 0 & 0 & \alpha \\ 0 & \beta \cdot e^{j\phi} & \alpha & 0 \end{bmatrix}$$

# Directional Coupler

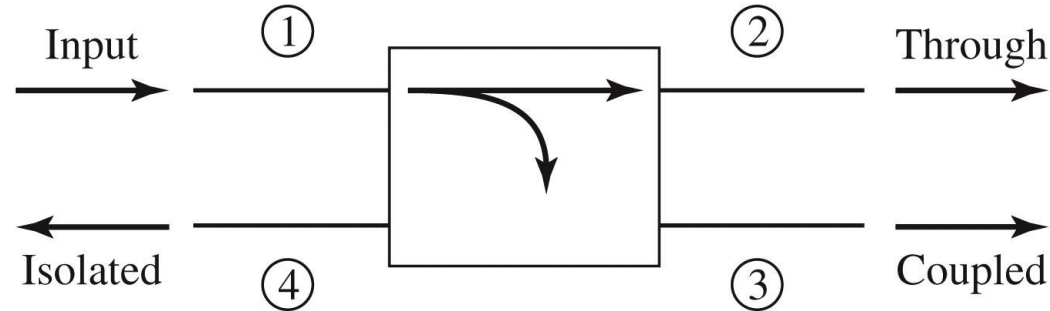

$$|S_{12}|^2 = \alpha^2 = 1 - \beta^2$$

$$|S_{13}|^2 = \beta^2$$

**Coupling**

$$C = 10 \log \frac{P_1}{P_3} = -20 \cdot \log(\beta) [\text{dB}]$$

**Directivity**

$$D = 10 \log \frac{P_3}{P_4} = 20 \cdot \log \left( \frac{\beta}{|S_{14}|} \right) [\text{dB}]$$

**Isolation**

$$I = 10 \log \frac{P_1}{P_4} = -20 \cdot \log |S_{14}| [\text{dB}]$$

$$I = D + C, \quad [\text{dB}]$$

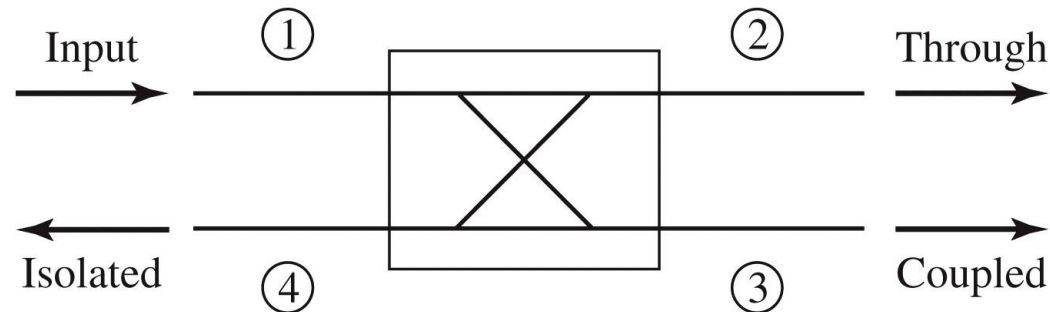


Figure 7.4  
© John Wiley & Sons, Inc. All rights reserved.

# Four-Port Networks

- two particular choices commonly occur in practice
  - A Symmetric Coupler  $\theta = \phi = \pi/2$

$$[S] = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$

- An Antisymmetric Coupler  $\theta = 0, \phi = \pi$

$$[S] = \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$

# Hybrid Couplers

Hybrid Couplers are directional couplers with 3 dB coupling factor

$$\alpha = \beta = 1/\sqrt{2}$$

The quadrature (90°) hybrid

$$(\theta = \phi = \pi/2)$$

$$[S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & j & 0 \\ 1 & 0 & 0 & j \\ j & 0 & 0 & 1 \\ 0 & j & 1 & 0 \end{bmatrix}$$

The 180° ring hybrid (rat-race)

$$(\theta = 0, \phi = \pi)$$

$$[S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$



# The quadrature ( $90^\circ$ ) hybrid


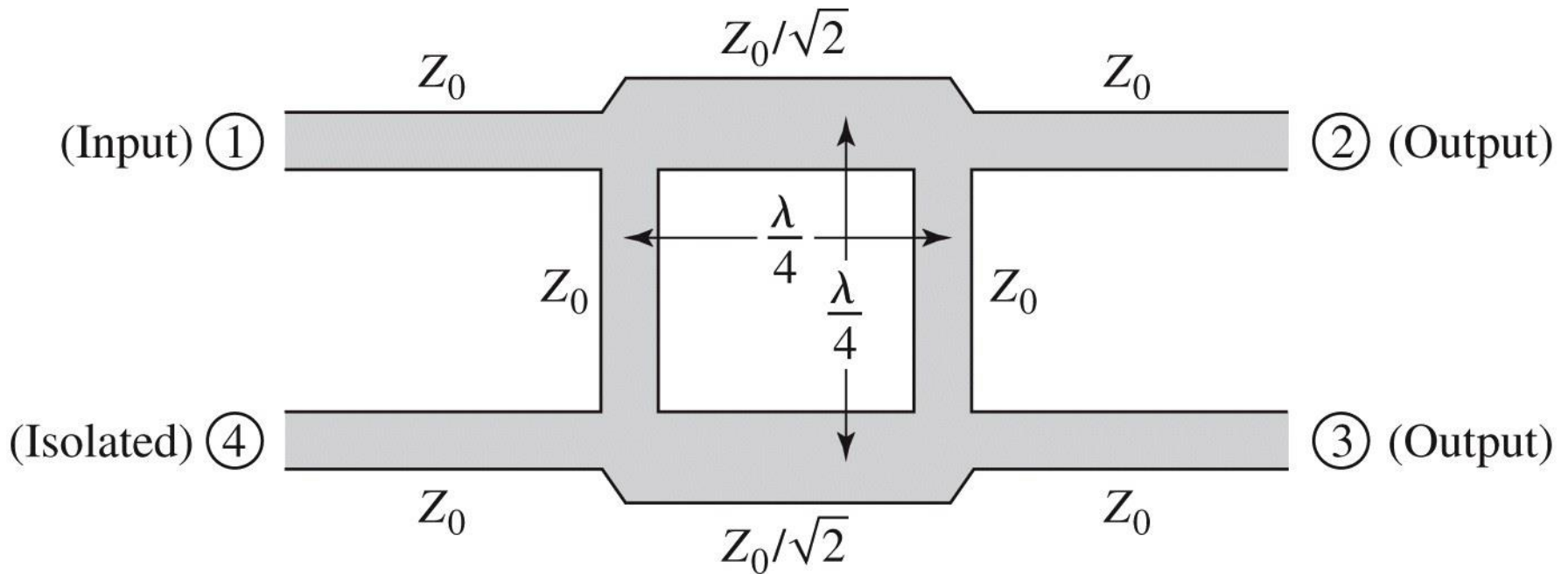



Figure 7.21  
© John Wiley & Sons, Inc. All rights reserved.

$$[S] = \frac{-1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$$


# Even/Odd Mode Analysis

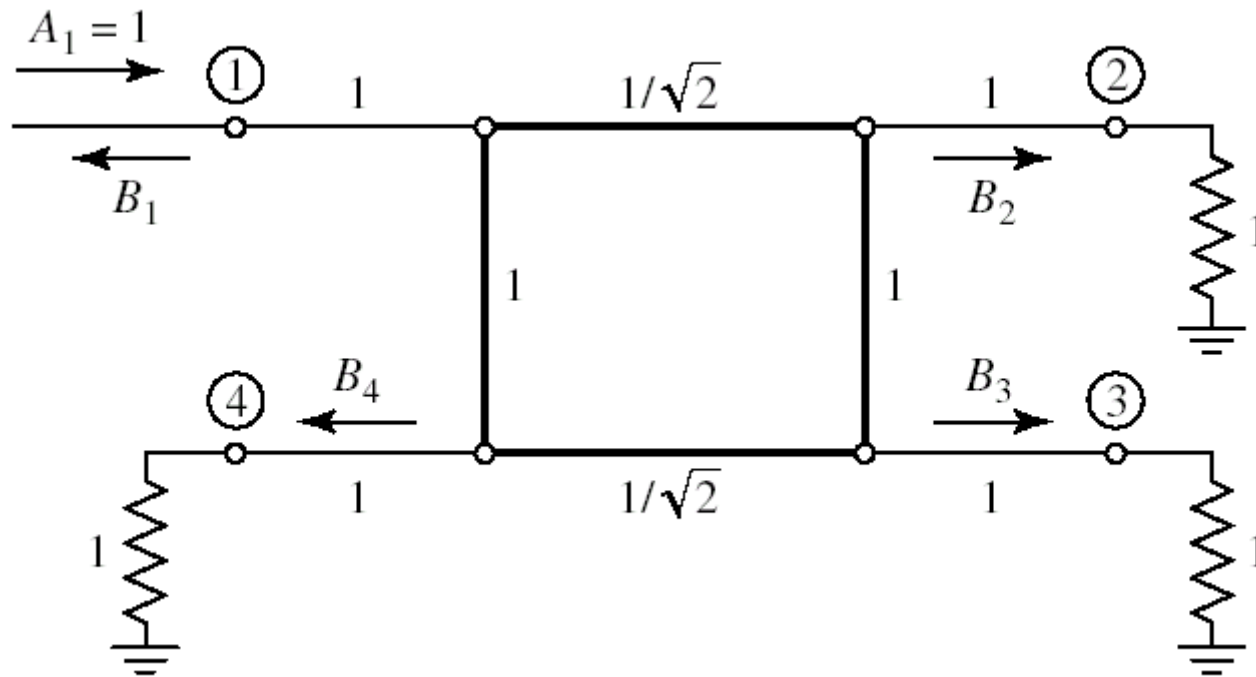

# Even/Odd Mode Analysis

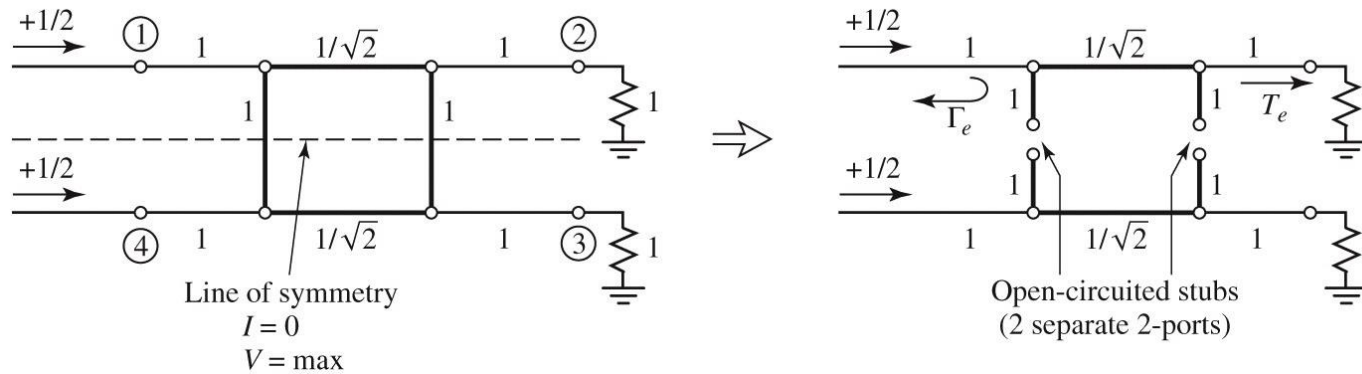

(a)

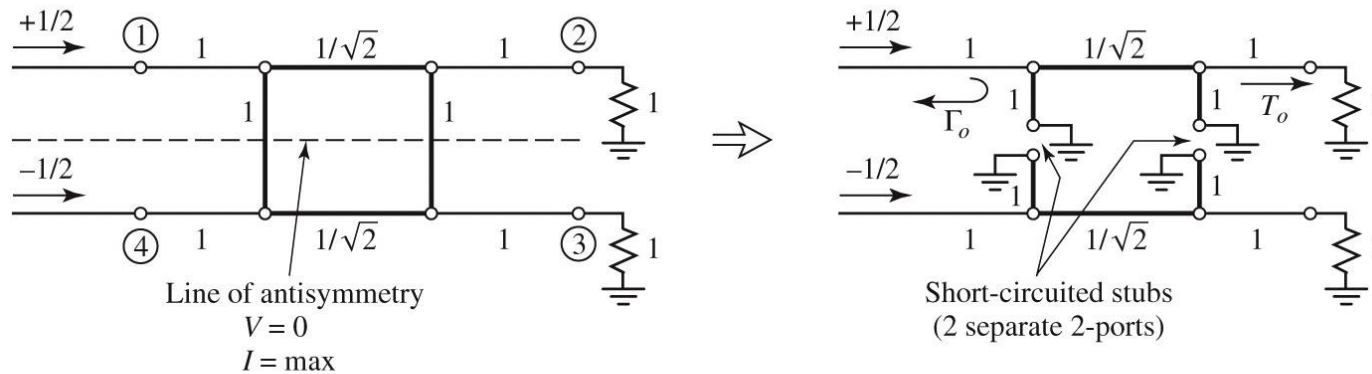

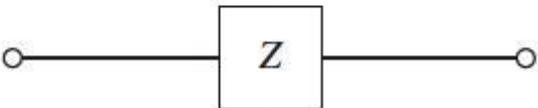
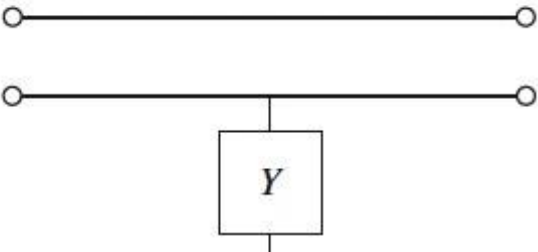
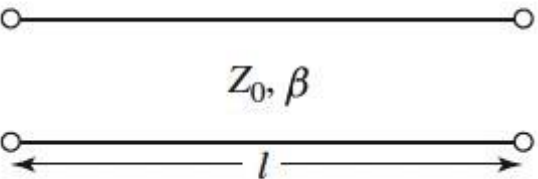
(b)

Figure 7.23  
 © John Wiley & Sons, Inc. All rights reserved.

$$b_1 = \frac{1}{2}\Gamma_e + \frac{1}{2}\Gamma_o \quad b_2 = \frac{1}{2}T_e + \frac{1}{2}T_o \quad b_3 = \frac{1}{2}T_e - \frac{1}{2}T_o \quad b_4 = \frac{1}{2}\Gamma_e - \frac{1}{2}\Gamma_o$$


# Library of ABCD matrices

TABLE 4.1 *ABCD* Parameters of Some Useful Two-Port Circuits


Circuit	<i>ABCD</i> Parameters	
	$A = 1$ $C = 0$	$B = Z$ $D = 1$
	$A = 1$ $C = Y$	$B = 0$ $D = 1$
	$A = \cos \beta l$ $C = jY_0 \sin \beta l$	$B = jZ_0 \sin \beta l$ $D = \cos \beta l$
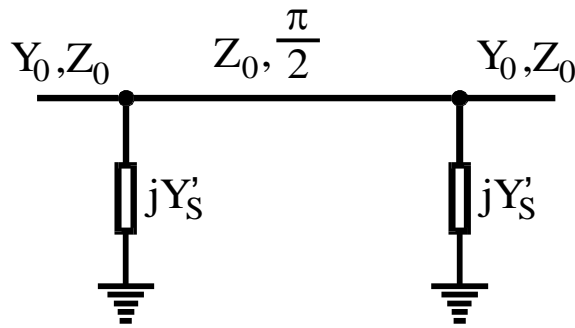
# S parameters (from ABCD)

$$Y'_s = \begin{cases} Y_1 & \text{even mode} \\ -Y_1 & \text{odd mode} \end{cases}$$



a)

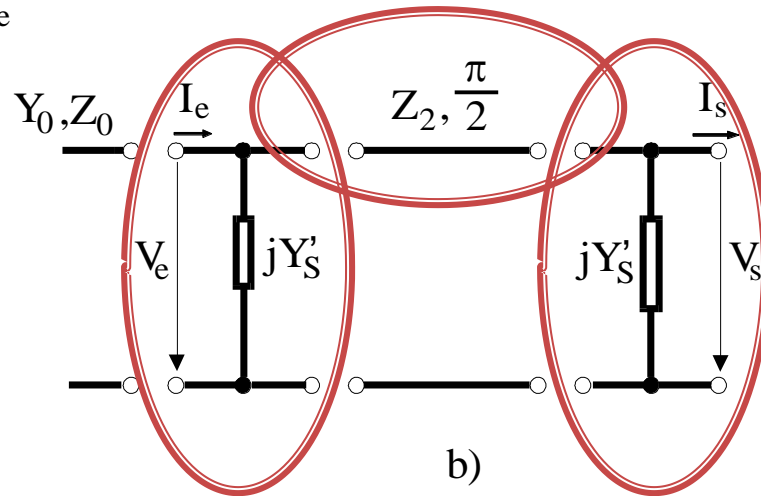

b)

$$\begin{bmatrix} V_e \\ I_e \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ jY'_s & 1 \end{bmatrix} \cdot \begin{bmatrix} 0 & jZ_2 \\ jY_2 & 0 \end{bmatrix} \cdot \begin{bmatrix} 1 & 0 \\ jY'_s & 1 \end{bmatrix} \cdot \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$\begin{bmatrix} V_e \\ I_e \end{bmatrix} = \begin{bmatrix} -Y'_s Z_2 & jZ_2 \\ -jY'^2_s Z_2 + jY_2 & -Y'_s Z_2 \end{bmatrix} \cdot \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$S_{11} = \frac{j\frac{Z_2}{Z_0} - Z_0(-jY'^2_s Z_2 + jY_2)}{-2Y'_s Z_2 + j\frac{Z_2}{Z_0} + Z_0(-jY'^2_s Z_2 + jY_2)}$$

$$S_{12} = \frac{2|(-Y'_s Z_2)^2 - jZ_2(-jY'^2_s Z_2 + jY_2)|}{-2Y'_s Z_2 + j\frac{Z_2}{Z_0} + Z_0(-jY'^2_s Z_2 + jY_2)}$$

$$\Gamma = S_{11} = \frac{j(z_2 - y_2 + y'^2_s z_2)}{-2y'_s z_2 + j(z_2 + y_2 - y'^2_s z_2)} = S_{22}$$

$$S_{21} = \frac{2}{-2Y'_s Z_2 + j\frac{Z_2}{Z_0} + Z_0(-jY'^2_s Z_2 + jY_2)}$$

$$S_{22} = \frac{j\frac{Z_2}{Z_0} - Z_0(-jY'^2_s Z_2 + jY_2)}{-2Y'_s Z_2 + j\frac{Z_2}{Z_0} + Z_0(-jY'^2_s Z_2 + jY_2)}$$

$$T = S_{21} = \frac{2}{-2y'_s z_2 + j(z_2 + y_2 - y'^2_s z_2)} = S_{12}$$

# Relation between two port S parameters and ABCD parameters

$$A = \sqrt{\frac{Z_{01}}{Z_{02}}} \frac{(1 + S_{11} - S_{22} - \Delta S)}{2S_{21}}$$

$$B = \sqrt{Z_{01}Z_{02}} \frac{(1 + S_{11} + S_{22} + \Delta S)}{2S_{21}}$$

$$C = \frac{1}{\sqrt{Z_{01}Z_{02}}} \frac{1 - S_{11} - S_{22} + \Delta S}{2S_{21}}$$

$$D = \sqrt{\frac{Z_{02}}{Z_{01}}} \frac{1 - S_{11} + S_{22} - \Delta S}{2S_{21}}$$

$$\Delta S = S_{11}S_{22} - S_{12}S_{21}$$

$$S_{11} = \frac{AZ_{02} + B - CZ_{01}Z_{02} - DZ_{01}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

$$S_{12} = \frac{2(AD - BC)\sqrt{Z_{01}Z_{02}}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

$$S_{21} = \frac{2\sqrt{Z_{01}Z_{02}}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

$$S_{22} = \frac{-AZ_{02} + B - CZ_{01}Z_{02} + DZ_{01}}{AZ_{02} + B + CZ_{01}Z_{02} + DZ_{01}}$$

# Matching and coupling factor

$$\Gamma_e = \frac{j \cdot (z_2 - y_2 + y_1^2 z_2)}{-2y_1 z_2 + j(z_2 + y_2 - y_1^2 z_2)}$$

$$\Gamma_o = \frac{j \cdot (z_2 - y_2 + y_1^2 z_2)}{2y_1 z_2 + j(z_2 + y_2 - y_1^2 z_2)}$$

$$T_e = \frac{2}{-2y_1 z_2 + j(z_2 + y_2 - y_1^2 z_2)}$$

$$T_o = \frac{2}{2y_1 z_2 + j(z_2 + y_2 - y_1^2 z_2)}$$

$$b_1 = \frac{\Gamma_e + \Gamma_o}{2} = \frac{z_2^2 - (y_2 - y_1^2 z_2)^2}{(2y_1 z_2)^2 + (z_2 + y_2 - y_1^2 z_2)^2}$$

$$b_2 = \frac{T_e + T_o}{2} = \frac{-2j(z_2 + y_2 - y_1^2 z_2)}{(2y_1 z_2)^2 + (z_2 + y_2 - y_1^2 z_2)^2}$$

$$b_3 = \frac{T_e - T_o}{2} = \frac{-4y_1 z_2}{(2y_1 z_2)^2 + (z_2 + y_2 - y_1^2 z_2)^2}$$

$$b_4 = \frac{\Gamma_e - \Gamma_o}{2} = \frac{-2jy_1 z_2 (z_2 - y_2 + y_1^2 z_2)}{(2y_1 z_2)^2 + (z_2 + y_2 - y_1^2 z_2)^2}$$

$$b_1 = 0 \Rightarrow z_2 - y_2 + y_1^2 z_2 = 0 \Rightarrow z_2^2 = \frac{1}{1 + y_1^2}$$

$$y_2^2 = 1 + y_1^2$$

$$C = 10 \log \frac{P_1}{P_3} = -20 \log |b_3|, \text{ dB}$$

$$b_1 = 0 \quad b_4 = 0 \quad b_3 = -y_1 z_2 \quad b_2 = -j z_2$$

$$b_3 = -\frac{\sqrt{y_2^2 - 1}}{y_2}, \quad b_2 = -\frac{j}{y_2}$$

$$\beta = \frac{\sqrt{y_2^2 - 1}}{y_2}$$

$$b_3 = -C$$

$$b_2 = -j\sqrt{1 - C^2}$$

$$[S] = \begin{bmatrix} 0 & -j\sqrt{1 - C^2} & -C & 0 \\ -j\sqrt{1 - C^2} & 0 & 0 & -C \\ -C & 0 & 0 & -j\sqrt{1 - C^2} \\ 0 & -C & -j\sqrt{1 - C^2} & 0 \end{bmatrix}$$

# The quadrature (90°) hybrid

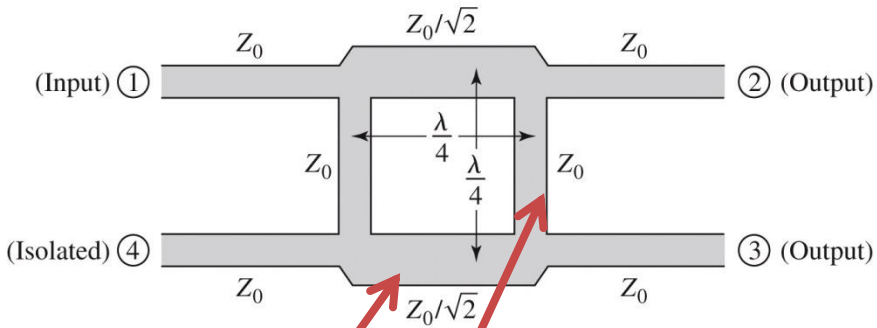


Figure 7.21  
© John Wiley & Sons, Inc. All rights reserved.

$$y_2^2 = 1 + y_1^2$$

$$|\beta| = \frac{\sqrt{y_2^2 - 1}}{y_2}$$

$$C[\text{dB}] = -20 \cdot \log_{10} \frac{\sqrt{y_2^2 - 1}}{y_2}$$

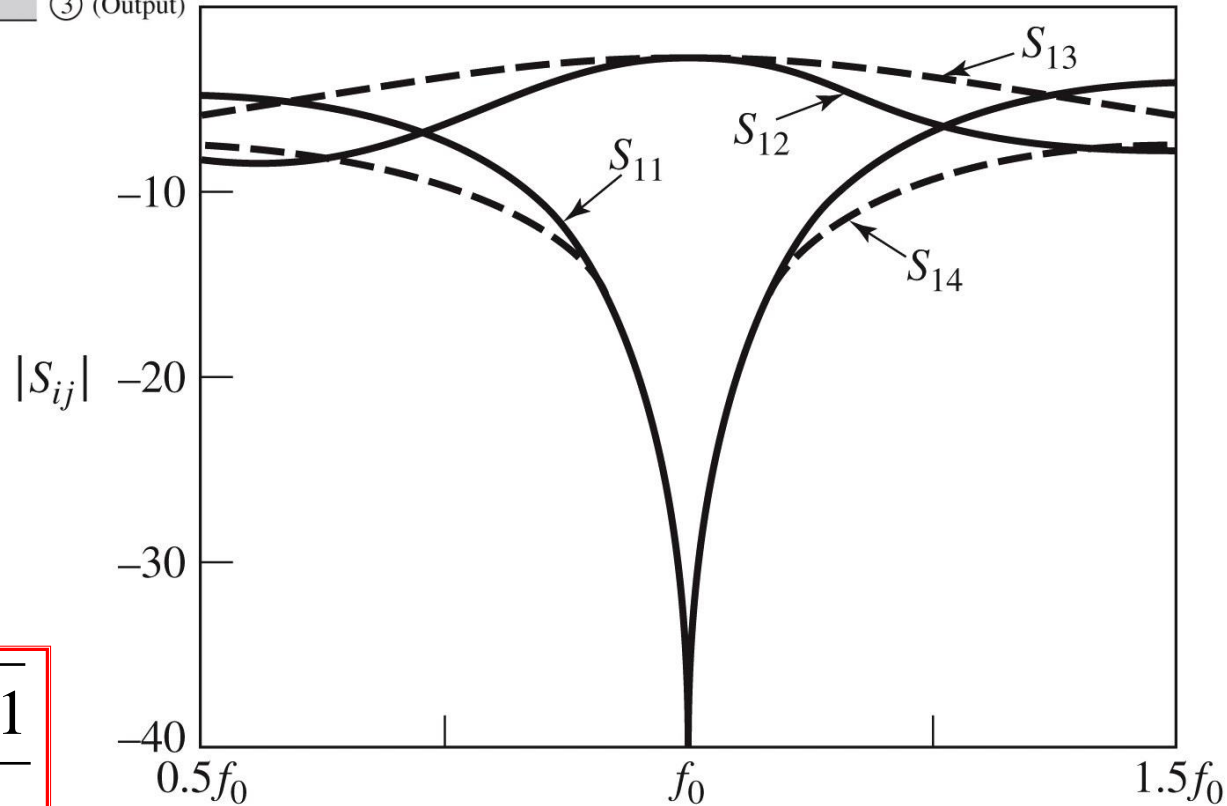


Figure 7.25  
© John Wiley & Sons, Inc. All rights reserved.



# Example

Design a quadrature ( $90^\circ$ ) hybrid working on  $50 \Omega$ , and plot the S parameters between

$0.5f_0$  and  $1.5f_0$ , where  $f_0$

is the frequency at which the length of the branches is  $\lambda/4$



# Solution

A quadrature ( $90^\circ$ ) hybrid has  $C = 3\text{dB}$ , then  $\beta = 1/\sqrt{2}$


$$y_2 = \sqrt{2} \quad \text{and} \quad y_1 = 1$$

$Z_0 = 50\Omega$  the characteristic impedances will be:
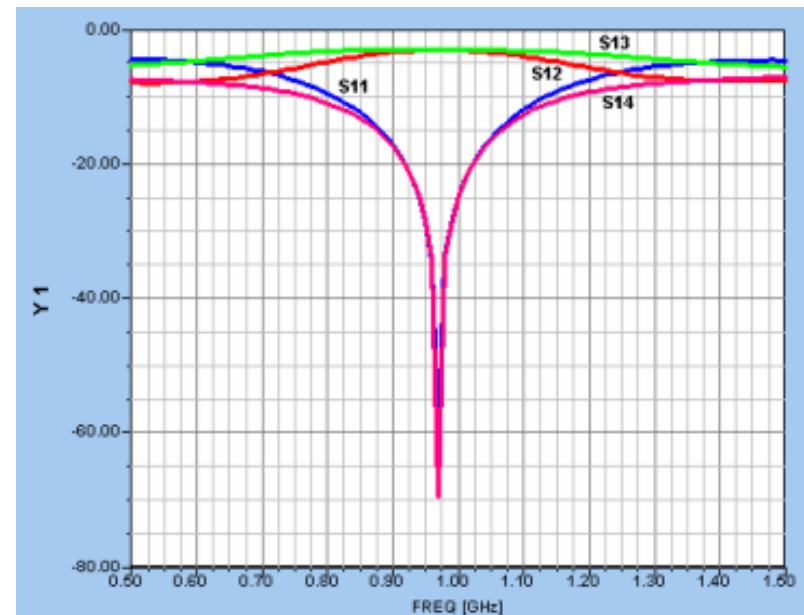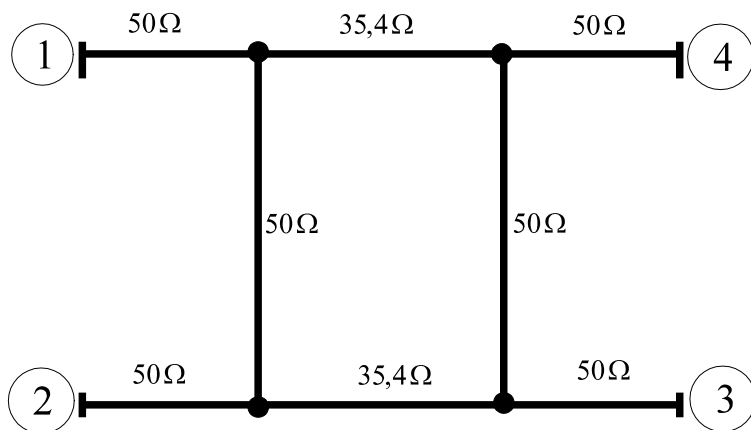
$$Z_1 = Z_0 = 50\Omega \quad Z_2 = \frac{Z_0}{\sqrt{2}} = 35.4\Omega$$



# The quadrature ( $90^\circ$ ) hybrid

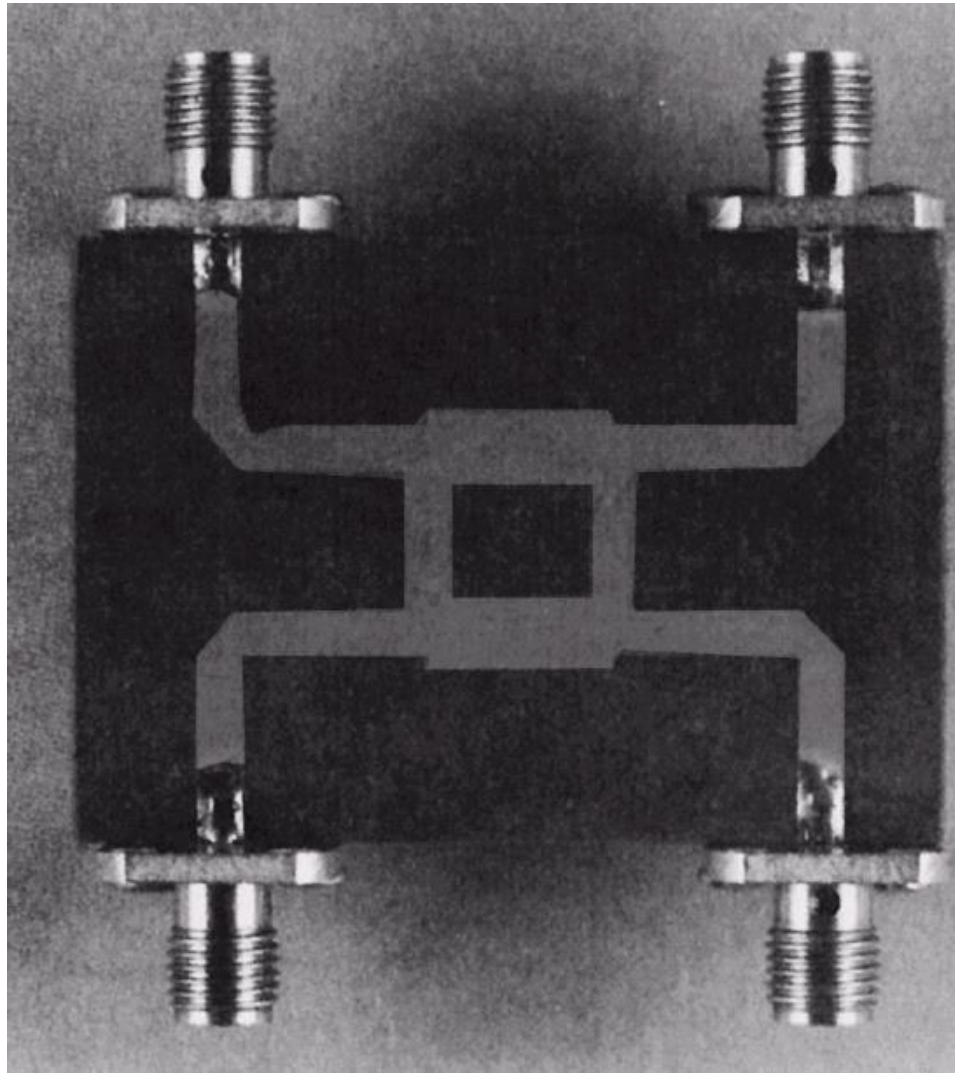

# The quadrature ( $90^\circ$ ) hybrid

- eight-way microstrip power divider with six quadrature hybrids in a Bailey configuration


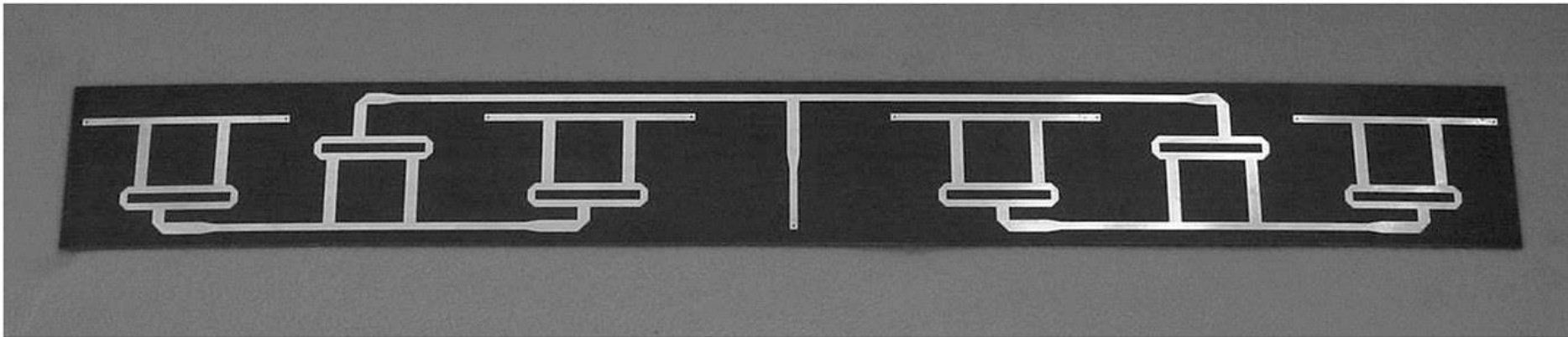



Figure 7.24  
Courtesy of ProSensing, Inc., Amherst, Mass.

# Datasheet

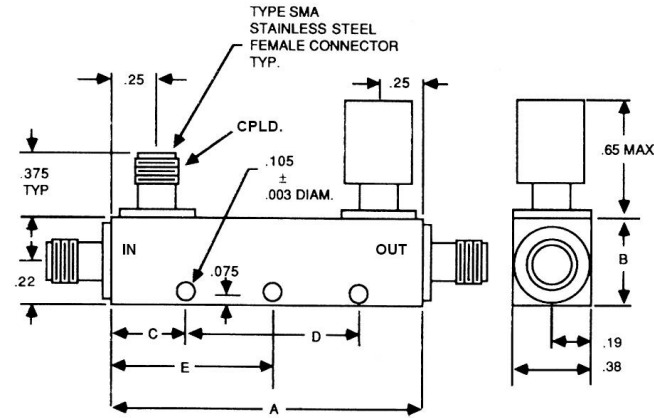

Model No.	Frequency Range (Ghz)	Coupling † (dB)	Freq. Sens. (dB)	Insertion Loss (dB)		Directivity (dB min.)	VSWR max.	
				Excl. Cpld Pwr	True		Primary Line	Secondary Line
MDC6223-6	0.5-1.0	6 ±1.00	±0.60	0.20	1.80	25	1.15	1.15
MDC6223-10	0.5-1.0	10 ±1.25	±0.75	0.20	0.80	25	1.10	1.10
MDC6223-20	0.5-1.0	20 ±1.25	±0.75	0.15	0.20	25	1.10	1.10
MDC6223-30	0.5-1.0	30 ±1.25	±0.75	0.15	0.20	25	1.10	1.10
MDC6224-6	1.0-2.0	6 ±1.00	±0.60	0.20	1.80	25	1.15	1.15
MDC6224-10	1.0-2.0	10 ±1.25	±0.75	0.20	0.80	25	1.10	1.10
MDC6224-20	1.0-2.0	20 ±1.25	±0.75	0.15	0.20	25	1.10	1.10
MDC6224-30	1.0-2.0	30 ±1.25	±0.75	0.15	0.20	25	1.10	1.10
MDC6225-6	2.0-4.0	6 ±1.00	±0.60	0.20	1.80	22	1.15	1.15
MDC6225-10	2.0-4.0	10 ±1.25	±0.75	0.20	0.80	22	1.15	1.15
MDC6225-20	2.0-4.0	20 ±1.25	±0.75	0.15	0.20	22	1.15	1.15
MDC6225-30	2.0-4.0	30 ±1.25	±0.75	0.15	0.20	22	1.15	1.15
MDC6266-6	2.6-5.2	6 ±1.00	±0.60	0.20	1.80	20	1.25	1.25
MDC6266-10	2.6-5.2	10 ±1.25	±0.75	0.20	0.80	20	1.25	1.25
MDC6266-20	2.6-5.2	20 ±1.25	±0.75	0.20	0.25	20	1.25	1.25
MDC6266-30	2.6-5.2	30 ±1.25	±0.75	0.20	0.20	20	1.25	1.25
MDC6226-6	4.0-8.0	6 ±1.00	±0.60	0.25	1.90	20	1.25	1.25
MDC6226-10	4.0-8.0	10 ±1.25	±0.75	0.25	0.90	20	1.25	1.25
MDC6226-20	4.0-8.0	20 ±1.25	±0.75	0.25	0.30	20	1.25	1.25
MDC6226-30	4.0-8.0	30 ±1.25	±0.75	0.25	0.25	20	1.25	1.25
MDC6227-6	7.0-12.4	6 ±1.00	±0.50	0.30	2.00	17	1.30	1.30
MDC6227-10	7.0-12.4	10 ±1.00	±0.50	0.30	1.00	17	1.30	1.30
MDC6227-20	7.0-12.4	20 ±1.00	±0.50	0.30	0.35	17	1.30	1.30
MDC6227-30	7.0-12.4	30 ±1.00	±0.50	0.30	0.20	17	1.30	1.30

# The $180^\circ$ ring hybrid (rat-race)

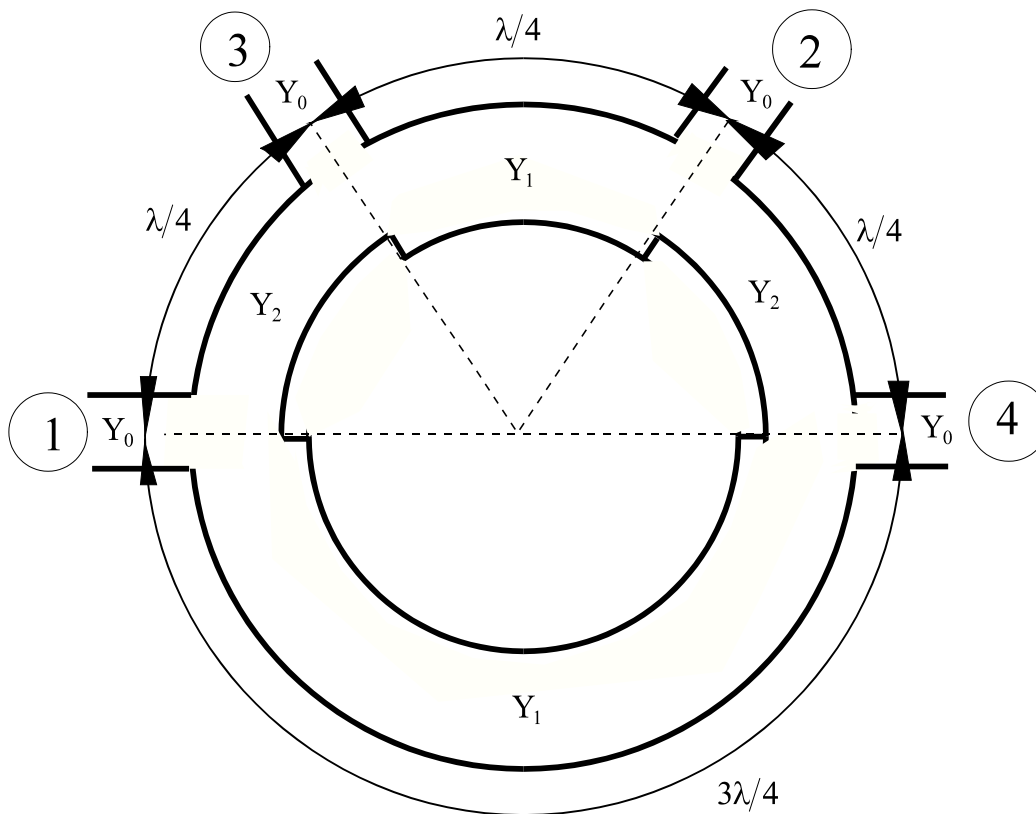

# The $180^\circ$ ring hybrid


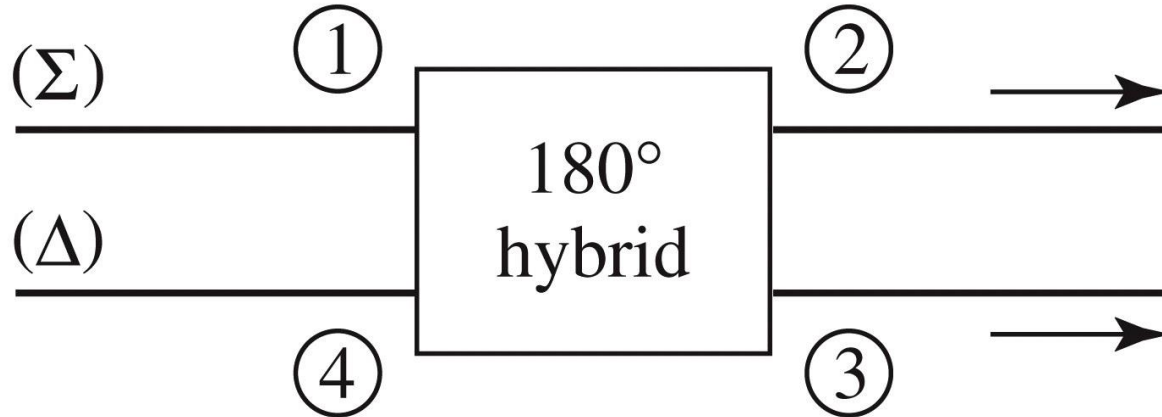



Figure 7.41  
© John Wiley & Sons, Inc. All rights reserved.

- The  $180^\circ$  ring hybrid can be operated in different modes:
  - a signal applied to port 1 will be evenly split into two in-phase components at ports 2 and 3
  - input applied to port 4 it will be equally split into two components with a  $180^\circ$  phase difference at ports 2 and 3
  - input signals applied at ports 2 and 3, the sum of the inputs will be formed at port 1, while the difference will be formed at port 4 (power combiner)

# Even/Odd Mode Analysis

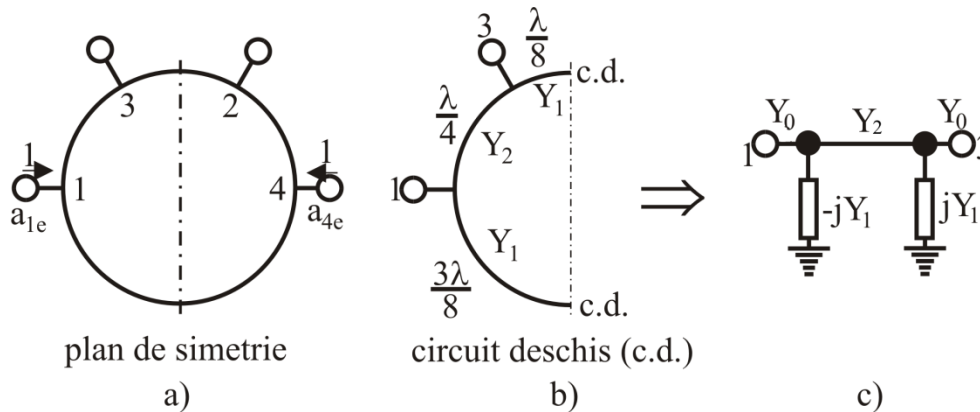

## Even Mode

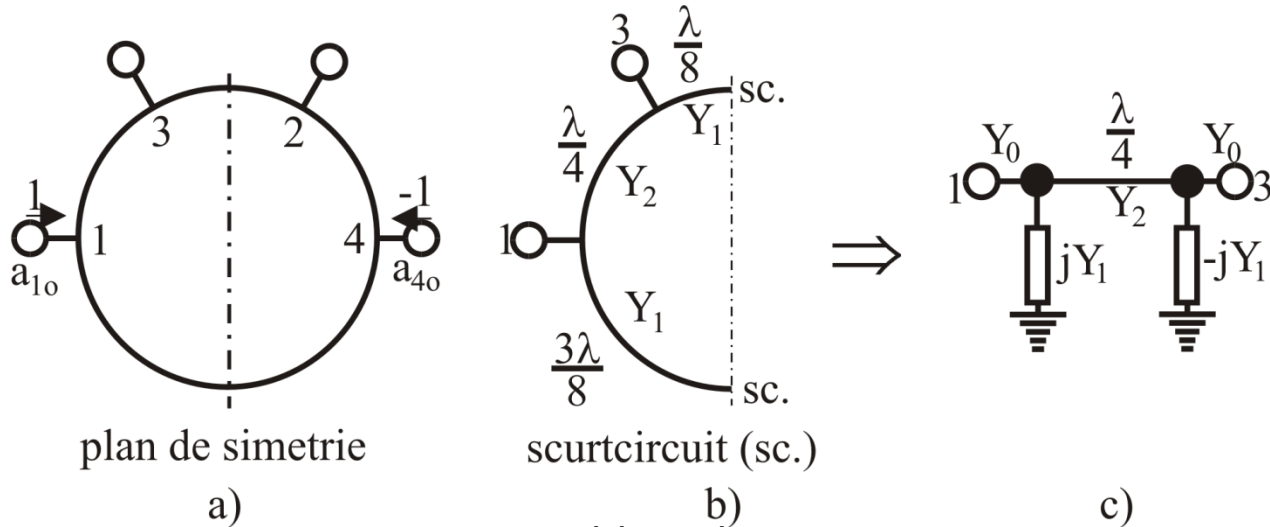

## Odd Mode



# Even/Odd Mode Analysis

$$S_{11} = \frac{jz_2 y_s + jz_2 - j(y_2 + y_e y_s z_2) - j y_e z_2}{jz_2 y_s + jz_2 + j(y_2 + y_e y_s z_2) + j y_e z_2}$$

$$S_{12} = \frac{2}{jz_2 y_s + jz_2 + j(y_2 + y_e y_s z_2) + j y_e z_2}$$

**Even mode:**


$$y_e = -jy_1$$

$$y_s = jy_1$$

$$S_{11e} = \frac{z_2 - y_2 - y_1^2 z_2 + 2jz_2 y_1}{z_2 + y_2 + y_1^2 z_2}$$

$$S_{12e} = S_{21e} = \frac{-2j}{z_2 + y_2 + y_1^2 z_2}$$
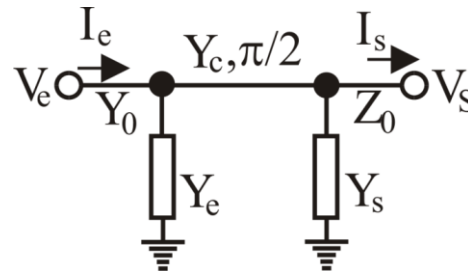
$$S_{22e} = \frac{z_2 - y_2 - y_1^2 z_2 - 2jz_2 y_1}{z_2 + y_2 + y_1^2 z_2}$$



**Matching condition**

$$y_1^2 + y_2^2 = 1$$

$$[S] = \begin{bmatrix} 0 & 0 & -jy_2 & jy_1 \\ 0 & 0 & -jy_1 & -jy_2 \\ -jy_2 & -jy_1 & 0 & 0 \\ jy_1 & -jy_2 & 0 & 0 \end{bmatrix}$$

$$S_{21} = \frac{2}{jz_2 y_s + jz_2 + j(y_2 + y_e y_s z_2) + j y_e z_2}$$

$$S_{22} = \frac{-jz_2 y_s + jz_2 - j(y_2 + y_e y_s z_2) + j y_e z_2}{jz_2 y_s + jz_2 + j(y_2 + y_e y_s z_2) + j y_e z_2}$$

**Odd mode:**

$$y_e = jy_1$$


$$y_s = -jy_1$$

$$S_{11o} = \frac{z_2 - y_2 - y_1^2 z_2 - 2jz_2 y_1}{z_2 + y_2 + y_1^2 z_2}$$

$$S_{12o} = S_{21o} = \frac{-2j}{z_2 + y_2 + y_1^2 z_2}$$

$$S_{22o} = \frac{z_2 - y_2 - y_1^2 z_2 + 2jz_2 y_1}{z_2 + y_2 + y_1^2 z_2}$$

# The 180° ring hybrid

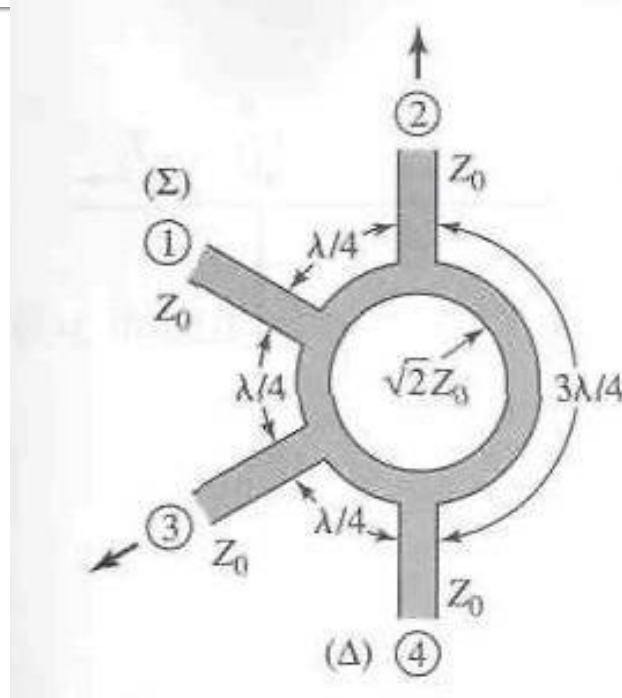

$$[S] = \begin{bmatrix} 0 & -jy_2 & -jy_1 & 0 \\ -jy_2 & 0 & 0 & jy_1 \\ -jy_1 & 0 & 0 & -jy_2 \\ 0 & jy_1 & -jy_2 & 0 \end{bmatrix} = -j \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$

$$C(dB) = -20 \log(\beta) = -20 \log(y_1)$$

# Example

Design a ring ( $180^\circ$ ) hybrid working on  $50 \Omega$ , and plot the S parameters between 0.5 and 1.5 of the design frequency.

$$C [\text{dB}] = -20 \log(y_1)$$

$$\sqrt{2}Z_0 = 70.7 \Omega$$


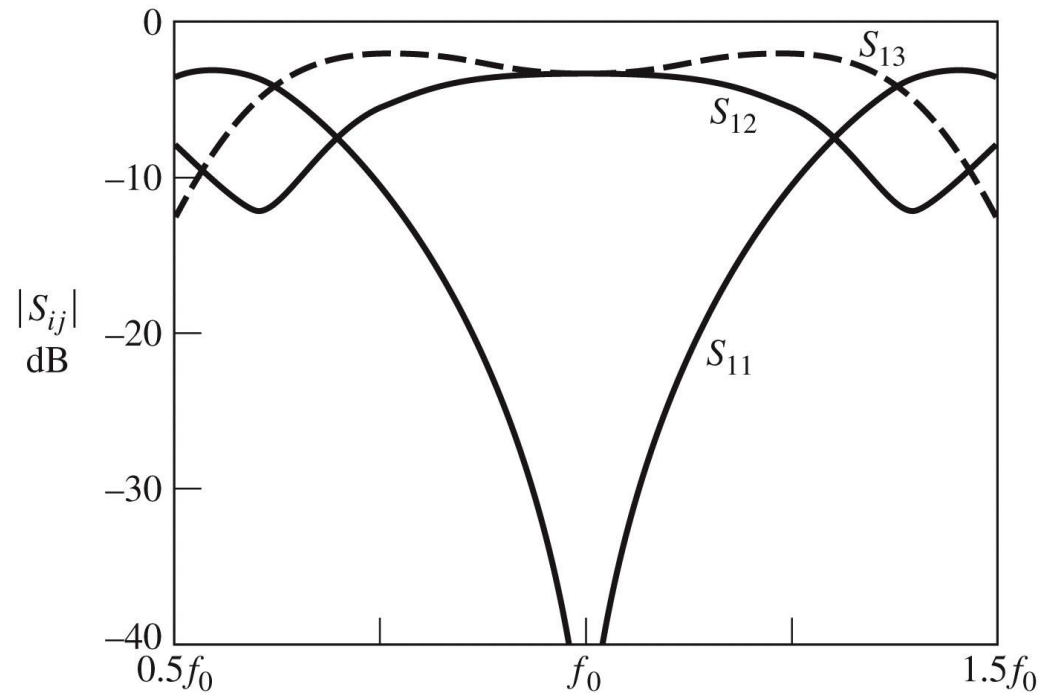


Figure 7.46  
© John Wiley & Sons, Inc. All rights reserved.

# The 180° ring hybrid

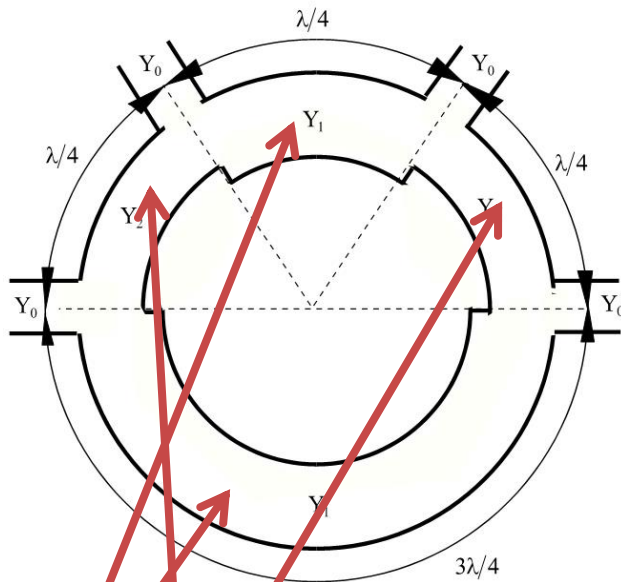

$$y_1^2 + y_2^2 = 1$$

$$|\beta| = y_1$$

$$C \text{ [dB]} = -20 \cdot \log_{10}(y_1)$$

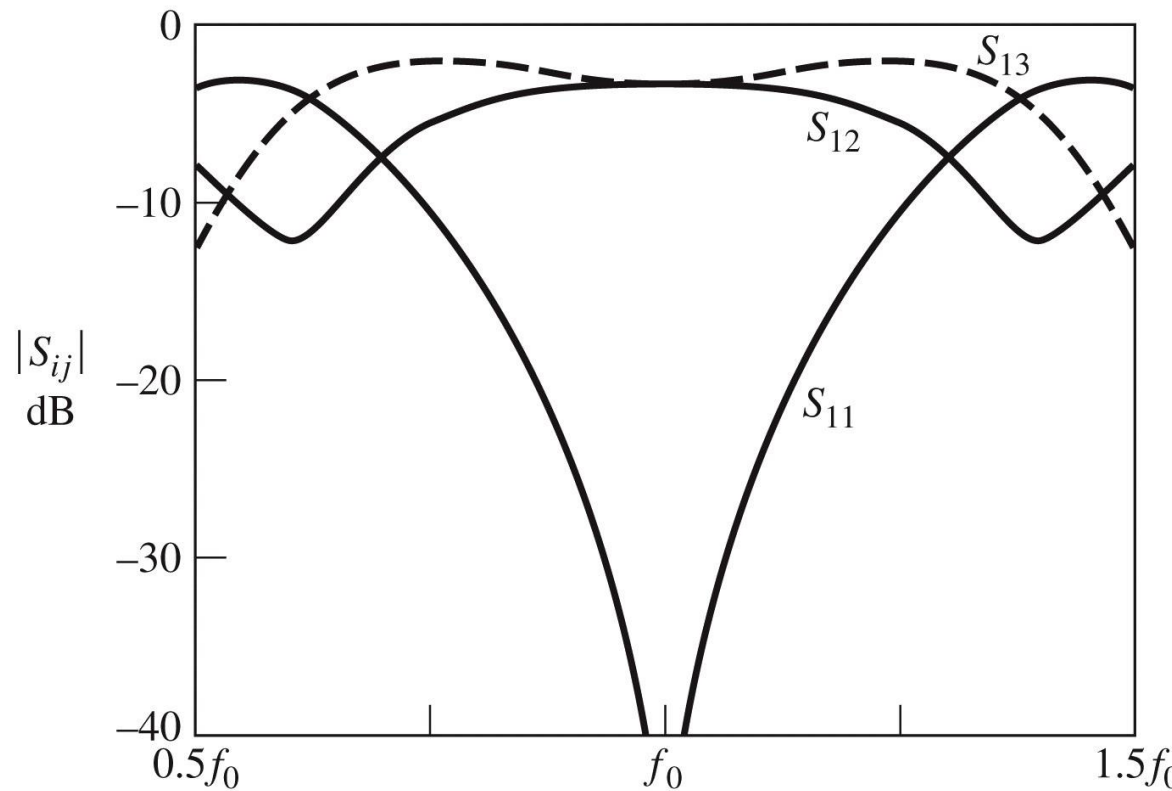


Figure 7.46  
© John Wiley & Sons, Inc. All rights reserved.

# The $180^\circ$ ring hybrid


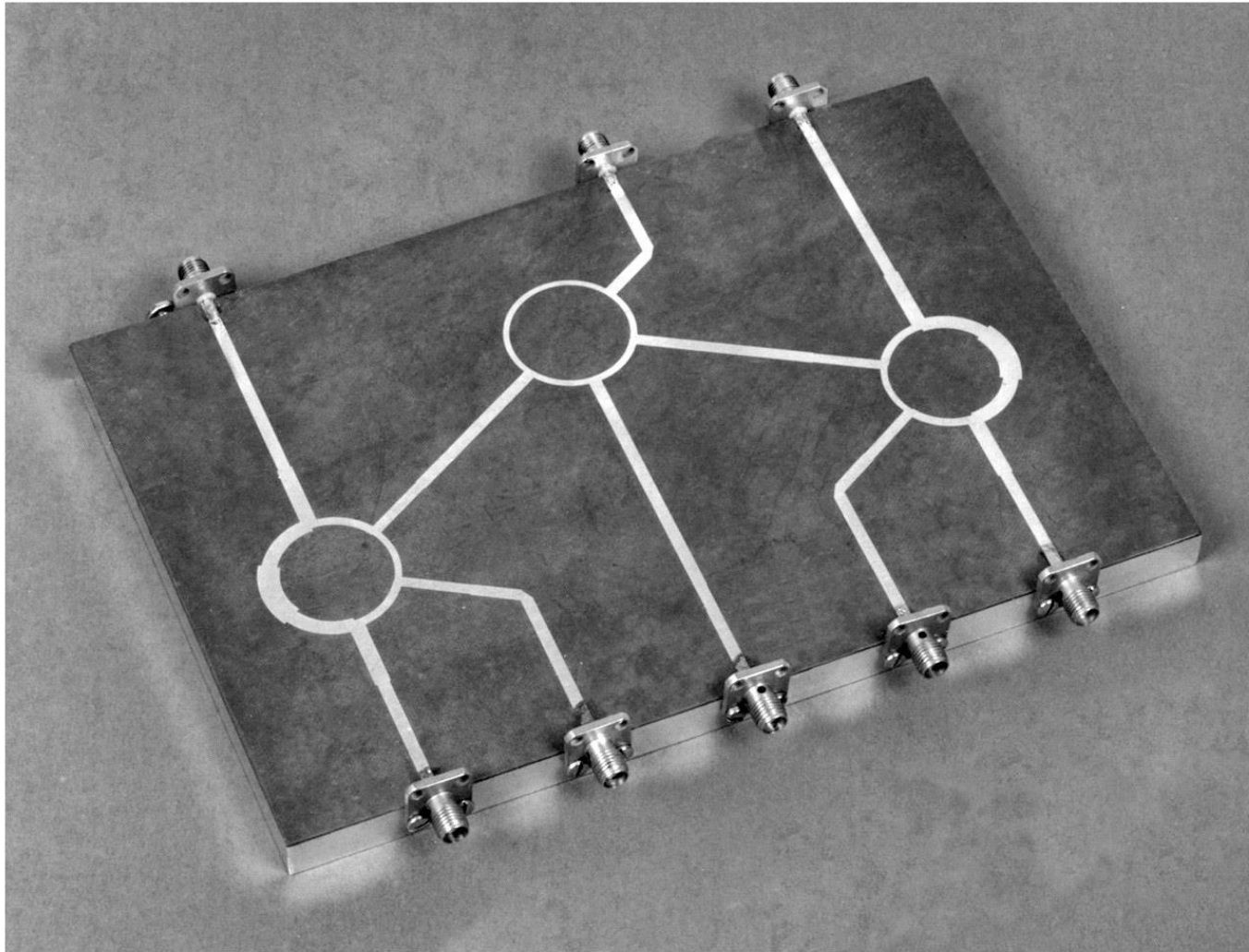


Figure 7.43  
Courtesy of M. D. Abouzahra, MIT Lincoln Laboratory, Lexington, Mass.

# Coupled Line Coupler

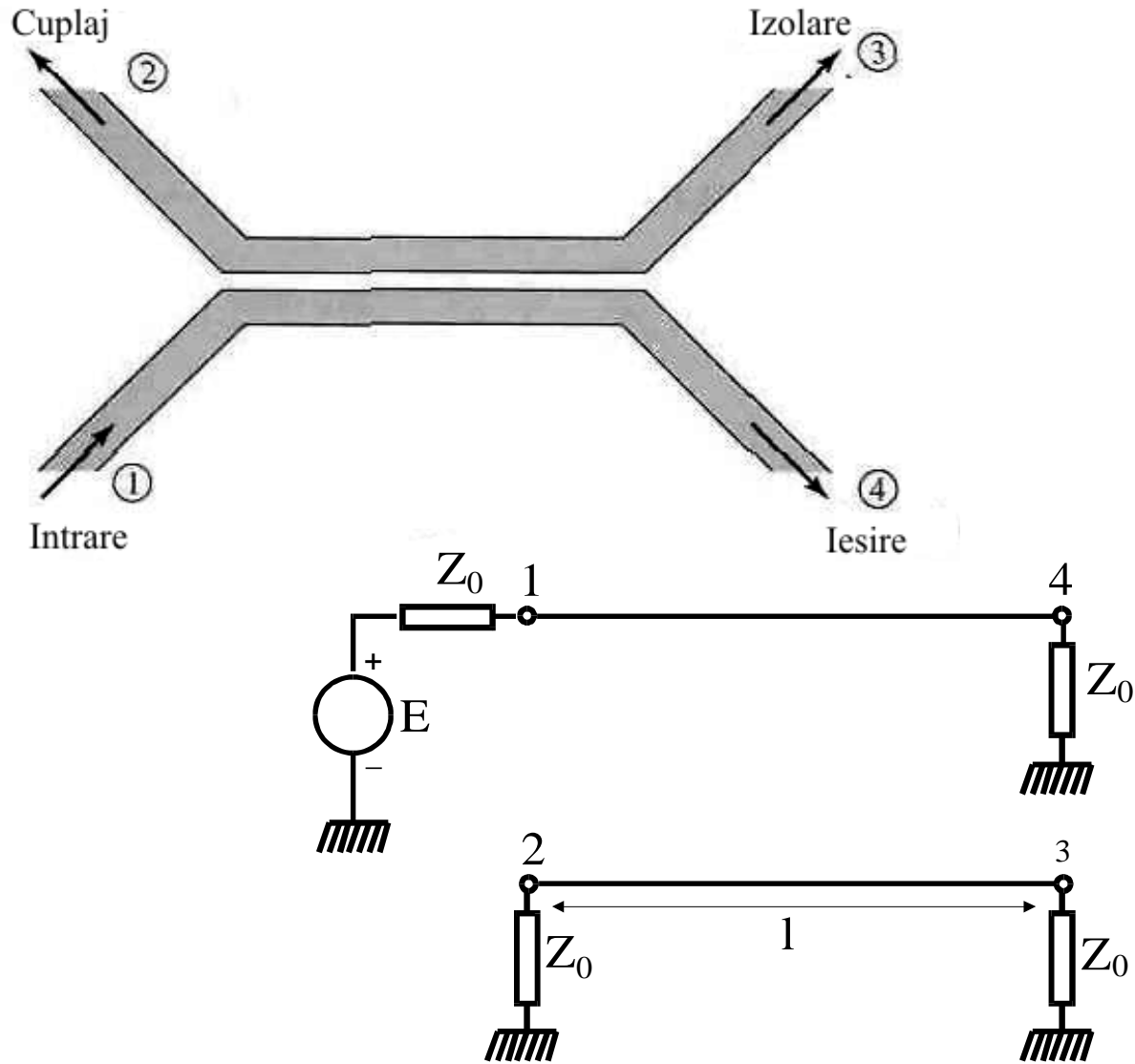

# Coupled Lines



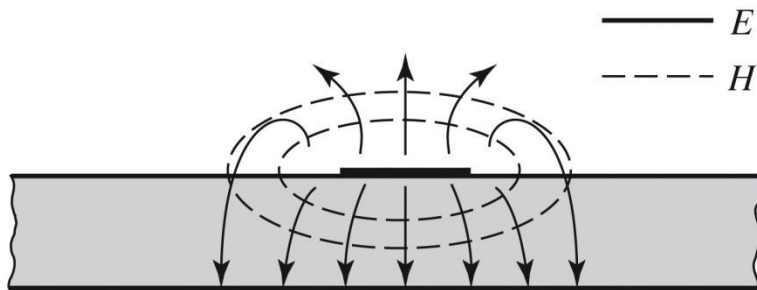


Figure 3.25b  
© John Wiley & Sons, Inc. All rights reserved.

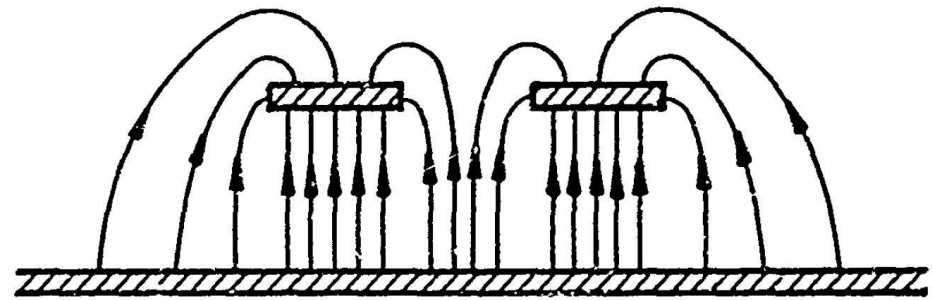

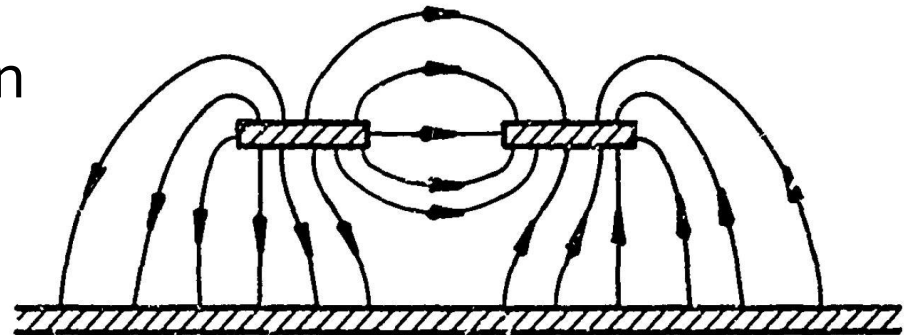b) EVEN MODE ELECTRIC FIELD PATTERN (SCHEMATIC)



c) ODD MODE ELECTRIC FIELD PATTERN (SCHEMATIC)

- Even mode - characterizes the common mode signal on the two lines
- Odd mode - characterizes the differential mode signal between the two lines
- Each of the two modes is characterized by **different** characteristic impedances

# Coupled Lines

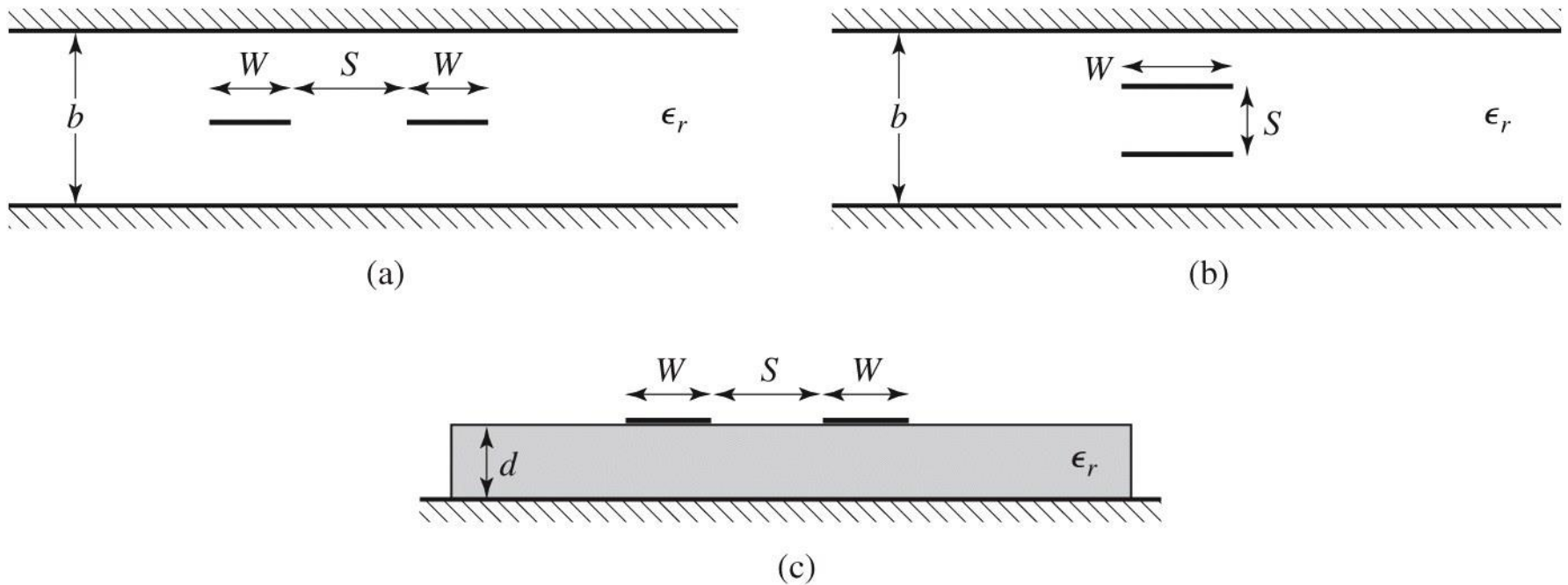






Figure 7.26  
© John Wiley & Sons, Inc. All rights reserved.




# Coupled Lines



Figure 7.27  
© John Wiley & Sons, Inc. All rights reserved.

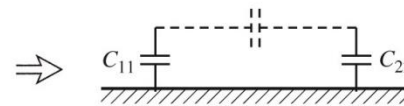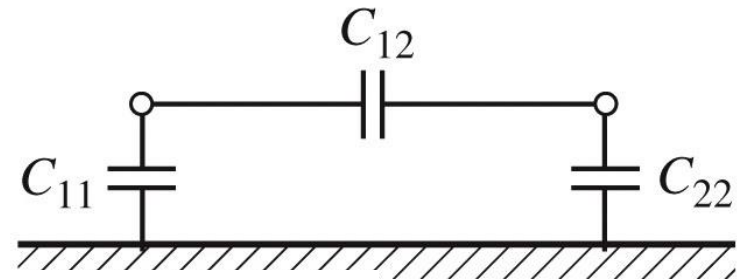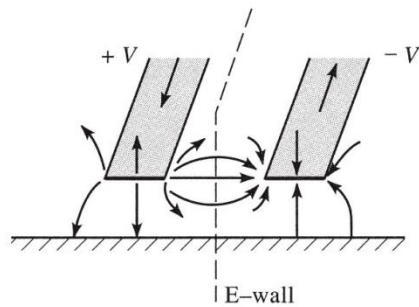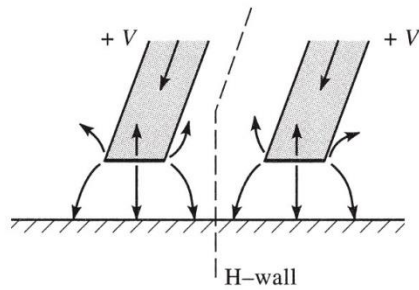


(a)

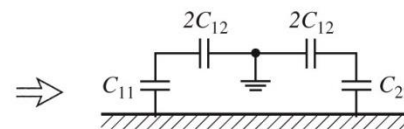

(b)


Figure 7.28  
© John Wiley & Sons, Inc. All rights reserved.

# Matching in Coupled Line Coupler

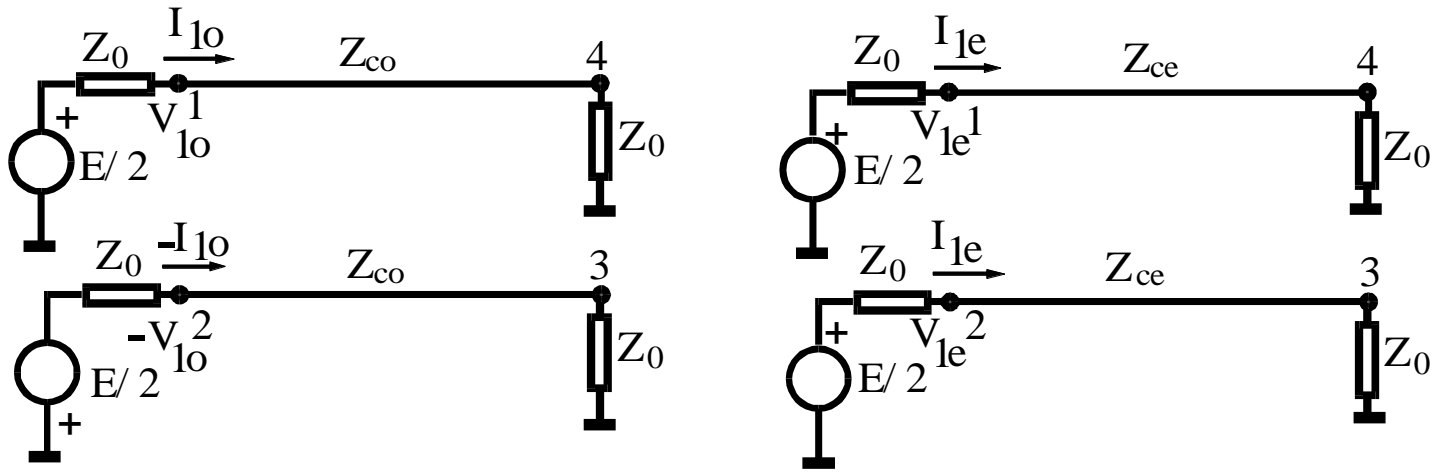


$$\begin{cases} Z_{ce}Z_{co} = Z_0^2 \\ \theta_e = \theta_o \end{cases}$$

# Directivity and Coupling factor

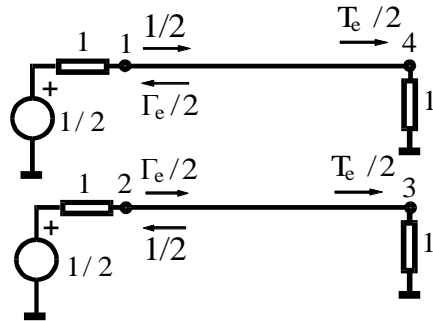

modul par

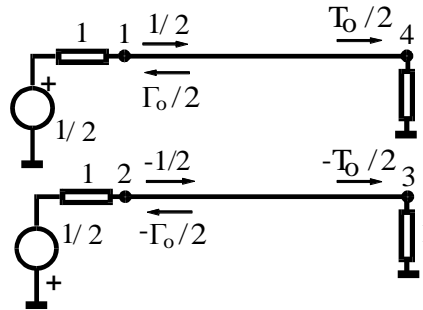

modul impar

$$a_1 = a_{1e} + a_{1o} = 1, \quad a_2 = a_3 = a_4 = 0$$

$$b_1 = \frac{1}{2}(\Gamma_e + \Gamma_o) = 0 \Leftrightarrow$$

$$b_2 = \frac{1}{2}(\Gamma_e - \Gamma_o) = \frac{jC \sin(\theta)}{\cos(\theta)\sqrt{1-C^2} + j\sin(\theta)}$$

$$b_3 = \frac{1}{2}(T_e - T_o) = 0$$

$$b_4 = \frac{1}{2}(T_e + T_o) = \frac{\sqrt{1-C^2}}{\cos(\theta)\sqrt{1-C^2} + j\sin(\theta)}$$

$$C = \frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}}$$

$$\theta = \pi/2$$

$$[S] = \begin{bmatrix} 0 & C & 0 & -j\sqrt{1-C^2} \\ C & 0 & -j\sqrt{1-C^2} & 0 \\ 0 & -j\sqrt{1-C^2} & 0 & C \\ -j\sqrt{1-C^2} & 0 & C & 0 \end{bmatrix}$$

# Coupled Line Coupler


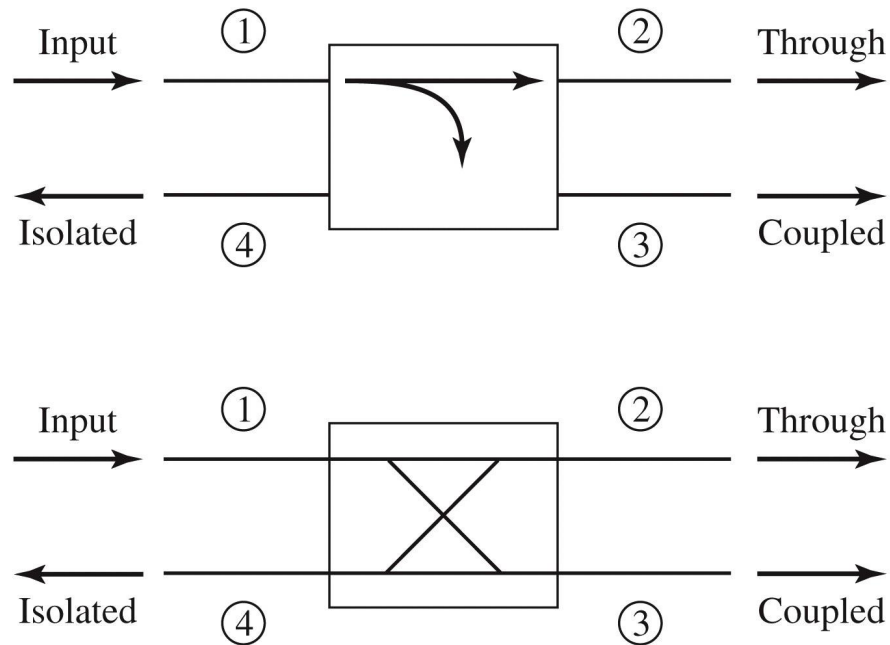



Figure 7.4  
© John Wiley & Sons, Inc. All rights reserved.

$$[S] = -j \cdot \begin{bmatrix} 0 & \sqrt{1-C^2} & jC & 0 \\ \sqrt{1-C^2} & 0 & 0 & jC \\ jC & 0 & 0 & \sqrt{1-C^2} \\ 0 & jC & \sqrt{1-C^2} & 0 \end{bmatrix} \quad [S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & j & 0 \\ 1 & 0 & 0 & j \\ j & 0 & 0 & 1 \\ 0 & j & 1 & 0 \end{bmatrix}$$

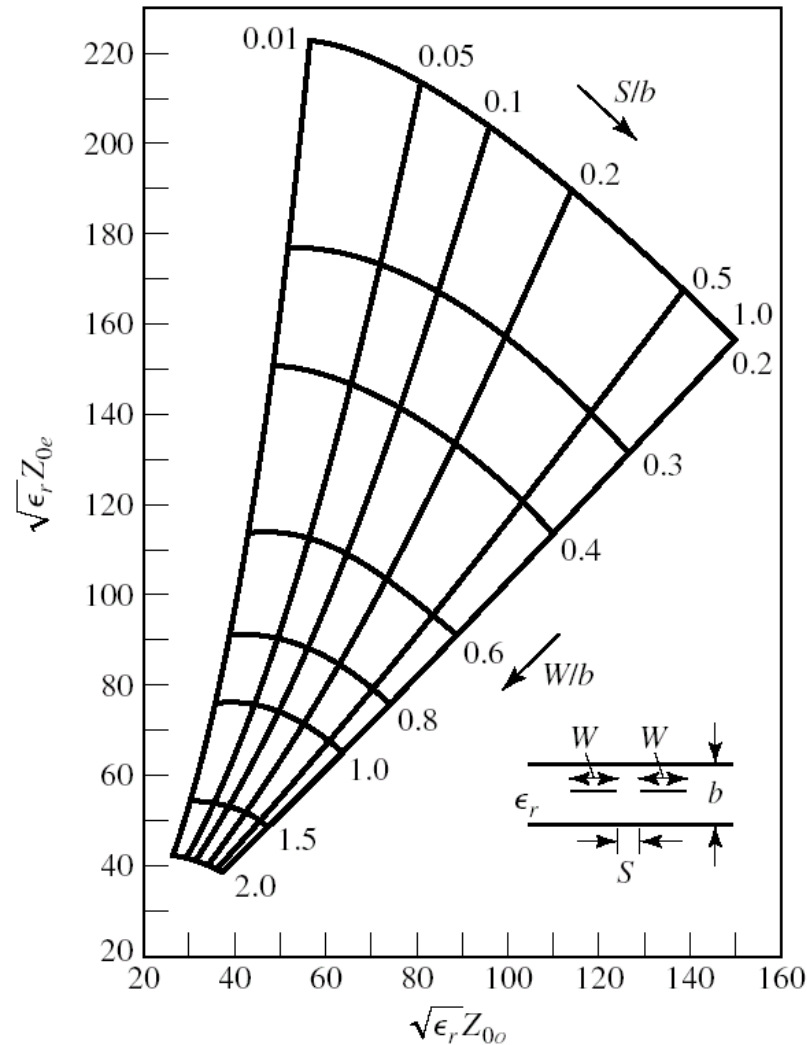
# Normalized even- and odd-mode characteristic impedance design data for edge-coupled striplines.



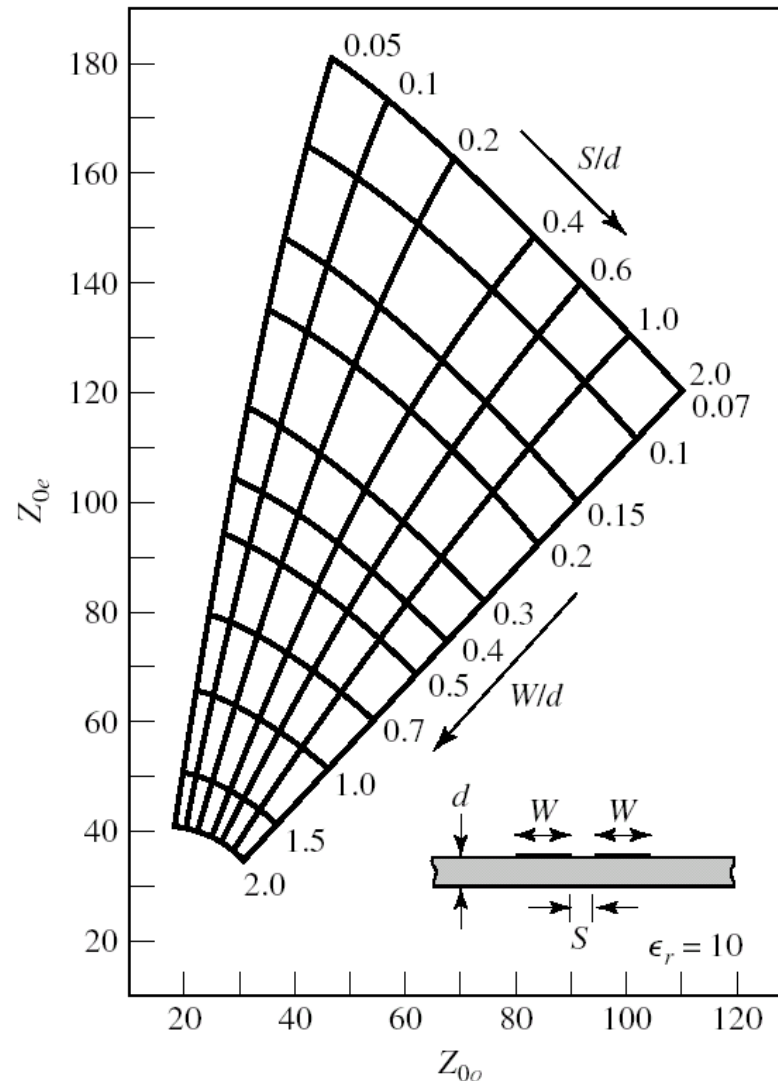
# Even- and odd-mode characteristic impedance design data for coupled microstrip lines on a substrate with $\epsilon_r = 10$ .



# Coupled Line Coupler

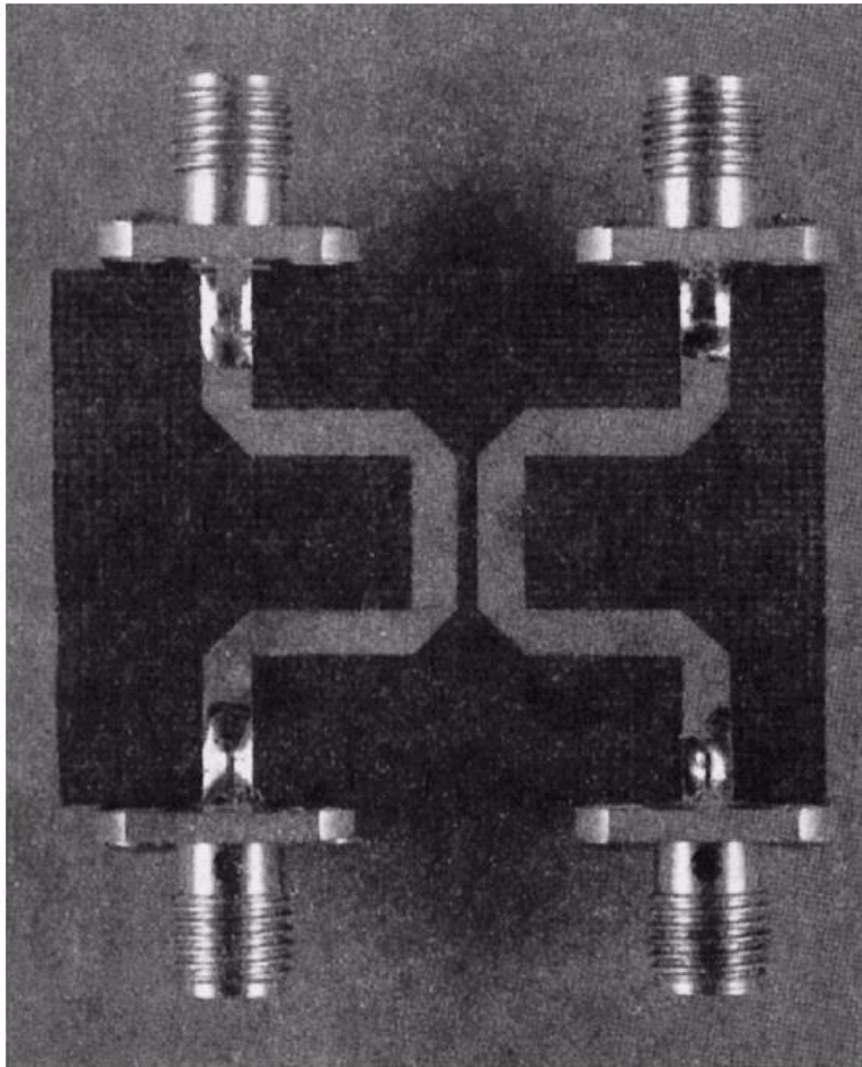

# Coupled Line Coupler

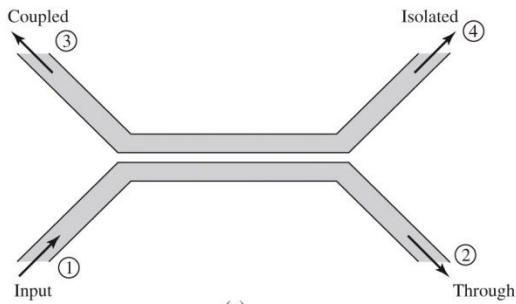

Coupling, Directivity (dB)

$$Z_{ce} Z_{co} = Z_0^2$$

$$|\beta| = \frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}}$$

$$C \text{ [dB]} = -20 \cdot \log_{10} \left( \frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}} \right)$$

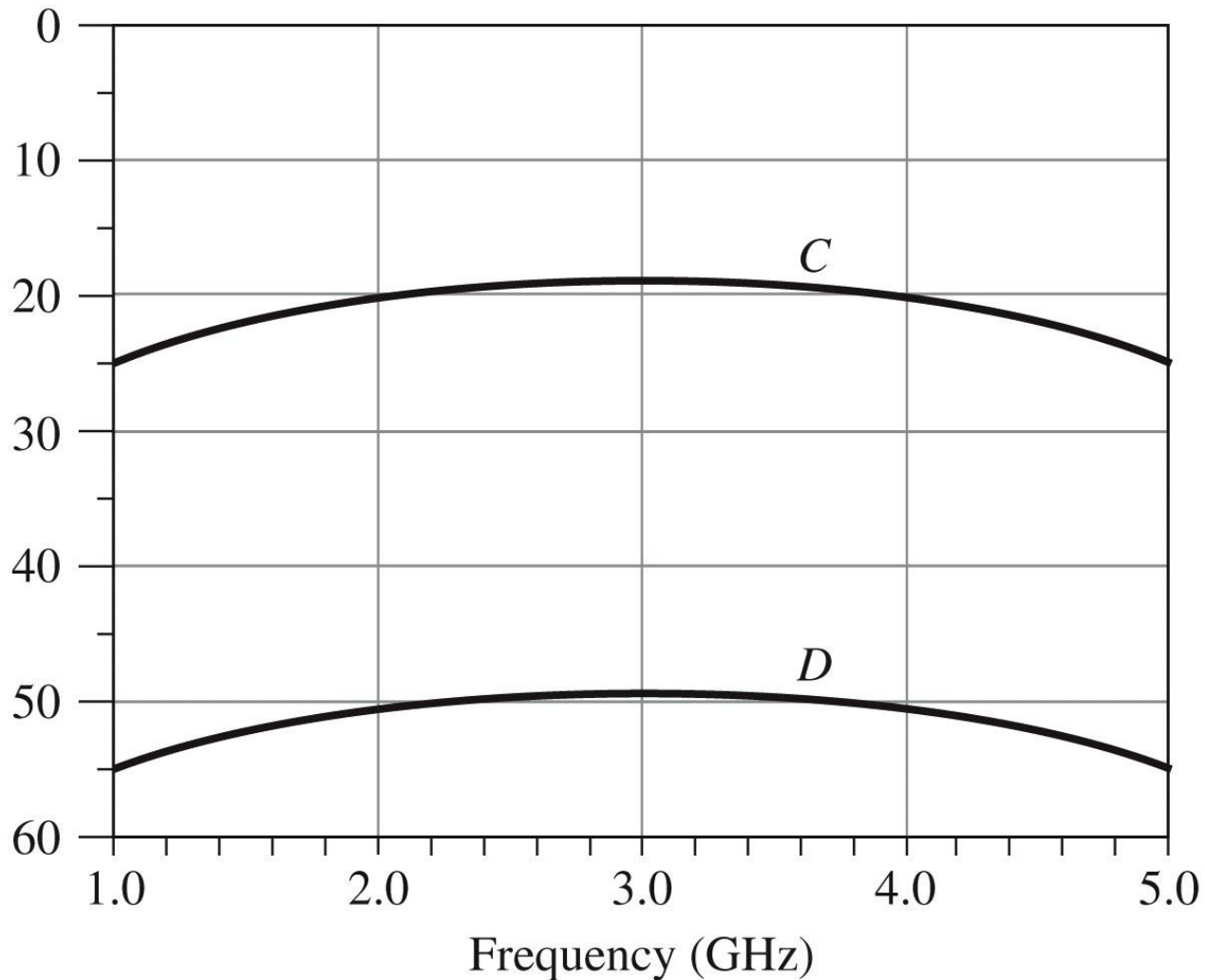


Figure 7.34  
© John Wiley & Sons, Inc. All rights reserved.



# Example

Design a coupled line coupler with 20 dB coupling factor, using stripline technology, with a distance between ground planes of 0.158 cm and an electrical permittivity of 2.56, working on  $50\Omega$ , at the design frequency of 3 GHz. Plot the coupling and directivity between 1 and 5 GHz.

# Solution

$$C = 10^{-20/20} = 0.1$$

$$Z_{co} = 50 \sqrt{\frac{0.9}{1.1}} = 45.23 \Omega$$

$$Z_{ce} = 50 \sqrt{\frac{1.1}{0.9}} = 55.28 \Omega$$

TRL - Edge-coupled Symmetric Stripline (CPL)1

File Edit View Structure Window Help

Edge-coupled Symmetric Stripline (CPL)1

Dimensions

W 1.14072  
S 0.51747  
P 15.6142

Electrical

Z0 50  
K 20  
E 90  
Zo 45.2267  
Ze 55.2771

Units

Dimension mm  
Frequency GHz  
Impedance Ohm  
Electrical Length Deg  
Resistivity uOhm\*cm

Frequency 3 Analysis Auto Calculate Off ! Reset All ! Synthesis 3

Substrate

Required B 1.58 ER 2.56  
Optional TAND 0

Metallization



Layers	Metal Name	Code	Resistivity	Thickness	
Bottom	*None*				Reset
Middle	*None*				Reset
Top	*None*				Reset

RGH 0 Add new metal

For Help, press F1


$$Z_{ce} = Z_0 \sqrt{\frac{1+C}{1-C}}, \quad Z_{co} = Z_0 \sqrt{\frac{1-C}{1+C}}$$

# Simulation

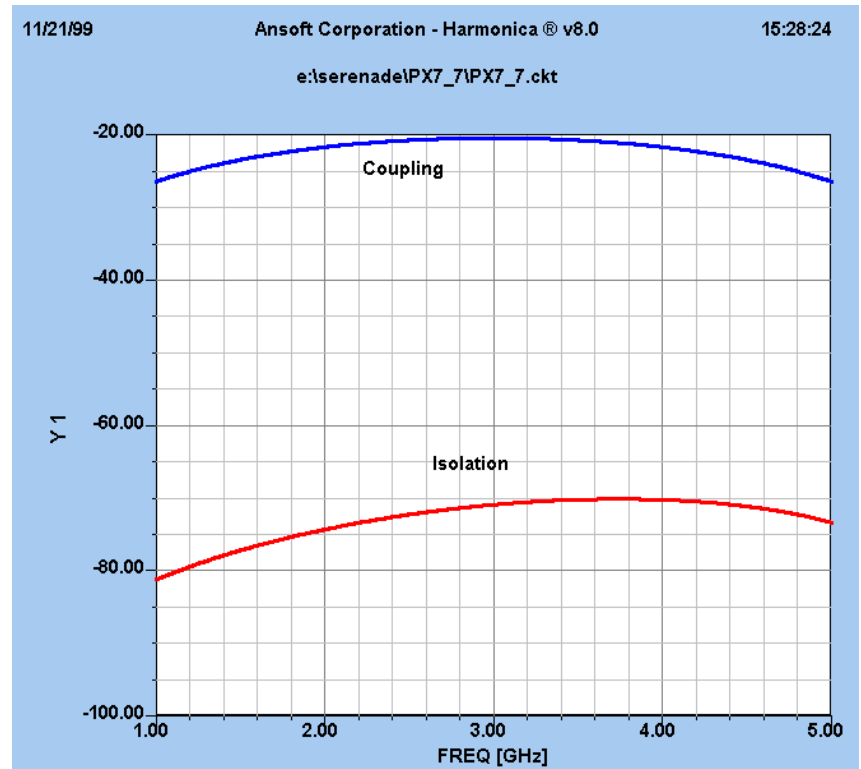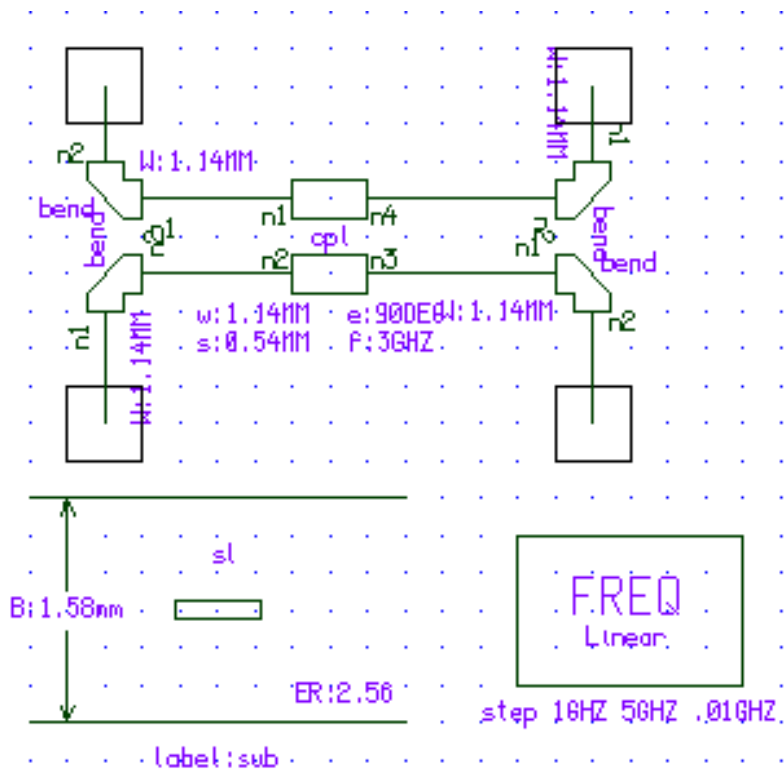
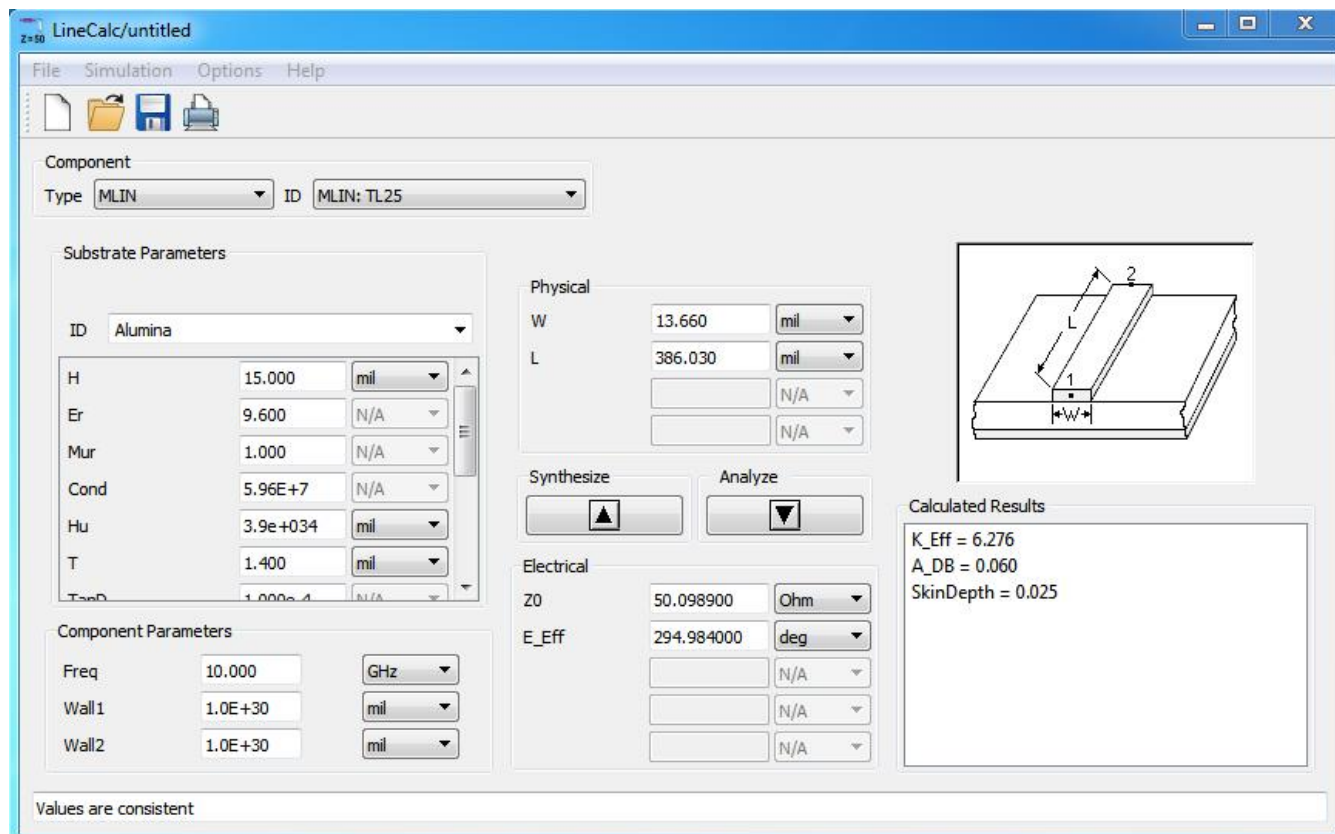
# ADS linecalc

- In schematics: >Tools>LineCalc>Start
- for Microstrip lines >Tools>LineCalc>Send to Linecalc




The screenshot displays the ADS LineCalc software interface. The window title is "LineCalc/untitled". The menu bar includes "File", "Simulation", "Options", and "Help". The interface is divided into several sections:

- Component:** Type: MLIN, ID: MLIN: TL25
- Substrate Parameters:** ID: Alumina. Parameters include H (15.000 mil), Er (9.600), Mur (1.000), Cond (5.96E+7), Hu (3.9e+034 mil), T (1.400 mil), and TanD (1.000e-4).
- Physical:** W (13.660 mil), L (386.030 mil).
- Electrical:** ZO (50.098900 Ohm), E\_Eff (294.984000 deg).
- Component Parameters:** Freq (10.000 GHz), Wall1 (1.0E+30 mil), Wall2 (1.0E+30 mil).
- Calculated Results:** K\_Eff = 6.276, A\_DB = 0.060, SkinDepth = 0.025.

A diagram on the right shows a 3D perspective of a microstrip line on a substrate, with labels for width (W), length (L), and height (H). The status bar at the bottom indicates "Values are consistent".


# ADS linecalc

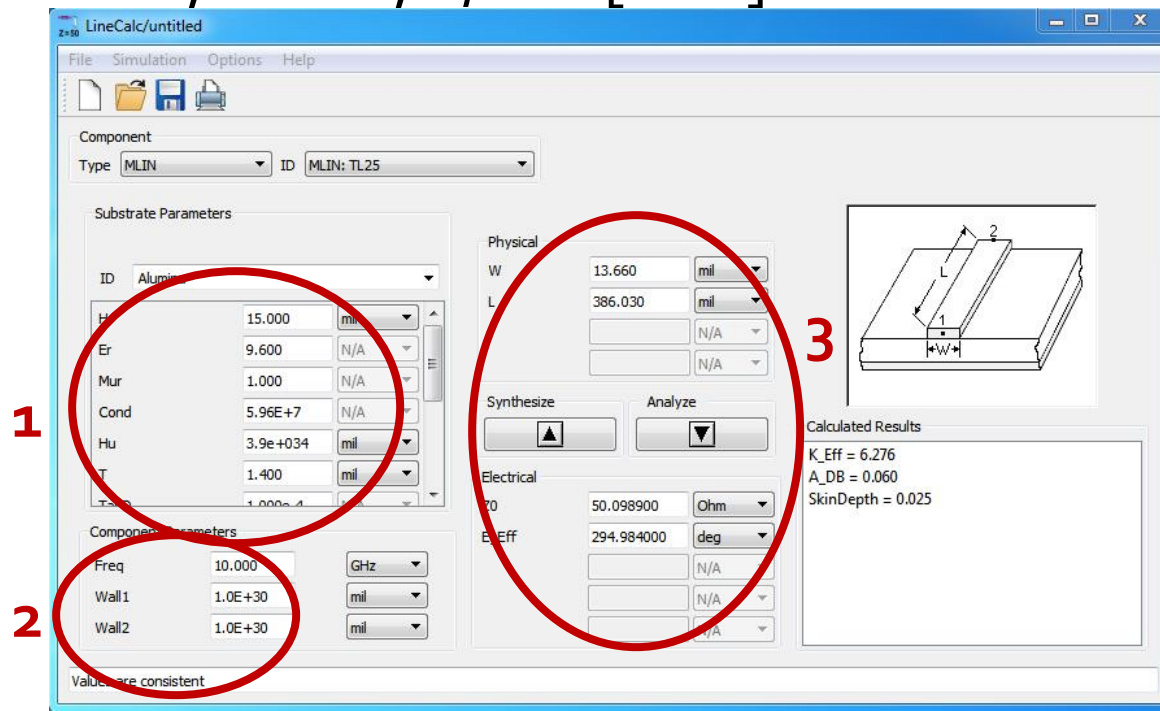- 1. Define substrate (receive from schematic)
- 2. Insert frequency
- 3. Insert input data
  - Analyze:  $W, L \rightarrow Z_o, E$  or  $Z_e, Z_o, E$  / at  $f$  [GHz]
  - Synthesis:  $Z_o, E \rightarrow W, L$  / at  $f$  [GHz]


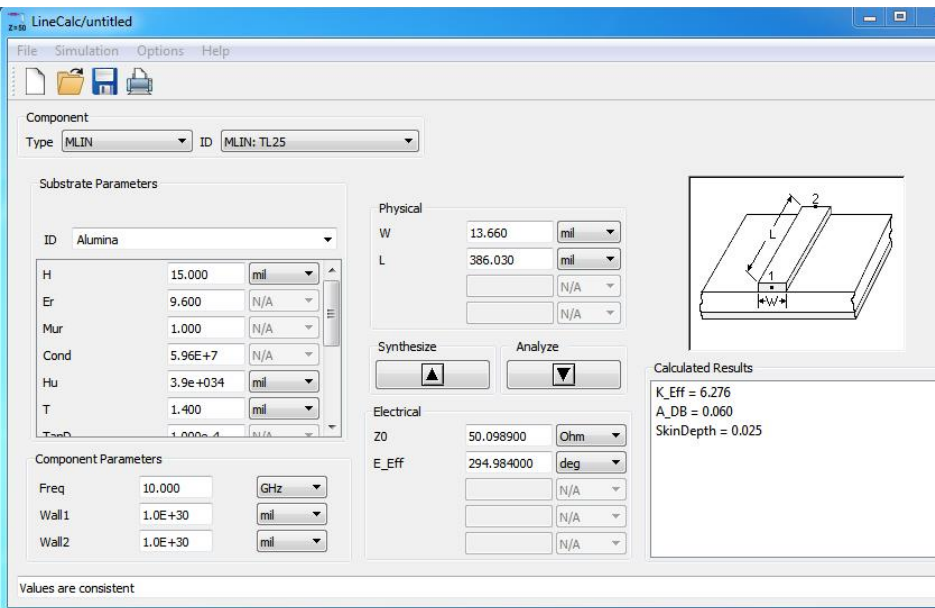
# ADS linecalc

- Can be used for:
  - microstrip lines MLIN:  $W, L \Leftrightarrow Z_0, E$
  - microstrip coupled lines MCLIN:  $W, L, S \Leftrightarrow Z_e, Z_0, E$




The screenshot shows the ADS LineCalc/untitled window for a single microstrip line (MLIN). The component type is MLIN and the ID is MLIN: TL25. The substrate parameters are set to Alumina. The physical parameters are W = 13.660 mil and L = 386.030 mil. The calculated results are K\_Eff = 6.276, A\_DB = 0.060, and SkinDepth = 0.025. The diagram shows a single microstrip line on a substrate with width W and length L.

Parameter	Value	Unit
W	13.660	mil
L	386.030	mil
H	15.000	mil
Er	9.600	N/A
Mur	1.000	N/A
Cond	5.96E+7	N/A
Hu	3.9e+034	mil
T	1.400	mil
Ze	1.000E+4	N/A

Parameter	Value	Unit
Z0	50.098900	Ohm
E_Eff	294.984000	deg

Calculated Results

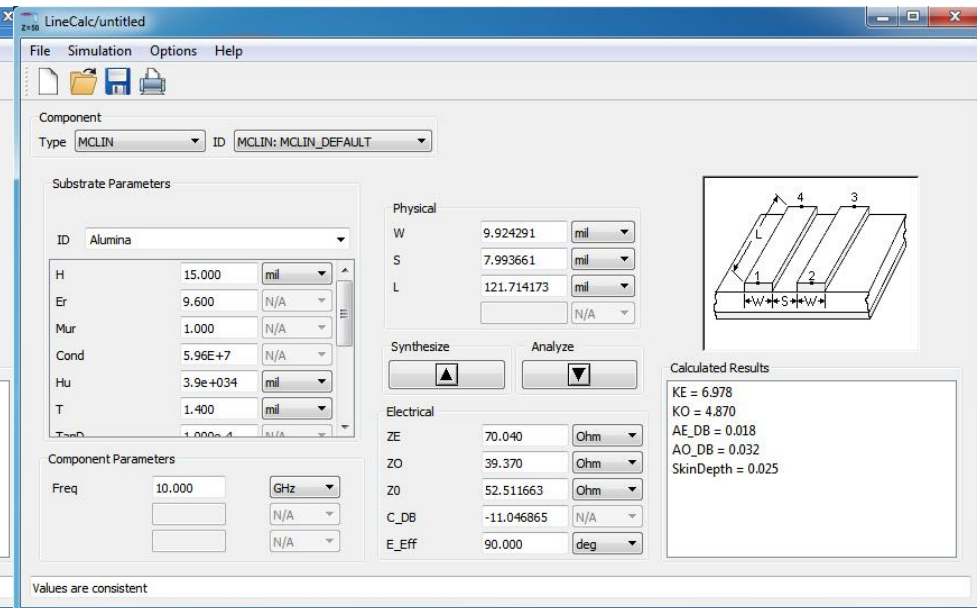- K\_Eff = 6.276
- A\_DB = 0.060
- SkinDepth = 0.025



The screenshot shows the ADS LineCalc/untitled window for a microstrip coupled line (MCLIN). The component type is MCLIN and the ID is MCLIN: MCLIN\_DEFAULT. The substrate parameters are set to Alumina. The physical parameters are W = 9.924291 mil, S = 7.993661 mil, and L = 121.714173 mil. The calculated results are KE = 6.978, KO = 4.870, AE\_DB = 0.018, AO\_DB = 0.032, and SkinDepth = 0.025. The diagram shows two coupled microstrip lines on a substrate with width W, spacing S, and length L.

Parameter	Value	Unit
W	9.924291	mil
S	7.993661	mil
L	121.714173	mil
H	15.000	mil
Er	9.600	N/A
Mur	1.000	N/A
Cond	5.96E+7	N/A
Hu	3.9e+034	mil
T	1.400	mil
Ze	1.000E+4	N/A

Parameter	Value	Unit
ZE	70.040	Ohm
ZO	39.370	Ohm
Z0	52.511663	Ohm
C_DB	-11.046865	N/A
E_Eff	90.000	deg

Calculated Results

- KE = 6.978
- KO = 4.870
- AE\_DB = 0.018
- AO\_DB = 0.032
- SkinDepth = 0.025

# ADS linecalc

LineCalc/untitled

File Simulation Options Help

Component  
Type: MCLIN ID: MCLIN: MCLIN\_DEFAULT

Substrate Parameters

Parameter	Value	Unit
ID	Alumina	
H	15.000	mil
Er	9.600	N/A
Mur	1.000	N/A
Cond	5.96E+7	N/A
Hu	3.9e+034	mil
T	1.400	mil
TanD	1.000e-4	N/A


Physical

W	9.924291	mil
S	7.993661	mil
L	121.714173	mil
		N/A

Synthesize Analyze

Electrical

ZE	70.040	Ohm
ZO	39.370	Ohm
Z0	52.511663	Ohm
C_DB	-11.046865	N/A
E_Eff	90.000	deg

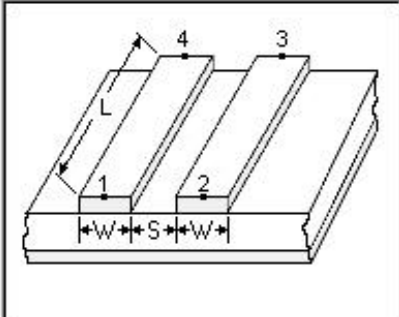

Calculated Results

KE = 6.978  
KO = 4.870  
AE\_DB = 0.018  
AO\_DB = 0.032  
SkinDepth = 0.025

Values are consistent

# Multisection Coupled Line Couplers

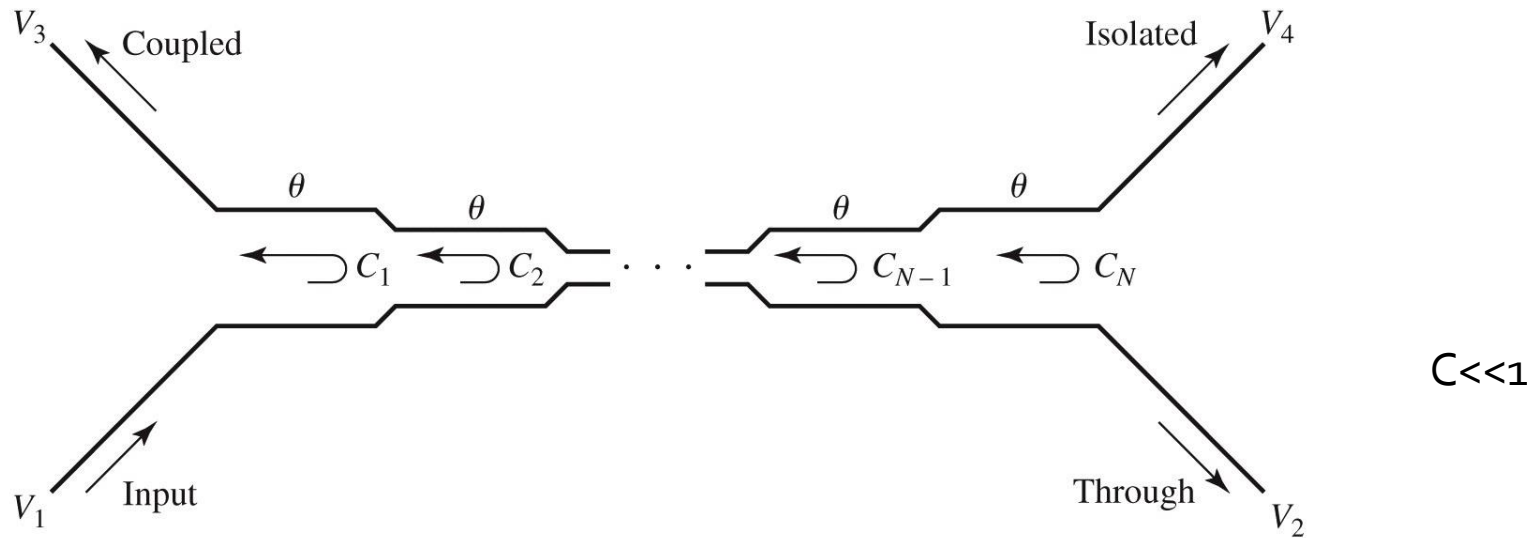


Figure 7.35  
© John Wiley & Sons, Inc. All rights reserved.

$$\frac{V_3}{V_1} = b_3 = \frac{jC \sin \theta}{\cos \theta \sqrt{1-C^2} + j \sin \theta} = \frac{jC \operatorname{tg} \theta}{\sqrt{1-C^2} + j \operatorname{tg} \theta} \approx \frac{jC \operatorname{tg} \theta}{1 + j \operatorname{tg} \theta} = jC \sin \theta e^{-j\theta}$$

$$\frac{V_2}{V_1} = b_2 = \frac{\sqrt{1-C^2}}{\cos \theta \sqrt{1-C^2} + j \sin \theta} \approx \frac{1}{\cos \theta + j \sin \theta} = e^{-j\theta}$$

$$C = \frac{V_3}{V_1} = 2j \sin \theta e^{-j\theta} e^{-j(N-1)\theta} \left[ C_1 \cos(N-1)\theta + C_2 \cos(N-3)\theta + \dots + \frac{1}{2} C_{\frac{N+1}{2}} \right]$$



# Example

Design a three sections coupled line coupler with 20 dB coupling factor, binomial characteristic (maximum flat), working on  $50\Omega$ , at the design frequency of 3 GHz. Plot the coupling and directivity between 1 and 5 GHz

# Solution

$$\left. \frac{d^n}{d\theta^n} C(\theta) \right|_{\theta=\pi/2} = 0, n = 1, 2$$

$$C = \left| \frac{V_3}{V_1} \right| = 2 \sin \theta \left[ C_1 \cos 2\theta + \frac{1}{2} C_2 \right] = C_1 (\sin 3\theta - \sin \theta) + C_2 \sin \theta$$

$$\left. \frac{dC}{d\theta} = [3C_1 \cos 3\theta + (C_2 - C_1) \cos \theta] \right|_{\theta=\pi/2} = 0$$

$$\left. \frac{d^2C}{d\theta^2} = [-9C_1 \sin 3\theta - (C_2 - C_1) \sin \theta] \right|_{\theta=\pi/2} = 10C_1 - C_2 = 0$$

$$\begin{cases} C_2 - 2C_1 = 0.1 \\ 10C_1 - C_2 = 0 \end{cases}$$

$$\begin{cases} C_1 = C_3 = 0.0125 \\ C_2 = 0.125 \end{cases}$$


$$Z_{0e}^1 = Z_{0e}^3 = 50 \sqrt{\frac{1.0125}{0.9875}} = 50.63 \Omega$$

$$Z_{0o}^1 = Z_{0o}^3 = 50 \sqrt{\frac{0.9875}{1.0125}} = 49.38 \Omega$$

$$Z_{0e}^2 = 50 \sqrt{\frac{1.125}{0.875}} = 56.69 \Omega$$

$$Z_{0o}^2 = 50 \sqrt{\frac{0.875}{1.125}} = 44.10 \Omega$$

# Simulare

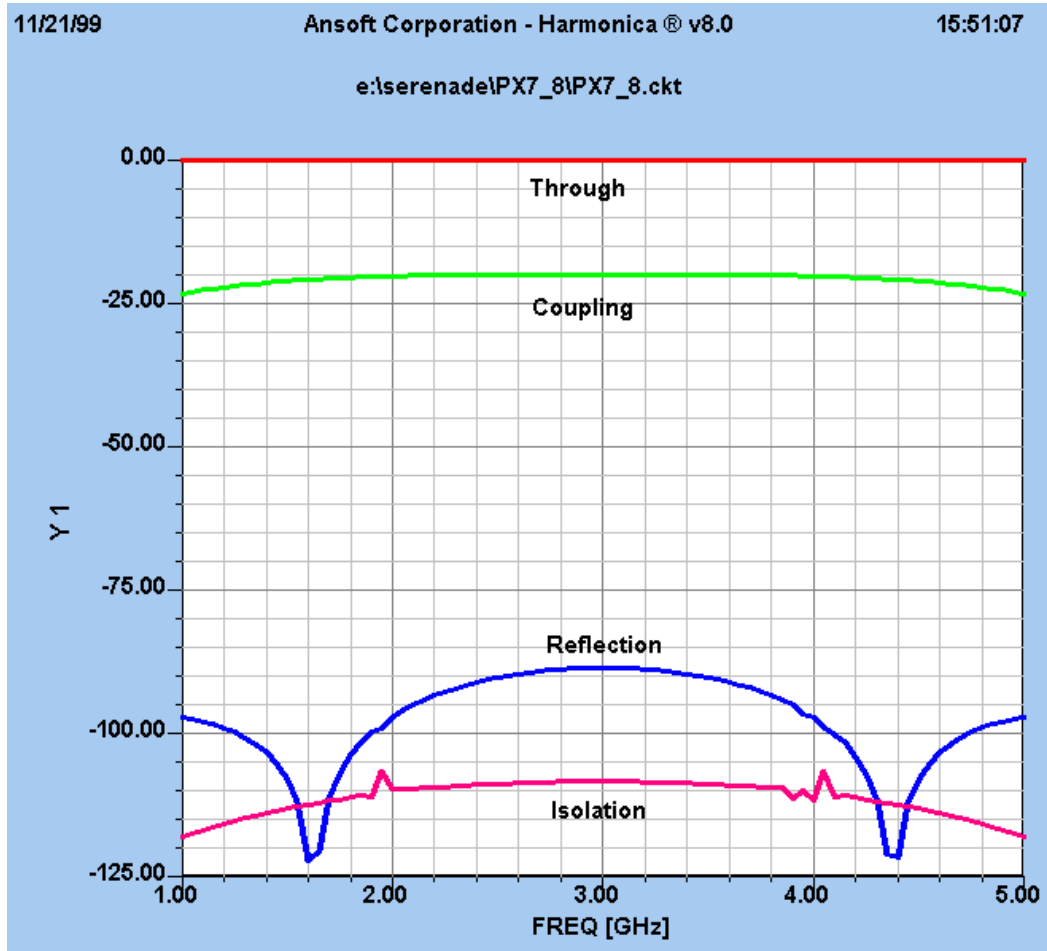

# The Lange Coupler

- allows achieving coupling factors of 3 or 6 dB


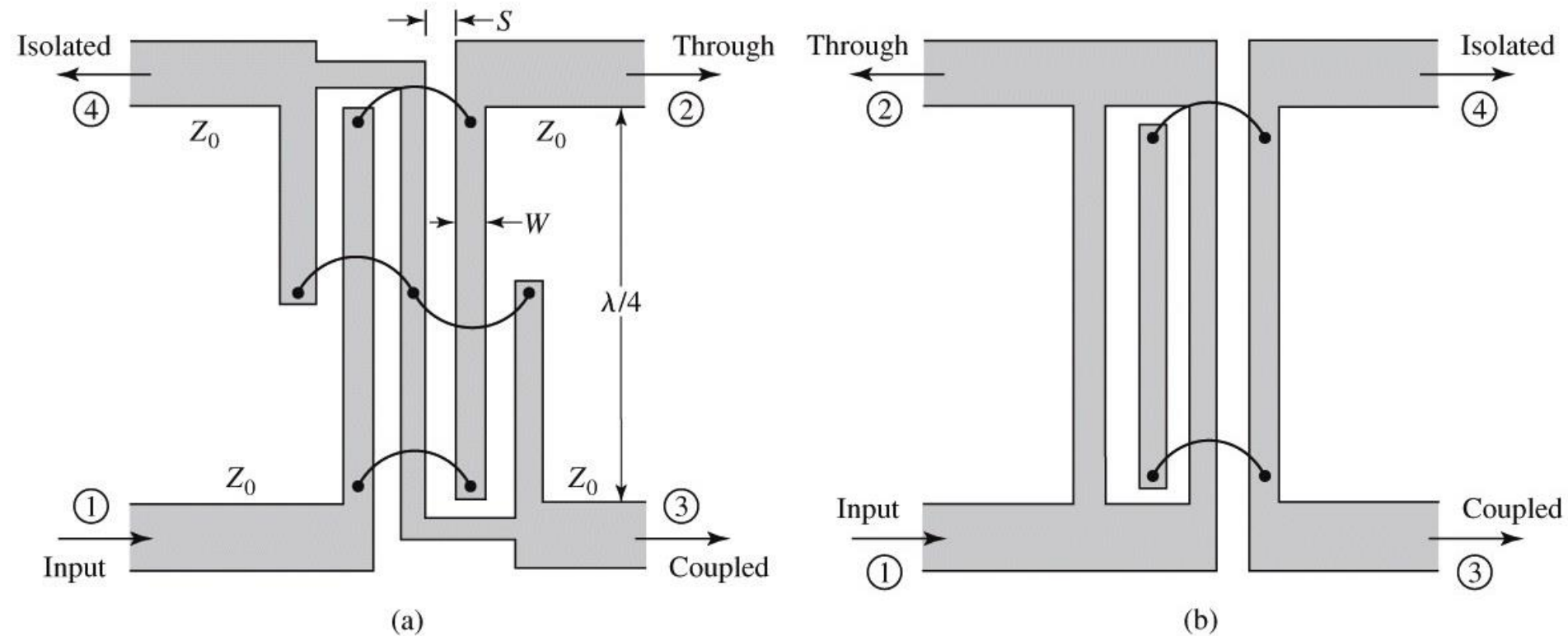



Figure 7.38

© John Wiley & Sons, Inc. All rights reserved.

# The Lange Coupler

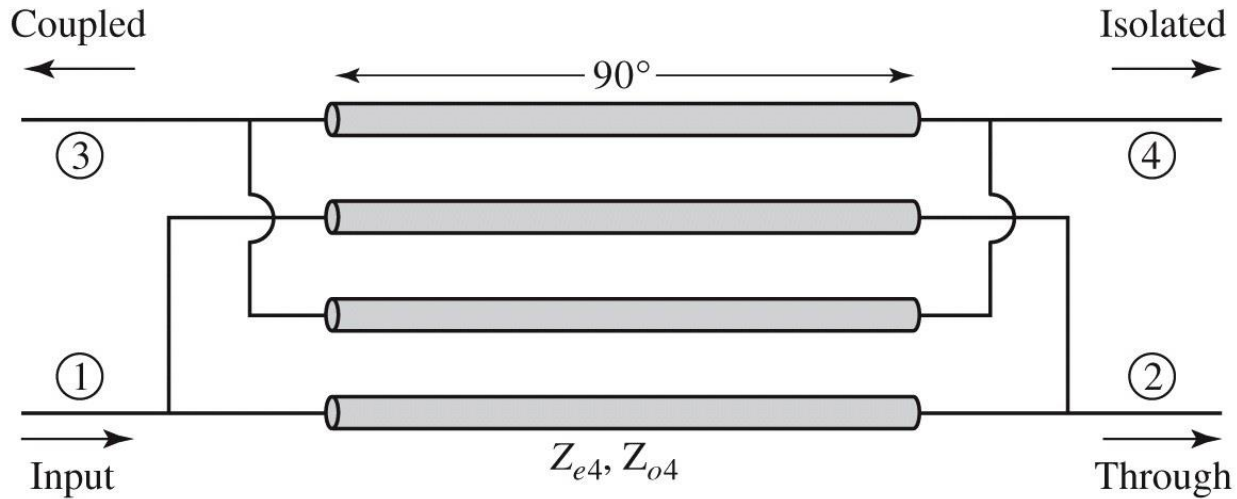


(a)

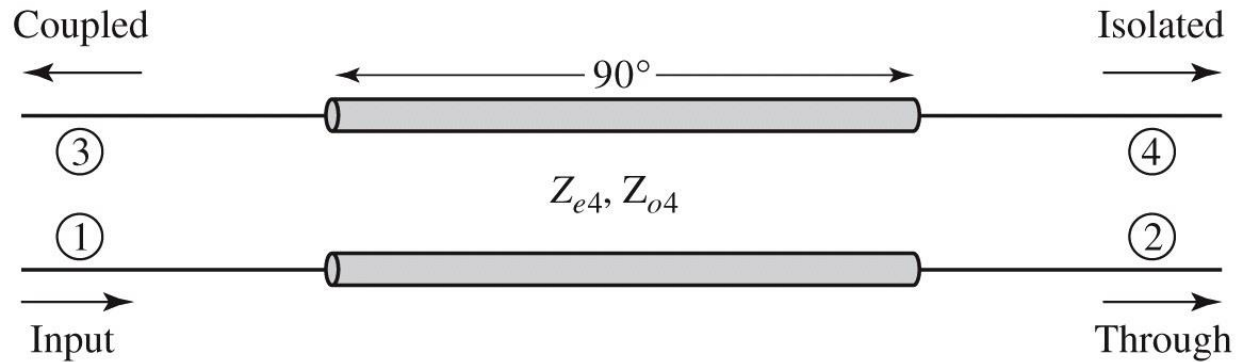

(b)


# Circuit model

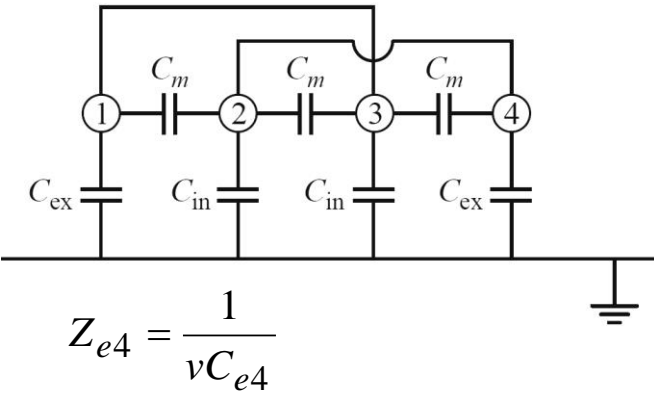

$$C_{in} = C_{ex} - \frac{C_{ex}C_m}{C_{ex} + C_m}$$

$$C_{e4} = C_{ex} + C_{in}$$

$$C_{o4} = C_{ex} + C_{in} + 6C_m$$

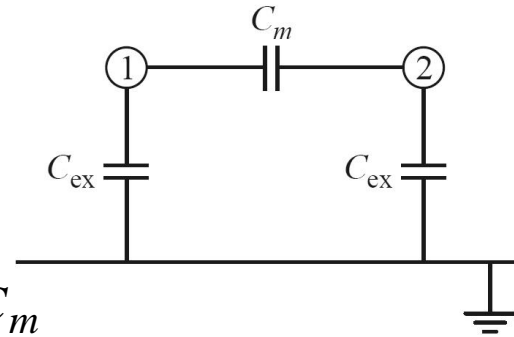

$$C_e = C_{ex}$$

$$C_o = C_{ex} + 2C_m$$

$$Z_{e4} = \frac{1}{vC_{e4}}$$

$$C_{e4} = \frac{C_e(3C_e + C_o)}{C_e + C_o}$$

$$C_{o4} = \frac{C_o(3C_o + C_e)}{C_e + C_o}$$

$$Z_{e4} = Z_{0e} \frac{Z_{0e} + Z_{0o}}{3Z_{0o} + Z_{0e}}$$

$$Z_{o4} = Z_{0o} \frac{Z_{0e} + Z_{0o}}{3Z_{0e} + Z_{0o}}$$


$$Z_0 = \sqrt{Z_{e4}Z_{o4}} = \sqrt{\frac{Z_{0e}Z_{0o}(Z_{0o} + Z_{0e})^2}{(3Z_{0o} + Z_{0e})(3Z_{0e} + Z_{0o})}}$$

$$C = \frac{Z_{e4} - Z_{o4}}{Z_{e4} + Z_{o4}} = \frac{3(Z_{0e}^2 - Z_{0o}^2)}{3(Z_{0e}^2 + Z_{0o}^2) + 2Z_{0e}Z_{0o}}$$

$$Z_{0e} = \frac{4C - 3 + \sqrt{9 - 8C^2}}{2C\sqrt{(1-C)/(1+C)}} Z_0$$

$$Z_{0o} = \frac{4C + 3 - \sqrt{9 - 8C^2}}{2C\sqrt{(1+C)/(1-C)}} Z_0$$

# The Lange Coupler

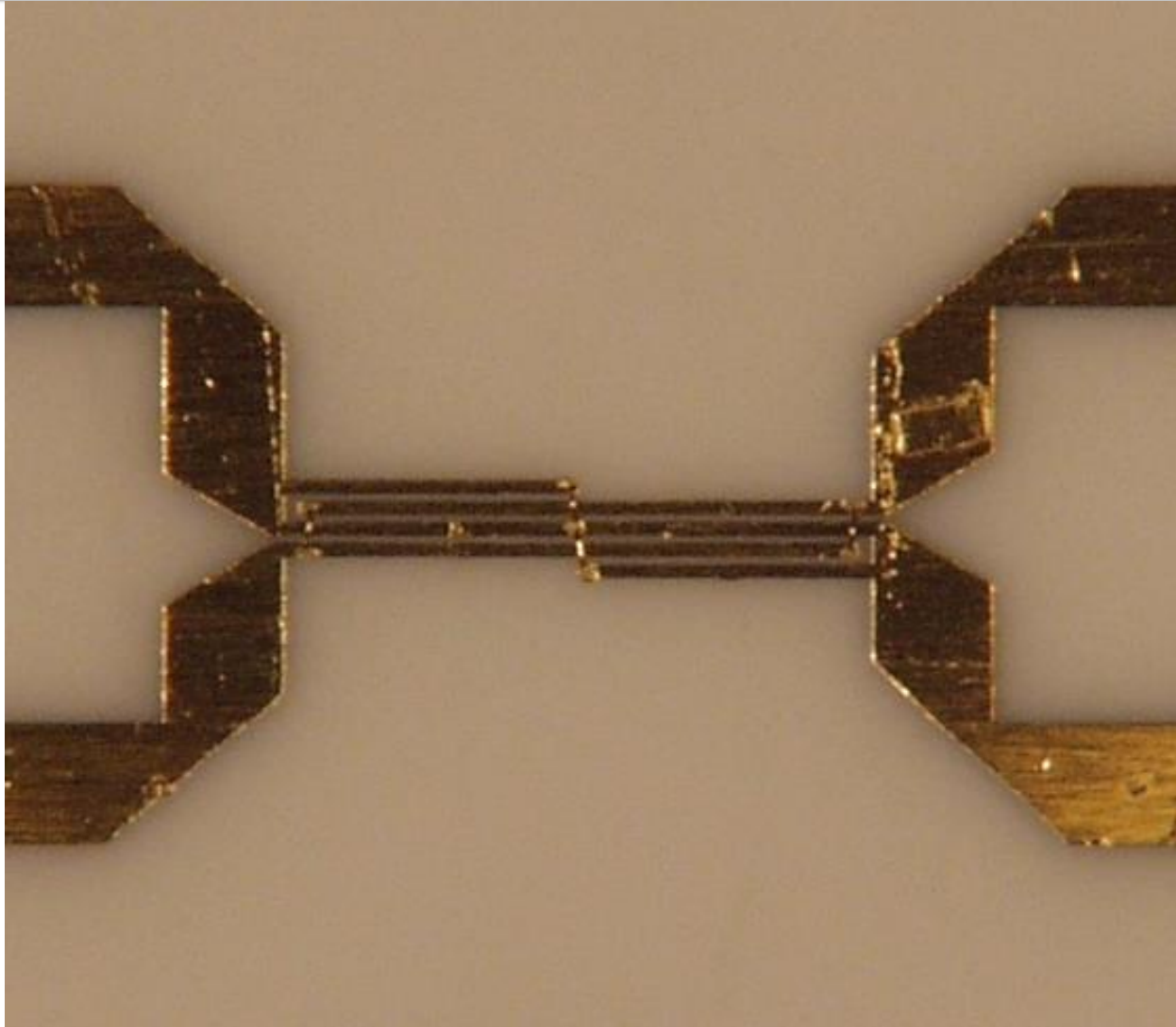


Directional Couplers

# Laboratory no. 2



# Directional Coupler

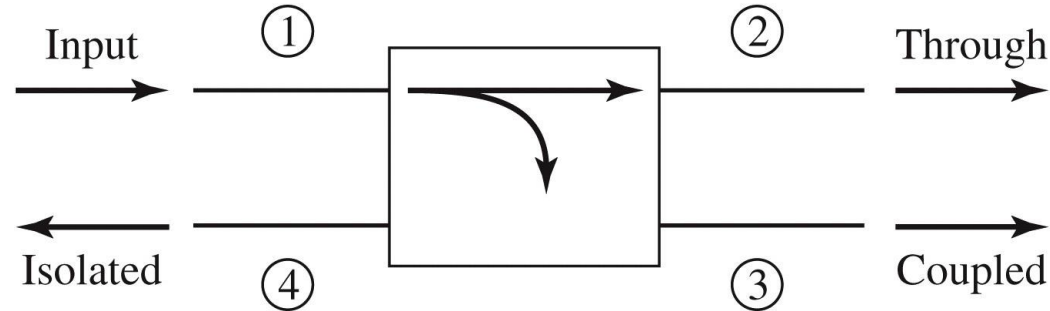

$$|S_{12}|^2 = \alpha^2 = 1 - \beta^2$$

$$|S_{13}|^2 = \beta^2$$

Cuplaj

$$C = 10 \log \frac{P_1}{P_3} = -20 \cdot \log(\beta) [\text{dB}]$$

Directivitate

$$D = 10 \log \frac{P_3}{P_4} = 20 \cdot \log \left( \frac{\beta}{|S_{14}|} \right) [\text{dB}]$$

Izolare

$$I = 10 \log \frac{P_1}{P_4} = -20 \cdot \log |S_{14}| [\text{dB}]$$

$$I = D + C, \text{ dB}$$

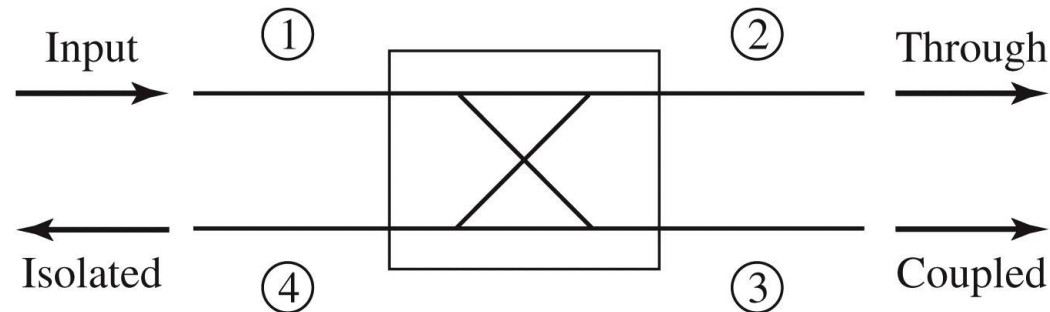


Figure 7.4  
© John Wiley & Sons, Inc. All rights reserved.

# The quadrature (90°) hybrid

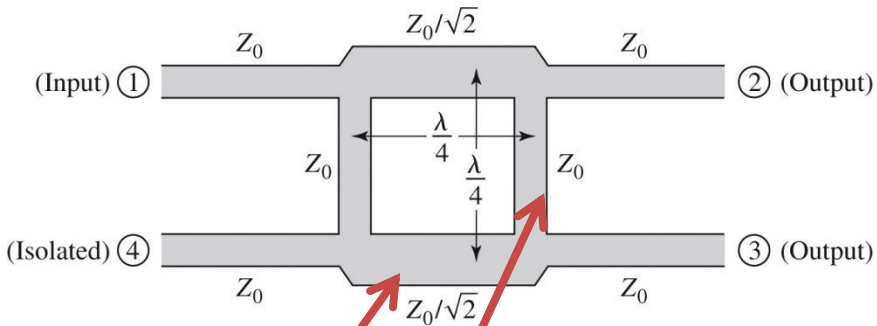


Figure 7.21  
© John Wiley & Sons, Inc. All rights reserved.

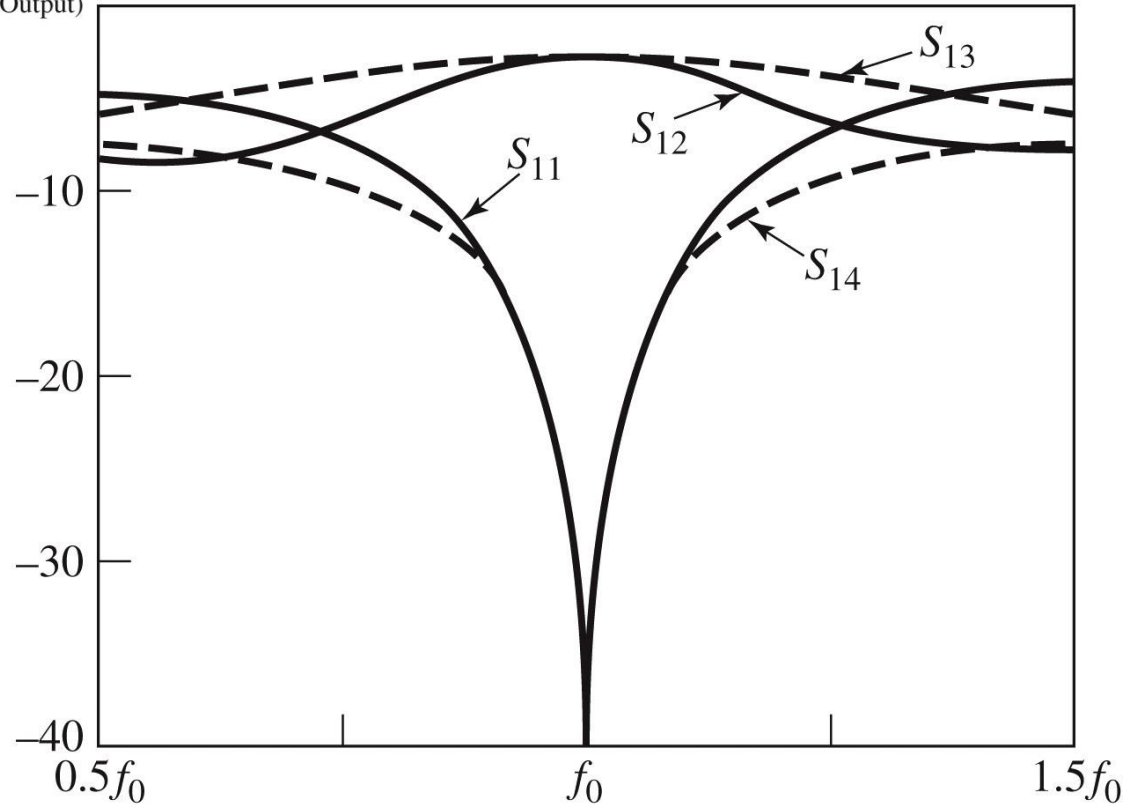



Figure 7.25  
© John Wiley & Sons, Inc. All rights reserved.

$$y_2^2 = 1 + y_1^2$$


$$|\beta| = \frac{\sqrt{y_2^2 - 1}}{y_2}$$

$$C[\text{dB}] = -20 \cdot \log_{10} \frac{\sqrt{y_2^2 - 1}}{y_2}$$

# Quadrature coupler

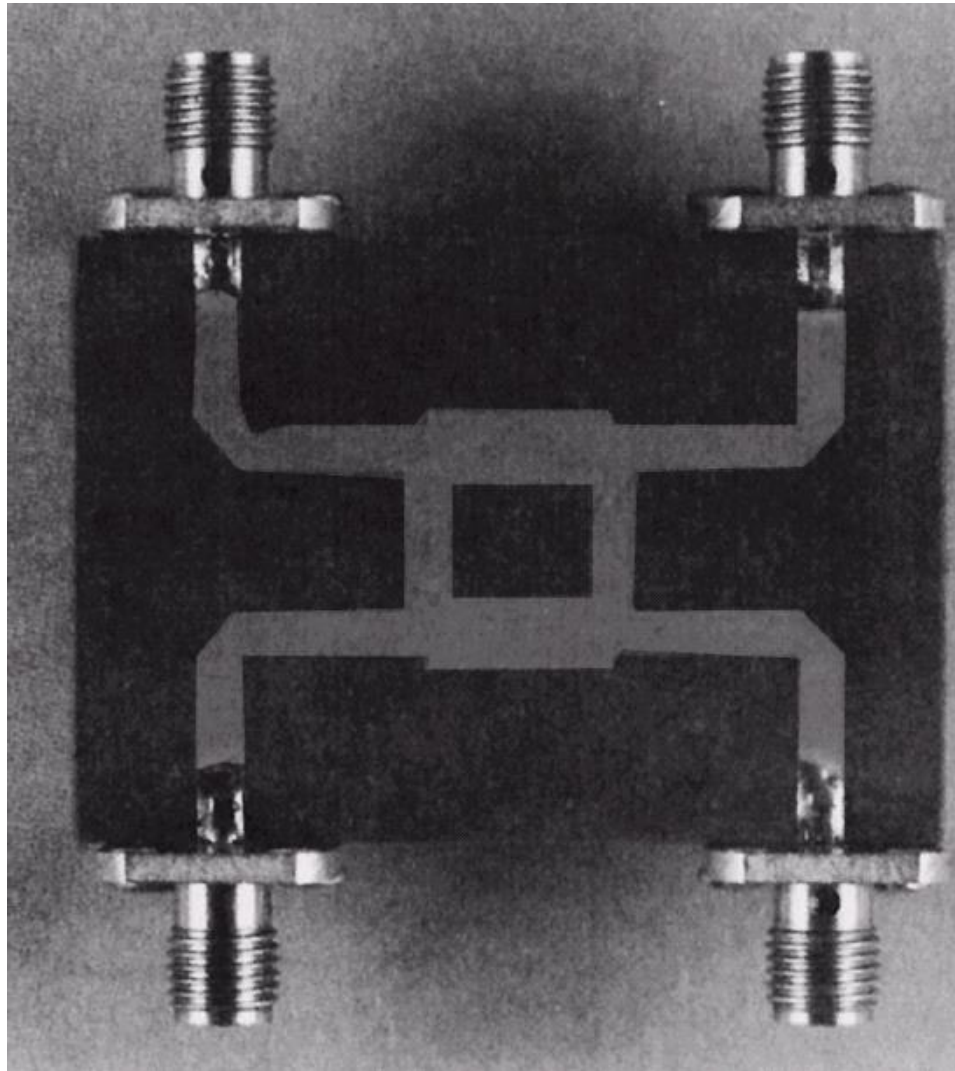

# The 180° ring hybrid (rat-race)

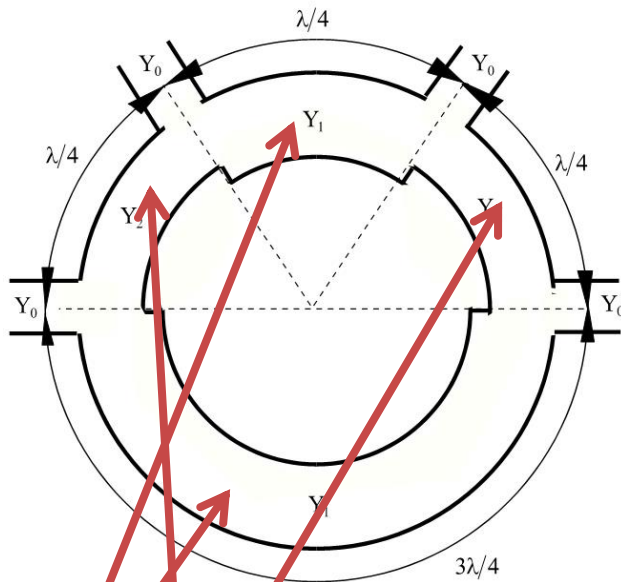

$$y_1^2 + y_2^2 = 1$$

$$|\beta| = y_1$$

$$C \text{ [dB]} = -20 \cdot \log_{10}(y_1)$$

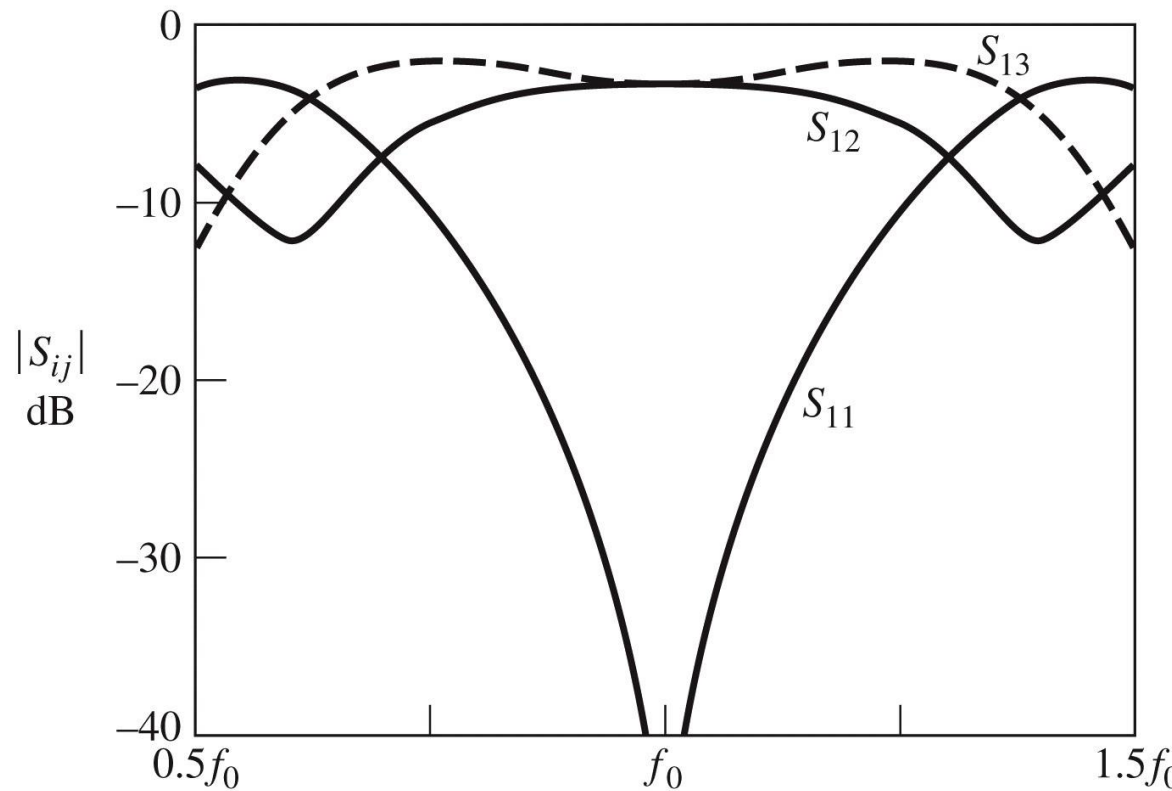


Figure 7.46  
© John Wiley & Sons, Inc. All rights reserved.

# Ring coupler


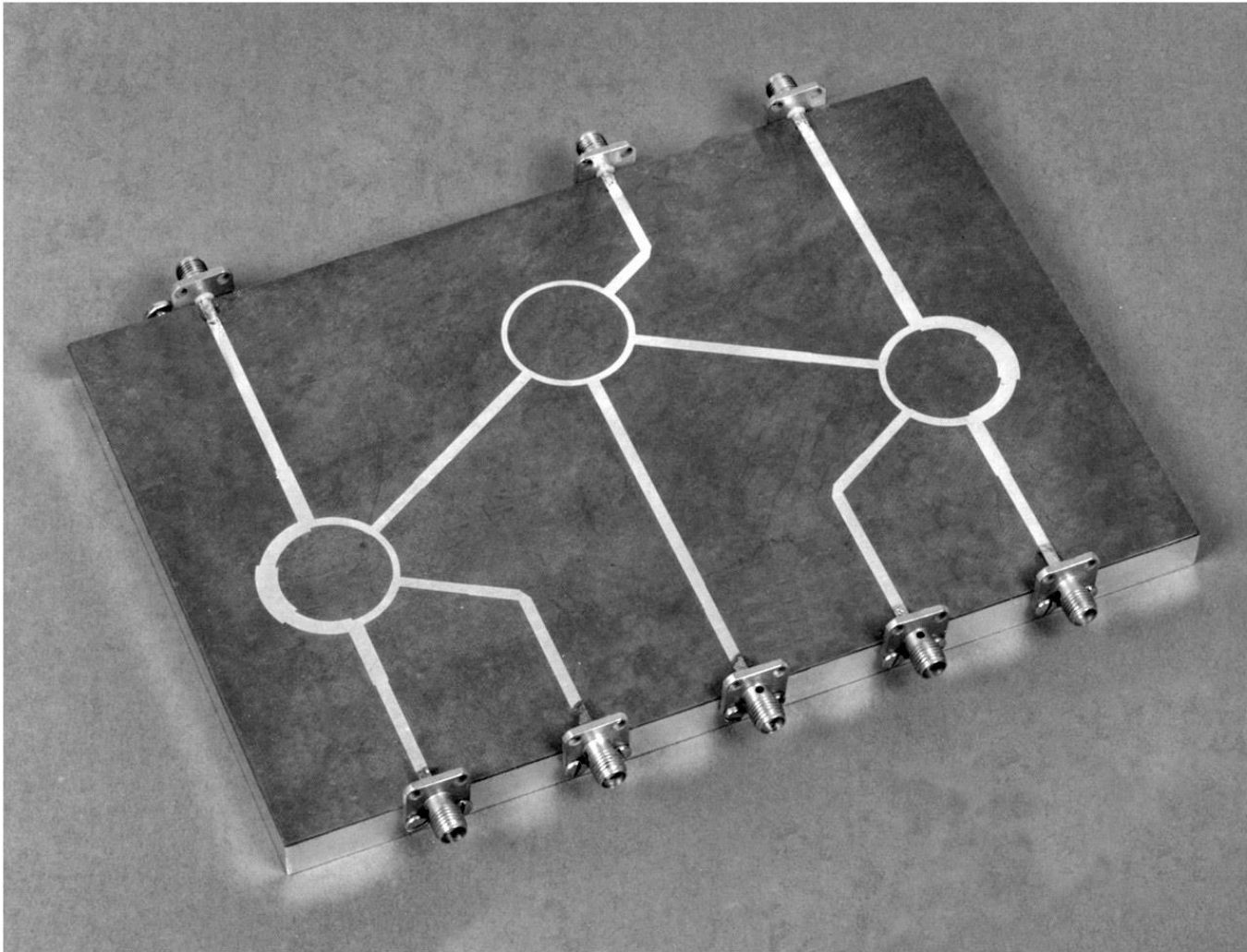


Figure 7.43  
Courtesy of M. D. Abouzahra, MIT Lincoln Laboratory, Lexington, Mass.

# Coupled Line Coupler

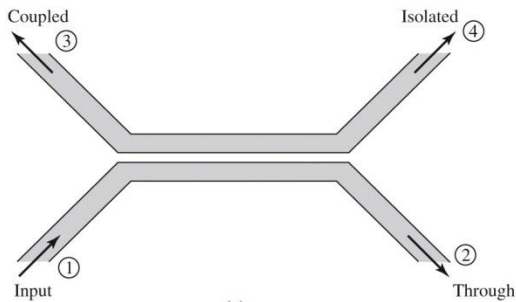

Coupling, Directivity (dB)

$$Z_{ce} Z_{co} = Z_0^2$$

$$|\beta| = \frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}}$$

$$C \text{ [dB]} = -20 \cdot \log_{10} \left( \frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}} \right)$$


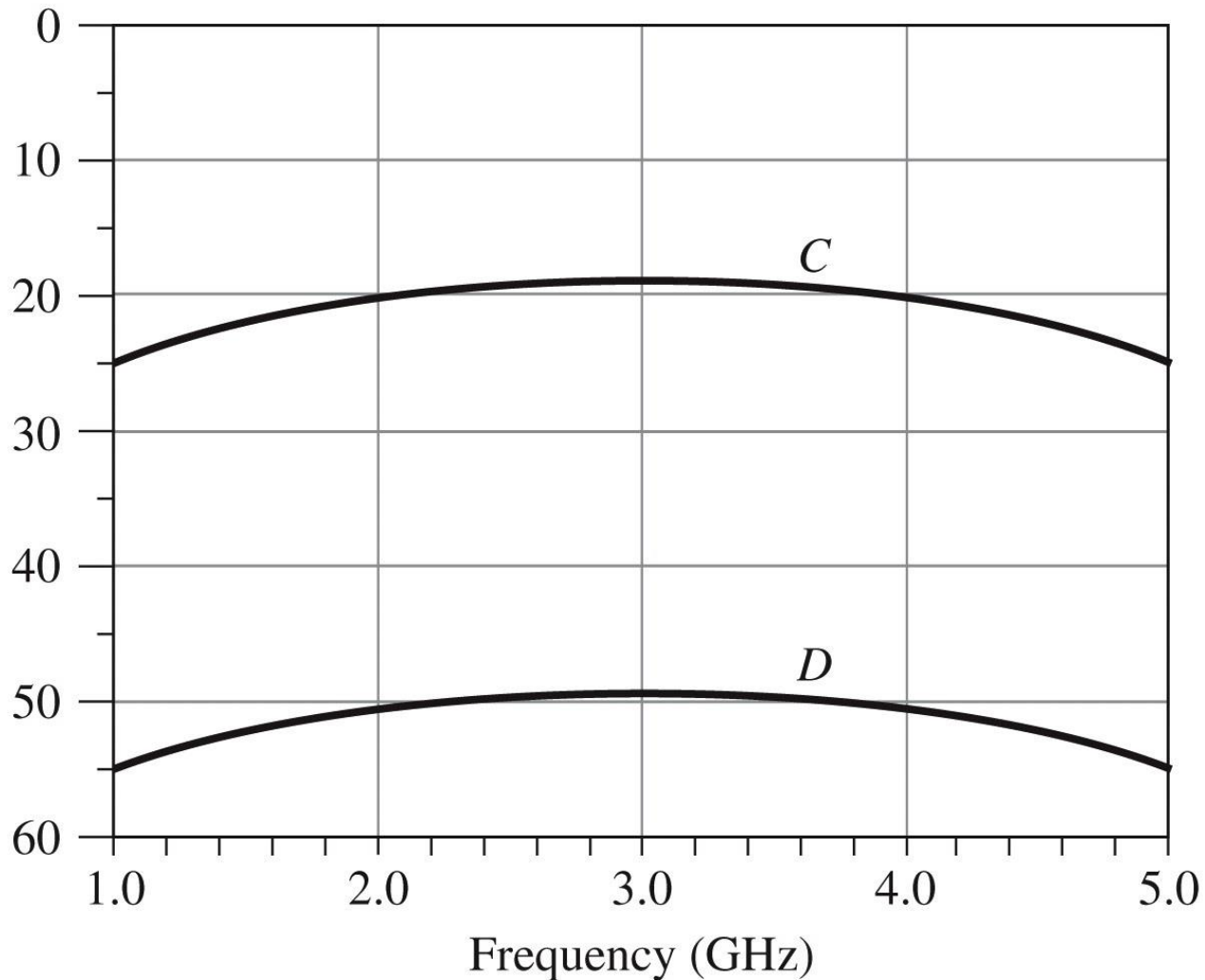


Figure 7.34  
© John Wiley & Sons, Inc. All rights reserved.

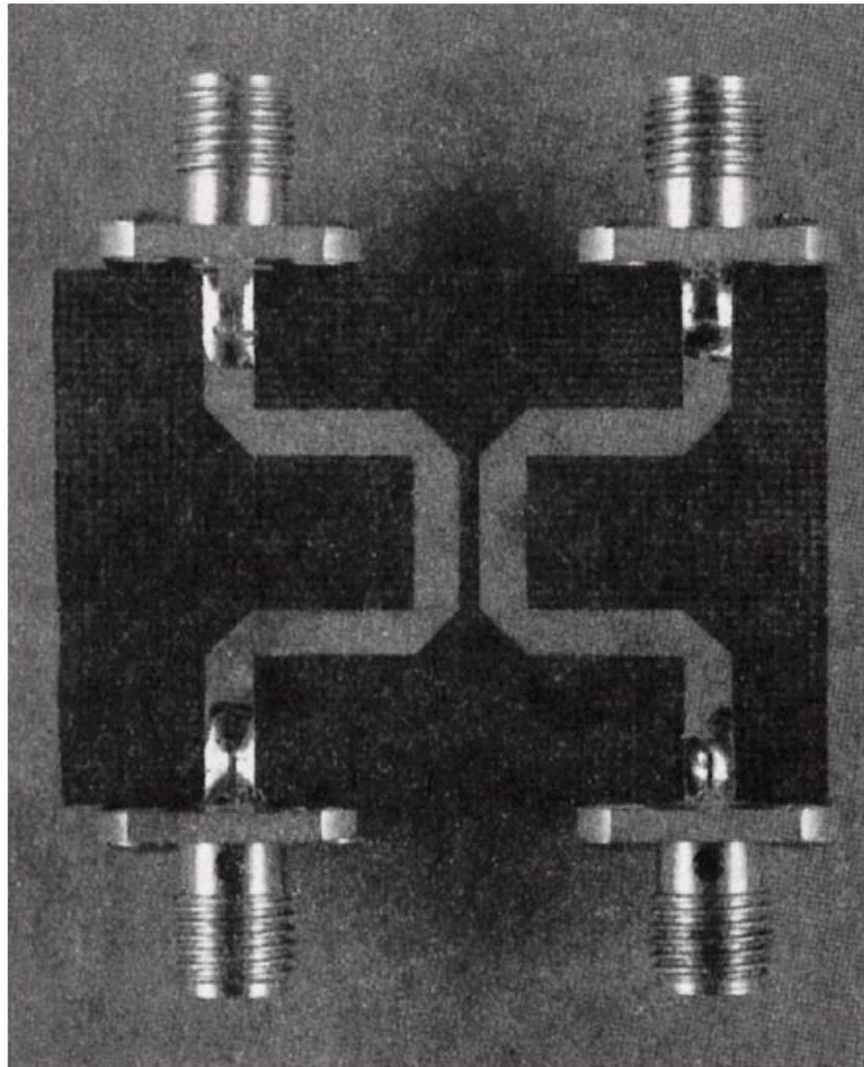

# Coupled line coupler



# Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.etti.tuiasi.ro>
- [rdamian@etti.tuiasi.ro](mailto:rdamian@etti.tuiasi.ro)