

Lecture 7
2017/2018

Microwave Devices and Circuits for Radiocommunications

Materials

- RF-OPTO
 - <http://rf-opto.etti.tuiasi.ro>
- **David Pozar, “Microwave Engineering”,**
Wiley; 4th edition , 2011
 - 1 exam problem ← Pozar
- Photos
 - sent by email: rdamian@etti.tuiasi.ro
 - used at lectures/laboratory

Software

- ADS 2016
- EmPro 2015
- based on IP from outside university or campus



Date:

Grupa	5601 (2017/2018)
Specializarea	Master Retele de Comunicatii
Marca	857

[Acceseaza ca acest student](#) | [Cere acces la licente](#)

Note obtinute

Disciplina	Tip	Data	Descriere	Nota	Puncte	Obs.
TMPAW			Tehnici moderne de proiectare a aplicatiilor web			
	N	29/05/2017	Nota finala	10	-	

Nume

Email

Cod de verificare

Trimite

Software

Advanced Design System Premier High-Frequency and High Speed Design Platform

2016.01



© Keysight Technologies 1985-2016

Advanced Design System

Select a product license

You have more than one product

Description

ADS Inclusive

GoldenGate All In

Update Availability

Legend: License available License in use or not available

ADS Inclusive


License is available

Number of licenses: 50

Used: 3


Version: 2018.07

Expires: 30-jul-

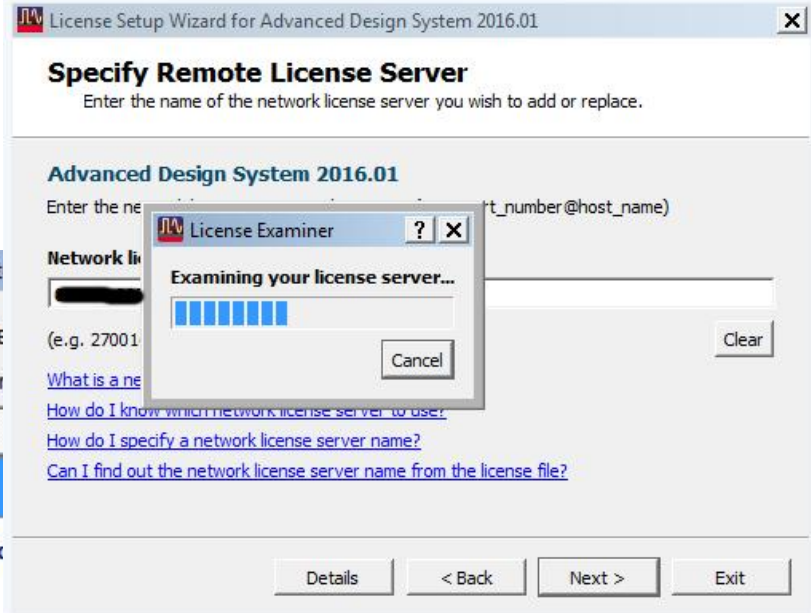


Matching

- Source matched to load ?

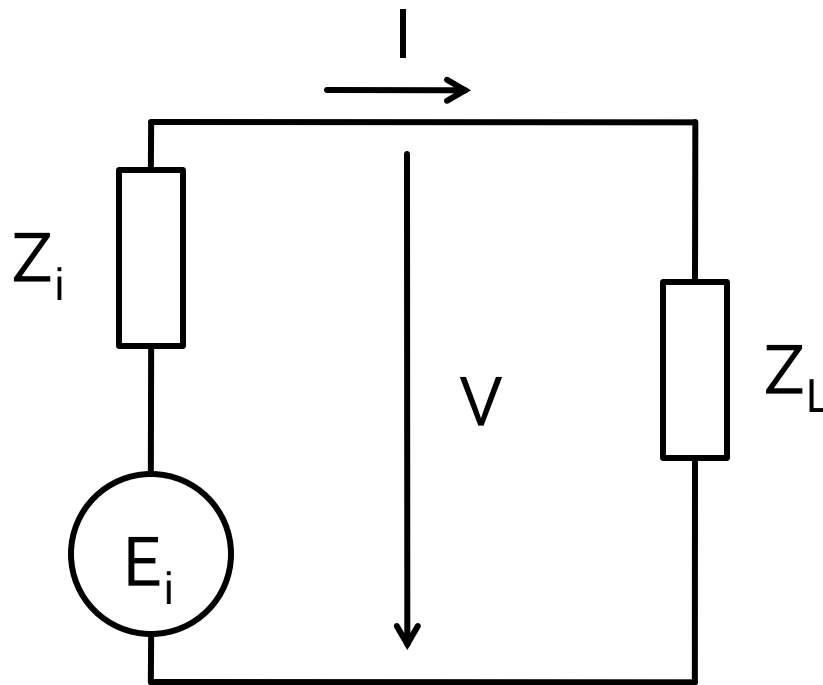

- impedance values ?
- existence of reflections ?


Matching, example

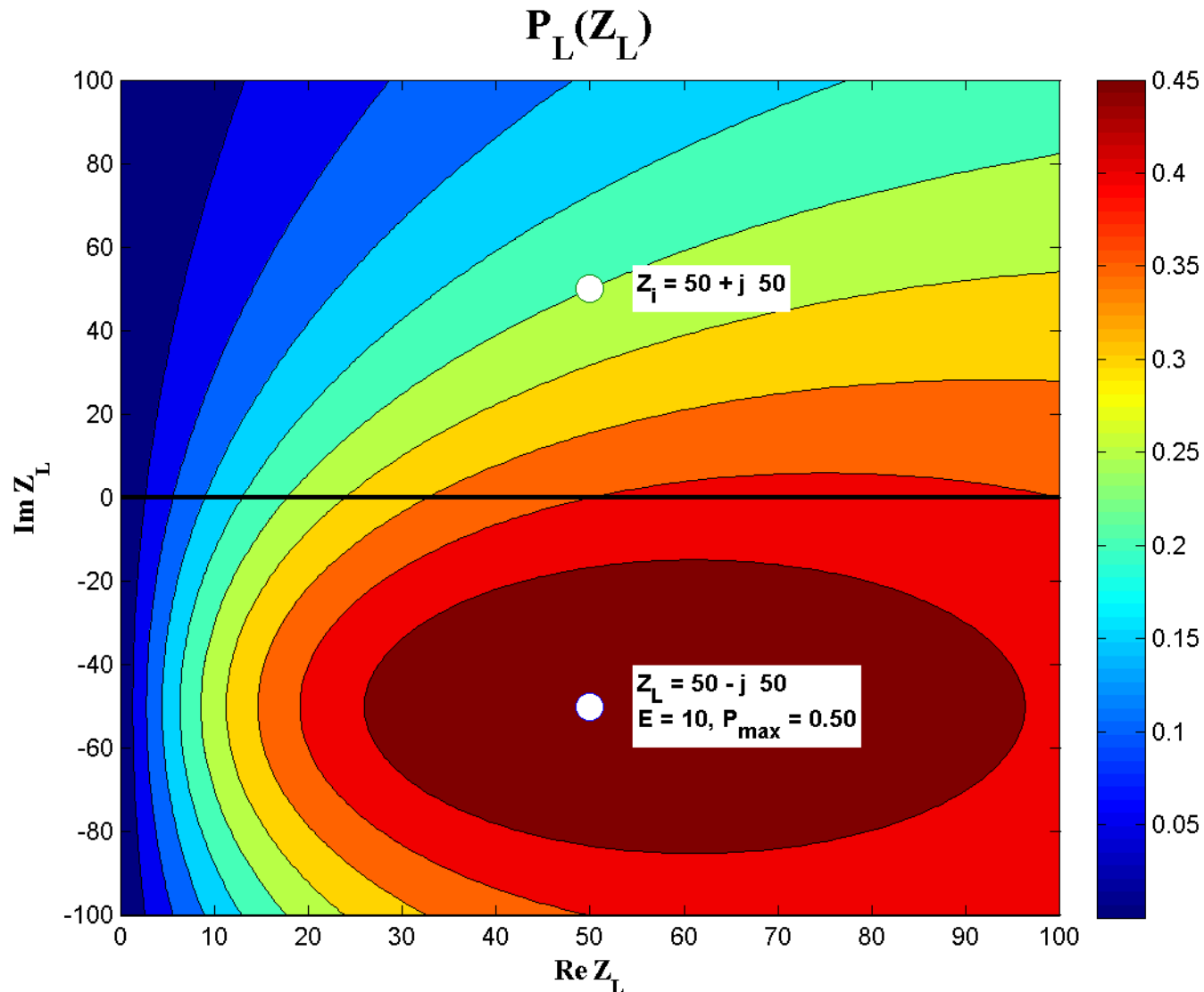

$$Z_L = Z_i^*$$

$$\Gamma_L = \Gamma_i^*$$

Reflection and power / Model

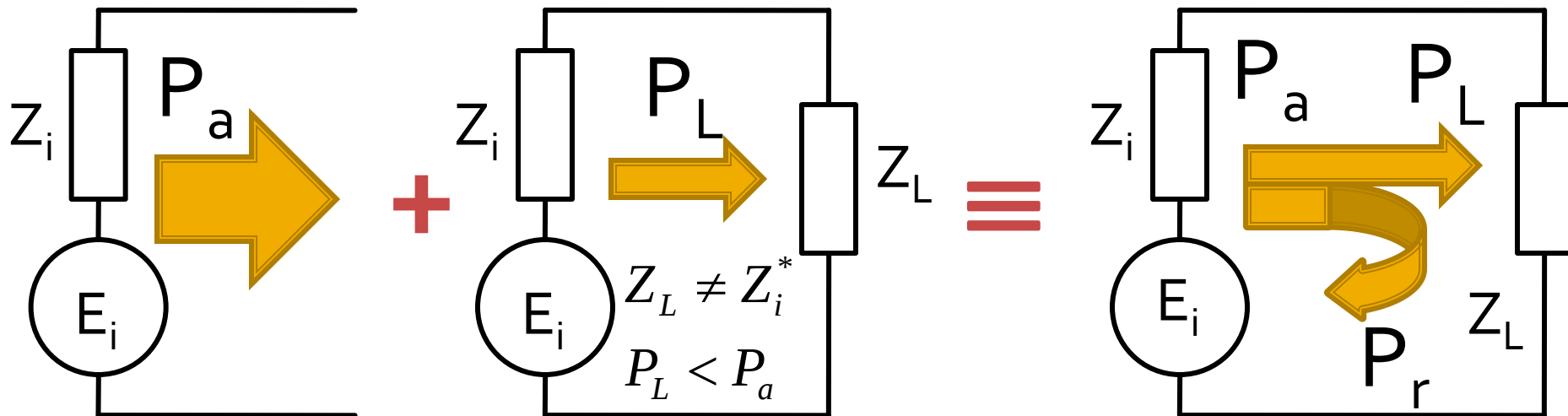


- The source has the ability to send to the load a certain maximum power (available power) P_a
- For a particular load the power sent to the load is less than the maximum (mismatch) $P_L < P_a$
- The phenomenon is **"as if"** (model) part of the input power is reflected $P_r = P_a - P_L$
- The power is a **scalar** !

TEM transmission lines

The lossless line

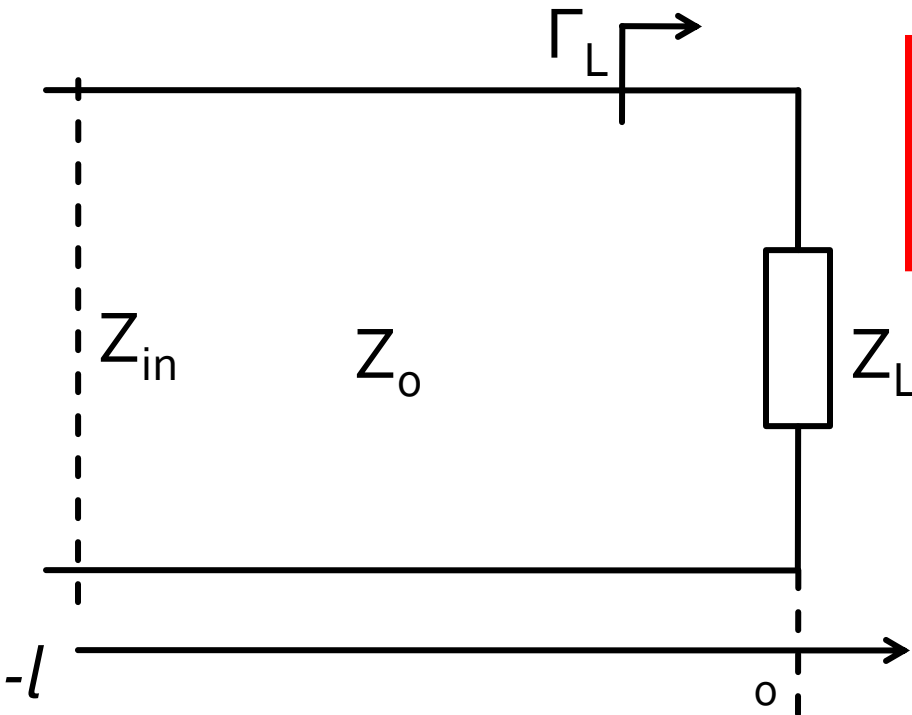
- input impedance of a length l of transmission line with characteristic impedance Z_0 , loaded with an arbitrary impedance Z_L



$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

Microwave Network Analysis


Scattering matrix – S

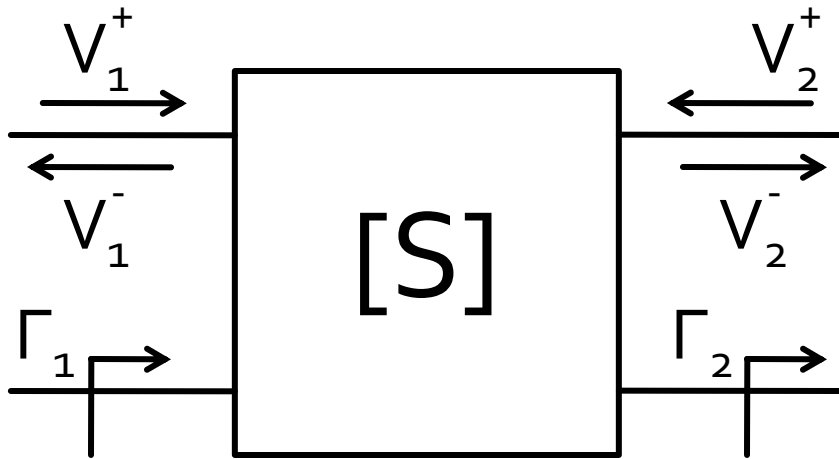

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$
$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+=0} = \Gamma_1|_{\Gamma_2=0}$$
$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+=0} = T_{21}|_{\Gamma_2=0}$$

- S_{11} is the reflection coefficient seen looking into port **1** when port **2** is terminated in matched load
- S_{21} is the transmission coefficient from port **1** (**second index**) to port **2** (**first index**) when port **2** is terminated in matched load

Scattering matrix – S

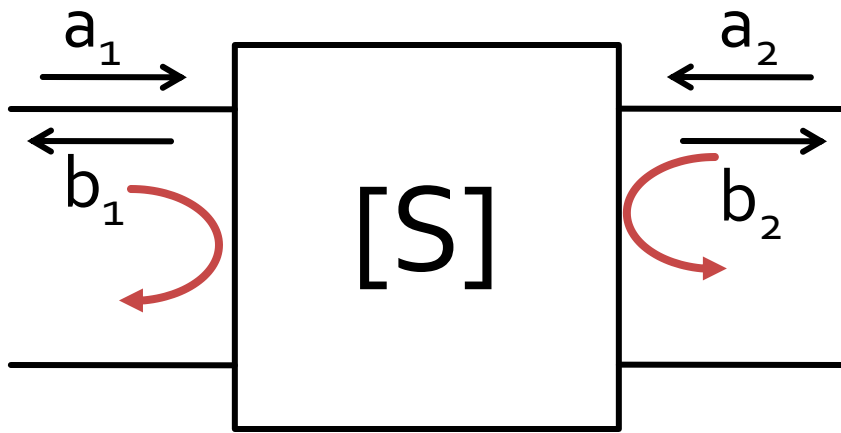


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

- S_{11} and S_{22} are reflection coefficients at ports 1 and 2 when the other port is matched

Scattering matrix – S

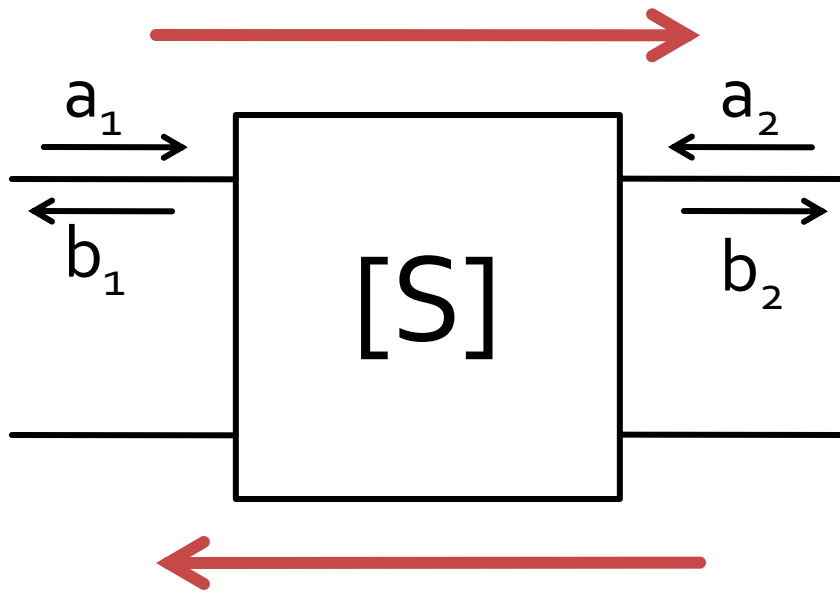


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$$

- S_{21} and S_{12} are signal amplitude gain when the other port is matched

Scattering matrix – S

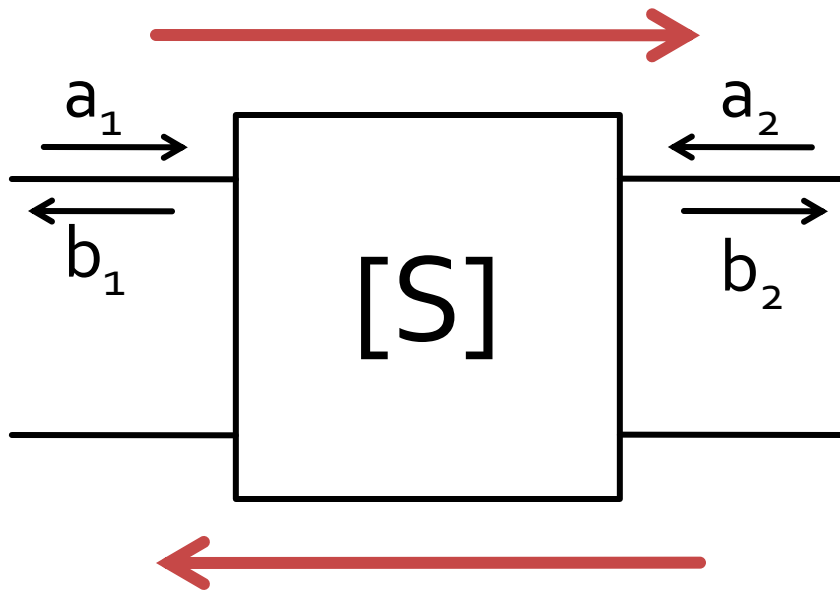

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$


$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- a, b
 - information about signal power **AND** signal phase
- S_{ij}
 - network effect (gain) over signal power **including** phase information

Impedance Matching




The Smith Chart

The Smith Chart

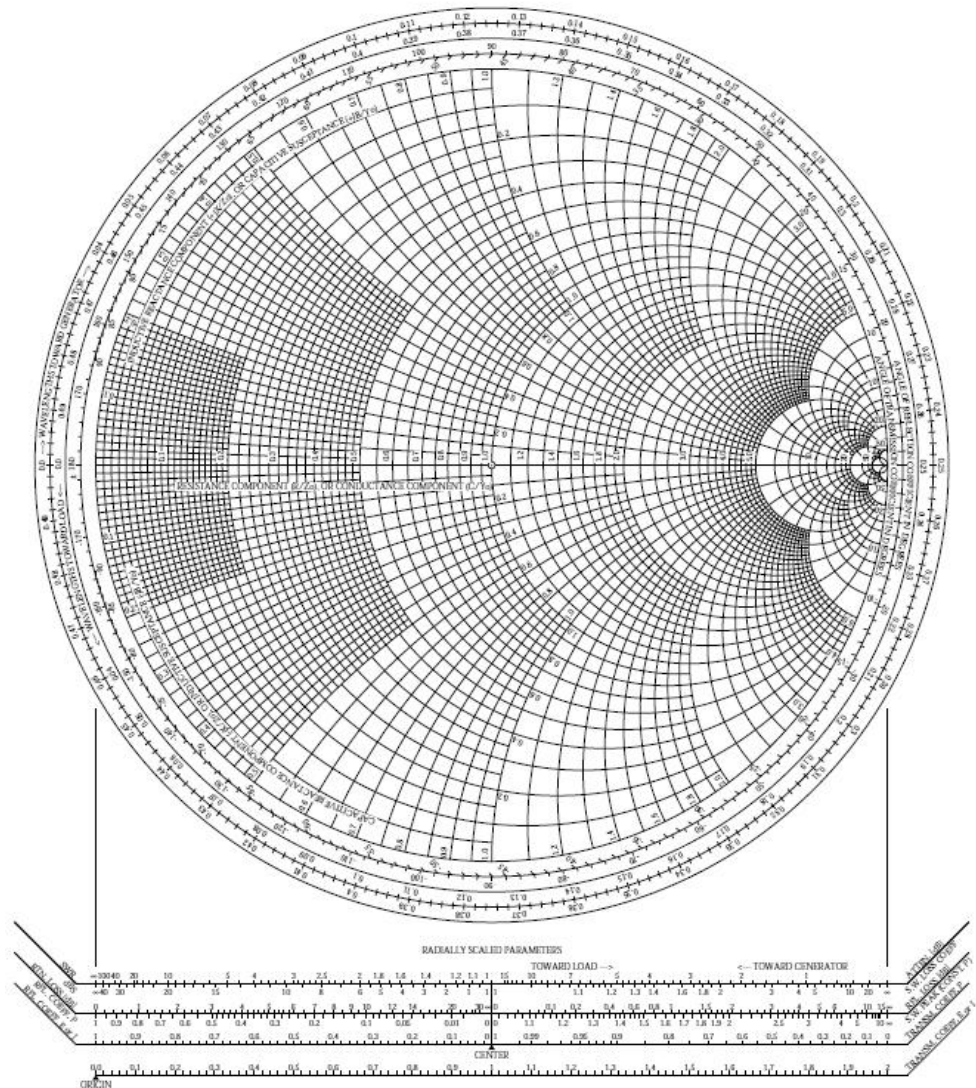


The Smith Chart

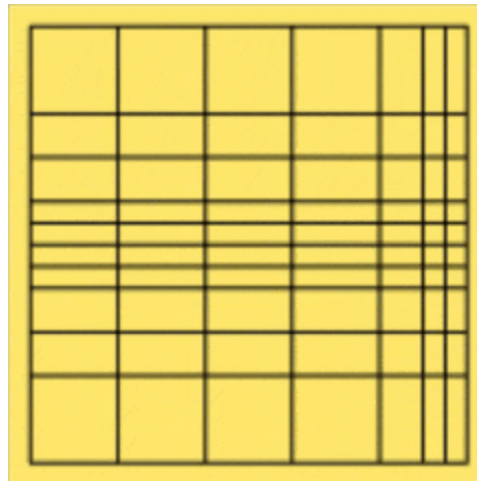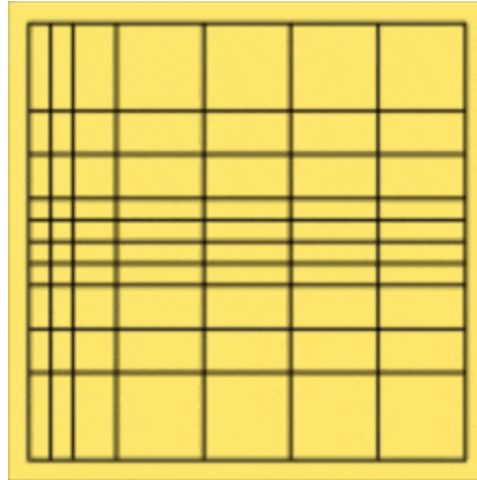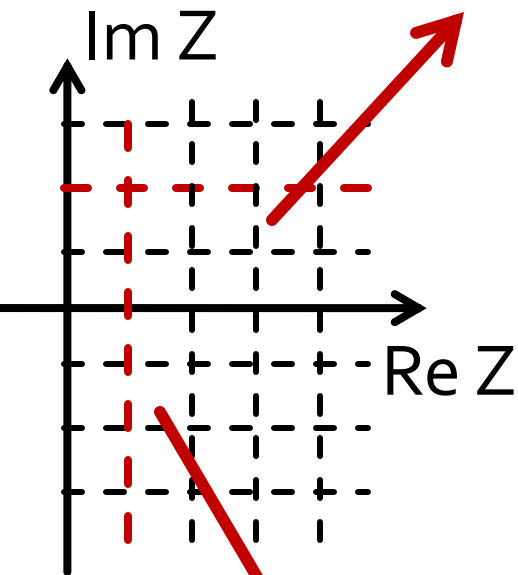
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$


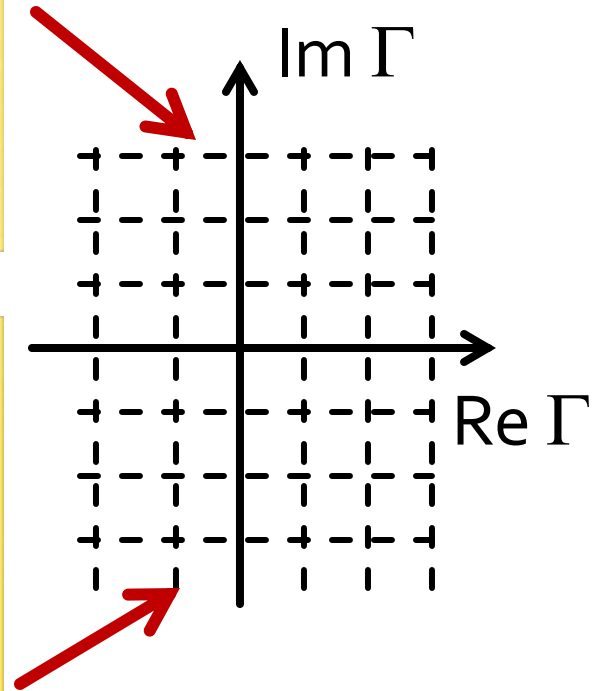
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Y_0 - Y_L}{Y_0 + Y_L} = \frac{1 - y_L}{1 + y_L}$$





The Smith Chart

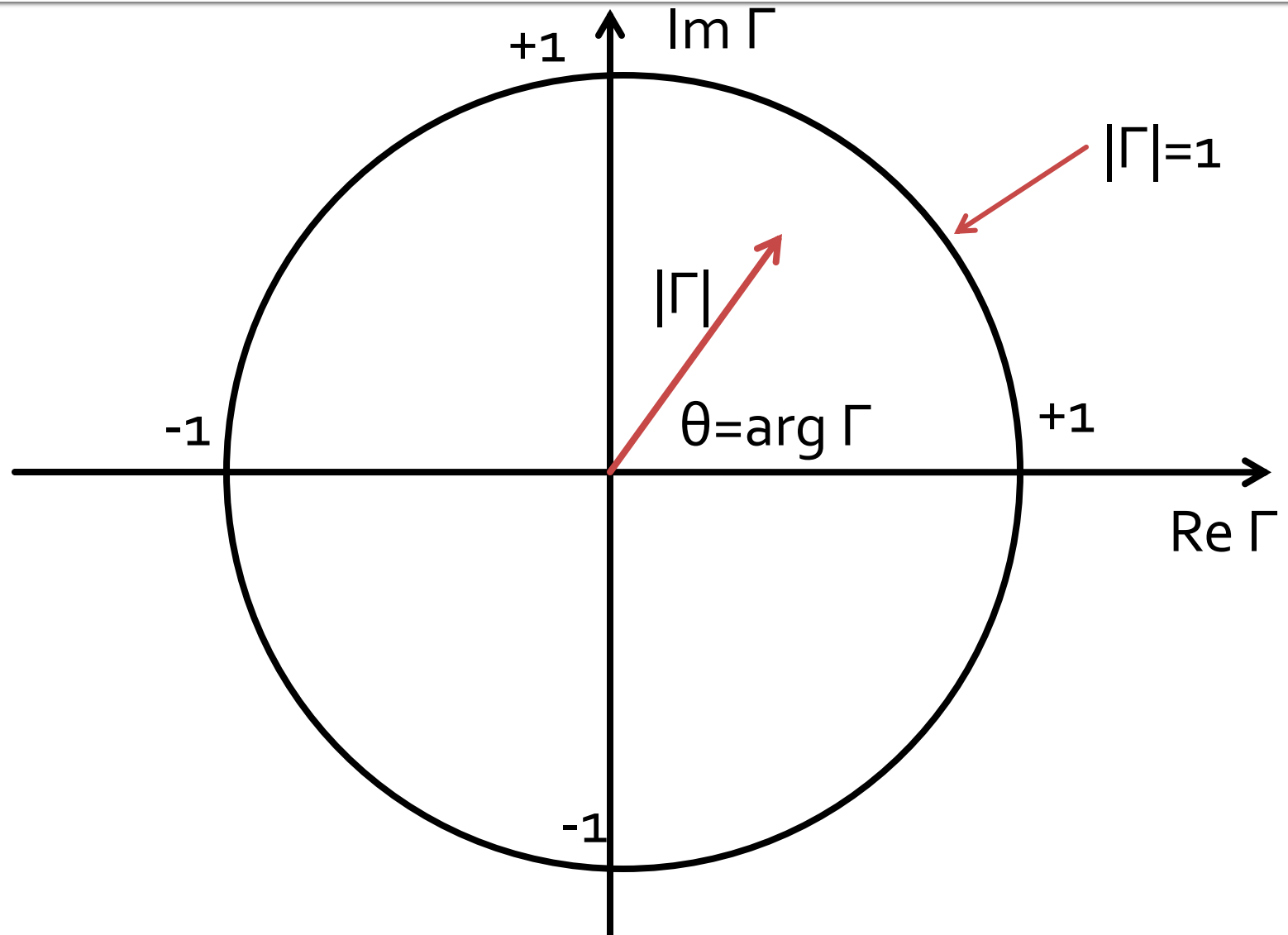

Impedance matching with lumped elements (L Networks)

Impedance Matching

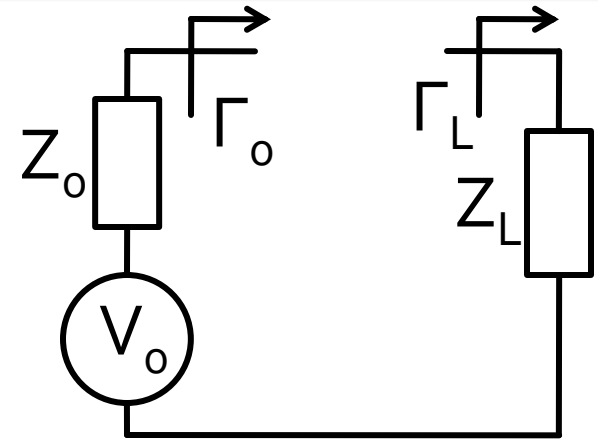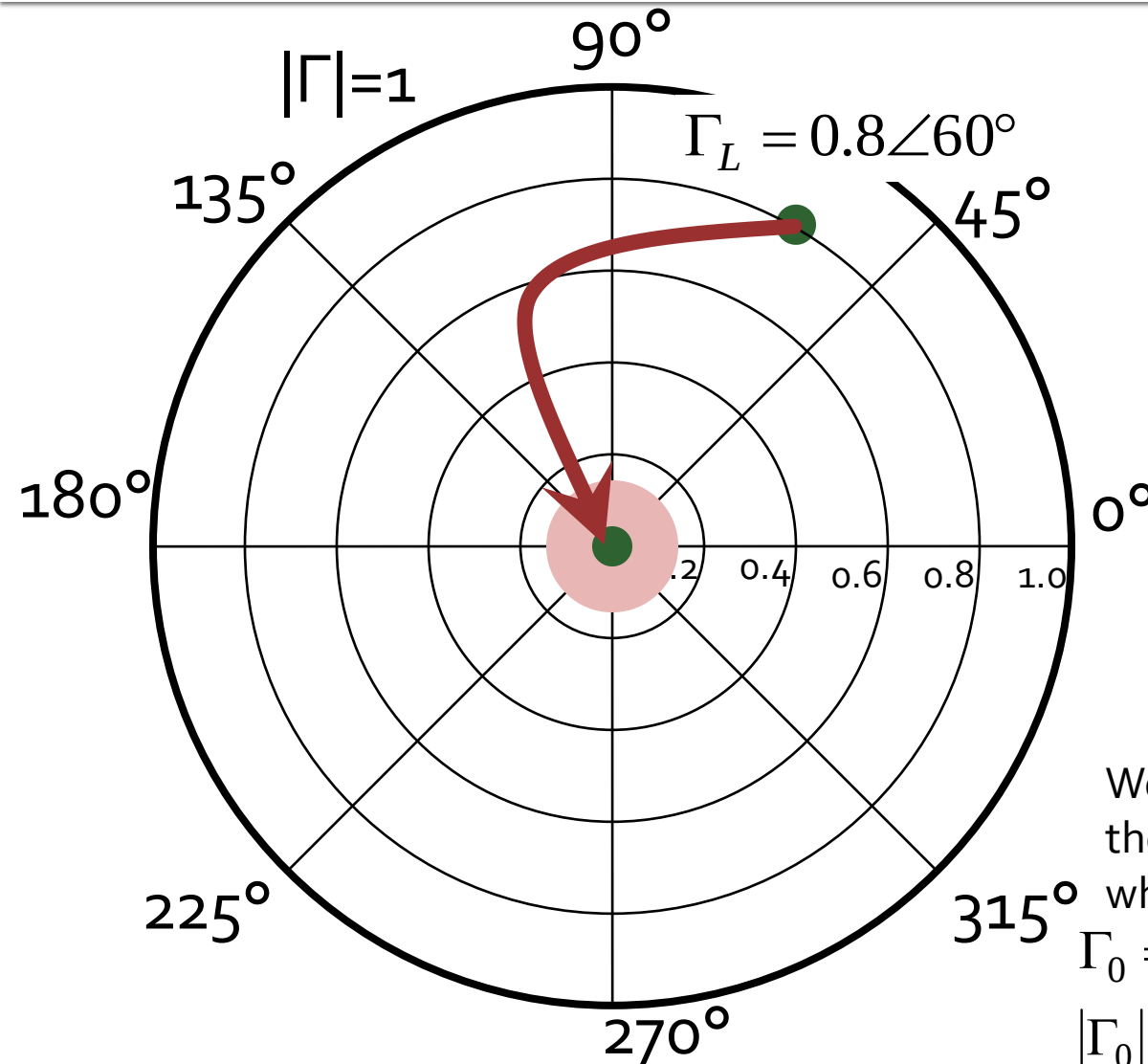The Smith Chart, reflection coefficient, impedance matching



Matching Z_L load to Z_o source.
We normalize Z_L over Z_o

$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

$$z_L = 0.429 + j \cdot 1.65$$


$$\Gamma_L = 0.8 \angle 60^\circ$$

We must move the point denoting the reflection coefficient in the area where with a Z_o source we have:




$$\Gamma_0 = 0 \quad \text{perfect match}$$

$$|\Gamma_0| \leq \Gamma_m \quad \text{"good enough" match}$$


Smith chart, $r=1$ and $g=1$

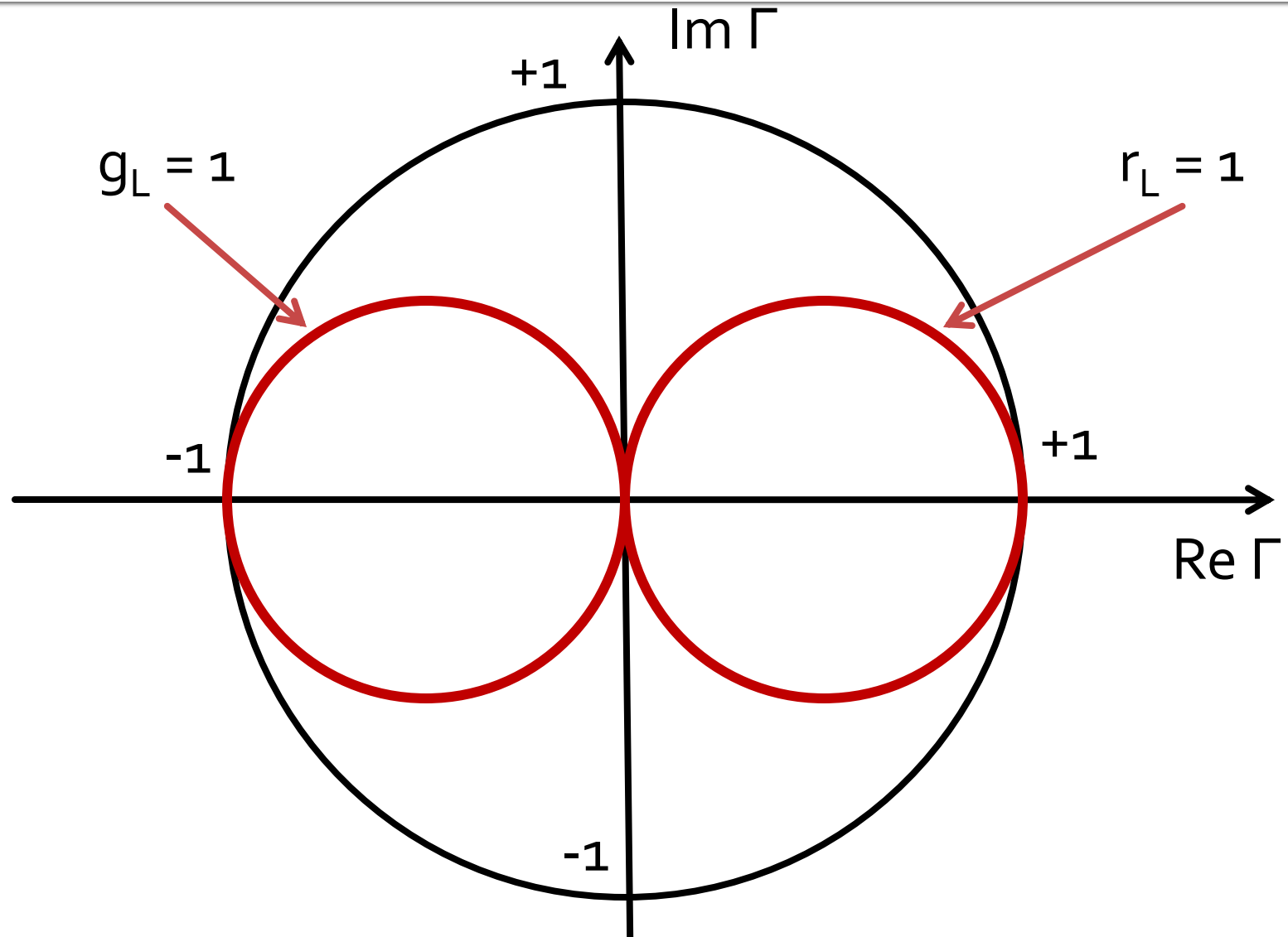


series L, shunt C / shunt C, series L

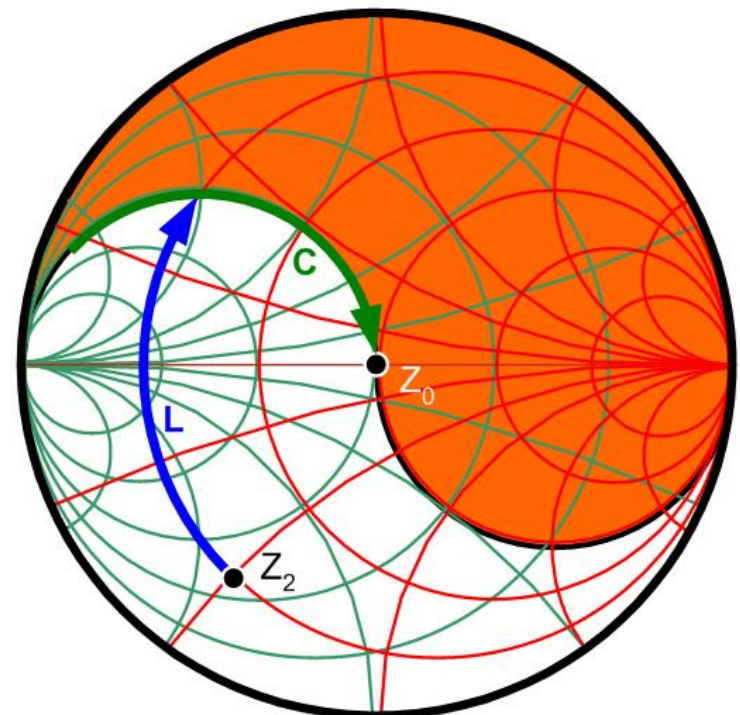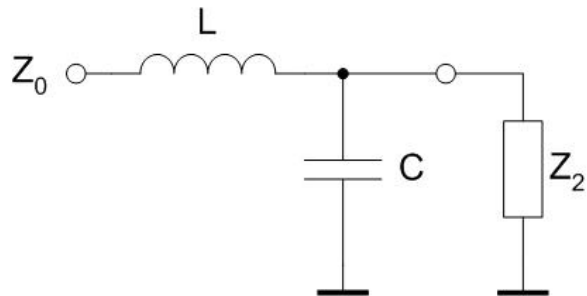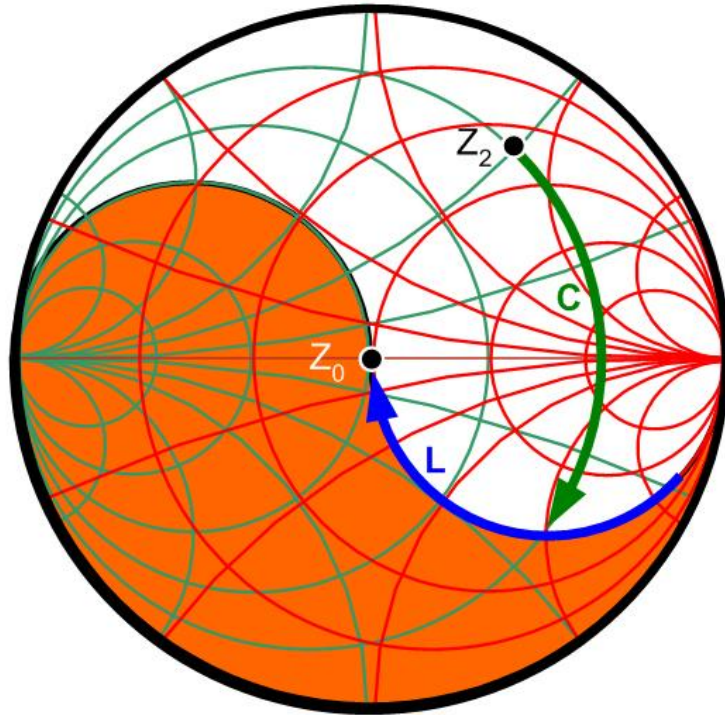

Forbidden area for
current network

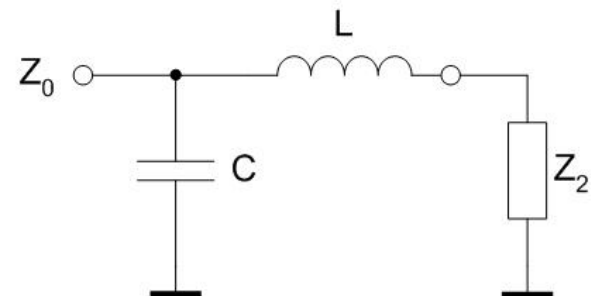

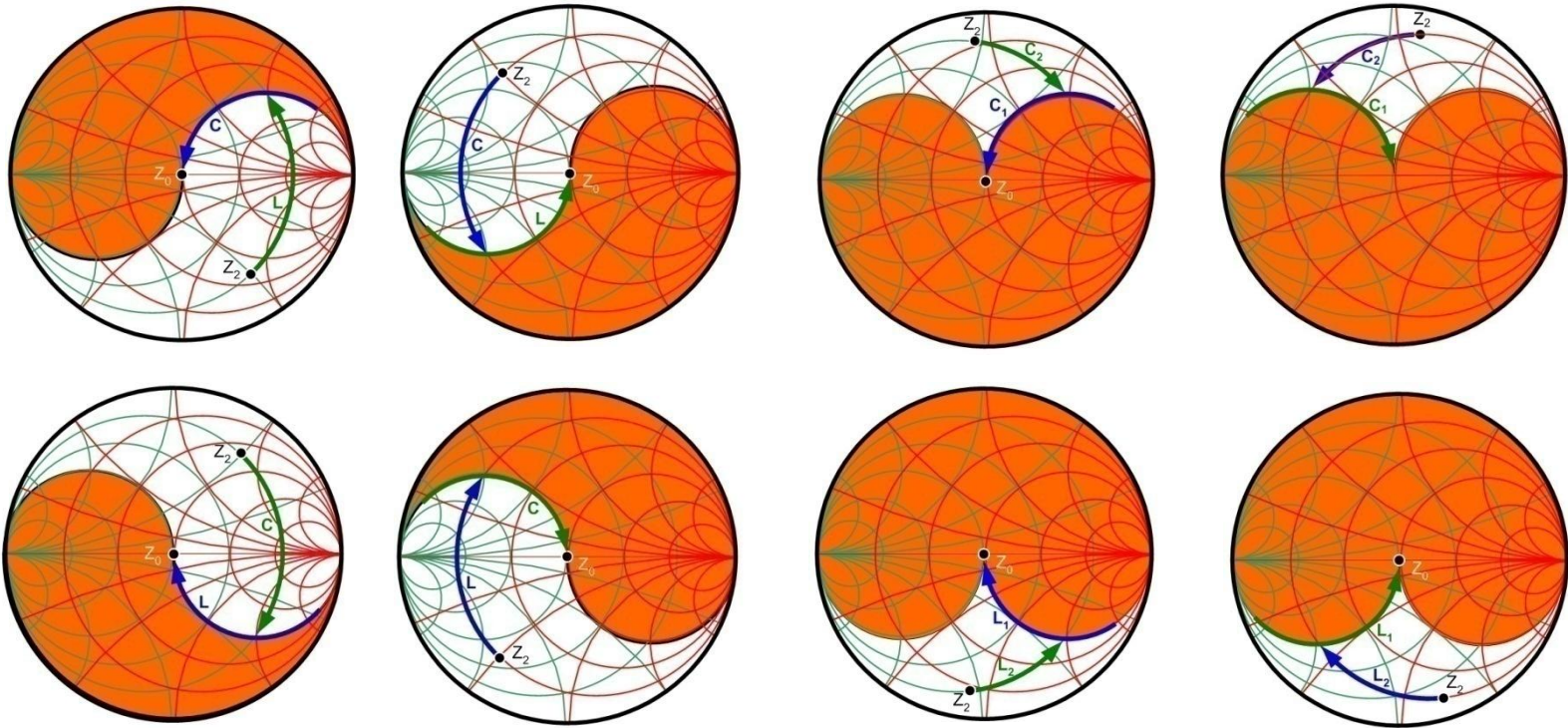Matching with 2 reactive elements (L Networks)



Forbidden area for
current network

Impedance Matching with Stubs


Impedance Matching

Stub

- **Stub** (en)="rest, ciot, cotor, capăt" (ro)
- We avoid the necessity to use lumped elements
- Matching is achieved (with higher accuracy) using usual Z_0 transmission lines of the circuit
- We use one or more lengths of transmission line (stub) connected either in parallel or in series with the transmission feed line :
 - open-circuited
 - short-circuited
- Usually open-circuited transmission lines are easier to implement and are preferred


Single stub tuning

- Shunt Stub

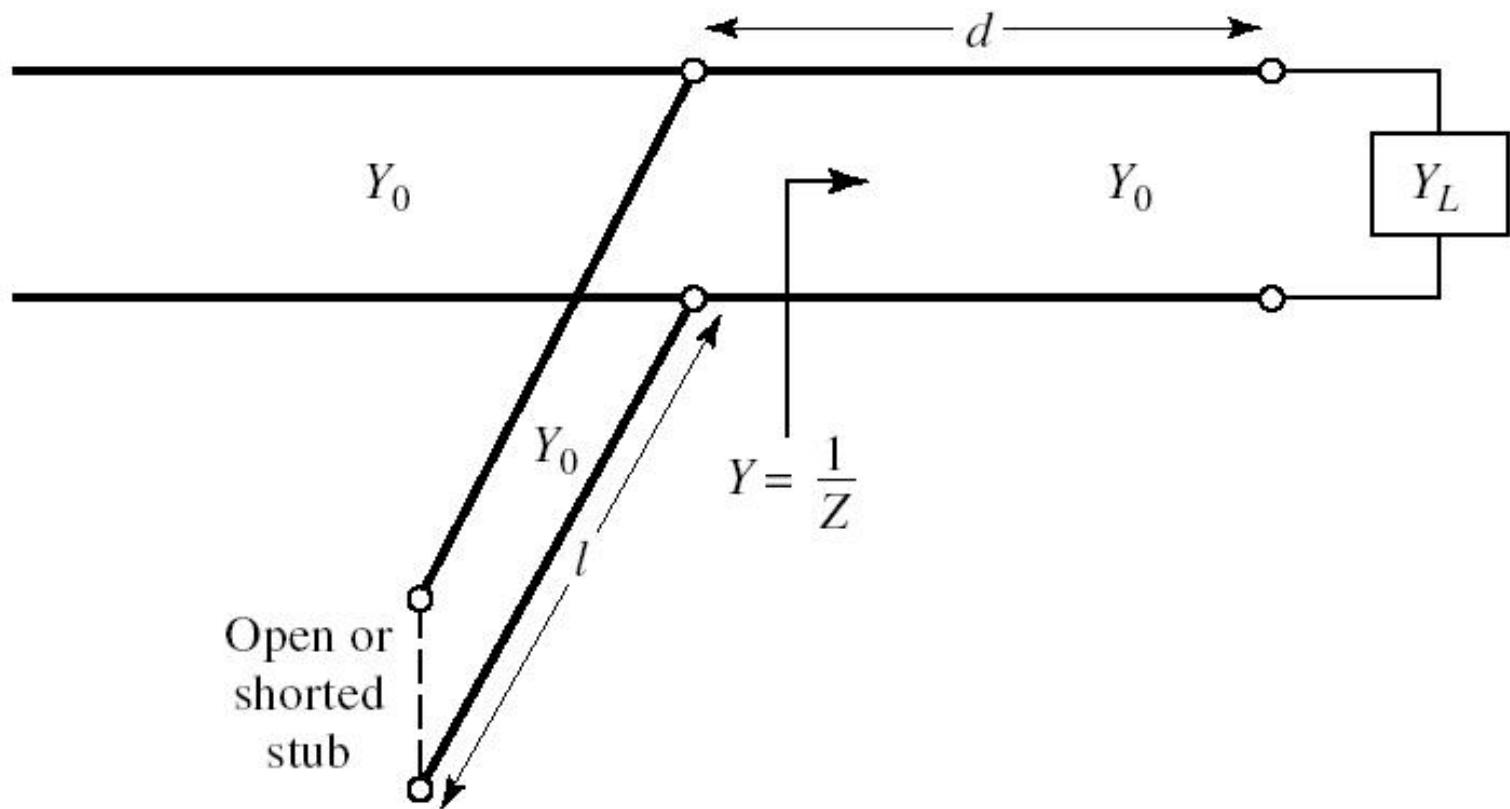


Single stub tuning

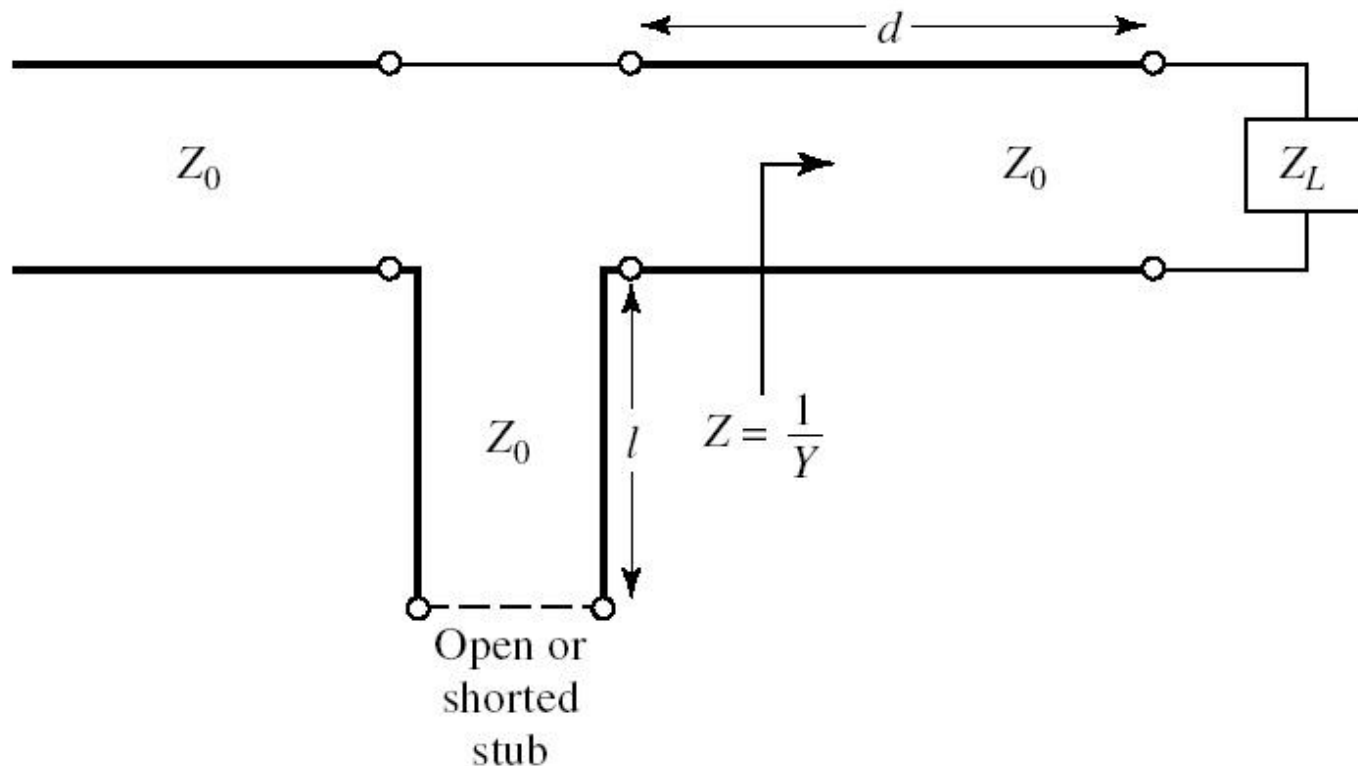- Series Stub
- difficult to realize in single conductor line technologies (microstrip)




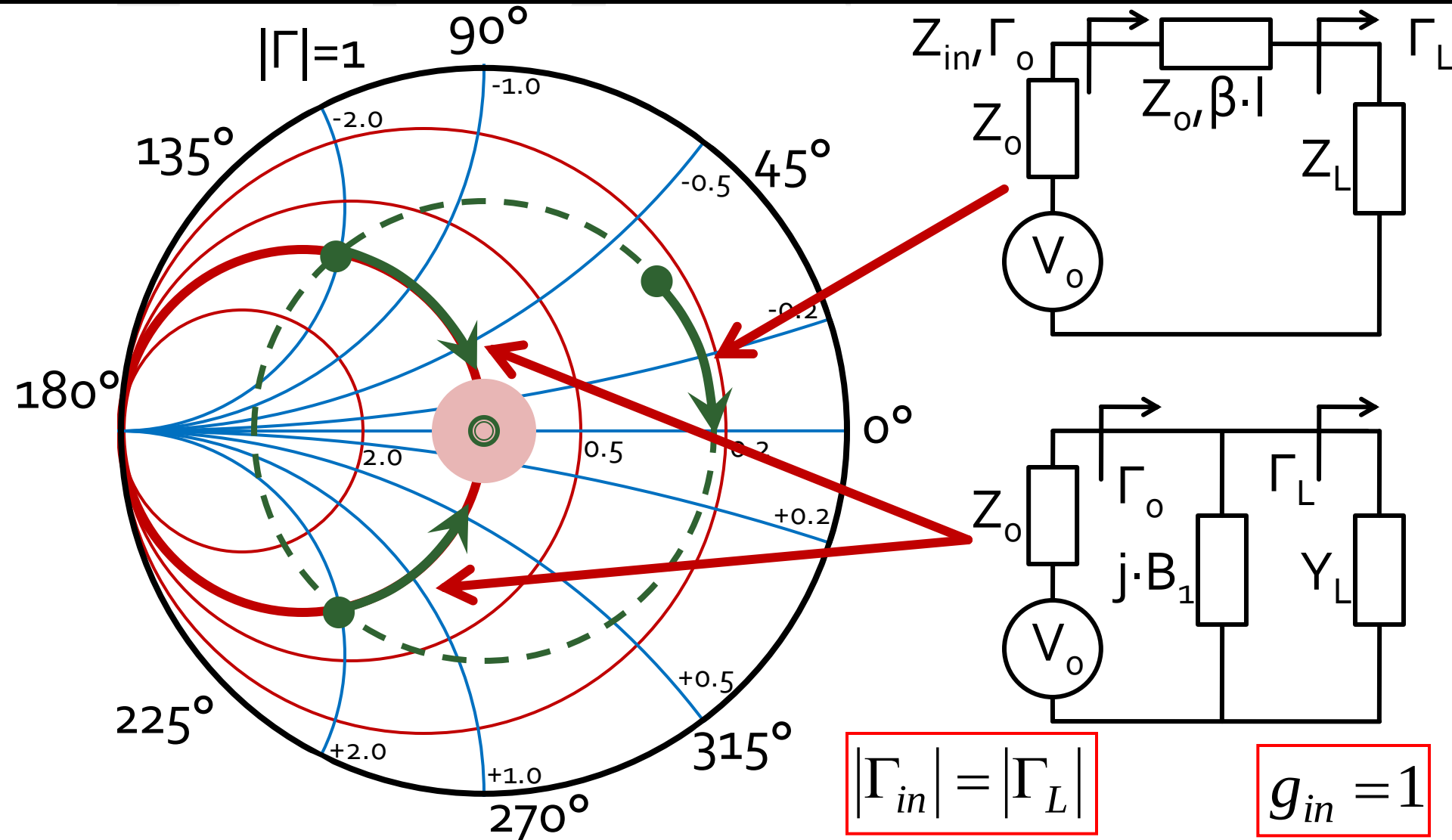Matching, series line + shunt susceptance



Analytical solution, reflection coefficient

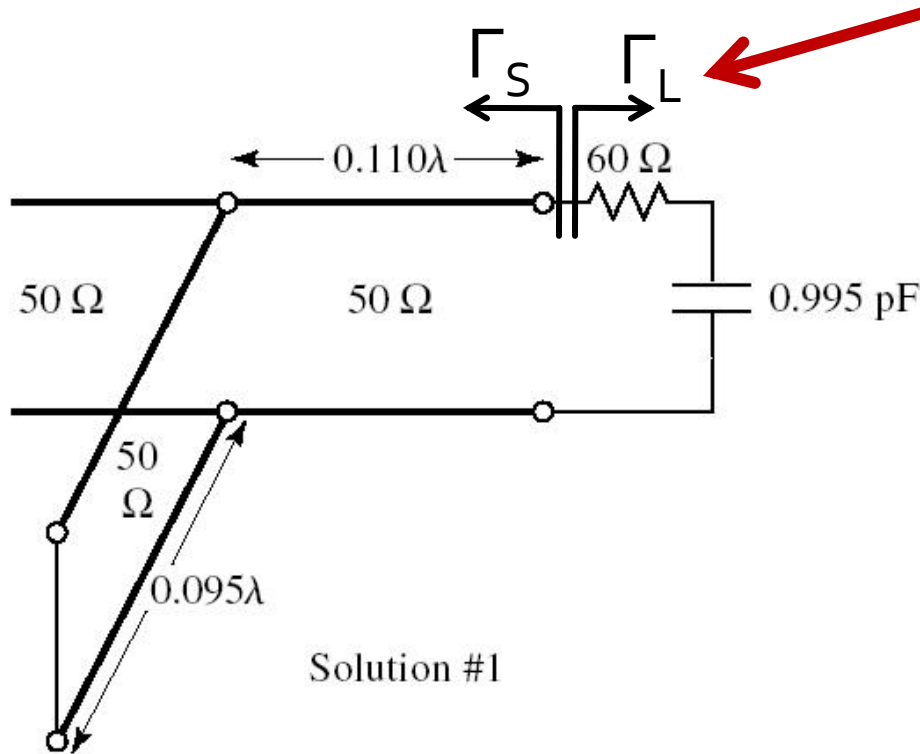- load: $60\ \Omega$ series with $0.995\ \text{pF}$ at 2GHz



$$Z_L = R_L + \frac{1}{j \cdot \omega \cdot C_L} = 60\ \Omega - j \cdot 79.977\ \Omega$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 0.405 - j \cdot 0.432$$

$$Y_L = \frac{1}{Z_L} = 0.006\text{S} + j \cdot 0.008\text{S}$$


$$y_L = \frac{Y_L}{Y_0} = 0.3 + j \cdot 0.4$$

- matching requires obtaining conjugate value for Γ

$$\Gamma_S = \Gamma_L^* = 0.405 + j \cdot 0.432 \quad \Gamma_S = 0.593 \angle 46.85^\circ \quad |\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ$$

Analytical solution, Γ

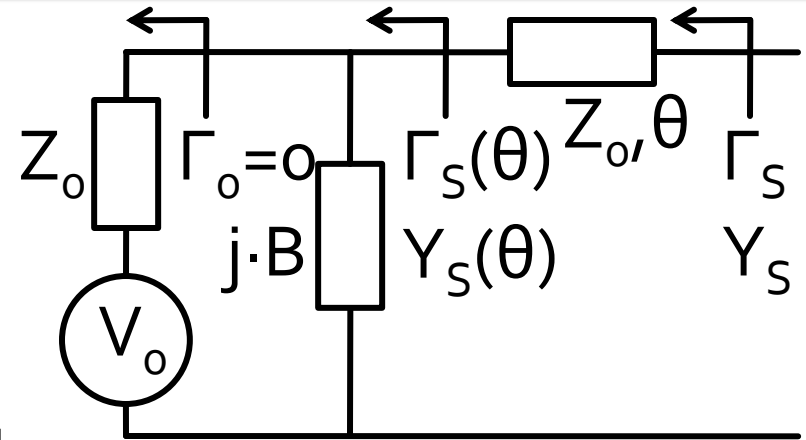- series line
 - electrical length $E = \beta \cdot l = \theta$
 - moves the reflection coefficient on the circle $g=1$
- shunt stub
 - electrical length $E = \beta \cdot l_{sp} = \theta_{sp}$
 - moves the reflection coefficient to the center of the Smith Chart ($\Gamma_o = 0$)



$$y_s = \frac{Y_s}{Y_0} = Y_s \cdot Z_0 = Y_s \cdot 50\Omega$$

$$y_s = \frac{1 - \Gamma_s}{1 + \Gamma_s} = 0.3 - j \cdot 0.4$$

$$\Gamma_s(\theta) = [\Gamma_L(\theta)]^* = [\Gamma_L \cdot e^{-2j\theta}]^*$$

$$\Gamma_s(\theta) = \Gamma_L^* \cdot e^{2j\theta} = \Gamma_s \cdot e^{2j\theta}$$

$$y_s(\theta) = \frac{1 - \Gamma_s(\theta)}{1 + \Gamma_s(\theta)} = \frac{1 - \Gamma_s \cdot e^{2j\theta}}{1 + \Gamma_s \cdot e^{2j\theta}}$$

Analytical solution, Γ , series line

- After the series line with electrical length θ :

$$\operatorname{Re}[y_s(\theta)] = 1$$

$$\operatorname{Im}[y_s(\theta)] = B$$

$$\operatorname{Re}[y_s(\theta)] = \frac{1}{2} \cdot [y_s(\theta) + y_s^*(\theta)]$$

$$\operatorname{Im}[y_s(\theta)] = \frac{1}{2j} \cdot [y_s(\theta) - y_s^*(\theta)]$$

$$\operatorname{Re}[y_s(\theta)] = \frac{1}{2} \cdot \left[\frac{1 - \Gamma_s \cdot e^{2j\theta}}{1 + \Gamma_s \cdot e^{2j\theta}} + \frac{1 - \Gamma_s^* \cdot e^{-2j\theta}}{1 + \Gamma_s^* \cdot e^{-2j\theta}} \right]$$

$$\Gamma_s = |\Gamma_s| \cdot e^{j\varphi}$$

$$\operatorname{Re}[y_s(\theta)] = \frac{1}{2} \cdot \left[\frac{(1 - |\Gamma_s| \cdot e^{j(\varphi+2\theta)}) \cdot (1 + |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) + (1 - |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 + |\Gamma_s| \cdot e^{j(\varphi+2\theta)})}{(1 + |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 + |\Gamma_s| \cdot e^{j(\varphi+2\theta)})} \right]$$

$$\operatorname{Re}[y_s(\theta)] = \frac{1}{2} \cdot \left[\frac{2 - 2 \cdot |\Gamma_s|^2}{1 + |\Gamma_s|^2 + 2 \cdot |\Gamma_s| \cdot \cos(\varphi + 2\theta)} \right] = 1 \Rightarrow \boxed{\cos(\varphi + 2\theta) = -|\Gamma_s|}$$

Analytical solution, Γ , series line

- Equations for computing the series line θ :

$$\operatorname{Re}[y_S(\theta)] = 1 \Rightarrow \cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = |\Gamma_S| \cdot e^{j\varphi} \quad \Gamma_S = 0.593 \angle 46.85^\circ \quad |\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ$$

- two solutions possible, in the $0 \div 180^\circ$ range (add $\lambda/2 \Leftrightarrow 180^\circ$ as needed)

$$\theta = \frac{1}{2} \cdot [\pm \cos^{-1}(-|\Gamma_S|) - \varphi + k \cdot 360^\circ] = \frac{1}{2} \cdot [\pm \cos^{-1}(-|\Gamma_S|) - \varphi] + k \cdot 180^\circ$$

$$\forall k \in \mathbb{N}$$

$$\cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^\circ$$

$$(46.85^\circ + 2\theta) = \begin{cases} +126.35^\circ \\ -126.35^\circ \end{cases}$$

$$\theta = \begin{cases} +39.7^\circ \\ -86.6^\circ + 180^\circ = +93.4^\circ \end{cases}$$

Analytical solution, Γ , shunt stub

- Equations for computing the shunt stub θ_{sp} :

$$\operatorname{Re}[y_s(\theta)] = 1 \qquad \cos(\varphi + 2\theta) = -|\Gamma_s|$$

$$\operatorname{Im}[y_s(\theta)] = \frac{1}{2j} \cdot \left[\frac{1 - \Gamma_s \cdot e^{2j\theta}}{1 + \Gamma_s \cdot e^{2j\theta}} - \frac{1 - \Gamma_s^* \cdot e^{-2j\theta}}{1 + \Gamma_s^* \cdot e^{-2j\theta}} \right] \qquad \Gamma_s = |\Gamma_s| \cdot e^{j\varphi}$$

$$\operatorname{Im}[y_s(\theta)] = \frac{1}{2j} \cdot \left[\frac{(1 - |\Gamma_s| \cdot e^{j(\varphi+2\theta)}) \cdot (1 + |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) - (1 - |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 + |\Gamma_s| \cdot e^{j(\varphi+2\theta)})}{(1 + |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 + |\Gamma_s| \cdot e^{j(\varphi+2\theta)})} \right]$$

$$\operatorname{Im}[y_s(\theta)] = \frac{1}{2j} \cdot \left[\frac{2 \cdot |\Gamma_s| \cdot e^{-j(\varphi+2\theta)} - 2 \cdot |\Gamma_s| \cdot e^{+j(\varphi+2\theta)}}{1 + |\Gamma_s|^2 + 2 \cdot |\Gamma_s| \cdot \cos(\varphi + 2\theta)} \right] = \frac{-2 \cdot |\Gamma_s| \cdot \sin(\varphi + 2\theta)}{1 + |\Gamma_s|^2 + 2 \cdot |\Gamma_s| \cdot \cos(\varphi + 2\theta)}$$

$$\cos(\varphi + 2\theta) = -|\Gamma_s| \Rightarrow \qquad \operatorname{Im}[y_s(\theta)] = \frac{-2 \cdot |\Gamma_s| \cdot \sin(\varphi + 2\theta)}{1 - |\Gamma_s|^2}$$

Analytical solution, Γ , shunt stub

- Equations for computing the shunt stub

$$\cos(\varphi + 2\theta) = -|\Gamma_S| \Rightarrow \sin(\varphi + 2\theta) = \pm \sqrt{1 - |\Gamma_S|^2}$$

$$\text{Im}[y_S(\theta)] = \frac{-2 \cdot |\Gamma_S| \cdot \sin(\varphi + 2\theta)}{1 - |\Gamma_S|^2} \Rightarrow \text{Im}[y_S(\theta)] = \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

- two cases

$$\varphi + 2\theta \in [0^\circ, 180^\circ] \Rightarrow \sin(\varphi + 2\theta) \geq 0 \quad \left\{ \begin{array}{l} \sin(\varphi + 2\theta) = \sqrt{1 - |\Gamma_S|^2} \\ \text{Im}[y_S(\theta)] = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} \end{array} \right.$$

$$\varphi + 2\theta \in (-180^\circ, 0^\circ) \Rightarrow \sin(\varphi + 2\theta) < 0 \quad \left\{ \begin{array}{l} \sin(\varphi + 2\theta) = -\sqrt{1 - |\Gamma_S|^2} \\ \text{Im}[y_S(\theta)] = \frac{2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} \end{array} \right.$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

Analytical solution, Γ , shunt stub

- We prefer (for microstrip) open circuited stub

$$Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$

- The normalized susceptance to be introduced to achieve the match
 - $Y(\theta)$ is the admittance seen **towards** the source, Z_0 parallel with $j \cdot B$

$$b = \text{Im} \left[\frac{Y_{in,oc}}{Y_0} \right] = \text{Im} \left[\frac{Z_0}{Z_{in,oc}} \right] = \tan \beta \cdot l = \text{Im}[y_s(\theta)]$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

Analytical solution, Γ

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = 0.593 \angle 46.85^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ \quad \cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **"+" solution** ↓

$$(46.85^\circ + 2\theta) = +126.35^\circ \quad \theta = +39.7^\circ \quad \text{Im } y_s = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.472$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_s) = -55.8^\circ (+180^\circ) \rightarrow \theta_{sp} = 124.2^\circ$$

- **"-" solution** ↓

$$(46.85^\circ + 2\theta) = -126.35^\circ \quad \theta = -86.6^\circ (+180^\circ) \rightarrow \theta = 93.4^\circ$$

$$\text{Im } y_s = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +1.472 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_s) = 55.8^\circ$$

Analytical solution, Γ

$$(\varphi + 2\theta) = \begin{cases} +126.35^\circ \\ -126.35^\circ \end{cases} \quad \theta = \begin{cases} 39.7^\circ \\ 93.4^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -1.472 \\ +1.472 \end{cases} \quad \theta_{sp} = \begin{cases} -55.8^\circ + 180^\circ = 124.2^\circ \\ +55.8^\circ \end{cases}$$



- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

$$l_1 = \frac{39.7^\circ}{360^\circ} \cdot \lambda = 0.110 \cdot \lambda$$

$$l_2 = \frac{124.2^\circ}{360^\circ} \cdot \lambda = 0.345 \cdot \lambda$$


$$l_1 = \frac{93.4^\circ}{360^\circ} \cdot \lambda = 0.259 \cdot \lambda$$
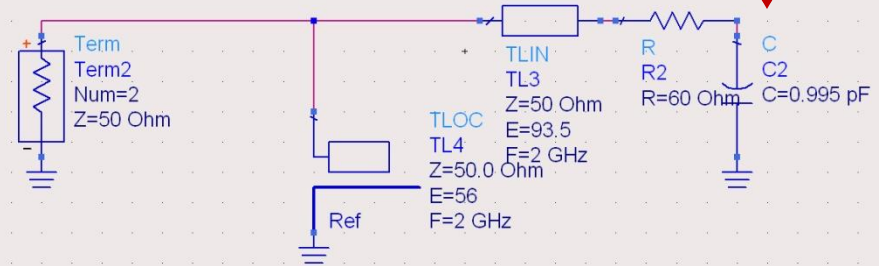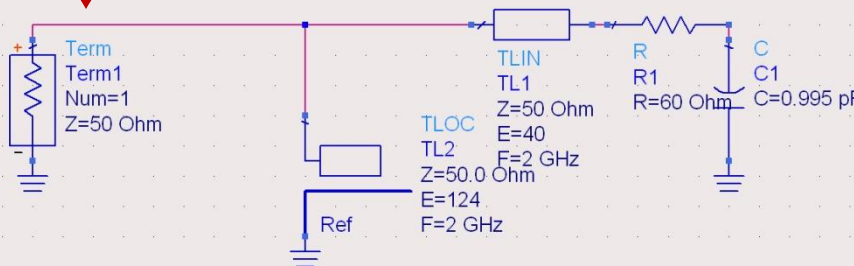
$$l_2 = \frac{55.8^\circ}{360^\circ} \cdot \lambda = 0.155 \cdot \lambda$$




Case 2, Series Stub

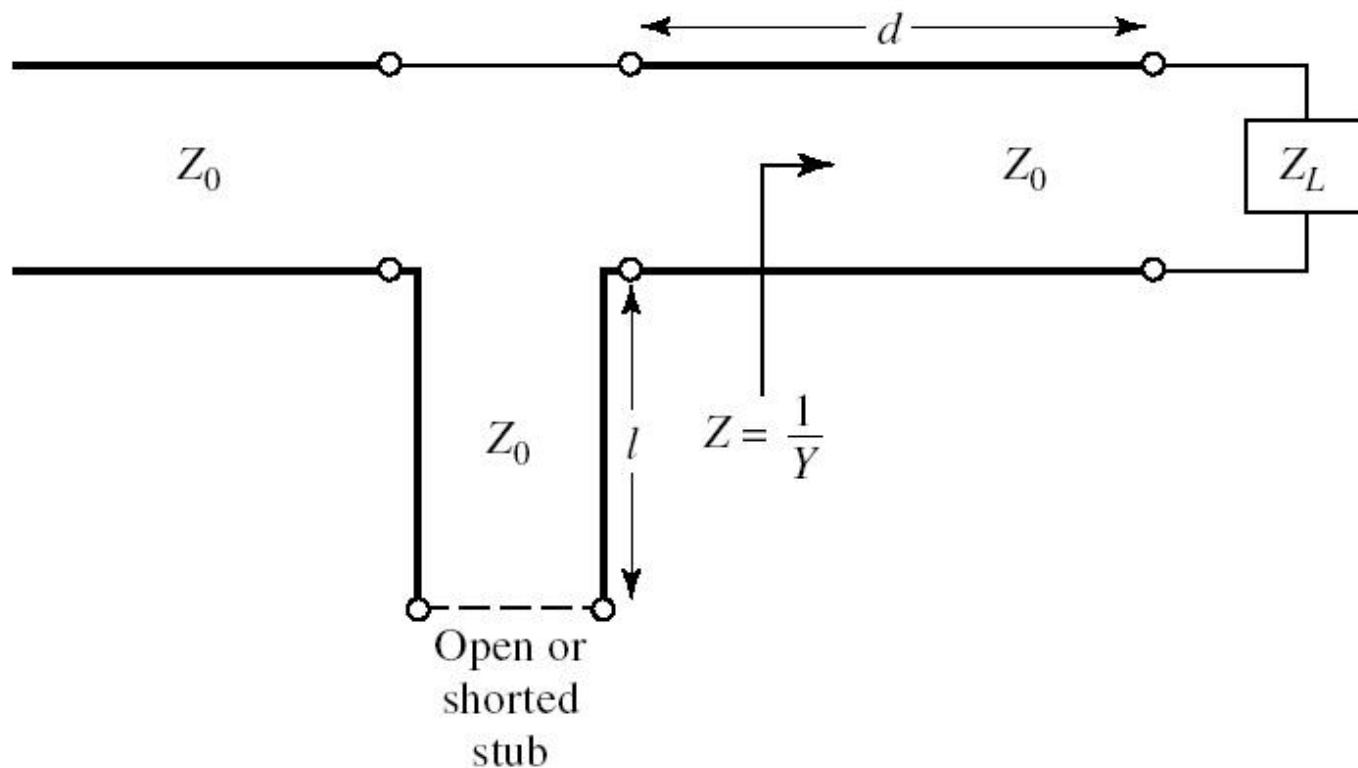- Series Stub
- difficult to realize in single conductor line technologies (microstrip)




Matching, series line + series reactance

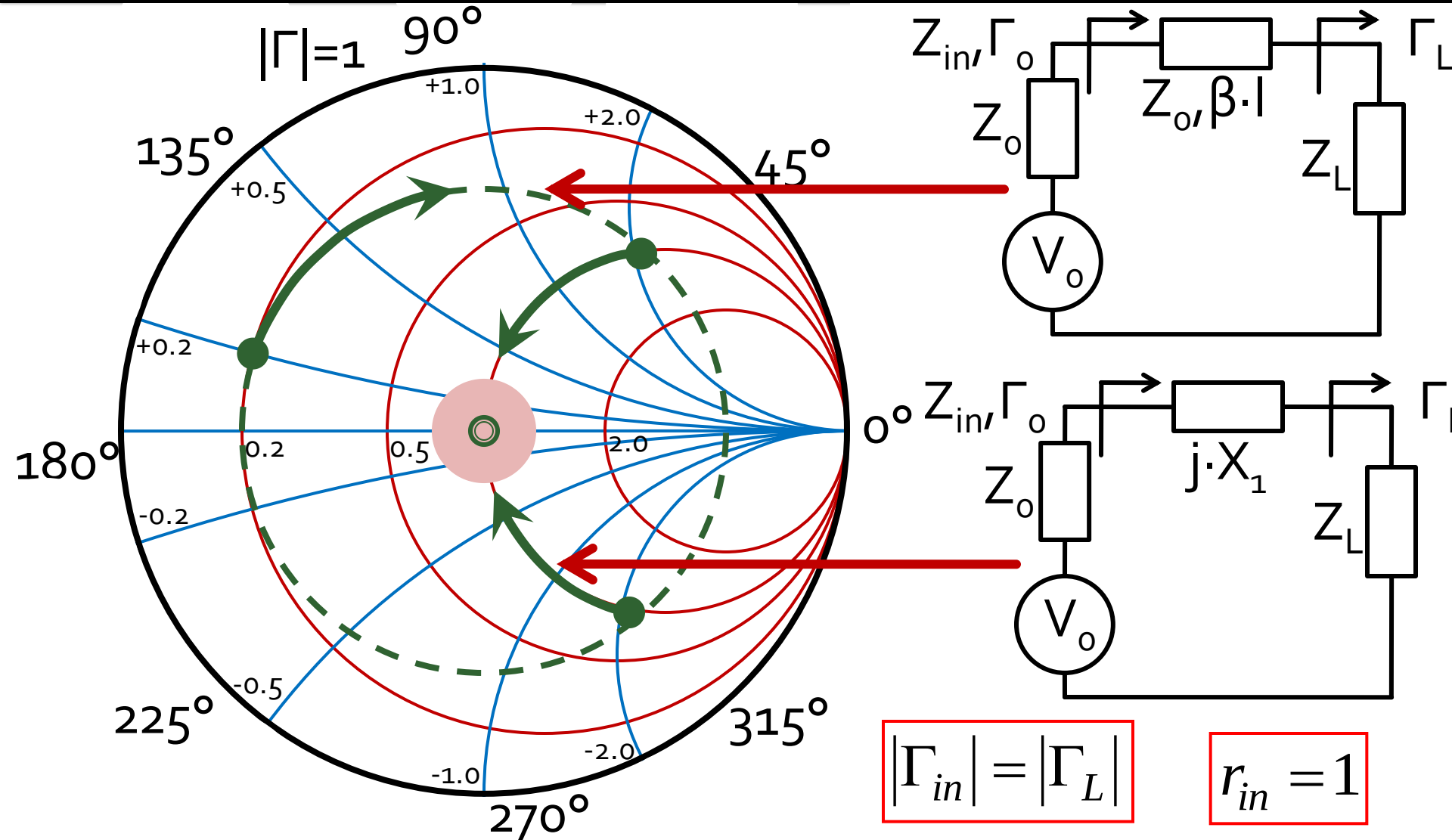

Analytical solution, reflection coefficient

- load: $100\ \Omega$ series with $6.37\ \text{nH}$ at $2\ \text{GHz}$

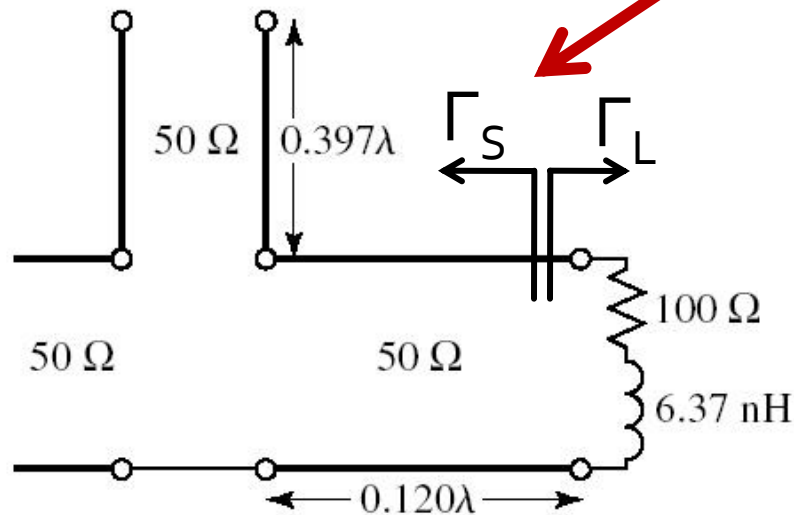

Solution 1

$$Z_L = R_L + \frac{1}{j \cdot \omega \cdot C_L} = 100\Omega + j \cdot 80.05\Omega$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 0.481 + j \cdot 0.277$$

$$z_L = \frac{Z_L}{Z_0} = 2 + j \cdot 1.6$$

- matching requires obtaining conjugate value for Γ

$$\Gamma_S = \Gamma_L^* = 0.481 - j \cdot 0.277$$

$$\Gamma_S = 0.555 \angle -29.92^\circ$$

$$|\Gamma_S| = 0.555; \quad \varphi = -29.92^\circ$$

Analytical solution, Γ

$$\cos(\varphi + 2\theta) = |\Gamma_s|$$

$$\theta_{ss} = \beta \cdot l = \cot^{-1} \frac{\mp 2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}}$$

$$\Gamma_s = 0.555 \angle -29.92^\circ$$

$$|\Gamma_s| = 0.555; \quad \varphi = -29.92^\circ \quad \cos(\varphi + 2\theta) = 0.555 \Rightarrow (\varphi + 2\theta) = \pm 56.28^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

- **"+" solution**

$$(-29.92^\circ + 2\theta) = +56.28^\circ$$

$$\theta = 43.1^\circ$$

$$\text{Im } z_s = \frac{+2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} = +1.335$$

$$\theta_{ss} = -\cot^{-1}(\text{Im } z_s) = -36.8^\circ (+180^\circ) \rightarrow \theta_{ss} = 143.2^\circ$$

- **"-" solution**

$$(-29.92^\circ + 2\theta) = -56.28^\circ$$

$$\theta = -13.2^\circ (+180^\circ) \rightarrow \theta = 166.8^\circ$$

$$\text{Im } z_s = \frac{-2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} = -1.335$$

$$\theta_{ss} = -\cot^{-1}(\text{Im } z_s) = 36.8^\circ$$

Analytical solution, Γ

$$(\varphi + 2\theta) = \begin{cases} +56.28^\circ \\ -56.28^\circ \end{cases} \quad \theta = \begin{cases} 43.1^\circ \\ 166.8^\circ \end{cases} \quad \text{Im}[z_s(\theta)] = \begin{cases} +1.335 \\ -1.335 \end{cases} \quad \theta_{ss} = \begin{cases} -36.8^\circ + 180^\circ = 143.2^\circ \\ +36.8^\circ \end{cases}$$

- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

$$l_1 = \frac{43.1^\circ}{360^\circ} \cdot \lambda = 0.120 \cdot \lambda$$

$$l_2 = \frac{143.2^\circ}{360^\circ} \cdot \lambda = 0.398 \cdot \lambda$$


$$l_1 = \frac{166.8^\circ}{360^\circ} \cdot \lambda = 0.463 \cdot \lambda$$

$$l_2 = \frac{36.8^\circ}{360^\circ} \cdot \lambda = 0.102 \cdot \lambda$$





Double stub tuning

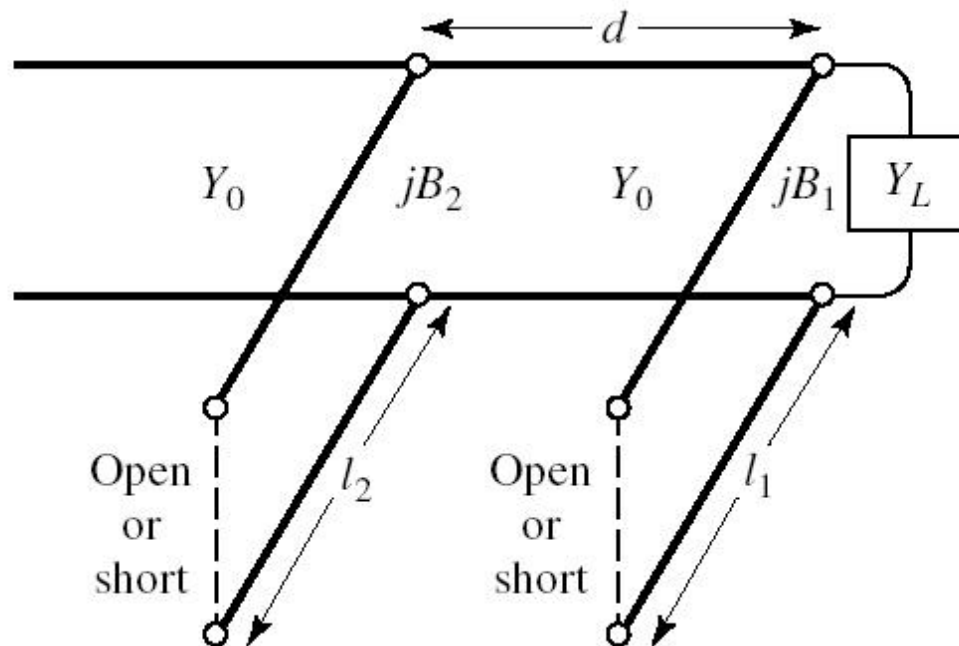- Double stub tuning
- uses two tuning stubs in fixed positions (a fixed length of line between the stubs)




Double stub tuning

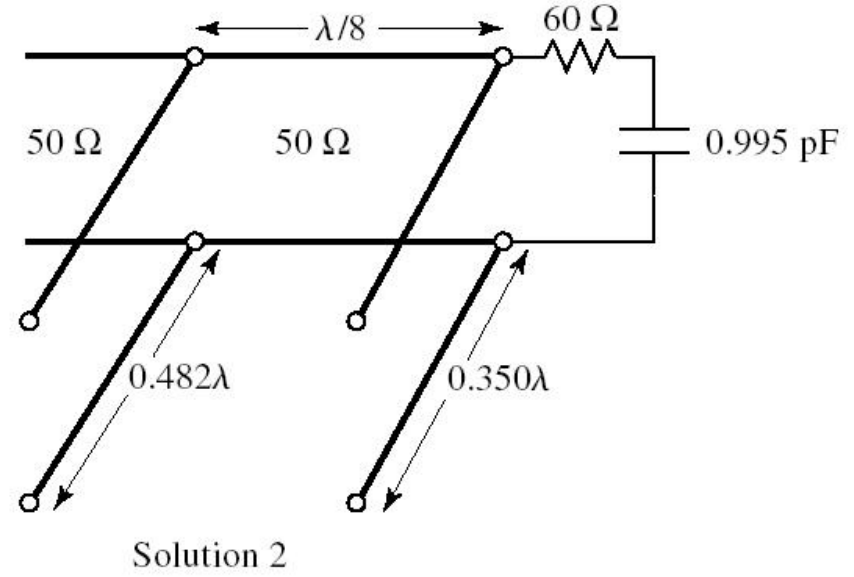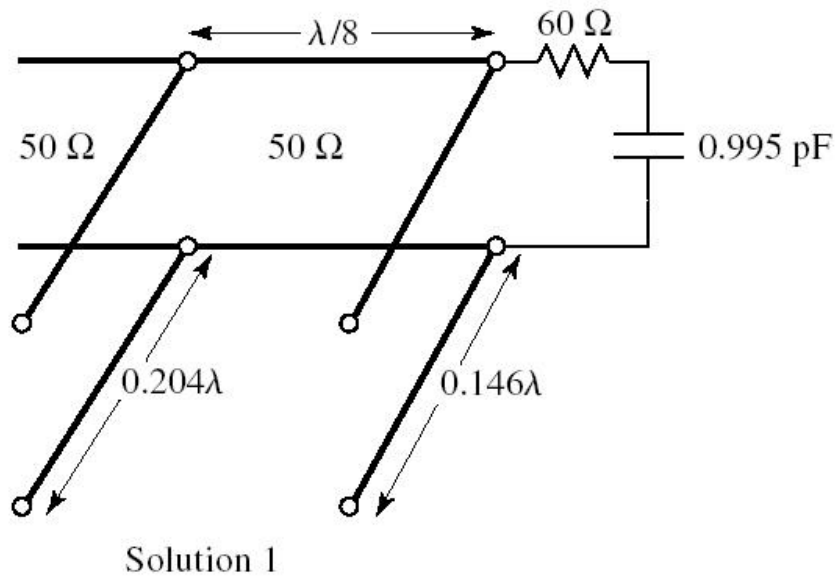- same load: $60\ \Omega$ series with $0.995\ \text{pF}$ at 2GHz
- two possible solutions




Double stub tuning

- two possible solutions





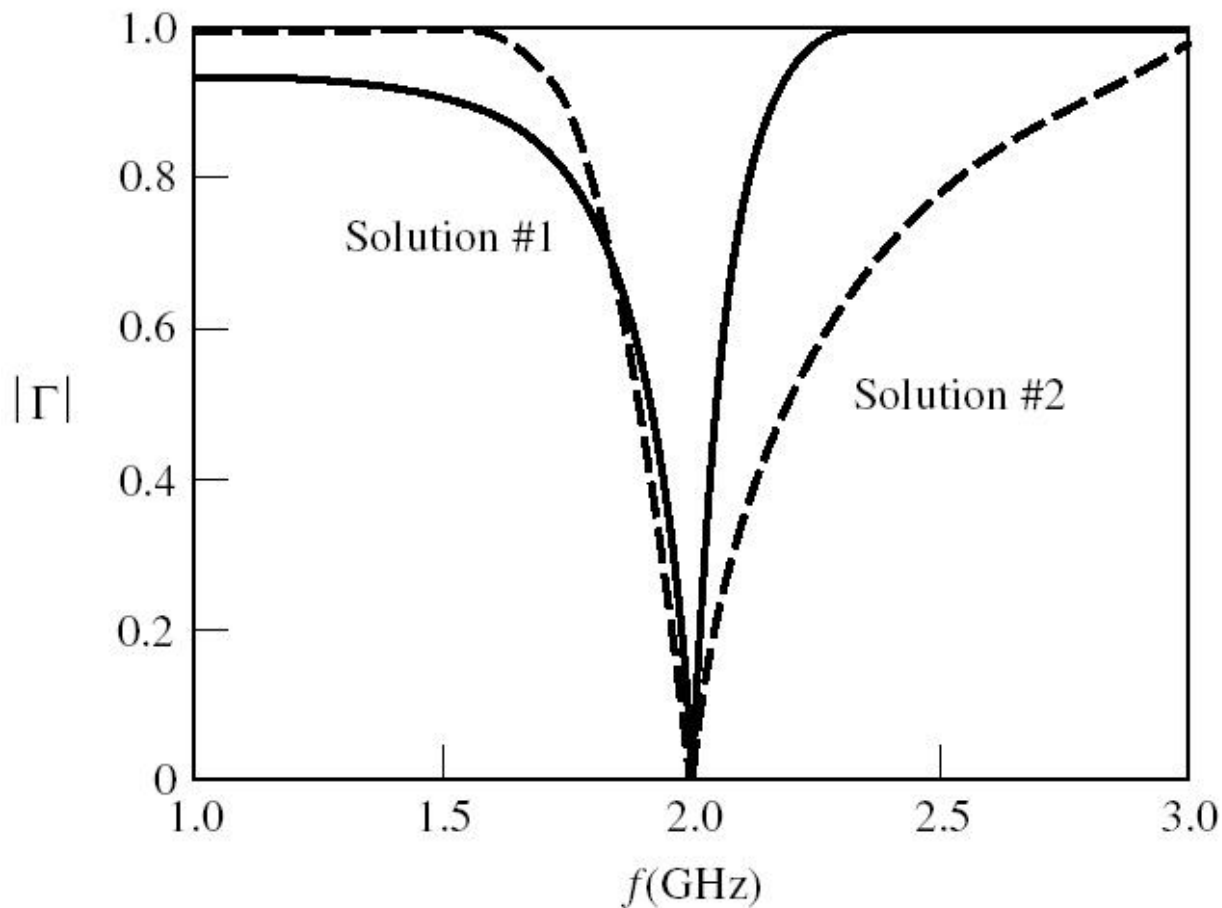


Double stub tuning

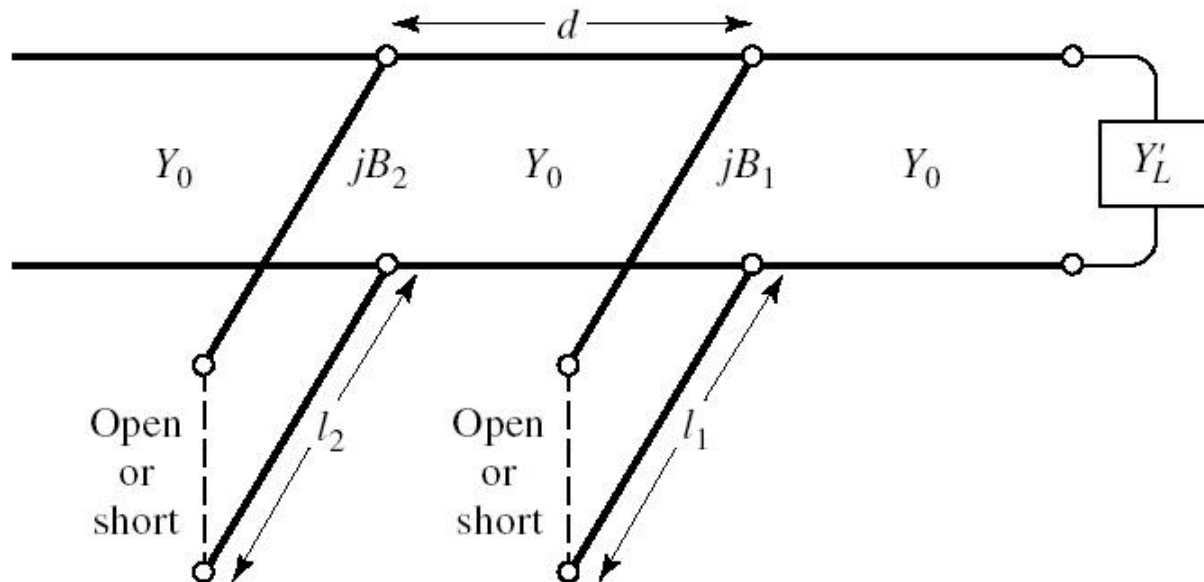- Typically $d = \lambda/8$ or $d = 3\lambda/8$
- **Not possible** for every load
 - unless we can add a specific length of line between the load and the first stub




Impedance Matching with Stubs

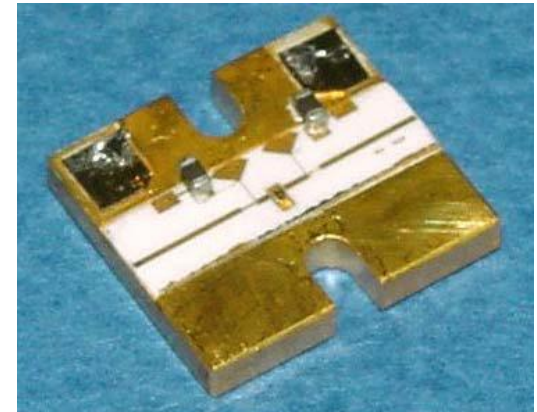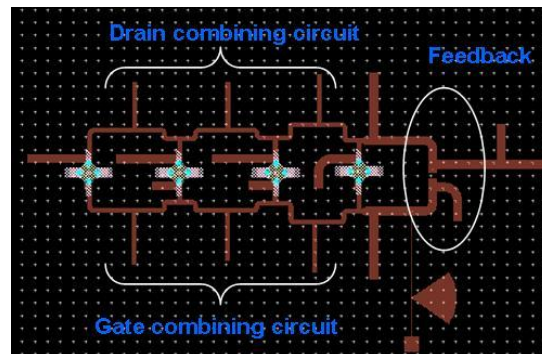
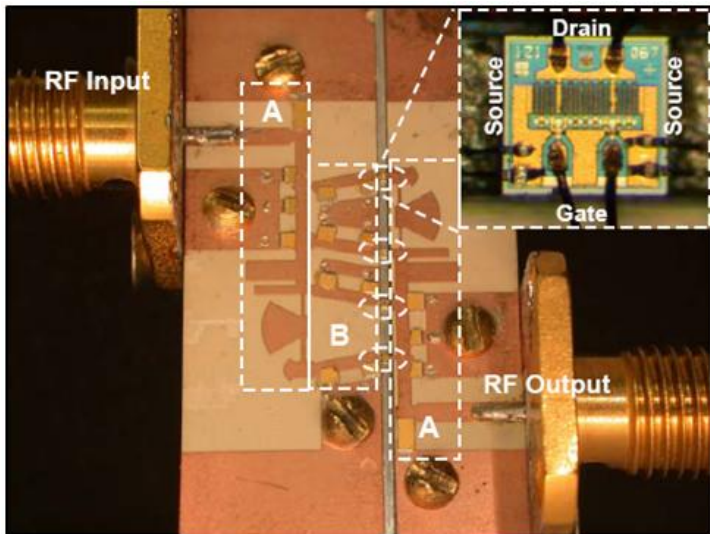
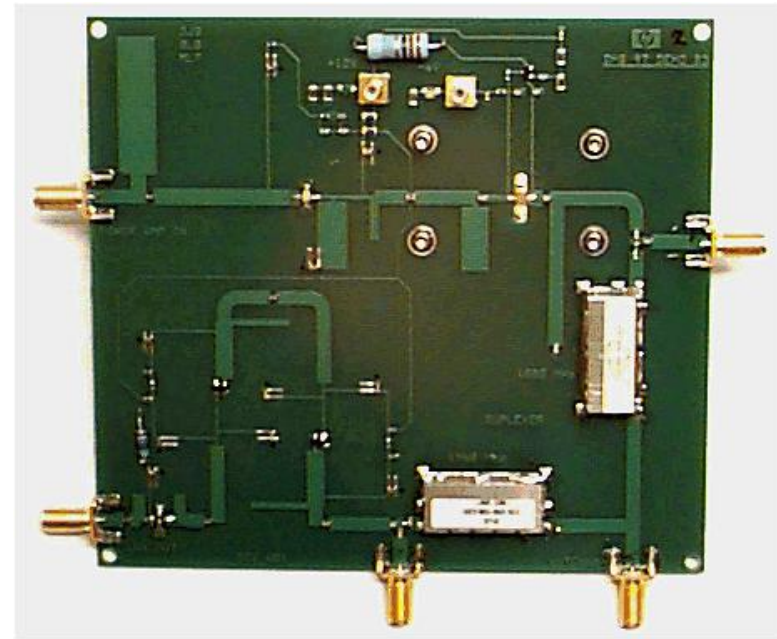
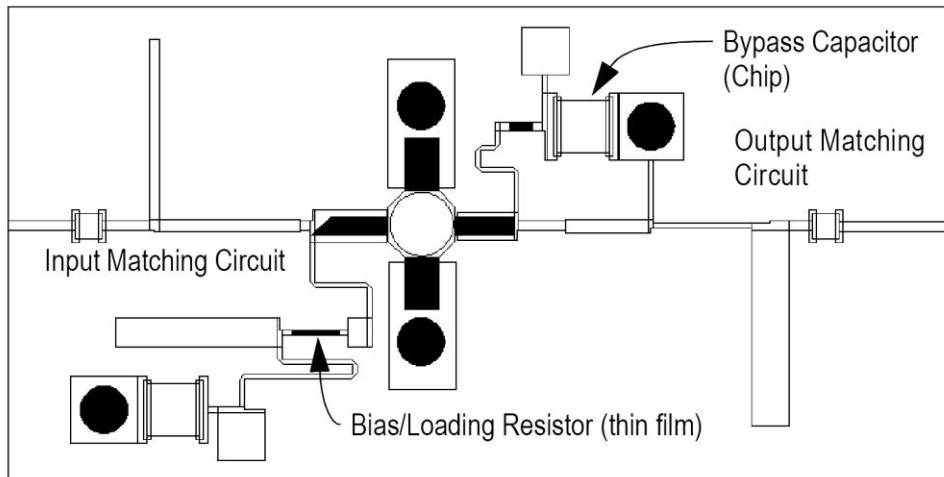


Microwave Amplifiers


Microwave Amplifiers

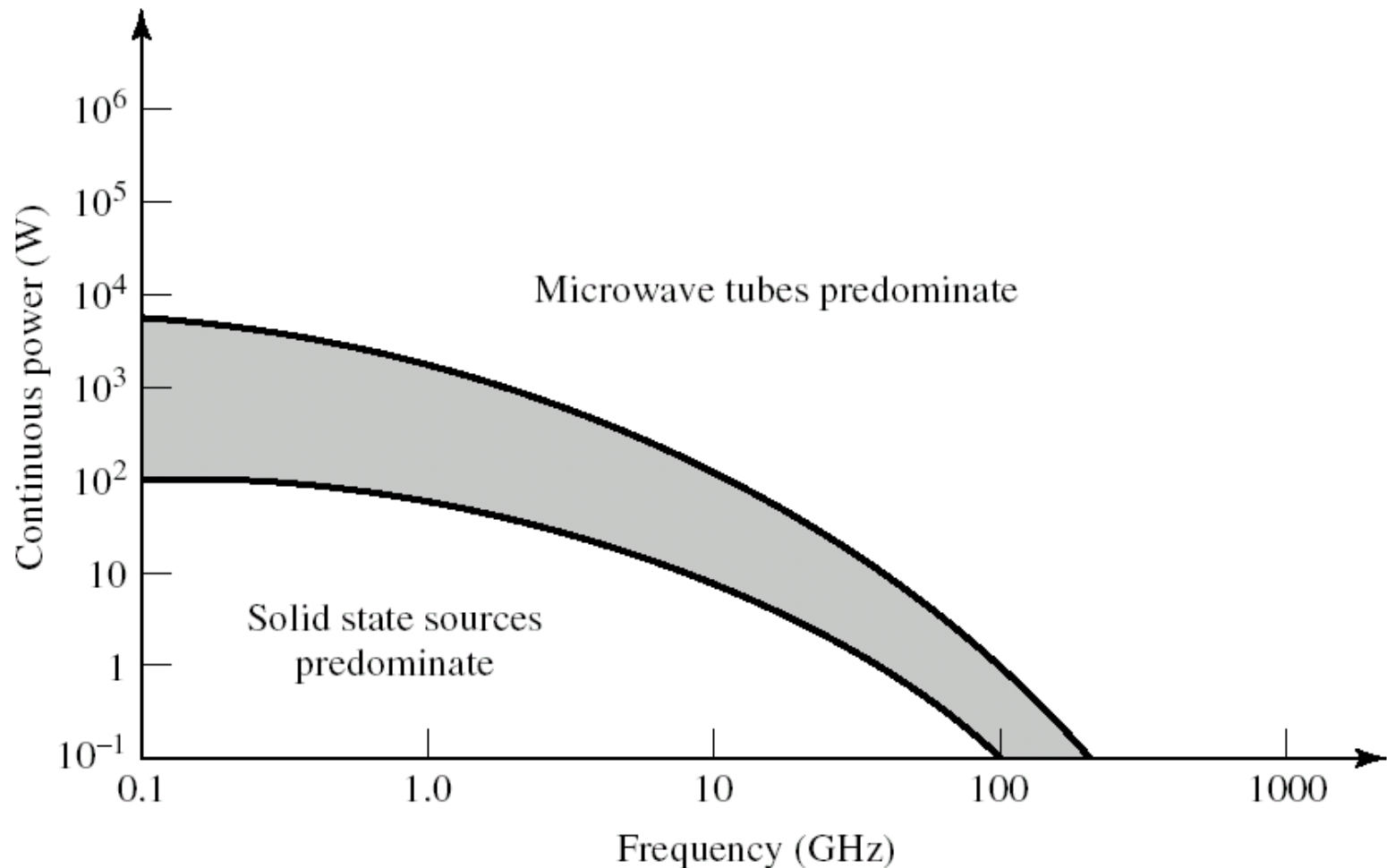

Microwave Integrated Circuits

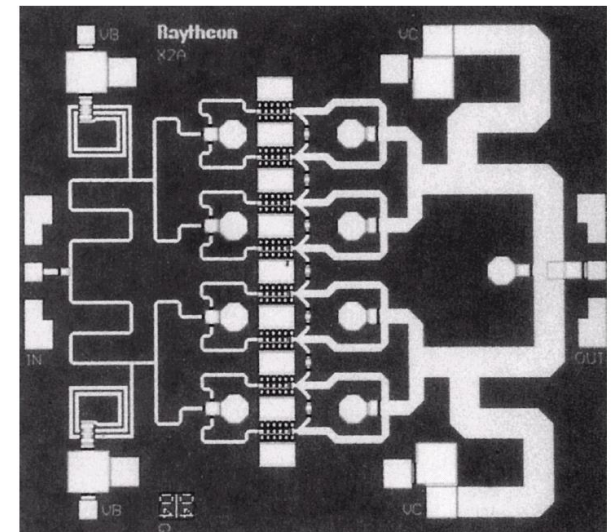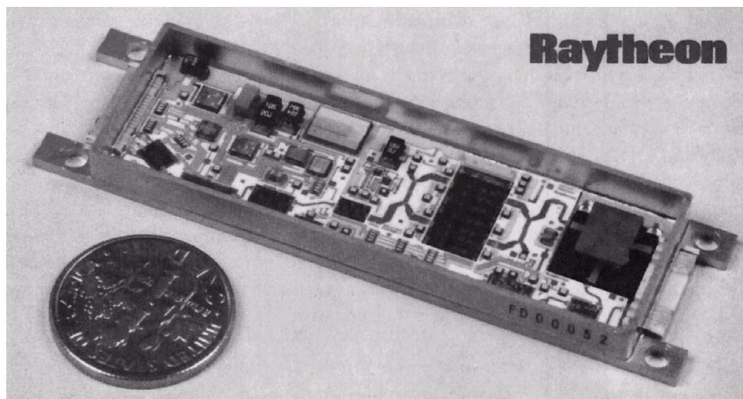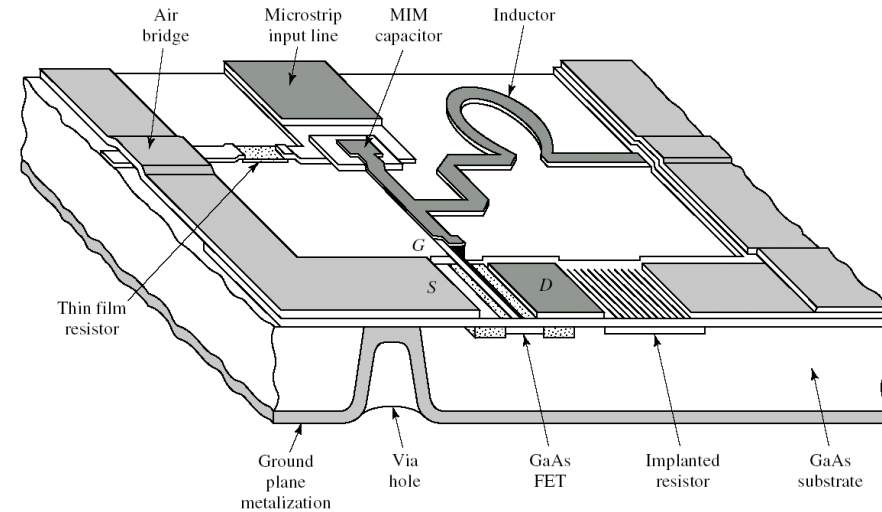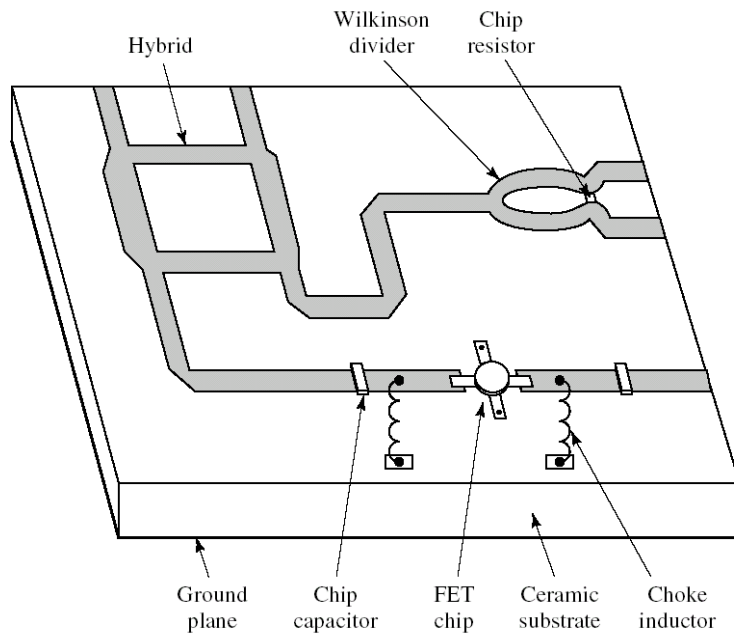

Amplifier as two-port

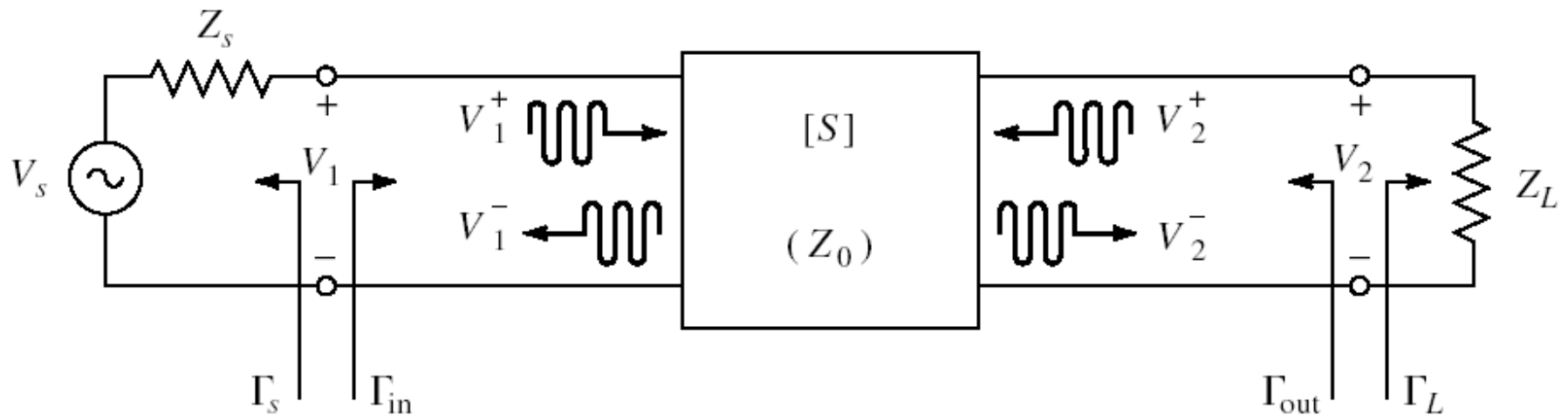

- Characterized with S parameters
- normalized at Z_0 (implicit 50Ω)
- Datasheets: S parameters for specific bias conditions

Datasheets

CEL

NE46100 / NE46134


NPN MEDIUM POWER MICROWAVE TRANSISTOR

FEATURES

- HIGH DYNAMIC RANGE
- LOW IM DISTORTION: -40 dBc
- HIGH OUTPUT POWER : 27.5 dBm at TYP
- LOW NOISE: 1.5 dB TYP at 500 MHz
- LOW COST

DESCRIPTION

The NE461 series of NPN silicon epitaxial bipolar transistors is designed for medium power applications requiring high dynamic range. This device exhibits an outstanding combination of high gain and low intermodulation distortion, as well as low noise figure. The NE461 series offers excellent performance and reliability at low cost through titanium, platinum, gold metallization system and direct nitride passivation of the surface of the chip. Devices are available in a low cost surface mount package (SOT-89) as well as in chip form.

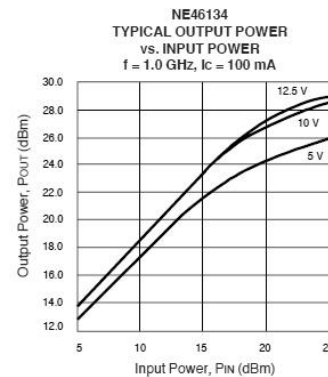

ELECTRICAL CHARACTERISTICS (TA = 25°C)

PART NUMBER EIAJ ¹ REGISTERED NUMBER PACKAGE OUTLINE			NE46100 00 (CHIP)			NE46134 2SC4536 34		
SYMBOLS	PARAMETERS AND CONDITIONS	UNITS	MIN	TYP	MAX	MIN	TYP	MAX
f _T	Gain Bandwidth Product at V _{CE} = 10 V, I _C = 100 mA	GHz		5.5			5.5	
NF _{MIN}	Minimum Noise Figure ³ at V _{CE} = 10 V, I _C = 50 mA, 500 MHz V _{CE} = 10 V, I _C = 50 mA, 1 GHz	dB		1.5 2.0			1.5 2.0	
G _L	Linear Gain, V _{CE} = 12.5 V, I _C = 100 mA, 2.0 GHz V _{CE} = 12.5 V, I _C = 100 mA, 1.0 GHz	dB		9.0			8.0	
IS _{21E} ²	Insertion Power Gain at 10 V, 50 mA, f = 1.0 GHz	dB		10.0		5.5	7.0	
h _{FE}	DC Current Gain ² at V _{CE} = 10 V, I _C = 50 mA		40		200	40		200
I _{CBO}	Collector Cutoff Current at V _{CB} = 20 V, I _E = 0 mA	μA			5.0			5.0
I _{EB0}	Emitter Cutoff Current at V _{EB} = 2 V, I _C = 0 mA	μA			5.0			5.0
P _{1dB}	Output Power at 1 dB Compression, V _{CE} = 12.5 V, I _C = 100 mA, 2.0 GHz V _{CE} = 12.5 V, I _C = 100 mA, 1.0 GHz	dBm	27.0				27.5	
IM ₃	Intermodulation Distortion, 10 V, 100 mA, F ₁ = 1.0 GHz, F ₂ = 0.99 GHz	dBm						

Datasheets

NE46100

VCE = 5 V, Ic = 50 mA

FREQUENCY (MHz)	S11		S21		S12		S22		K	MAG ² (dB)
	MAG	ANG	MAG	ANG	MAG	ANG	MAG	ANG		
100	0.778	-137	26.776	114	0.028	30	0.555	-102	0.16	29.8
200	0.815	-159	14.407	100	0.035	29	0.434	-135	0.36	26.2
500	0.826	-177	5.855	84	0.040	38	0.400	-162	0.75	21.7
800	0.827	176	3.682	76	0.052	43	0.402	-169	0.91	18.5
1000	0.826	173	2.963	71	0.058	47	0.405	-172	1.02	16.3
1200	0.825	170	2.441	66	0.064	47	0.412	-174	1.08	14.0
1400	0.820	167	2.111	61	0.069	47	0.413	-176	1.17	12.4
1600	0.828	165	1.863	57	0.078	54	0.426	-177	1.15	11.4
1800	0.827	162	1.671	53	0.087	50	0.432	-178	1.14	10.6
2000	0.828	159	1.484	49	0.093	50	0.431	-180	1.17	9.5
2500	0.822	153	1.218	39	0.11	48	0.462	177	1.18	7.8
3000	0.818	148	1.010	30	0.135	46	0.490	174	1.16	6.3
3500	0.824	142	0.876	21	0.147	44	0.507	170	1.16	5.3
4000	0.812	137	0.762	13	0.168	38	0.535	167	1.14	4.3



VCE = 5 V, Ic = 100 mA

100	0.778	-144	27.669	111	0.027	35	0.523	-114	0.27	30.2
200	0.820	-164	14.559	97	0.029	29	0.445	-144	0.42	27.0
500	0.832	-179	5.885	84	0.035	38	0.435	-166	0.81	22.2
800	0.833	175	3.691	76	0.048	45	0.435	-173	0.95	18.8
1000	0.831	172	2.980	71	0.056	51	0.437	-176	1.05	16.0
1200	0.836	169	2.464	67	0.061	52	0.432	-178	1.11	14.0
1400	0.829	166	2.121	61	0.072	53	0.447	-180	1.12	12.6
1600	0.831	164	1.867	58	0.080	54	0.445	179	1.14	11.4

Datasheets

NE46100, NE46134

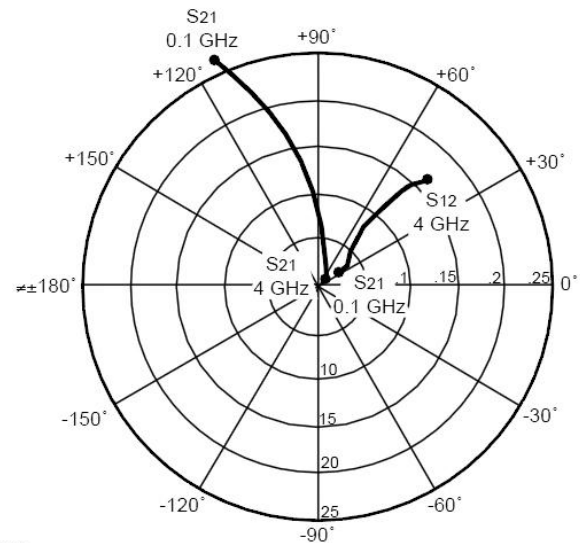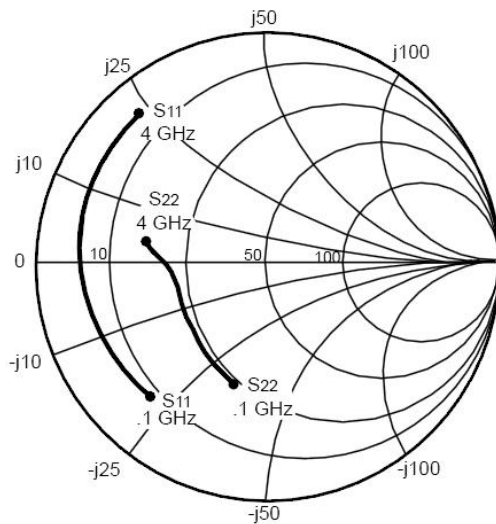TYPICAL COMMON EMITTER SCATTERING PARAMETERS¹ ($T_A = 25^\circ\text{C}$)






Coordinates in Ohms
Frequency in GHz
 $V_{CE} = 5\text{ V}$, $I_c = 50\text{ mA}$

S2P - Touchstone


- Touchstone file format (*.s2p)

```
! SIEMENS Small Signal Semiconductors
! VDS = 3.5 V   ID = 15 mA
# GHz S MA R 50
! f      S11      S21      S12      S22
! GHz   MAG ANG   MAG ANG   MAG ANG   MAG ANG
1.000 0.9800 -18.0 2.230 157.0 0.0240 74.0 0.6900 -15.0
2.000 0.9500 -39.0 2.220 136.0 0.0450 57.0 0.6600 -30.0
3.000 0.8900 -64.0 2.210 110.0 0.0680 40.0 0.6100 -45.0
4.000 0.8200 -89.0 2.230 86.0 0.0850 23.0 0.5600 -62.0
5.000 0.7400 -115.0 2.190 61.0 0.0990 7.0 0.4900 -80.0
6.000 0.6500 -142.0 2.110 36.0 0.1070 -10.0 0.4100 -98.0
!
! f      Fmin  Gammaopt rn/50
! GHz    dB   MAG ANG  -
2.000    1.00 0.72 27 0.84
4.000    1.40 0.64 61 0.58
```

S parameters for transistors

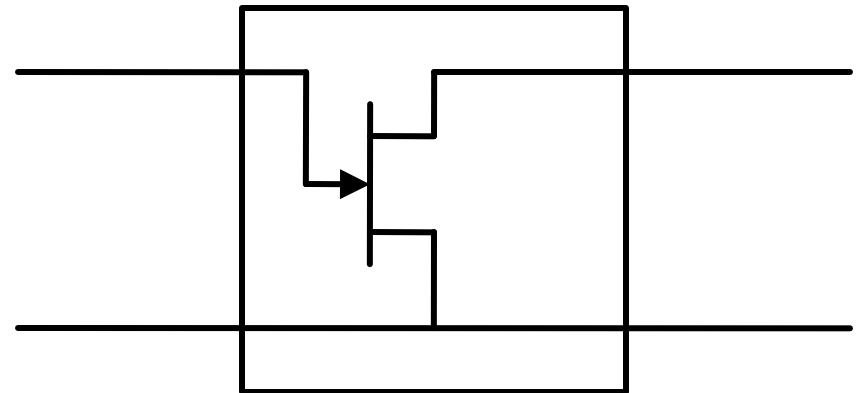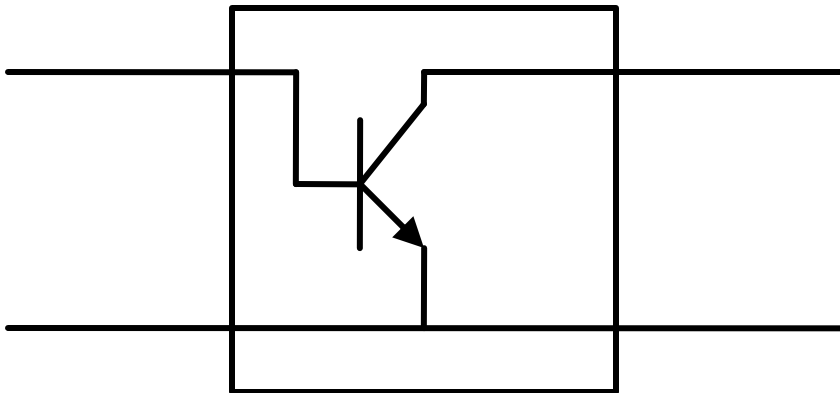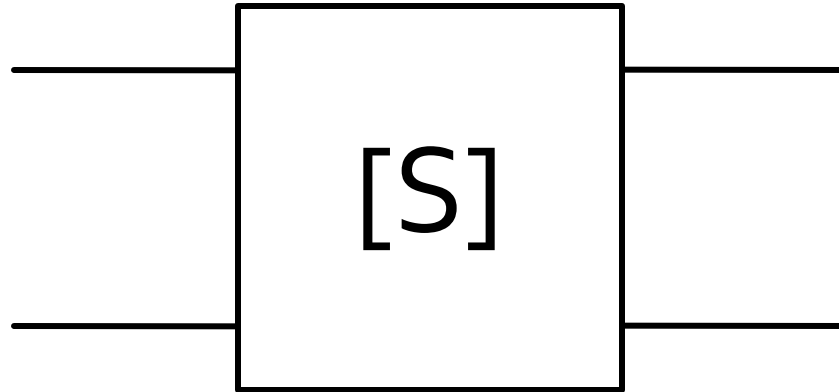

Amplifier as two-port

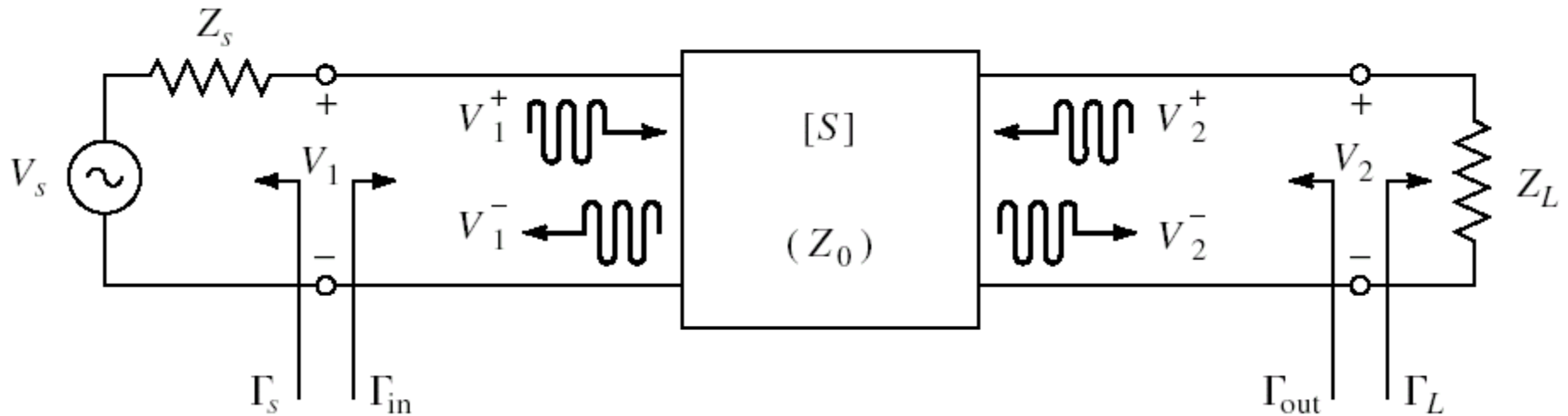


$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \Gamma_s = \frac{Z_s - Z_0}{Z_s + Z_0} \quad \begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$\Gamma_L = \frac{V_2^+}{V_2^-} \quad V_1^- = S_{11} \cdot V_1^+ + S_{12} \cdot V_2^+ = S_{11} \cdot V_1^+ + S_{12} \cdot \Gamma_L \cdot V_2^-$$

$$V_2^- = S_{21} \cdot V_1^+ + S_{22} \cdot V_2^+ = S_{21} \cdot V_1^+ + S_{22} \cdot \Gamma_L \cdot V_2^-$$

Amplifier as two-port

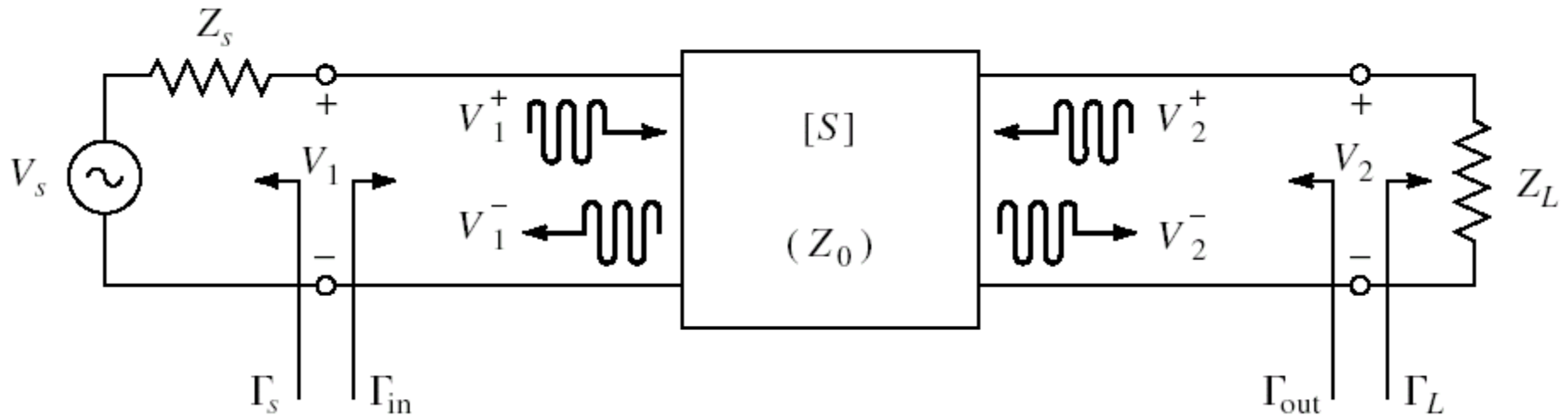

$$V_1^- = S_{11} \cdot V_1^+ + S_{12} \cdot V_2^+ = S_{11} \cdot V_1^+ + S_{12} \cdot \Gamma_L \cdot V_2^-$$


$$V_2^- = S_{21} \cdot V_1^+ + S_{22} \cdot V_2^+ = S_{21} \cdot V_1^+ + S_{22} \cdot \Gamma_L \cdot V_2^-$$

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

■ similarly

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

Amplifier as two-port

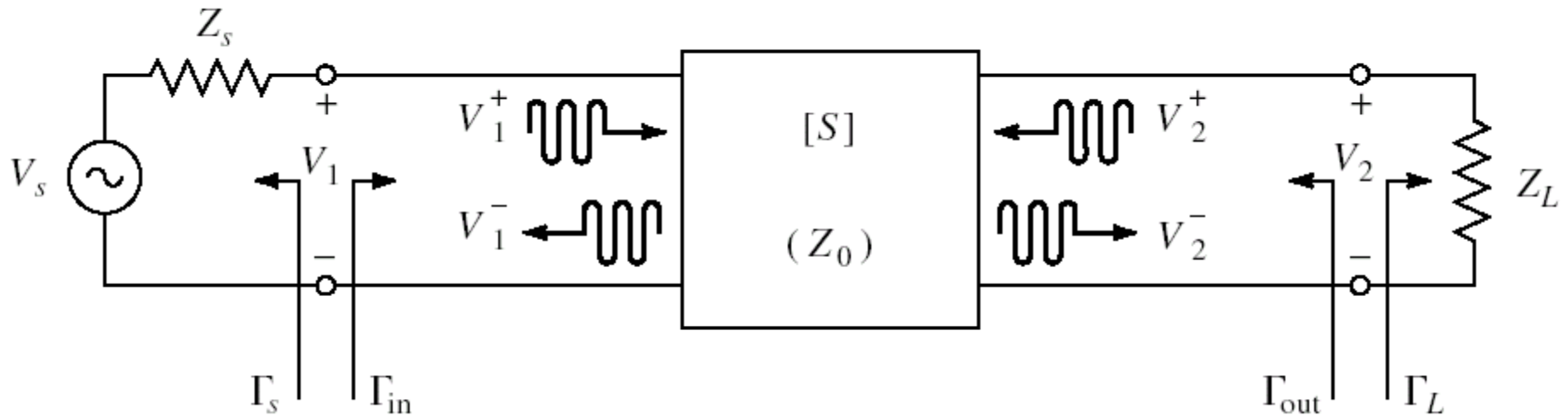

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_s}{1 - S_{11} \cdot \Gamma_s}$$

Signal power

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$V_1 = \frac{V_S \cdot Z_{in}}{Z_S + Z_{in}} = V_1^+ + V_1^- = V_1^+ \cdot (1 + \Gamma_{in})$$

$$V_1^+ = \frac{V_S}{2} \frac{(1 - \Gamma_S)}{(1 - \Gamma_S \cdot \Gamma_{in})}$$

■ C3 $P_{in} = \frac{1}{2 \cdot Z_0} \cdot |V_1^+|^2 \cdot (1 - |\Gamma_{in}|^2)$

$$P_L = \frac{1}{2 \cdot Z_0} \cdot |V_2^-|^2 \cdot (1 - |\Gamma_L|^2)$$

$$P_{in} = \frac{|V_S|^2}{8 \cdot Z_0} \cdot \frac{|1 - \Gamma_S|^2}{|1 - \Gamma_S \cdot \Gamma_{in}|^2} (1 - |\Gamma_{in}|^2)$$

$$V_2^- = S_{21} \cdot V_1^+ + S_{22} \cdot V_2^+ = S_{21} \cdot V_1^+ + S_{22} \cdot \Gamma_L \cdot V_2^-$$

$$V_2^- = \frac{S_{21} \cdot V_1^+}{1 - S_{22} \cdot \Gamma_L}$$

$$P_L = \frac{|V_1^+|^2}{2 \cdot Z_0} \cdot \frac{|S_{21}|^2}{|1 - S_{22} \cdot \Gamma_L|^2} (1 - |\Gamma_L|^2)$$

$$P_L = \frac{|V_S|^2}{8 \cdot Z_0} \cdot \frac{|S_{21}|^2 \cdot (1 - |\Gamma_L|^2)}{|1 - S_{22} \cdot \Gamma_L|^2} \cdot \frac{|1 - \Gamma_S|^2}{|1 - \Gamma_S \cdot \Gamma_{in}|^2}$$

Signal power

- Signal power

$$P_{in} = \frac{|V_S|^2}{8 \cdot Z_0} \cdot \frac{|1 - \Gamma_S|^2}{|1 - \Gamma_S \cdot \Gamma_{in}|^2} (1 - |\Gamma_{in}|^2)$$

$$P_L = \frac{|V_S|^2}{8 \cdot Z_0} \cdot \frac{|S_{21}|^2 \cdot (1 - |\Gamma_L|^2)}{|1 - S_{22} \cdot \Gamma_L|^2} \cdot \frac{|1 - \Gamma_S|^2}{|1 - \Gamma_S \cdot \Gamma_{in}|^2}$$

- Power available from the source

$$P_{avS} = P_{in}|_{\Gamma_{in}=\Gamma_S^*} = \frac{|V_S|^2}{8 \cdot Z_0} \cdot \frac{|1 - \Gamma_S|^2}{(1 - |\Gamma_S|^2)}$$

- Power available on the load (from the network)

$$P_{avL} = P_L|_{\Gamma_L=\Gamma_{out}^*} = \frac{|V_S|^2}{8 \cdot Z_0} \cdot \frac{|S_{21}|^2 \cdot |1 - \Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2 \cdot (1 - |\Gamma_{out}|^2)}$$

Two-Port Power Gains

- Power Gain

$$G = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) \cdot |1 - S_{22} \cdot \Gamma_L|^2}$$

$$P_{in} = P_{in}(\Gamma_S, \Gamma_{in}(\Gamma_L), S)$$

$$P_L = P_L(\Gamma_S, \Gamma_{in}(\Gamma_L), S)$$

- The **actual** power gain **introduced** by the amplifier is less important because a higher gain may be accompanied by a **decrease** in input power (power actually drained from the source)
- We prefer to characterize the amplifier effect looking to the **power actually delivered to the load** in relation to the power **available from the source** (which is a constant)

Two-Port Power Gains

- **Available** power gain

$$G_A = \frac{P_{avL}}{P_{avS}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2)}{|1 - S_{22} \cdot \Gamma_L|^2 \cdot (1 - |\Gamma_{out}|^2)}$$

- **Transducer** power gain

$$G_T = \frac{P_L}{P_{avS}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2}$$

$$\Gamma_{in} = \Gamma_{in}(\Gamma_L)$$

- **Unilateral transducer** power gain


$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$S_{12} \cong 0$$

$$\Gamma_{in} = S_{11}$$

Input and output can be treated independently

Amplifier as two-port

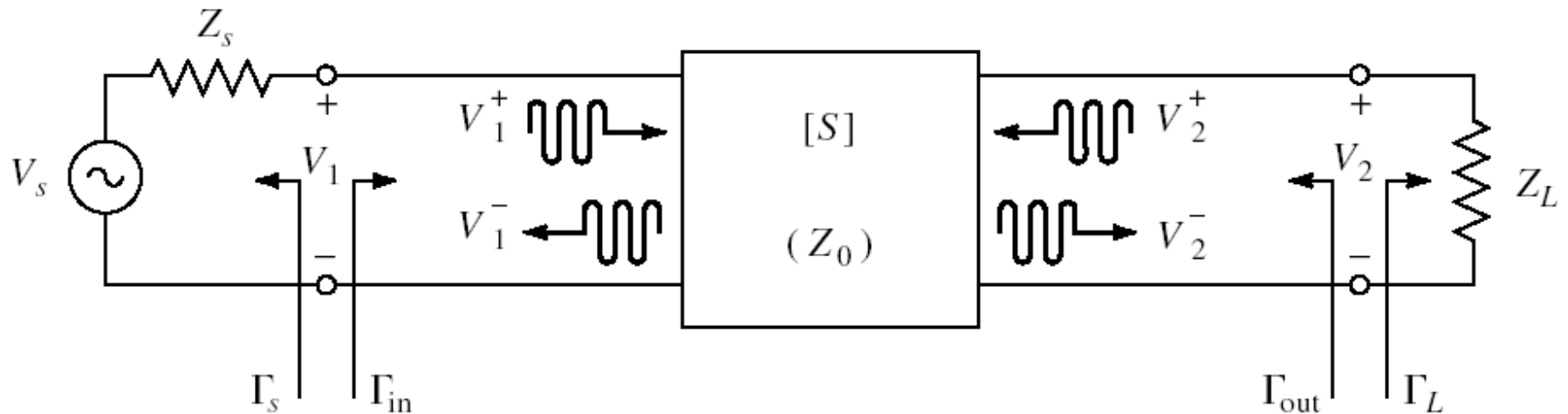


- For an amplifier two-port we are interested in:
 - stability
 - power gain
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)

Preview (pentru laborator 3-4)

Amplificatoare de microunde

Proiectare pentru castig impus

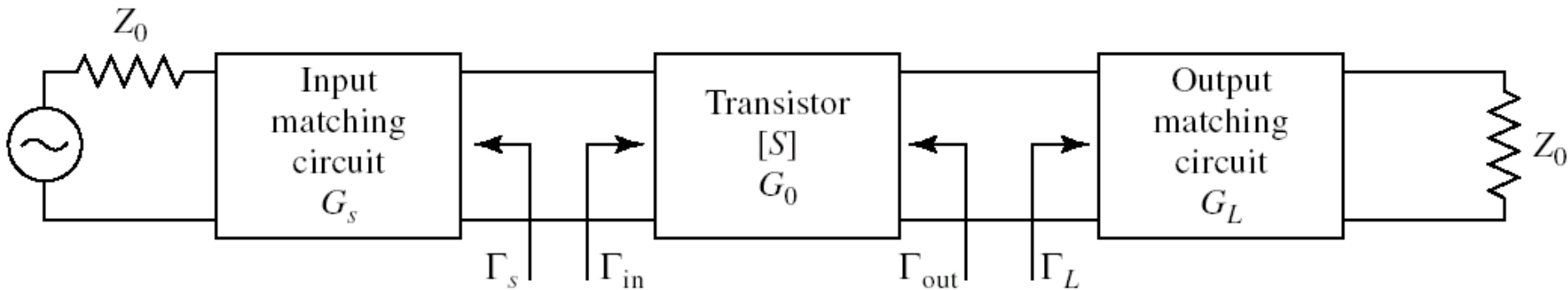

- Daca ipoteza tranzistorului unilateral este justificata:


$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_s|^2}{|1 - S_{11} \cdot \Gamma_s|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$G_s = \frac{1 - |\Gamma_s|^2}{|1 - S_{11} \cdot \Gamma_s|^2}$$

$$G_0 = |S_{21}|^2$$

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

Proiectare pentru castig impus

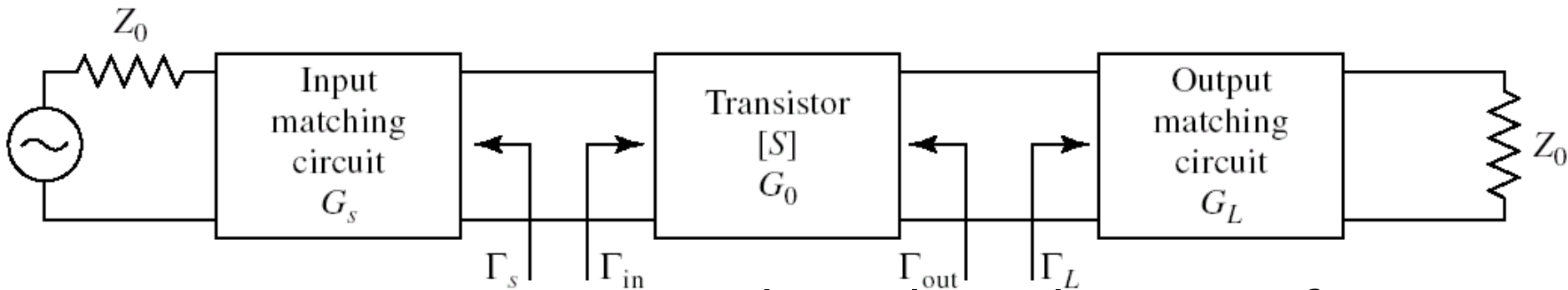


- Dacă ipoteza tranzistorului unilateral este justificată:
 - castigul adăugat prin adaptare mai bună la intrare **nu** depinde de adaptarea la ieșire
 - castigul adăugat prin adaptare mai bună la ieșire **nu** depinde de adaptarea la intrare
- Adaptările la intrare/ieșire pot fi tratate independente
 - Se pot impune cerințe diferite intrare/ieșire
 - se ține cont de compunerea câștigurilor generate

$$G_T = G_S \cdot G_0 \cdot G_L$$


$$G_T[dB] = G_S[dB] + G_0[dB] + G_L[dB]$$

$G_S(\Gamma_S)$

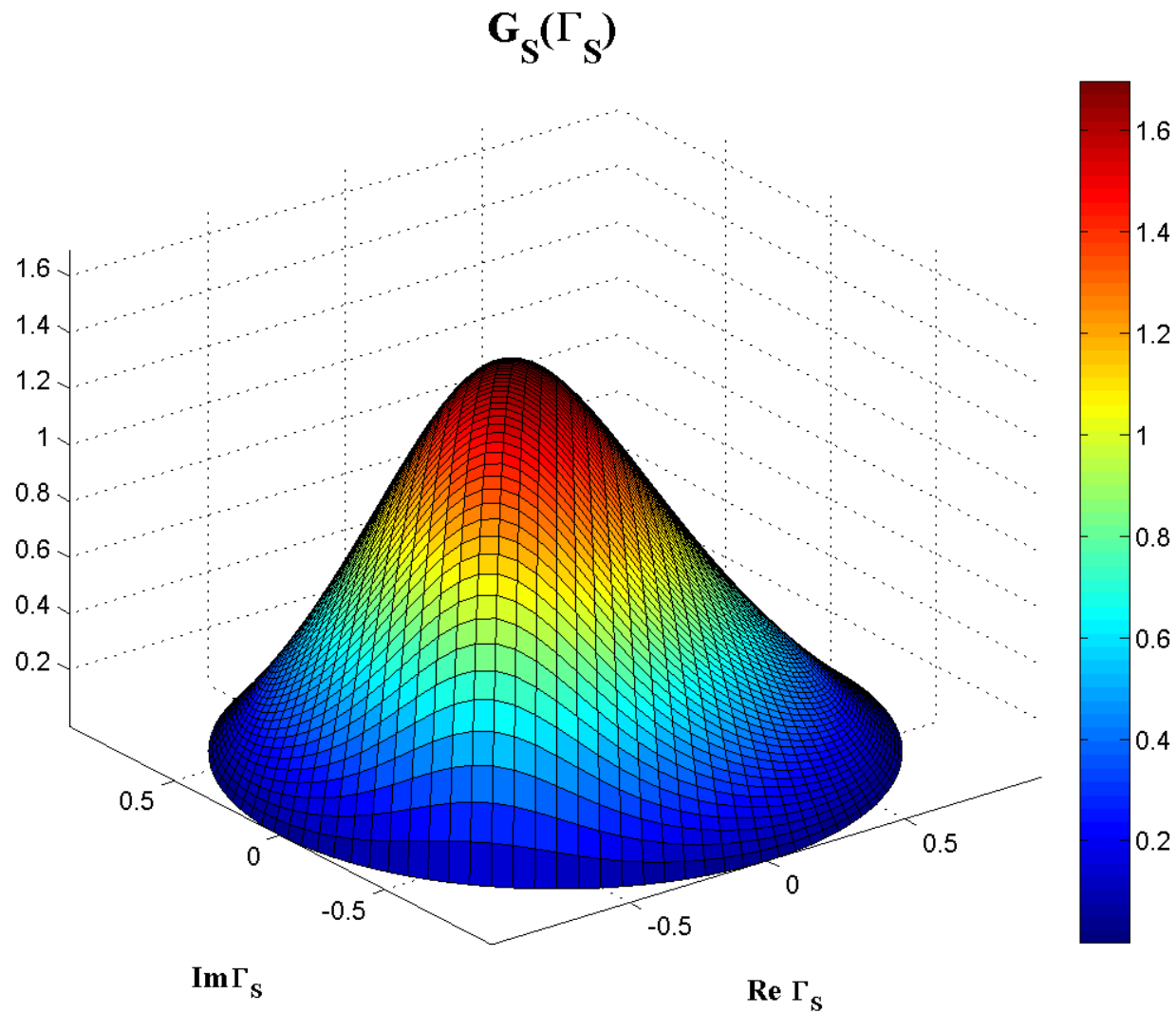


$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2}$$

$G_S(\Gamma_S)$, nivel constant

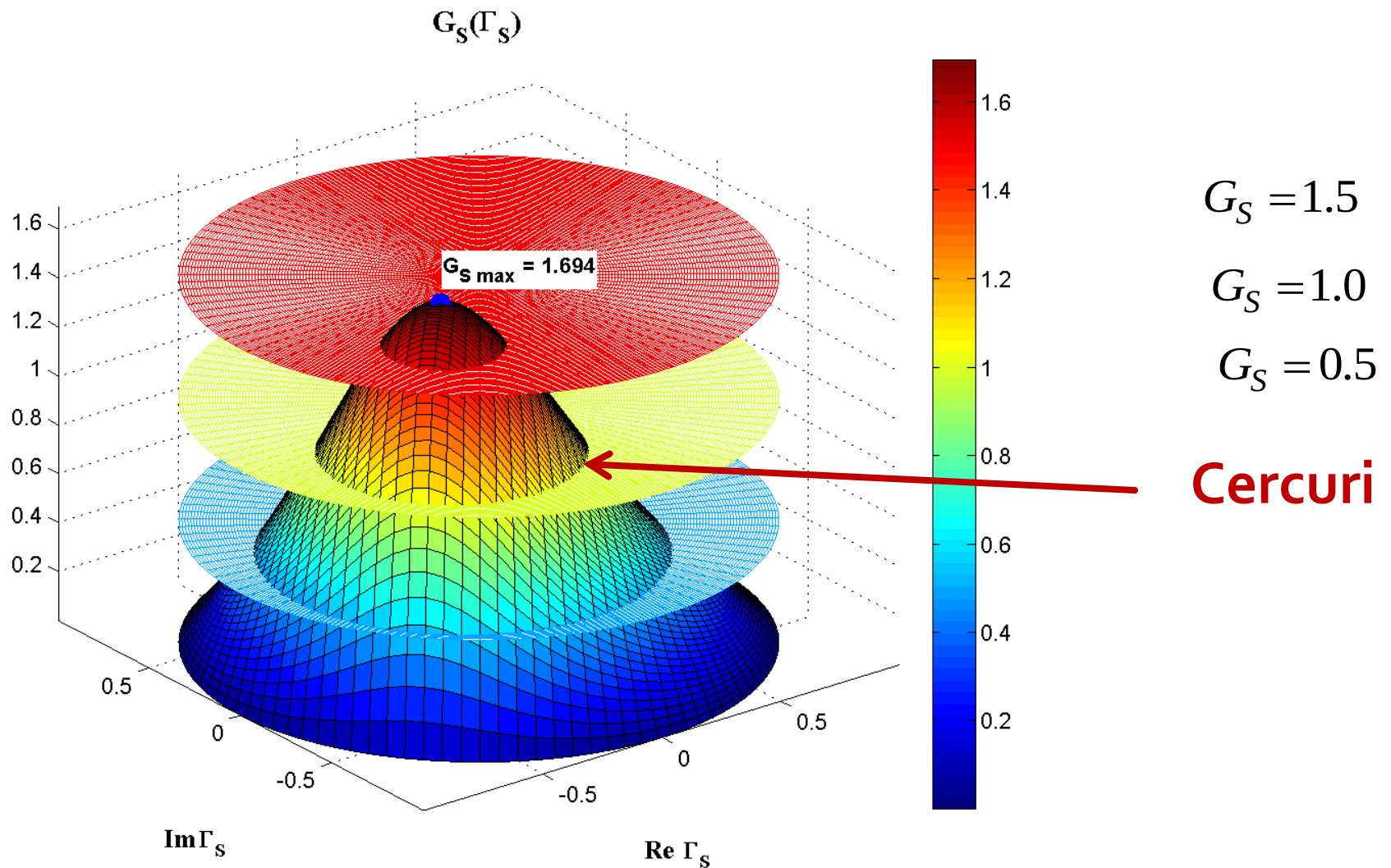


$G_S(\Gamma_S)$, diagrama de nível

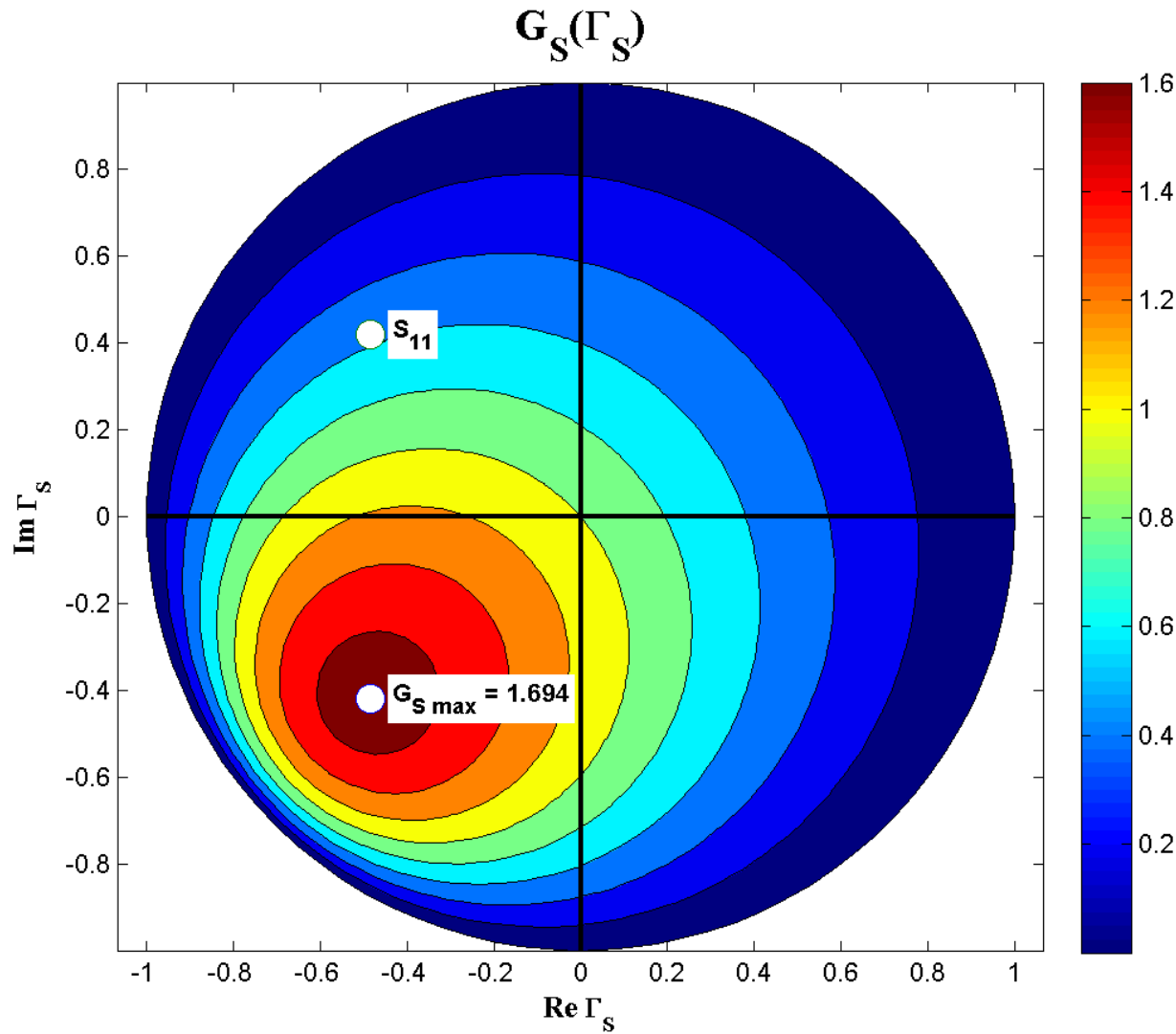

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2}$$

$$G_{S \max} = G_S|_{\Gamma_S = s_{11}^*}$$

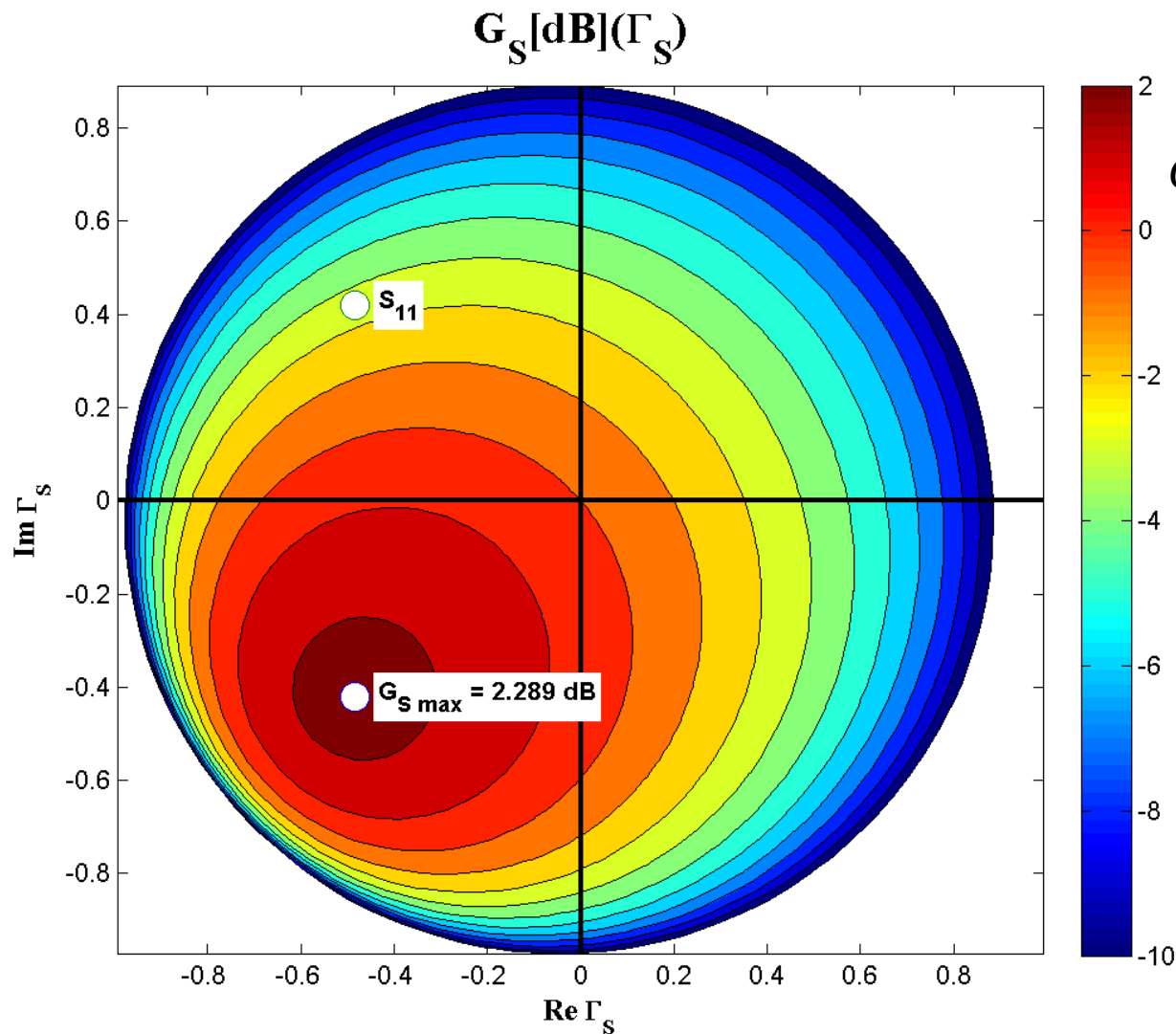$G_S[\text{dB}](\Gamma_S)$, diagrama de nivel



$$G_S[\text{dB}] = 10 \cdot \log \left(\frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \right)$$


$$G_{S \text{ max}} = G_S|_{\Gamma_S = S_{11}^*}$$

Cercuri de castig constant la intrare

$$\left| \Gamma_S - \frac{g_S \cdot S_{11}^*}{1 - (1 - g_S) \cdot |S_{11}|^2} \right| = \frac{\sqrt{1 - g_S} \cdot (1 - |S_{11}|^2)}{1 - (1 - g_S) \cdot |S_{11}|^2} \quad |\Gamma_S - C_S| = R_S$$
$$C_S = \frac{g_S \cdot S_{11}^*}{1 - (1 - g_S) \cdot |S_{11}|^2} \quad R_S = \frac{\sqrt{1 - g_S} \cdot (1 - |S_{11}|^2)}{1 - (1 - g_S) \cdot |S_{11}|^2}$$


- Ecuatia unui cerc in planul complex in care reprezinta Γ_S
- **Interpretare:** Orice punct Γ_S care este reprezentat in planul complex se gaseste **pe** cercul desenat pentru $g_{\text{cerc}} = G_{\text{cerc}}/G_{\text{Smax}}$ va conduce la obtinerea castigului $G_S = G_{\text{cerc}}$
 - Orice punct **in exteriorul** acestui cerc va genera un castig $G_S < G_{\text{cerc}}$
 - Orice punct **in interiorul** acestui cerc va genera un castig $G_S > G_{\text{cerc}}$
- Discutie similara la iesire **CCIN, CCOUT**

CCGIN, CCCOUT

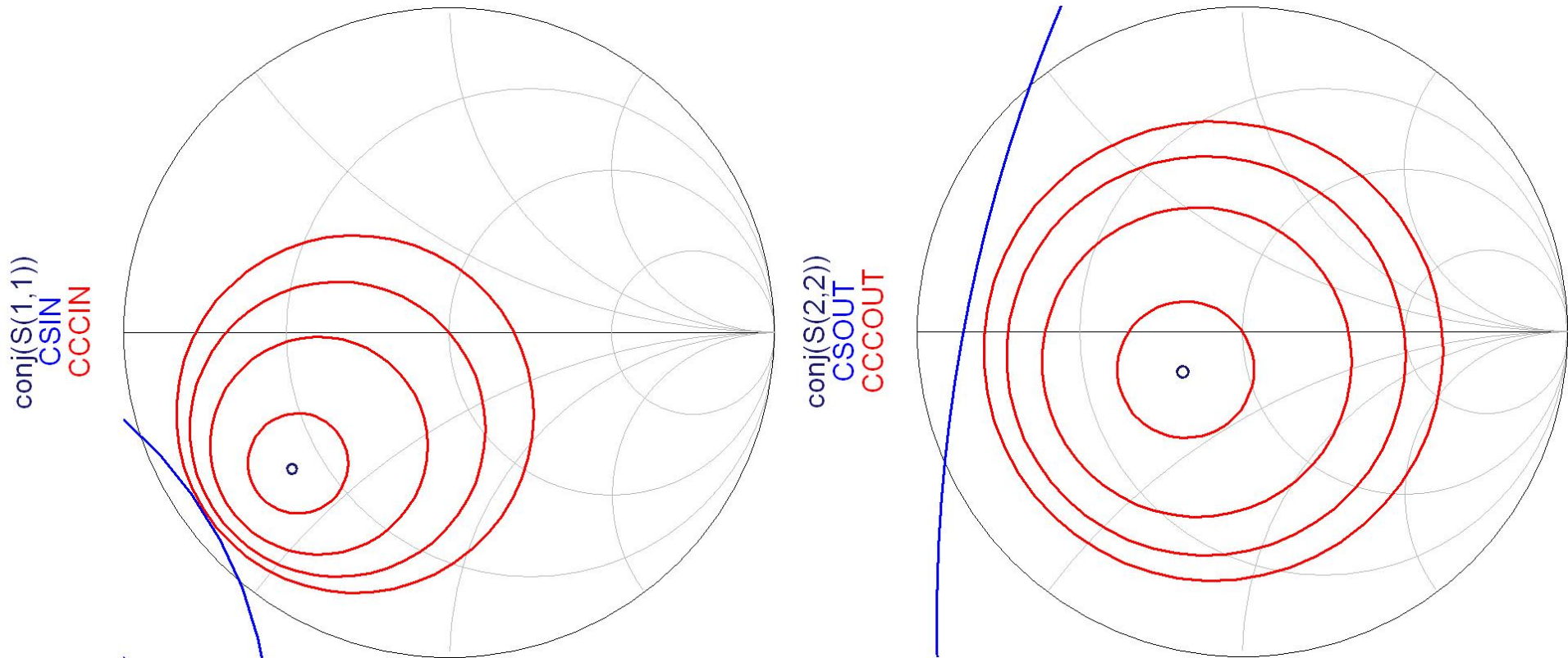

- Cercurile se reprezinta pentru valorile cerute in dB
- Este utila calcularea $G_{S_{\max}}$ si $G_{L_{\max}}$ anterior


Factor de zgomot

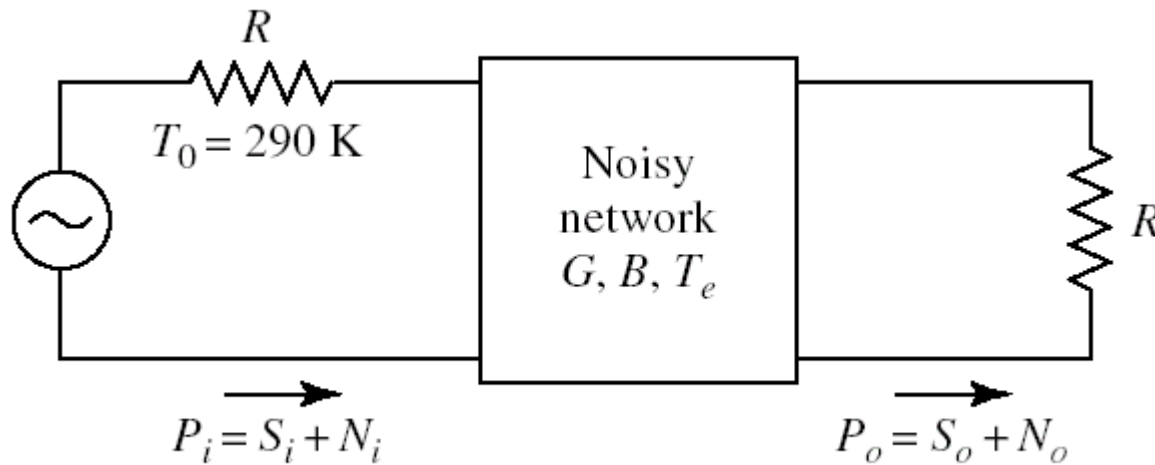


- Factorul de zgomot F caracterizeaza degradarea raportului semnal/zgomot între intrarea și ieșirea unei componente

$$F = \frac{S_i/N_i}{S_o/N_o}$$


$F(\Gamma_s)$

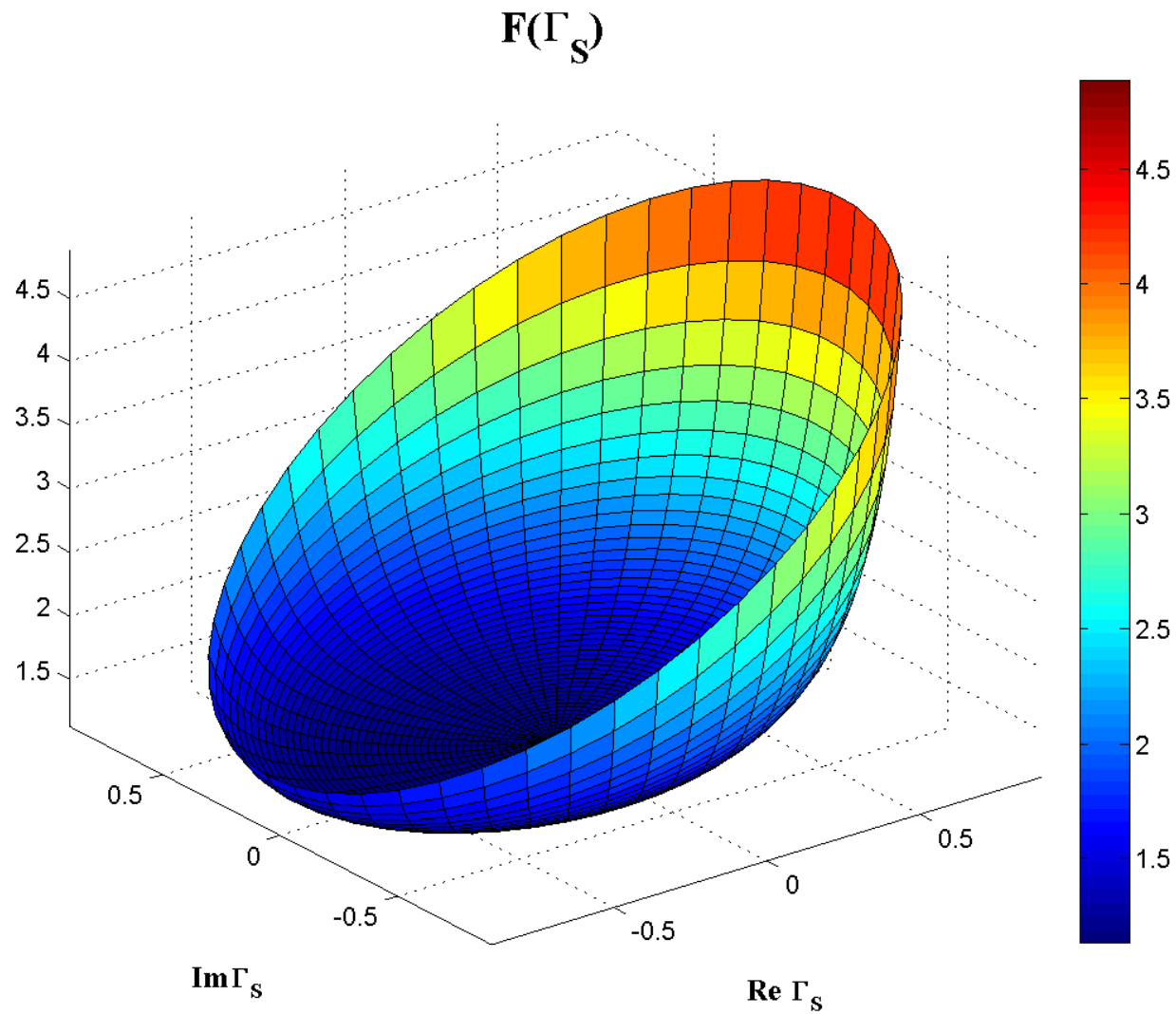


$F[\text{dB}](\Gamma_s)$

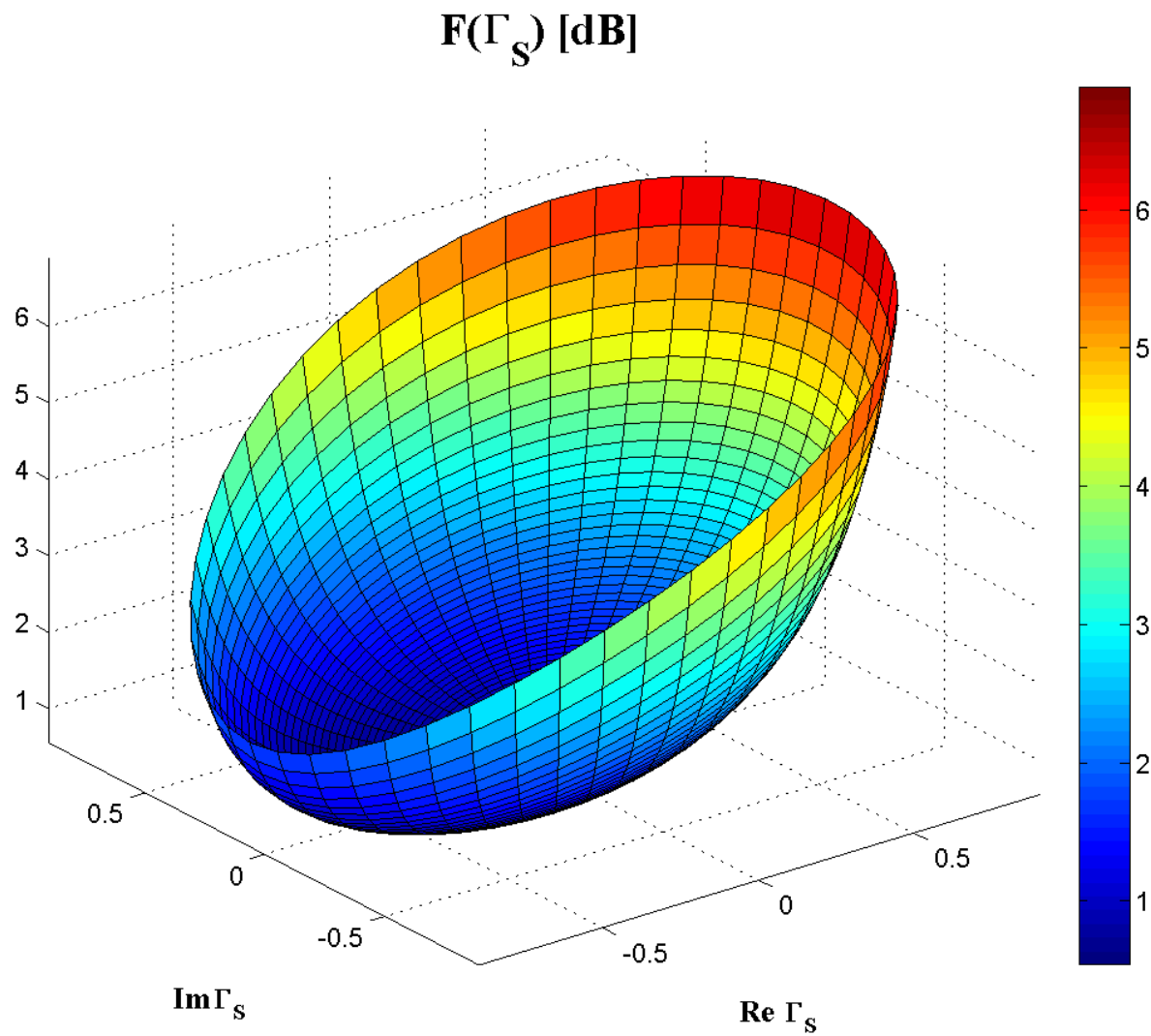

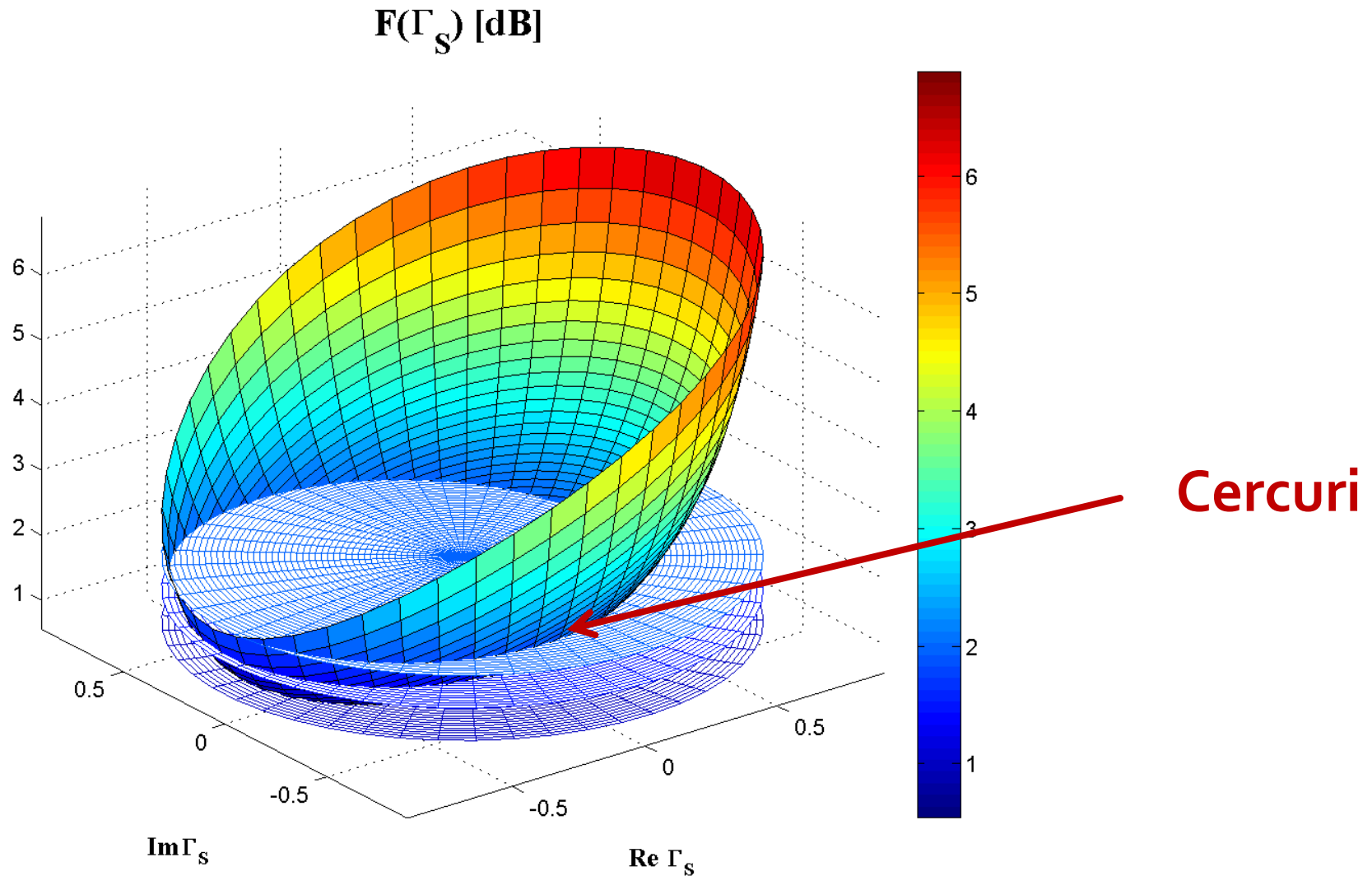$F[\text{dB}](\Gamma_s)$, diagrama de nivel




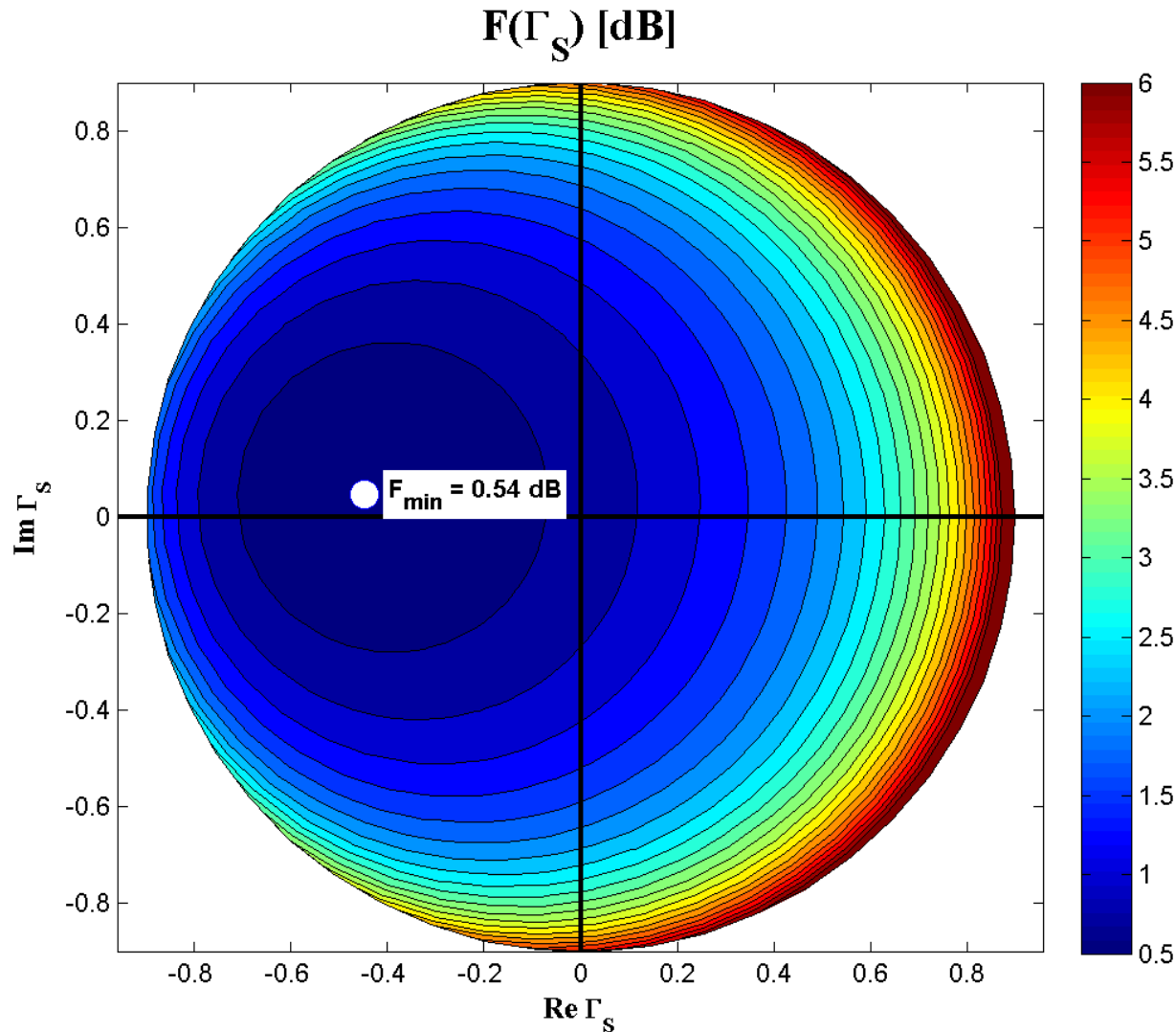$G_s[\text{dB}](\Gamma_s)$, diagrama de nivel



$$\Gamma_{\text{opt}} = 0.45 \angle 174^\circ$$


CZ – numai la intrare !

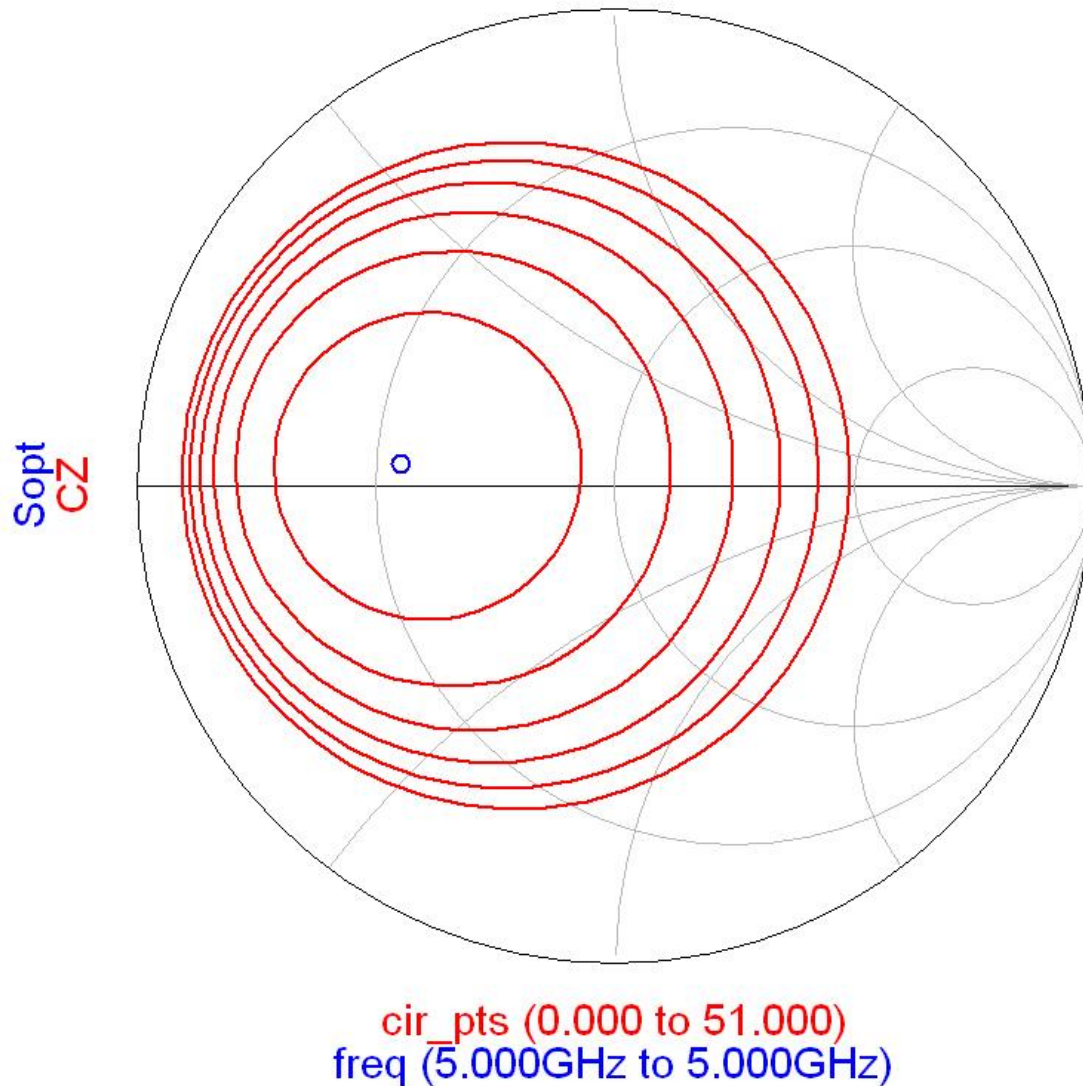

Exemplu, LNA @ 5 GHz


- Amplificator de zgomot redus
- La intrare e necesar un compromis intre
 - zgomot (cerc de zgomot constant **la intrare**)
 - castig (cerc de castig constant la intrare)
 - stabilitate (cerc de stabilitate la intrare)
- La iesire zgomotul **nu intervine** (nu exista influenta). Compromis intre:
 - castig (cerc de castig constant la iesire)
 - stabilitate (cerc de stabilitate la iesire)

Adaptare la intrare

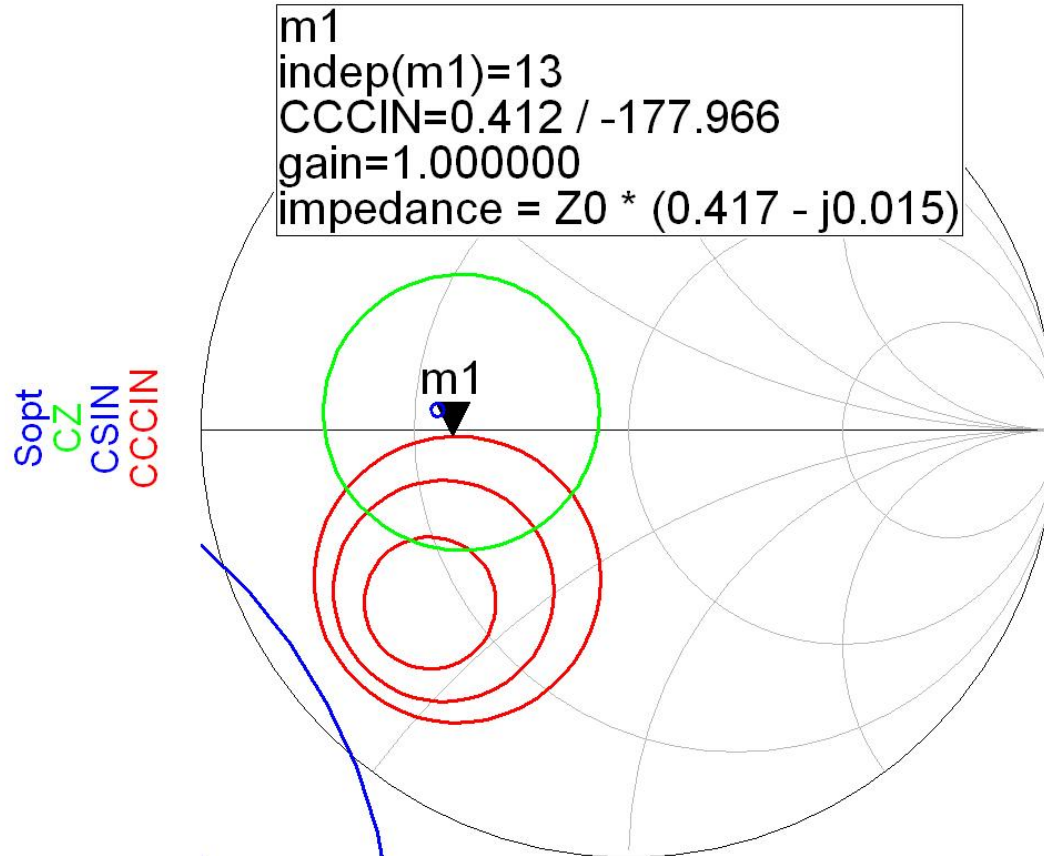

- Daca se sacrifica 1.2dB castig la intrare pentru conditii convenabile F,Q ($G_s = 1$ dB)
- Se prefera obtinerea unui zgomot mai mic


Adaptare la iesire

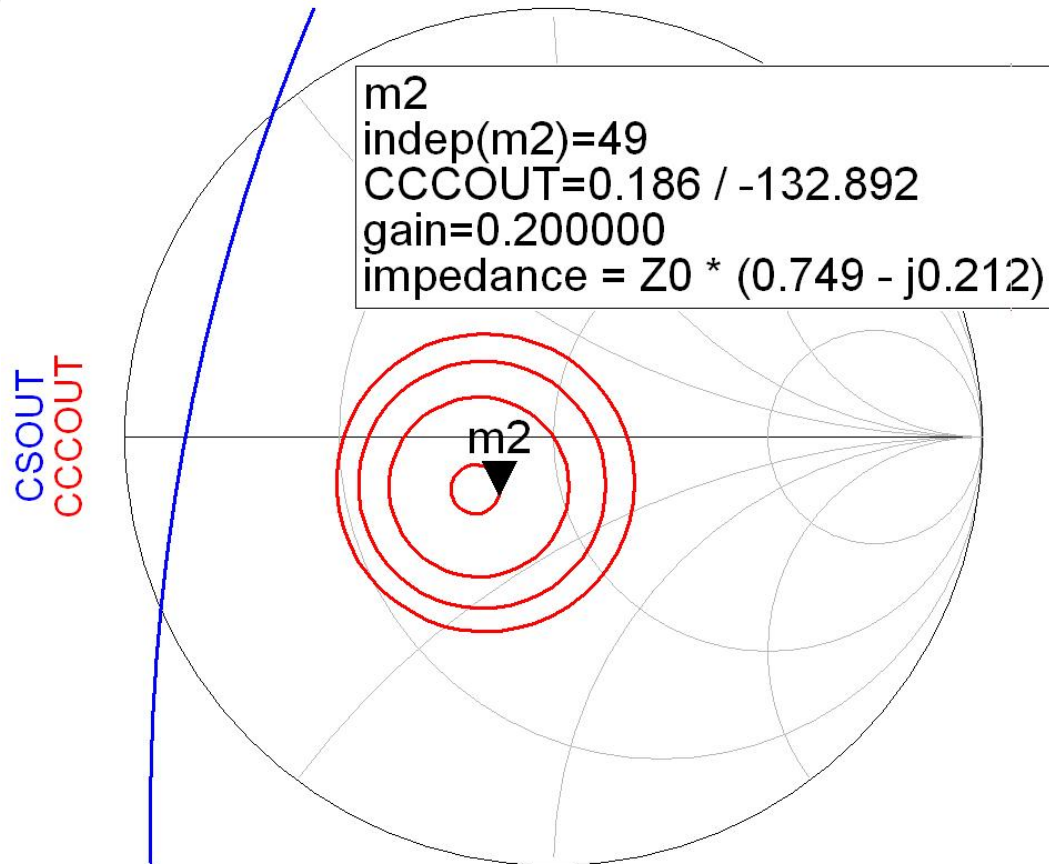

- $CCCOUT$: -0.4dB, -0.2dB, 0dB, +0.2dB
- Lipsa conditiilor privitoare la zgomot ofera posibilitatea obtinerii unui castig mai mare (spre maxim)

LNA

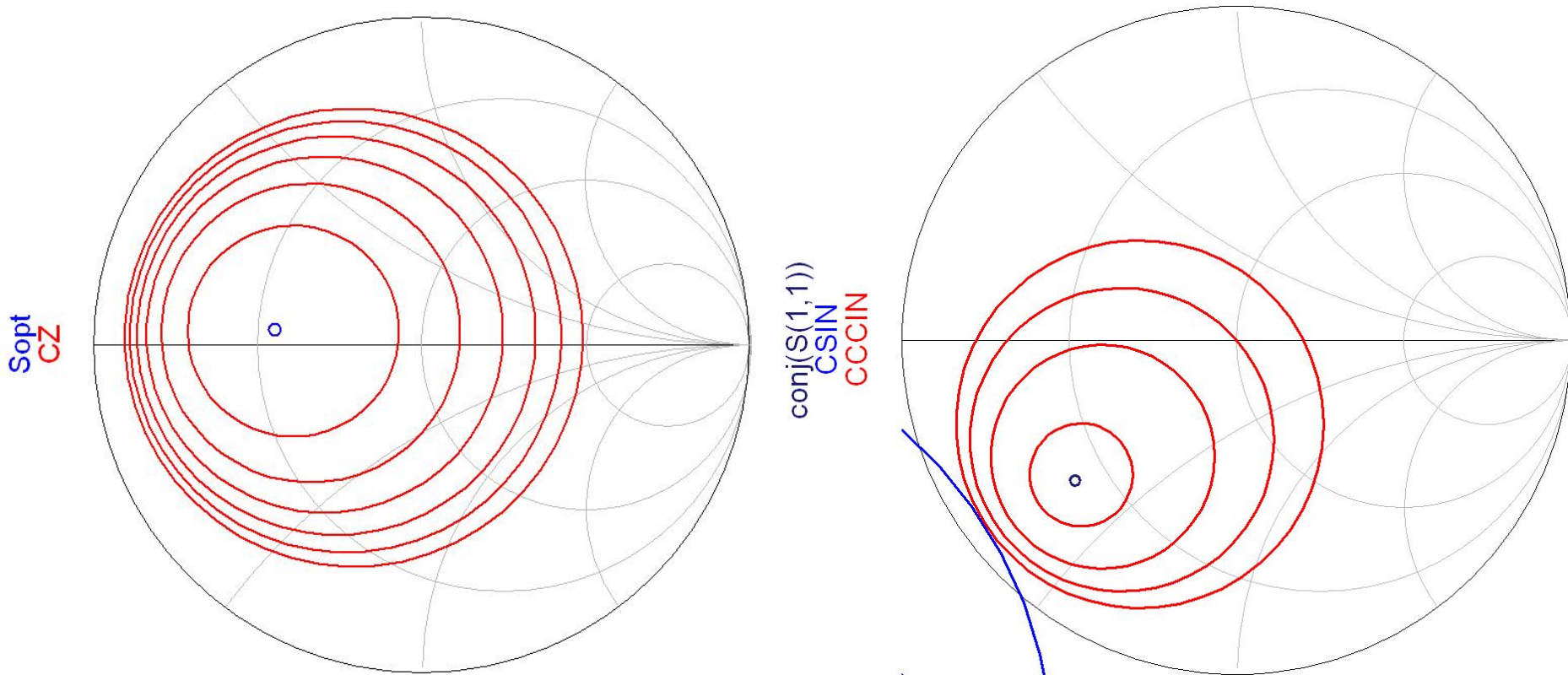- De obicei un tranzistor potrivit pentru implementarea unui LNA la o anumita frecventa va avea cercurile de castig la intrare si cercurile de zgomot in aceeasi zona pentru Γ_S



Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.etti.tuiasi.ro>
- rdamian@etti.tuiasi.ro