

Lecture 8

2017/2018

Microwave Devices and Circuits for Radiocommunications

Test

■ Wisdom of the crowd ??

Google

radiatie electromagnetica polarizata informational

All Images Videos News Maps

About 5,000 results (0.64 seconds)

✓ **Radiație electromagnetică - Wikipedia**
https://ro.wikipedia.org/wiki/Radiație_electroma
În funcție de frecvența sau lungimea de undă cu c undele electromagnetice se pot manifesta în div
[Clasificare](#) · [Teorie](#) · [Proprietăți](#)

WIKIPEDIA
Enciclopedia liberă

Pagina principală
Schimbări recente
Cafenea
Articol aleatoriu
Facebook

Participare
Cum încep pe Wikipedia
Ajutor
Portaluri tematice
Articole cerute
Donații

Tipărire/exportare
Creare carte
Descarcă PDF
Versiune de tipărit

În alte proiecte
Wikimedia Commons

Trusa de unelte
Ce trimite aici

Nu sunteți autentificat [Discuții](#) [Contribuții](#) [Creare cont](#) [Autentificare](#)

Articol [Discuție](#) [Lectură](#) [Modificare](#) [Modificare sursă](#) [Istoric](#)

Radiație electromagnetică [ascunde]

De la Wikipedia, enciclopedia liberă

Acest articol sau această secțiune are bibliografia incompletă sau inexistentă.
Puteti contribui prin adăugarea de referințe în vederea susținerii bibliografice a afirmațiilor pe care le conține.

Undele electromagnetice sau **radiația electromagnetică** sunt **fenomene fizice** în general naturale, care constă dintr-un **câmp electric** și unul **magnetic** în același spațiu, și care se generează reciproc pe măsură ce se propagă.

Cuprins [ascunde]


- 1 [Clasificare](#)
- 2 [Teorie](#)
- 3 [Proprietăți](#)
- 4 [Vezi și](#)
- 5 [Bibliografie](#)
- 6 [Legături externe](#)

Clasificare [modificare] [modificare sursă]

În funcție de

Test


- Wisdom of the crowd

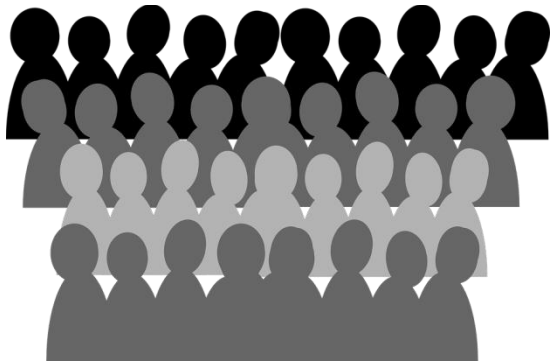

Google

Test

- Wisdom of the crowd ??

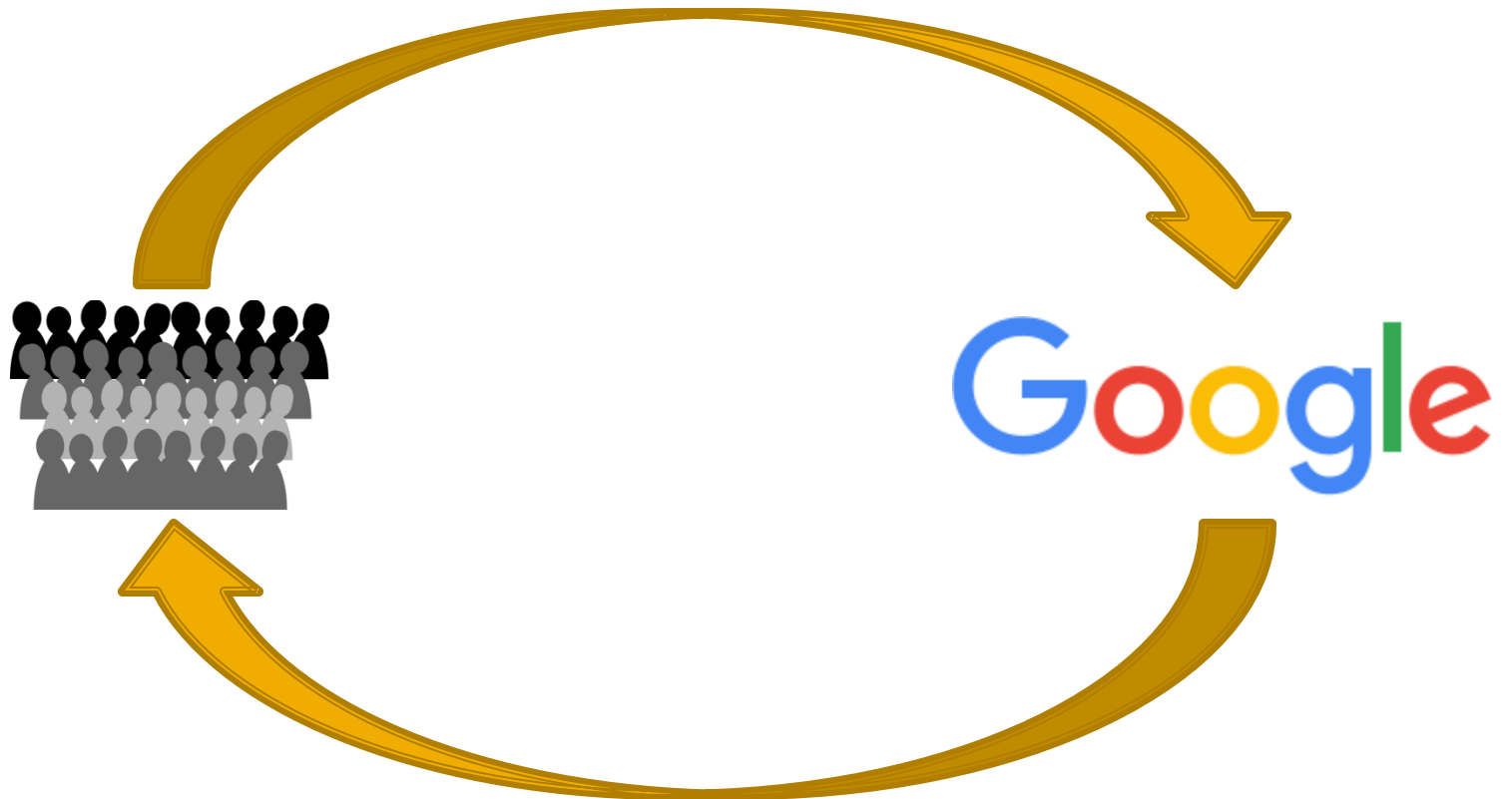

Materials

- RF-OPTO
 - <http://rf-opto.etti.tuiasi.ro>
- **David Pozar, “Microwave Engineering”,**
Wiley; 4th edition , 2011
 - 1 exam problem ← Pozar
- Photos
 - sent by email: rdamian@etti.tuiasi.ro
 - used at lectures/laboratory

Software

- ADS ~~2016~~ **2017**
- EmPro ~~2015~~ **2017**
- based on IP from outside university or campus



Date:

Grupa	5601 (2017/2018)
Specializarea	Master Retele de Comunicatii
Marca	857

[Acceseaza ca acest student](#) | [Cere acces la licente](#)

Note obtinute

Disciplina	Tip	Data	Descriere	Nota	Puncte	Obs.
TMPAW	Tehnici moderne de proiectare a aplicatiilor web					
	N	29/05/2017	Nota finala	10	-	

Nume

Email

Cod de verificare

Trimite

Software

Advanced Design System Premier High-Frequency and High Speed Design Platform

2016.01



© Keysight Technologies 1985-2016

Advanced Design System

Select a product license

You have more than one product license

Description

ADS Inclusive

GoldenGate All In

Update Availability

Legend: License available License in use or not available

ADS Inclusive


License is available

Number of licenses: 50


Used: 3

Version: 2018.07

Expires: 30-jul-

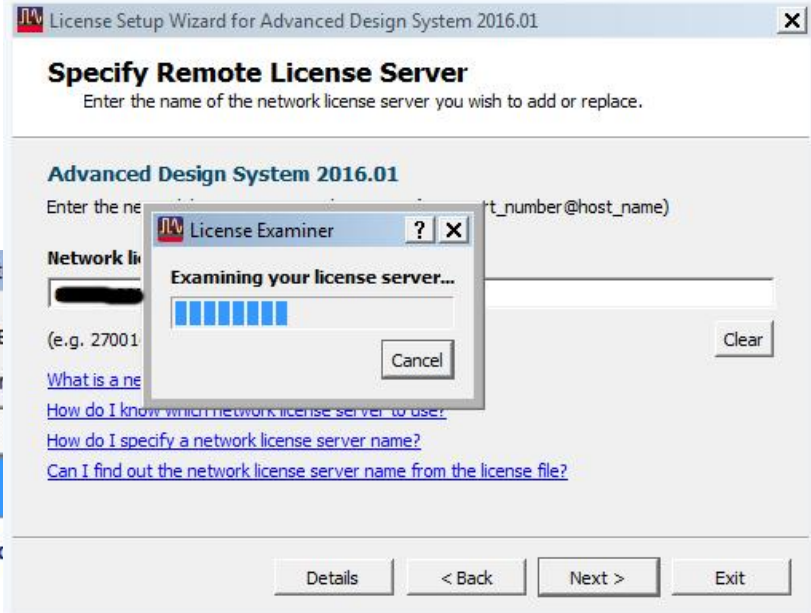

Reflection and power / Model

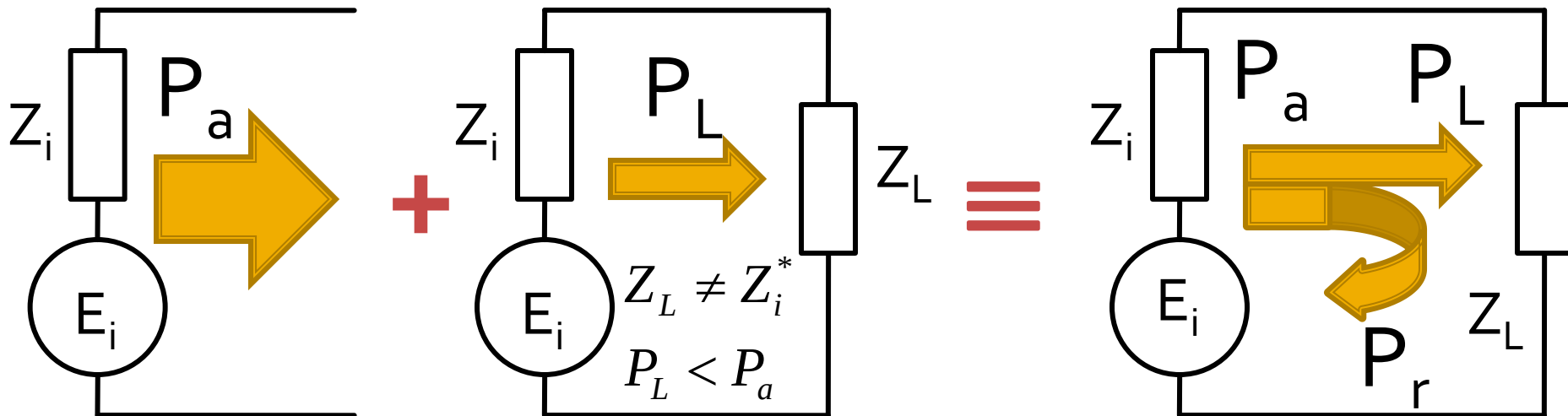


- The source has the ability to send to the load a certain maximum power (available power) P_a
- For a particular load the power sent to the load is less than the maximum (mismatch) $P_L < P_a$
- The phenomenon is **"as if"** (model) part of the input power is reflected $P_r = P_a - P_L$
- The power is a **scalar** !

TEM transmission lines

The lossless line

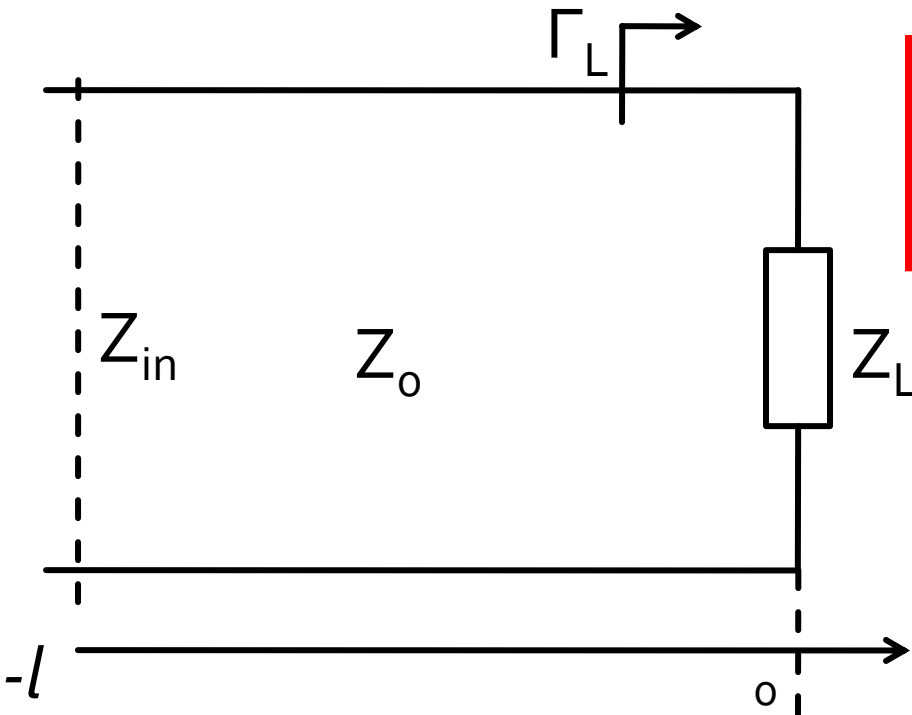
- input impedance of a length l of transmission line with characteristic impedance Z_0 , loaded with an arbitrary impedance Z_L



$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

Microwave Network Analysis

Scattering matrix – S

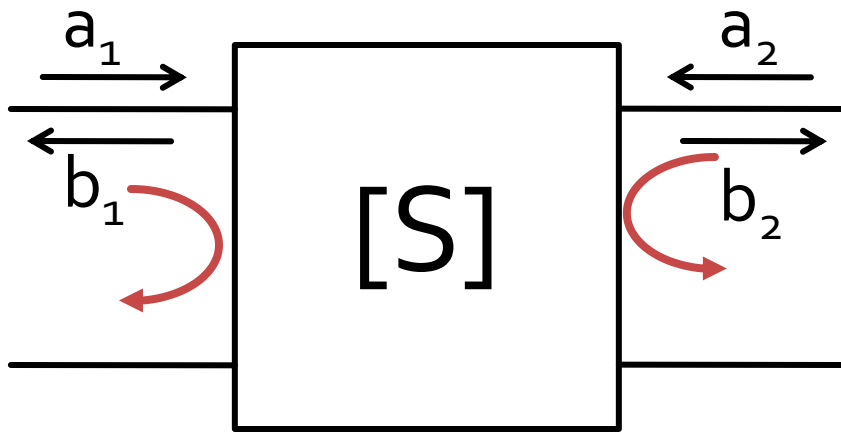


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

- S_{11} and S_{22} are reflection coefficients at ports 1 and 2 when the other port is matched

Scattering matrix – S

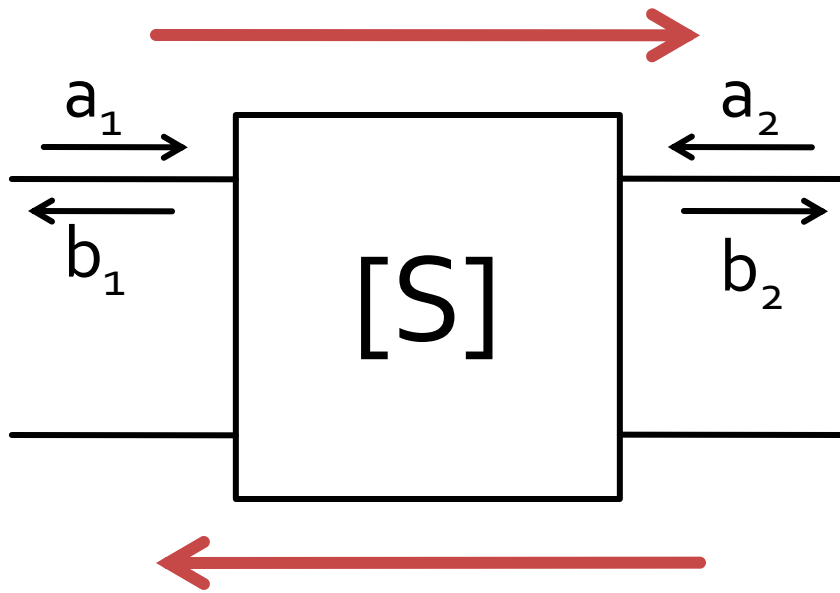


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$$

- S_{21} and S_{12} are signal amplitude gain when the other port is matched

Scattering matrix – S

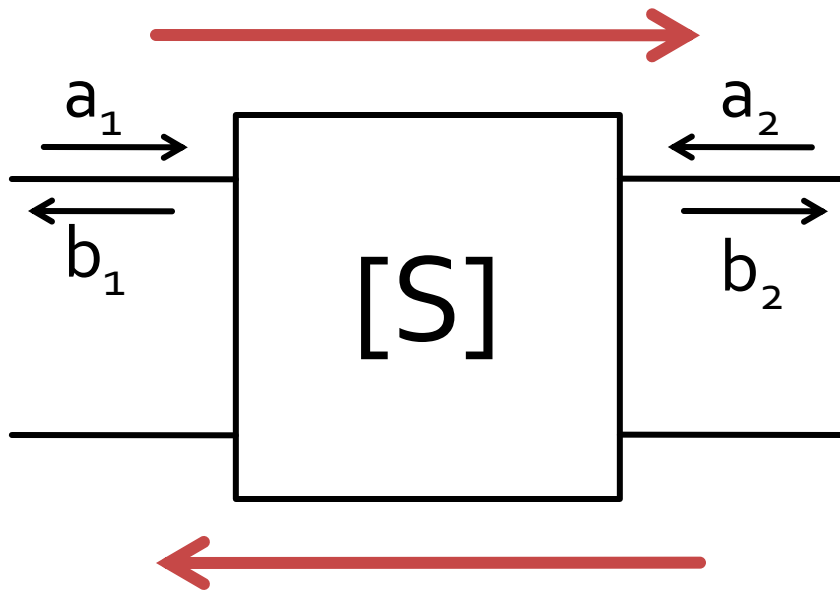

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$


$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- a, b
 - information about signal power **AND** signal phase
- S_{ij}
 - network effect (gain) over signal power **including** phase information

Impedance Matching




The Smith Chart

The Smith Chart

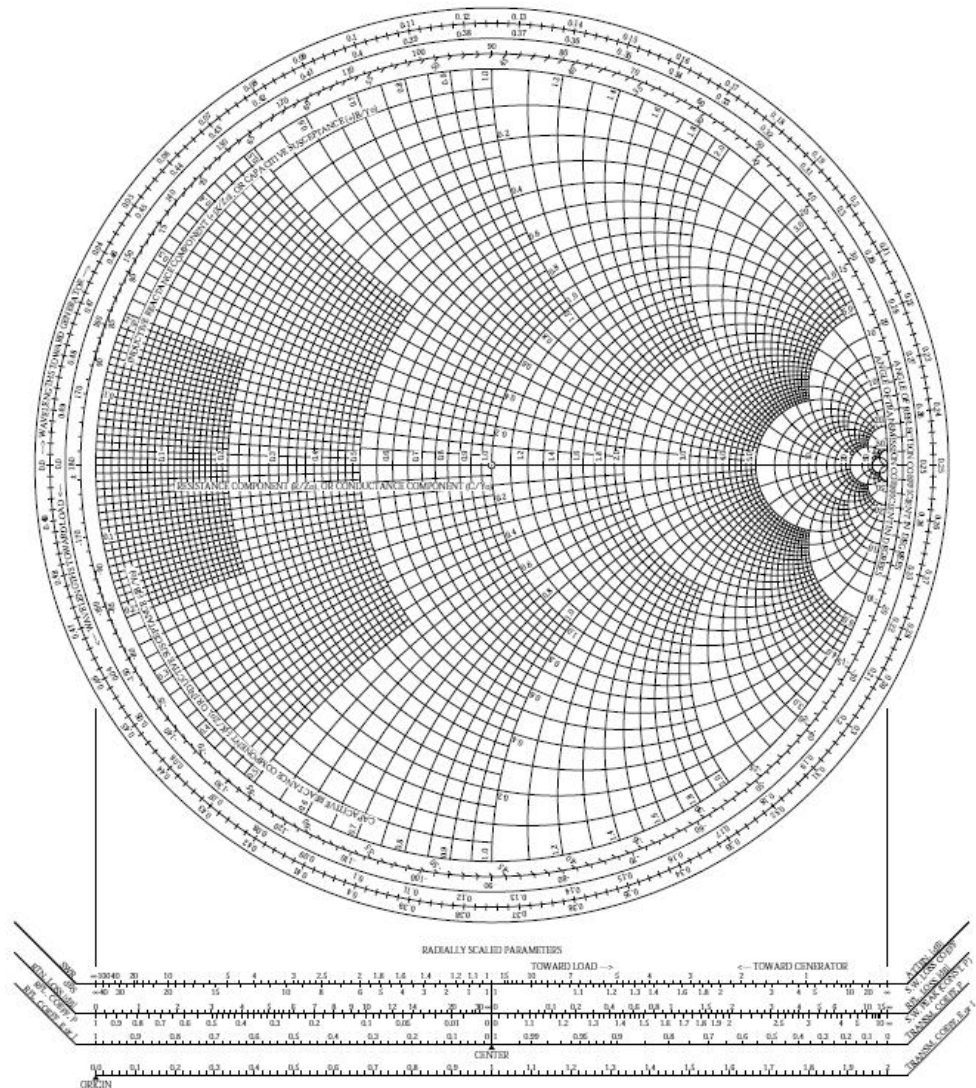


The Smith Chart

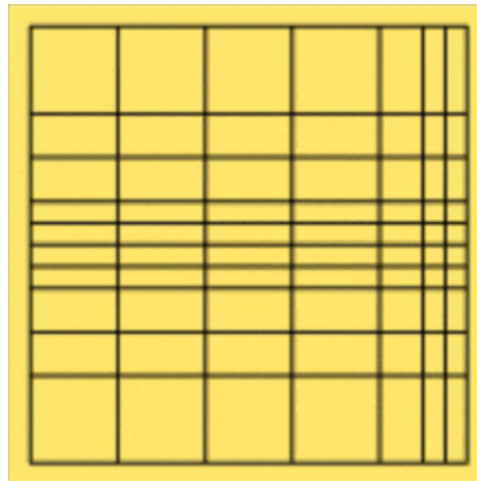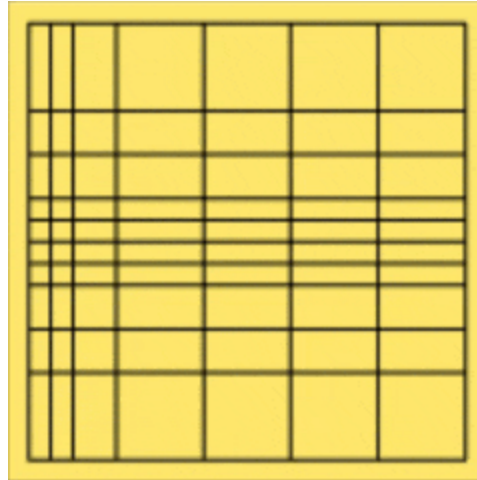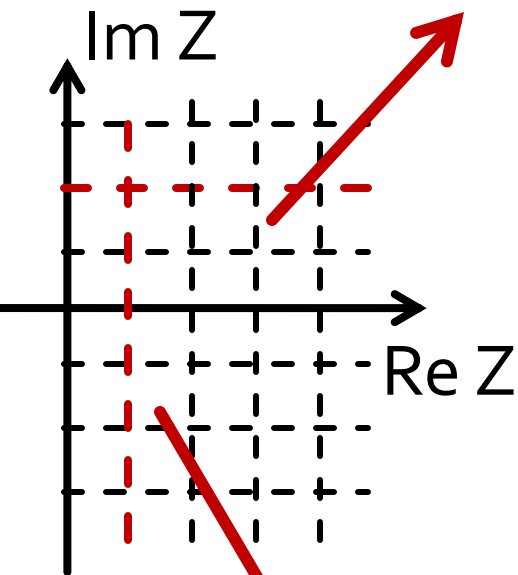
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$


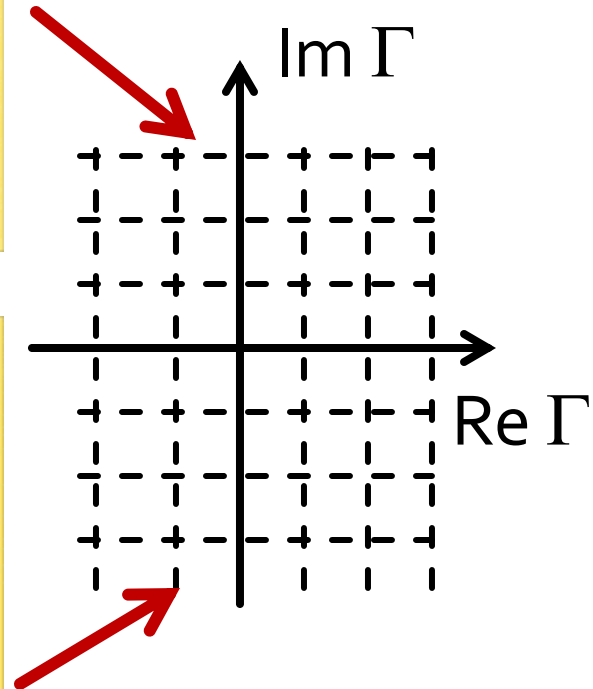
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Y_0 - Y_L}{Y_0 + Y_L} = \frac{1 - y_L}{1 + y_L}$$



The Smith Chart

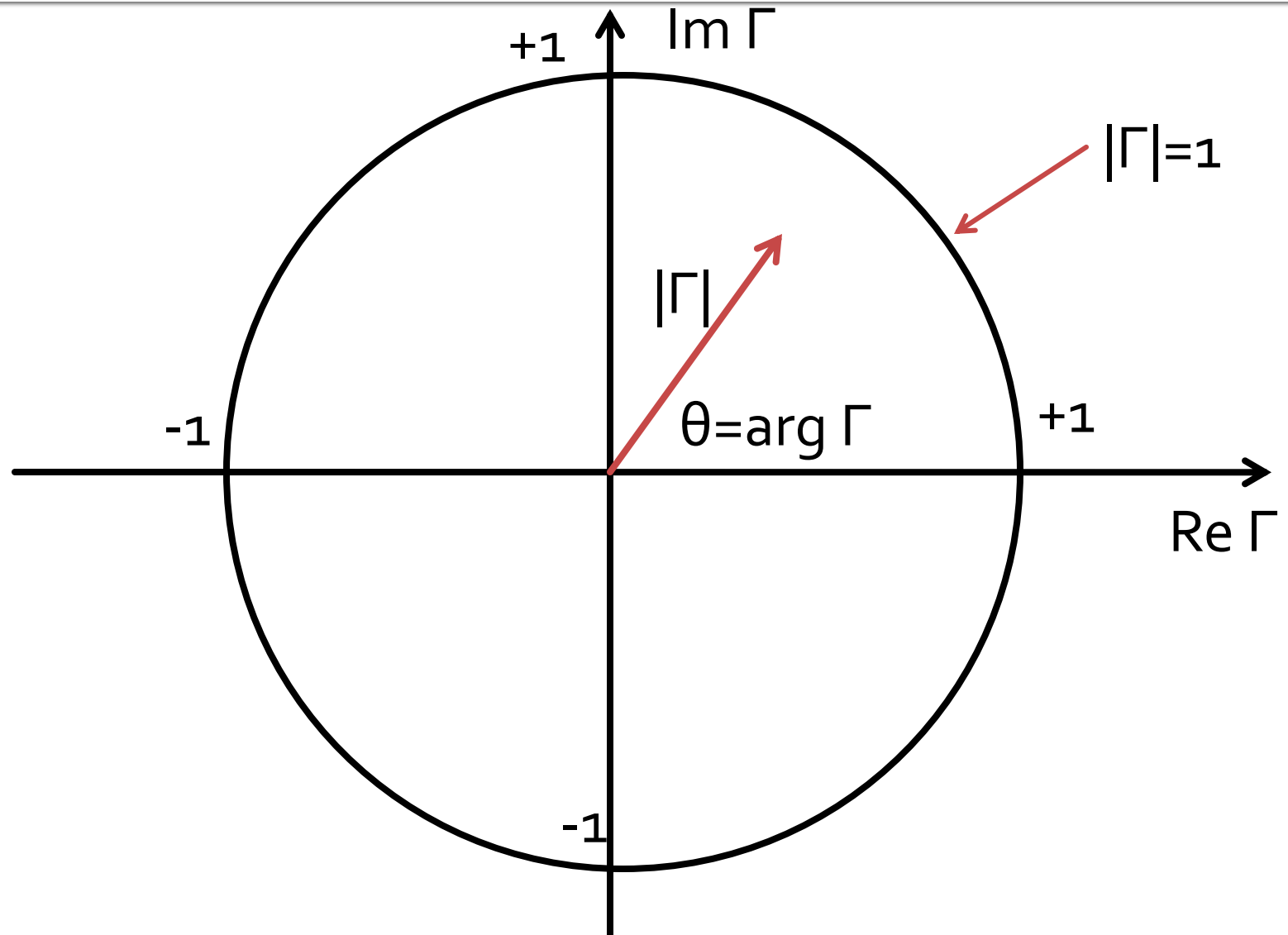


Impedance Matching with Stubs

Impedance Matching


Single stub tuning

- Shunt Stub

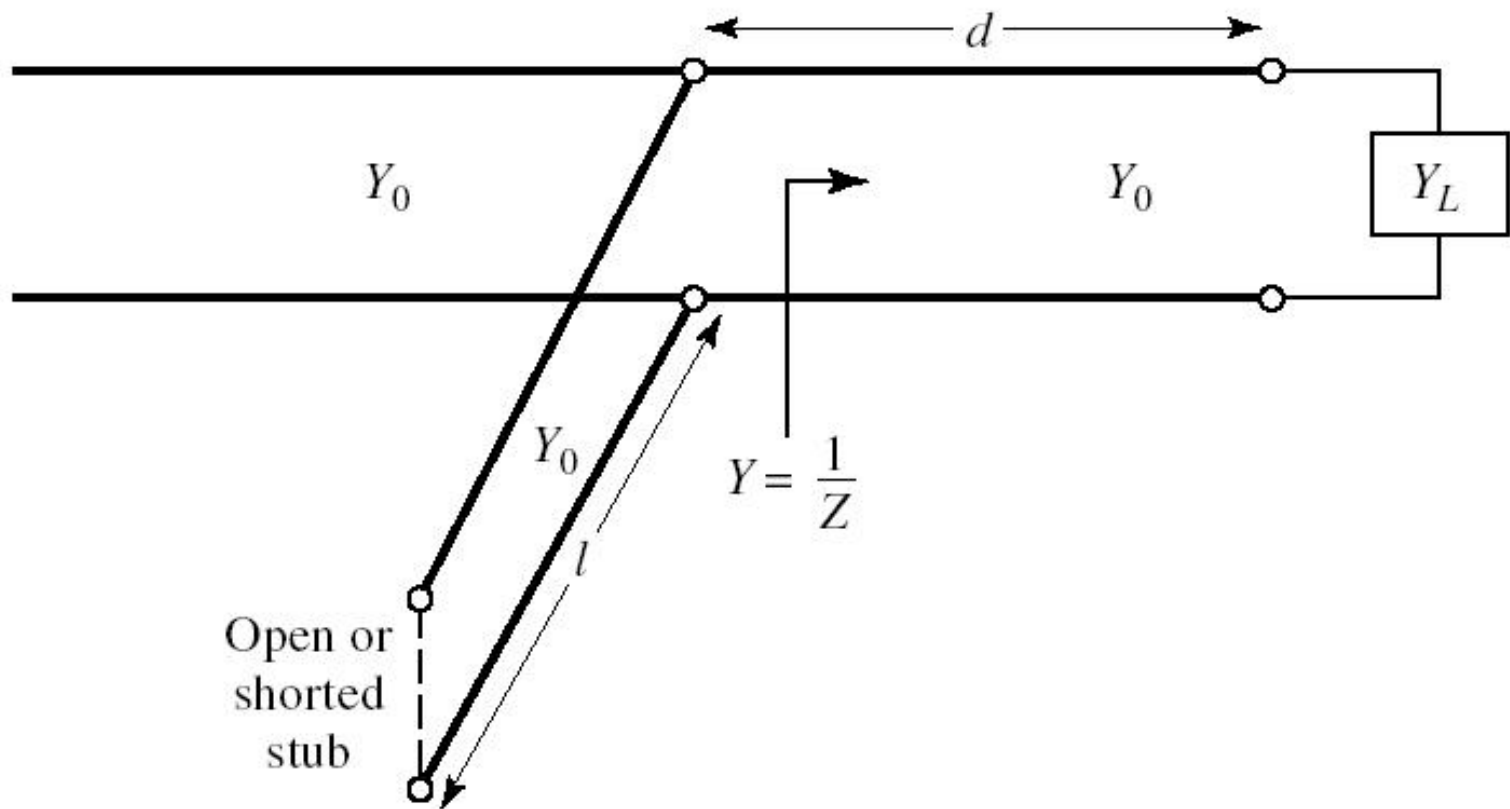


Single stub tuning

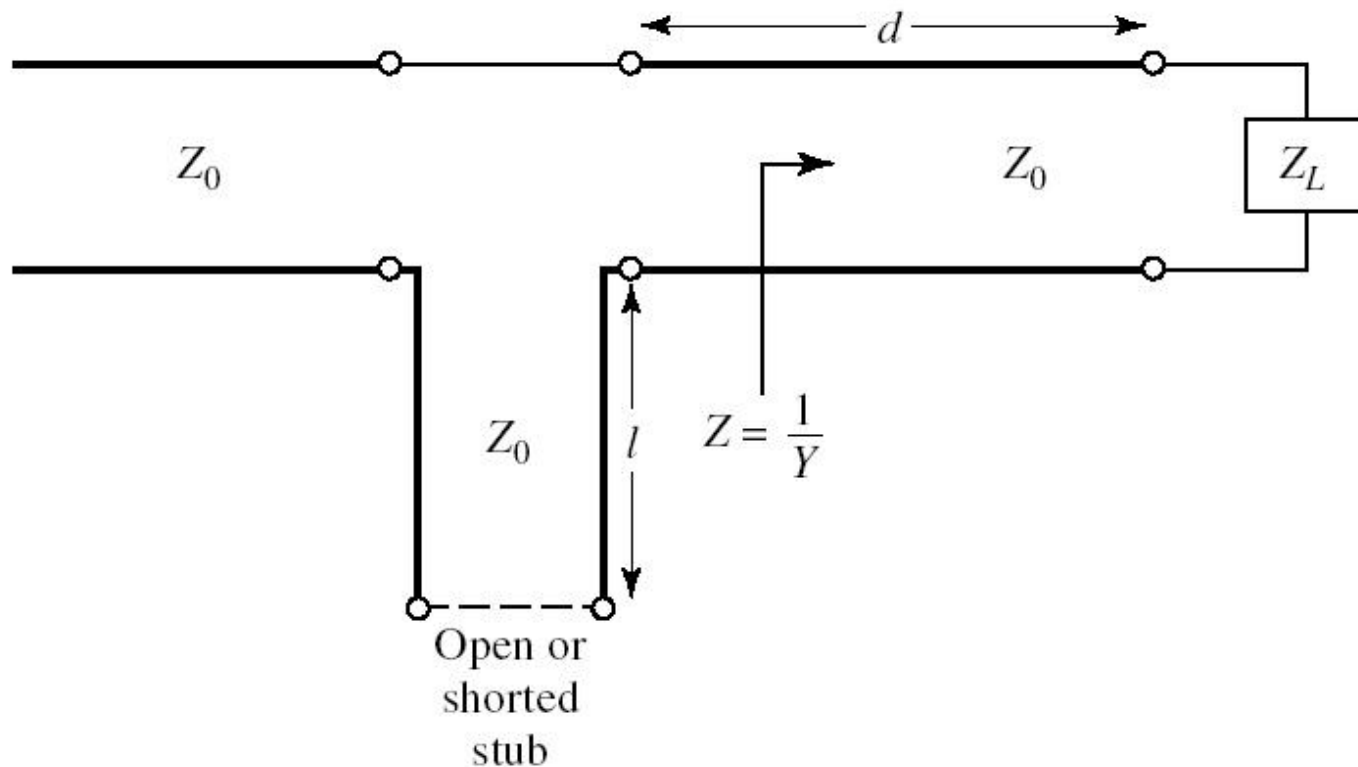- Series Stub
- difficult to realize in single conductor line technologies (microstrip)



Analytical solution, reflection coefficient

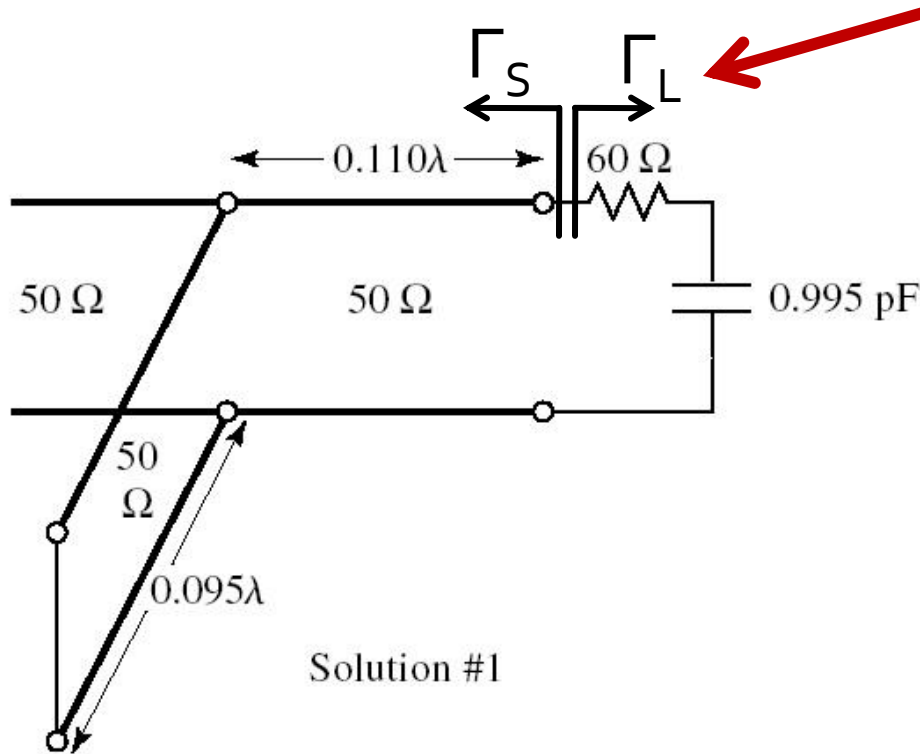- load: $60\ \Omega$ series with $0.995\ \text{pF}$ at 2GHz



$$Z_L = R_L + \frac{1}{j \cdot \omega \cdot C_L} = 60\Omega - j \cdot 79.977\Omega$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 0.405 - j \cdot 0.432$$

$$Y_L = \frac{1}{Z_L} = 0.006S + j \cdot 0.008S$$

$$y_L = \frac{Y_L}{Y_0} = 0.3 + j \cdot 0.4$$

- matching requires obtaining conjugate value for Γ


$$\Gamma_S = \Gamma_L^* = 0.405 + j \cdot 0.432$$

$$\Gamma_S = 0.593 \angle 46.85^\circ$$

$$|\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ$$

Analytical solution, Γ

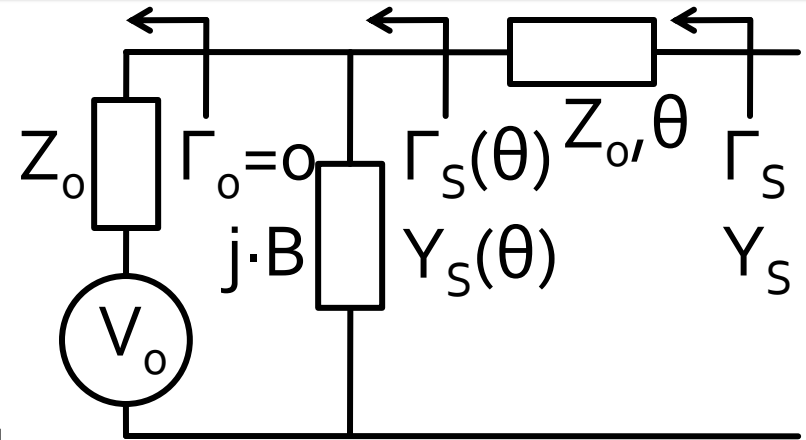- series line
 - electrical length $E = \beta \cdot l = \theta$
 - moves the reflection coefficient on the circle $g=1$
- shunt stub
 - electrical length $E = \beta \cdot l_{sp} = \theta_{sp}$
 - moves the reflection coefficient to the center of the Smith Chart ($\Gamma_o = 0$)



$$y_s = \frac{Y_s}{Y_0} = Y_s \cdot Z_0 = Y_s \cdot 50\Omega$$

$$y_s = \frac{1 - \Gamma_s}{1 + \Gamma_s} = 0.3 - j \cdot 0.4$$

$$\Gamma_s(\theta) = [\Gamma_L(\theta)]^* = [\Gamma_L \cdot e^{-2j\theta}]^*$$

$$\Gamma_s(\theta) = \Gamma_L^* \cdot e^{2j\theta} = \Gamma_s \cdot e^{2j\theta}$$

$$y_s(\theta) = \frac{1 - \Gamma_s(\theta)}{1 + \Gamma_s(\theta)} = \frac{1 - \Gamma_s \cdot e^{2j\theta}}{1 + \Gamma_s \cdot e^{2j\theta}}$$

Analytical solution, Γ , series line

- After the series line with electrical length θ :

$$\operatorname{Re}[y_s(\theta)] = 1$$

$$\operatorname{Im}[y_s(\theta)] = B$$

$$\operatorname{Re}[y_s(\theta)] = \frac{1}{2} \cdot [y_s(\theta) + y_s^*(\theta)]$$

$$\operatorname{Im}[y_s(\theta)] = \frac{1}{2j} \cdot [y_s(\theta) - y_s^*(\theta)]$$

$$\operatorname{Re}[y_s(\theta)] = \frac{1}{2} \cdot \left[\frac{1 - \Gamma_s \cdot e^{2j\theta}}{1 + \Gamma_s \cdot e^{2j\theta}} + \frac{1 - \Gamma_s^* \cdot e^{-2j\theta}}{1 + \Gamma_s^* \cdot e^{-2j\theta}} \right]$$

$$\Gamma_s = |\Gamma_s| \cdot e^{j\varphi}$$

$$\operatorname{Re}[y_s(\theta)] = \frac{1}{2} \cdot \left[\frac{(1 - |\Gamma_s| \cdot e^{j(\varphi+2\theta)}) \cdot (1 + |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) + (1 - |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 + |\Gamma_s| \cdot e^{j(\varphi+2\theta)})}{(1 + |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 + |\Gamma_s| \cdot e^{j(\varphi+2\theta)})} \right]$$

$$\operatorname{Re}[y_s(\theta)] = \frac{1}{2} \cdot \left[\frac{2 - 2 \cdot |\Gamma_s|^2}{1 + |\Gamma_s|^2 + 2 \cdot |\Gamma_s| \cdot \cos(\varphi + 2\theta)} \right] = 1 \Rightarrow \boxed{\cos(\varphi + 2\theta) = -|\Gamma_s|}$$

Analytical solution, Γ , series line

- Equations for computing the series line θ :

$$\operatorname{Re}[y_S(\theta)] = 1 \Rightarrow \cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = |\Gamma_S| \cdot e^{j\varphi} \quad \Gamma_S = 0.593 \angle 46.85^\circ \quad |\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ$$

- two solutions possible, in the $0 \div 180^\circ$ range (add $\lambda/2 \Leftrightarrow 180^\circ$ as needed)

$$\theta = \frac{1}{2} \cdot [\pm \cos^{-1}(-|\Gamma_S|) - \varphi + k \cdot 360^\circ] = \frac{1}{2} \cdot [\pm \cos^{-1}(-|\Gamma_S|) - \varphi] + k \cdot 180^\circ$$

$$\forall k \in \mathbb{N}$$

$$\cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^\circ$$

$$(46.85^\circ + 2\theta) = \begin{cases} +126.35^\circ \\ -126.35^\circ \end{cases}$$

$$\theta = \begin{cases} +39.7^\circ \\ -86.6^\circ + 180^\circ = +93.4^\circ \end{cases}$$

Analytical solution, Γ , shunt stub

- Equations for computing the shunt stub θ_{sp} :

$$\operatorname{Re}[y_s(\theta)] = 1 \qquad \cos(\varphi + 2\theta) = -|\Gamma_s|$$

$$\operatorname{Im}[y_s(\theta)] = \frac{1}{2j} \cdot \left[\frac{1 - \Gamma_s \cdot e^{2j\theta}}{1 + \Gamma_s \cdot e^{2j\theta}} - \frac{1 - \Gamma_s^* \cdot e^{-2j\theta}}{1 + \Gamma_s^* \cdot e^{-2j\theta}} \right] \qquad \Gamma_s = |\Gamma_s| \cdot e^{j\varphi}$$

$$\operatorname{Im}[y_s(\theta)] = \frac{1}{2j} \cdot \left[\frac{(1 - |\Gamma_s| \cdot e^{j(\varphi+2\theta)}) \cdot (1 + |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) - (1 - |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 + |\Gamma_s| \cdot e^{j(\varphi+2\theta)})}{(1 + |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 + |\Gamma_s| \cdot e^{j(\varphi+2\theta)})} \right]$$

$$\operatorname{Im}[y_s(\theta)] = \frac{1}{2j} \cdot \left[\frac{2 \cdot |\Gamma_s| \cdot e^{-j(\varphi+2\theta)} - 2 \cdot |\Gamma_s| \cdot e^{+j(\varphi+2\theta)}}{1 + |\Gamma_s|^2 + 2 \cdot |\Gamma_s| \cdot \cos(\varphi + 2\theta)} \right] = \frac{-2 \cdot |\Gamma_s| \cdot \sin(\varphi + 2\theta)}{1 + |\Gamma_s|^2 + 2 \cdot |\Gamma_s| \cdot \cos(\varphi + 2\theta)}$$

$$\cos(\varphi + 2\theta) = -|\Gamma_s| \Rightarrow \qquad \operatorname{Im}[y_s(\theta)] = \frac{-2 \cdot |\Gamma_s| \cdot \sin(\varphi + 2\theta)}{1 - |\Gamma_s|^2}$$

Analytical solution, Γ , shunt stub

- Equations for computing the shunt stub

$$\cos(\varphi + 2\theta) = -|\Gamma_S| \Rightarrow \sin(\varphi + 2\theta) = \pm \sqrt{1 - |\Gamma_S|^2}$$

$$\text{Im}[y_S(\theta)] = \frac{-2 \cdot |\Gamma_S| \cdot \sin(\varphi + 2\theta)}{1 - |\Gamma_S|^2} \Rightarrow \text{Im}[y_S(\theta)] = \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

- two cases

$$\varphi + 2\theta \in [0^\circ, 180^\circ] \Rightarrow \sin(\varphi + 2\theta) \geq 0 \quad \left\{ \begin{array}{l} \sin(\varphi + 2\theta) = \sqrt{1 - |\Gamma_S|^2} \\ \text{Im}[y_S(\theta)] = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} \end{array} \right.$$

$$\varphi + 2\theta \in (-180^\circ, 0^\circ) \Rightarrow \sin(\varphi + 2\theta) < 0 \quad \left\{ \begin{array}{l} \sin(\varphi + 2\theta) = -\sqrt{1 - |\Gamma_S|^2} \\ \text{Im}[y_S(\theta)] = \frac{2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} \end{array} \right.$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

Analytical solution, Γ , shunt stub

- We prefer (for microstrip) open circuited stub

$$Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$

- The normalized susceptance to be introduced to achieve the match
 - $Y(\theta)$ is the admittance seen **towards** the source, Z_0 parallel with $j \cdot B$

$$b = \text{Im} \left[\frac{Y_{in,oc}}{Y_0} \right] = \text{Im} \left[\frac{Z_0}{Z_{in,oc}} \right] = \tan \beta \cdot l = \text{Im}[y_s(\theta)]$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

Analytical solution, Γ

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = 0.593 \angle 46.85^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ \quad \cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **"+" solution** ↓

$$(46.85^\circ + 2\theta) = +126.35^\circ \quad \theta = +39.7^\circ \quad \text{Im } y_s = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.472$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_s) = -55.8^\circ (+180^\circ) \rightarrow \theta_{sp} = 124.2^\circ$$

- **"-" solution** ↓

$$(46.85^\circ + 2\theta) = -126.35^\circ \quad \theta = -86.6^\circ (+180^\circ) \rightarrow \theta = 93.4^\circ$$

$$\text{Im } y_s = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +1.472 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_s) = 55.8^\circ$$

Analytical solution, Γ

$$(\varphi + 2\theta) = \begin{cases} +126.35^\circ \\ -126.35^\circ \end{cases} \quad \theta = \begin{cases} 39.7^\circ \\ 93.4^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -1.472 \\ +1.472 \end{cases} \quad \theta_{sp} = \begin{cases} -55.8^\circ + 180^\circ = 124.2^\circ \\ +55.8^\circ \end{cases}$$



- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

$$l_1 = \frac{39.7^\circ}{360^\circ} \cdot \lambda = 0.110 \cdot \lambda$$

$$l_2 = \frac{124.2^\circ}{360^\circ} \cdot \lambda = 0.345 \cdot \lambda$$


$$l_1 = \frac{93.4^\circ}{360^\circ} \cdot \lambda = 0.259 \cdot \lambda$$
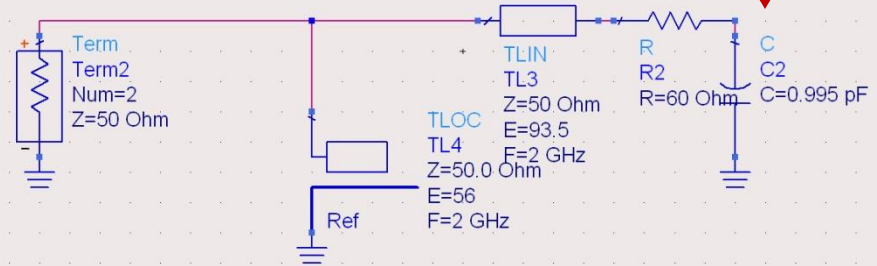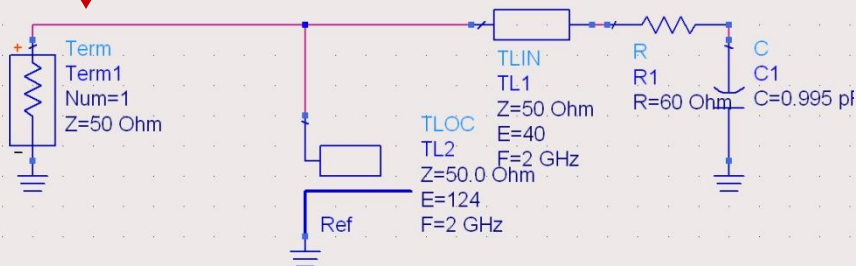
$$l_2 = \frac{55.8^\circ}{360^\circ} \cdot \lambda = 0.155 \cdot \lambda$$




Case 2, Series Stub

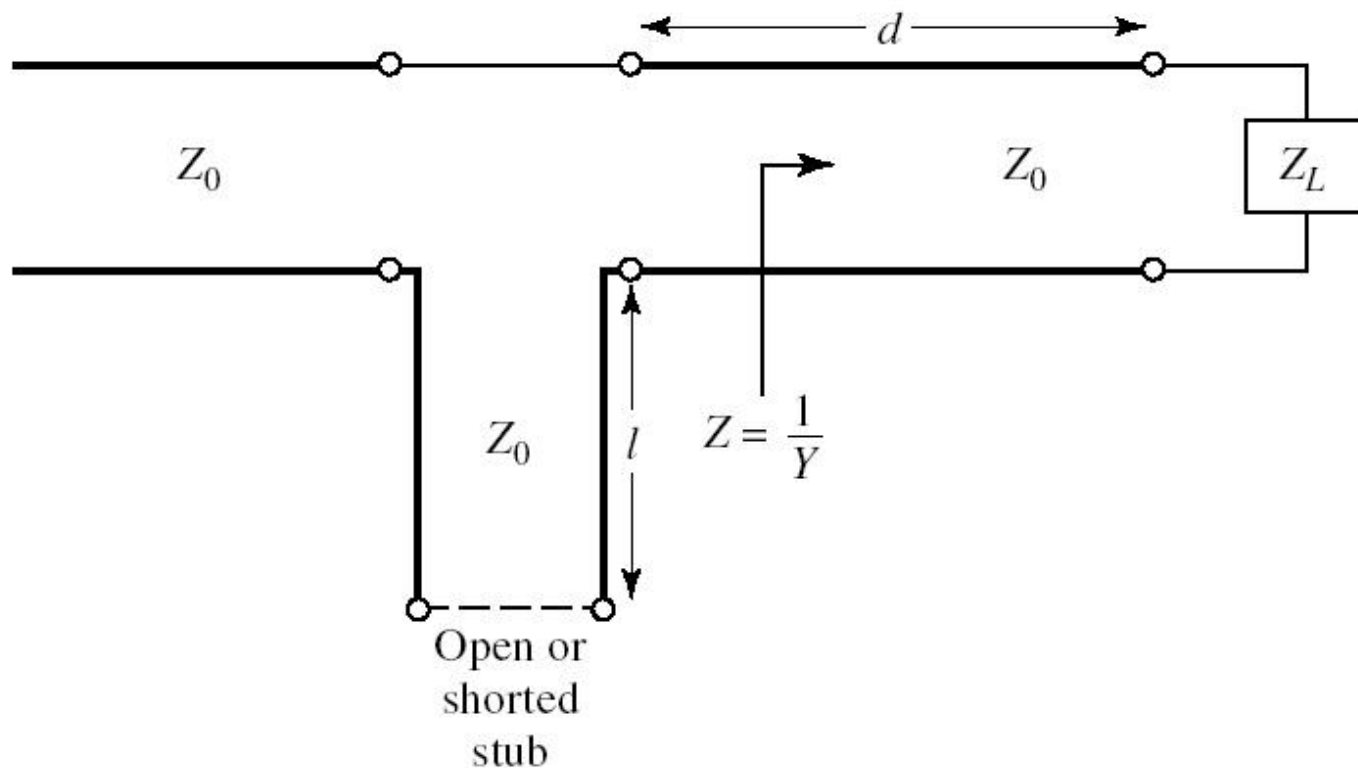- Series Stub
- difficult to realize in single conductor line technologies (microstrip)



Analytical solution, reflection coefficient

- load: $100\ \Omega$ series with $6.37\ \text{nH}$ at $2\ \text{GHz}$

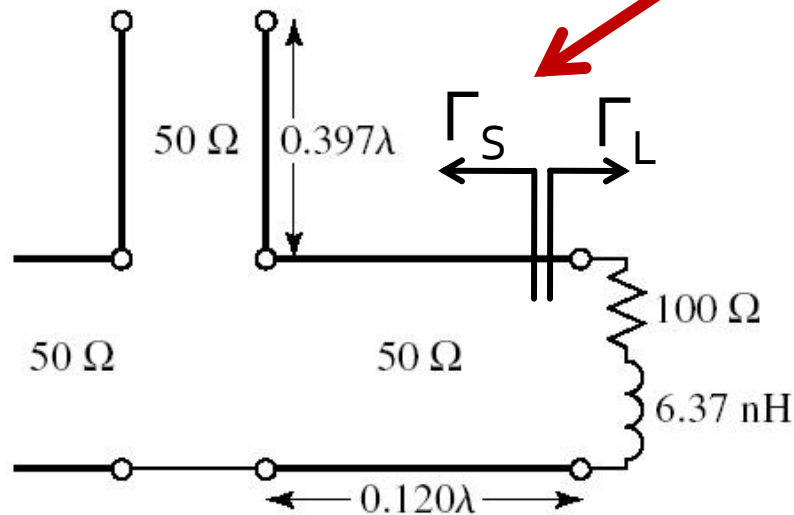

Solution 1

$$Z_L = R_L + \frac{1}{j \cdot \omega \cdot C_L} = 100\Omega + j \cdot 80.05\Omega$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 0.481 + j \cdot 0.277$$

$$z_L = \frac{Z_L}{Z_0} = 2 + j \cdot 1.6$$

- matching requires obtaining conjugate value for Γ

$$\Gamma_S = \Gamma_L^* = 0.481 - j \cdot 0.277$$

$$\Gamma_S = 0.555 \angle -29.92^\circ$$

$$|\Gamma_S| = 0.555; \quad \varphi = -29.92^\circ$$

Analytical solution, Γ

$$\cos(\varphi + 2\theta) = |\Gamma_s|$$

$$\theta_{ss} = \beta \cdot l = \cot^{-1} \frac{\mp 2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}}$$

$$\Gamma_s = 0.555 \angle -29.92^\circ$$

$$|\Gamma_s| = 0.555; \quad \varphi = -29.92^\circ \quad \cos(\varphi + 2\theta) = 0.555 \Rightarrow (\varphi + 2\theta) = \pm 56.28^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

- **"+" solution**

$$(-29.92^\circ + 2\theta) = +56.28^\circ$$

$$\theta = 43.1^\circ$$

$$\text{Im } z_s = \frac{+2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} = +1.335$$

$$\theta_{ss} = -\cot^{-1}(\text{Im } z_s) = -36.8^\circ (+180^\circ) \rightarrow \theta_{ss} = 143.2^\circ$$

- **"-" solution**

$$(-29.92^\circ + 2\theta) = -56.28^\circ$$

$$\theta = -13.2^\circ (+180^\circ) \rightarrow \theta = 166.8^\circ$$

$$\text{Im } z_s = \frac{-2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} = -1.335$$

$$\theta_{ss} = -\cot^{-1}(\text{Im } z_s) = 36.8^\circ$$

Analytical solution, Γ

$$(\varphi + 2\theta) = \begin{cases} +56.28^\circ \\ -56.28^\circ \end{cases} \quad \theta = \begin{cases} 43.1^\circ \\ 166.8^\circ \end{cases} \quad \text{Im}[z_s(\theta)] = \begin{cases} +1.335 \\ -1.335 \end{cases} \quad \theta_{ss} = \begin{cases} -36.8^\circ + 180^\circ = 143.2^\circ \\ +36.8^\circ \end{cases}$$



- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

$$l_1 = \frac{43.1^\circ}{360^\circ} \cdot \lambda = 0.120 \cdot \lambda$$

$$l_2 = \frac{143.2^\circ}{360^\circ} \cdot \lambda = 0.398 \cdot \lambda$$


$$l_1 = \frac{166.8^\circ}{360^\circ} \cdot \lambda = 0.463 \cdot \lambda$$
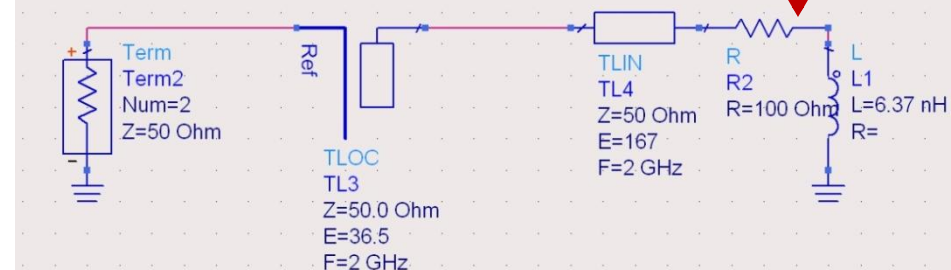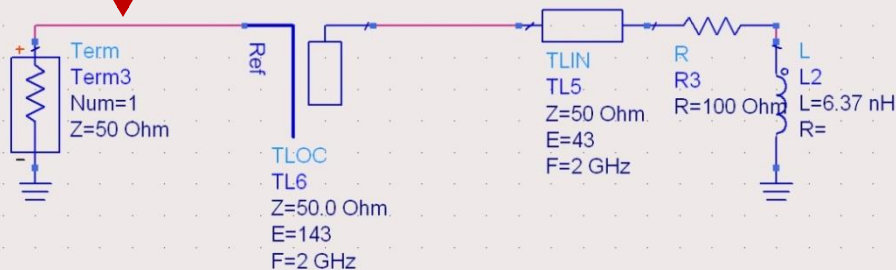
$$l_2 = \frac{36.8^\circ}{360^\circ} \cdot \lambda = 0.102 \cdot \lambda$$



Microwave Amplifiers

Amplifier as two-port

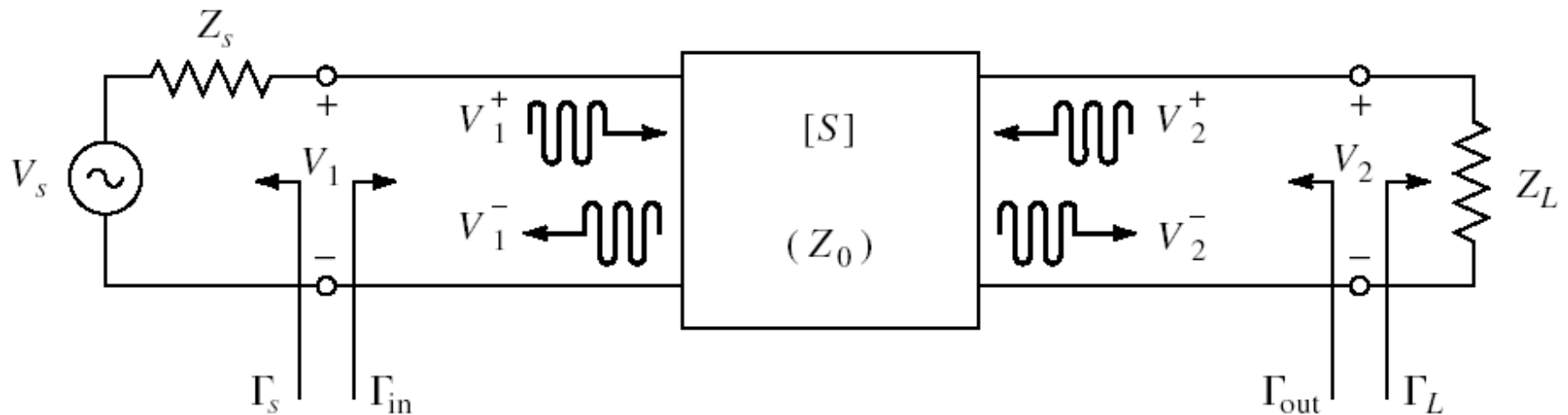

- Characterized with S parameters
- normalized at Z_0 (implicit 50Ω)
- Datasheets: S parameters for specific bias conditions

Datasheets

NE46100

VCE = 5 V, Ic = 50 mA

FREQUENCY (MHz)	S11		S21		S12		S22		K	MAG ² (dB)
	MAG	ANG	MAG	ANG	MAG	ANG	MAG	ANG		
100	0.778	-137	26.776	114	0.028	30	0.555	-102	0.16	29.8
200	0.815	-159	14.407	100	0.035	29	0.434	-135	0.36	26.2
500	0.826	-177	5.855	84	0.040	38	0.400	-162	0.75	21.7
800	0.827	176	3.682	76	0.052	43	0.402	-169	0.91	18.5
1000	0.826	173	2.963	71	0.058	47	0.405	-172	1.02	16.3
1200	0.825	170	2.441	66	0.064	47	0.412	-174	1.08	14.0
1400	0.820	167	2.111	61	0.069	47	0.413	-176	1.17	12.4
1600	0.828	165	1.863	57	0.078	54	0.426	-177	1.15	11.4
1800	0.827	162	1.671	53	0.087	50	0.432	-178	1.14	10.6
2000	0.828	159	1.484	49	0.093	50	0.431	-180	1.17	9.5
2500	0.822	153	1.218	39	0.11	48	0.462	177	1.18	7.8
3000	0.818	148	1.010	30	0.135	46	0.490	174	1.16	6.3
3500	0.824	142	0.876	21	0.147	44	0.507	170	1.16	5.3
4000	0.812	137	0.762	13	0.168	38	0.535	167	1.14	4.3

VCE = 5 V, Ic = 100 mA


100	0.778	-144	27.669	111	0.027	35	0.523	-114	0.27	30.2
200	0.820	-164	14.559	97	0.029	29	0.445	-144	0.42	27.0
500	0.832	-179	5.885	84	0.035	38	0.435	-166	0.81	22.2
800	0.833	175	3.691	76	0.048	45	0.435	-173	0.95	18.8
1000	0.831	172	2.980	71	0.056	51	0.437	-176	1.05	16.0
1200	0.836	169	2.464	67	0.061	52	0.432	-178	1.11	14.0
1400	0.829	166	2.121	61	0.072	53	0.447	-180	1.12	12.6
1600	0.831	164	1.867	58	0.080	54	0.445	179	1.14	11.4

S2P - Touchstone

- Touchstone file format (*.s2p)

```
! SIEMENS Small Signal Semiconductors
! VDS = 3.5 V   ID = 15 mA
# GHz S MA R 50
! f      S11      S21      S12      S22
! GHz   MAG ANG   MAG ANG   MAG ANG   MAG ANG
1.000 0.9800 -18.0 2.230 157.0 0.0240 74.0 0.6900 -15.0
2.000 0.9500 -39.0 2.220 136.0 0.0450 57.0 0.6600 -30.0
3.000 0.8900 -64.0 2.210 110.0 0.0680 40.0 0.6100 -45.0
4.000 0.8200 -89.0 2.230 86.0 0.0850 23.0 0.5600 -62.0
5.000 0.7400 -115.0 2.190 61.0 0.0990 7.0 0.4900 -80.0
6.000 0.6500 -142.0 2.110 36.0 0.1070 -10.0 0.4100 -98.0
!
! f      Fmin  Gammaopt rn/50
! GHz    dB   MAG ANG  -
2.000    1.00 0.72 27 0.84
4.000    1.40 0.64 61 0.58
```

Amplifier as two-port

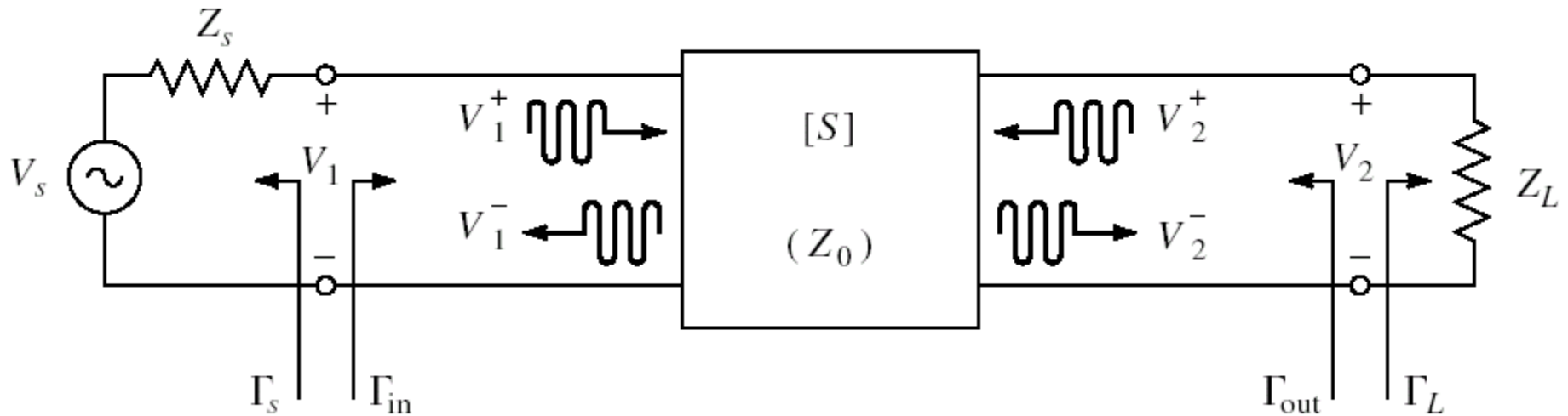

$$\Gamma_{in} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_{out} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_s}{1 - S_{11} \cdot \Gamma_s}$$

Two-Port Power Gains

- Power Gain

$$G = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) \cdot |1 - S_{22} \cdot \Gamma_L|^2}$$

$$P_{in} = P_{in}(\Gamma_S, \Gamma_{in}(\Gamma_L), S)$$

$$P_L = P_L(\Gamma_S, \Gamma_{in}(\Gamma_L), S)$$

- The **actual** power gain **introduced** by the amplifier is less important because a higher gain may be accompanied by a **decrease** in input power (power actually drained from the source)
- We prefer to characterize the amplifier effect looking to the **power actually delivered to the load** in relation to the power **available from the source** (which is a constant)

Two-Port Power Gains

- **Available** power gain

$$G_A = \frac{P_{avL}}{P_{avS}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2)}{|1 - S_{22} \cdot \Gamma_L|^2 \cdot (1 - |\Gamma_{out}|^2)}$$

- **Transducer** power gain

$$G_T = \frac{P_L}{P_{avS}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2}$$

$$\Gamma_{in} = \Gamma_{in}(\Gamma_L)$$

- **Unilateral transducer** power gain


$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$S_{12} \cong 0$$

$$\Gamma_{in} = S_{11}$$

Input and output can be treated independently

Amplifier as two-port

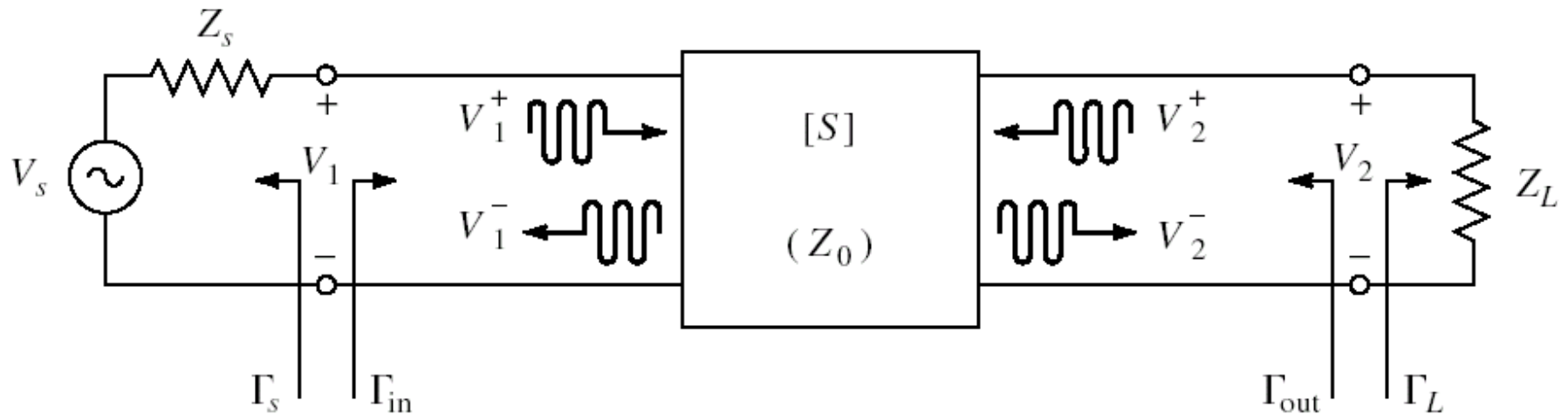

- For an amplifier two-port we are interested in:
 - stability
 - power gain
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)

Stability

Microwave Amplifiers

Stability

- C6 $\Gamma = \Gamma_r + j \cdot \Gamma_i$ $r_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$
 Z_{in} $\Gamma_{in} = \Gamma_r + j \cdot \Gamma_i$

- instability

$$\operatorname{Re}\{Z_{in}\} < 0 \Leftrightarrow 1 - \Gamma_r^2 - \Gamma_i^2 < 0 \quad |\Gamma_{in}| > 1$$

- stability, Z_{in}

- conditions to be met by Γ_L to achieve (input) stability

$$|\Gamma_{in}| < 1 \quad \left| S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \right| < 1$$

- similarly Z_{out}

- conditions to be met by Γ_S to achieve (output) stability

Stability

$$|\Gamma_{in}| < 1 \quad \left| S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \right| < 1$$

- We can calculate conditions to be met by Γ_L to achieve stability

$$|\Gamma_{out}| < 1 \quad \left| S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S} \right| < 1$$

- We can calculate conditions to be met by Γ_S to achieve stability

Stability

$$|\Gamma_{in}| < 1 \quad \left| S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \right| < 1$$

- The limit between stability/instability

$$|\Gamma_{in}| = 1 \quad \left| S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \right| = 1$$

$$|S_{11} \cdot (1 - S_{22} \cdot \Gamma_L) + S_{12} \cdot S_{21} \cdot \Gamma_L| = |1 - S_{22} \cdot \Gamma_L|$$

- determinant of the S matrix $\Delta = S_{11} \cdot S_{22} - S_{12} \cdot S_{21}$

$$|S_{11} - \Delta \cdot \Gamma_L| = |1 - S_{22} \cdot \Gamma_L|$$

$$|S_{11} - \Delta \cdot \Gamma_L|^2 = |1 - S_{22} \cdot \Gamma_L|^2$$

Stability

$$|S_{11} - \Delta \cdot \Gamma_L|^2 = |1 - S_{22} \cdot \Gamma_L|^2$$

$$a \cdot a^* = |a| \cdot e^{j\theta} \cdot |a| \cdot e^{-j\theta} = |a|^2$$

$$|a + b|^2 = (a + b) \cdot (a + b)^* = (a + b) \cdot (a^* + b^*) = |a|^2 + |b|^2 + a^* \cdot b + a \cdot b^*$$


$$|S_{11}|^2 + |\Delta|^2 \cdot |\Gamma_L|^2 - (\Delta \cdot \Gamma_L \cdot S_{11}^* + \Delta^* \cdot \Gamma_L^* \cdot S_{11}) = 1 + |S_{22}|^2 \cdot |\Gamma_L|^2 - (S_{22}^* \cdot \Gamma_L^* + S_{22} \cdot \Gamma_L)$$

$$(|S_{22}|^2 - |\Delta|^2) \cdot \Gamma_L \cdot \Gamma_L^* - (S_{22} - \Delta \cdot S_{11}^*) \cdot \Gamma_L - (S_{22}^* - \Delta^* \cdot S_{11}) \cdot \Gamma_L^* = |S_{11}|^2 - 1$$

$$\Gamma_L \cdot \Gamma_L^* - \frac{(S_{22} - \Delta \cdot S_{11}^*) \cdot \Gamma_L + (S_{22}^* - \Delta^* \cdot S_{11}) \cdot \Gamma_L^*}{|S_{22}|^2 - |\Delta|^2} = \frac{|S_{11}|^2 - 1}{|S_{22}|^2 - |\Delta|^2} + \frac{|S_{22} - \Delta \cdot S_{11}^*|^2}{(|S_{22}|^2 - |\Delta|^2)^2}$$

$$\left| \Gamma_L - \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \right|^2 = \frac{|S_{11}|^2 - 1}{|S_{22}|^2 - |\Delta|^2} + \frac{|S_{22} - \Delta \cdot S_{11}^*|^2}{(|S_{22}|^2 - |\Delta|^2)^2}$$

Stability

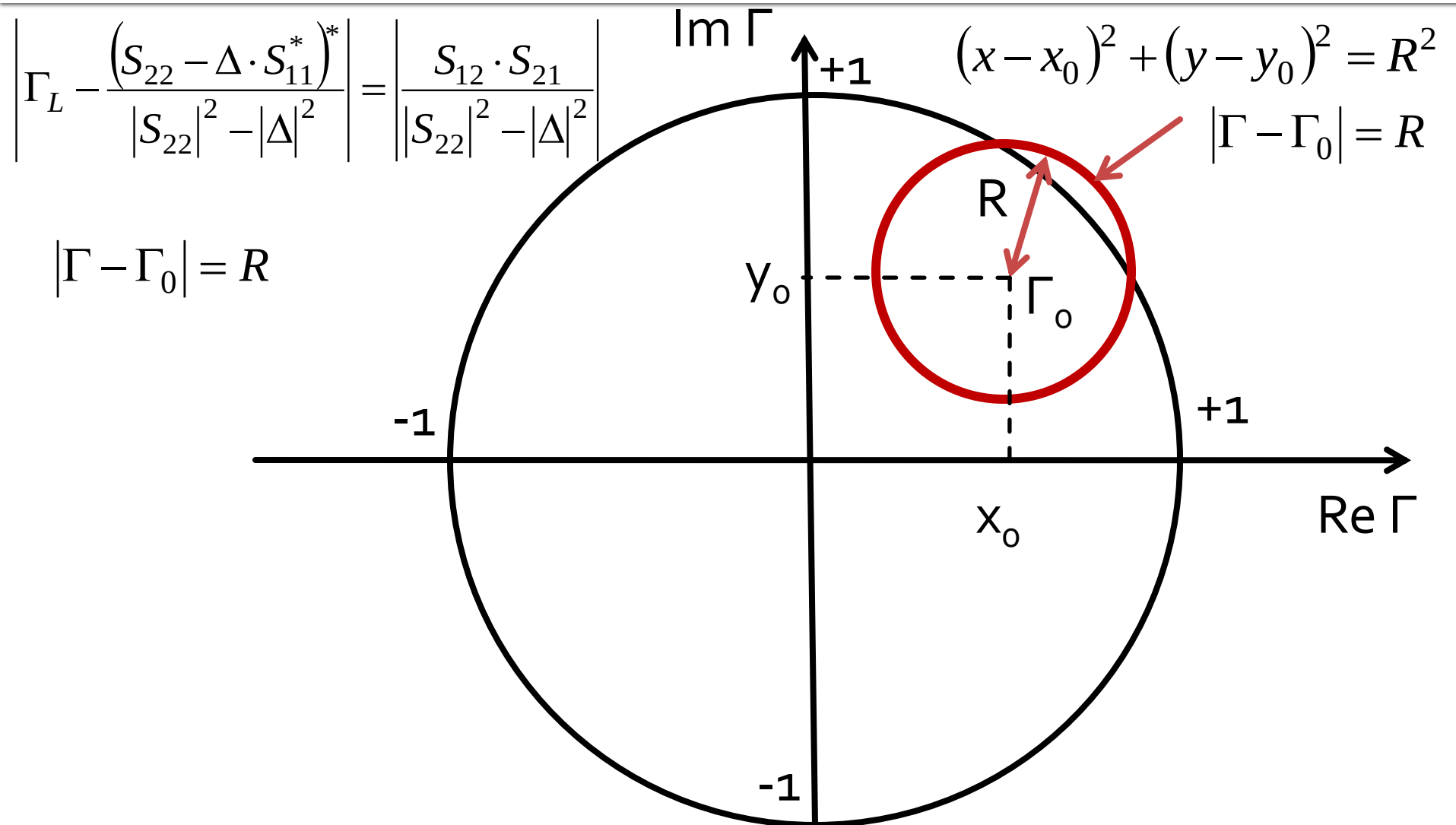

Output stability circle (CSOUT)

$$\left| \Gamma_L - \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12} \cdot S_{21}}{|S_{22}|^2 - |\Delta|^2} \right| \quad |\Gamma_L - C_L| = R_L$$

- We obtain the equation of a circle in the complex plane, which represents the locus of Γ_L for the **limit between stability and instability** ($|\Gamma_{in}| = 1$)
- This circle is the **output stability circle** (Γ_L)

$$C_L = \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \quad R_L = \frac{|S_{12} \cdot S_{21}|}{\left| |S_{22}|^2 - |\Delta|^2 \right|}$$

Input stability circle (CSOUT)



- Similarly
$$\left| \Gamma_{out} \right| = 1 \quad \left| S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S} \right| = 1$$
- We obtain the equation of a circle in the complex plane, which represents the locus of Γ_S for the **limit between stability and instability** ($|\Gamma_{out}| = 1$)
- This circle is the **input stability circle** (Γ_S)

$$C_S = \frac{(S_{11} - \Delta \cdot S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \quad R_S = \frac{|S_{12} \cdot S_{21}|}{\left| |S_{11}|^2 - |\Delta|^2 \right|}$$

Output stability circle (CSOUT)

- The **output stability circle** represents the locus of Γ_L for the **limit between stability and instability** ($|\Gamma_{in}| = 1$)
- The circle divides the complex planes in two areas, the **inside** and the **outside** of the circle
- The two areas will represent the locus of Γ_L for stability ($|\Gamma_{in}| < 1$) / instability ($|\Gamma_{in}| > 1$)

Output stability circle (CSOUT)

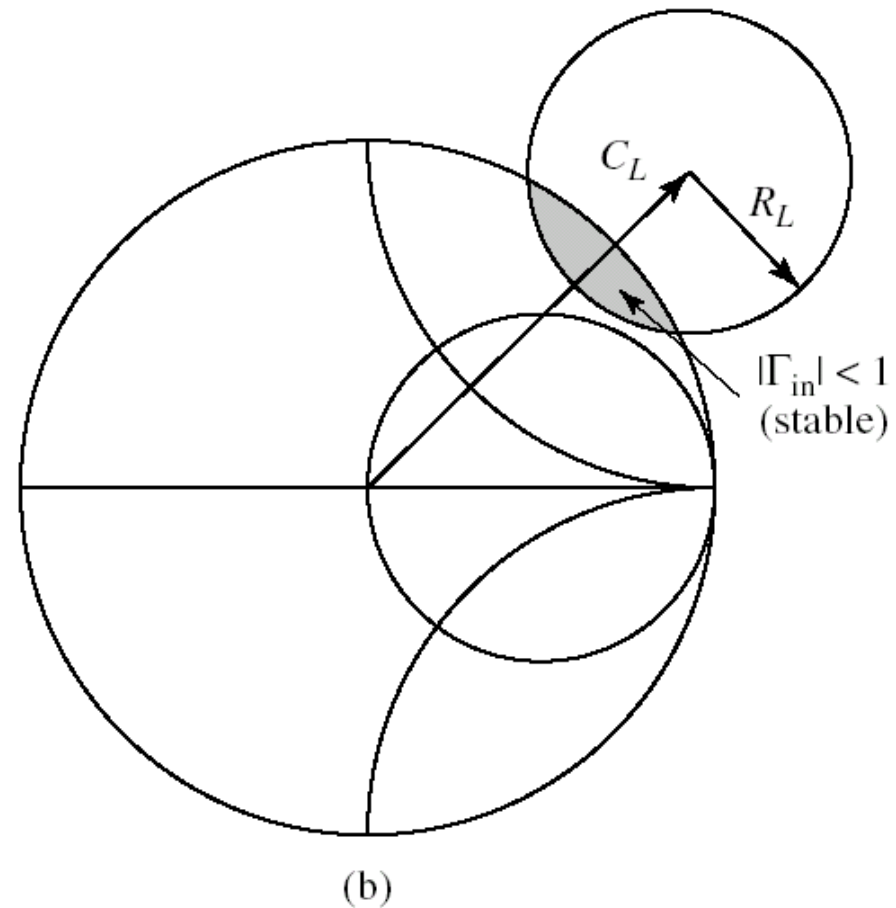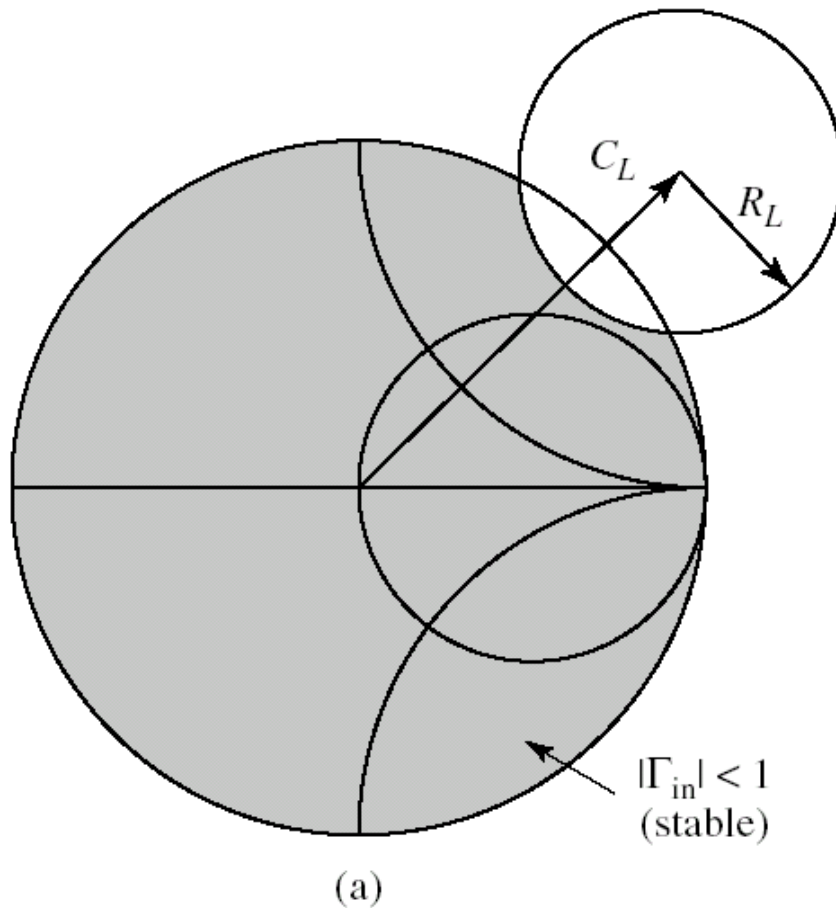

- Two cases possible: (a) stable outside/ (b) stable inside

Output stability circle (CSOUT)

- Identification of the stability / instability regions
 - Center of the Smith Chart in Γ_L complex plane correspond to $\Gamma_L = 0$
 - Input reflection coefficient

$$\Gamma_{in} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \quad \Gamma_{in}|_{\Gamma_L=0} = S_{11} \quad |\Gamma_{in}|_{\Gamma_L=0} = |S_{11}|$$

- A decision can be made based on $|S_{11}|$ value the position of the center of the Smith chart (origin of the complex plane) relative to the circle

Identification of the stability / instability regions

- Output stability circle
 - $|S_{11}| < 1 \rightarrow$ the center of the Smith chart on which Γ_L is represented is a **stable point**, so it's placed in the stability region (most often situation)
 - $|S_{11}| > 1 \rightarrow$ the center of the Smith chart on which Γ_L is represented is a **unstable point**, so it's placed in the instability region
- Input stability circle
 - $|S_{22}| < 1 \rightarrow$ the center of the Smith chart on which Γ_S is represented is a **stable point**, so it's placed in the stability region (most often situation)
 - $|S_{22}| > 1 \rightarrow$ the center of the Smith chart on which Γ_S is represented is a **unstable point**, so it's placed in the instability region

Example

- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.

- @5GHz

- $S_{11} = 0.64 \angle 139^\circ$
- $S_{12} = 0.119 \angle -21^\circ$
- $S_{21} = 3.165 \angle 16^\circ$
- $S_{22} = 0.22 \angle 146^\circ$

IATF-34143
IS-PARAMETERS at Vds=3V Id=20mA. LAST UPDATED 01-29-99

ghz s ma r 50


2.0	0.75	-126	6.306	90	0.088	23	0.26	-120
2.5	0.72	-145	5.438	75	0.095	15	0.25	-140
3.0	0.69	-162	4.762	62	0.102	7	0.23	-156
4.0	0.65	166	3.806	38	0.111	-8	0.22	174
5.0	0.64	139	3.165	16	0.119	-21	0.22	146
6.0	0.65	114	2.706	-5	0.125	-35	0.23	118
7.0	0.66	89	2.326	-27	0.129	-49	0.25	91
8.0	0.69	67	2.017	-47	0.133	-62	0.29	67
9.0	0.72	48	1.758	-66	0.135	-75	0.34	46

IFREQ Fopt GAMMA OPT RN/Zo
IGHZ dB MAG ANG -


2.0	0.19	0.71	66	0.09
2.5	0.23	0.65	83	0.07
3.0	0.29	0.59	102	0.06
4.0	0.42	0.51	138	0.03
5.0	0.54	0.45	174	0.03
6.0	0.67	0.42	-151	0.05
7.0	0.79	0.42	-118	0.10
8.0	0.92	0.45	-88	0.18
9.0	1.04	0.51	-63	0.30
10.0	1.16	0.61	-43	0.46

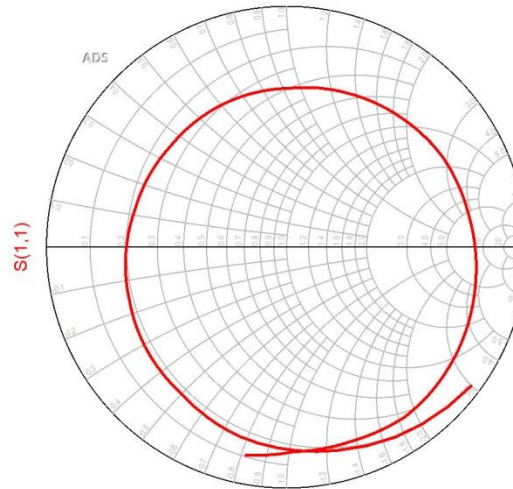Example


- ATF-34143
- at
 - $V_{ds}=3V$
 - $I_d=20mA$.




freq (500.0MHz to 18.00GHz)

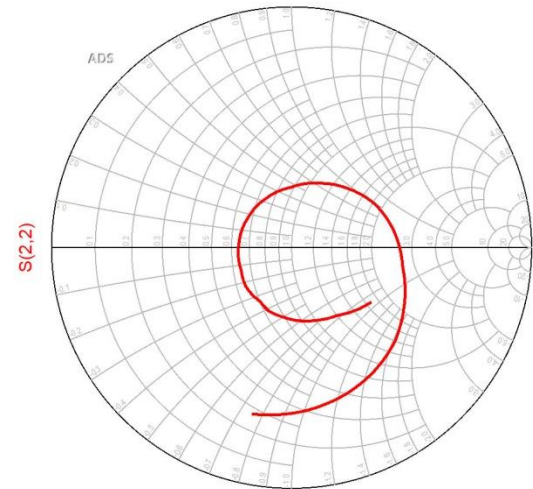

freq (500.0MHz to 18.00GHz)

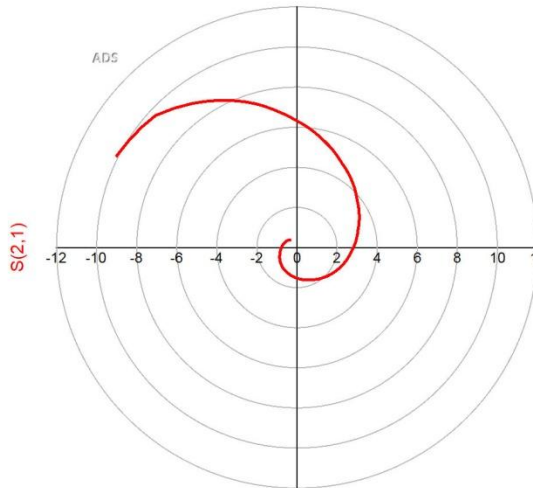

freq (500.0MHz to 18.00GHz)

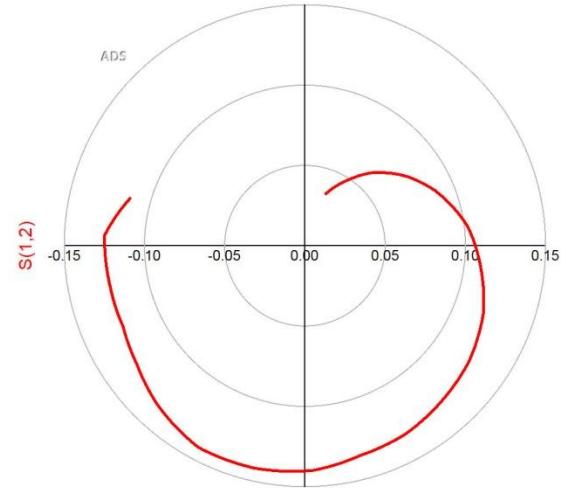

freq (500.0MHz to 18.00GHz)

Solution + region identification

- S parameters

- $S_{11} = -0.483 + 0.42 \cdot j$

- $S_{12} = 0.111 - 0.043 \cdot j$

- $S_{21} = 3.042 + 0.872 \cdot j$

- $S_{22} = -0.182 + 0.123 \cdot j$

$$C_L = \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} = 3.931 - 0.897 \cdot j$$

$$|C_L| = 4.032$$

$$R_L = \frac{|S_{12} \cdot S_{21}|}{||S_{22}|^2 - |\Delta|^2|} = 4.891$$

- $|S_{22}| < 1$

- $|C_L| < R_L, o \in \text{CSOUT}$

- The center of the Smith chart is placed inside the output stability circle ($o \in \text{CSOUT}$) and is a stable point

- the inside of the output stability circle – stability region
 - the outside of the output stability circle – instability region

Solution + region identification

- S parameters

- $S_{11} = -0.483 + 0.42 \cdot j$
- $S_{12} = 0.111 - 0.043 \cdot j$
- $S_{21} = 3.042 + 0.872 \cdot j$
- $S_{22} = -0.182 + 0.123 \cdot j$

$$C_S = \frac{(S_{11} - \Delta \cdot S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} = -1.871 - 1.265 \cdot j$$

$$|C_S| = 2.259$$

$$R_S = \frac{|S_{12} \cdot S_{21}|}{||S_{11}|^2 - |\Delta|^2|} = 1.325$$


- $|S_{11}| < 1$

- $|C_S| > R_S, 0 \notin \text{CSIN}$

- The center of the Smith chart is placed outside the input stability circle ($0 \notin \text{CSIN}$) and is a stable point


- the outside of the input stability circle – stability region
- the inside of the input stability circle – instability region

ADS

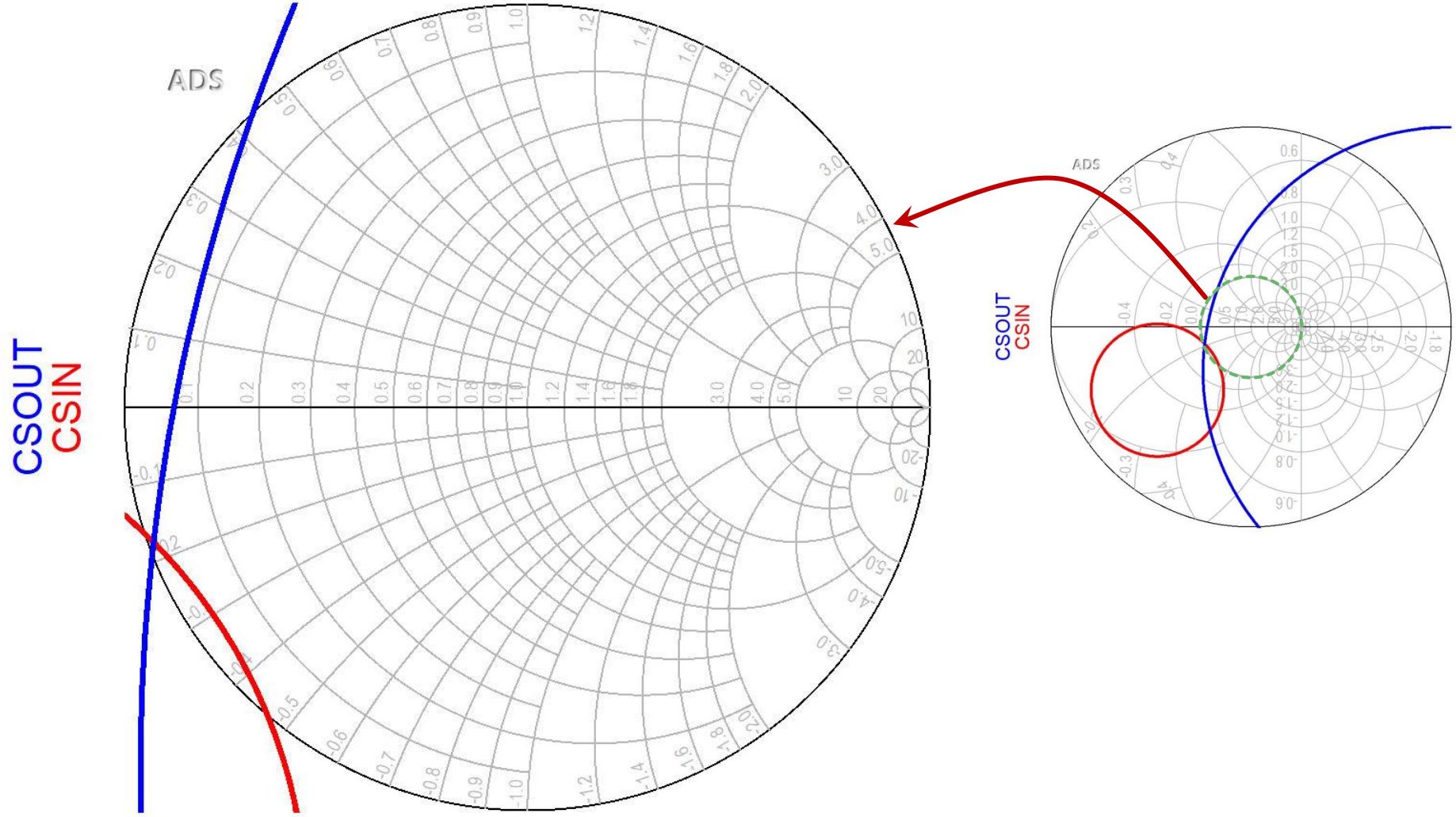



3D representation of $|\Gamma_{in}|$, $|\Gamma_{out}|$

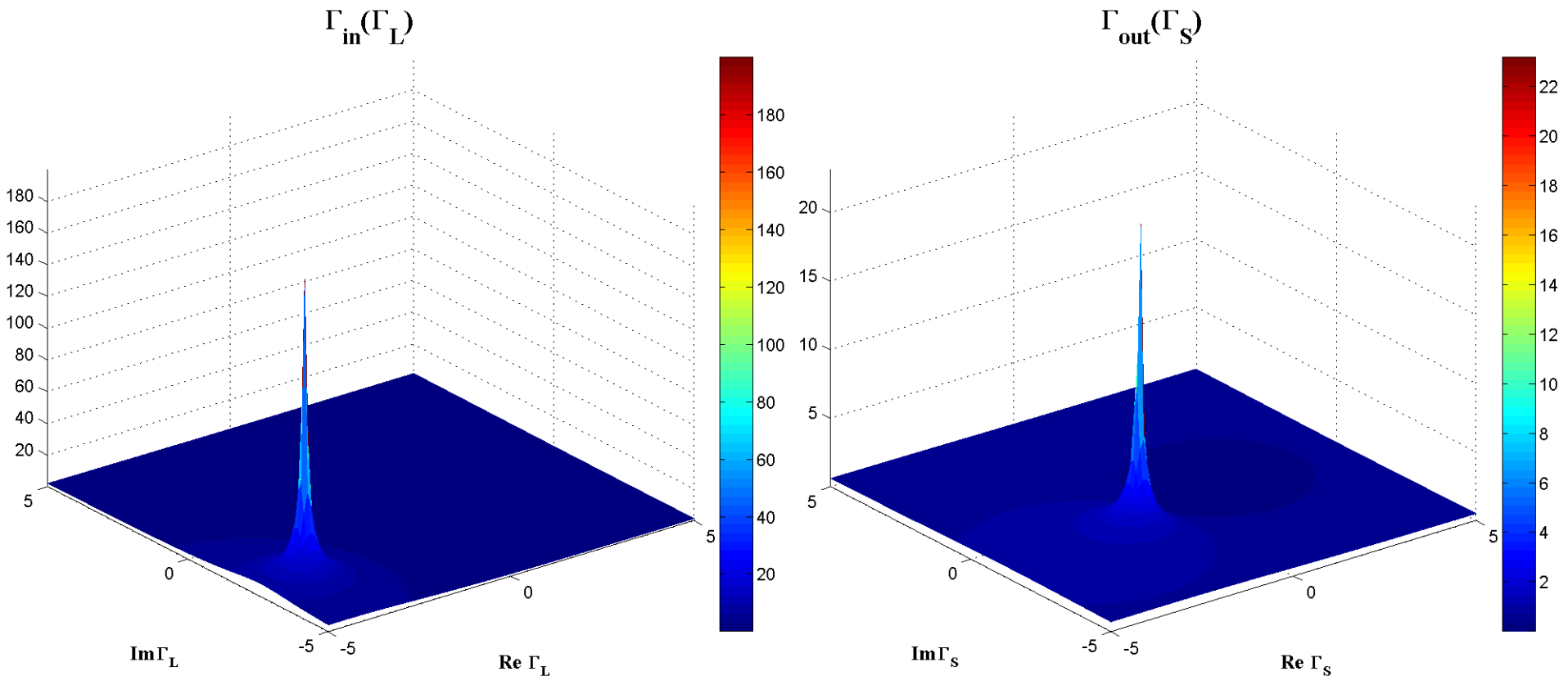- High variations -> we change to z logarithmic scale





3D representation of $|\Gamma_{in}|$, $|\Gamma_{out}|$

■ $\log_{10}|\Gamma_{in}|, \log_{10}|\Gamma_{out}|$

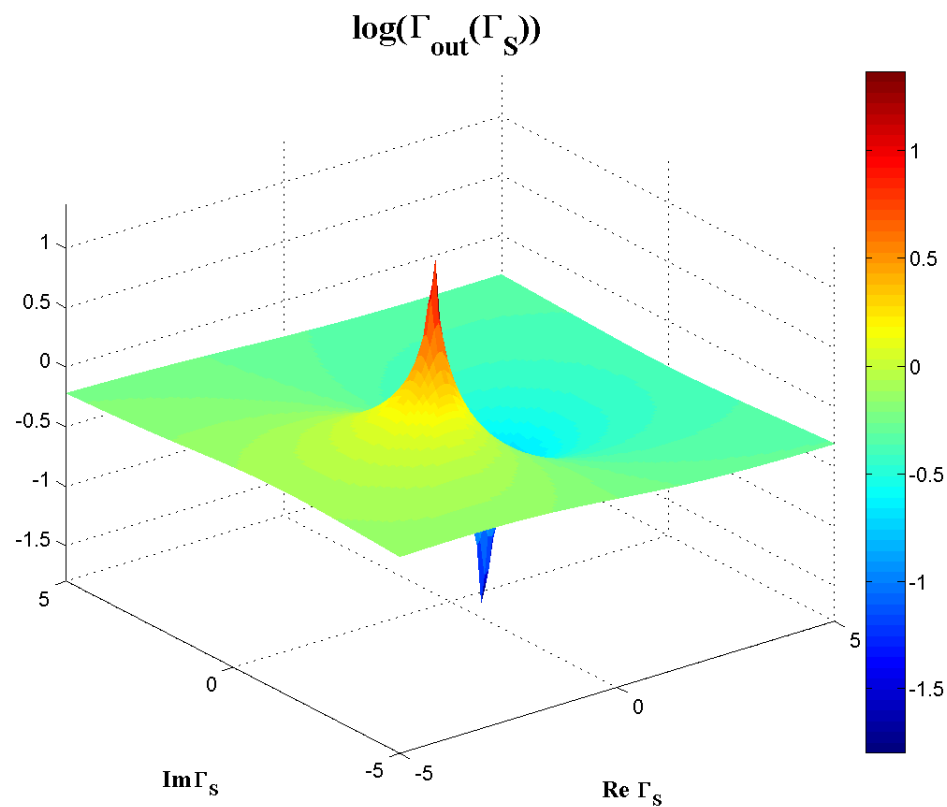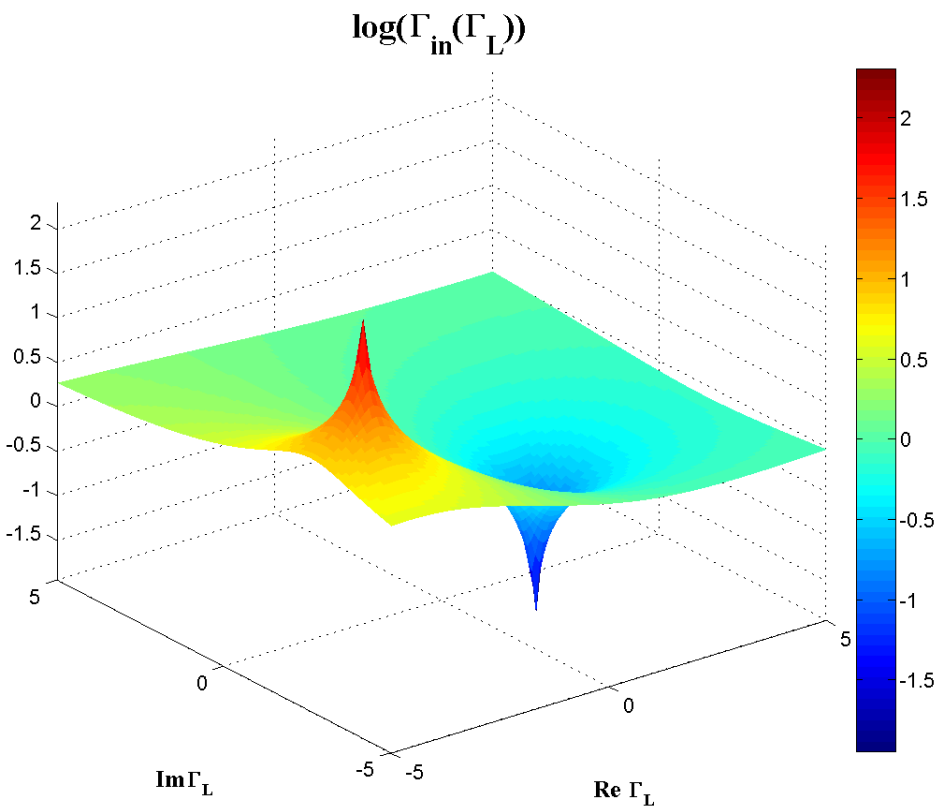


3D representation of $|\Gamma_{in}|$, $|\Gamma_{out}|$, $|\Gamma|=1$


- $|\Gamma| = 1 \rightarrow \log_{10}|\Gamma| = 0$, the intersection with the plane $z = 0$ is a circle

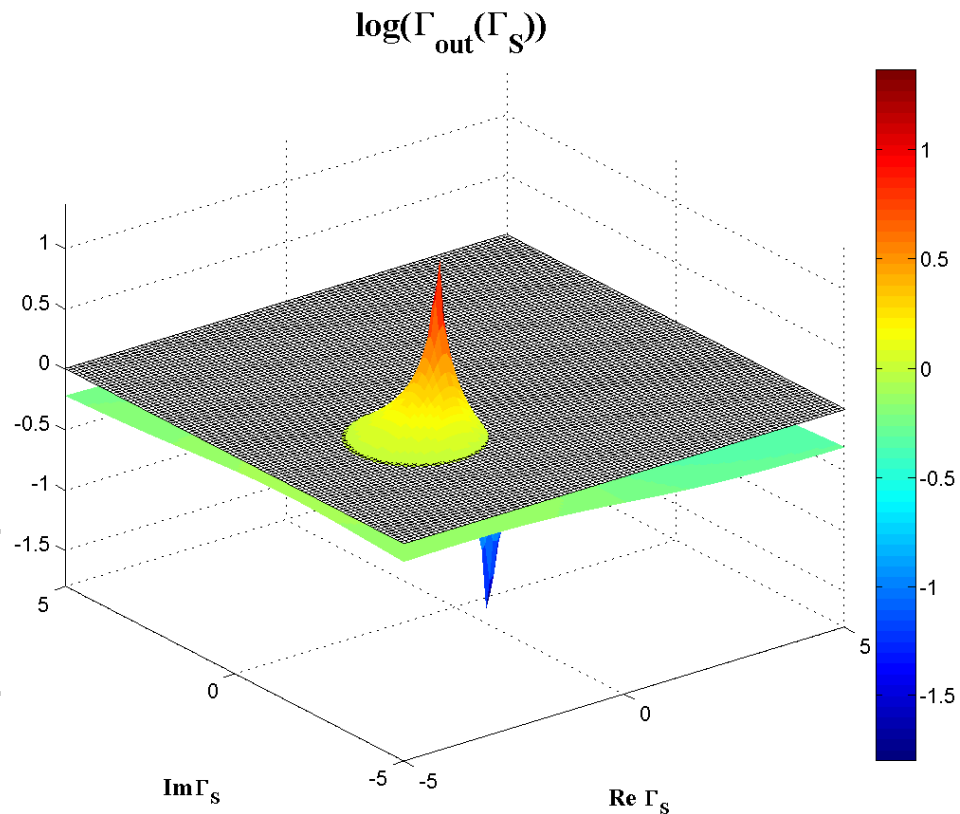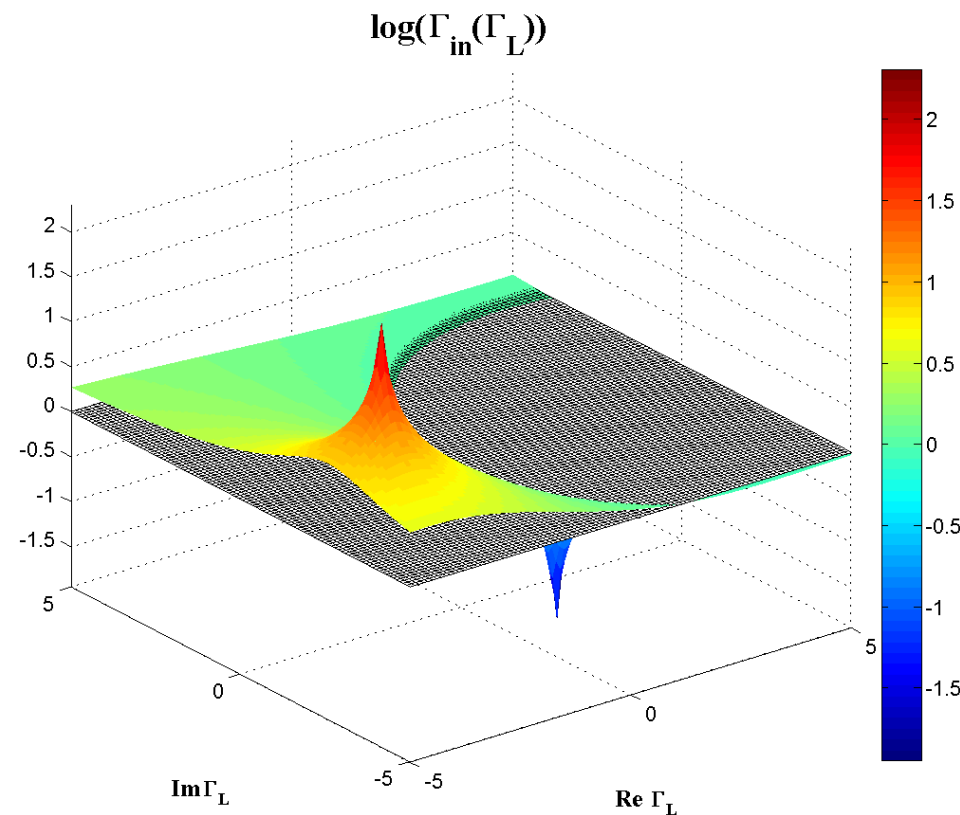

Contour map/lines

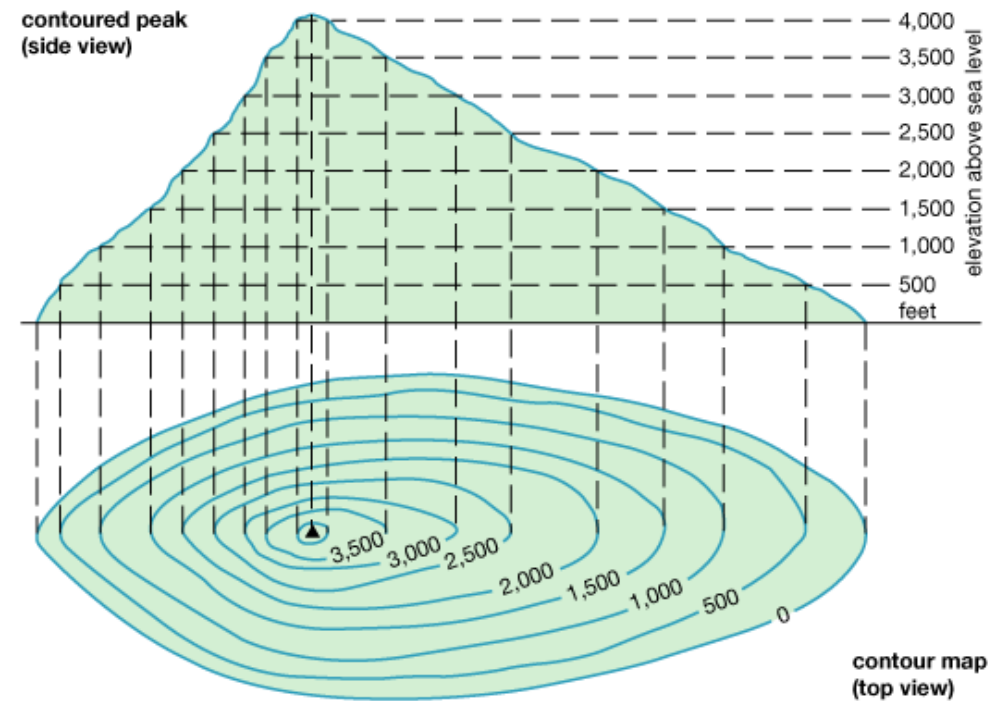


© 2011 Encyclopædia Britannica, Inc.

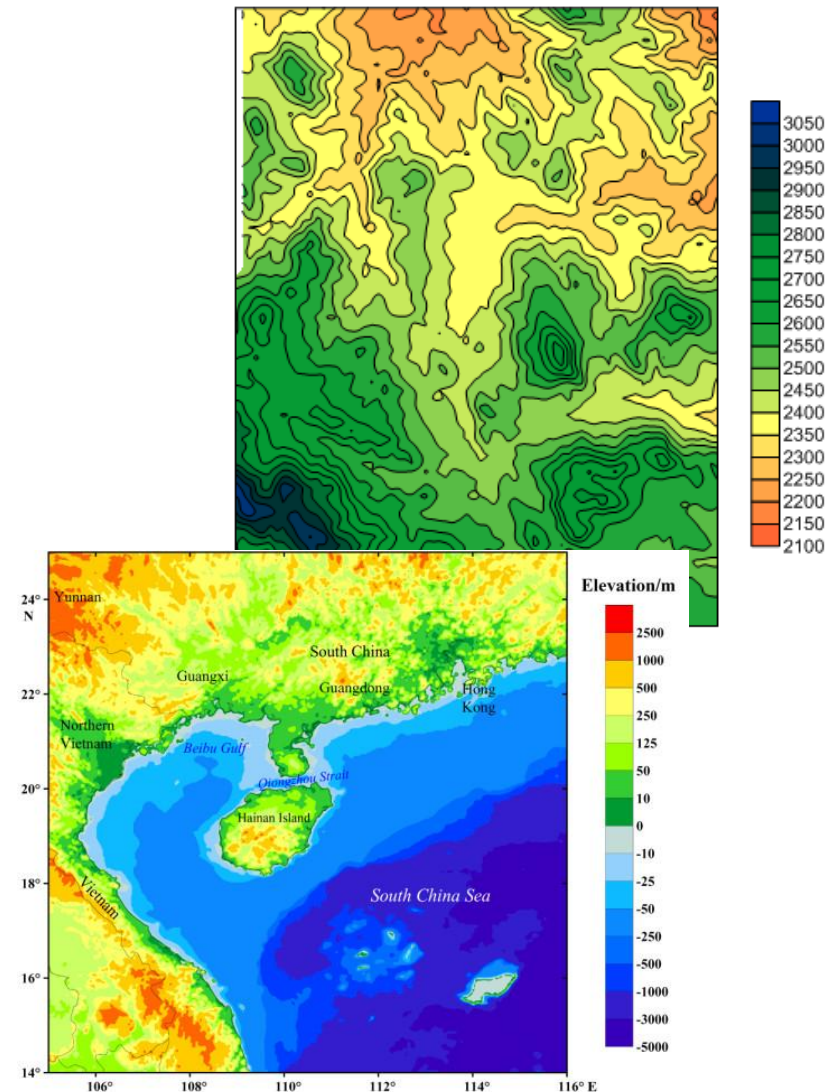

Contour lines of $\log_{10}|\Gamma_{in}|$


- $\log_{10}|\Gamma_{in}| = 0, \Gamma_L, \text{CSOUT}$

$$\log_{10}|\Gamma_{in}| = 0, \\ |\Gamma_{in}| = 1$$



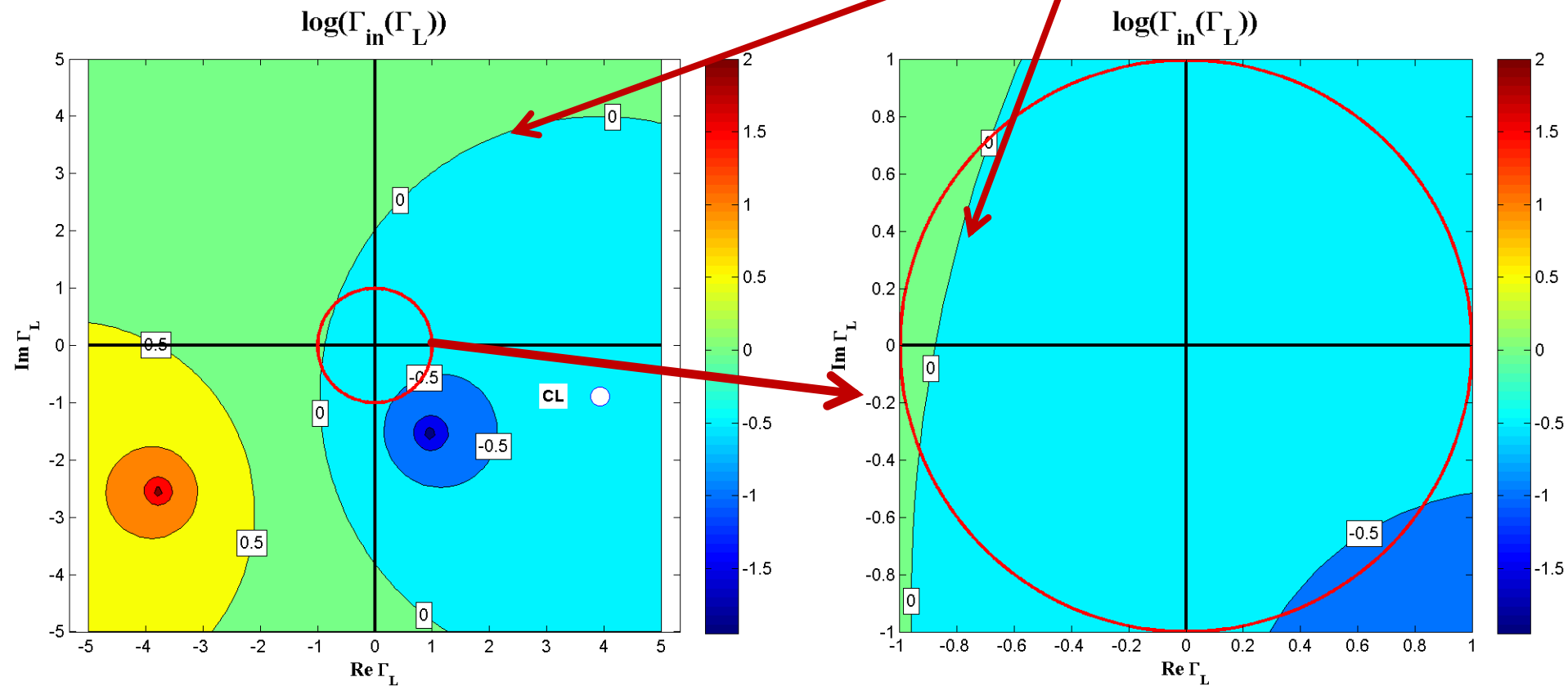


Contour lines of $\log_{10}|\Gamma_{\text{out}}|$


- $\log_{10}|\Gamma_{\text{out}}| = 0, \Gamma_S, \text{CSIN}$

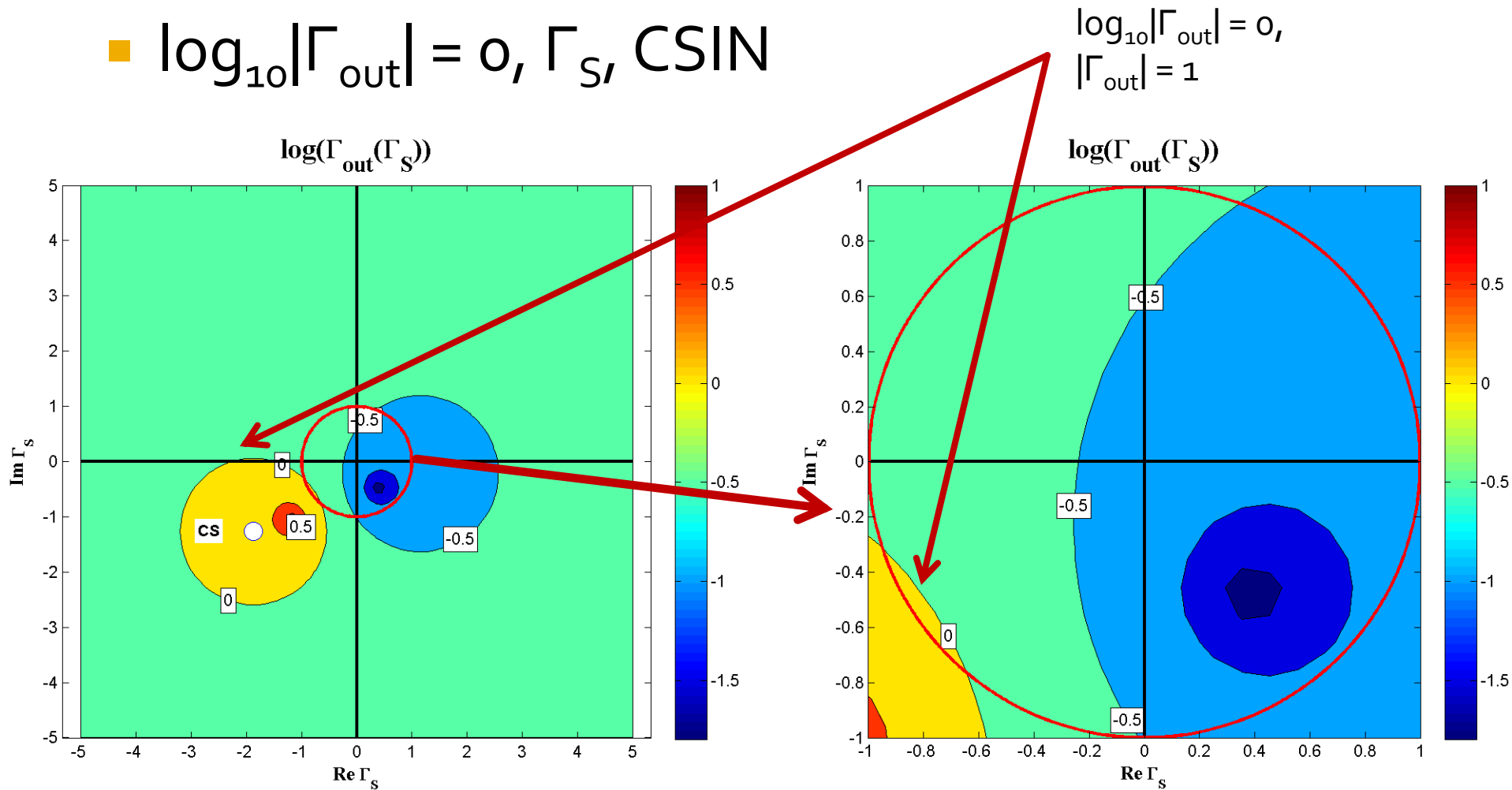


CSIN, CSOUT

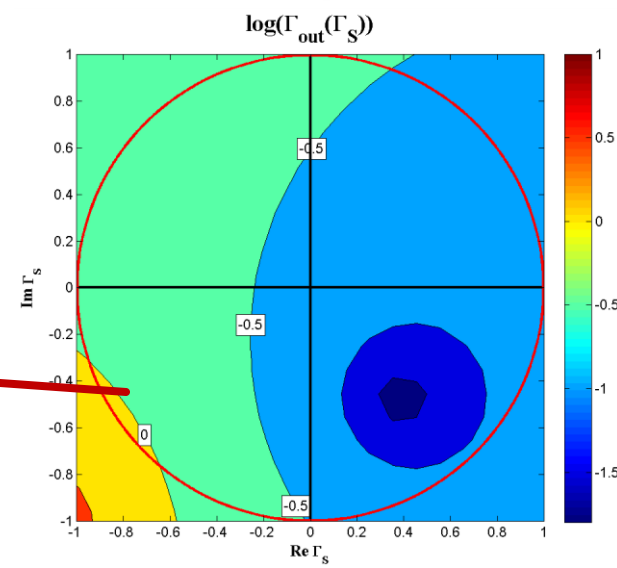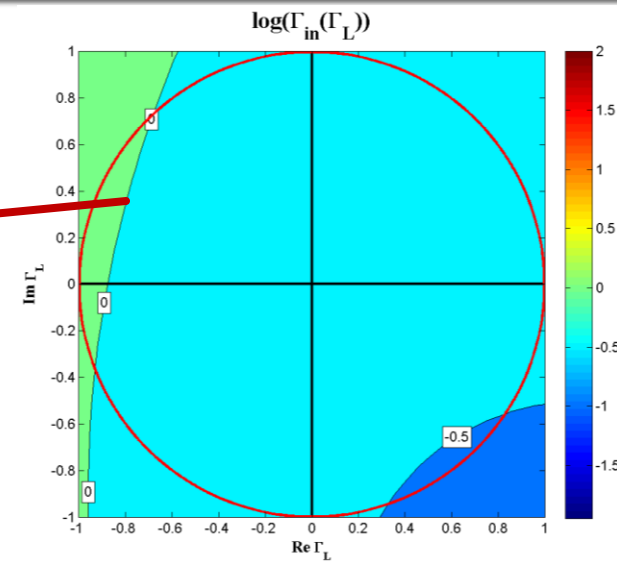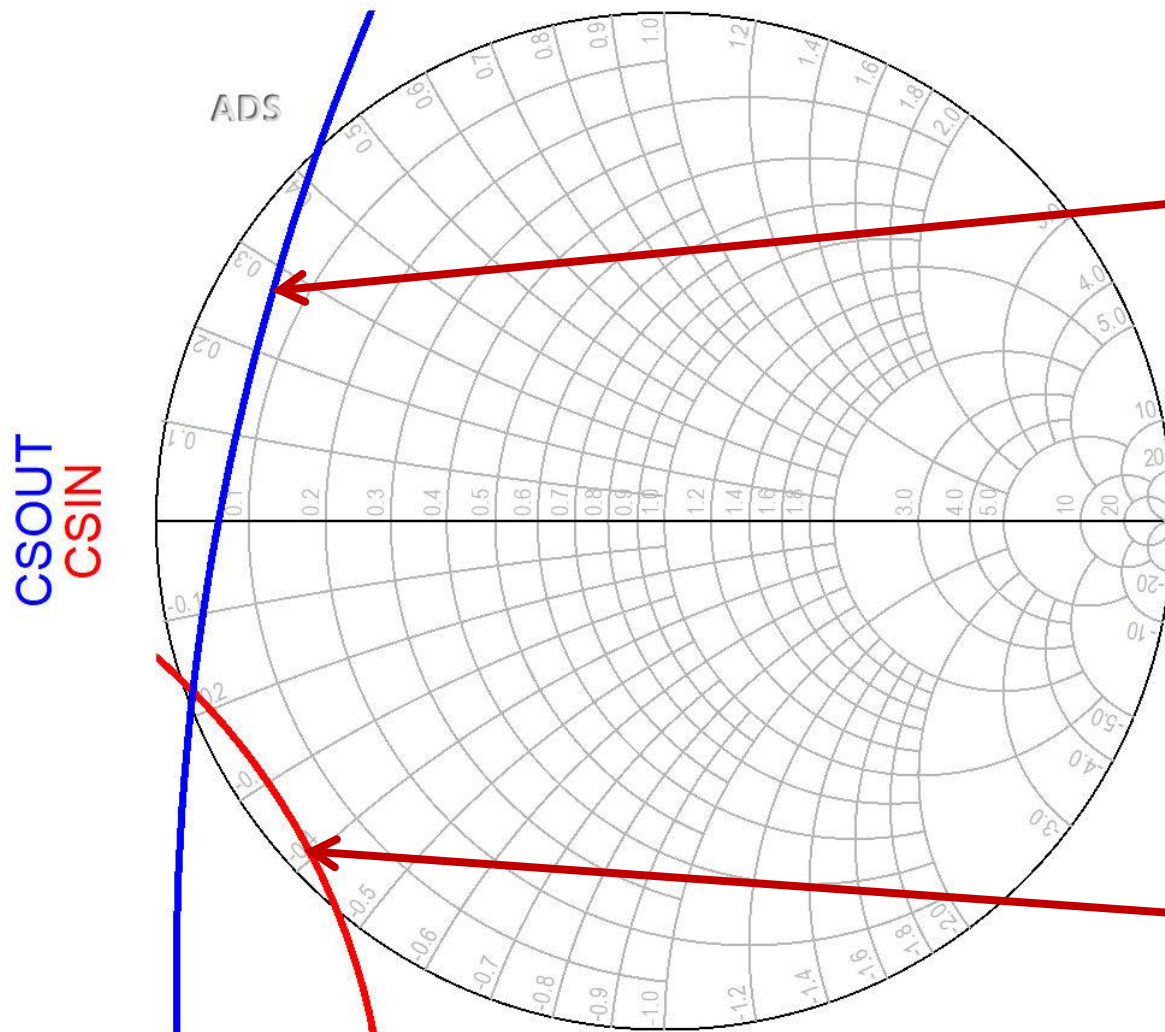


Several possible positioning

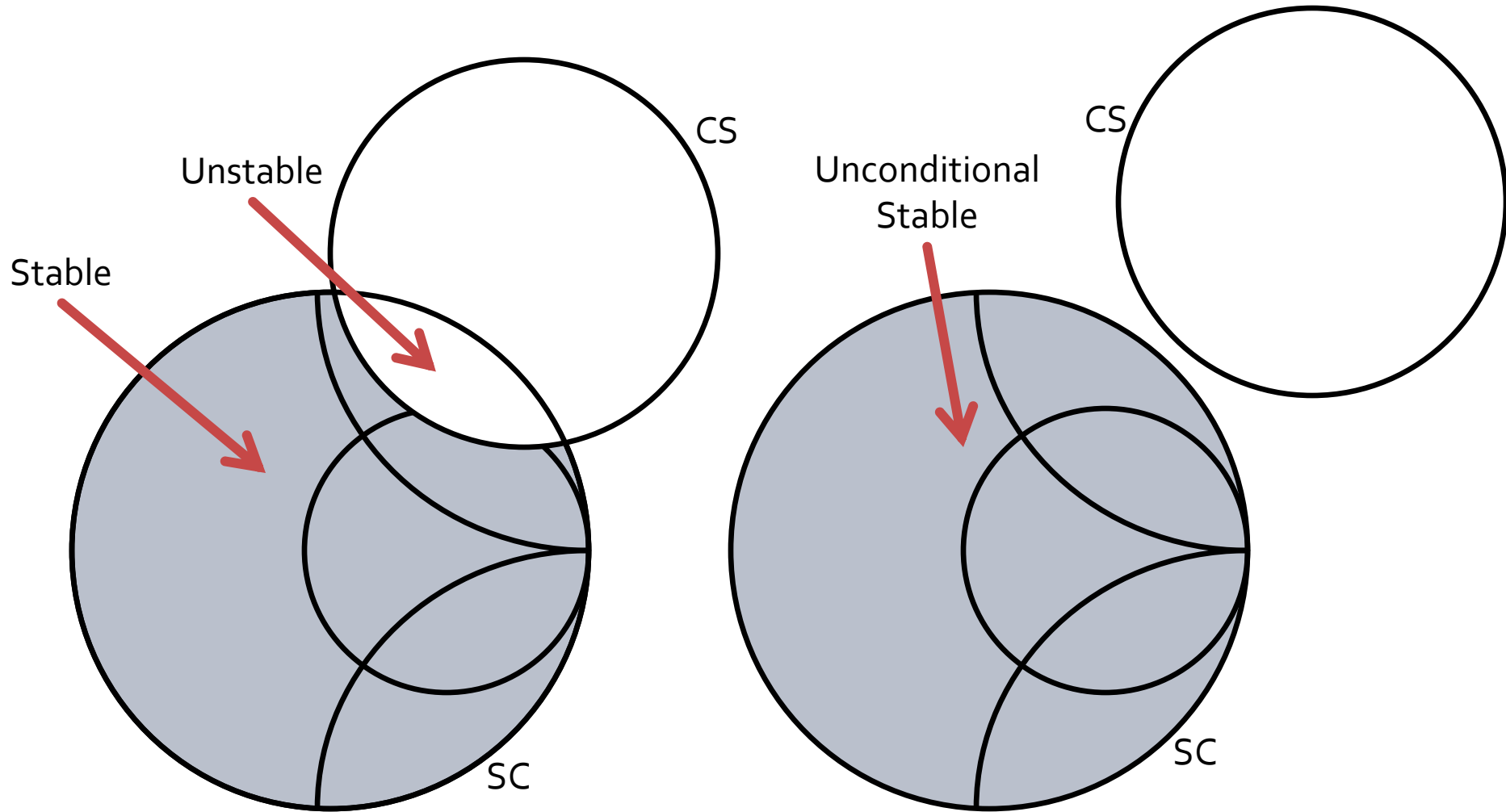



Several possible positioning

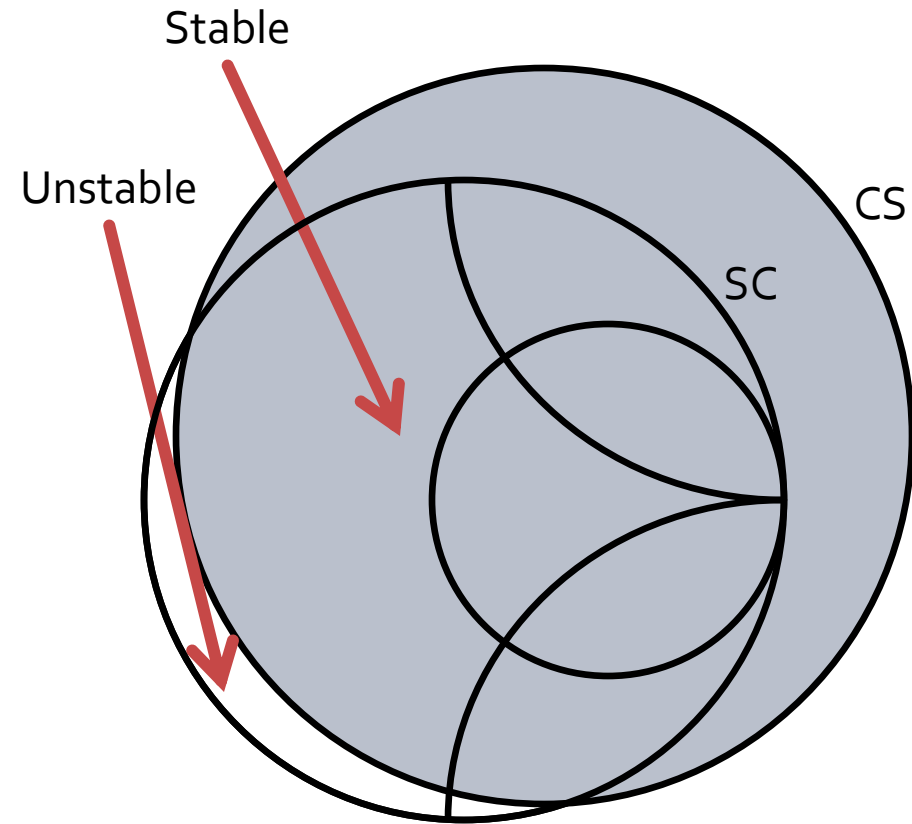

Unconditional
Stable

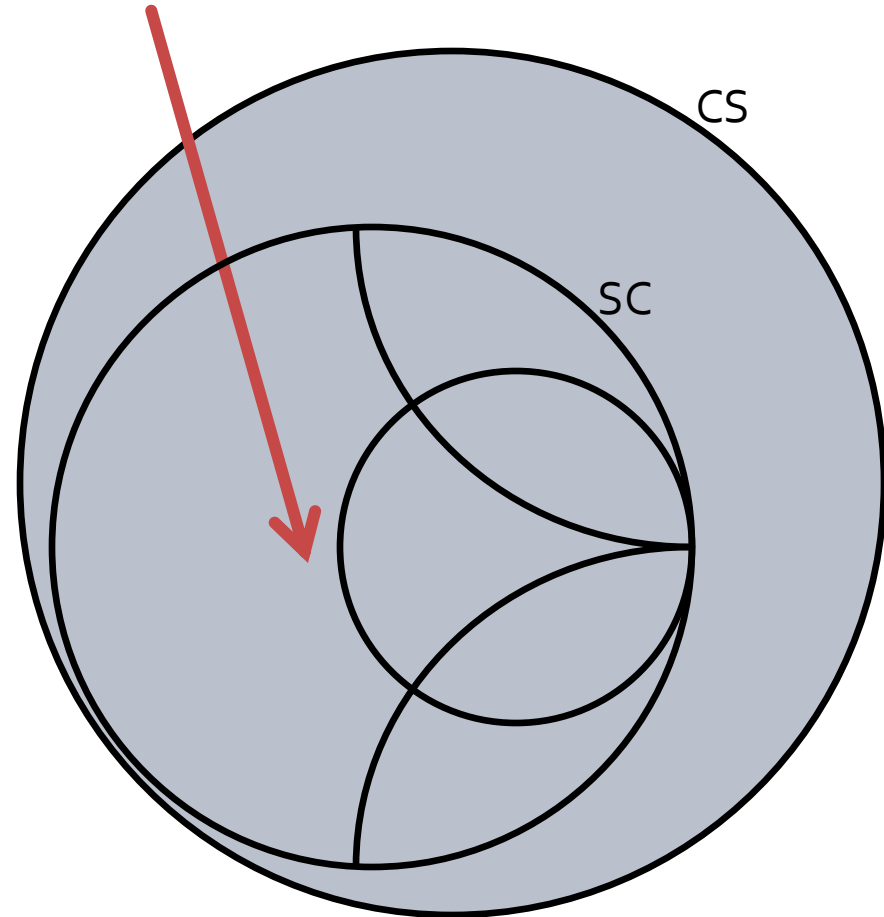

(Quite) Rare positioning

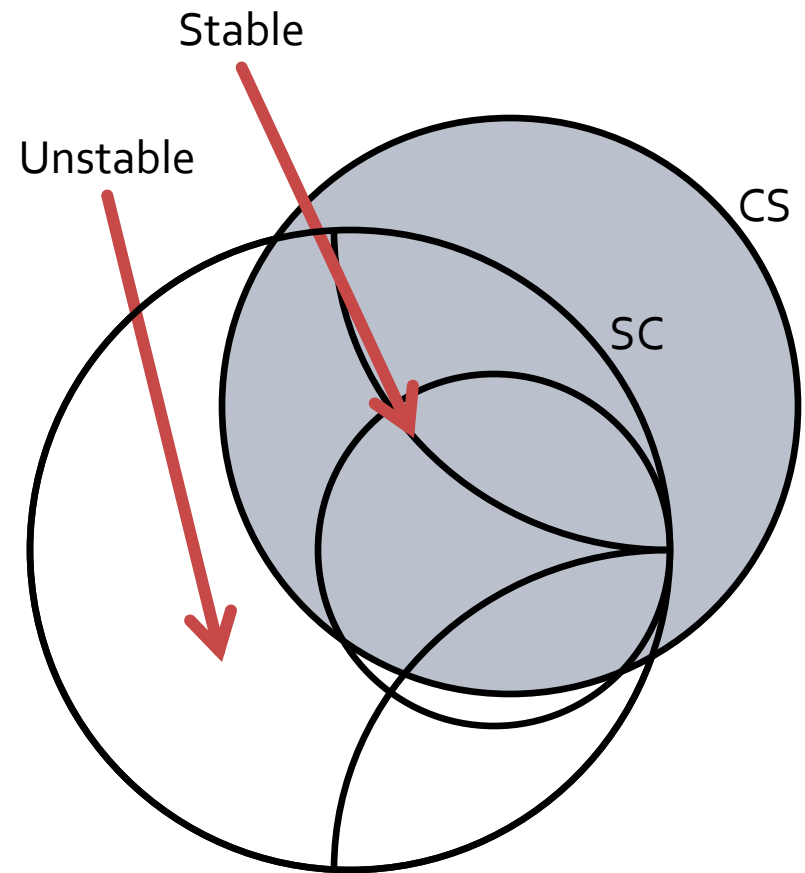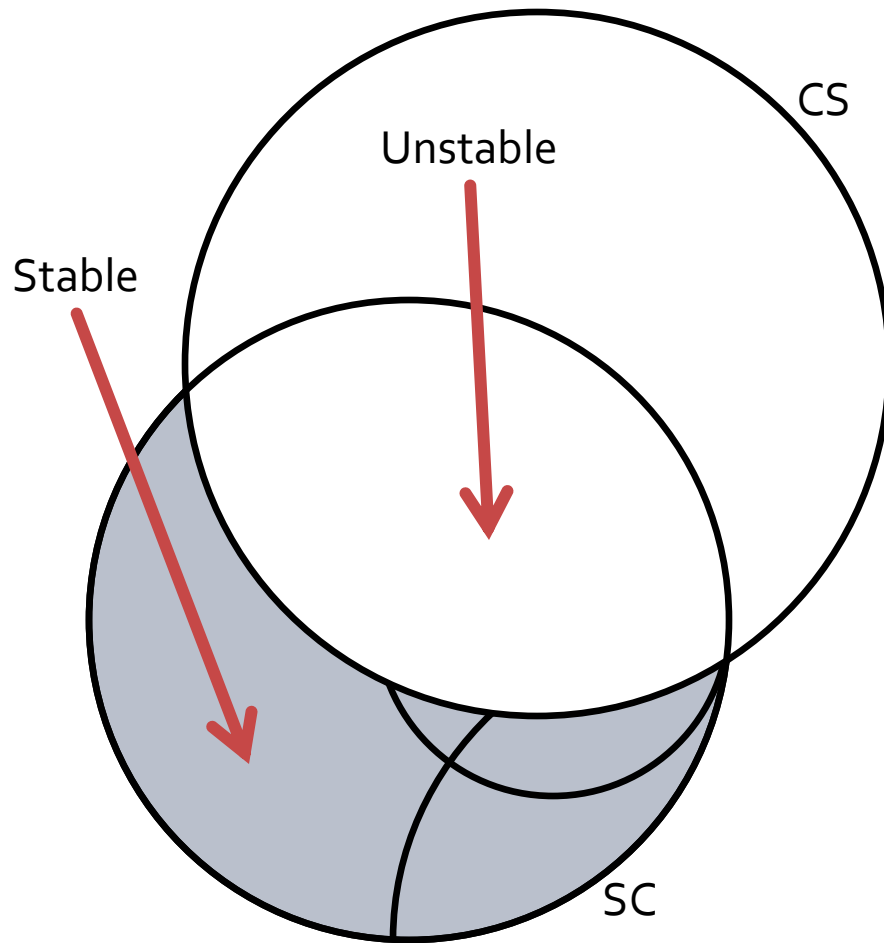

Stability

- **Unconditional stability:** the circuit is unconditionally stable if $|\Gamma_{in}| < 1$ and $|\Gamma_{out}| < 1$ for **any** passive impedance of the load/source
- **Conditional stability:** the circuit is conditionally stable if $|\Gamma_{in}| < 1$ and $|\Gamma_{out}| < 1$ only for **some** passive impedance of the load/source



Unconditional stability

- The two-port is unconditionally stable if:
 - The stability circle is disjoint with the Smith Chart (exterior to the Chart) and the stable region is outside the circle
 - The stability circle encloses the entire Smith Chart and the stable region is inside the circle
- One mandatory condition for unconditional stability is $|S_{11}| < 1$ (CSOUT) or $|S_{22}| < 1$ (CSIN) – if in at least one point the two-port is not stable then it cannot be unconditionally stable
- Mathematically :
$$\left\{ \begin{array}{l} \left| |C_L| - R_L \right| > 1 \\ |S_{11}| < 1 \end{array} \right. \quad \left\{ \begin{array}{l} \left| |C_S| - R_S \right| > 1 \\ |S_{22}| < 1 \end{array} \right.$$

Tests for Unconditional Stability

- Useful for wide frequency range analysis
- It is not enough to check the stability only at the operating frequencies
 - we must obtain stable operation for chosen Γ_L and Γ_S at **any** frequency

Circles in wide frequency range

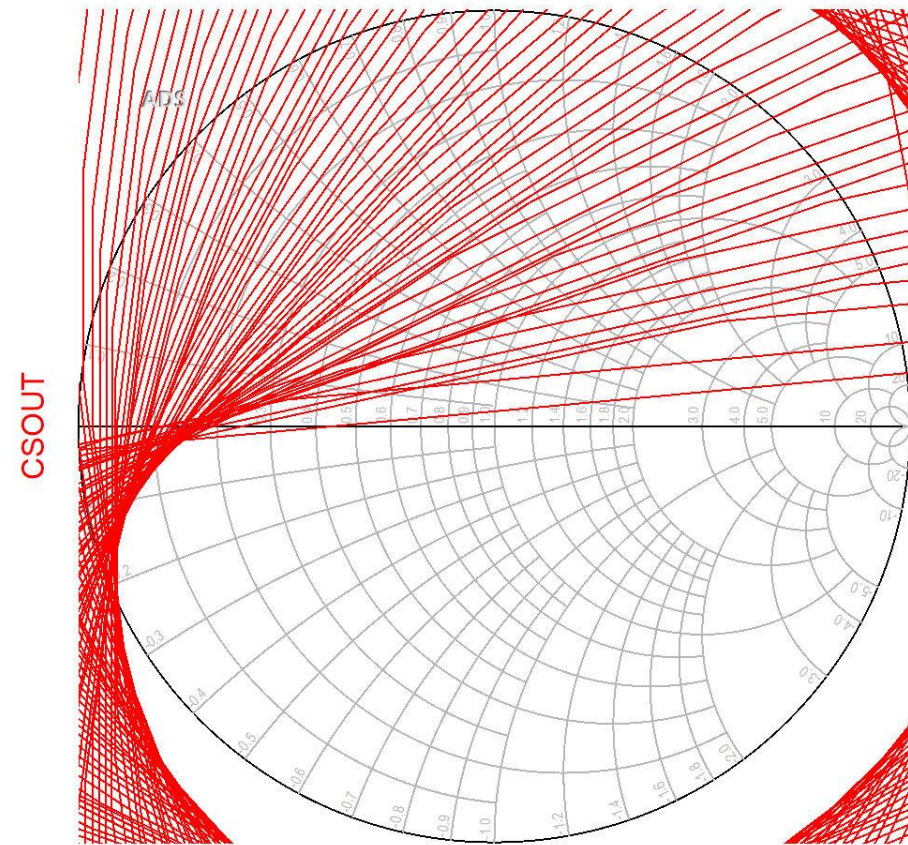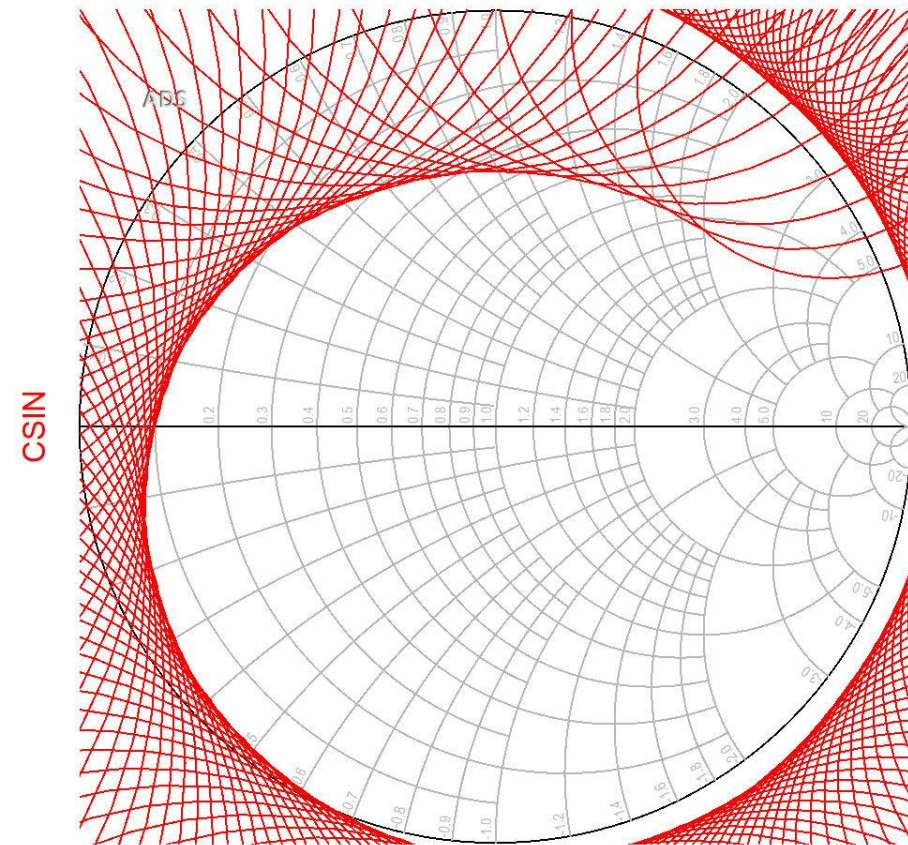

Rollet's condition

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 \cdot |S_{12} \cdot S_{21}|}$$

$$\Delta = S_{11} \cdot S_{22} - S_{12} \cdot S_{21}$$

- The two-port is **unconditionally stable** if:
- two conditions are simultaneously satisfied:
 - $K > 1$
 - $|\Delta| < 1$
- together with the implicit conditions:
 - $|S_{11}| < 1$
 - $|S_{22}| < 1$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 \cdot |S_{12} \cdot S_{21}|} > 1$$

$$|\Delta| = |S_{11} \cdot S_{22} - S_{12} \cdot S_{21}| < 1$$

μ Criterion

- Rollet's condition cannot be used to compare the relative stability of two or more devices because it involves constraints on two separate parameters, K and Δ

$$\mu = \frac{1 - |S_{11}|^2}{|S_{22} - \Delta \cdot S_{11}^*| + |S_{12} \cdot S_{21}|} > 1$$

- The two-port is **unconditionally stable** if:
 - $\mu > 1$
- together with the implicit conditions:
 - $|S_{11}| < 1$
 - $|S_{22}| < 1$
- In addition, it can be said that larger values of μ imply greater stability
 - μ is the distance from the center of the Smith Chart to the closest output stability circle

μ' Criterion


- Dual parameter to μ , determined in relation to the input stability circles

$$\mu' = \frac{1 - |S_{22}|^2}{|S_{11} - \Delta \cdot S_{22}^*| + |S_{12} \cdot S_{21}|} > 1$$

- The two-port is **unconditionally stable** if:
 - $\mu' > 1$
- together with the implicit conditions:
 - $|S_{11}| < 1$
 - $|S_{22}| < 1$
- In addition, it can be said that larger values of μ' imply greater stability
 - μ' is the distance from the center of the Smith Chart to the closest input stability circle


Rollet's condition

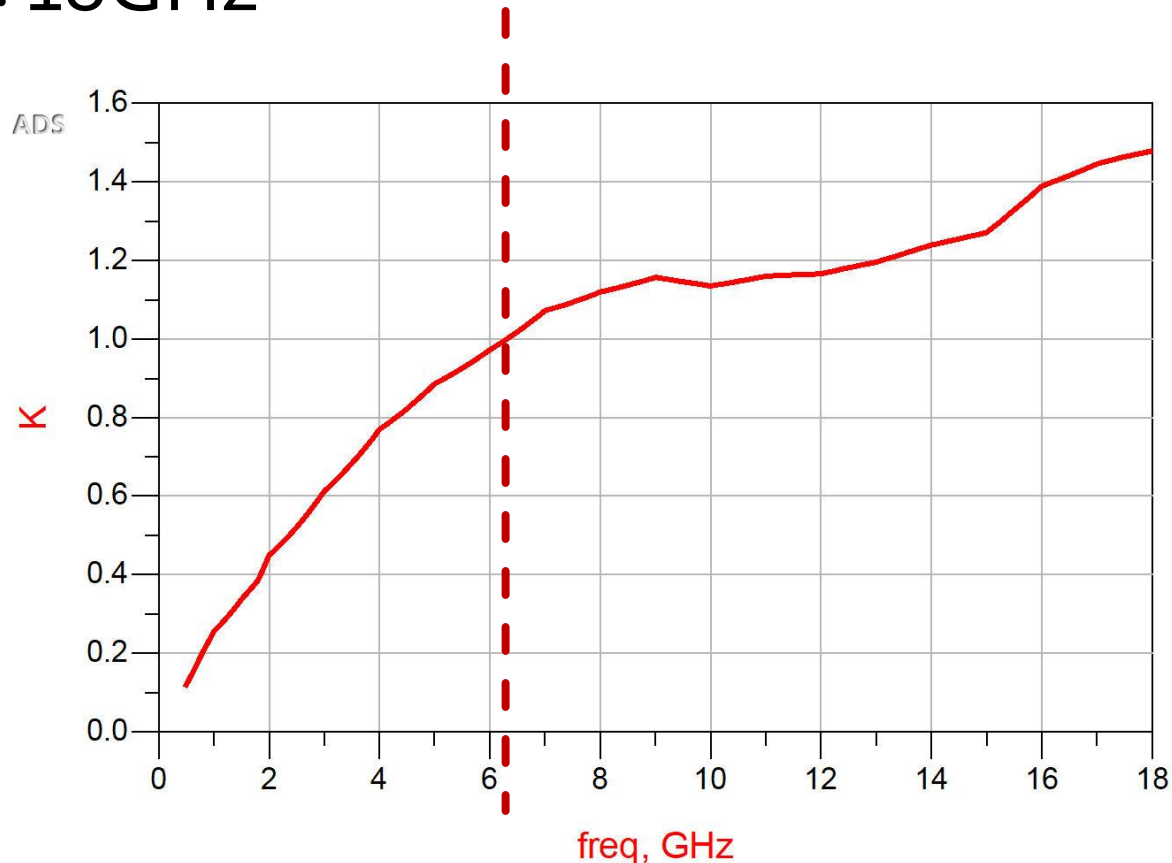- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz




μ Criterion

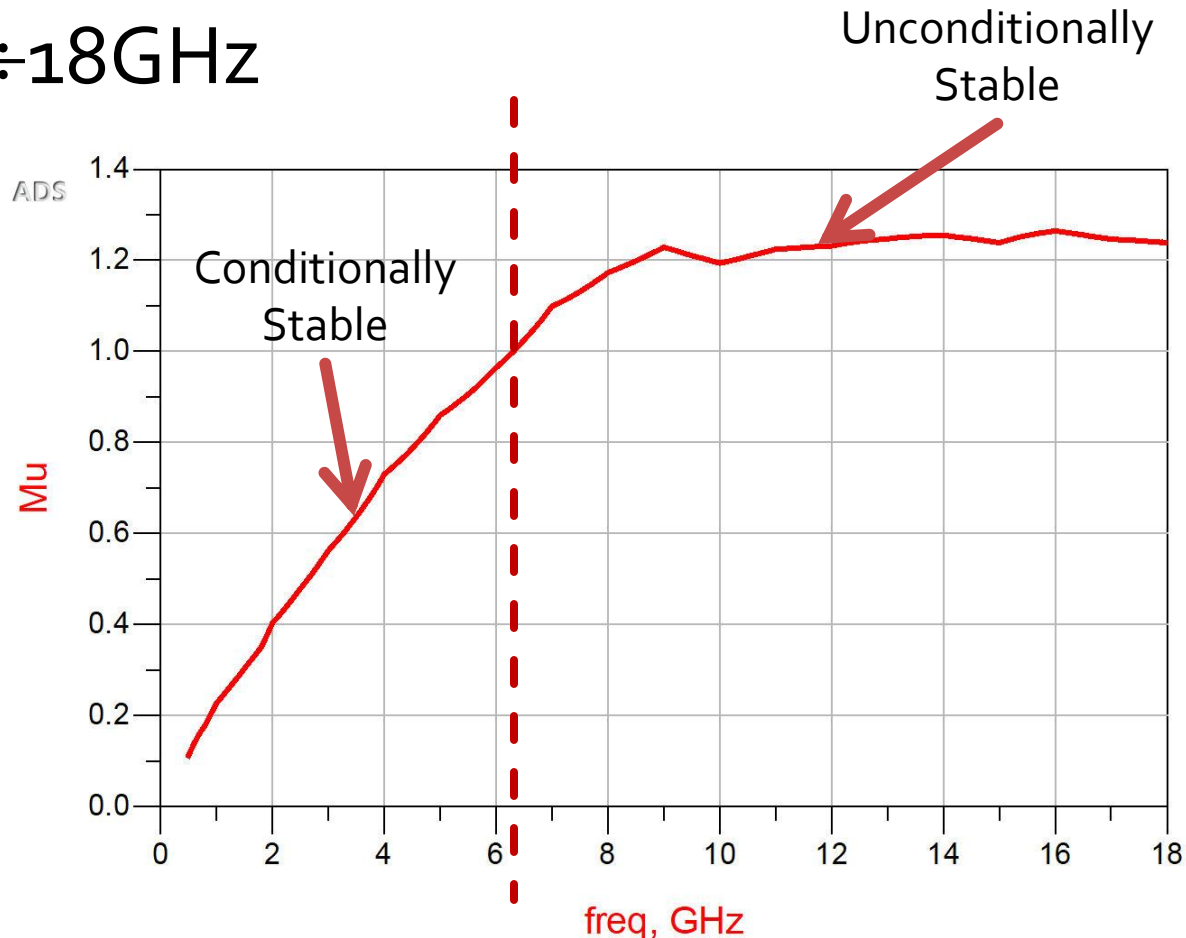- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz





μ' Criterion

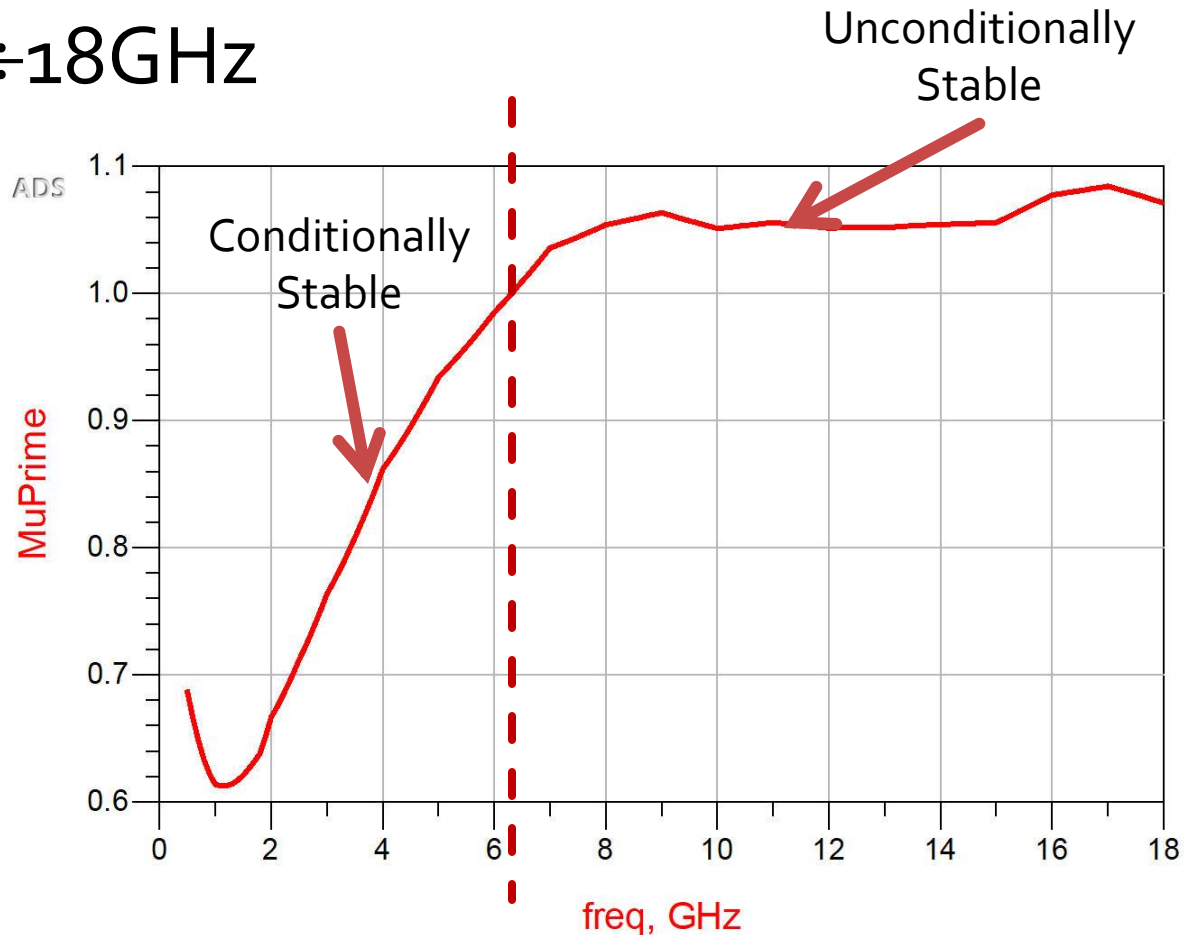- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz



Stability

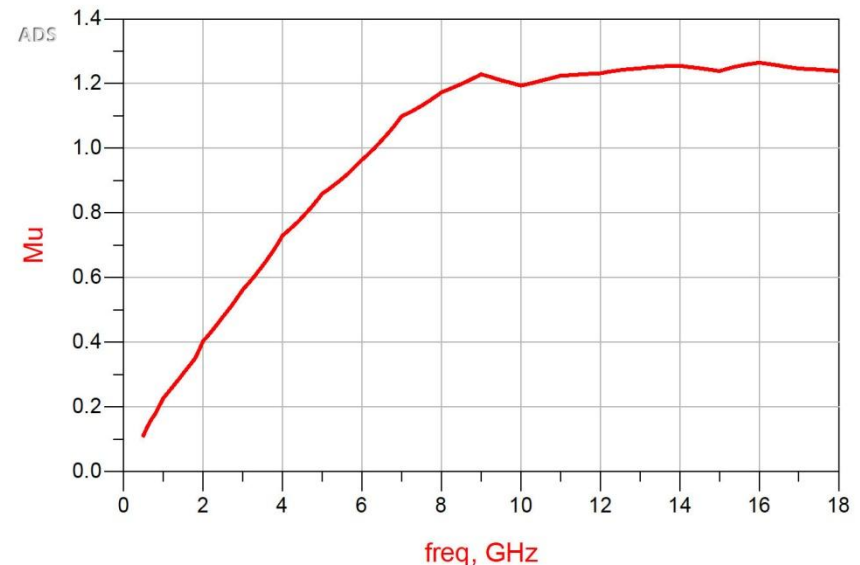
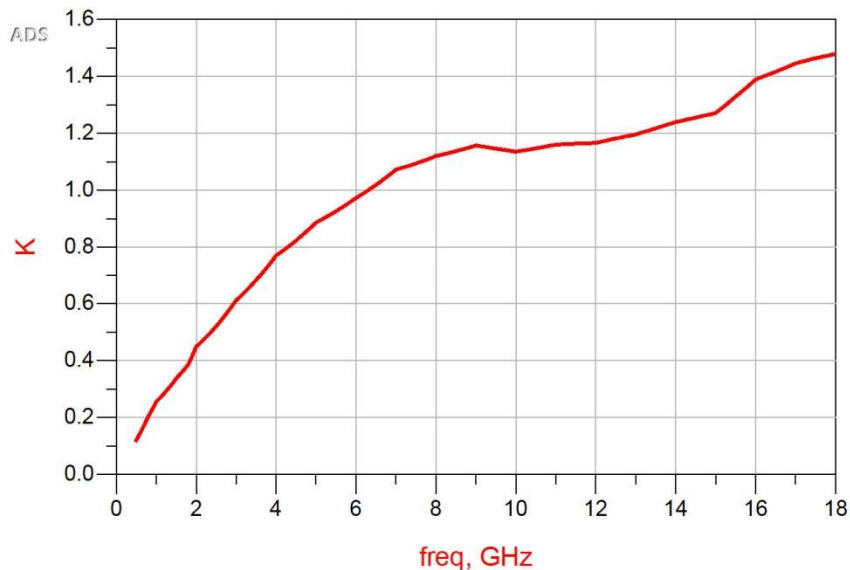
- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz
- unconditionally stable for $f > 6.31GHz$



Stabilization of two-port


- Unconditional stability in a wide frequency range has some important advantages
 - Ex: We can use ATF 34143 to design a (conditionally) stable amplifier at 5GHz, but this design is useless if the amplifier oscillates at 500MHz ($\mu \approx 0.1$)
- **The minimal requirement** when working with conditionally stable devices is to **check stability** at several frequencies over the operating bandwidth and outside the bandwidth
- Unconditional stability can be forced by inserting series/shunt resistors at two-port's input/output (with loss of gain!)

Input series resistor

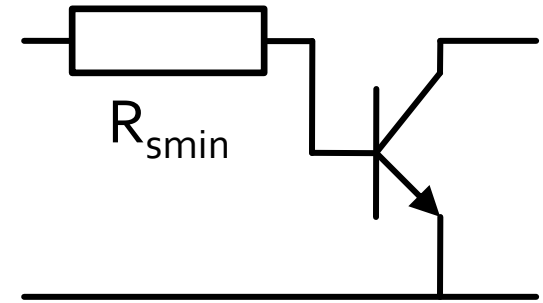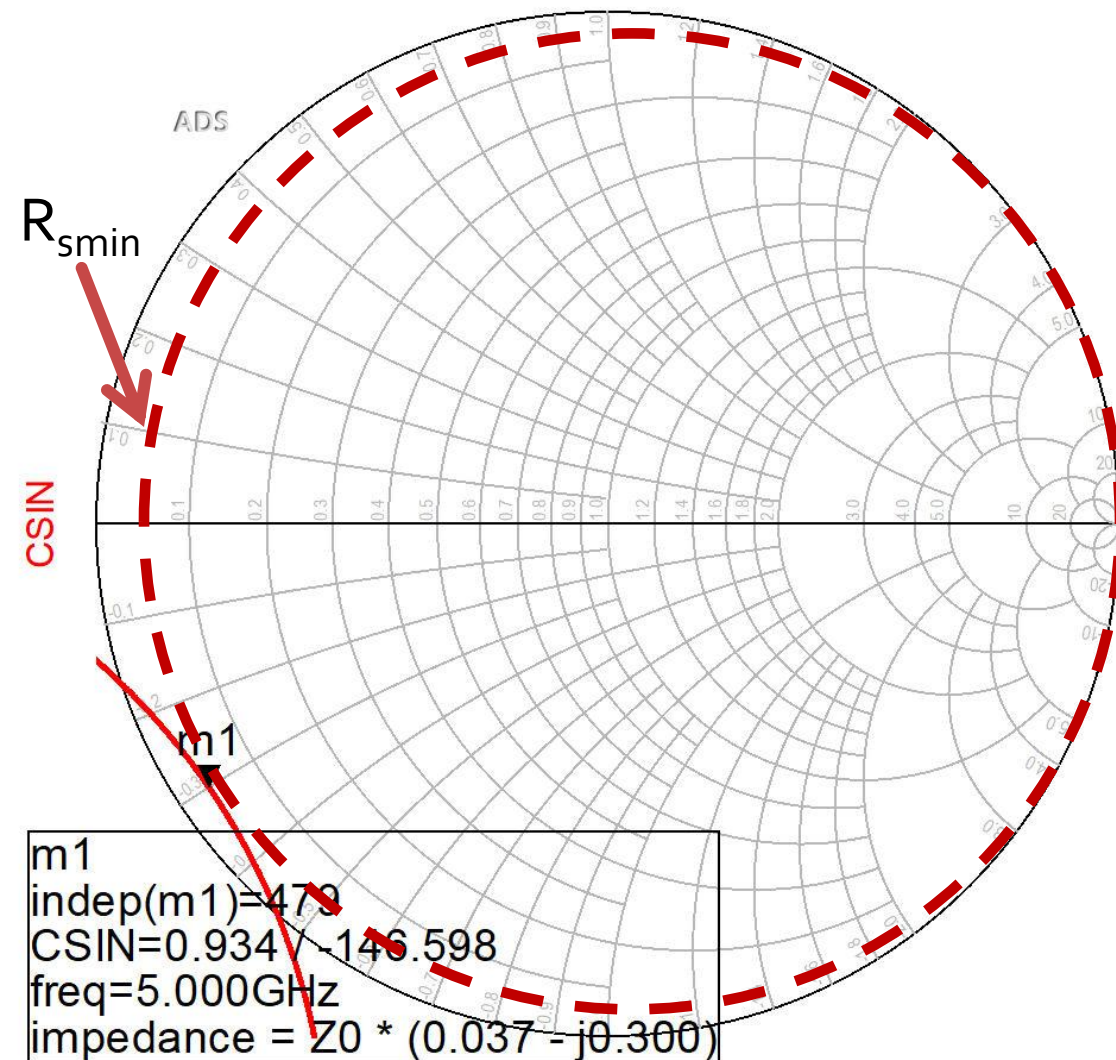



$$R_{smin} = 0.037 \cdot 50\Omega = 1.85\Omega$$

ADS, $R_s = 2\Omega$


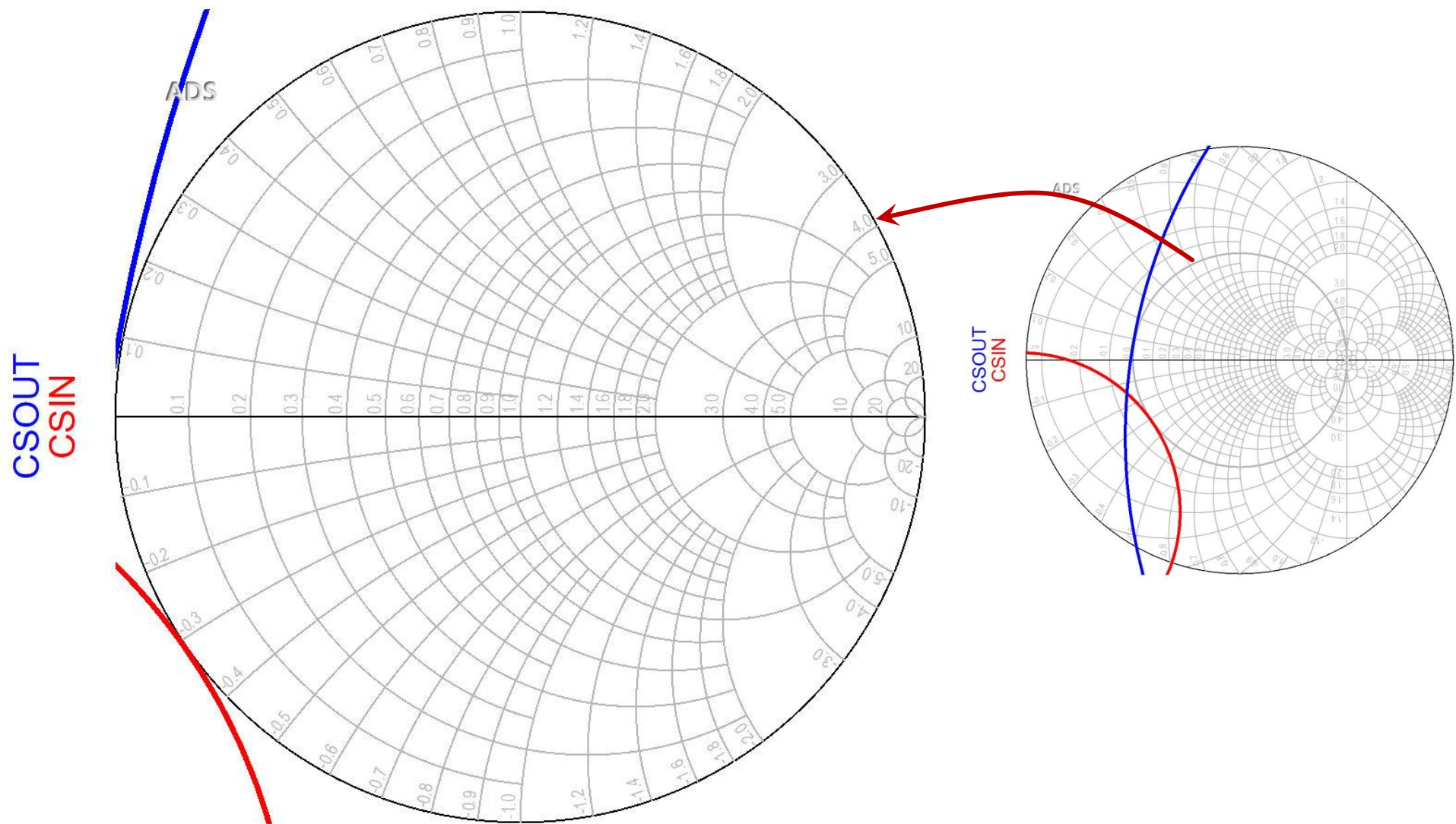


Input series resistor

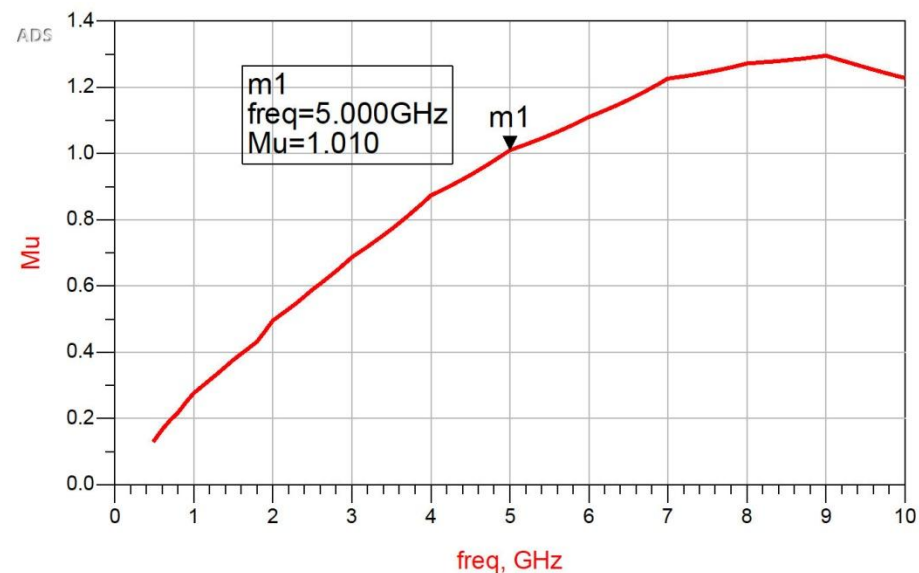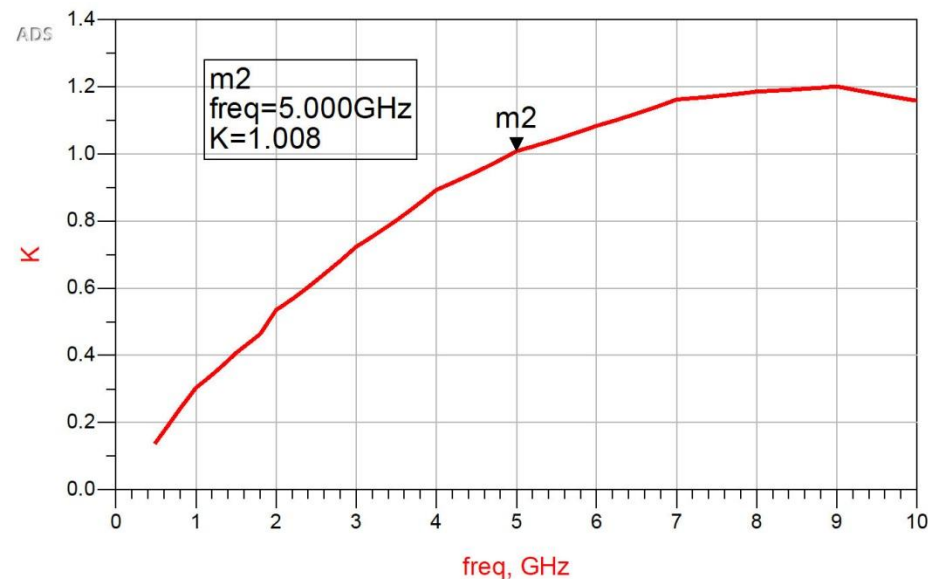- $R_s = 2\Omega$
- $K = 1.008$, $MAG = 13.694\text{dB}$ @ 5GHz
 - no stabilization, $K = 0.886$, $MAG = 14.248\text{dB}$ @ 5GHz



Input shunt resistor

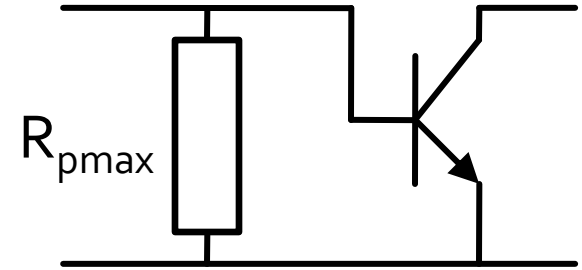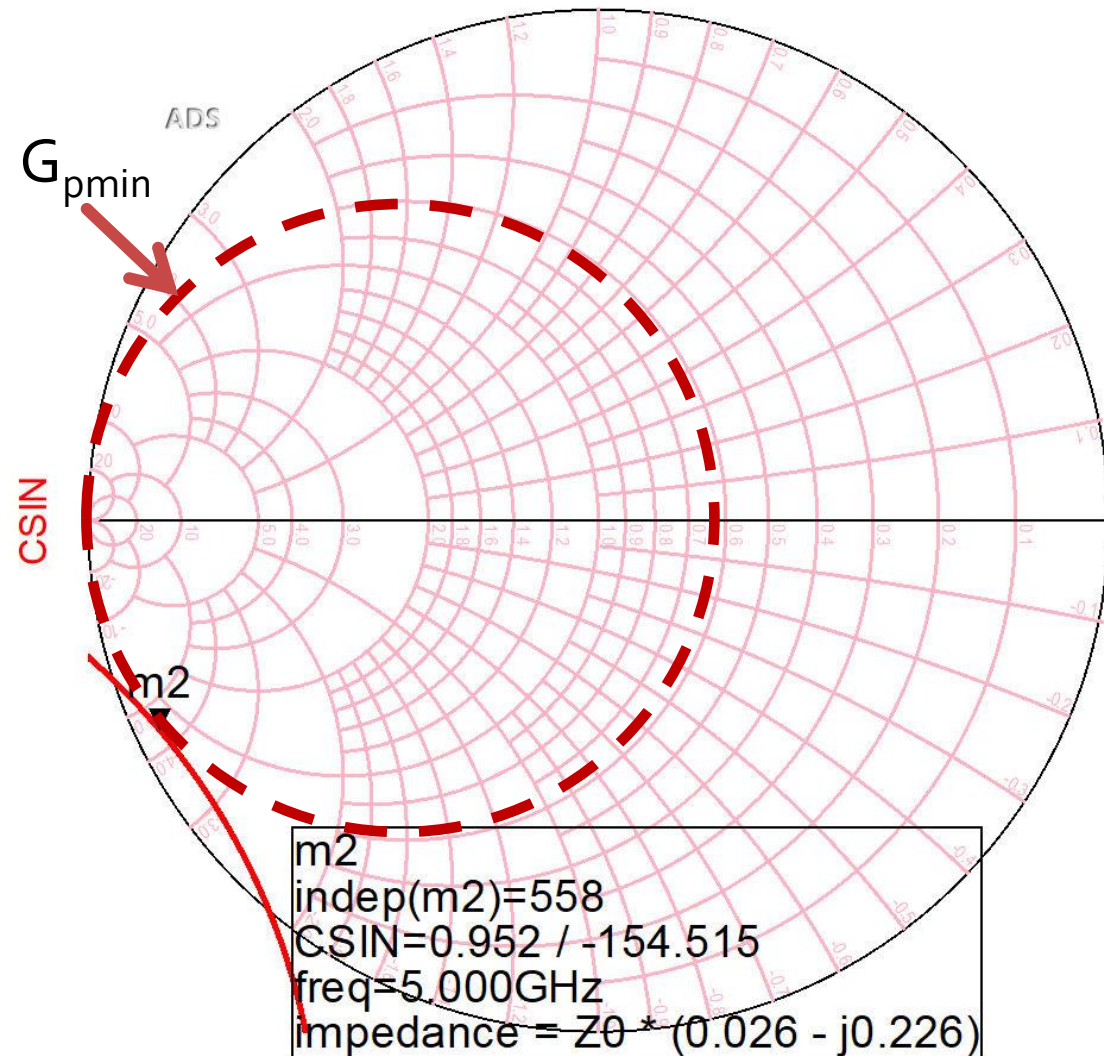


$$R_{pmax} = \frac{1}{G_{pmin}}$$

$$\frac{1}{0.026 - j \cdot 0.226} = 0.502 + j \cdot 4.367$$



$$R_{pmax} = \frac{50\Omega}{0.502} = 99.6\Omega$$

ADS, $R_p = 90^\circ\Omega$

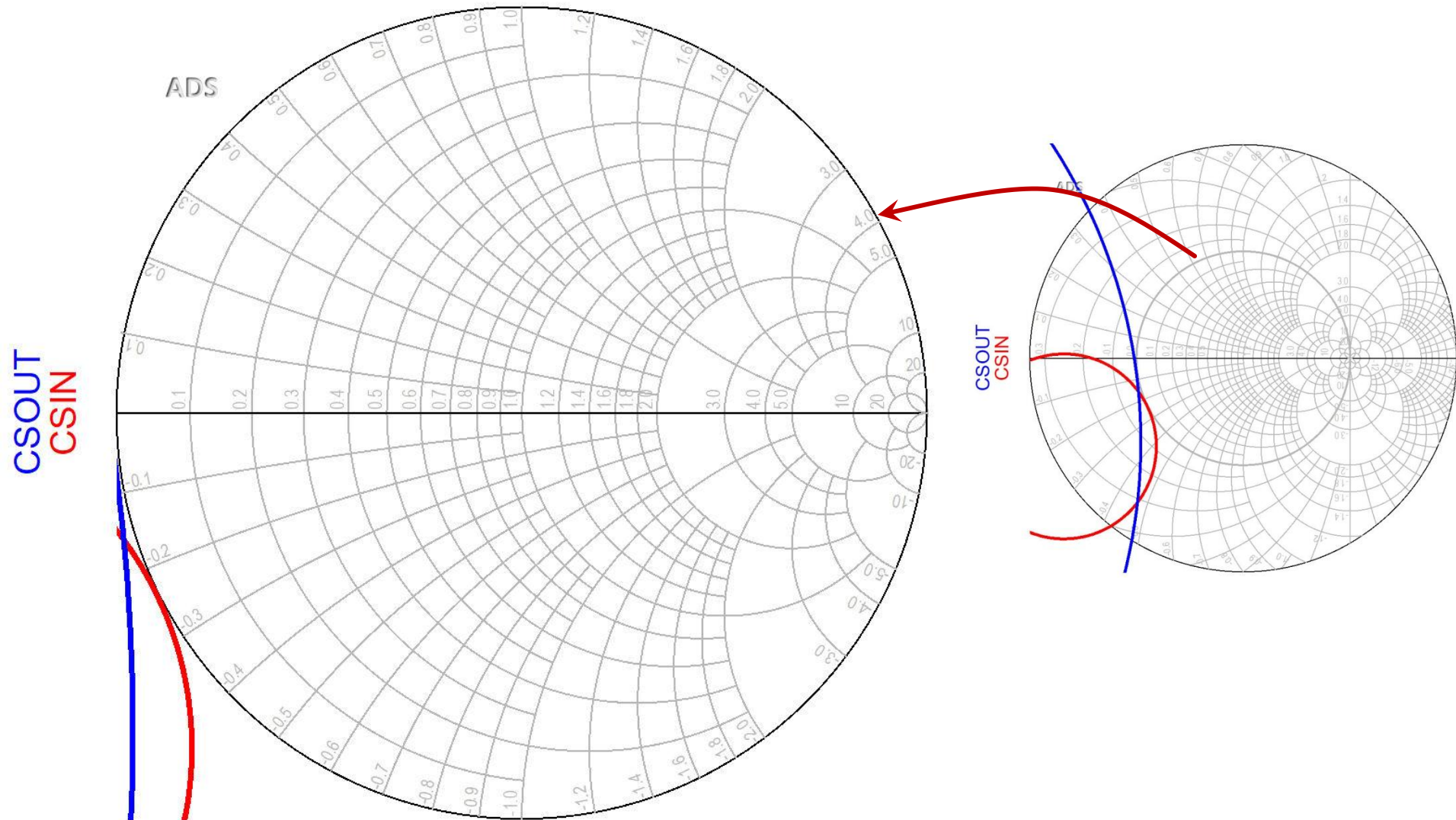



Input shunt resistor

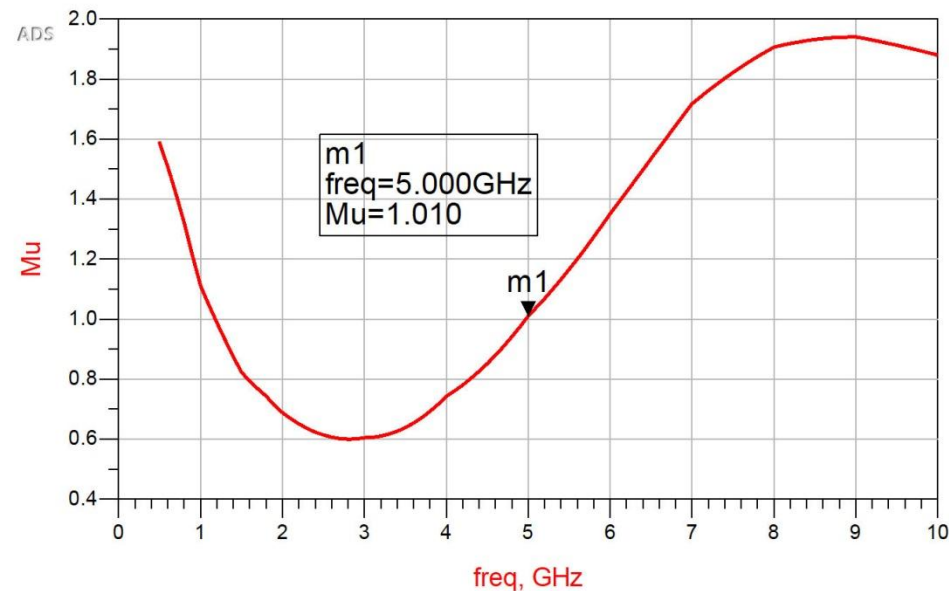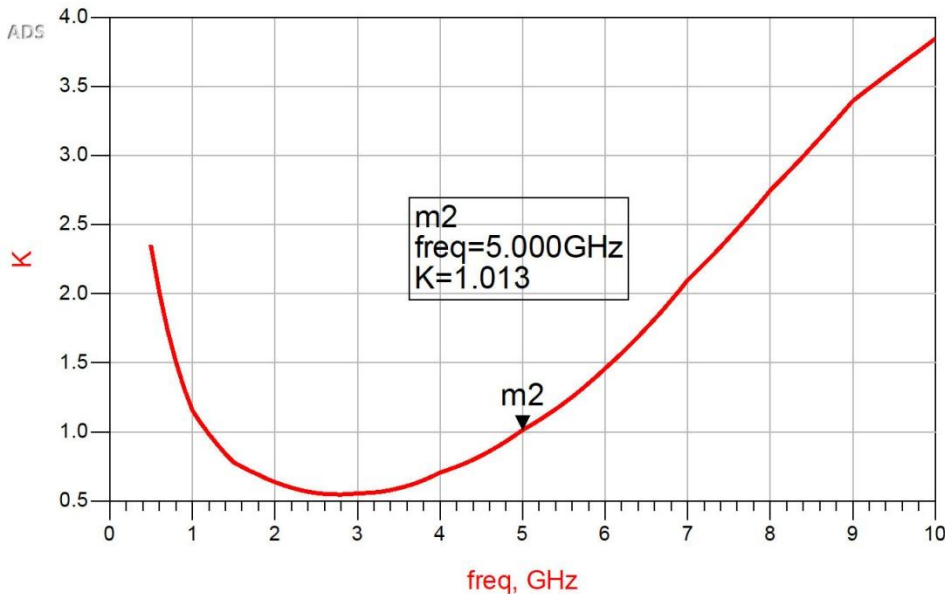- $R_p = 90\Omega$
- $K = 1.013$, $MAG = 13.561\text{dB}$ @ 5GHz
 - no stabilization, $K = 0.886$, $MAG = 14.248\text{dB}$ @ 5GHz



Output series/shunt resistor

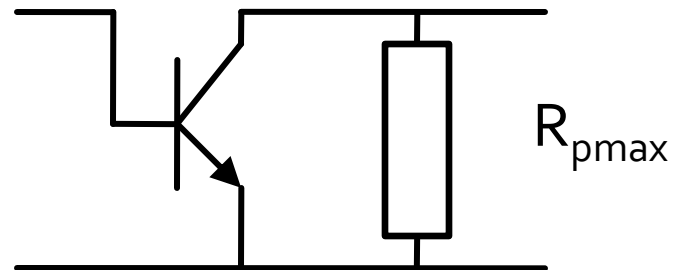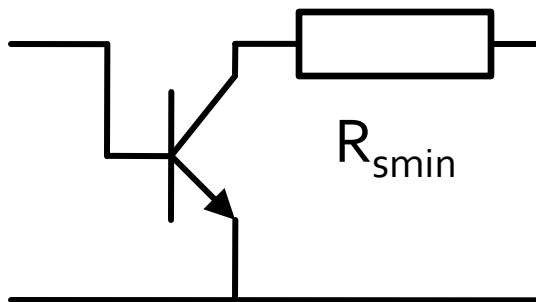
- The procedure can be applied similarly at the output (finding g/r circles tangent to CSOUT)
- From previous examples, resistive loading at the input has a positive effect over output stability and vice versa (resistive loading at the output, effect over input stability)



Stabilization of two-port

- Negative effect over the power gain
 - we must check MAG/MSG while designing resistive loading
- Negative effect over the noise (next lectures)
- We can choose one of the 4 possibilities or a combination which offers better results (depending on transistor, application etc.)
- We can use frequency selective loading
 - Ex: RL, RC circuits which sacrifice performance only when needed to improve stability and have no effect at frequencies where the device is already stable
- It might be possible (and should be checked) that stability is improved as an effect of parasitic elements of biasing circuits (bypass capacitors and RF chokes)

Stabilization of two-port

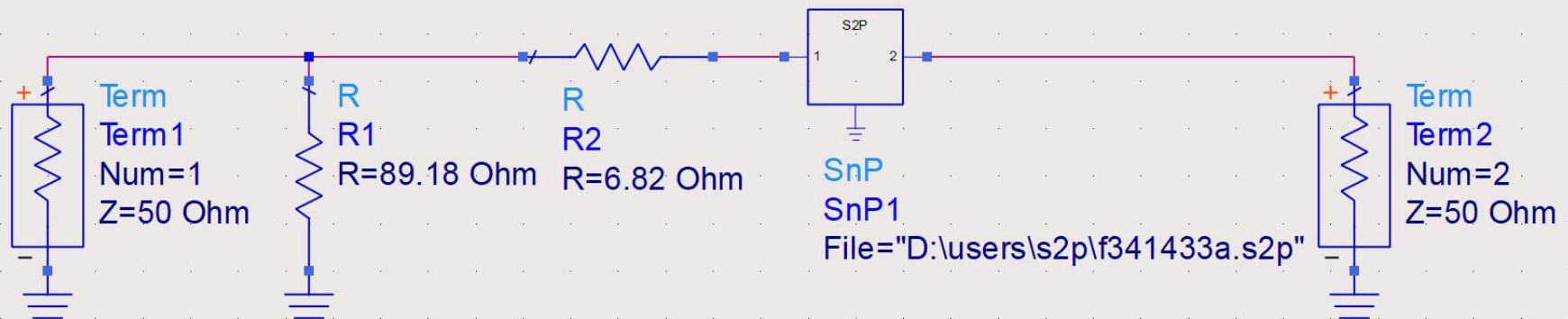

S-PARAMETERS


S_Param

SP1

Start=0.5 GHz

Stop=10.0 GHz

Step=0.1 GHz

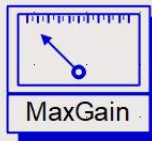


MaxGain

MaxGain

MAG

MAG=max_gain(S)

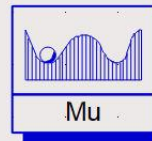


Mu

Mu

Mu1

Mu=mu(S)

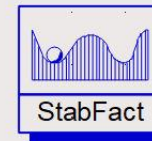



StabFact

StabFact


K

K=stab_fact(S)



Stabilization of two-port

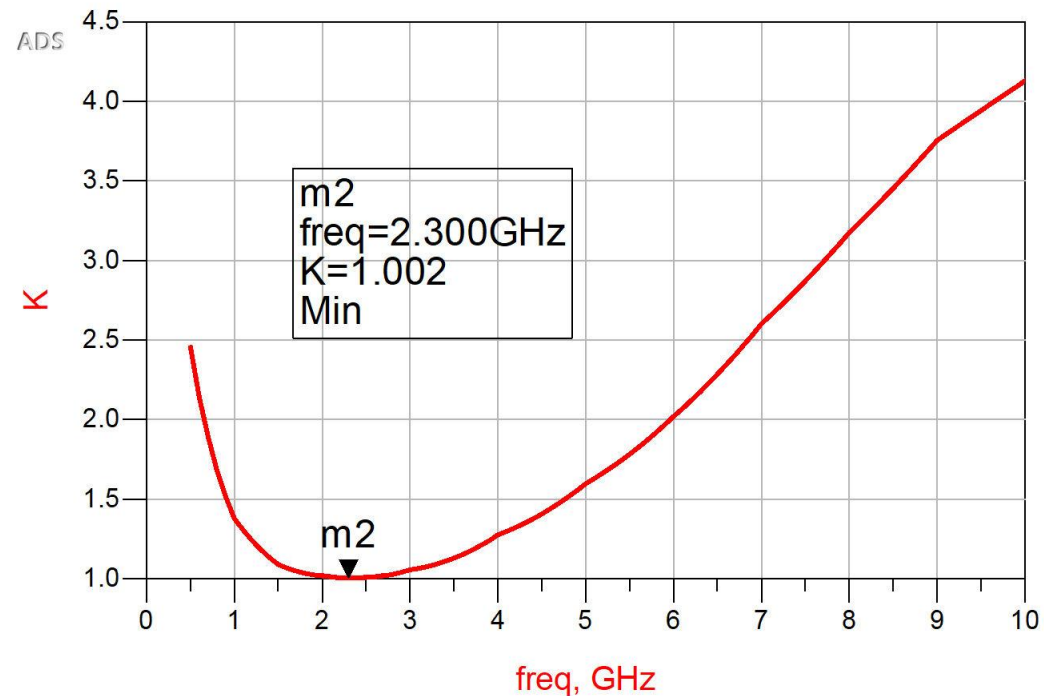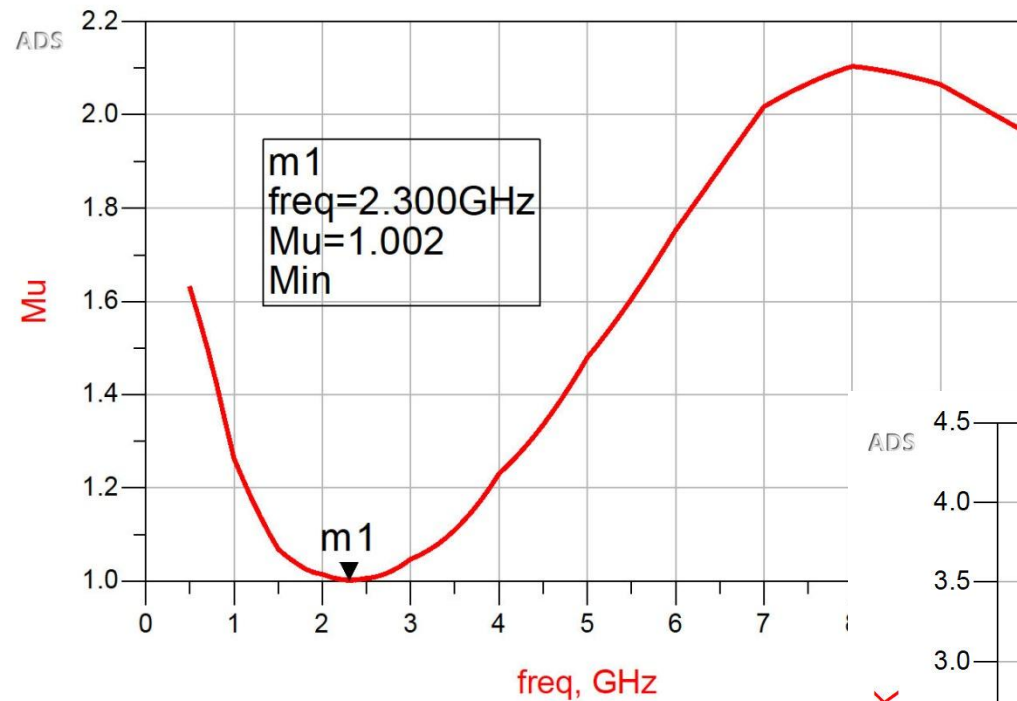

Stabilization of two-port

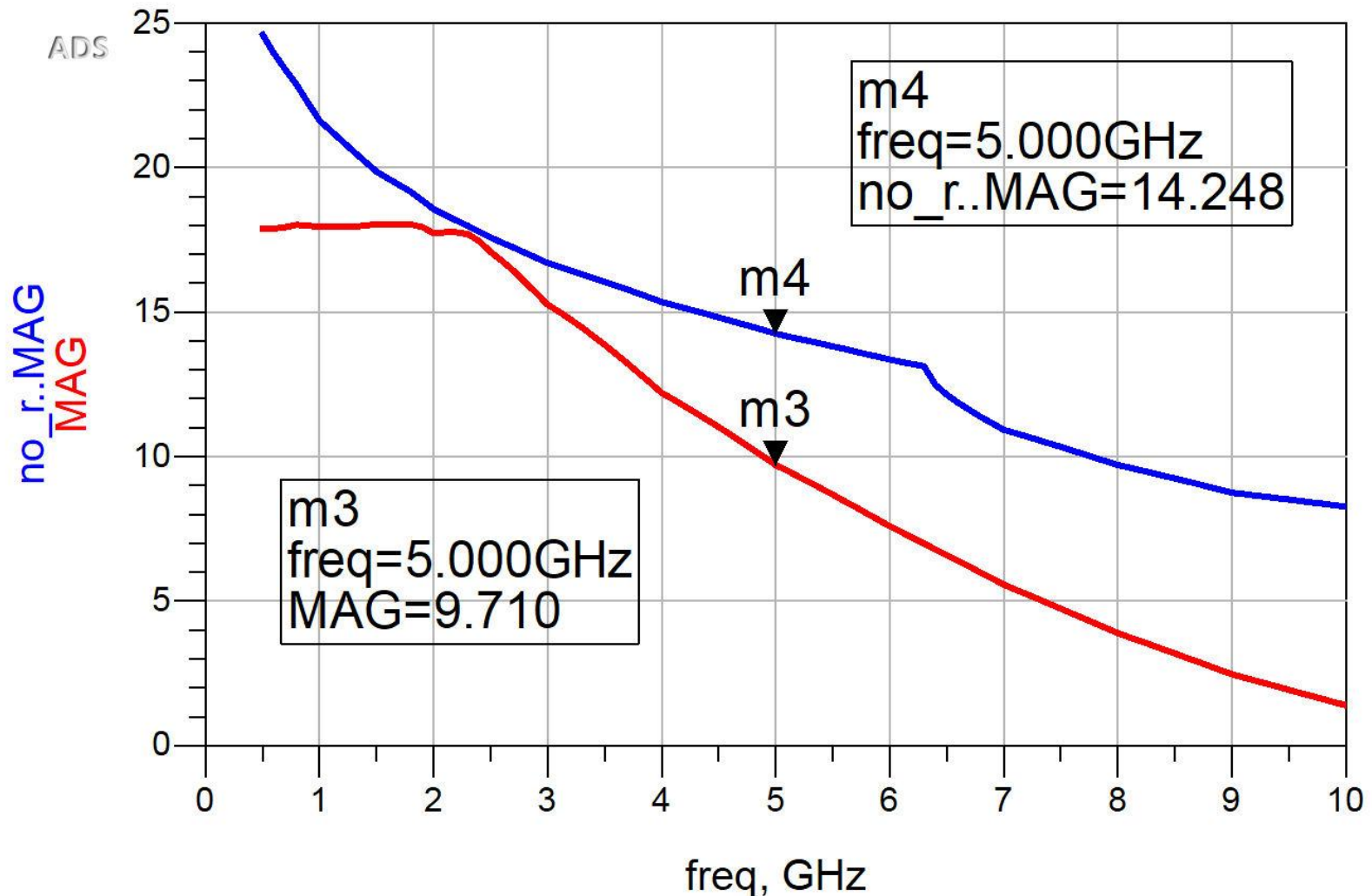

Stabilization of two-port

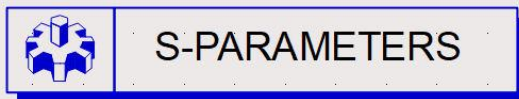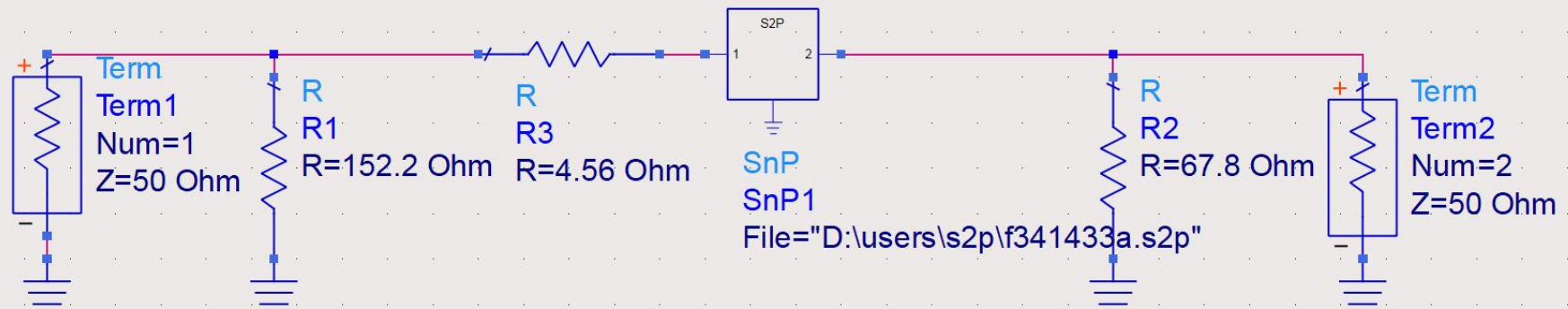


S_Param

SP1

Start=0.5 GHz

Stop=10.0 GHz


Step=0.1 GHz

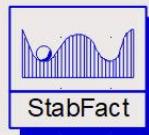

StabFact

K


$K=\text{stab_fact}(S)$

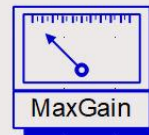

MaxGain

MAG

$\text{MAG}=\text{max_gain}(S)$


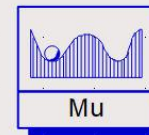


Mu


Mu1

$\text{Mu}=\text{mu}(S)$

Stabilization of two-port

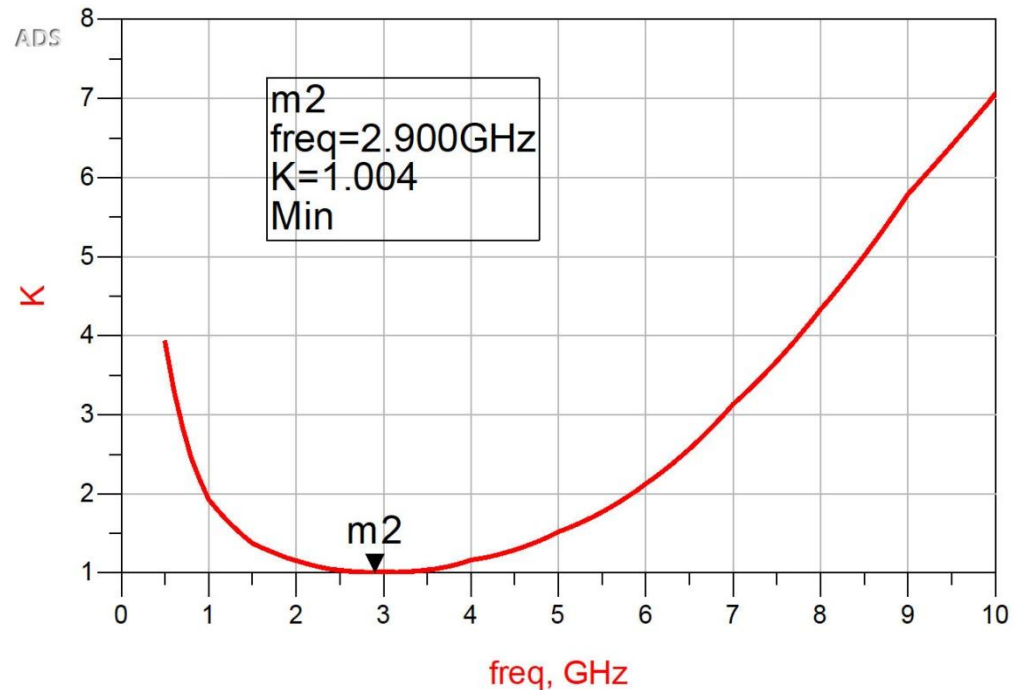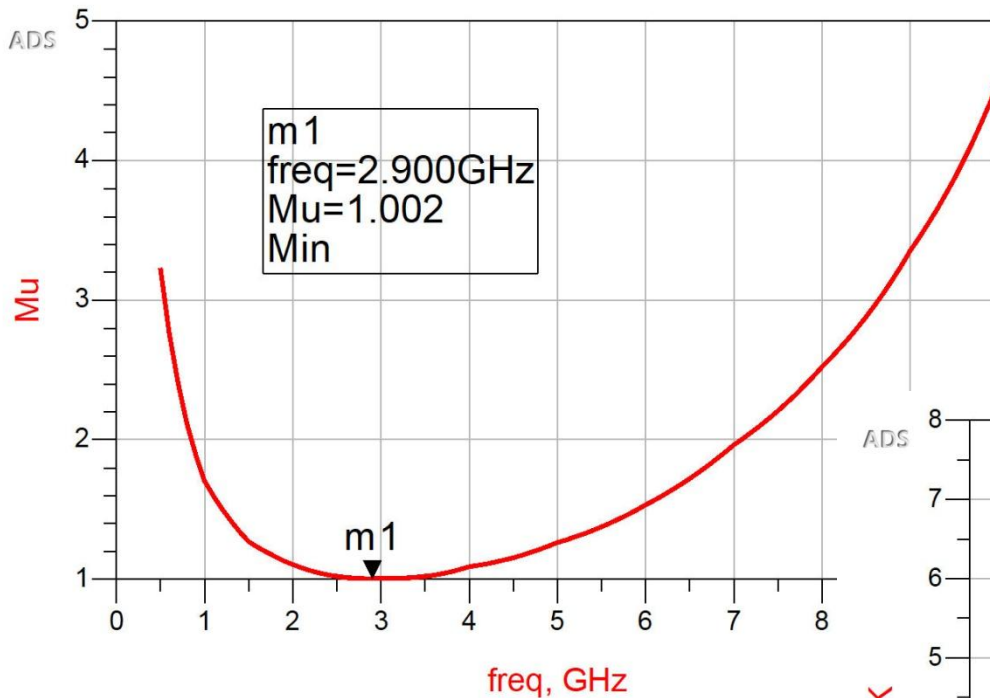


Stabilization of two-port

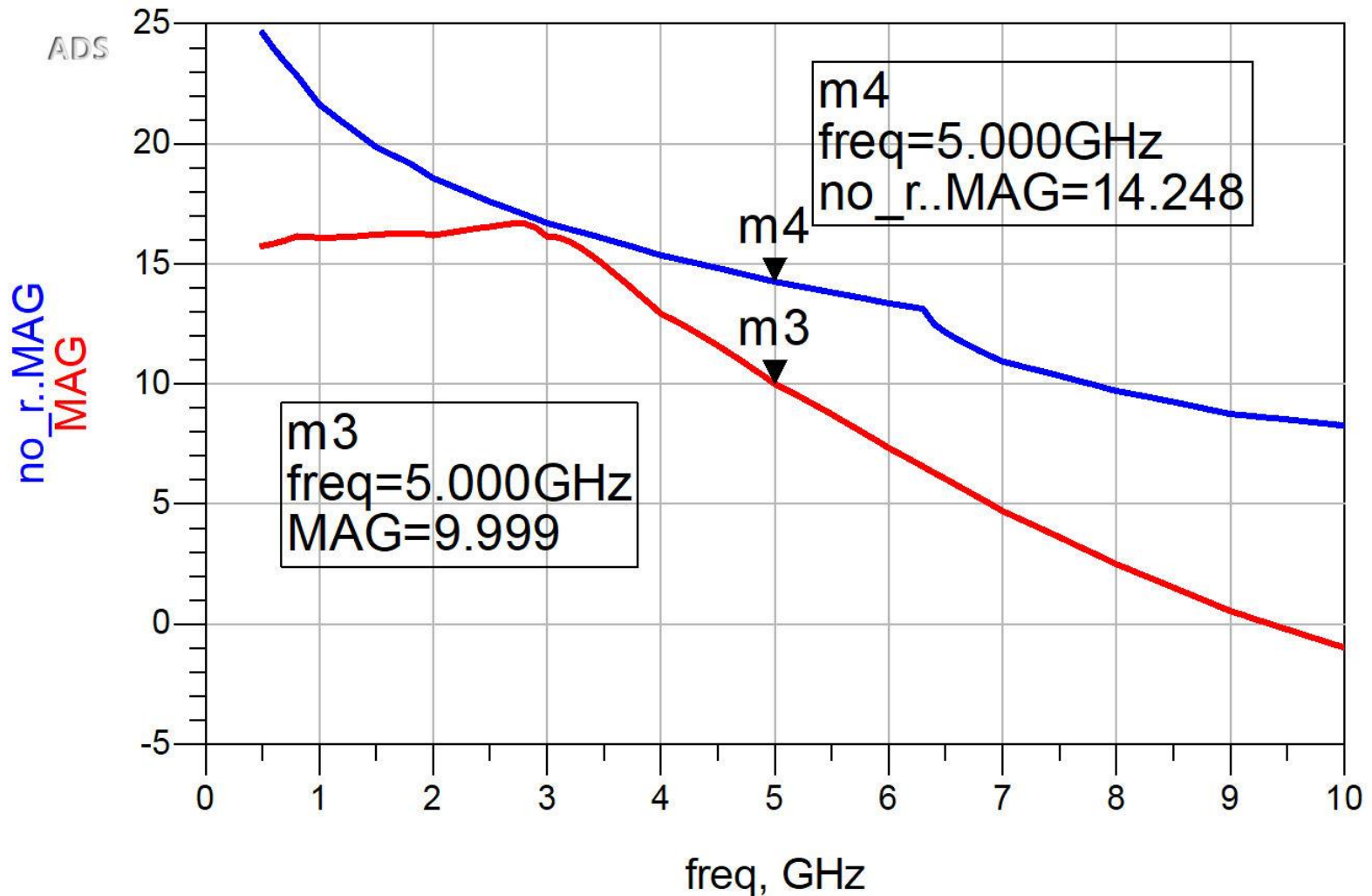

Power Gain of Microwave Amplifiers

Microwave Amplifiers

Design for Maximum Gain

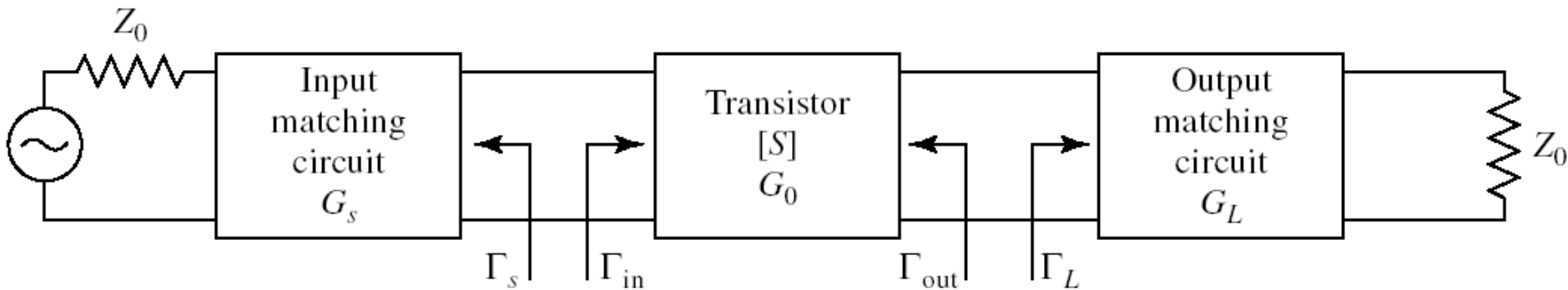

- Maximum power gain (complex conjugate matching):

$$\Gamma_{in} = \Gamma_S^* \quad \Gamma_{out} = \Gamma_L^*$$



- For lossless matching sections

$$G_{T \max} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2} \quad G_{T \max} = \frac{1}{1 - |\Gamma_S|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

- For the general case of the bilateral transistor ($S_{12} \neq 0$)

Γ_{in} and Γ_{out} depend on each other so the input and output sections must be matched simultaneously

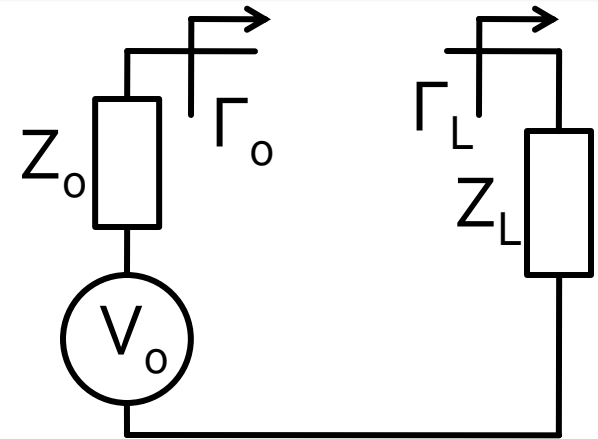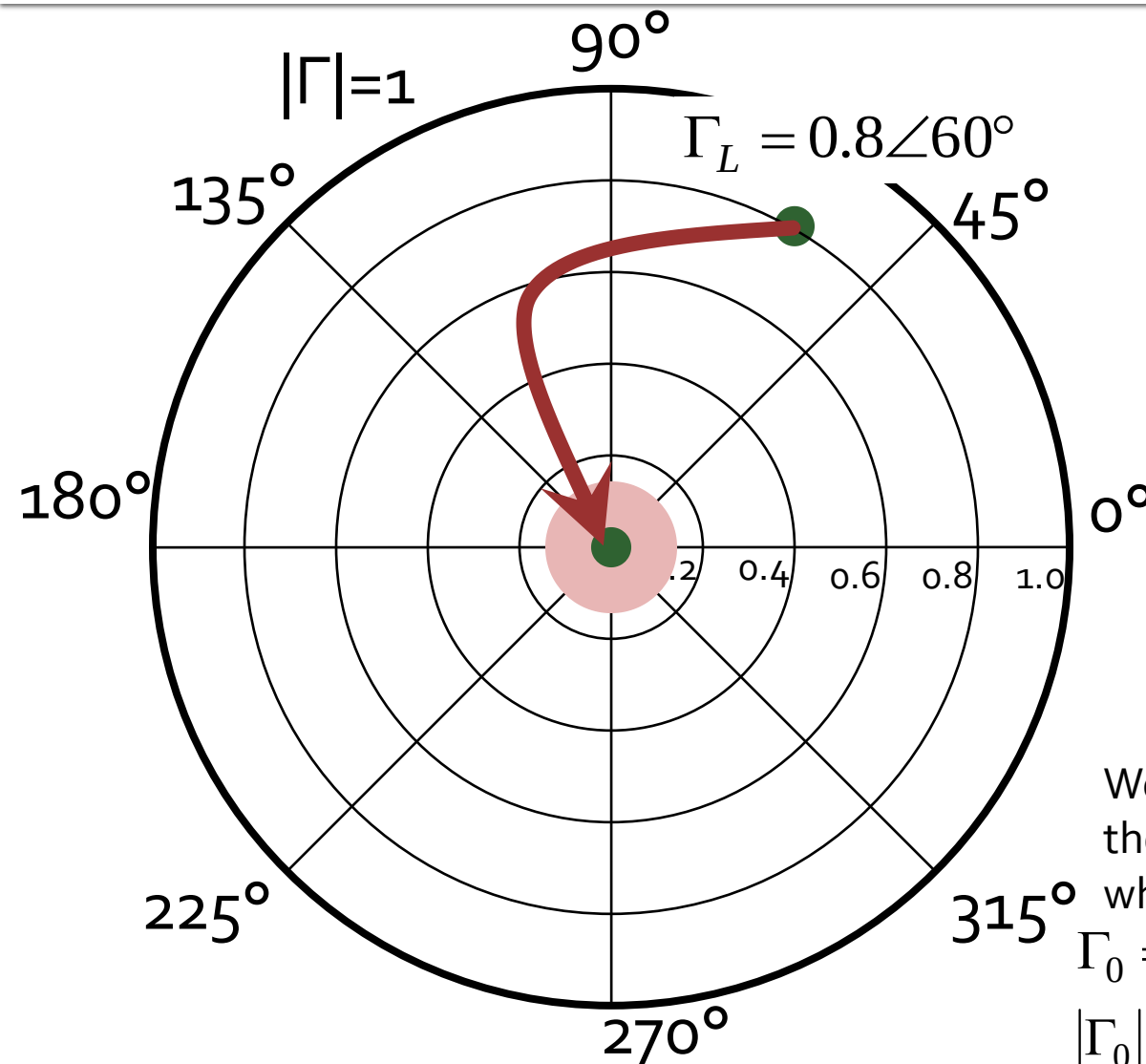The Smith Chart, matching, $Z_L \neq Z_o$



Matching Z_L load to Z_o source.
We normalize Z_L over Z_o

$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

$$z_L = 0.429 + j \cdot 1.65$$



$$\Gamma_L = 0.8 \angle 60^\circ$$

We must move the point denoting the reflection coefficient in the area where with a Z_o source we have:

$$\Gamma_o = 0 \quad \text{perfect match}$$

$$|\Gamma_o| \leq \Gamma_m \quad \text{"good enough" match}$$

The Smith Chart, matching, $Z_L = Z_o$

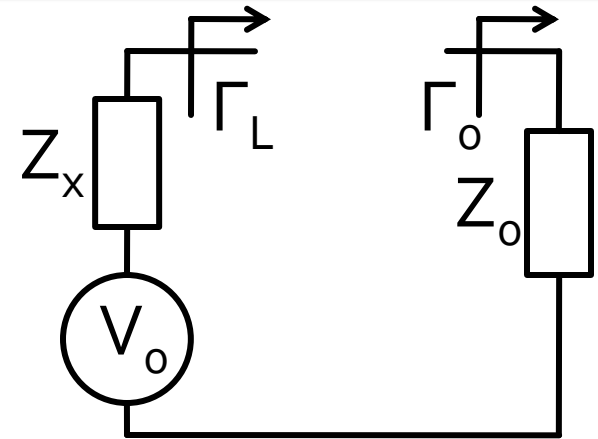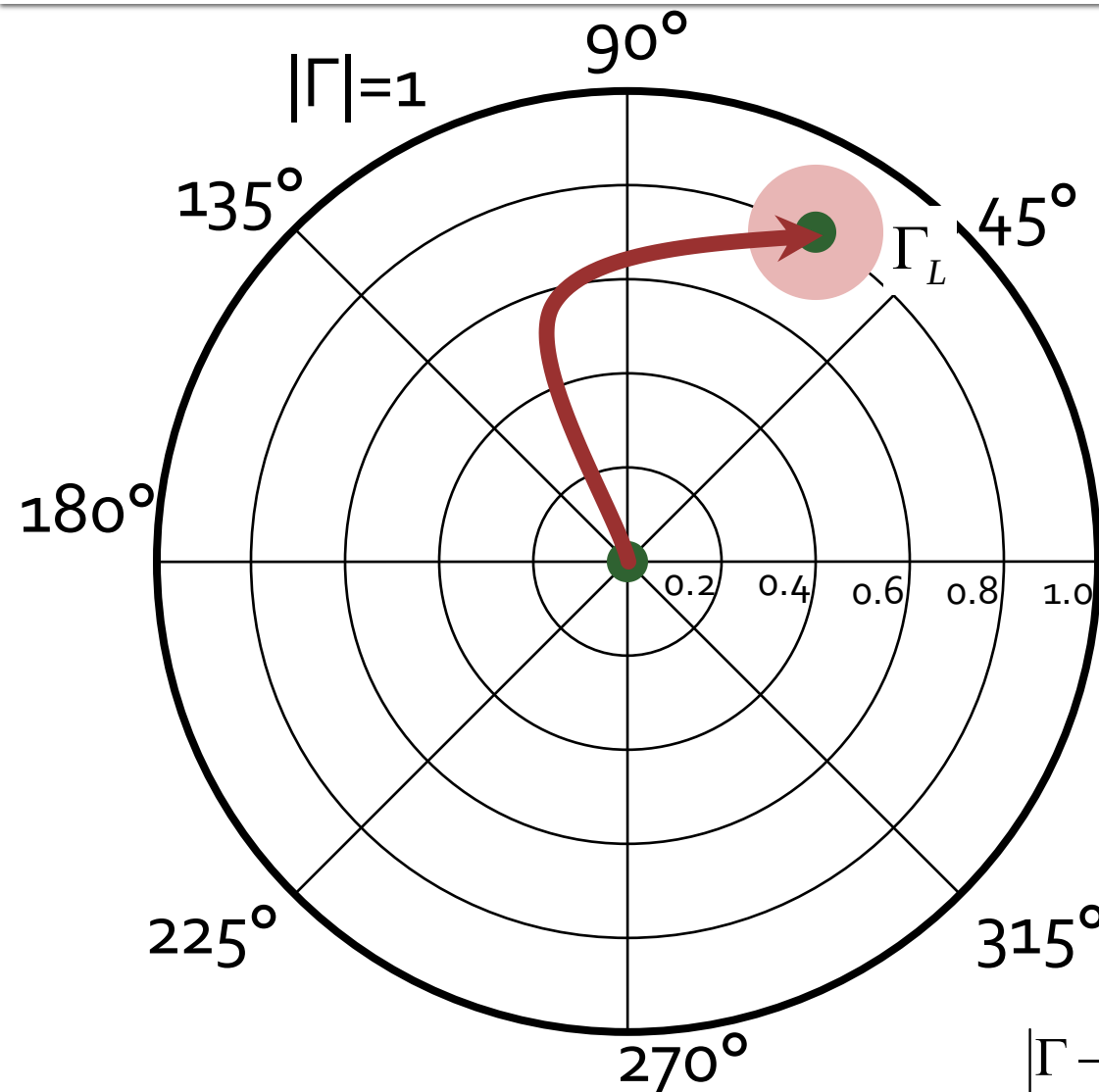

0° The source (eg. the transistor) having Z_x needs to see a certain reflection coefficient Γ_L towards the load Z_o


The matching circuit must move the point denoting the reflection coefficient in the area where for a Z_o load ($\Gamma_o = 0$) we see towards it:

$\Gamma = \Gamma_L$ perfect match

$|\Gamma - \Gamma_L| \leq \Gamma_m$ "good enough" match

The Smith Chart, matching ,

$Z_L \neq Z_o, Z_L = Z_o$

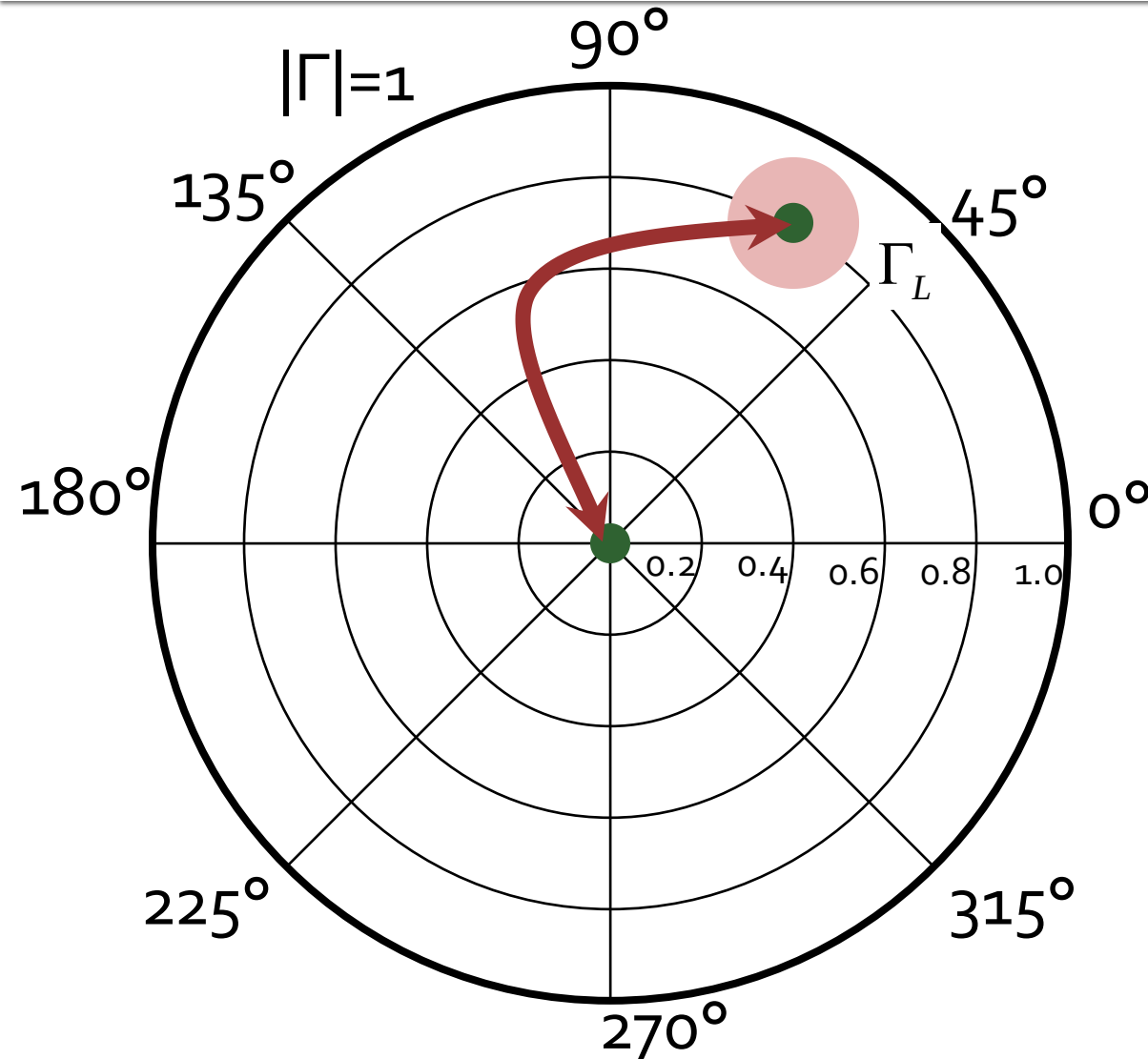

- The matching sections needed to move
 - Γ_L in Γ_o
 - Γ_o in Γ_L
- are **identical**. They differ only by the **order** in which the elements are introduced into the matching circuit
- As a result, we can use in match design the same:
 - **methods**
 - **formulae**

Simultaneous matching

$$\Gamma_{in} = \Gamma_S^*$$

$$\Gamma_{in} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_S^* = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_{out} = \Gamma_L^*$$

$$\Gamma_{out} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

$$\Gamma_L^* = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

■ We find Γ_S

$$\Gamma_S = S_{11}^* + \frac{S_{12}^* \cdot S_{21}^*}{1/\Gamma_L^* - S_{22}^*}$$

$$\Gamma_L^* = \frac{S_{22} - \Delta \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

$$\Gamma_S \cdot (1 - |S_{22}|^2) + \Gamma_S^2 \cdot (\Delta \cdot S_{22}^* - S_{11}) = \Gamma_S \cdot (\Delta \cdot S_{11}^* \cdot S_{22}^* - |S_{22}|^2 - \Delta \cdot S_{12}^* \cdot S_{21}^*) + S_{11}^* \cdot (1 - |S_{22}|^2) + S_{12}^* \cdot S_{21}^* \cdot S_{22}$$

Simultaneous matching

$$\Delta \cdot (S_{11}^* \cdot S_{22}^* - S_{12}^* \cdot S_{21}^*) = |\Delta|^2$$

$$\Gamma_S^2 \cdot (S_{11} - \Delta \cdot S_{22}^*) + \Gamma_S \cdot (|\Delta|^2 - |S_{11}|^2 + |S_{22}|^2 - 1) + (S_{11}^* - \Delta^* \cdot S_{22}) = 0$$

- A quadratic equation

$$\Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

- Similarly

$$\Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

- With variables defined as:

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases} \quad \begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

Simultaneous matching

- Simultaneous matching is possible if:

$$B_1^2 - 4 \cdot |C_1|^2 > 0 \quad B_2^2 - 4 \cdot |C_2|^2 > 0$$

$$\Delta \cdot (S_{11}^* \cdot S_{22}^* - S_{12}^* \cdot S_{21}^*) = |\Delta|^2$$

$$|C_1|^2 = |S_{11} - \Delta \cdot S_{22}^*|^2 = |S_{12}|^2 \cdot |S_{21}|^2 + (1 - |S_{22}|^2) \cdot (|S_{11}|^2 - |\Delta|^2)$$

$$B_1^2 - 4 \cdot |C_1|^2 = (1 + |S_{11}|^2)^2 + (|S_{22}|^2 + |\Delta|^2)^2 - \\ - 2 \cdot (1 + |S_{11}|^2) \cdot (|S_{22}|^2 + |\Delta|^2) - 4 \cdot |S_{12} \cdot S_{21}|^2 - 4 \cdot (1 - |S_{22}|^2) \cdot (|S_{22}|^2 - |\Delta|^2)$$

$$B_1^2 - 4 \cdot |C_1|^2 = (1 + |S_{11}|^2)^2 + (|S_{22}|^2 + |\Delta|^2)^2 - \\ - 4 \cdot |S_{11}|^2 - 4 \cdot |S_{22}|^2 \cdot |\Delta|^2 - 2 \cdot (1 - |S_{11}|^2) \cdot (|S_{22}|^2 - |\Delta|^2) - 4 \cdot |S_{12} \cdot S_{21}|^2$$

Simultaneous matching

$$B_1^2 - 4 \cdot |C_1|^2 = \left(1 + |S_{11}|^2\right)^2 + \left(|S_{22}|^2 + |\Delta|^2\right)^2 - 4 \cdot |S_{11}|^2 - 4 \cdot |S_{22}|^2 \cdot |\Delta|^2 - 2 \cdot \left(1 - |S_{11}|^2\right) \cdot \left(|S_{22}|^2 - |\Delta|^2\right) - 4 \cdot |S_{12} \cdot S_{21}|^2$$

$$B_1^2 - 4 \cdot |C_1|^2 = \left(1 - |S_{11}|^2\right)^2 + \left(|S_{22}|^2 - |\Delta|^2\right)^2 - 2 \cdot \left(1 - |S_{11}|^2\right) \cdot \left(|S_{22}|^2 - |\Delta|^2\right) - 4 \cdot |S_{12} \cdot S_{21}|^2$$

$$B_1^2 - 4 \cdot |C_1|^2 = \left(1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2\right)^2 - 4 \cdot |S_{12} \cdot S_{21}|^2$$

$$B_1^2 - 4 \cdot |C_1|^2 = \left(K \cdot 2 \cdot |S_{12} \cdot S_{21}|\right)^2 - 4 \cdot |S_{12} \cdot S_{21}|^2$$

$$B_1^2 - 4 \cdot |C_1|^2 = 4 \cdot |S_{12}|^2 \cdot |S_{21}|^2 \cdot (K^2 - 1)$$

■ Similarly

$$B_2^2 - 4 \cdot |C_2|^2 = 4 \cdot |S_{12}|^2 \cdot |S_{21}|^2 \cdot (K^2 - 1)$$

Simultaneous matching

$$\Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

$$\Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

■ Necesari pentru solutii

$$|\Gamma_S| < 1 \quad |\Gamma_L| < 1$$

$$|\Delta| = |S_{11} \cdot S_{22} - S_{12} \cdot S_{21}| < 1$$

$$\begin{cases} B_1 > 0 \\ B_2 > 0 \end{cases}$$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 \cdot |S_{12} \cdot S_{21}|} > 1$$

$$\begin{cases} B_1^2 - 4 \cdot |C_1|^2 = 4 \cdot |S_{12}|^2 \cdot |S_{21}|^2 \cdot (K^2 - 1) > 0 \\ B_2^2 - 4 \cdot |C_2|^2 = 4 \cdot |S_{12}|^2 \cdot |S_{21}|^2 \cdot (K^2 - 1) > 0 \end{cases}$$

Simultaneous matching

- Simultaneous matching can be achieved **if and only if** the amplifier is **unconditionally stable** at the operating frequency, and $|\Gamma| < 1$ solutions are those with “–” sign of quadratic solutions

$$\Gamma_S = \frac{B_1 - \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases}$$

$$\Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

$$\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

Simultaneous matching

- In the case of the simultaneous matching the amplifier achieves the maximum transducer power gain for the bilateral transistor


$$G_{T\max} = \frac{|S_{21}|}{|S_{12}|} \cdot (K - \sqrt{K^2 - 1})$$

- If the device is **not unconditionally stable** at a certain frequency we can use MSG (Maximum Stable Gain) as an indicator of the capability to obtain a power gain in stable conditions

$$G_{MSG} = \frac{|S_{21}|}{|S_{12}|}$$


Maximum Available Gain

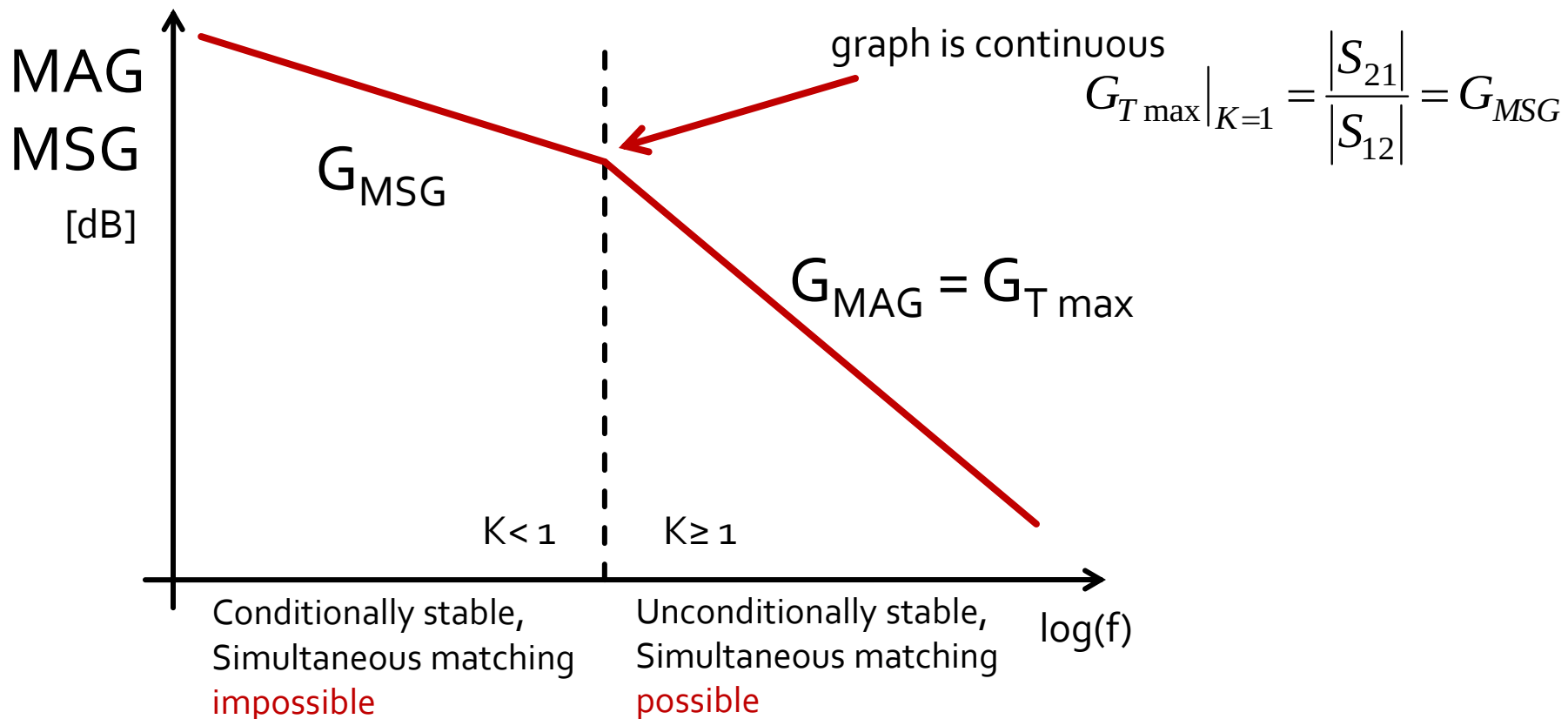- Indicator across full frequency range of the capability to obtain a power gain




Stability

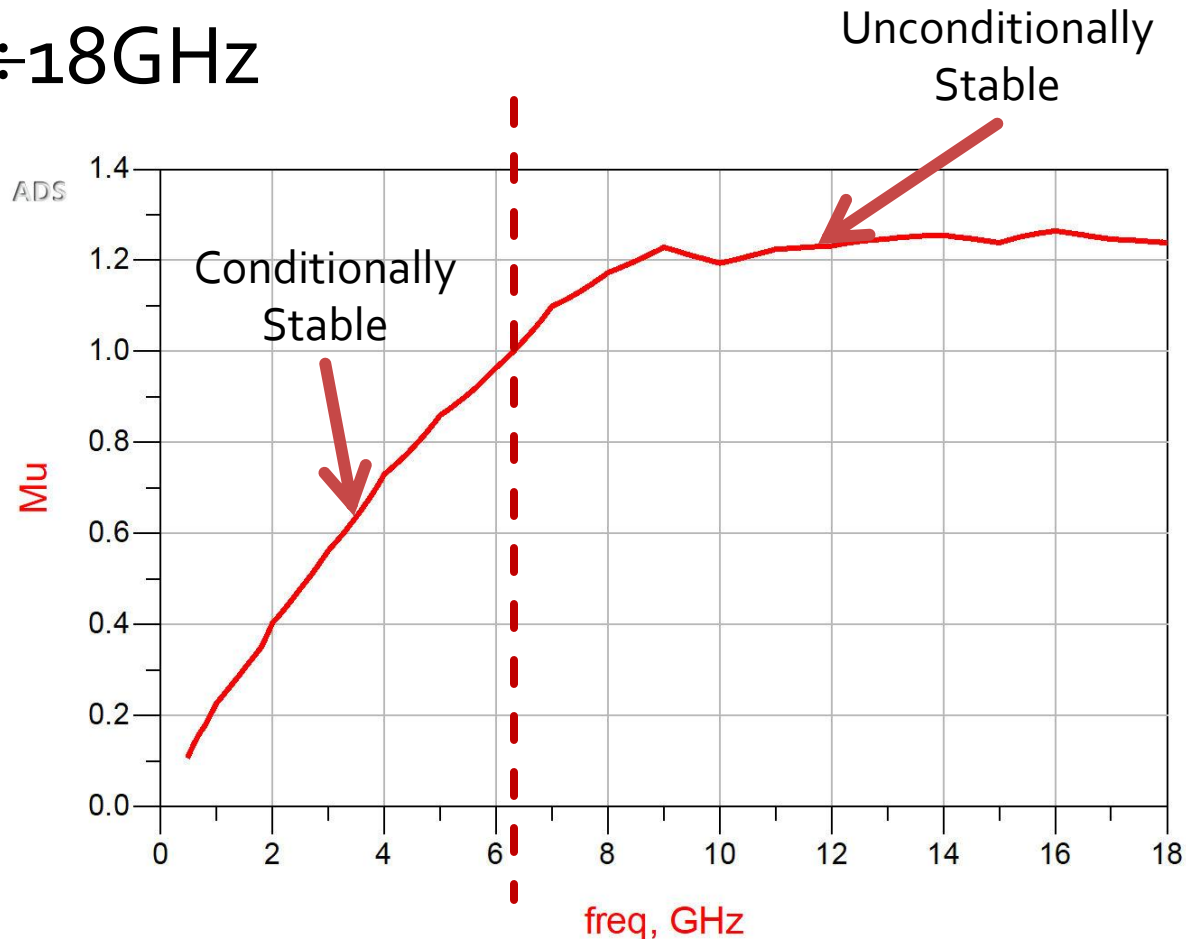- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz




MAG/MSG

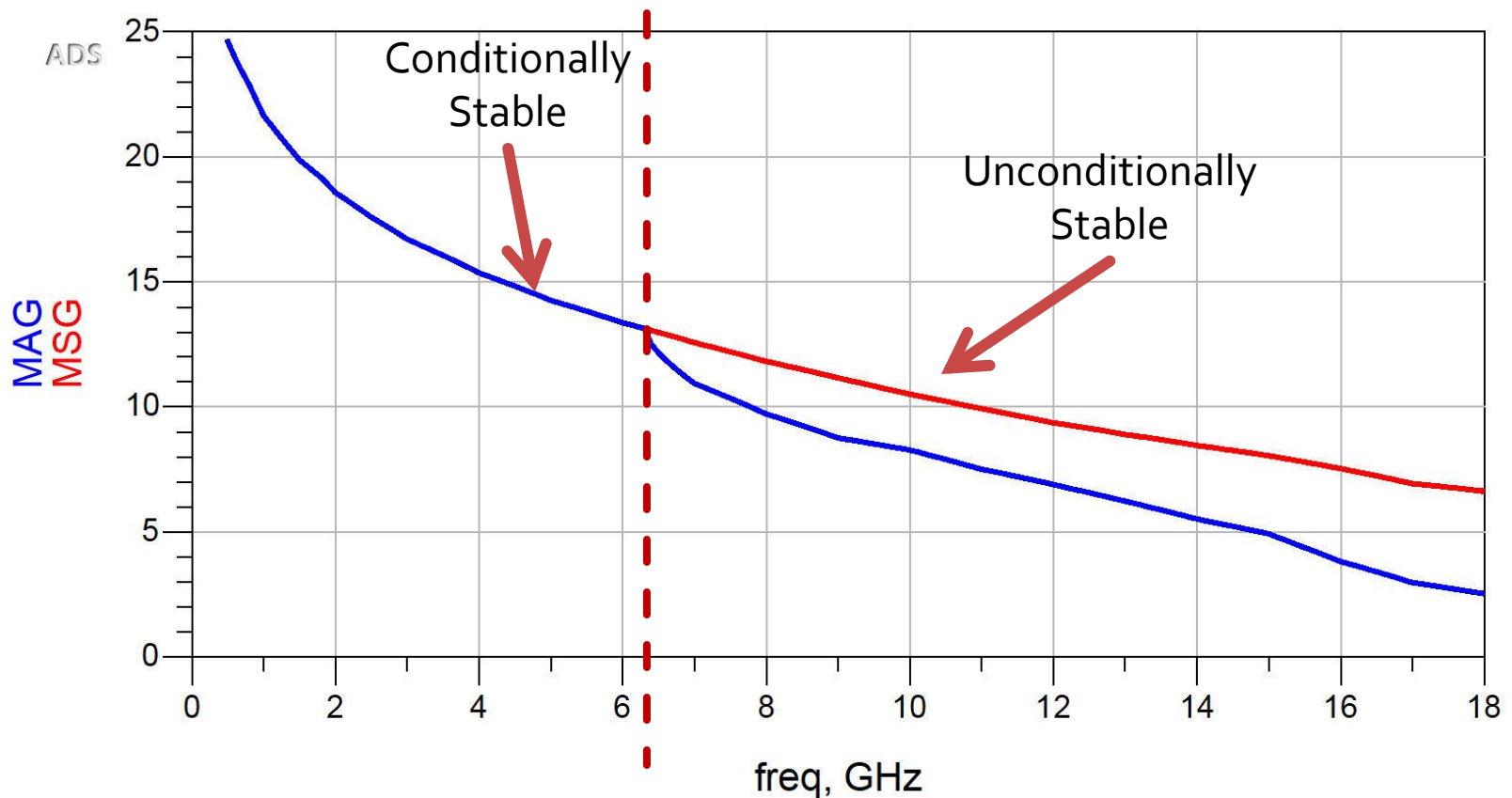- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz



Simultaneous matching, unilateral transistor

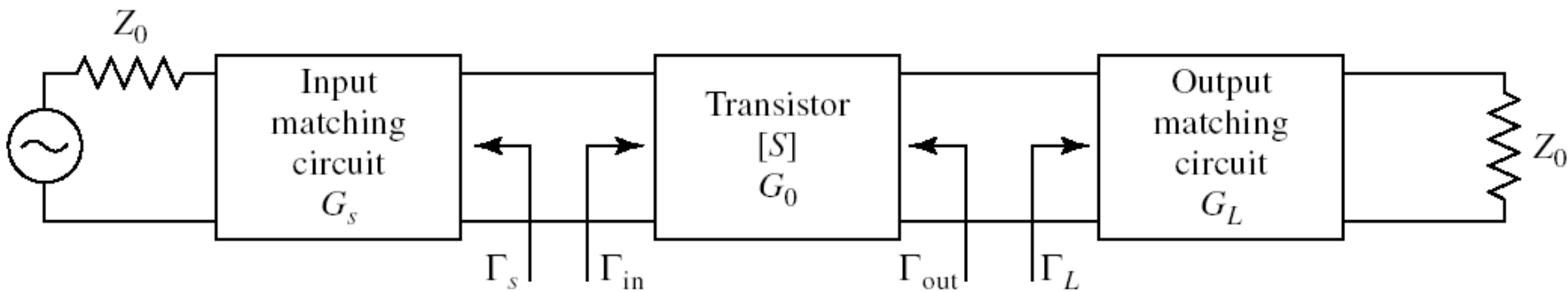- In the case of **unilateral** amplifier/transistor ($S_{12} = 0$) simultaneous matching implies:



$$\Gamma_{in} = S_{11}$$

$$\Gamma_{out} = S_{22}$$

$$\Gamma_s = S_{11}^*$$

$$\Gamma_L = S_{22}^*$$

$$G_{T \max} = \frac{1}{1 - |\Gamma_s|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$G_{TU \max} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2}$$

Example

- ATF-34143 **at $V_{ds}=3V$ $I_d=20mA$.**
 - without stabilization $K = 0.886$, $MAG = 14.248dB$ @ 5GHz
 - cannot be used with this bias conditions
- ATF-34143 **at $V_{ds}=4V$ $I_d=40mA$**
 - without stabilization $K = 1.031$, $MAG = 12.9dB$ @ 5GHz
 - we use this bias conditions for simultaneous matching

Example

- ATF-34143 at $V_{ds}=4V$ $I_d=40mA$.
- @5GHz
 - $S_{11} = 0.64 \angle 111^\circ$
 - $S_{12} = 0.117 \angle -27^\circ$
 - $S_{21} = 2.923 \angle -6^\circ$
 - $S_{22} = 0.21 \angle 111^\circ$

Computations

■ Complex S Parameters

- $S_{11} = -0.229 + 0.597 \cdot j$
- $S_{12} = 0.104 - 0.053 \cdot j$
- $S_{21} = 2.907 - 0.306 \cdot j$
- $S_{22} = -0.075 + 0.196 \cdot j$

$$G_{T \max} = \frac{|S_{21}|}{|S_{12}|} \cdot \left(K - \sqrt{K^2 - 1} \right) = 19.497 = 12.9 \text{ dB}$$

$$G_{TU \max} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2} = 15.139 = 11.8 \text{ dB}$$

Computations

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases}$$

$$\begin{cases} B_1 = ? \\ C_1 = ? \end{cases}$$

$$\Gamma_S = \frac{B_1 - \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

$$\Gamma_S = ?$$

$$\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

$$\begin{cases} B_2 = ? \\ C_2 = ? \end{cases}$$

$$\Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

$$\Gamma_L = ?$$

Computations

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases}$$

$$\begin{cases} B_1 = 1.207 \\ C_1 = -0.277 + j \cdot 0.529 \end{cases}$$

$$\Gamma_S = \frac{B_1 - \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

$$\Gamma_S = -0.403 - j \cdot 0.768$$

$$|\Gamma_S| = 0.867 < 1$$

$$\Gamma_S = 0.867 \angle -117.7^\circ$$

$$\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

$$\begin{cases} B_2 = 0.476 \\ C_2 = -0.222 - j \cdot 0.013 \end{cases}$$


$$\Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

$$\Gamma_L = -0.685 + j \cdot 0.04$$

$$|\Gamma_L| = 0.686 < 1$$

$$\Gamma_L = 0.686 \angle 176.7^\circ$$

Shunt stub matching, C6-7

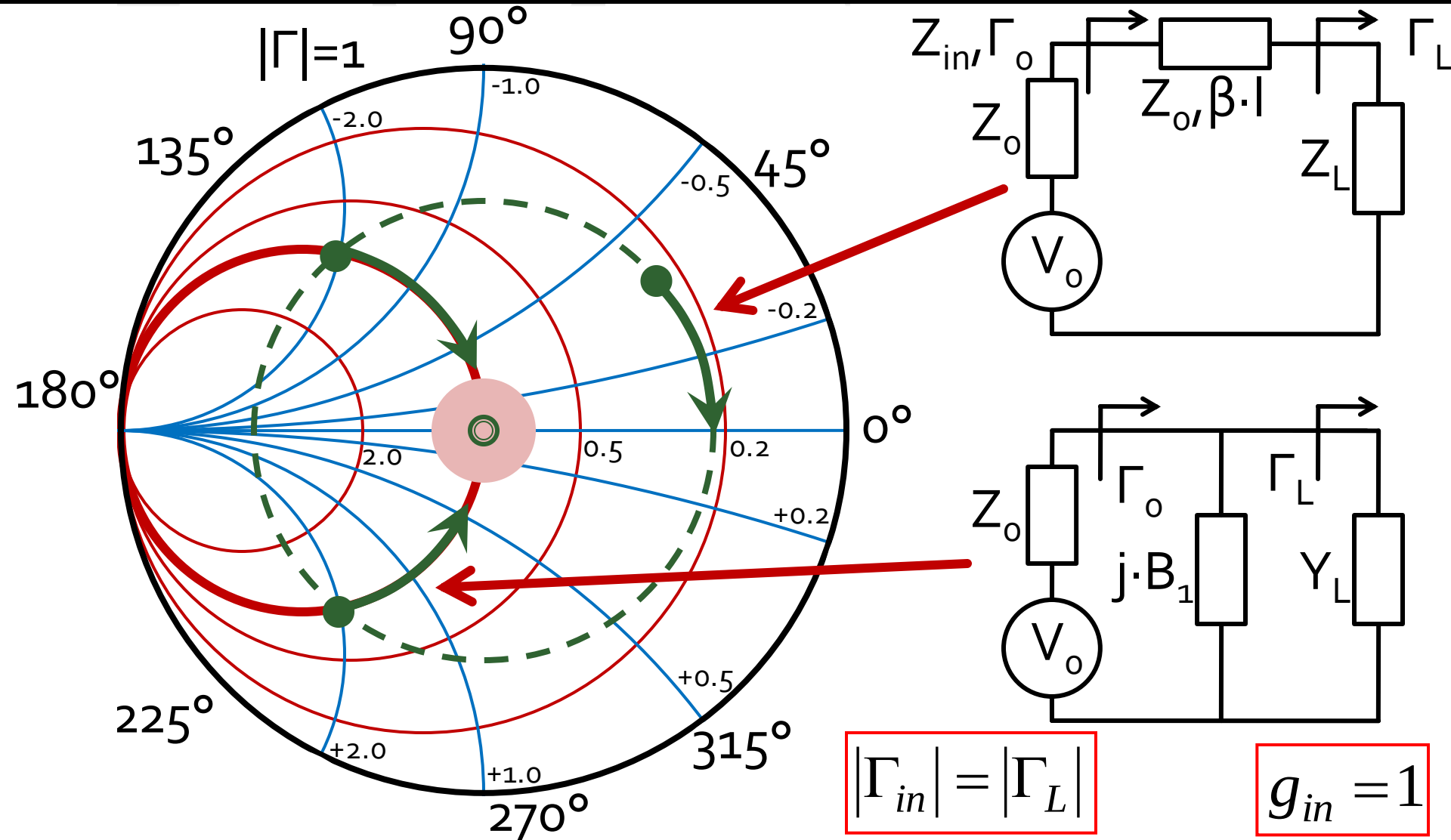

Analytical solution (Γ_S)

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = 0.867 \angle -117.7^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.867; \quad \varphi = -117.7^\circ \quad \cos(\varphi + 2\theta) = -0.867 \Rightarrow (\varphi + 2\theta) = \pm 150.1^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **"+" solution**

$$(-117.7^\circ + 2\theta) = +150.1^\circ \quad \theta = 133.9^\circ \quad \text{Im } y_s = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -3.477$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_s) = -74^\circ (+180^\circ) \rightarrow \theta_{sp} = 106^\circ$$

- **"-" solution**

$$(-117.7^\circ + 2\theta) = -150.1^\circ \quad \theta = -16.2^\circ (+180^\circ) \rightarrow \theta = 163.8^\circ$$

$$\text{Im } y_s = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +3.477 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_s) = 74^\circ$$

Analytical solution (Γ_L)

$$\cos(\varphi + 2\theta) = -|\Gamma_L|$$

$$\Gamma_L = 0.686 \angle 176.7^\circ$$

$$|\Gamma_L| = 0.686; \quad \varphi = 176.7^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}}$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation
 - **“+” solution**
 - **“-” solution**

Analytical solution (Γ_L)

$$\cos(\varphi + 2\theta) = -|\Gamma_L|$$

$$\Gamma_L = 0.686 \angle 176.7^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}}$$

$$|\Gamma_L| = 0.686; \quad \varphi = 176.7^\circ \quad \cos(\varphi + 2\theta) = -0.686 \Rightarrow (\varphi + 2\theta) = \pm 133.3^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **"+" solution**

$$(176.7^\circ + 2\theta) = +133.3^\circ \quad \theta = -21.7^\circ (+180^\circ) \rightarrow \theta = 158.3^\circ$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_L) = -62.1^\circ (+180^\circ) \rightarrow \theta_{sp} = 117.9^\circ \quad \text{Im } y_L = \frac{-2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}} = -1.885$$

- **"-" solution**

$$(176.7^\circ + 2\theta) = -133.3^\circ \quad \theta = -155^\circ (+180^\circ) \rightarrow \theta = 25^\circ$$

$$\text{Im } y_L = \frac{+2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}} = +1.885 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_L) = 62.1^\circ$$

Complete analytical solution

- We choose **one** of the two possible solutions for the input matching


$$(\varphi + 2\theta) = \begin{cases} +150.1^\circ \\ -150.1^\circ \end{cases} \quad \theta = \begin{cases} 133.9^\circ \\ 163.8^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -3.477 \\ +3.477 \end{cases} \quad \theta_{sp} = \begin{cases} -74^\circ + 180^\circ = 106^\circ \\ +74^\circ \end{cases}$$

- Similarly for the output matching

$$(\varphi + 2\theta) = \begin{cases} +133.3^\circ \\ -133.3^\circ \end{cases} \quad \theta = \begin{cases} 158.3^\circ \\ 25.0^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -1.885 \\ +1.885 \end{cases} \quad \theta_{sp} = \begin{cases} 117.9^\circ \\ 62.1^\circ \end{cases}$$


- In total there are **4** possible solutions input/output

ADS

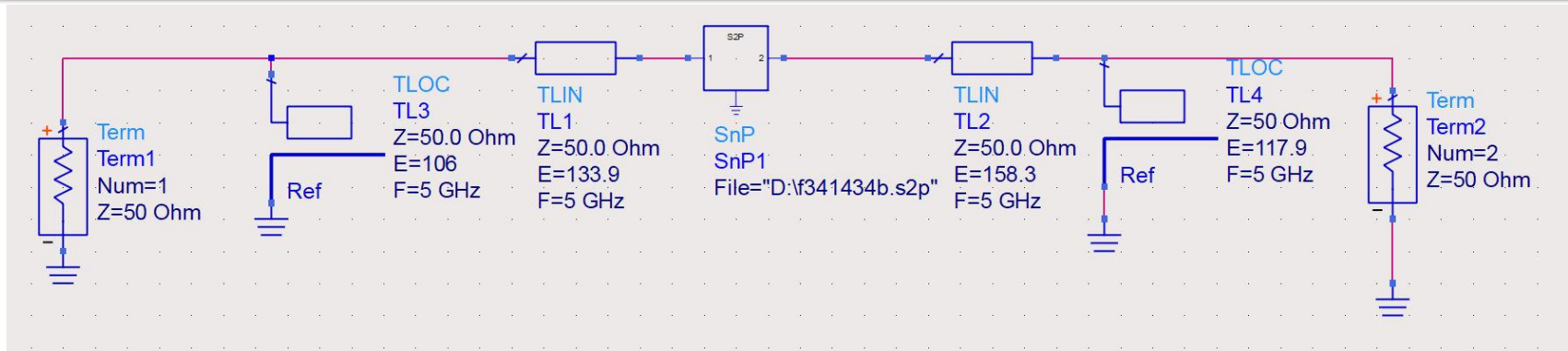



$$EqnGT=10*\log(\text{mag}(S(2,1))^2)$$

freq	S(2,1)	GT	S(1,1)	S(2,2)
5.000 GHz	4.415 / 157.353	12.900	0.004 / 86.088	0.004 / 37.766

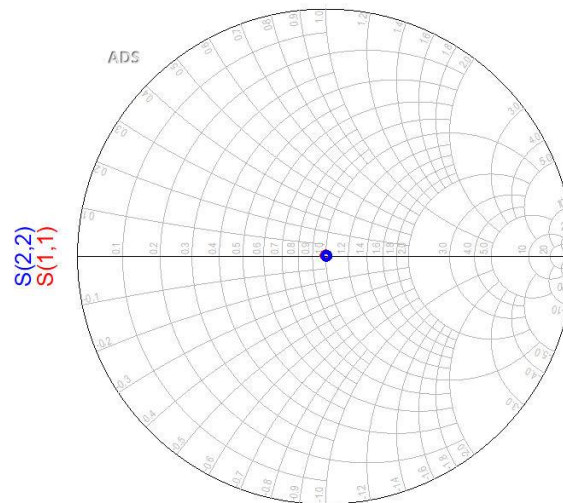

freq (5.000GHz to 5.000GHz)

ADS

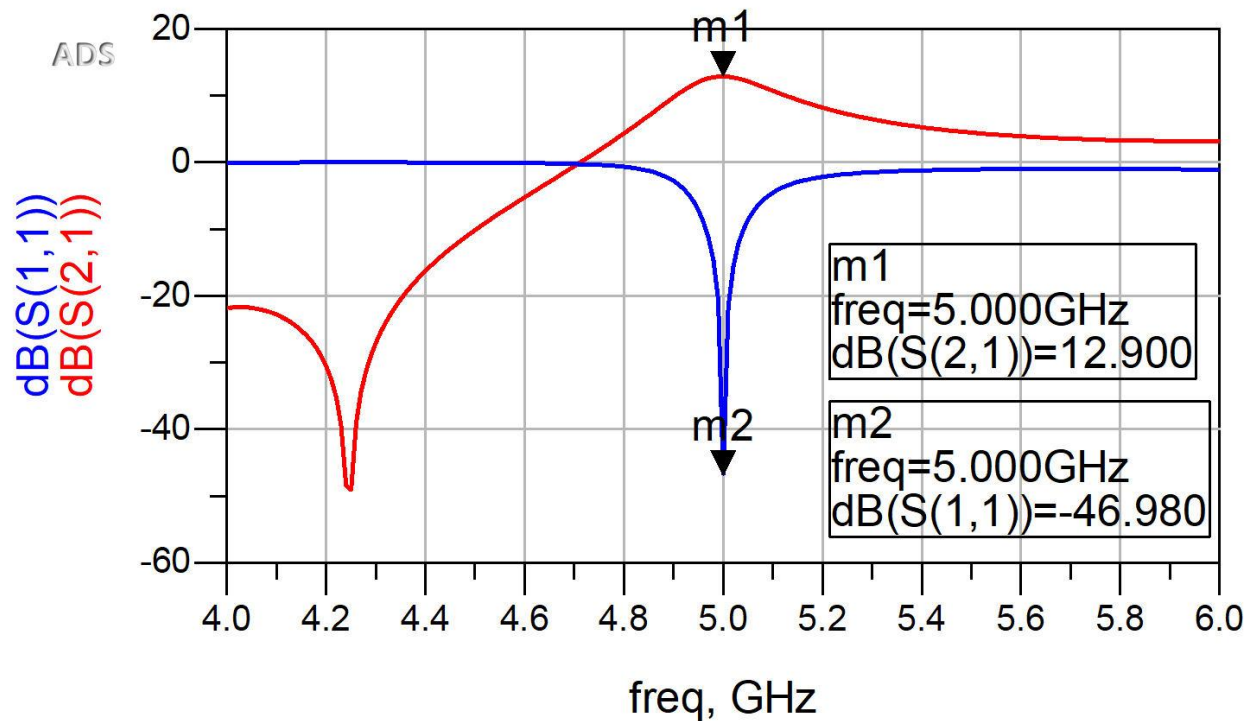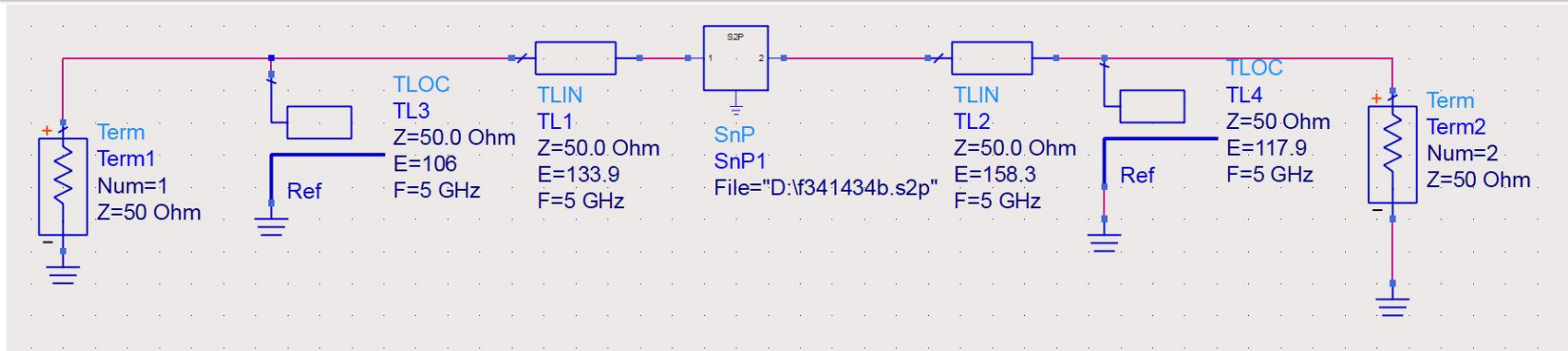

Preview (for laboratories 3-4)


Microwave Low Noise Amplifier

Proiectare pentru castig impus

- Deseori este necesara o alta abordare decat "forta bruta" si se prefera obtinerea unui **castig mai mic** decat cel maxim posibil pentru:
 - conditii de zgomot avantajoase (L_3)
 - conditii de stabilitate mai bune
 - obtinerea unui VSWR mai mic
 - controlul performantelor la mai multe frecvente
 - banda de functionare a amplificatorului


Amplificator de banda larga

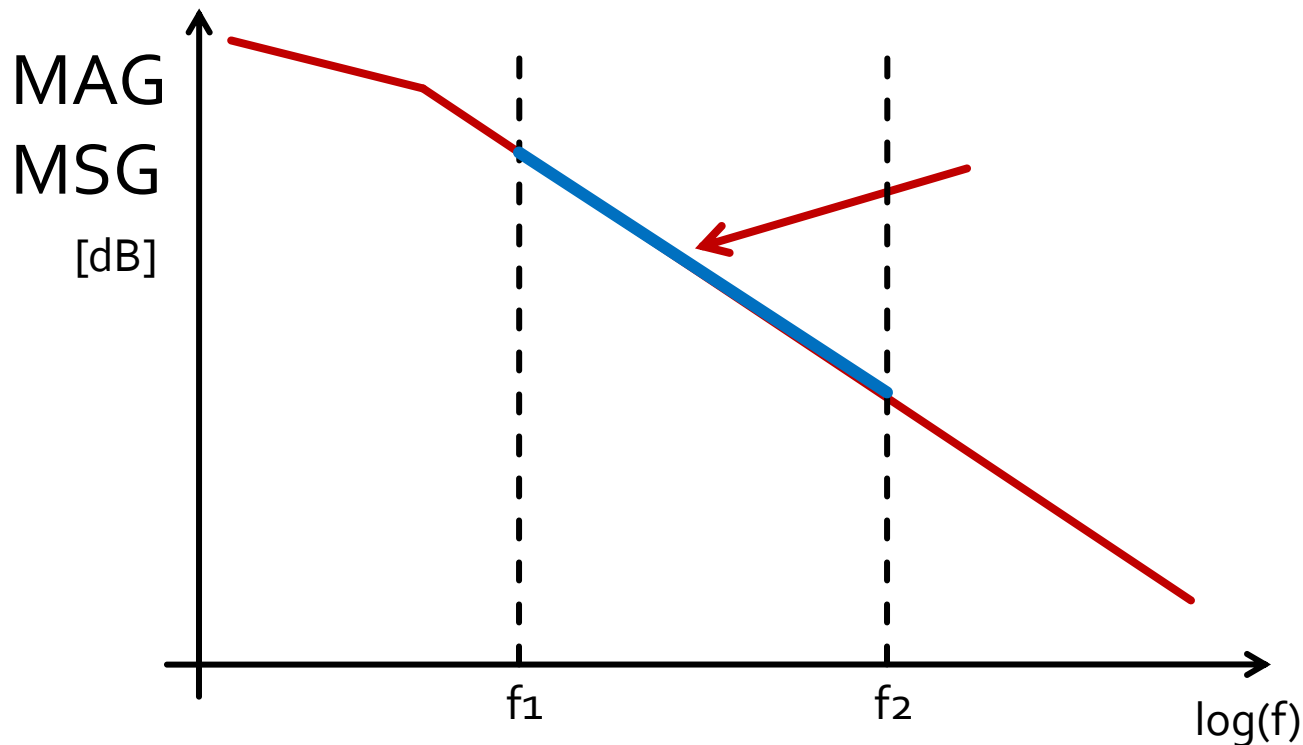- Adaptarea pentru castig maxim la doua frecvente genereaza o comportare dezechilibrata




Amplificator de banda larga

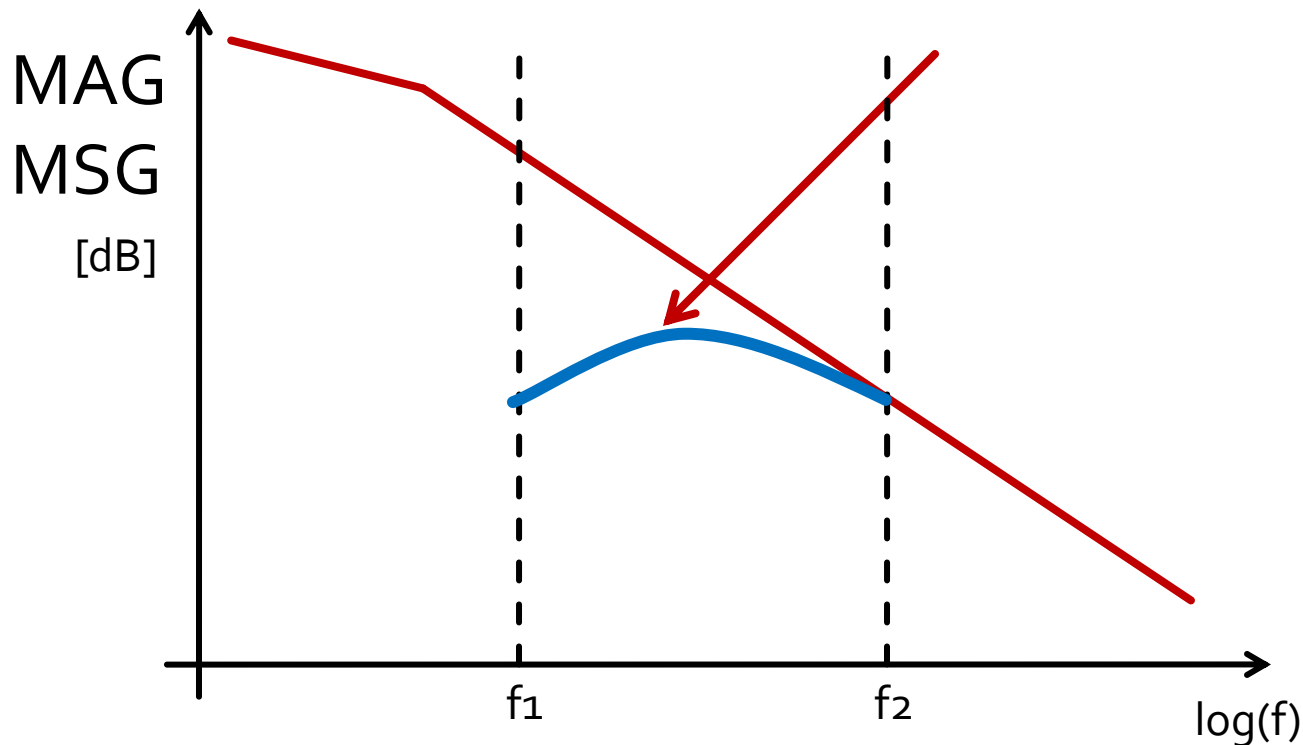- Adaptare pentru castig maxim la frecventa maxima
- Dezadaptare controlata la frecventa minima
 - eventual la mai multe frecvente din banda



Proiectare pentru castig impus

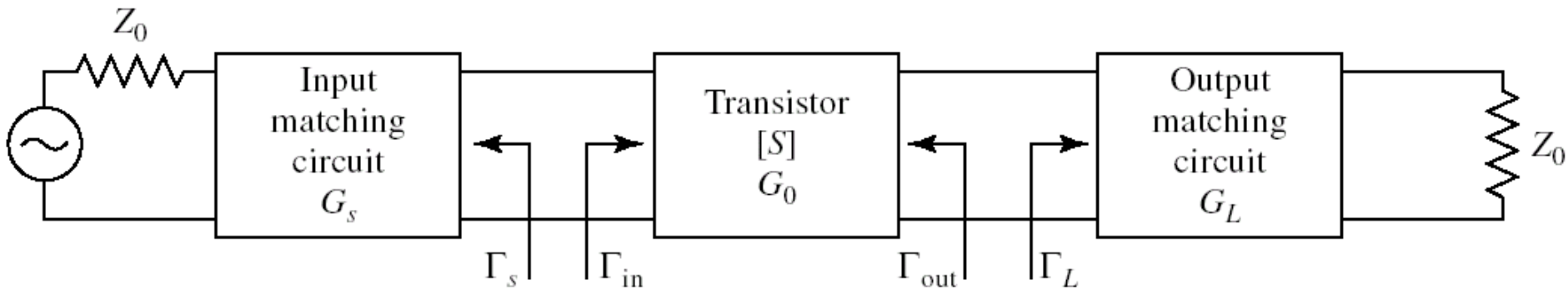

- Daca ipoteza tranzistorului unilateral este justificata:


$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_s|^2}{|1 - S_{11} \cdot \Gamma_s|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$G_s = \frac{1 - |\Gamma_s|^2}{|1 - S_{11} \cdot \Gamma_s|^2}$$

$$G_0 = |S_{21}|^2$$

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

Proiectare pentru castig impus

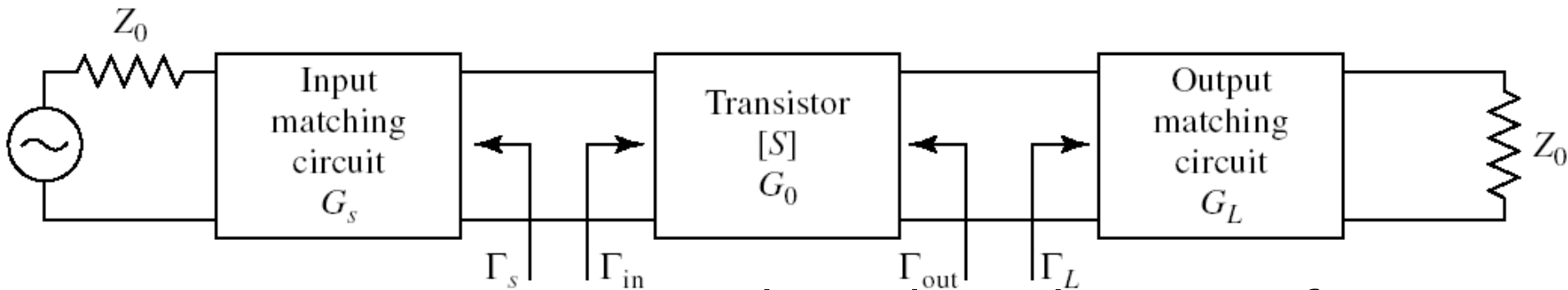


- Dacă ipoteza tranzistorului unilateral este justificată:
 - castigul adăugat prin adaptare mai bună la intrare **nu** depinde de adaptarea la ieșire
 - castigul adăugat prin adaptare mai bună la ieșire **nu** depinde de adaptarea la intrare
- Adaptările la intrare/ieșire pot fi tratate independente
 - Se pot impune cerințe diferite intrare/ieșire
 - se ține cont de compunerea câștigurilor generate

$$G_T = G_S \cdot G_0 \cdot G_L$$


$$G_T[dB] = G_S[dB] + G_0[dB] + G_L[dB]$$

$G_S(\Gamma_S)$

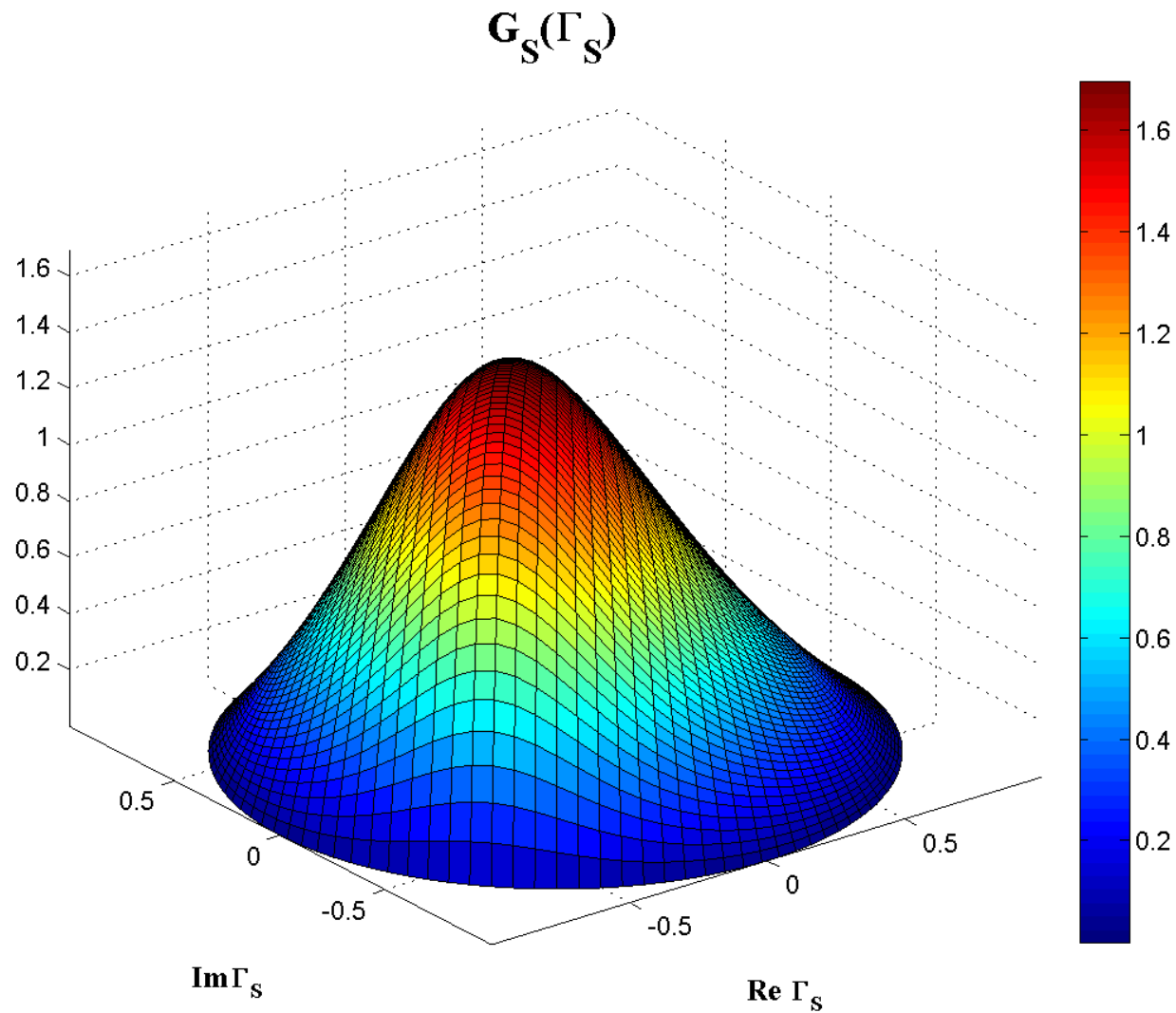


$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2}$$

$G_S(\Gamma_S)$, nivel constant

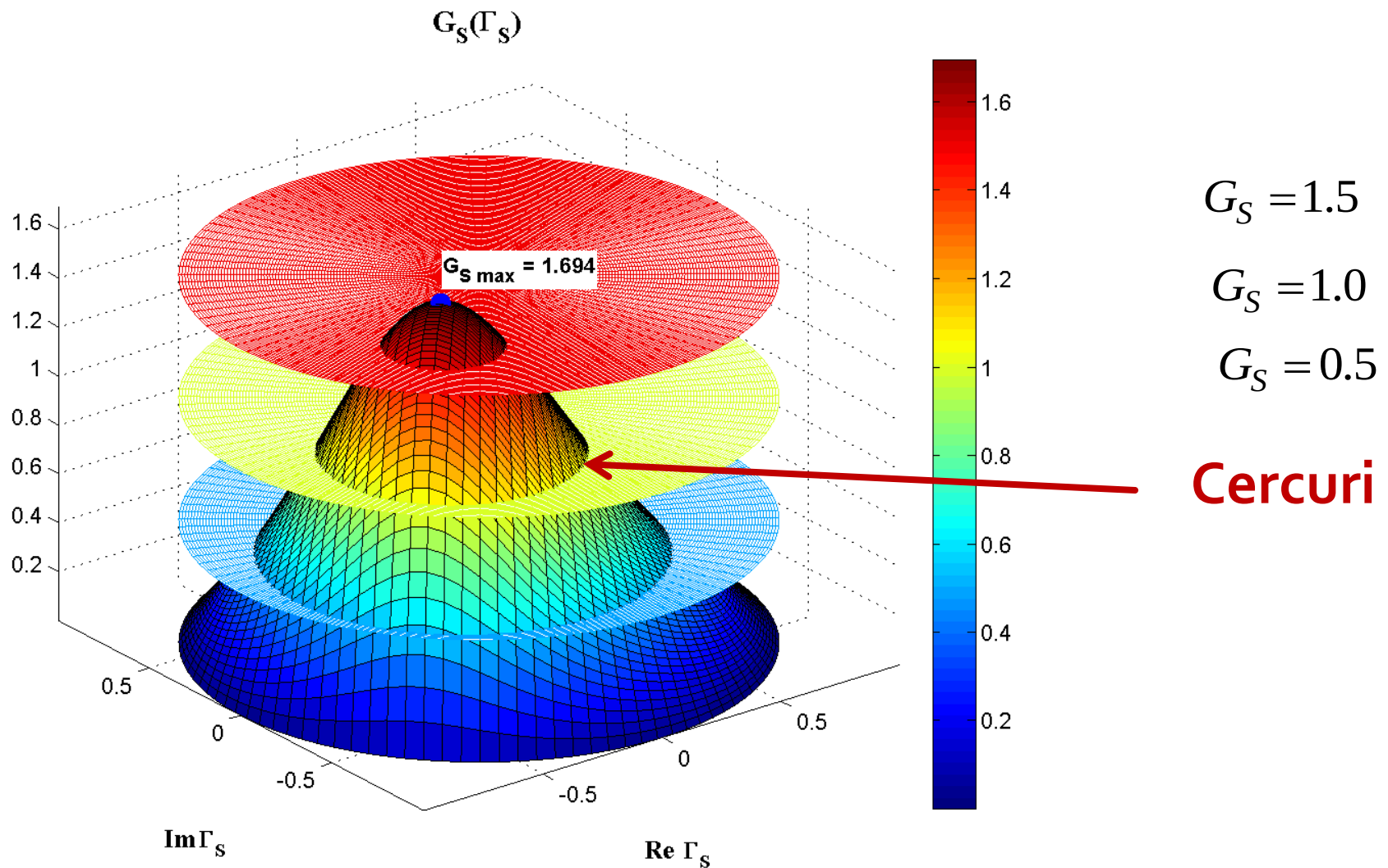


$G_S(\Gamma_S)$, diagrama de nível

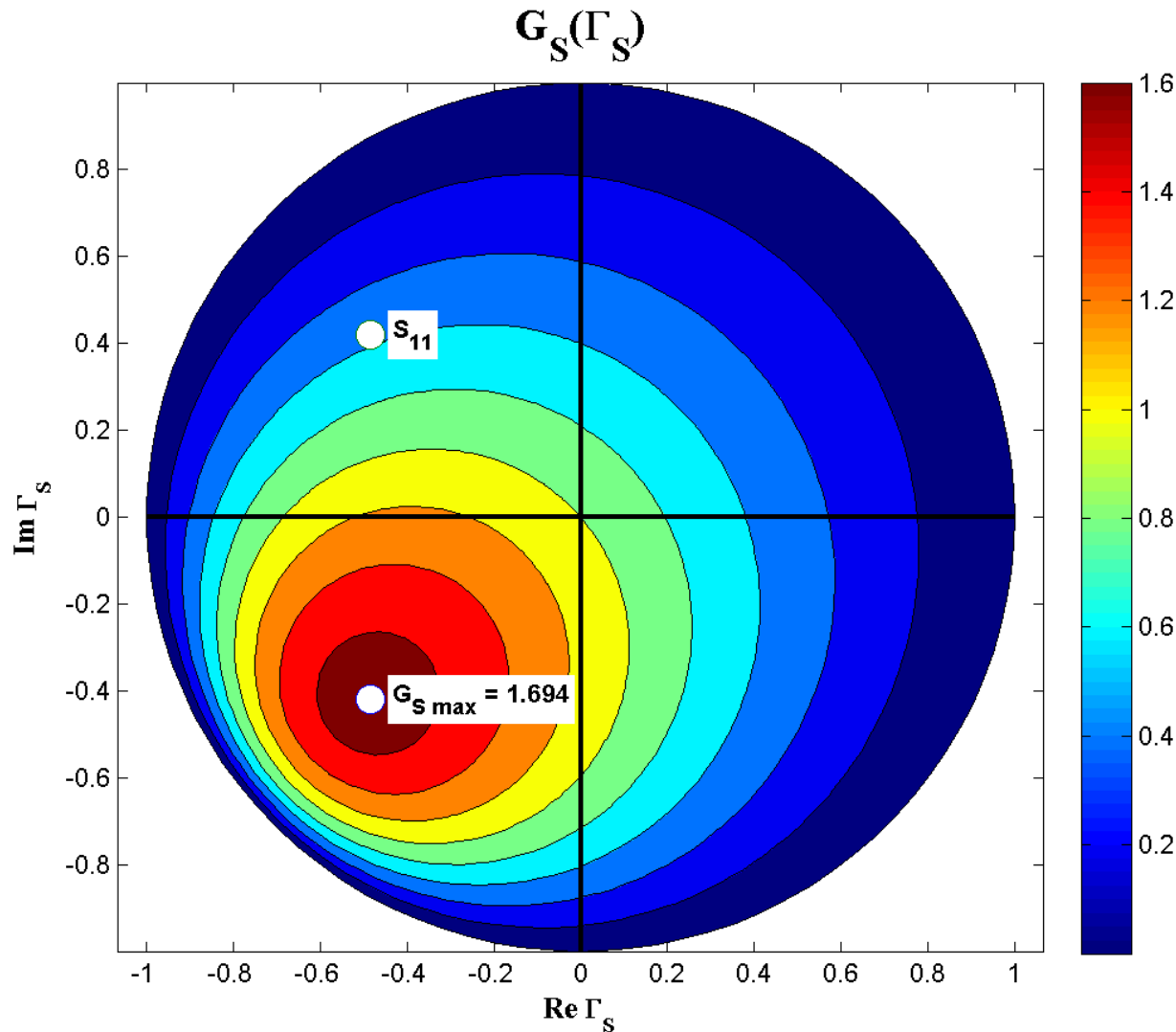

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2}$$

$$G_{S \max} = G_S|_{\Gamma_S = S_{11}^*}$$

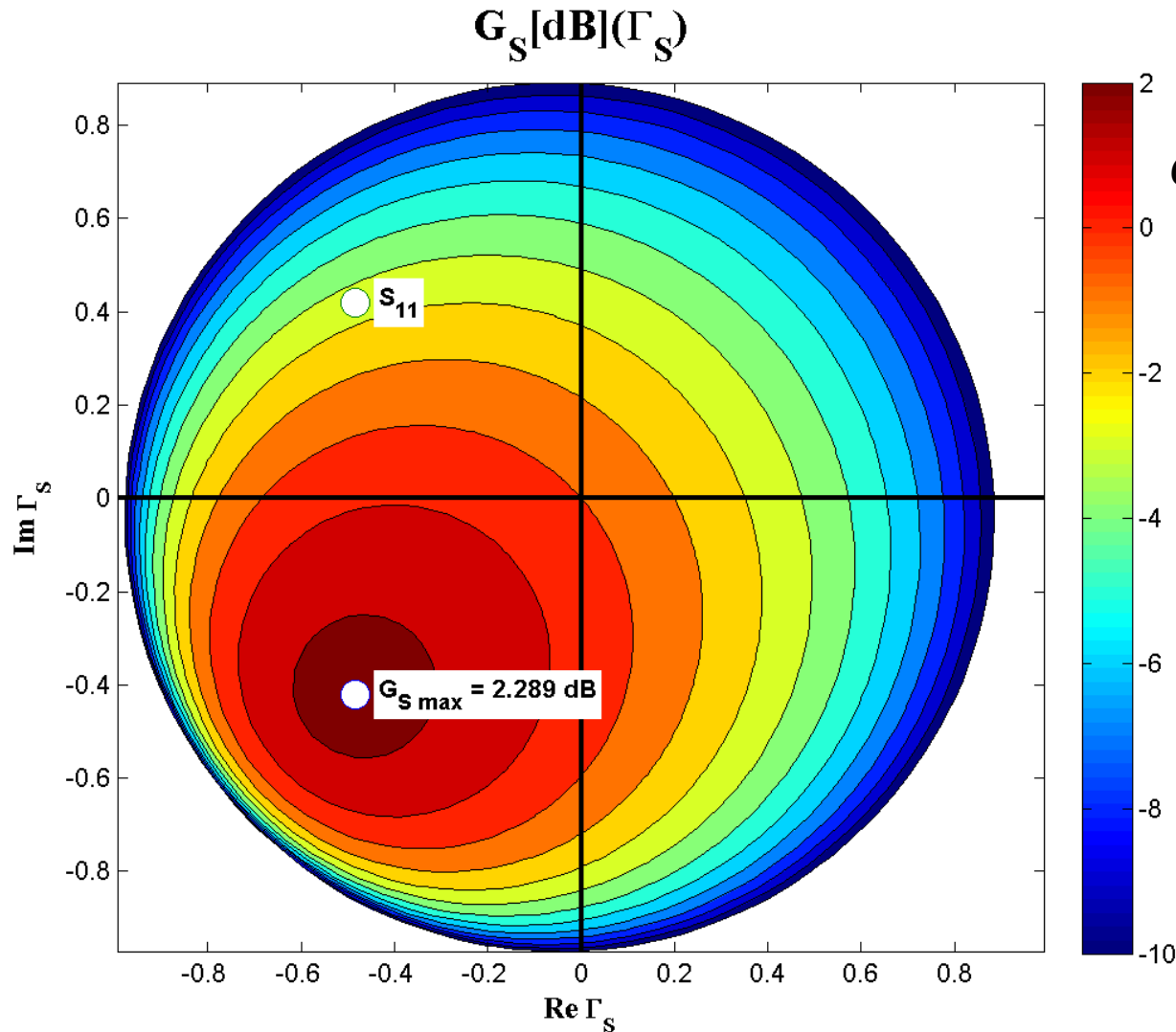$G_S[\text{dB}](\Gamma_S)$, diagrama de nivel



$$G_S[\text{dB}] = 10 \cdot \log \left(\frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \right)$$



$$G_{S \max} = G_S|_{\Gamma_S = S_{11}^*}$$

Cercuri de castig constant la intrare

$$\left| \Gamma_S - \frac{g_S \cdot S_{11}^*}{1 - (1 - g_S) \cdot |S_{11}|^2} \right| = \frac{\sqrt{1 - g_S} \cdot (1 - |S_{11}|^2)}{1 - (1 - g_S) \cdot |S_{11}|^2} \quad |\Gamma_S - C_S| = R_S$$
$$C_S = \frac{g_S \cdot S_{11}^*}{1 - (1 - g_S) \cdot |S_{11}|^2} \quad R_S = \frac{\sqrt{1 - g_S} \cdot (1 - |S_{11}|^2)}{1 - (1 - g_S) \cdot |S_{11}|^2}$$


- Ecuatia unui cerc in planul complex in care reprezinta Γ_S
- **Interpretare:** Orice punct Γ_S care este reprezentat in planul complex se gaseste **pe** cercul desenat pentru $g_{\text{cerc}} = G_{\text{cerc}}/G_{\text{Smax}}$ va conduce la obtinerea castigului $G_S = G_{\text{cerc}}$
 - Orice punct **in exteriorul** acestui cerc va genera un castig $G_S < G_{\text{cerc}}$
 - Orice punct **in interiorul** acestui cerc va genera un castig $G_S > G_{\text{cerc}}$
- Discutie similara la iesire **CCIN, CCOUT**

CCCIN, CCCOUT

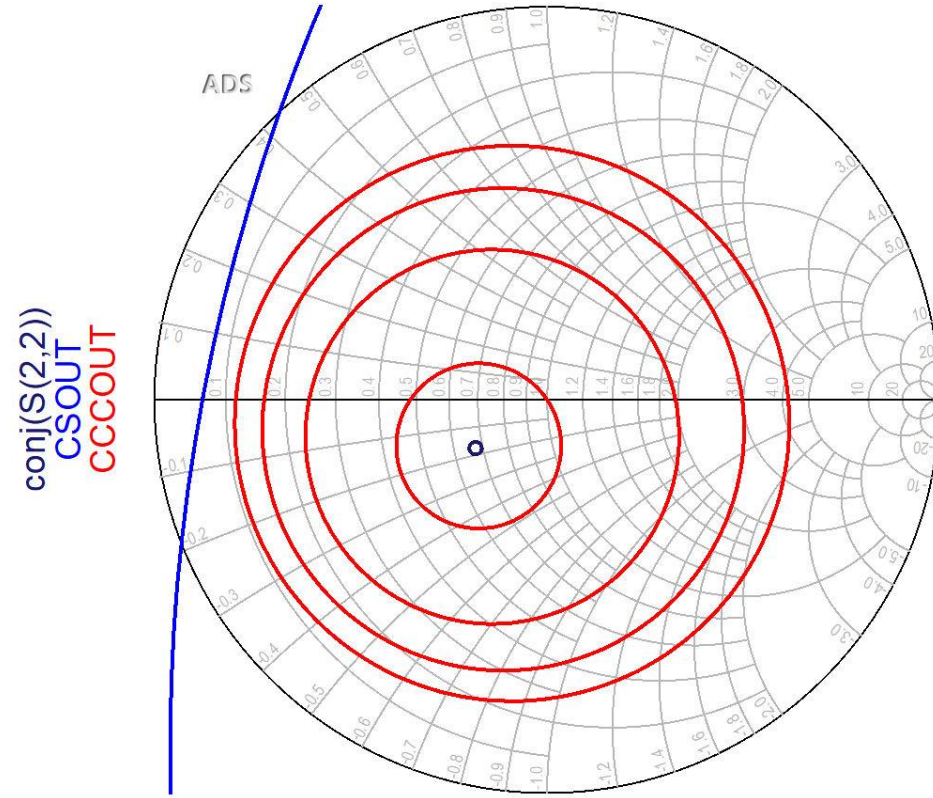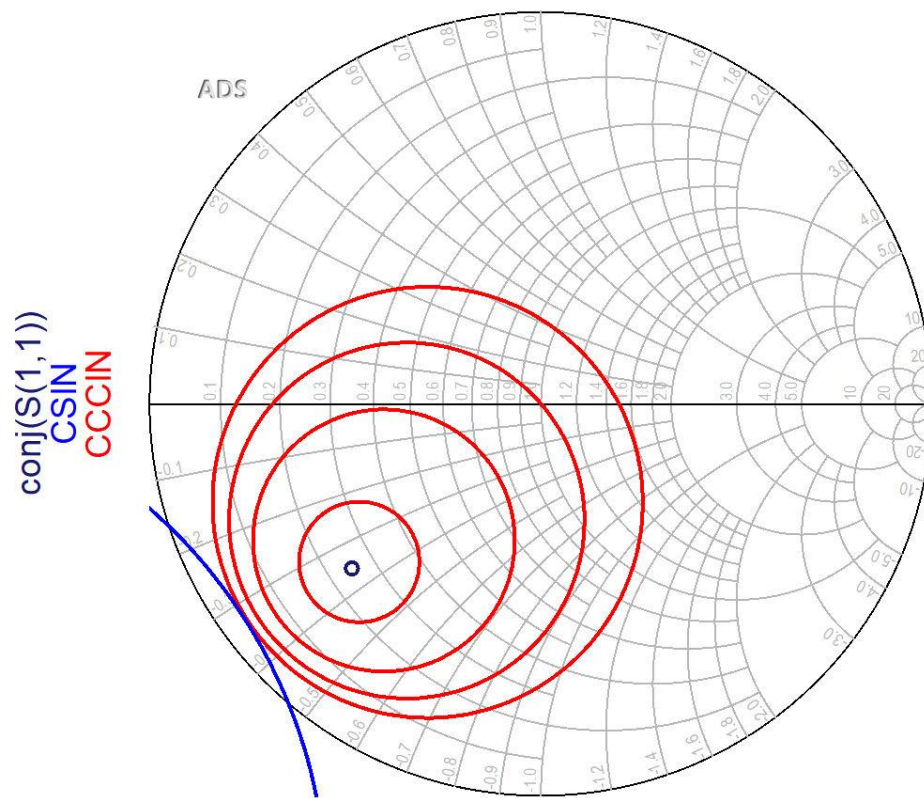

- Cercurile se reprezinta pentru valorile cerute in dB
- Este utila calcularea $G_{S_{\max}}$ si $G_{L_{\max}}$ anterior


Factor de zgomot

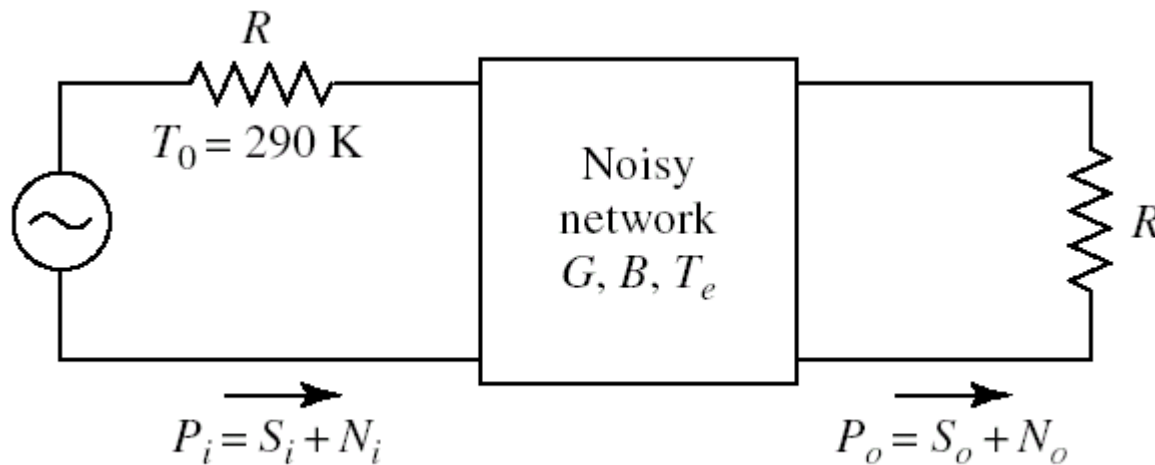


- Factorul de zgomot F caracterizeaza degradarea raportului semnal/zgomot între intrarea și ieșirea unei componente

$$F = \frac{S_i/N_i}{S_o/N_o}$$


$F(\Gamma_s)$

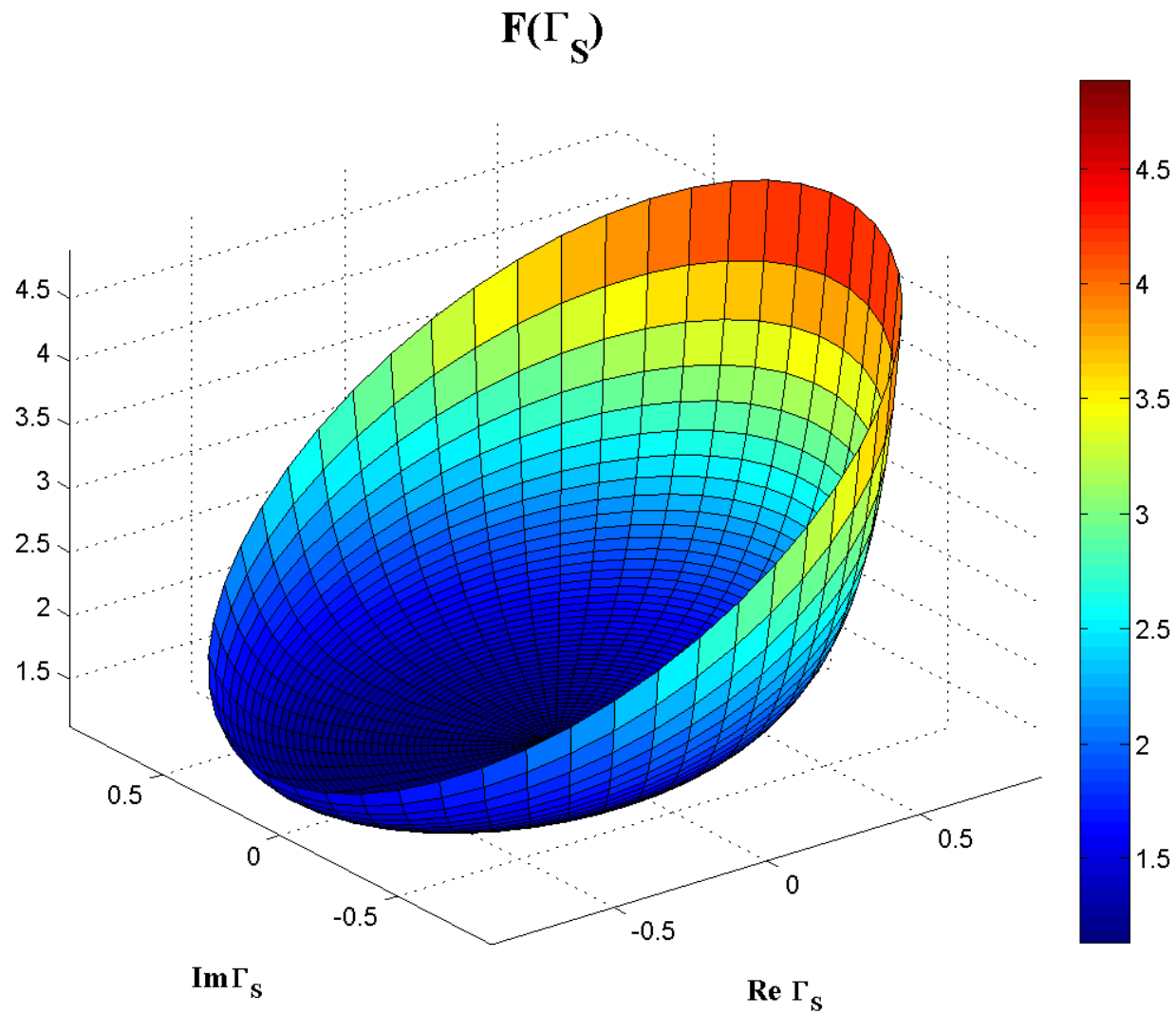


$F[\text{dB}](\Gamma_s)$

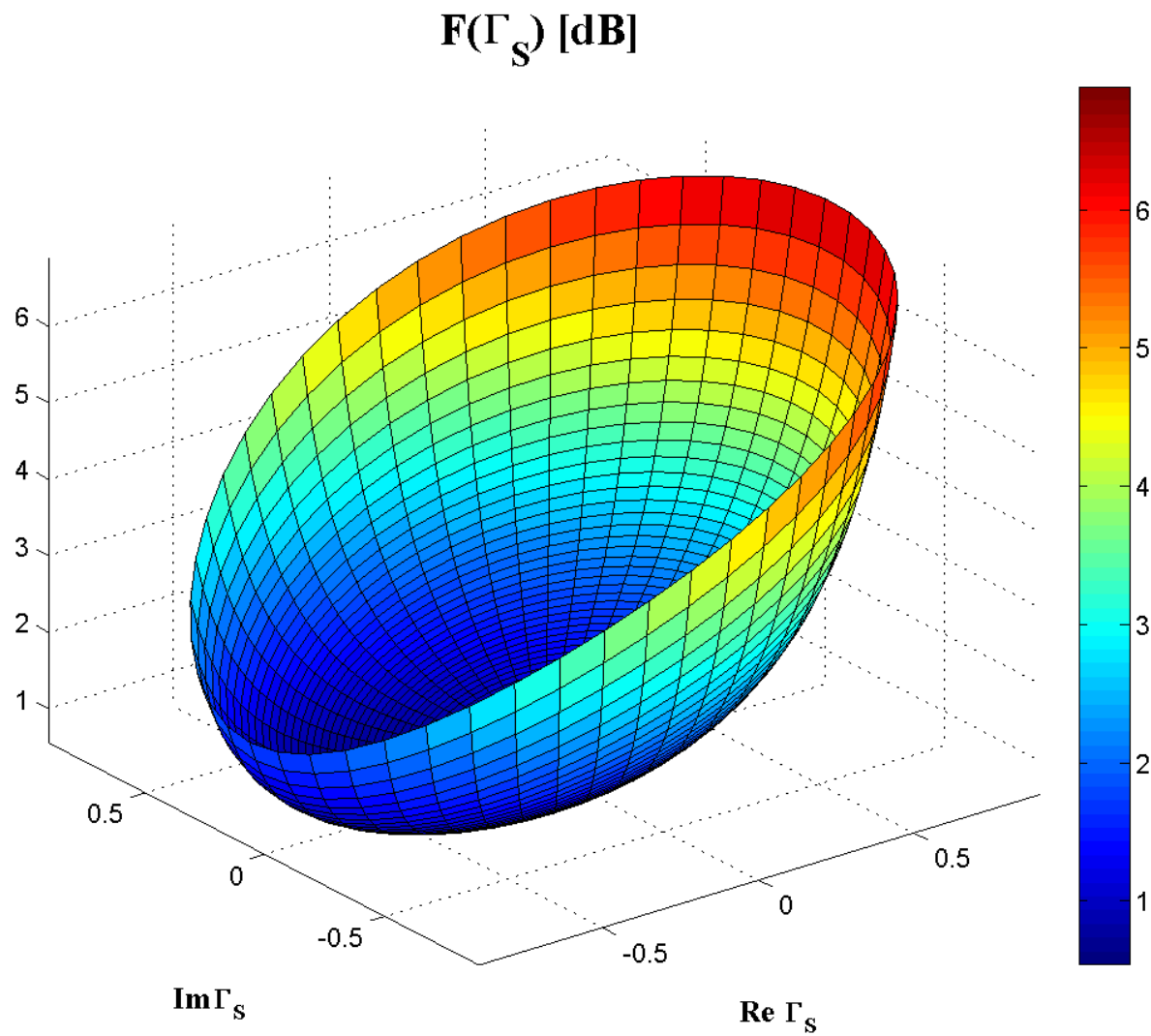

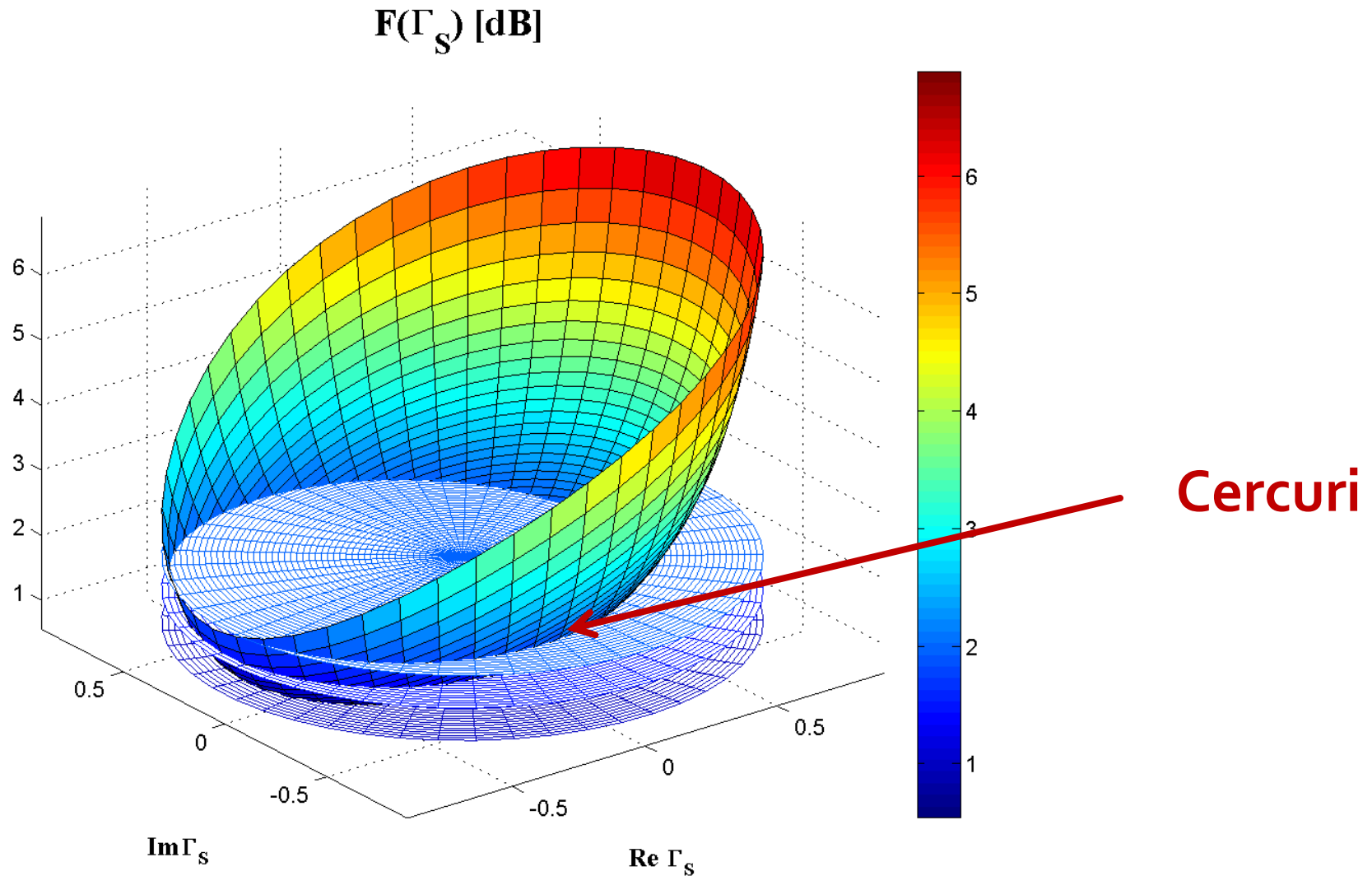$F[\text{dB}](\Gamma_s)$, diagrama de nivel




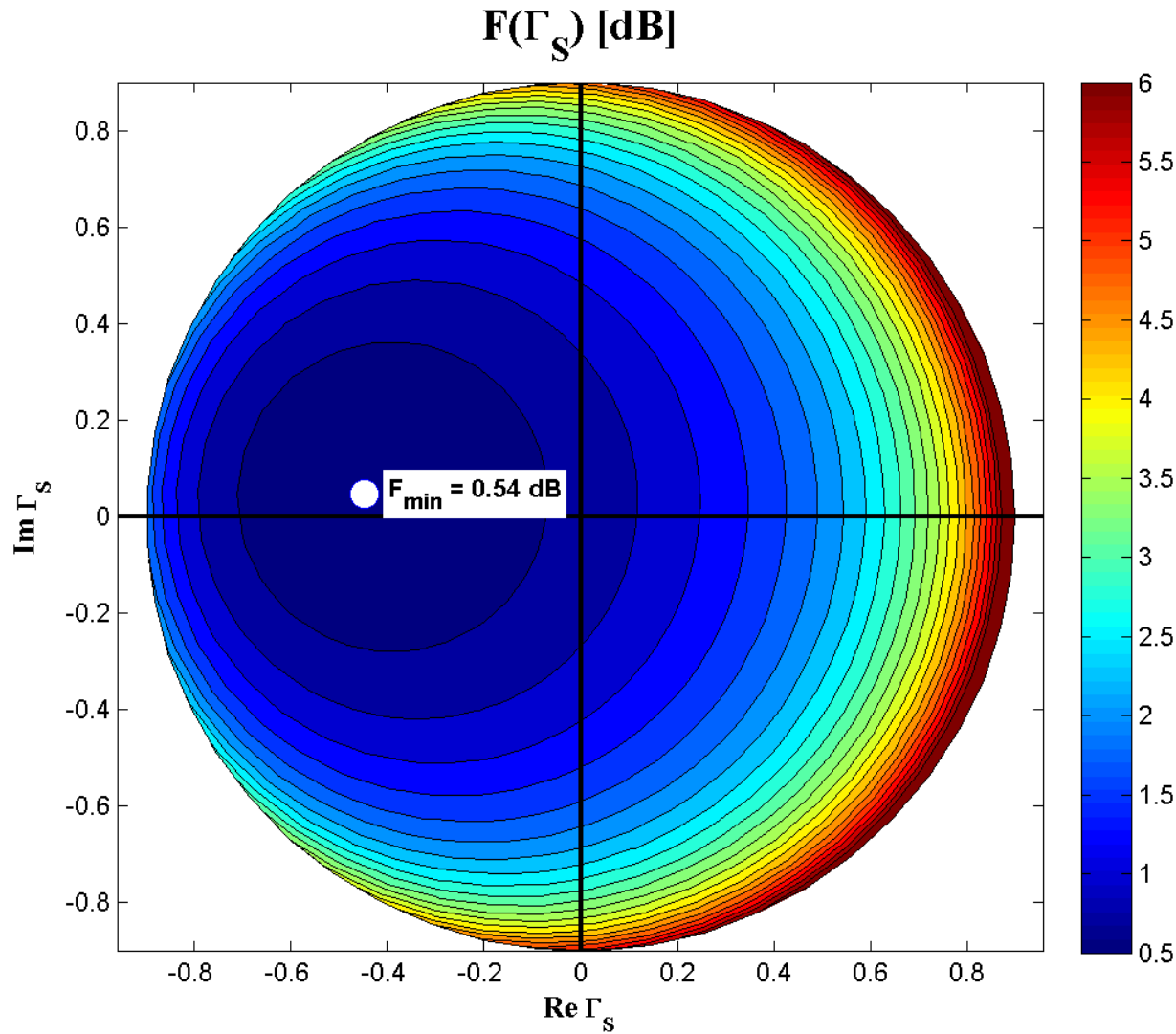$G_s[\text{dB}](\Gamma_s)$, diagrama de nivel



$$\Gamma_{\text{opt}} = 0.45 \angle 174^\circ$$


CZ – numai la intrare !

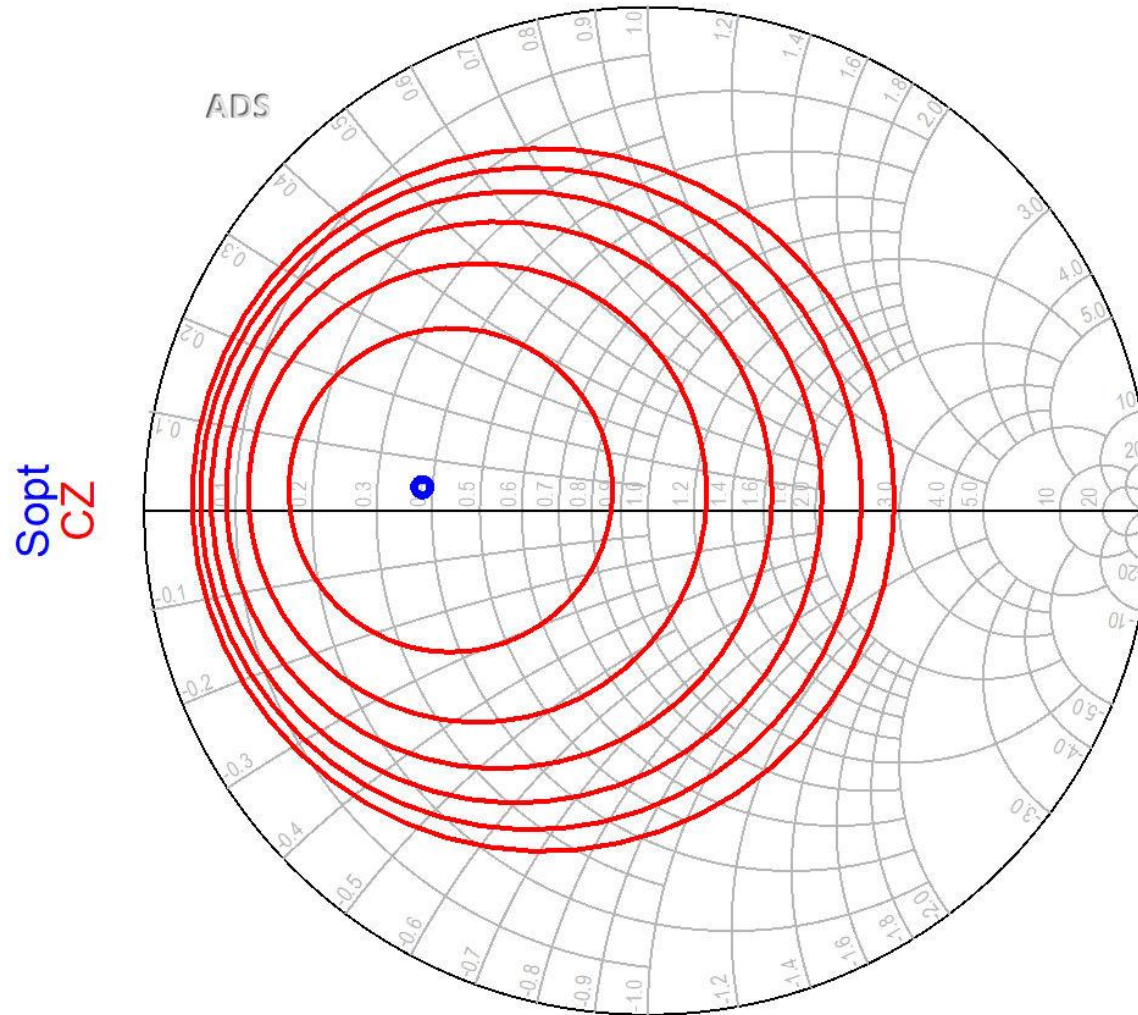

Exemplu, LNA @ 5 GHz


- Amplificator de zgomot redus
- La intrare e necesar un compromis intre
 - zgomot (cerc de zgomot constant **la intrare**)
 - castig (cerc de castig constant la intrare)
 - stabilitate (cerc de stabilitate la intrare)
- La iesire zgomotul **nu intervine** (nu exista influenta). Compromis intre:
 - castig (cerc de castig constant la iesire)
 - stabilitate (cerc de stabilitate la iesire)

Adaptare la intrare

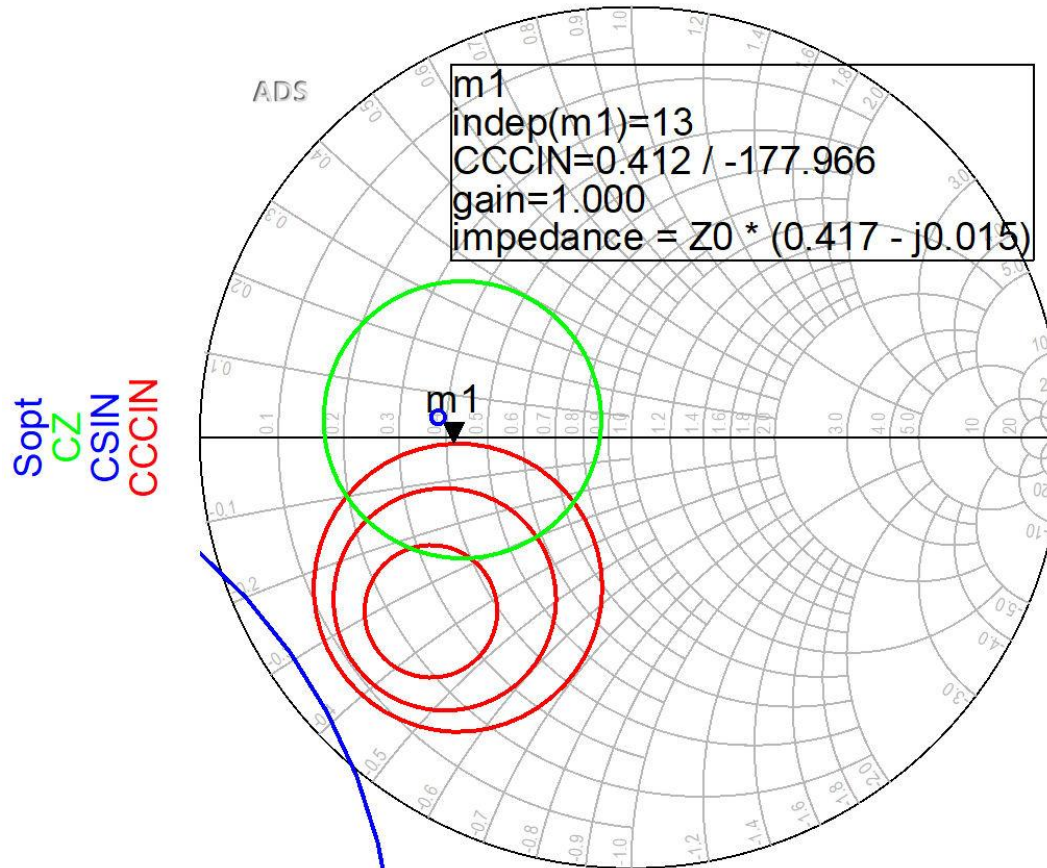

- Daca se sacrifica 1.2dB castig la intrare pentru conditii convenabile F,Q ($G_s = 1$ dB)
- Se prefera obtinerea unui zgomot mai mic


Adaptare la iesire

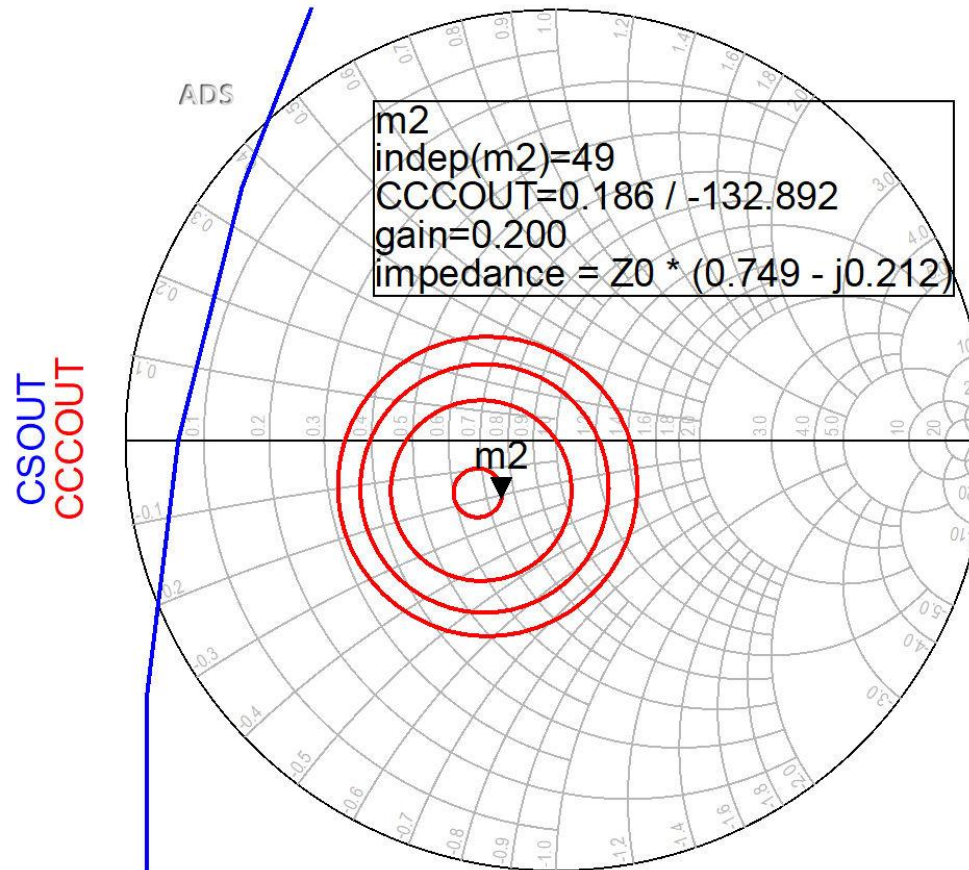

- CCCOUT: -0.4dB, -0.2dB, 0dB, +0.2dB
- Lipsa conditiilor privitoare la zgomot ofera posibilitatea obtinerii unui castig mai mare (spre maxim)

LNA

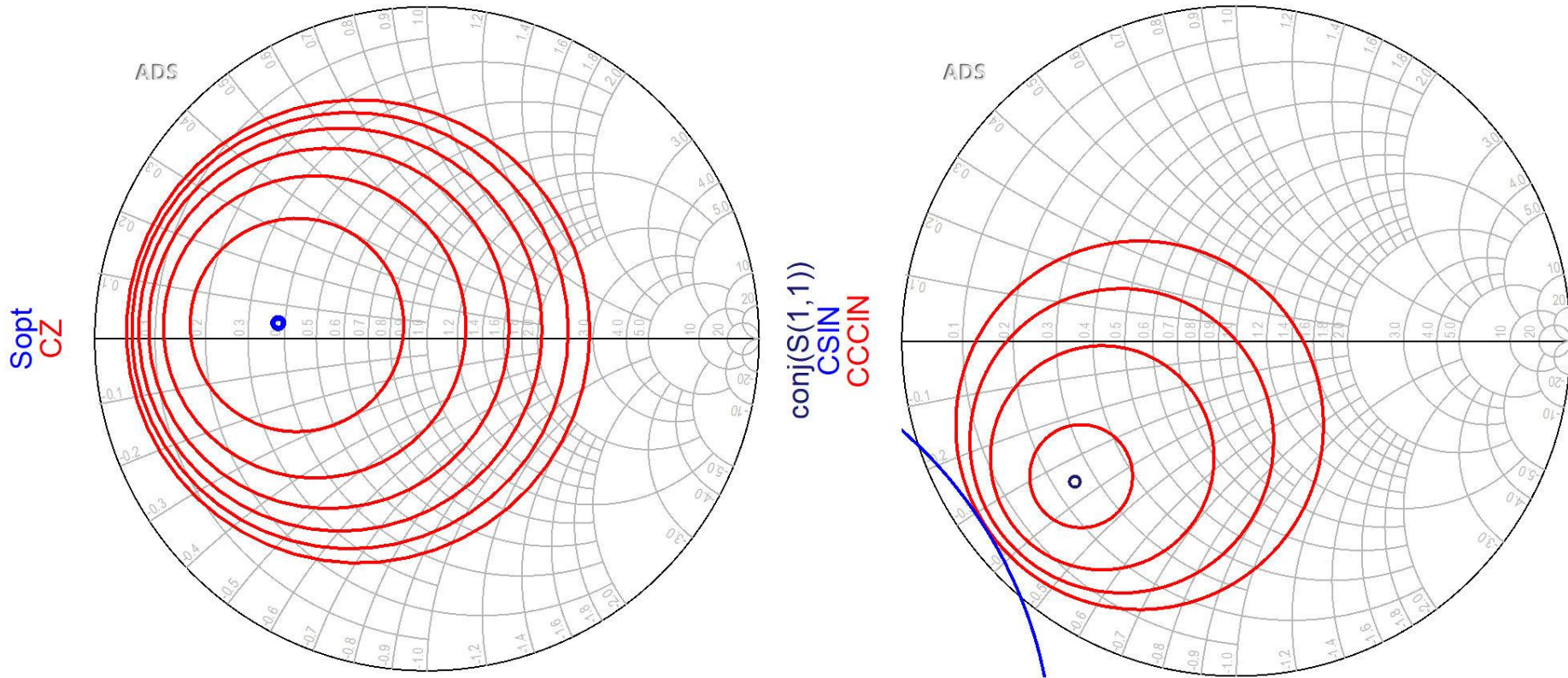- De obicei un tranzistor potrivit pentru implementarea unui LNA la o anumita frecventa va avea cercurile de castig la intrare si cercurile de zgomot in aceeasi zona pentru Γ_S



Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.etti.tuiasi.ro>
- rdamian@etti.tuiasi.ro