

Lecture 8

2018/2019

Microwave Devices and Circuits for Radiocommunications

2018/2019

- 2C/1L, **MDCR**
- Attendance at minimum 7 sessions (course + laboratory)
- Lectures- **associate professor Radu Damian**
 - Friday 09-11, Il.13
 - E – 50% final grade
 - problems + (2p atten. lect.) + (**3 tests**) + (bonus activity)
 - 3p=+0.5p
 - all materials/equipments authorized
- Laboratory – **associate professor Radu Damian**
 - Wednesday 12-14, Il.12 odd weeks
 - L – 25% final grade
 - P – 25% final grade

Materials

■ <http://rf-opto.etti.tuiasi.ro>

Laboratorul de Microunde și Opto X

Not secure | rf-opto.etti.tuiasi.ro/microwave_cd.php?chg_lang=0

Main **Courses** Master Staff Research Students Admin

Microwave CD Optical Communications Optoelectronics Internet Antennas Practica Networks Educational software

Microwave Devices and Circuits for Radiocommunications (English)

Course: MDCR (2017-2018)

Course Coordinator: Assoc.P. Dr. Radu-Florin Damian
Code: EDOS412T
Discipline Type: DOS; Alternative, Specialty
Credits: 4
Enrollment Year: 4, **Sem.** 7

Activities

Course: Instructor: Assoc.P. Dr. Radu-Florin Damian, 2 Hours/Week, Specialization Section, Timetable:
Laboratory: Instructor: Assoc.P. Dr. Radu-Florin Damian, 1 Hours/Week, Group, Timetable:

Evaluation

Type: **Examen**

A: 50%, (Test/Colloquium)
B: 25%, (Seminary/Laboratory/Project Activity)
D: 25%, (Homework/Specialty papers)

Grades

[Aggregate Results](#)

Attendance

[Course](#)
[Laboratory](#)

Lists

[Bonus-uri acumulate \(final\)](#)
[Studenti care nu pot intra in examen](#)

Materials

Course Slides

[MDCR Lecture 1](#) (pdf, 5.43 MB, en, [99](#))
[MDCR Lecture 2](#) (pdf, 3.67 MB, en, [99](#))
[MDCR Lecture 3](#) (pdf, 4.76 MB, en, [99](#))
[MDCR Lecture 4](#) (pdf, 5.58 MB, en, [99](#))

Examen: Logarithmic scales

$$\text{dB} = 10 \cdot \log_{10} (P_2 / P_1)$$

$$0 \text{ dB} = 1$$

$$+ 0.1 \text{ dB} = 1.023 (+2.3\%)$$

$$+ 3 \text{ dB} = 2$$

$$+ 5 \text{ dB} = 3$$

$$+ 10 \text{ dB} = 10$$

$$-3 \text{ dB} = 0.5$$

$$-10 \text{ dB} = 0.1$$

$$-20 \text{ dB} = 0.01$$

$$-30 \text{ dB} = 0.001$$

$$\text{dBm} = 10 \cdot \log_{10} (P / 1 \text{ mW})$$

$$0 \text{ dBm} = 1 \text{ mW}$$

$$3 \text{ dBm} = 2 \text{ mW}$$

$$5 \text{ dBm} = 3 \text{ mW}$$

$$10 \text{ dBm} = 10 \text{ mW}$$

$$20 \text{ dBm} = 100 \text{ mW}$$

$$-3 \text{ dBm} = 0.5 \text{ mW}$$

$$-10 \text{ dBm} = 100 \mu\text{W}$$

$$-30 \text{ dBm} = 1 \mu\text{W}$$

$$-60 \text{ dBm} = 1 \text{ nW}$$

$$[\text{dBm}] + [\text{dB}] = [\text{dBm}]$$

$$[\text{dBm/Hz}] + [\text{dB}] = [\text{dBm/Hz}]$$

$$[x] + [\text{dB}] = [x]$$

Examen

- Complex numbers arithmetic!!!!
- $z = a + j \cdot b ; j^2 = -1$

Impedance Matching

Matching , from the point of view of power transmission


$$Z_L = Z_i^*$$

If we choose a real Z_0

$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

$$\Gamma_L = \Gamma_i^*$$

- complex numbers
- in the complex plane

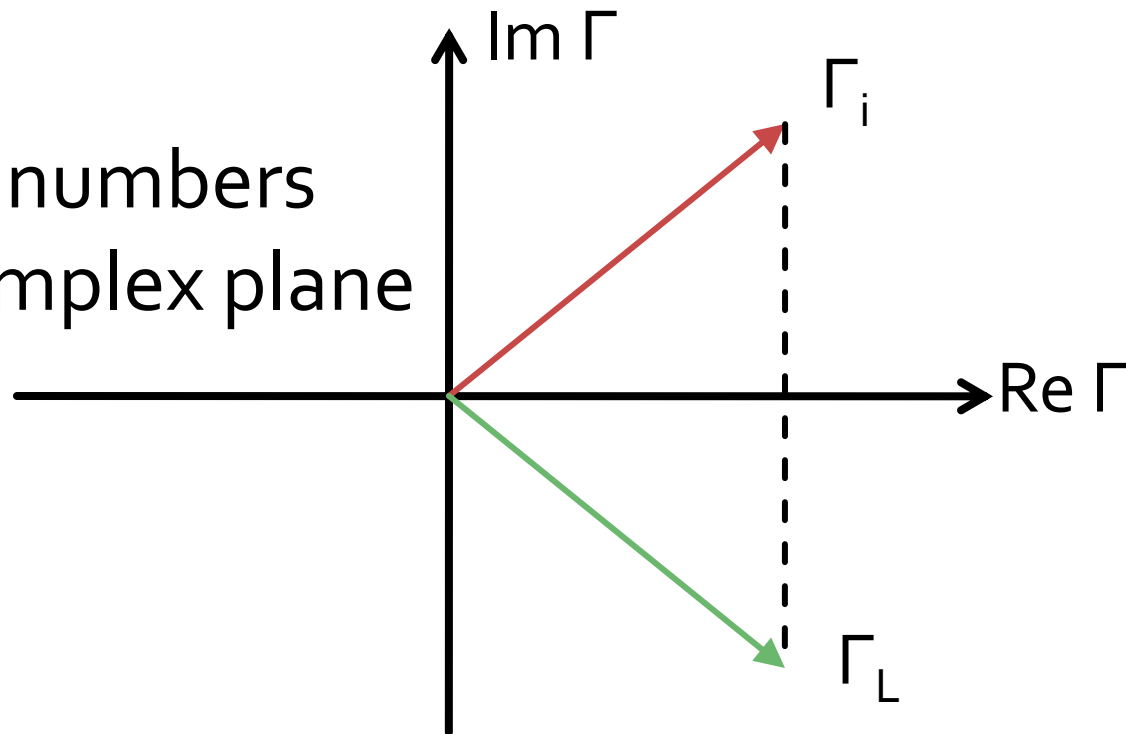


Lecture 3-4

Microwave Network Analysis

Scattering matrix – S

- Scattering parameters

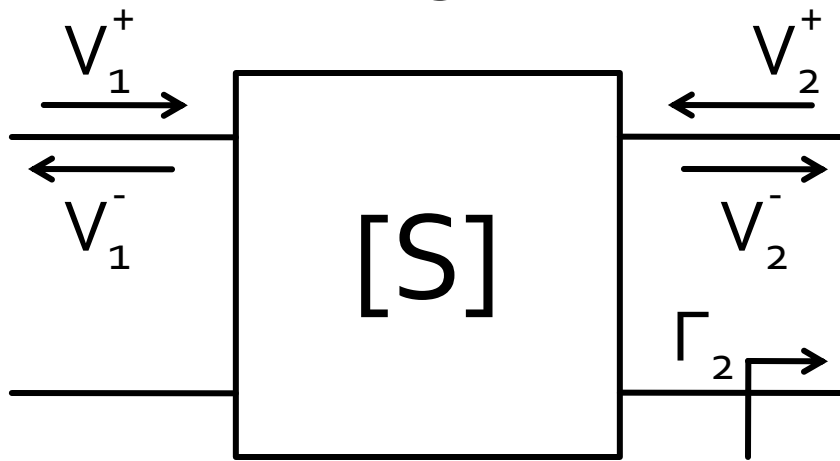


$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0}$$

- $V_2^+ = 0$ meaning: port 2 is terminated in matched load to avoid reflections towards the port

$$\Gamma_2 = 0 \rightarrow V_2^+ = 0$$

Scattering matrix – S

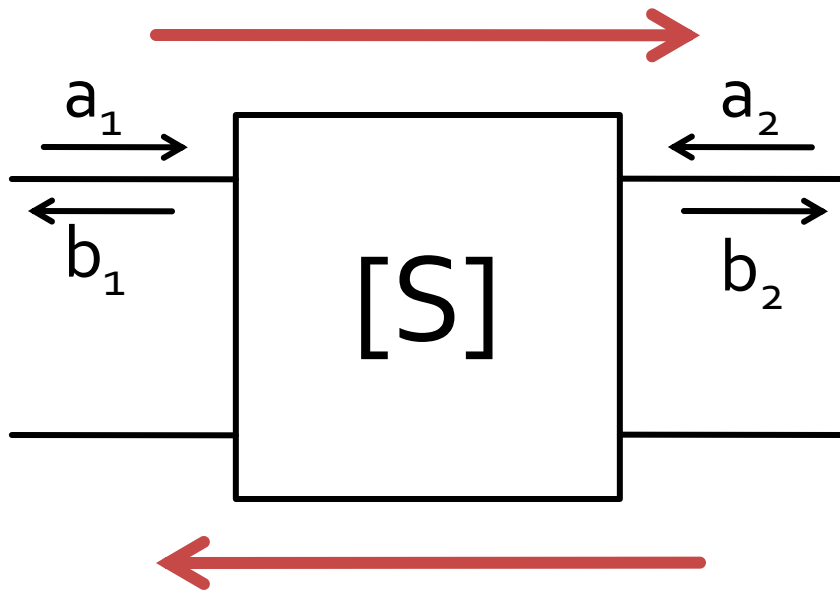

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$


$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- a, b
 - information about signal power **AND** signal phase
- S_{ij}
 - network effect (gain) over signal power **including** phase information


Impedance Matching

The Smith Chart

The Smith Chart

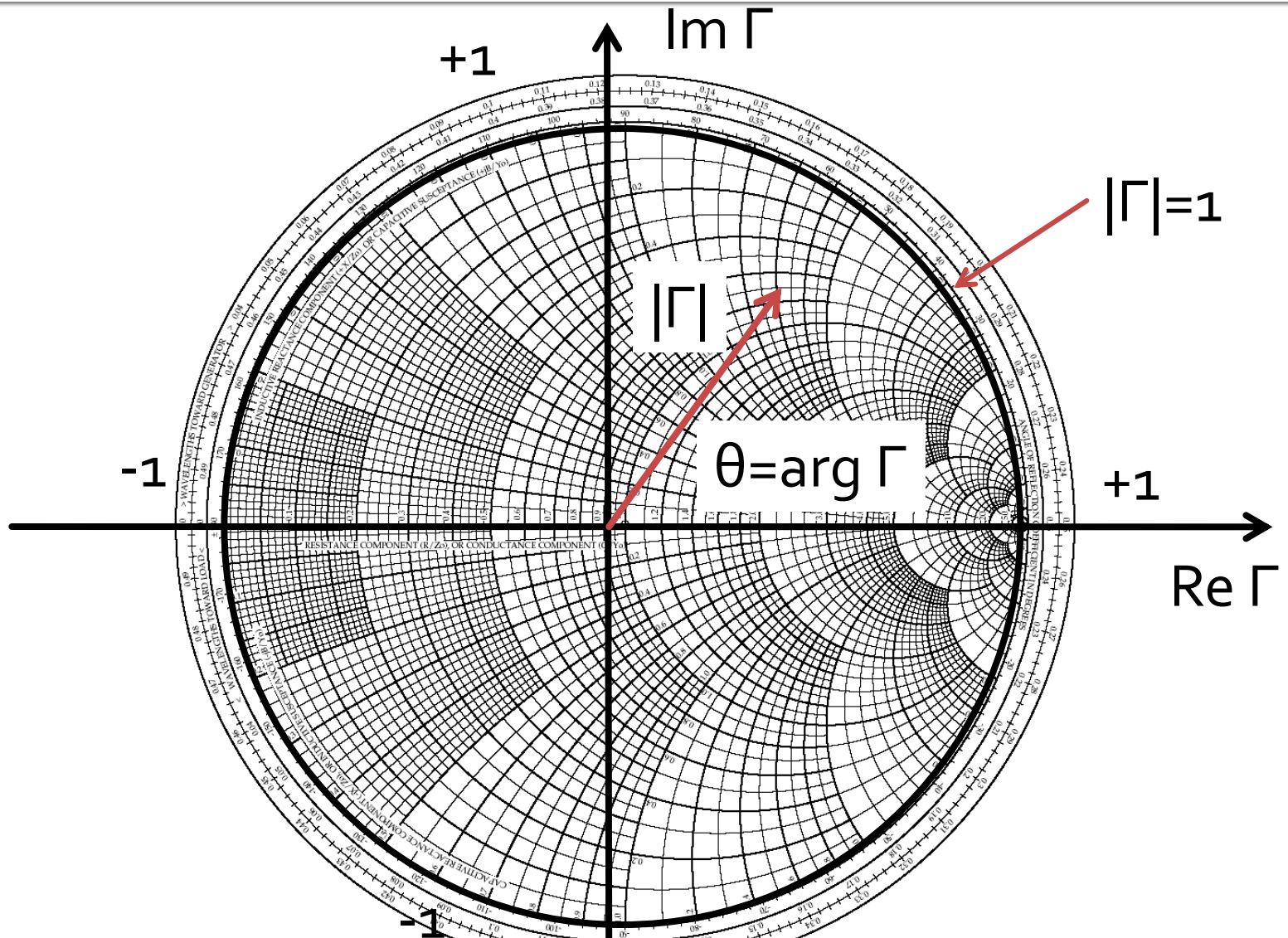



The Smith Chart

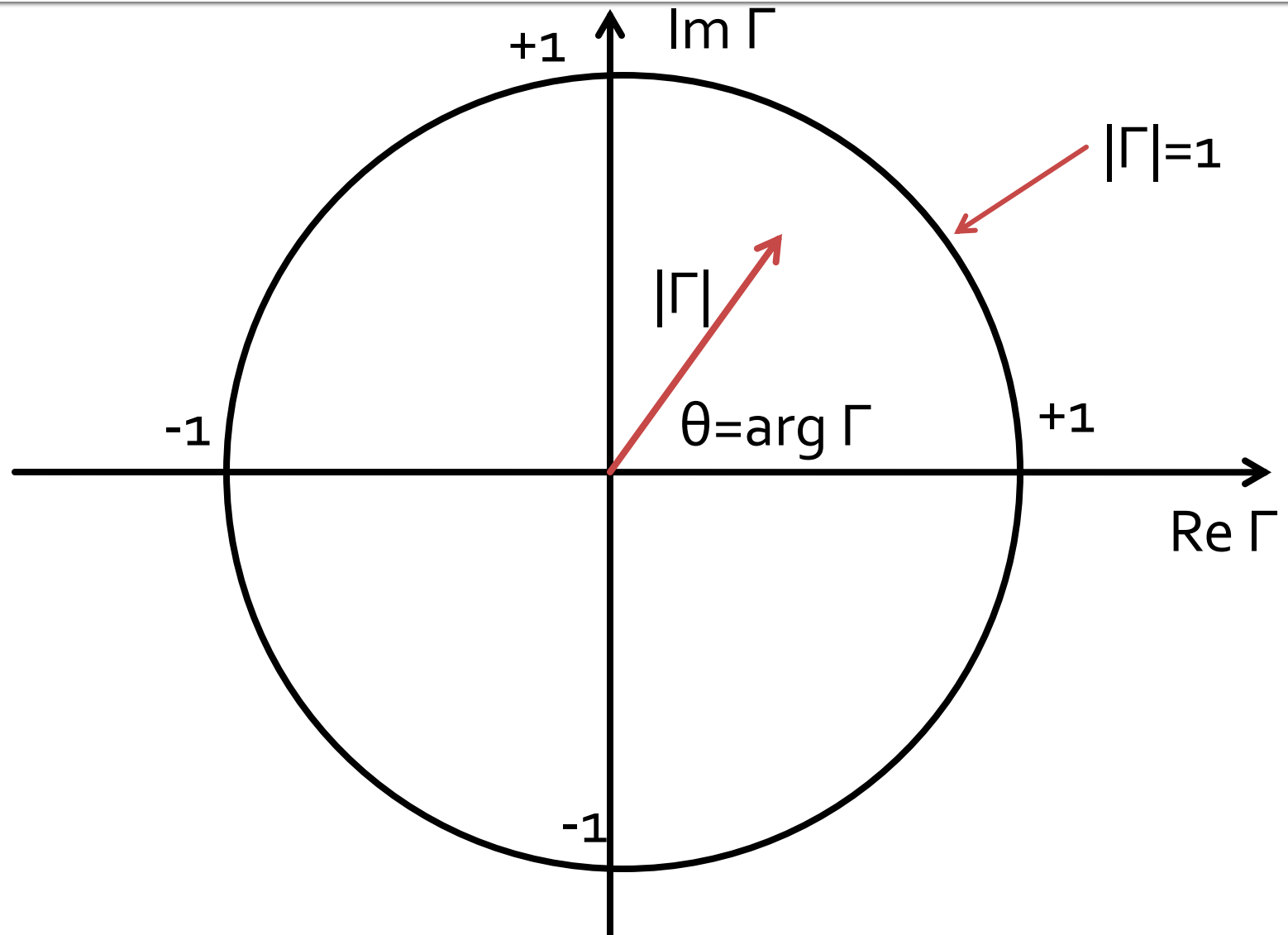

Impedance matching with lumped elements (L Networks)

Impedance Matching

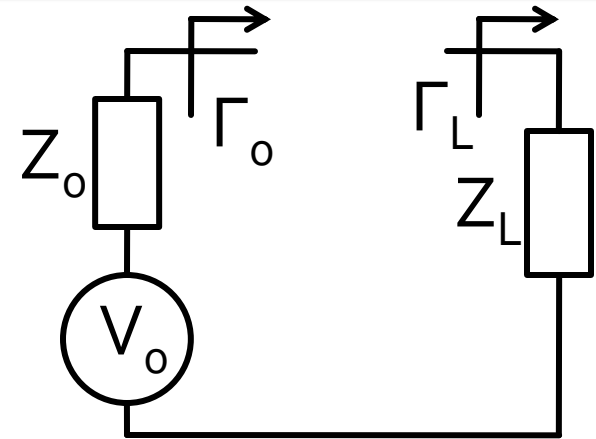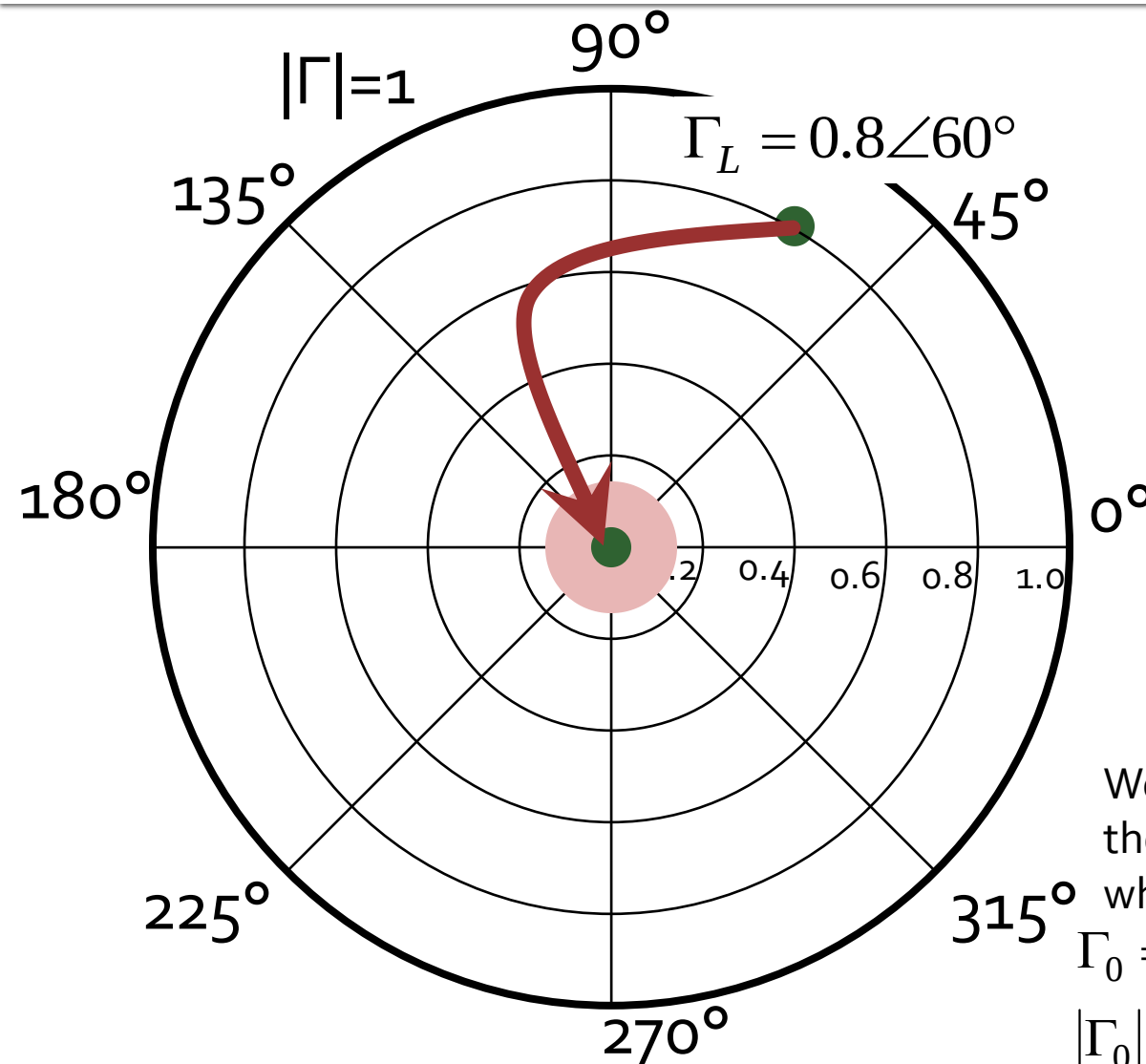The Smith Chart, reflection coefficient, impedance matching



Matching Z_L load to Z_o source.
We normalize Z_L over Z_o

$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

$$z_L = 0.429 + j \cdot 1.65$$


$$\Gamma_L = 0.8\angle 60^\circ$$

We must move the point denoting the reflection coefficient in the area where with a Z_o source we have:


$$\Gamma_o = 0 \quad \text{perfect match}$$

$$|\Gamma_o| \leq \Gamma_m \quad \text{"good enough" match}$$

Smith chart, $r=1$ and $g=1$

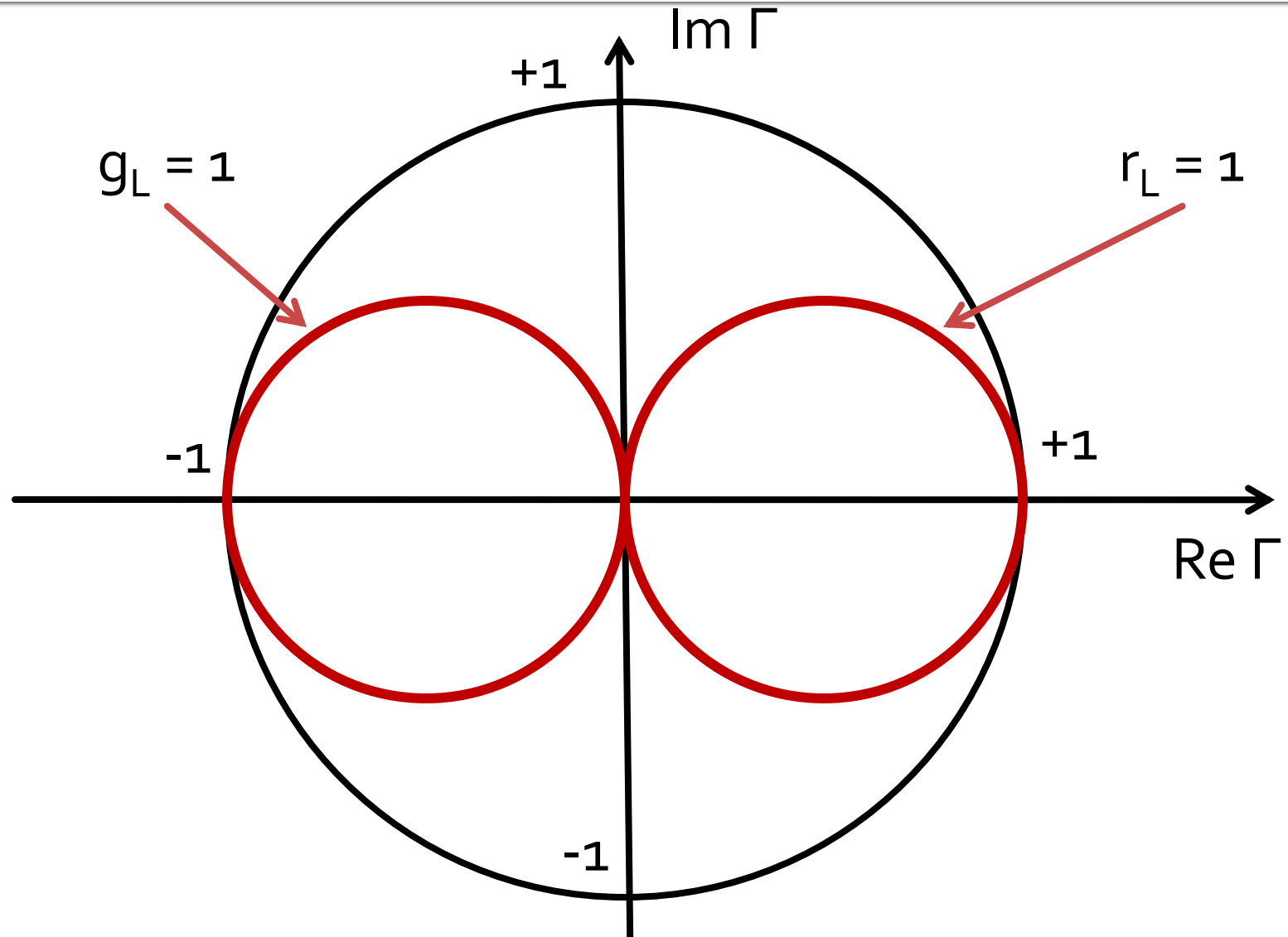

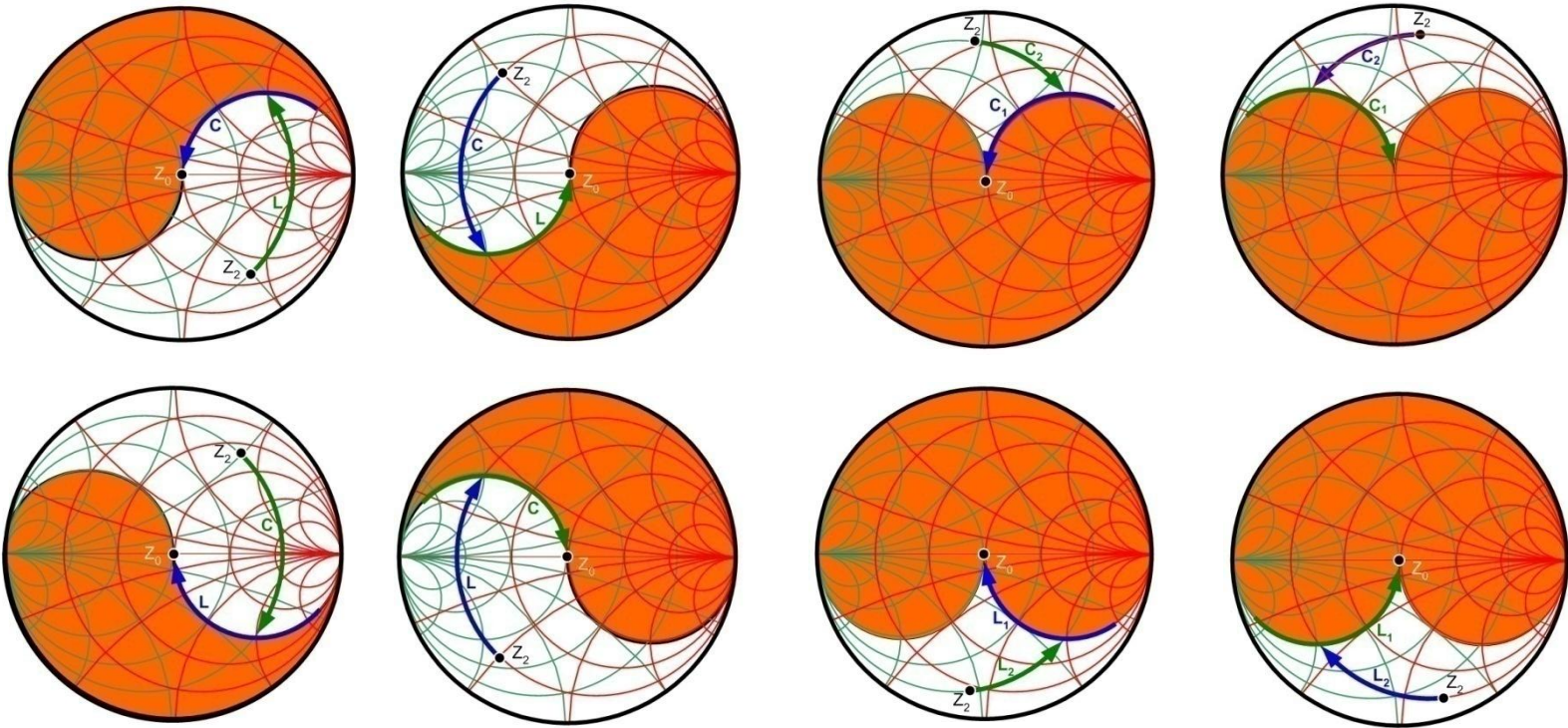Matching with 2 reactive elements (L Networks)




Forbidden area for
current network

Impedance Matching with Stubs


Impedance Matching

Smith chart, $r=1$ and $g=1$

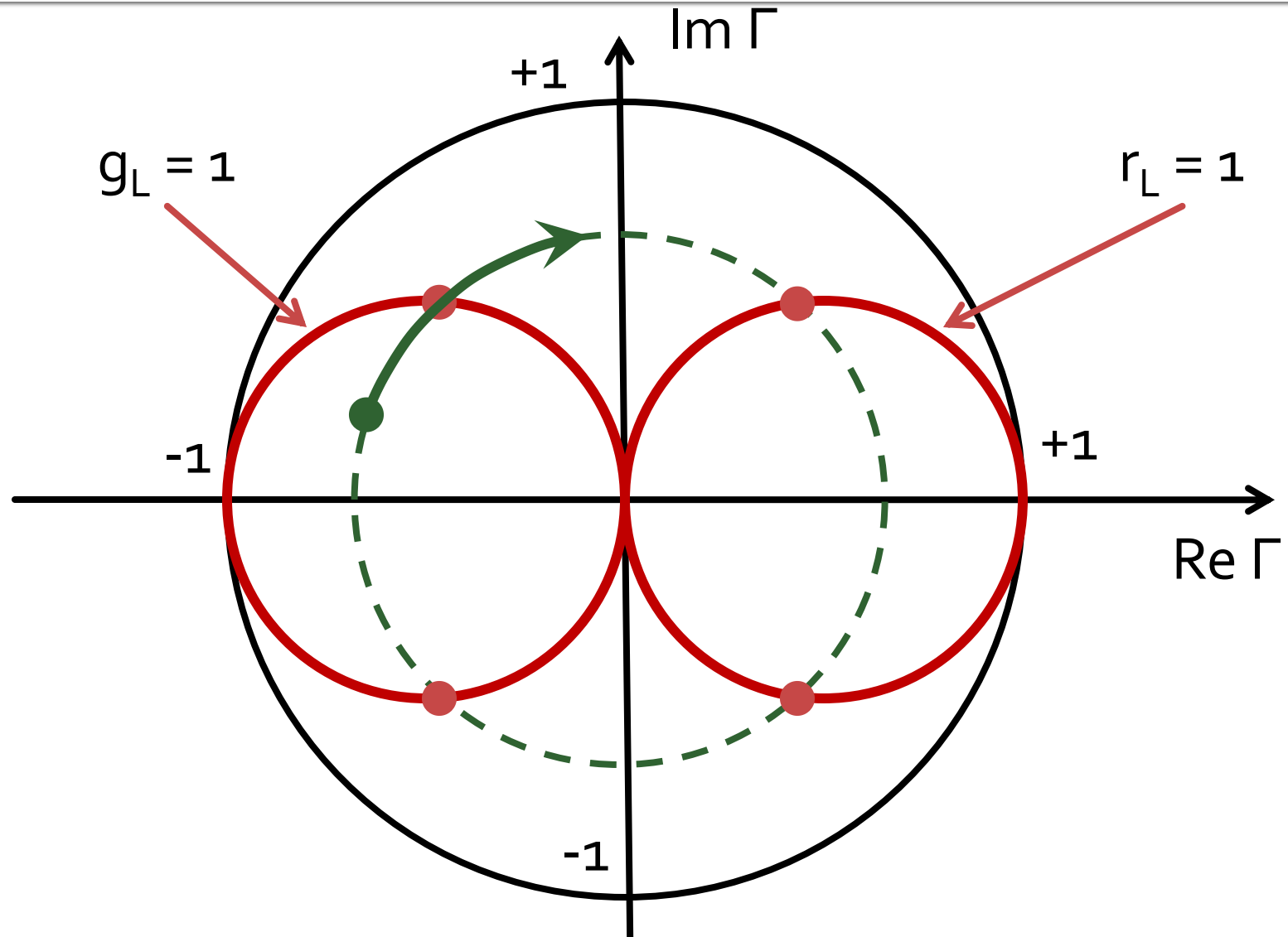


Single stub tuning

- Shunt Stub

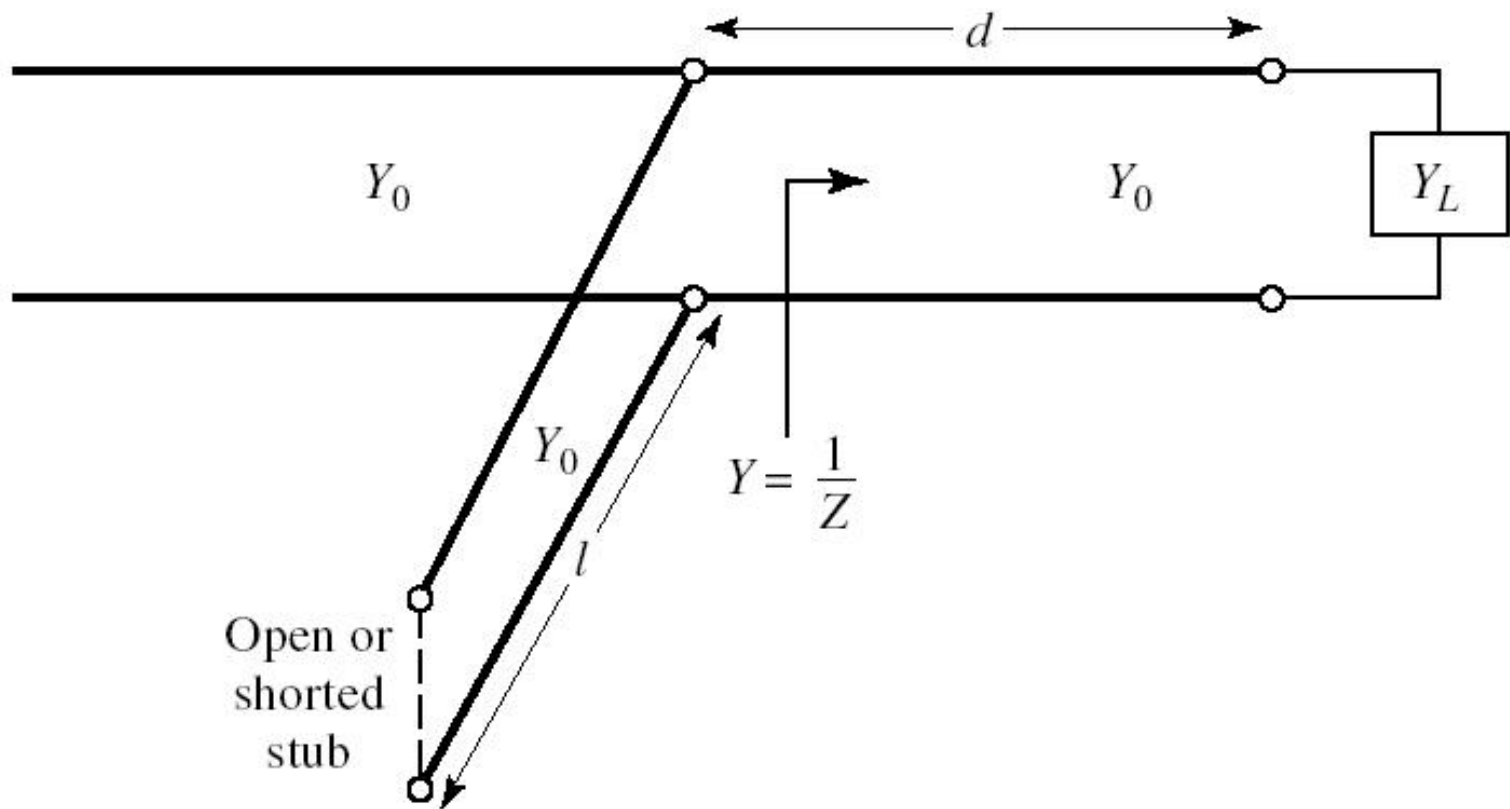


Single stub tuning

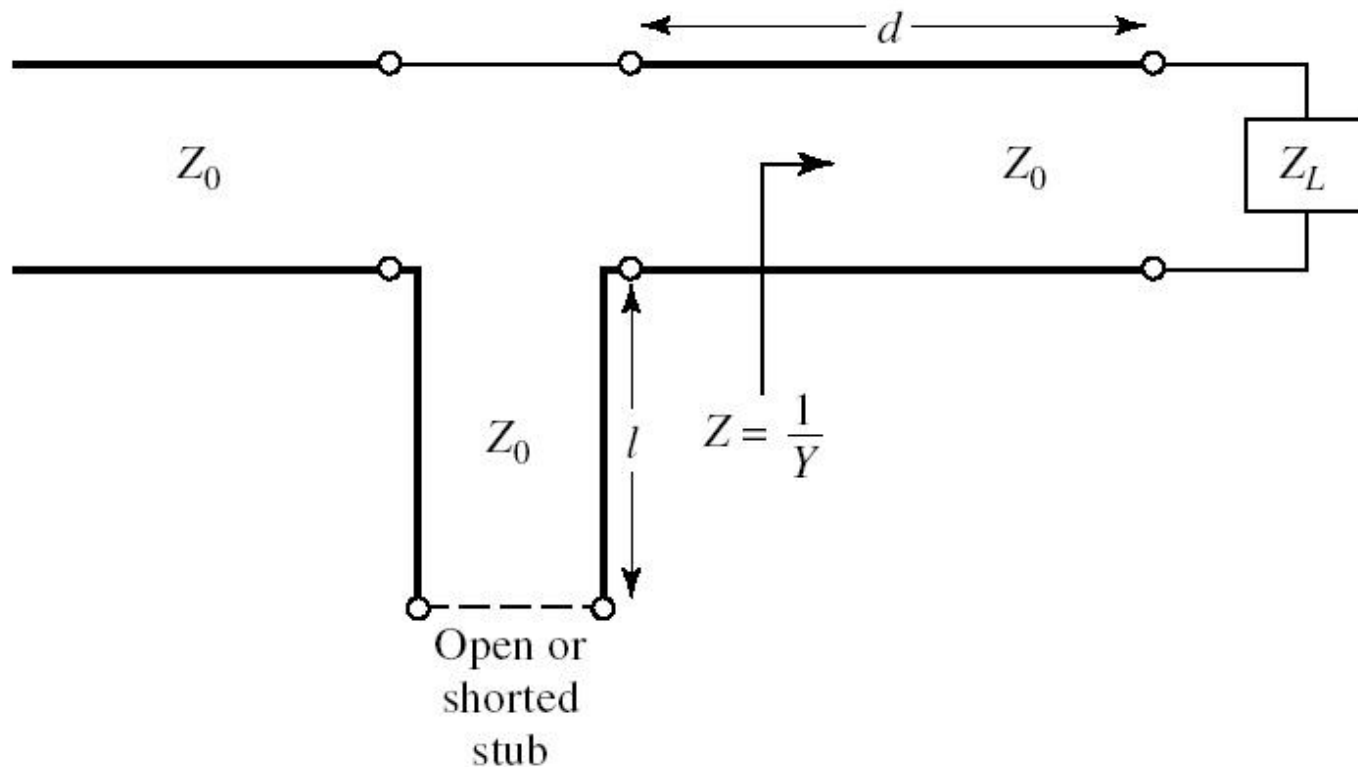- Series Stub
- difficult to realize in single conductor line technologies (microstrip)



Microwave Amplifiers

Amplifier as two-port

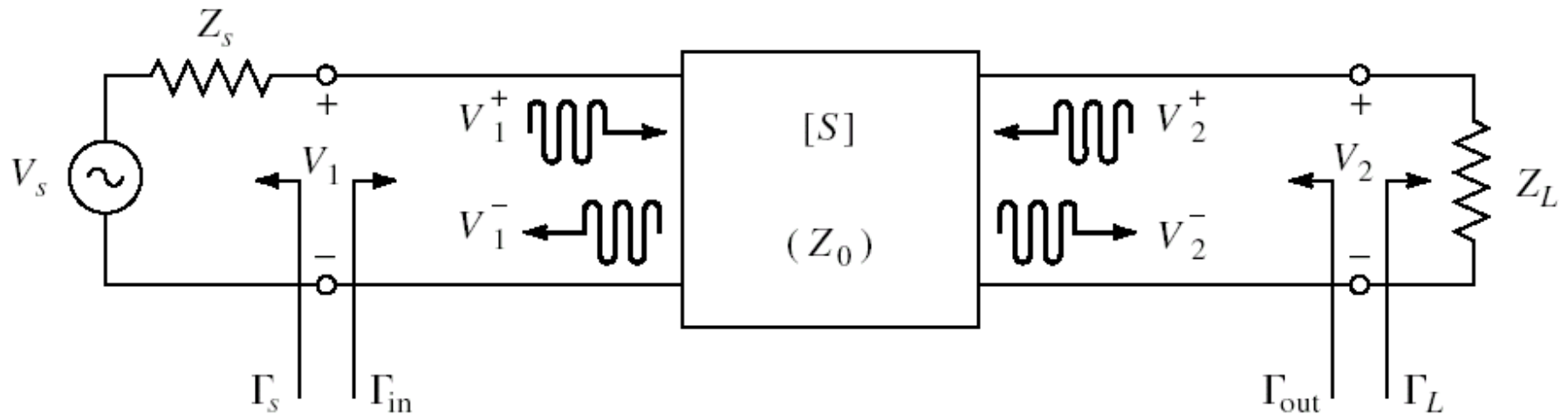

- Characterized with S parameters
- normalized at Z_0 (implicit 50Ω)
- Datasheets: S parameters for specific bias conditions

Datasheets

NE46100

VCE = 5 V, Ic = 50 mA

FREQUENCY (MHz)	S11		S21		S12		S22		K	MAG ² (dB)
	MAG	ANG	MAG	ANG	MAG	ANG	MAG	ANG		
100	0.778	-137	26.776	114	0.028	30	0.555	-102	0.16	29.8
200	0.815	-159	14.407	100	0.035	29	0.434	-135	0.36	26.2
500	0.826	-177	5.855	84	0.040	38	0.400	-162	0.75	21.7
800	0.827	176	3.682	76	0.052	43	0.402	-169	0.91	18.5
1000	0.826	173	2.963	71	0.058	47	0.405	-172	1.02	16.3
1200	0.825	170	2.441	66	0.064	47	0.412	-174	1.08	14.0
1400	0.820	167	2.111	61	0.069	47	0.413	-176	1.17	12.4
1600	0.828	165	1.863	57	0.078	54	0.426	-177	1.15	11.4
1800	0.827	162	1.671	53	0.087	50	0.432	-178	1.14	10.6
2000	0.828	159	1.484	49	0.093	50	0.431	-180	1.17	9.5
2500	0.822	153	1.218	39	0.11	48	0.462	177	1.18	7.8
3000	0.818	148	1.010	30	0.135	46	0.490	174	1.16	6.3
3500	0.824	142	0.876	21	0.147	44	0.507	170	1.16	5.3
4000	0.812	137	0.762	13	0.168	38	0.535	167	1.14	4.3

VCE = 5 V, Ic = 100 mA


100	0.778	-144	27.669	111	0.027	35	0.523	-114	0.27	30.2
200	0.820	-164	14.559	97	0.029	29	0.445	-144	0.42	27.0
500	0.832	-179	5.885	84	0.035	38	0.435	-166	0.81	22.2
800	0.833	175	3.691	76	0.048	45	0.435	-173	0.95	18.8
1000	0.831	172	2.980	71	0.056	51	0.437	-176	1.05	16.0
1200	0.836	169	2.464	67	0.061	52	0.432	-178	1.11	14.0
1400	0.829	166	2.121	61	0.072	53	0.447	-180	1.12	12.6
1600	0.831	164	1.867	58	0.080	54	0.445	179	1.14	11.4

S2P - Touchstone

- Touchstone file format (*.s2p)

```
! SIEMENS Small Signal Semiconductors
! VDS = 3.5 V   ID = 15 mA
# GHz S MA R 50
! f      S11      S21      S12      S22
! GHz   MAG  ANG   MAG  ANG   MAG  ANG   MAG  ANG
1.000 0.9800 -18.0 2.230 157.0 0.0240 74.0 0.6900 -15.0
2.000 0.9500 -39.0 2.220 136.0 0.0450 57.0 0.6600 -30.0
3.000 0.8900 -64.0 2.210 110.0 0.0680 40.0 0.6100 -45.0
4.000 0.8200 -89.0 2.230 86.0 0.0850 23.0 0.5600 -62.0
5.000 0.7400 -115.0 2.190 61.0 0.0990 7.0 0.4900 -80.0
6.000 0.6500 -142.0 2.110 36.0 0.1070 -10.0 0.4100 -98.0
!
! f      Fmin  Gammaopt rn/50
! GHz   dB   MAG  ANG  -
2.000   1.00 0.72 27 0.84
4.000   1.40 0.64 61 0.58
```

Amplifier as two-port

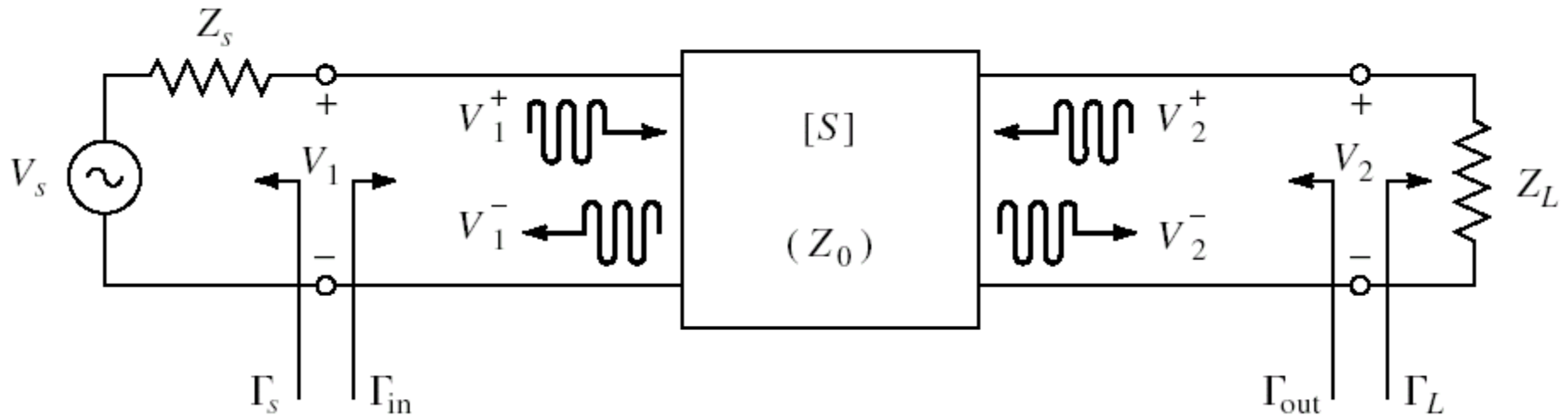

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_s}{1 - S_{11} \cdot \Gamma_s}$$

Two-Port Power Gains

- Power Gain

$$G = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) \cdot |1 - S_{22} \cdot \Gamma_L|^2}$$

$$P_{in} = P_{in}(\Gamma_S, \Gamma_{in}(\Gamma_L), S)$$

$$P_L = P_L(\Gamma_S, \Gamma_{in}(\Gamma_L), S)$$

- The **actual** power gain **introduced** by the amplifier is less important because a higher gain may be accompanied by a **decrease** in input power (power actually drained from the source)
- We prefer to characterize the amplifier effect looking to the **power actually delivered to the load** in relation to the power **available from the source** (which is a constant)

Two-Port Power Gains

- **Available** power gain

$$G_A = \frac{P_{av L}}{P_{av S}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2)}{|1 - S_{22} \cdot \Gamma_L|^2 \cdot (1 - |\Gamma_{out}|^2)}$$

- **Transducer** power gain

$$G_T = \frac{P_L}{P_{av S}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2}$$

$$\Gamma_{in} = \Gamma_{in}(\Gamma_L)$$

- **Unilateral transducer** power gain

$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$S_{12} \cong 0$$


$$\Gamma_{in} = S_{11}$$

Input and output can be treated independently

Stability

Microwave Amplifiers

Amplifier as two-port

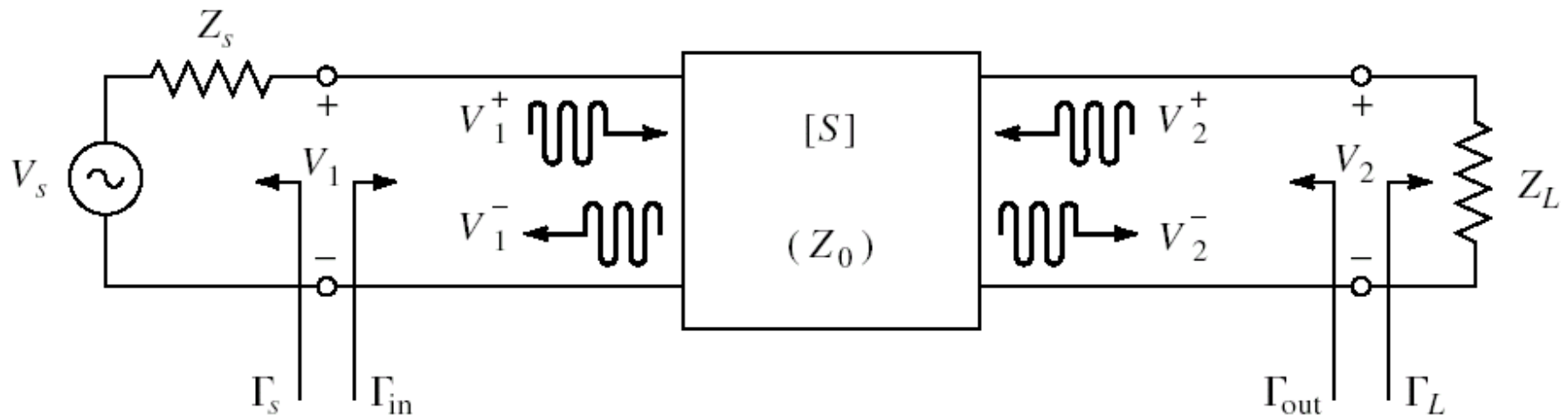

- For an amplifier two-port we are interested in:
 - **stability**
 - power gain
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)

Stability

$$|\Gamma_{in}| < 1 \quad \left| S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \right| < 1$$

- We can calculate conditions to be met by Γ_L to achieve stability

$$|\Gamma_{out}| < 1 \quad \left| S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S} \right| < 1$$

- We can calculate conditions to be met by Γ_S to achieve stability

Stability

$$|\Gamma_{in}| < 1 \quad \left| S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \right| < 1$$

- The limit between stability/instability

$$|\Gamma_{in}| = 1 \quad \log_{10} |\Gamma_{in}| = 0 \quad \left| S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \right| = 1$$

$$|S_{11} \cdot (1 - S_{22} \cdot \Gamma_L) + S_{12} \cdot S_{21} \cdot \Gamma_L| = |1 - S_{22} \cdot \Gamma_L|$$


- determinant of the S matrix $\Delta = S_{11} \cdot S_{22} - S_{12} \cdot S_{21}$

$$|S_{11} - \Delta \cdot \Gamma_L| = |1 - S_{22} \cdot \Gamma_L|$$

$$|S_{11} - \Delta \cdot \Gamma_L|^2 = |1 - S_{22} \cdot \Gamma_L|^2$$

Stability

$$|\Gamma - \Gamma_0| = R$$

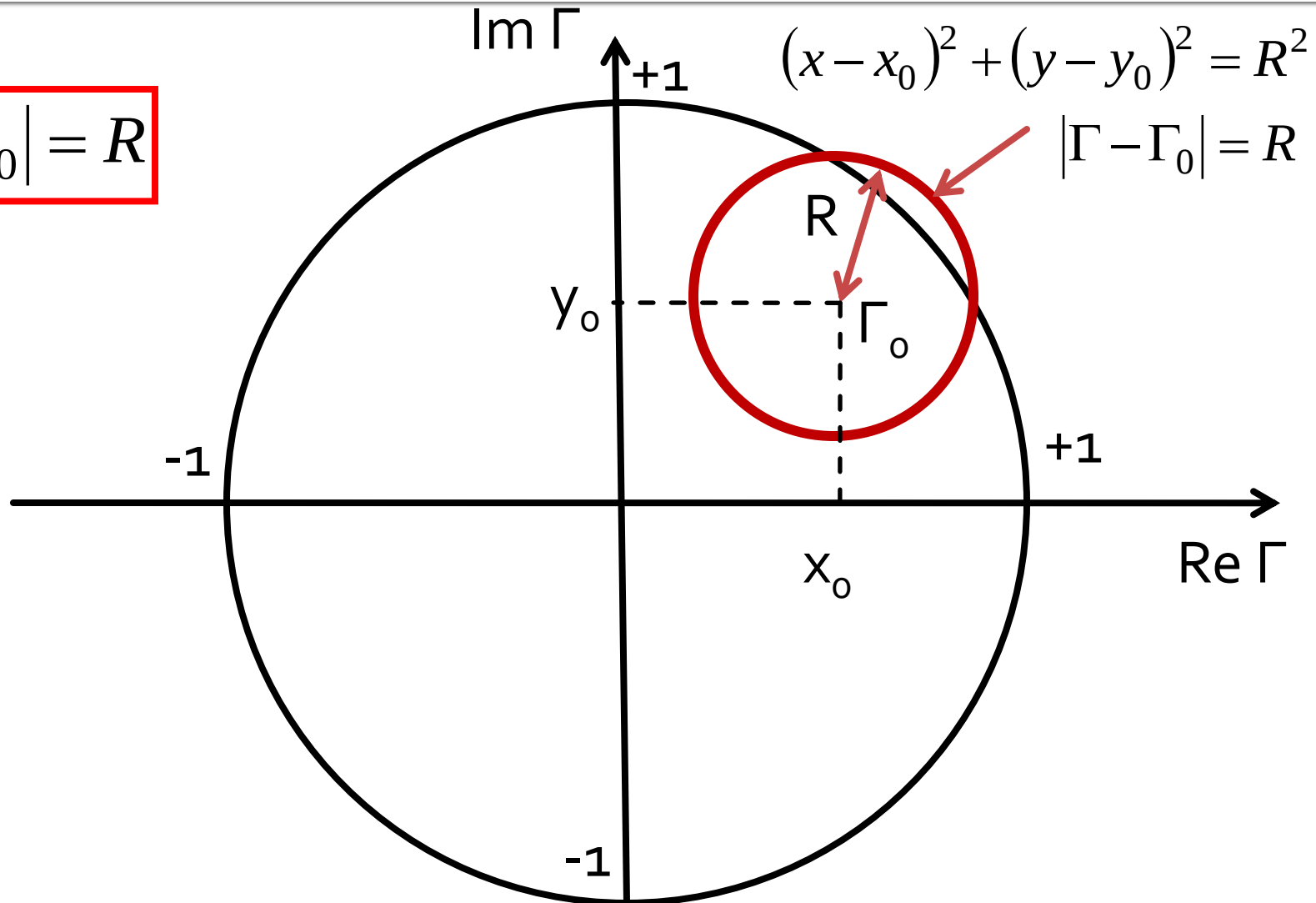

Output stability circle (CSOUT)

$$\left| \Gamma_L - \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12} \cdot S_{21}}{|S_{22}|^2 - |\Delta|^2} \right| \quad |\Gamma_L - C_L| = R_L$$

- We obtain the equation of a circle in the complex plane, which represents the locus of Γ_L for the **limit between stability and instability** ($|\Gamma_{in}| = 1$)
- This circle is the **output stability circle** (Γ_L)



$$C_L = \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \quad R_L = \frac{|S_{12} \cdot S_{21}|}{\left| |S_{22}|^2 - |\Delta|^2 \right|}$$

Input stability circle (CSIN)

- Similarly
$$\left| \Gamma_{out} \right| = 1 \quad \left| S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S} \right| = 1$$
- We obtain the equation of a circle in the complex plane, which represents the locus of Γ_S for the **limit between stability and instability** ($|\Gamma_{out}| = 1$)
- This circle is the **input stability circle** (Γ_S)

$$C_S = \frac{(S_{11} - \Delta \cdot S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \quad R_S = \frac{|S_{12} \cdot S_{21}|}{\left| |S_{11}|^2 - |\Delta|^2 \right|}$$

Output stability circle (CSOUT)

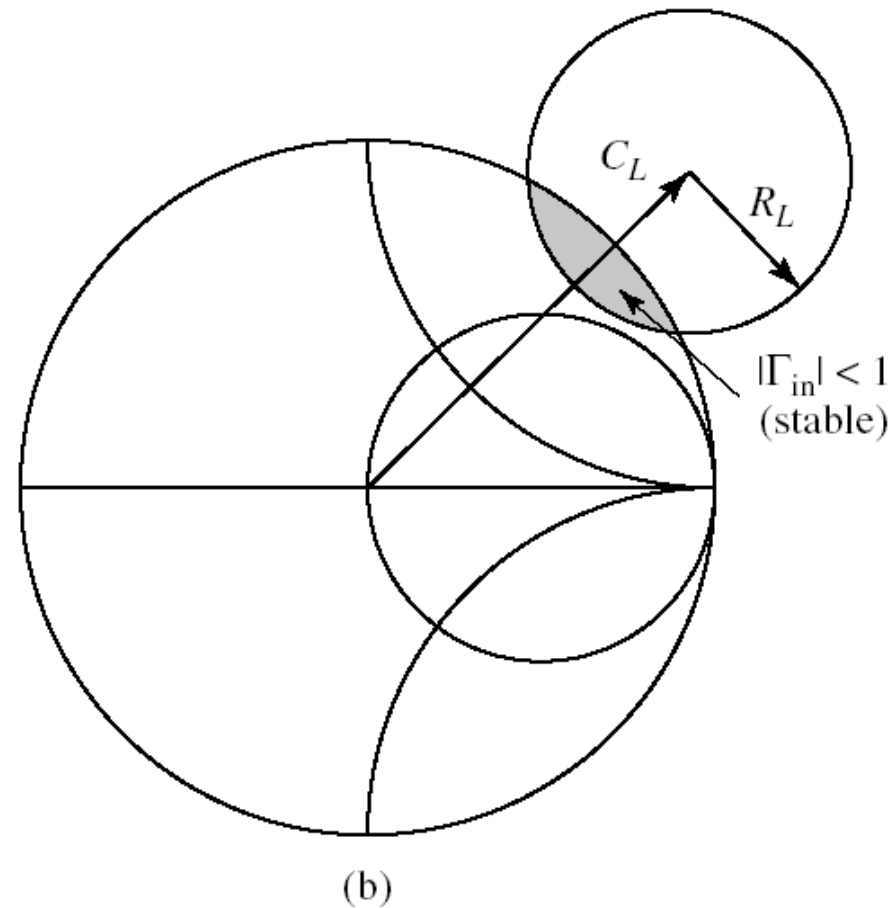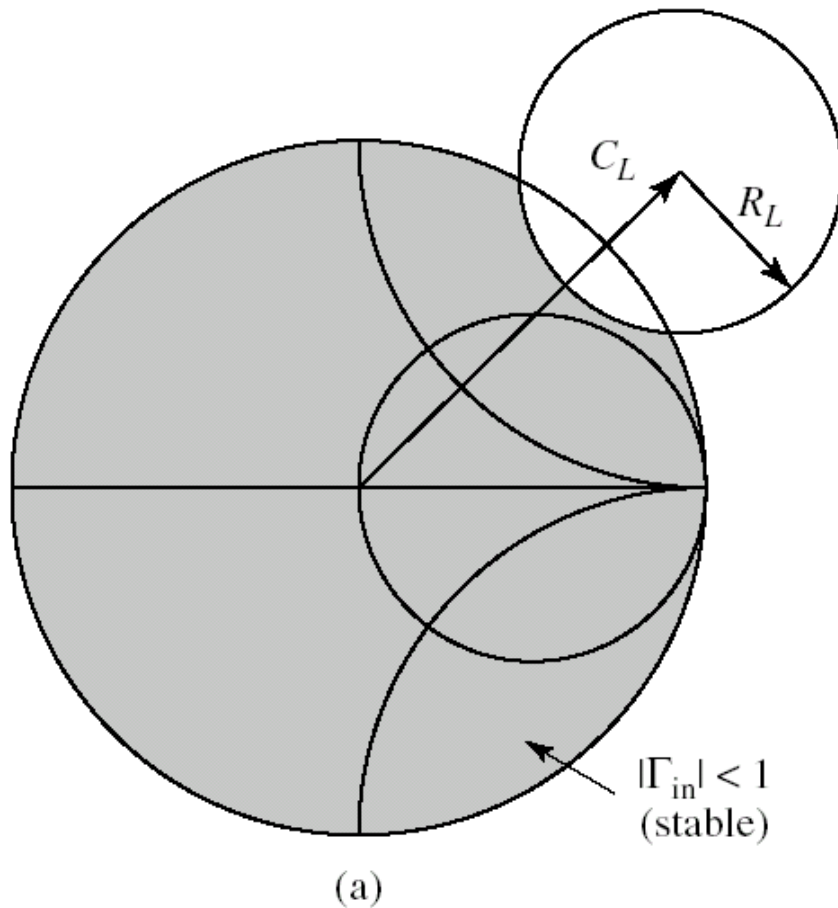

- Two cases possible: (a) stable outside/ (b) stable inside

Output stability circle (CSOUT)

- Identification of the stability / instability regions
 - Center of the Smith Chart in Γ_L complex plane correspond to $\Gamma_L = 0$
 - Input reflection coefficient

$$\Gamma_{in} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \quad \Gamma_{in}|_{\Gamma_L=0} = S_{11} \quad |\Gamma_{in}|_{\Gamma_L=0} = |S_{11}|$$

- A decision can be made based on $|S_{11}|$ value the position of the center of the Smith chart (origin of the complex plane) relative to the circle

Identification of the stability / instability regions

- Output stability circle
 - $|S_{11}| < 1 \rightarrow$ the center of the Smith chart on which Γ_L is represented is a **stable point**, so it's placed in the stability region (most often situation)
 - $|S_{11}| > 1 \rightarrow$ the center of the Smith chart on which Γ_L is represented is a **unstable point**, so it's placed in the instability region
- Input stability circle
 - $|S_{22}| < 1 \rightarrow$ the center of the Smith chart on which Γ_S is represented is a **stable point**, so it's placed in the stability region (most often situation)
 - $|S_{22}| > 1 \rightarrow$ the center of the Smith chart on which Γ_S is represented is a **unstable point**, so it's placed in the instability region

Example

- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.

- @5GHz

- $S_{11} = 0.64 \angle 139^\circ$
- $S_{12} = 0.119 \angle -21^\circ$
- $S_{21} = 3.165 \angle 16^\circ$
- $S_{22} = 0.22 \angle 146^\circ$

IATF-34143
IS-PARAMETERS at Vds=3V Id=20mA. LAST UPDATED 01-29-99

ghz s ma r 50

2.0	0.75	-126	6.306	90	0.088	23	0.26	-120
2.5	0.72	-145	5.438	75	0.095	15	0.25	-140
3.0	0.69	-162	4.762	62	0.102	7	0.23	-156
4.0	0.65	166	3.806	38	0.111	-8	0.22	174
5.0	0.64	139	3.165	16	0.119	-21	0.22	146
6.0	0.65	114	2.706	-5	0.125	-35	0.23	118
7.0	0.66	89	2.326	-27	0.129	-49	0.25	91
8.0	0.69	67	2.017	-47	0.133	-62	0.29	67
9.0	0.72	48	1.758	-66	0.135	-75	0.34	46

IFREQ Fopt GAMMA OPT RN/Zo
IGHZ dB MAG ANG -

2.0	0.19	0.71	66	0.09
2.5	0.23	0.65	83	0.07
3.0	0.29	0.59	102	0.06
4.0	0.42	0.51	138	0.03
5.0	0.54	0.45	174	0.03
6.0	0.67	0.42	-151	0.05
7.0	0.79	0.42	-118	0.10
8.0	0.92	0.45	-88	0.18
9.0	1.04	0.51	-63	0.30
10.0	1.16	0.61	-43	0.46

Solution + region identification

- S parameters

- $S_{11} = -0.483 + 0.42 \cdot j$

- $S_{12} = 0.111 - 0.043 \cdot j$

- $S_{21} = 3.042 + 0.872 \cdot j$

- $S_{22} = -0.182 + 0.123 \cdot j$

$$C_L = \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} = 3.931 - 0.897 \cdot j$$

$$|C_L| = 4.032$$

$$R_L = \frac{|S_{12} \cdot S_{21}|}{\left| |S_{22}|^2 - |\Delta|^2 \right|} = 4.891$$

- $|S_{22}| < 1$

- $|C_L| < R_L, o \in \text{CSOUT}$

- The center of the Smith chart is placed inside the output stability circle ($o \in \text{CSOUT}$) and is a stable point

- the inside of the output stability circle – stability region
 - the outside of the output stability circle – instability region

Solution + region identification

- S parameters

- $S_{11} = -0.483 + 0.42 \cdot j$

- $S_{12} = 0.111 - 0.043 \cdot j$

- $S_{21} = 3.042 + 0.872 \cdot j$

- $S_{22} = -0.182 + 0.123 \cdot j$

- $|S_{11}| < 1$

- $|C_S| > R_S, o \notin \text{CSIN}$

- The center of the Smith chart is placed outside the input stability circle ($o \notin \text{CSIN}$) and is a stable point

- the outside of the input stability circle – stability region


- the inside of the input stability circle – instability region

$$C_S = \frac{(S_{11} - \Delta \cdot S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} = -1.871 - 1.265 \cdot j$$

$$|C_S| = 2.259$$


$$R_S = \frac{|S_{12} \cdot S_{21}|}{||S_{11}|^2 - |\Delta|^2|} = 1.325$$

ADS

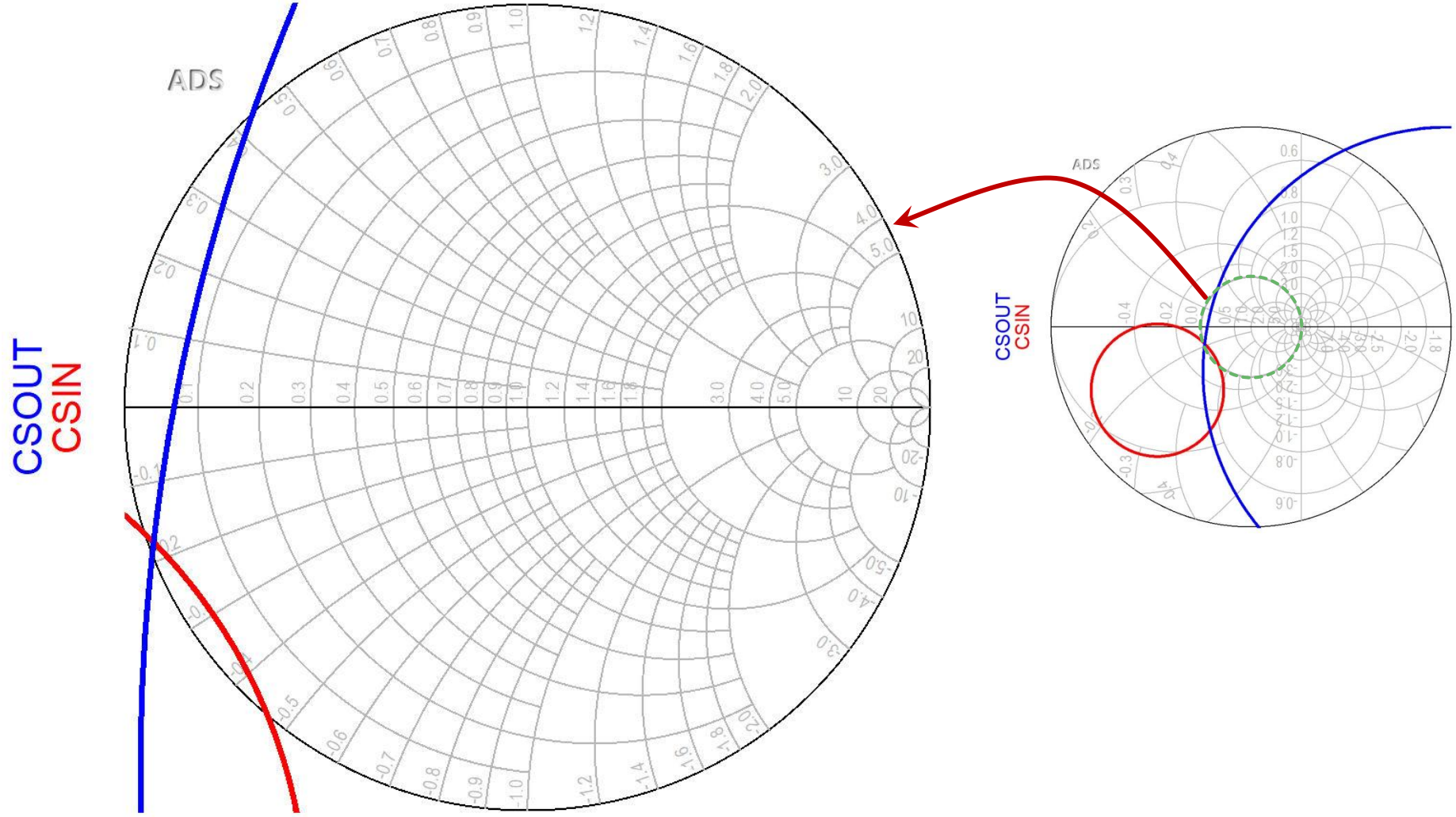



3D representation of $|\Gamma_{in}|$, $|\Gamma_{out}|$

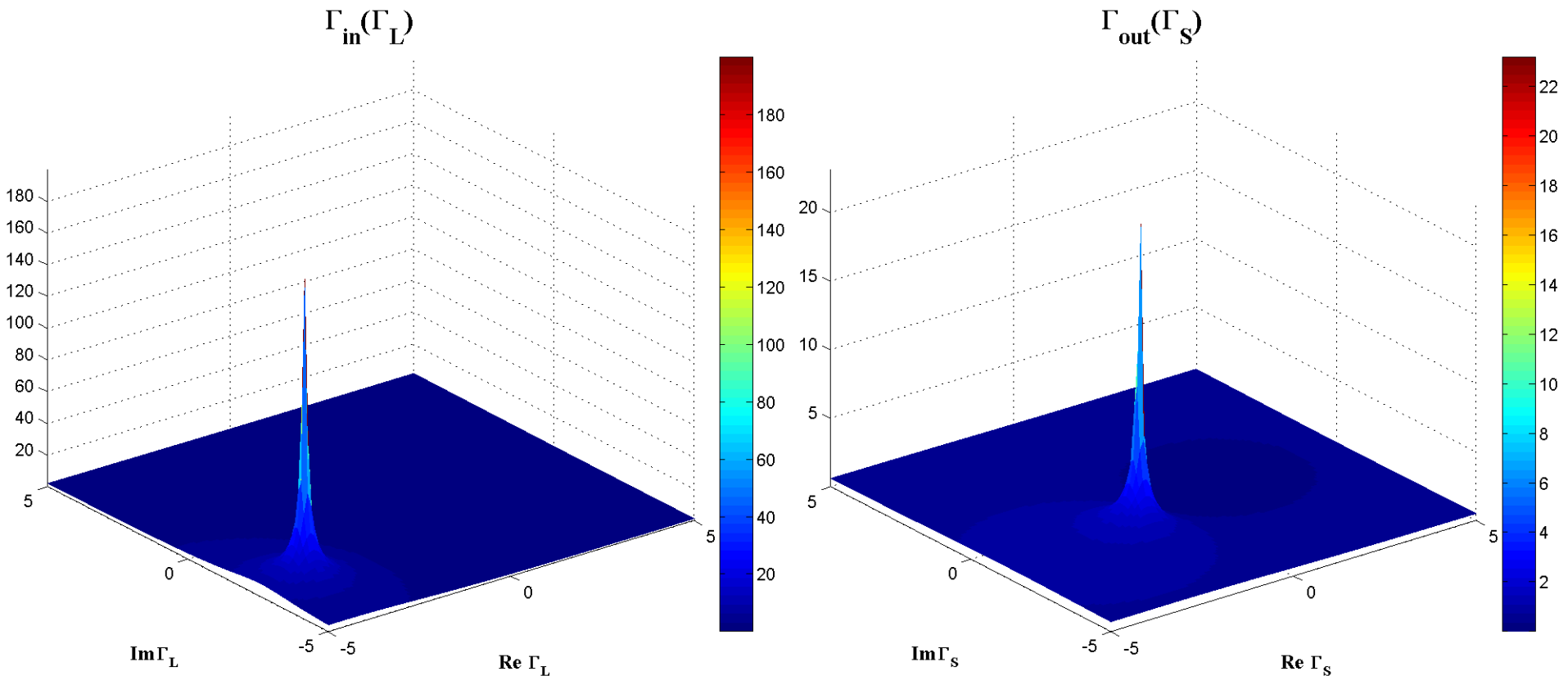- High variations -> we change to z logarithmic scale





3D representation of $|\Gamma_{in}|$, $|\Gamma_{out}|$

■ $\log_{10}|\Gamma_{in}|, \log_{10}|\Gamma_{out}|$

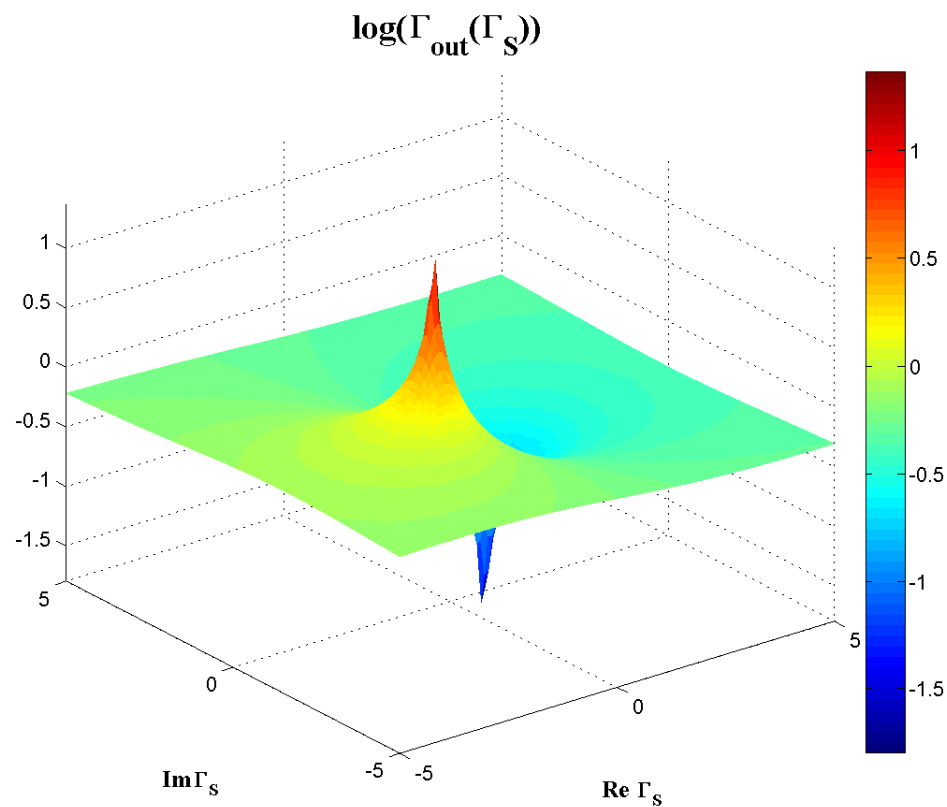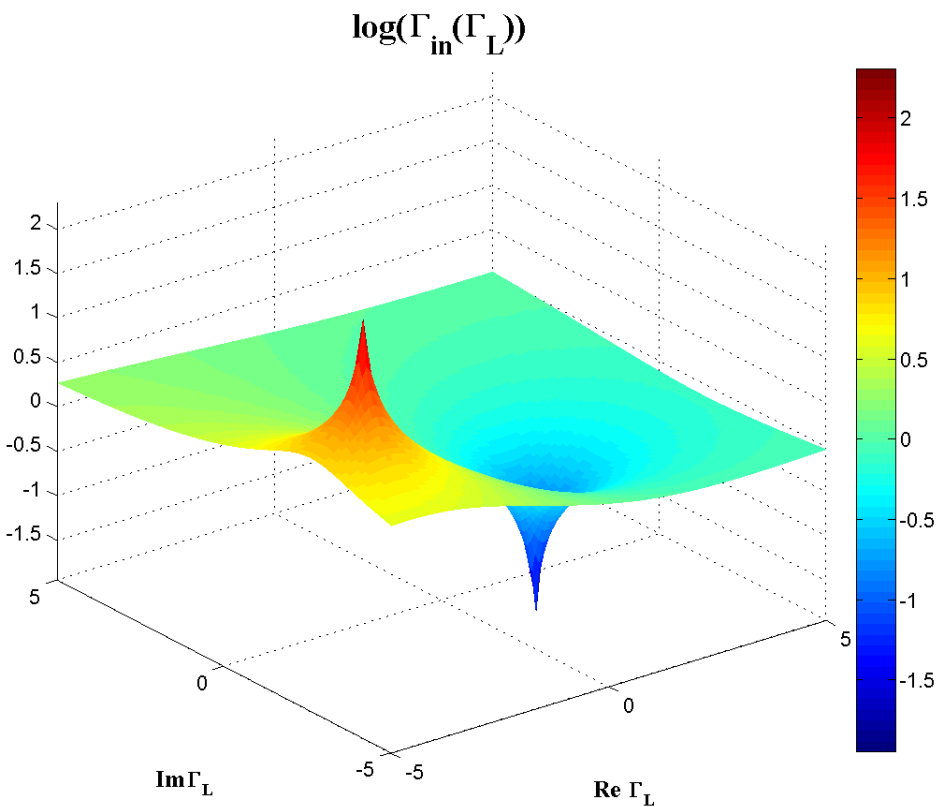


3D representation of $|\Gamma_{in}|$, $|\Gamma_{out}|$, $|\Gamma|=1$


- $|\Gamma| = 1 \rightarrow \log_{10}|\Gamma| = 0$, the intersection with the plane $z = 0$ is a circle

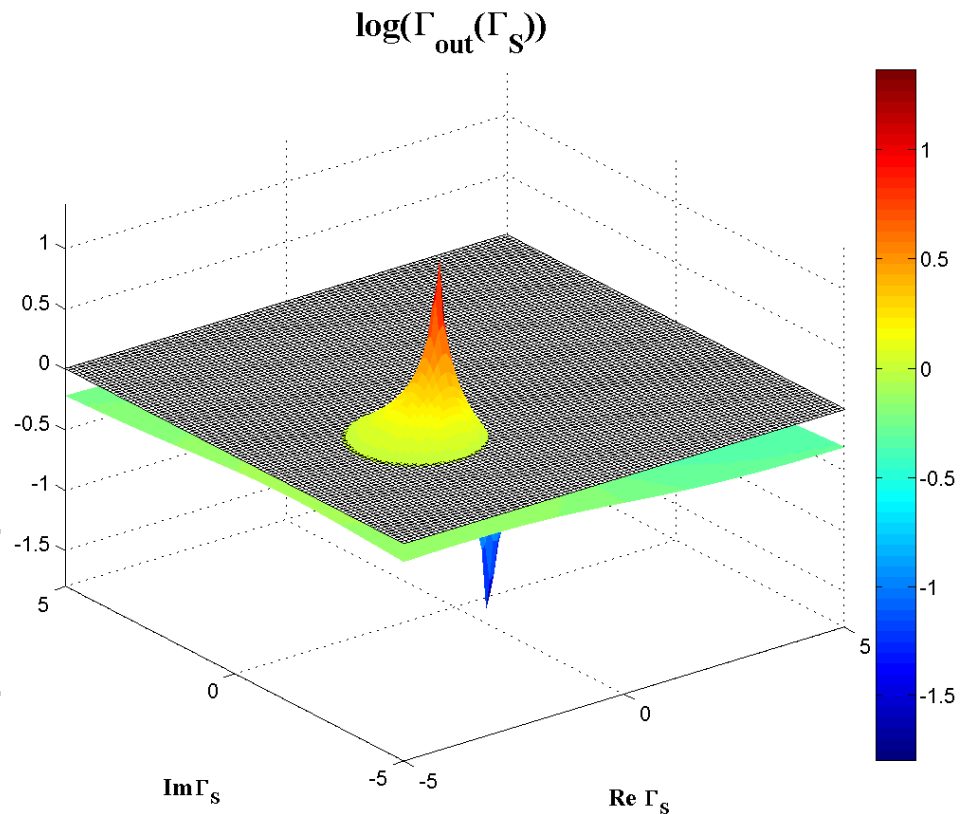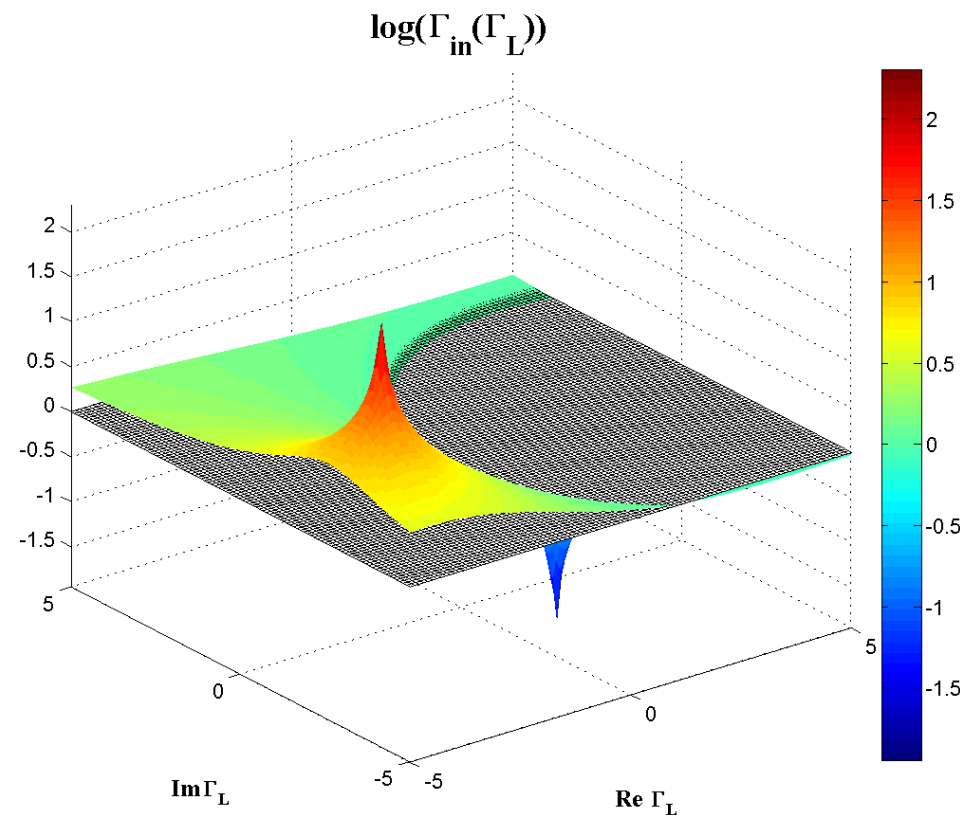

Contour map/lines

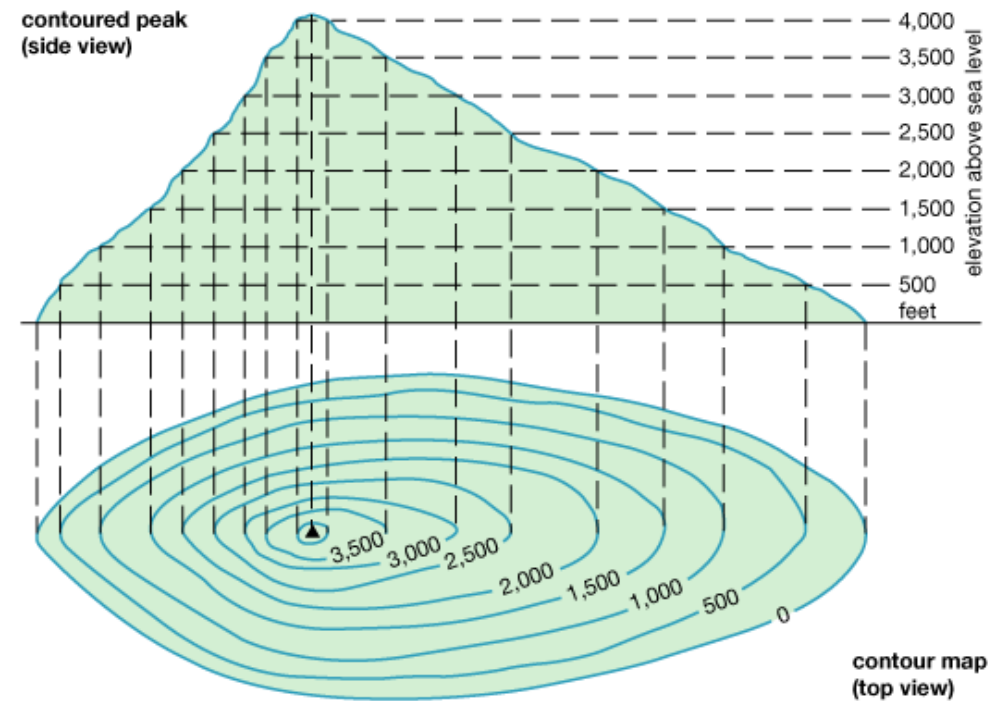


© 2011 Encyclopædia Britannica, Inc.

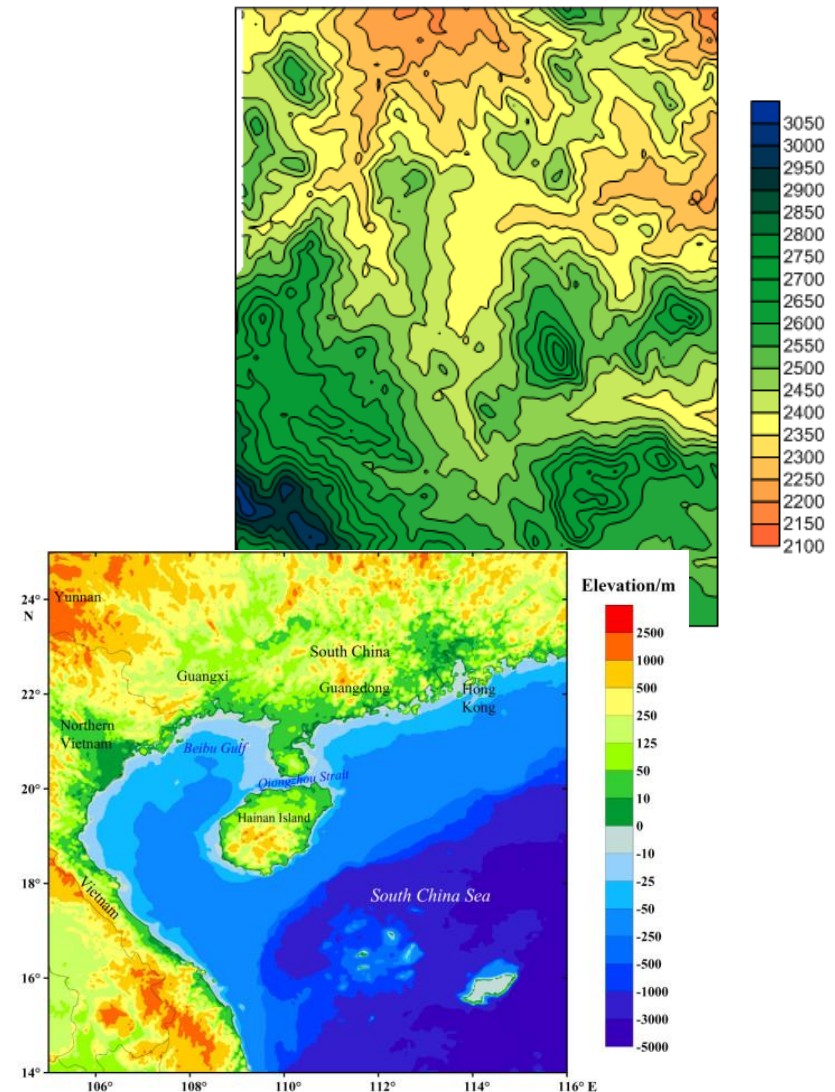

Contour lines of $\log_{10}|\Gamma_{in}|$


- $\log_{10}|\Gamma_{in}| = 0, \Gamma_L, \text{CSOUT}$

$$\log_{10}|\Gamma_{in}| = 0, \\ |\Gamma_{in}| = 1$$

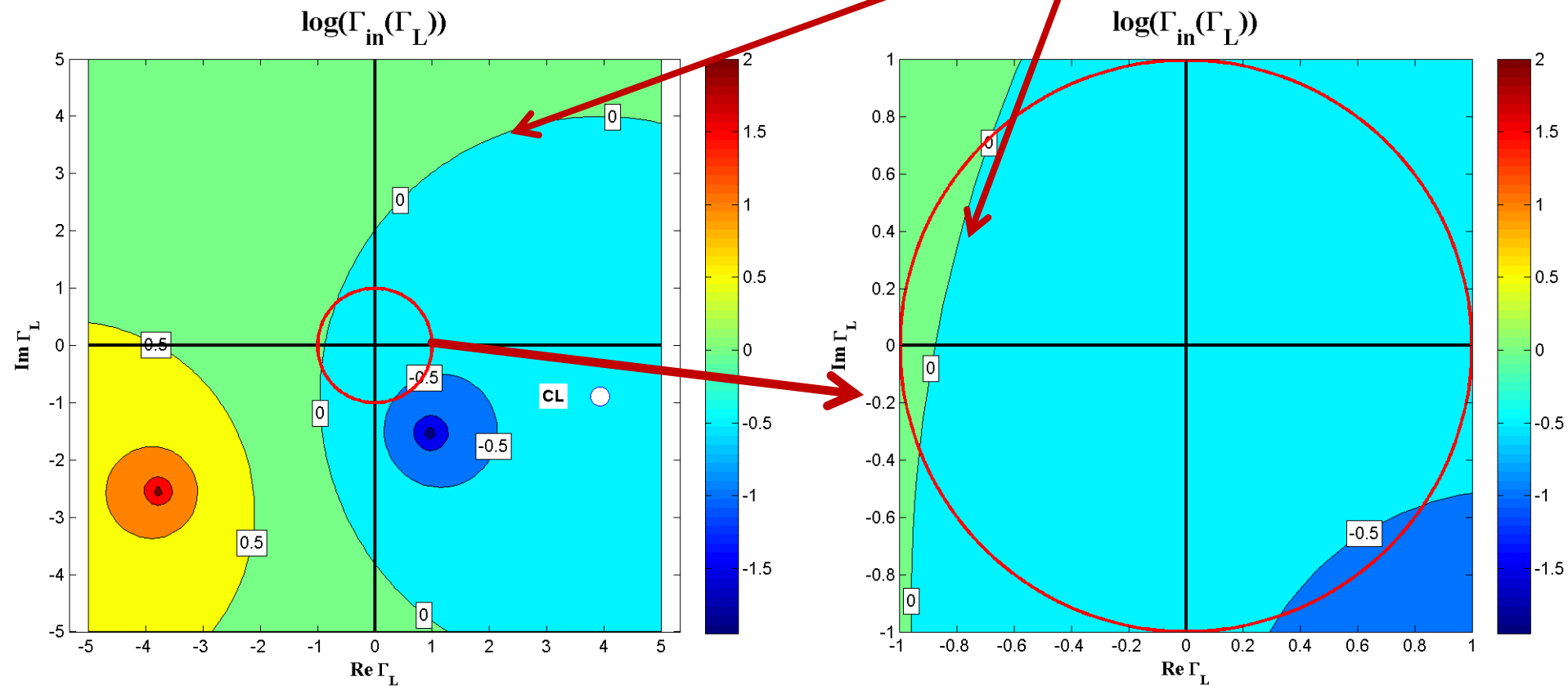




Contour lines of $\log_{10}|\Gamma_{\text{out}}|$

- $\log_{10}|\Gamma_{\text{out}}| = 0, \Gamma_S, \text{CSIN}$

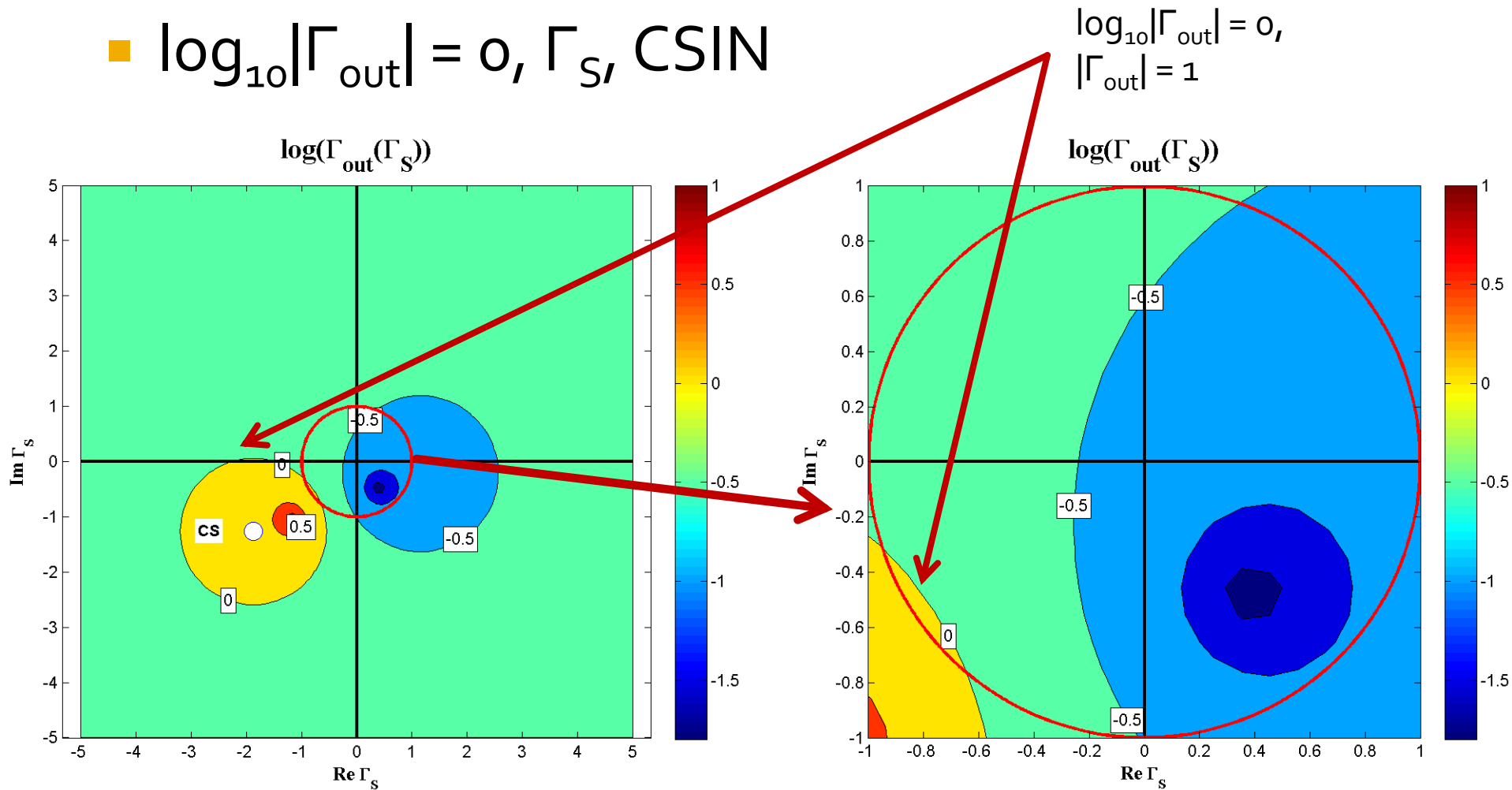

CSIN, CSOUT


CSOUT
CSIN

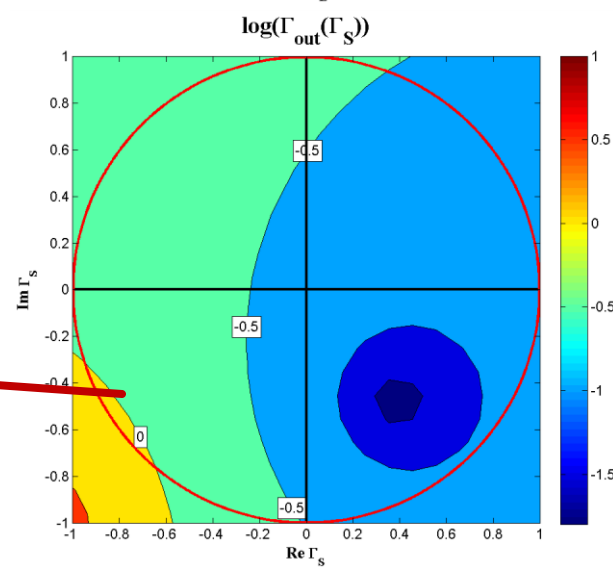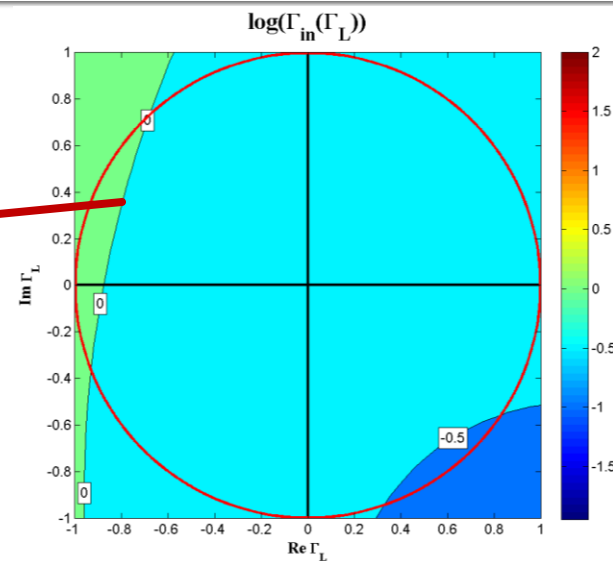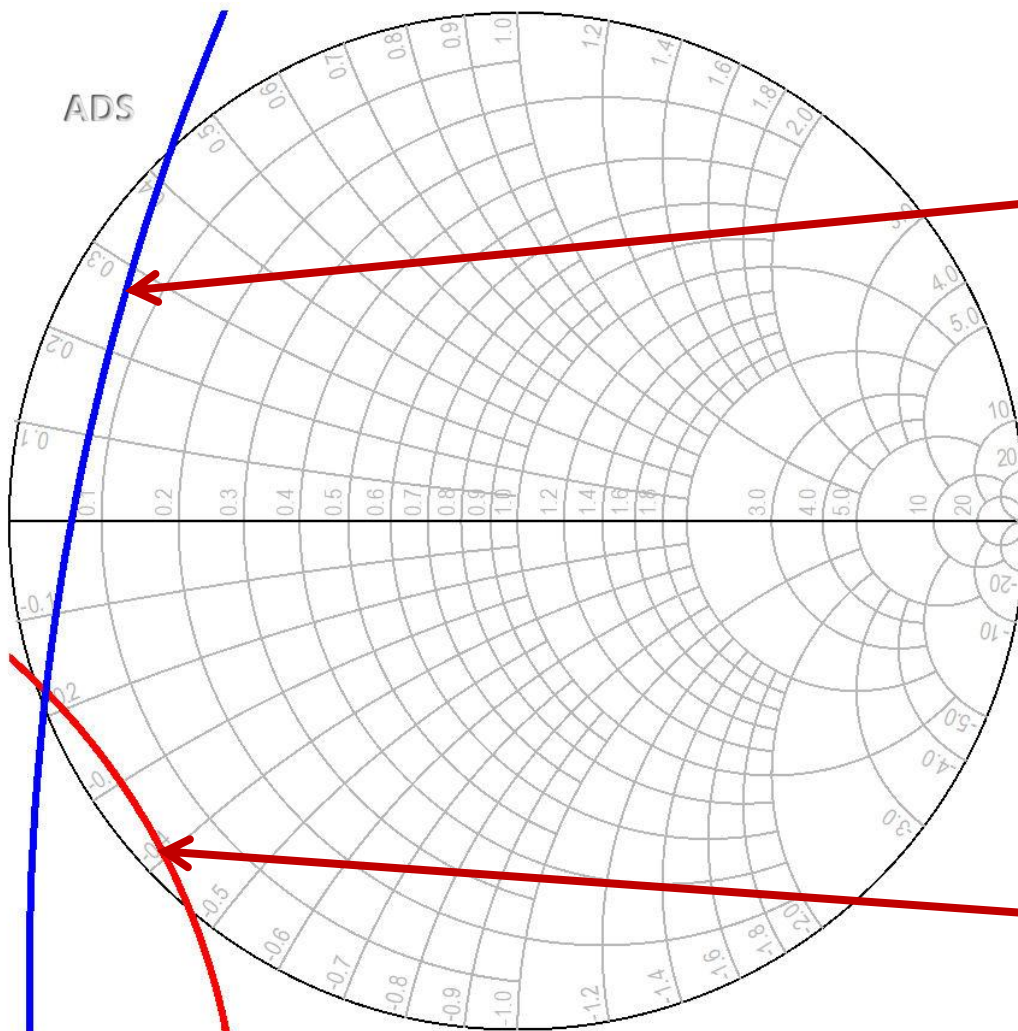


Continued

Amplifiers - Stability


Several possible positioning

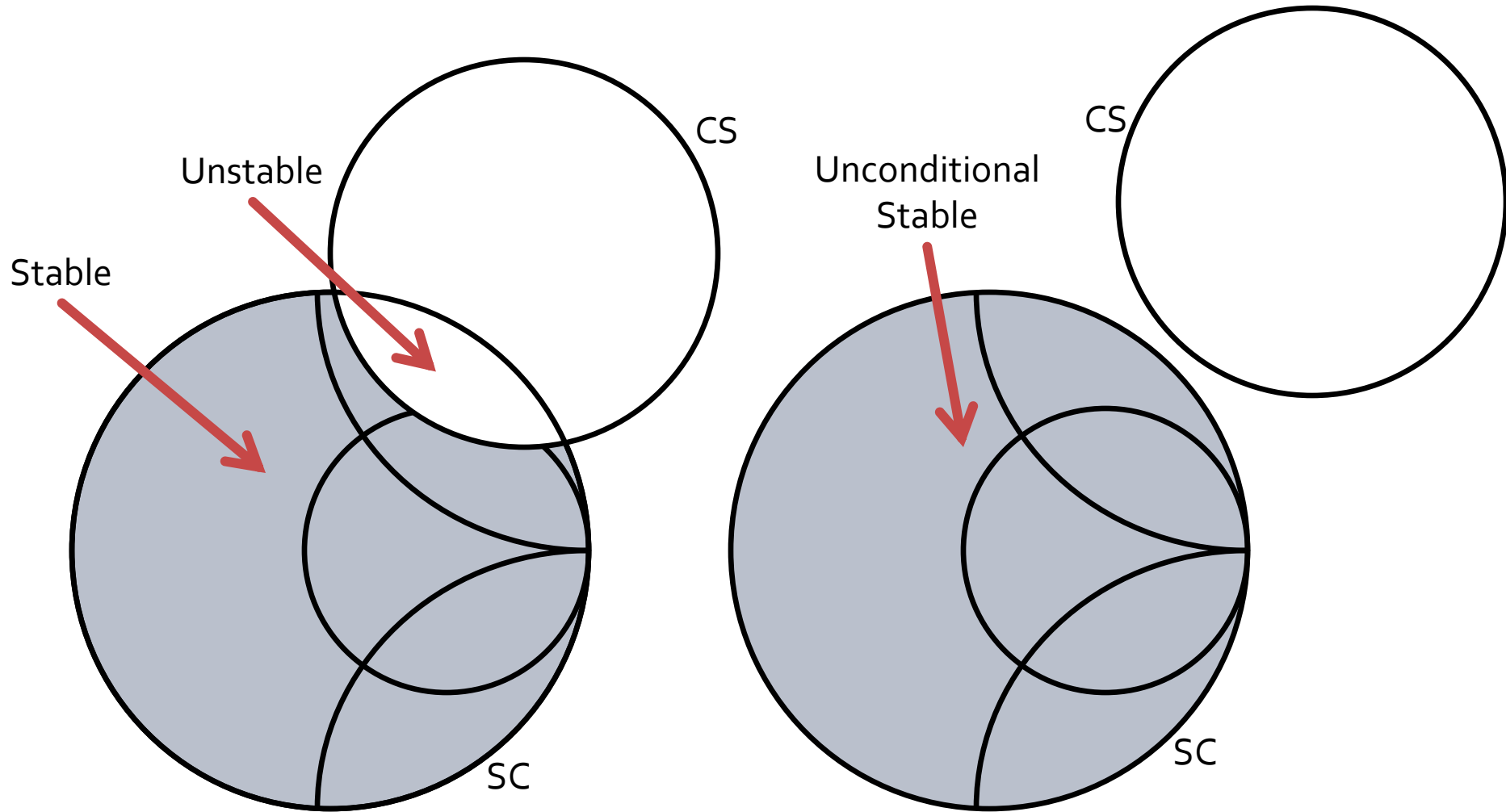



Several possible positioning

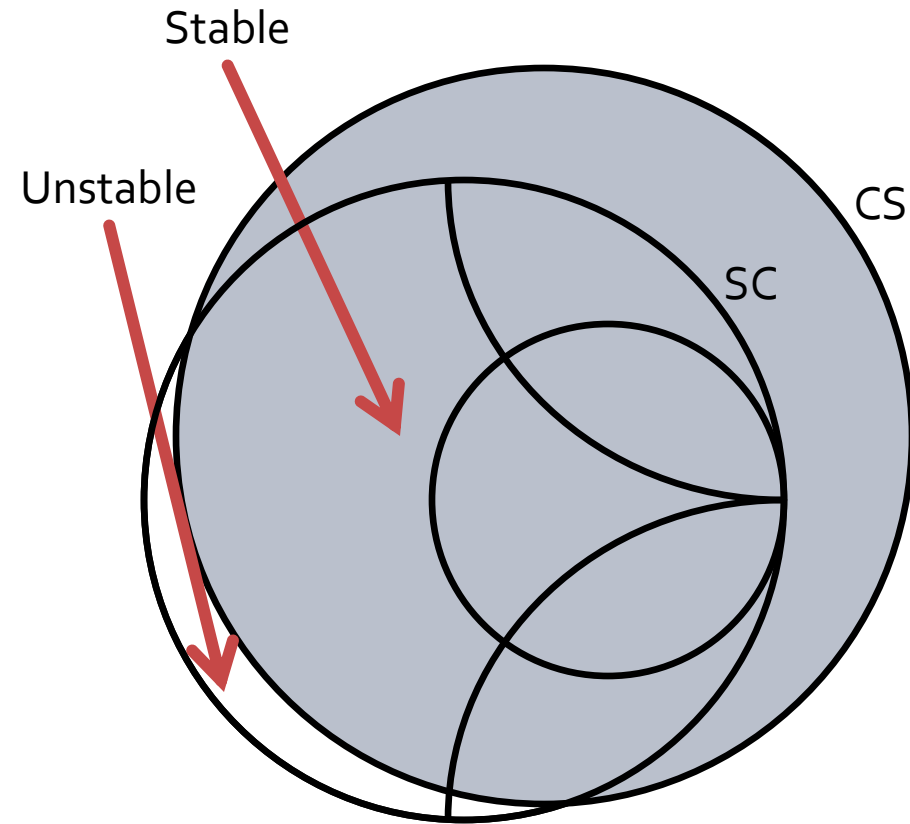

Unconditional
Stable

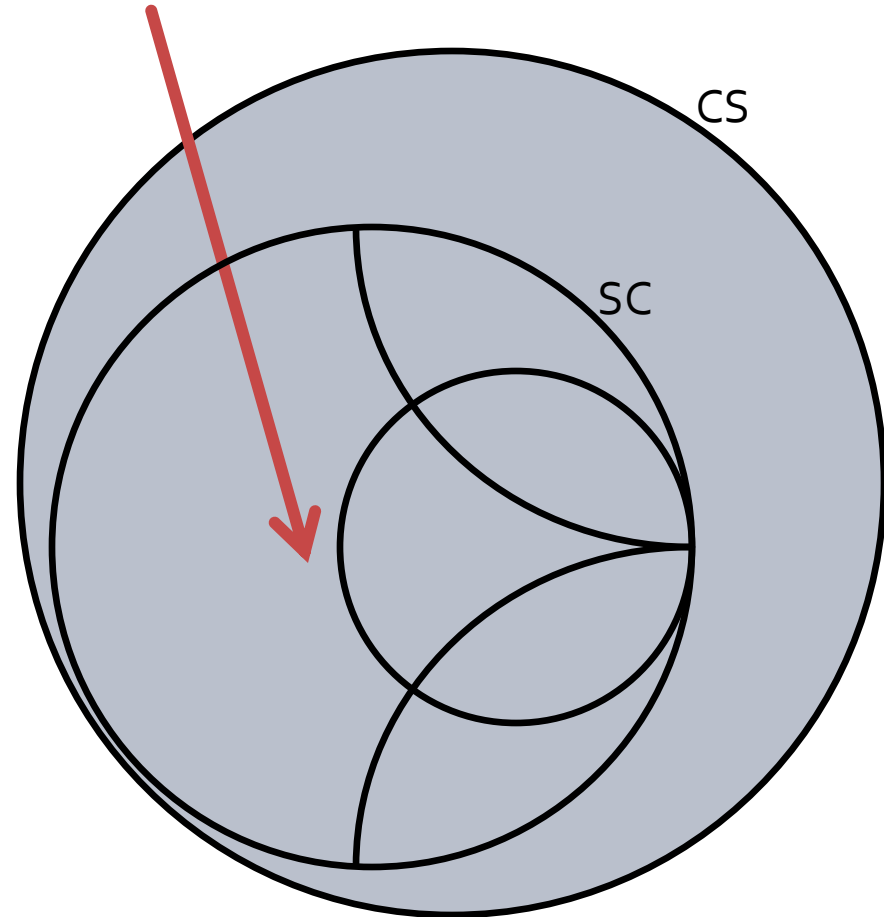

(Quite) Rare positioning

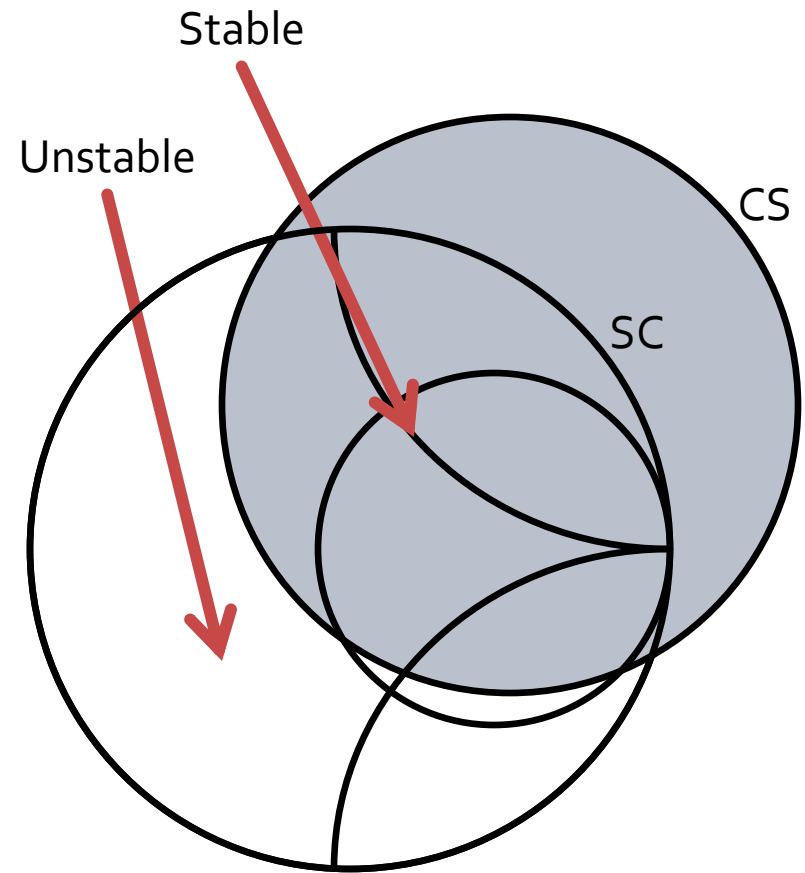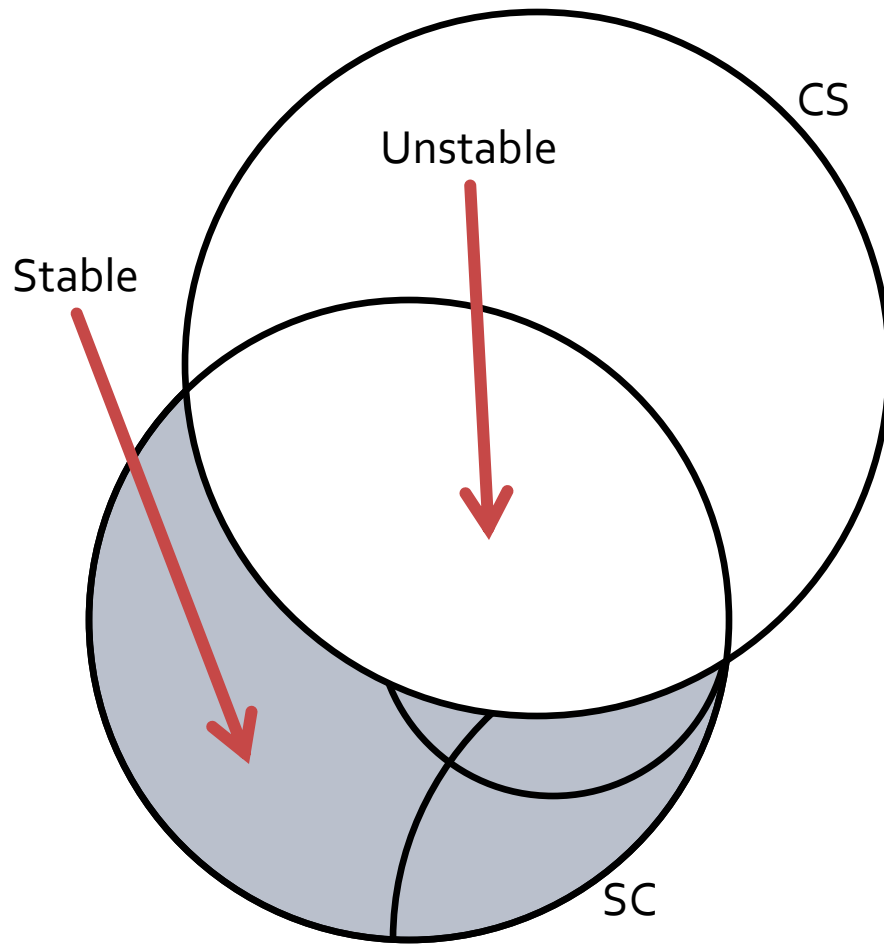

Stability

- **Unconditional stability:** the circuit is unconditionally stable if $|\Gamma_{in}| < 1$ and $|\Gamma_{out}| < 1$ for **any** passive impedance of the load/source
- **Conditional stability:** the circuit is conditionally stable if $|\Gamma_{in}| < 1$ and $|\Gamma_{out}| < 1$ only for **some** passive impedance of the load/source



Unconditional stability

- The two-port is unconditionally stable if:
 - The stability circle is disjoint with the Smith Chart (exterior to the Chart) and the stable region is outside the circle
 - The stability circle encloses the entire Smith Chart and the stable region is inside the circle
- One mandatory condition for unconditional stability is $|S_{11}| < 1$ (CSOUT) or $|S_{22}| < 1$ (CSIN) – if in at least one point the two-port is not stable then it cannot be unconditionally stable
- Mathematically :
$$\left\{ \begin{array}{l} \left| |C_L| - R_L \right| > 1 \\ |S_{11}| < 1 \end{array} \right. \quad \left\{ \begin{array}{l} \left| |C_S| - R_S \right| > 1 \\ |S_{22}| < 1 \end{array} \right.$$

Tests for Unconditional Stability

- Useful for wide frequency range analysis
- It is not enough to check the stability only at the operating frequencies
 - we must obtain stable operation for chosen Γ_L and Γ_S at **any** frequency

Circles in wide frequency range

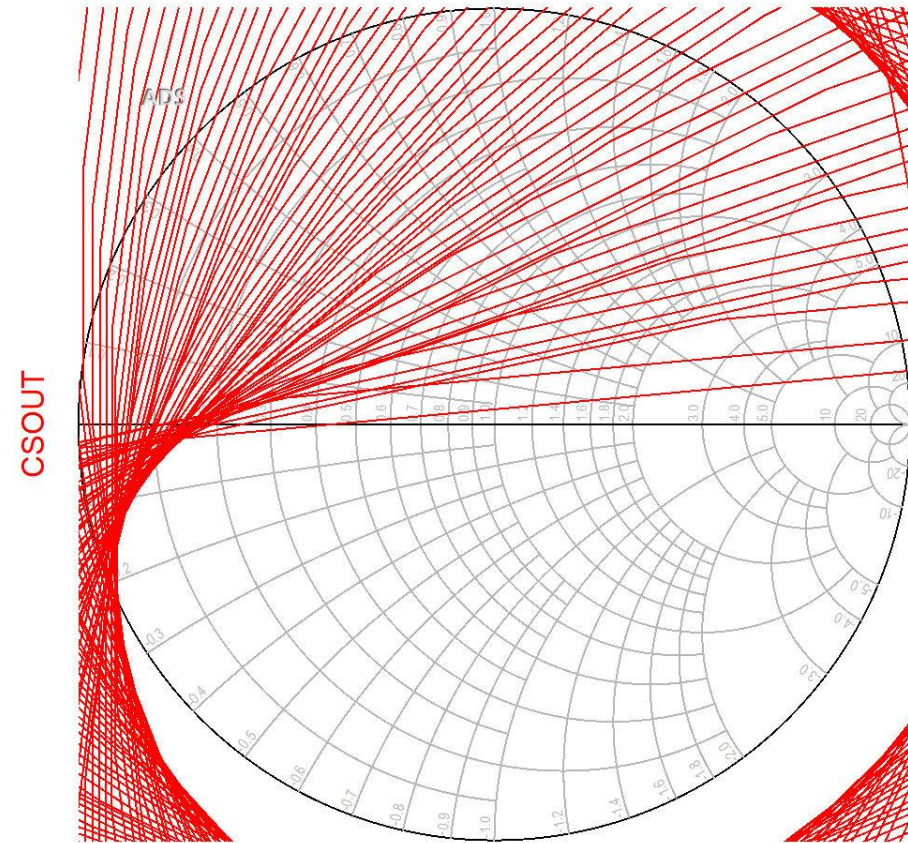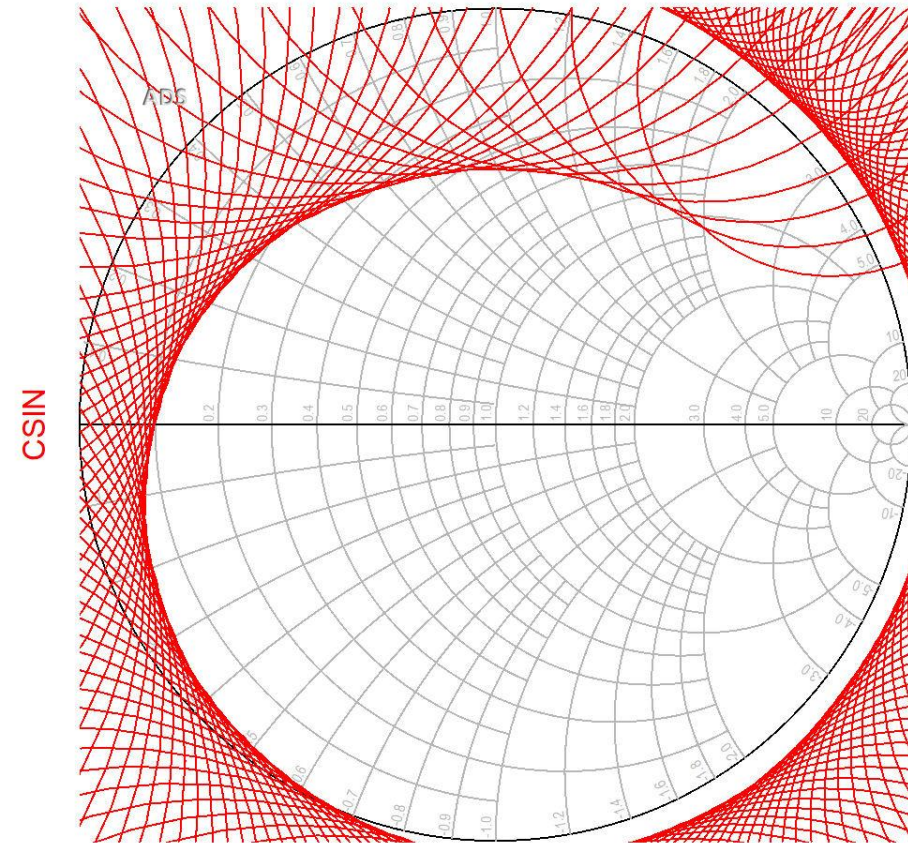

Rollet's condition

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 \cdot |S_{12} \cdot S_{21}|}$$

$$\Delta = S_{11} \cdot S_{22} - S_{12} \cdot S_{21}$$

- The two-port is **unconditionally stable** if:
- two conditions are simultaneously satisfied:
 - $K > 1$
 - $|\Delta| < 1$
- together with the implicit conditions:
 - $|S_{11}| < 1$
 - $|S_{22}| < 1$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 \cdot |S_{12} \cdot S_{21}|} > 1$$

$$|\Delta| = |S_{11} \cdot S_{22} - S_{12} \cdot S_{21}| < 1$$

μ Criterion

- Rollet's condition cannot be used to compare the relative stability of two or more devices because it involves constraints on two separate parameters, K and Δ

$$\mu = \frac{1 - |S_{11}|^2}{|S_{22} - \Delta \cdot S_{11}^*| + |S_{12} \cdot S_{21}|} > 1$$

- The two-port is **unconditionally stable** if:
 - $\mu > 1$
- together with the implicit conditions:
 - $|S_{11}| < 1$
 - $|S_{22}| < 1$
- In addition, it can be said that larger values of μ imply greater stability
 - μ is the distance from the center of the Smith Chart to the closest output stability circle

μ' Criterion


- Dual parameter to μ , determined in relation to the input stability circles

$$\mu' = \frac{1 - |S_{22}|^2}{|S_{11} - \Delta \cdot S_{22}^*| + |S_{12} \cdot S_{21}|} > 1$$

- The two-port is **unconditionally stable** if:
 - $\mu' > 1$
- together with the implicit conditions:
 - $|S_{11}| < 1$
 - $|S_{22}| < 1$
- In addition, it can be said that larger values of μ' imply greater stability
 - μ' is the distance from the center of the Smith Chart to the closest input stability circle


Rollet's condition

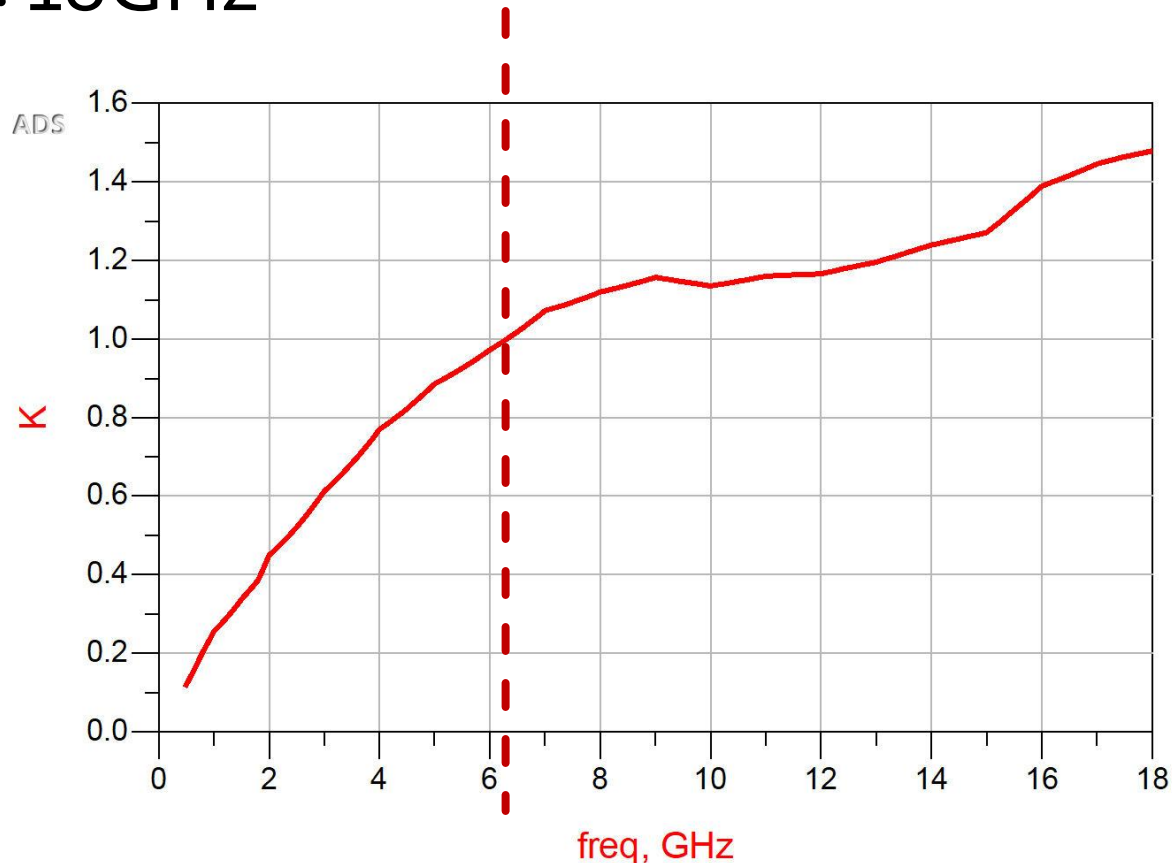- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz




μ Criterion

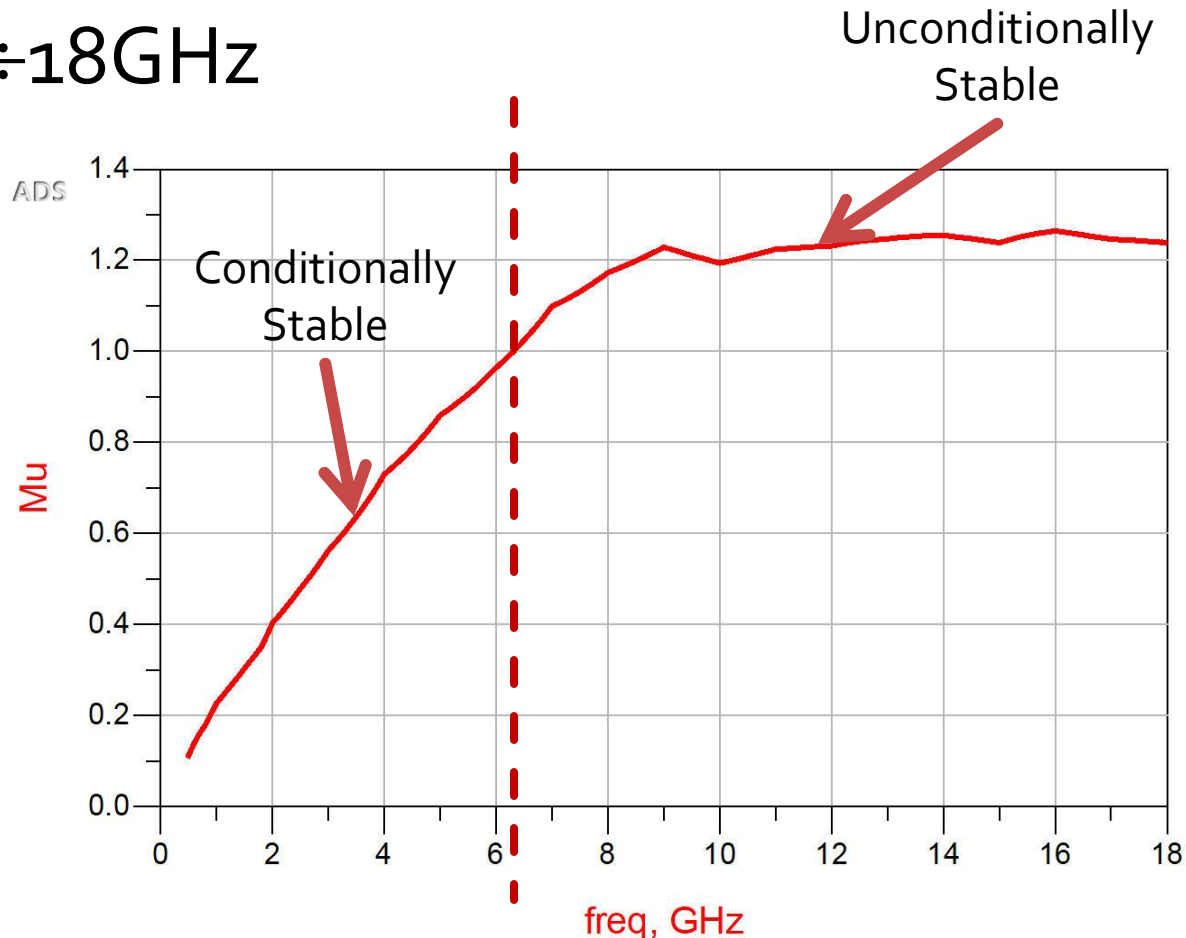- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz





μ' Criterion

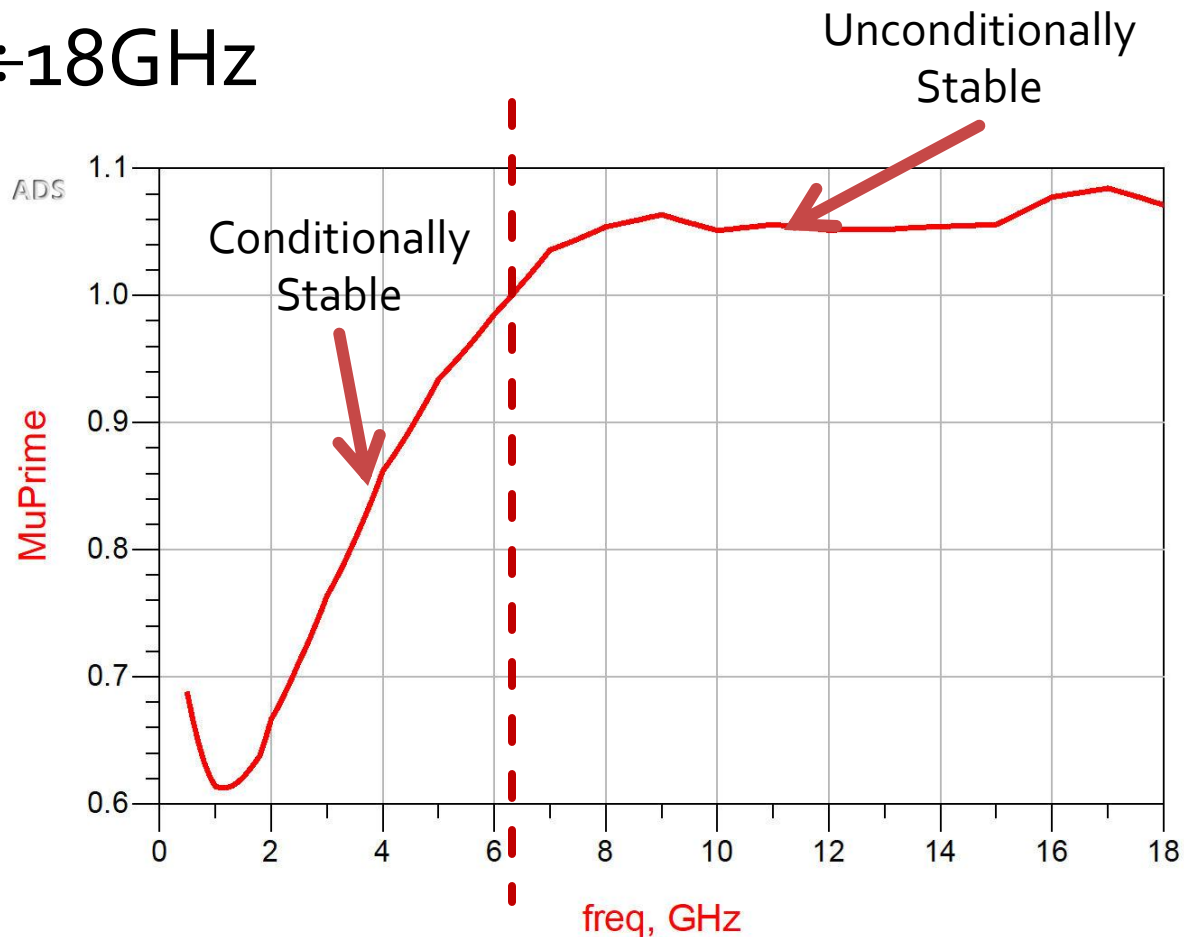- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz



Stability

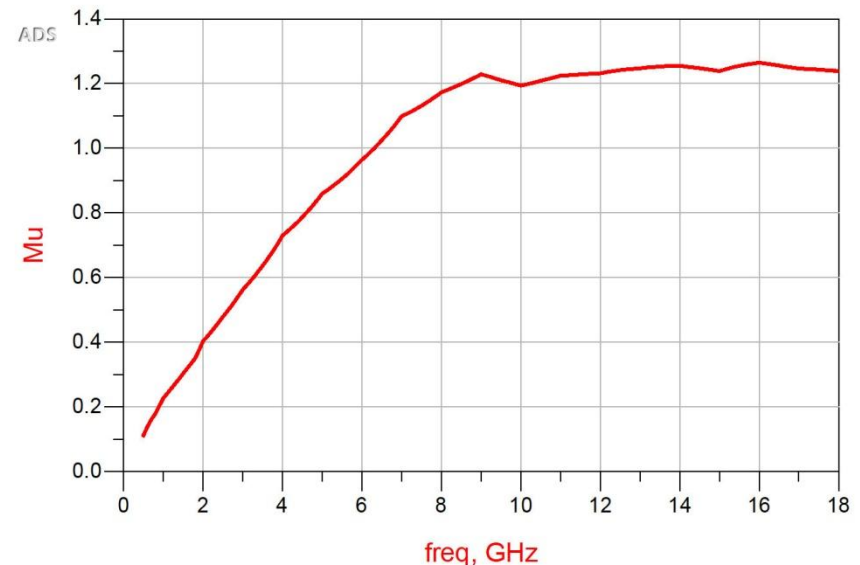
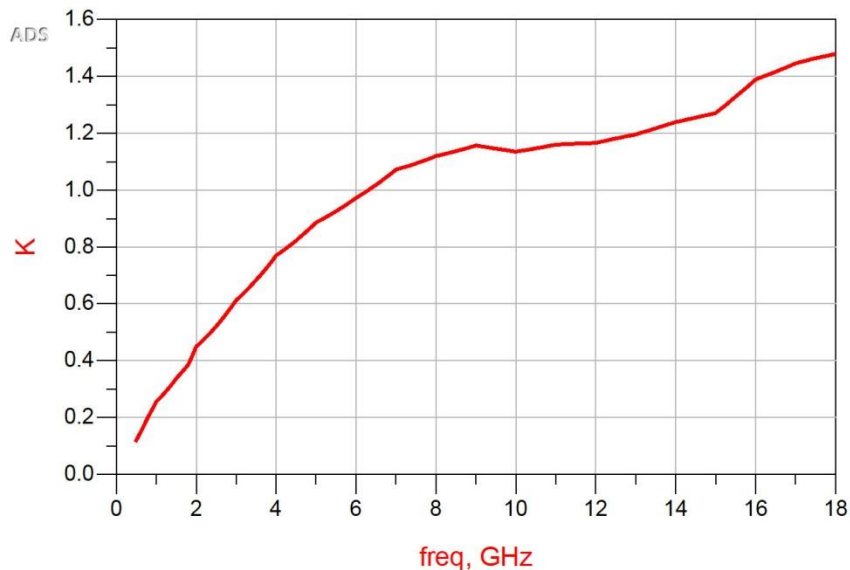
- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz
- unconditionally stable for $f > 6.31GHz$



Stabilization of two-port


- Unconditional stability in a wide frequency range has some important advantages
 - Ex: We can use ATF 34143 to design a (conditionally) stable amplifier at 5GHz, but this design is useless if the amplifier oscillates at 500MHz ($\mu \approx 0.1$)
- **The minimal requirement** when working with conditionally stable devices is to **check stability** at several frequencies over the operating bandwidth and outside the bandwidth
- Unconditional stability can be forced by inserting series/shunt resistors at two-port's input/output (with loss of gain!)

Input series resistor

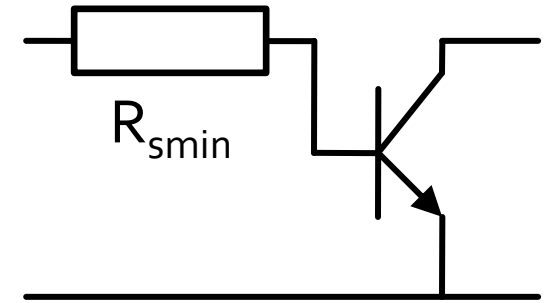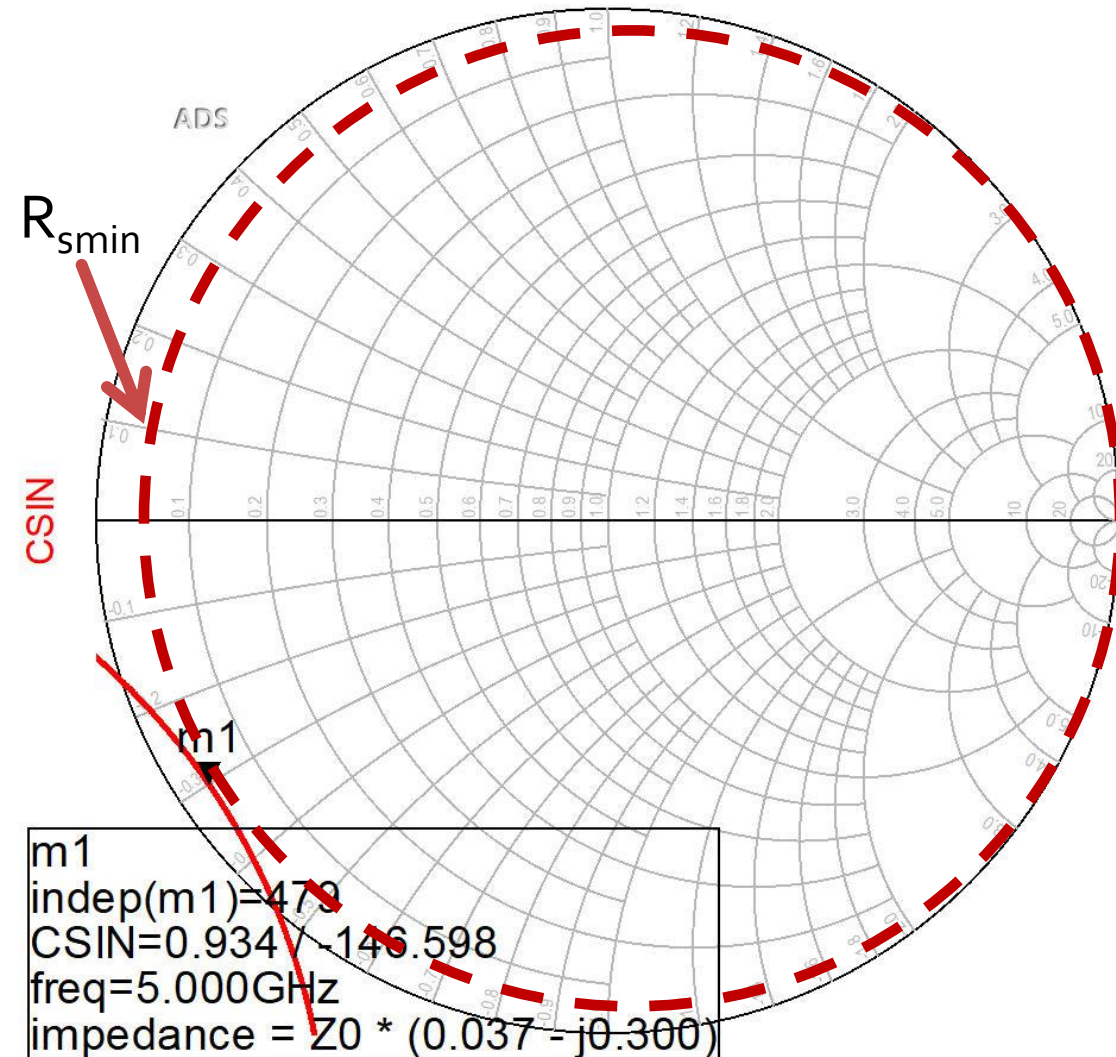



$$R_{smin} = 0.037 \cdot 50\Omega = 1.85\Omega$$

ADS, $R_s = 2\Omega$


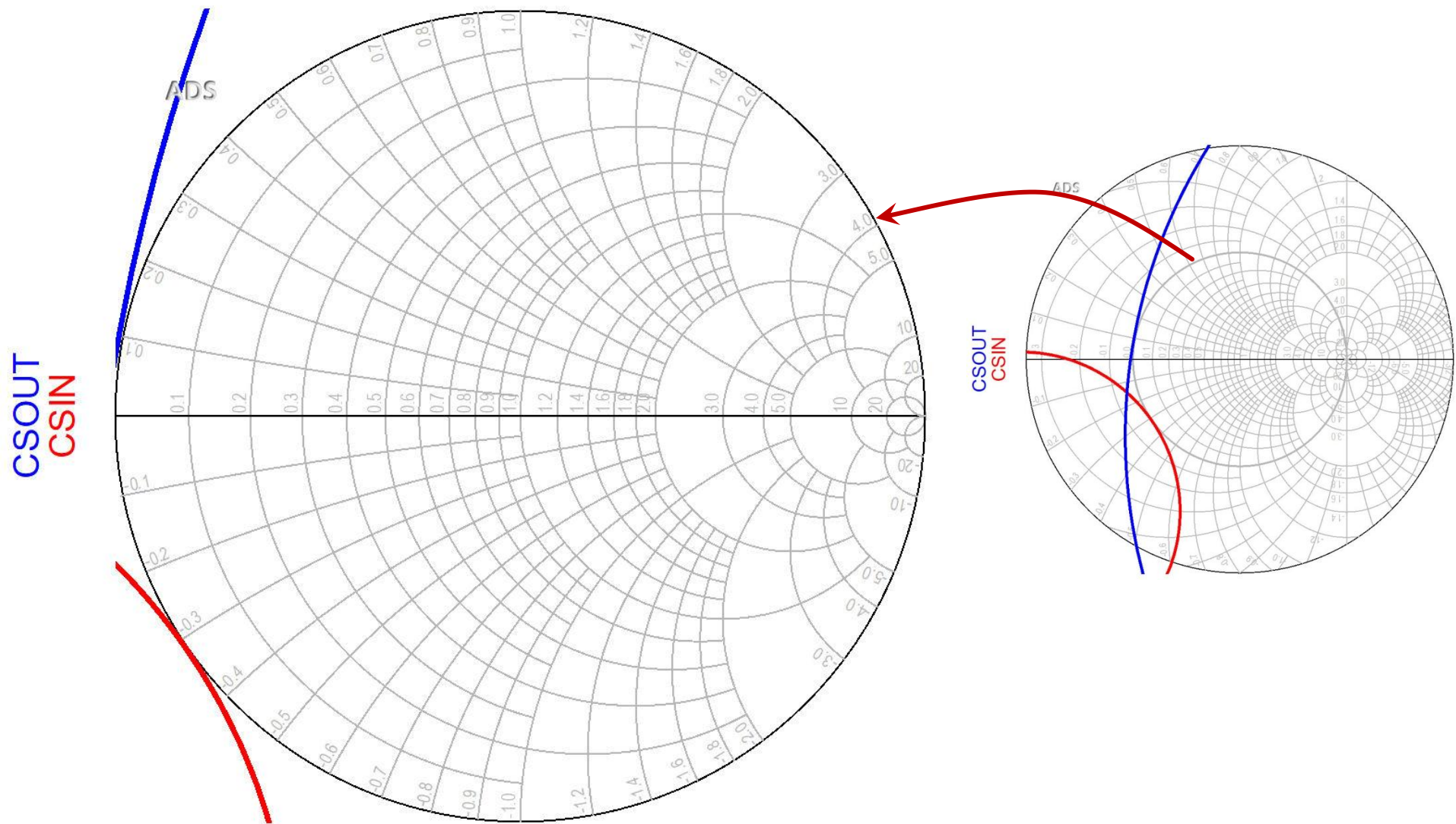


Input series resistor

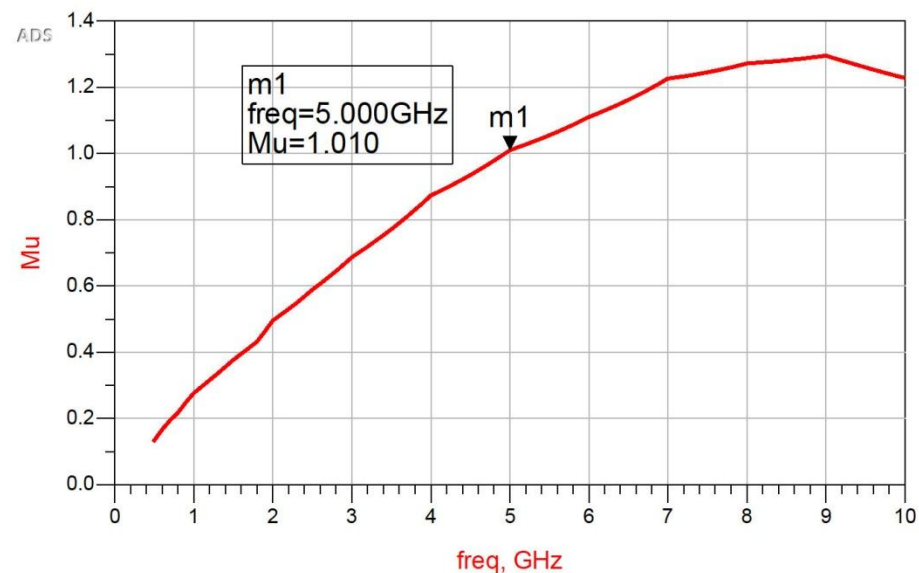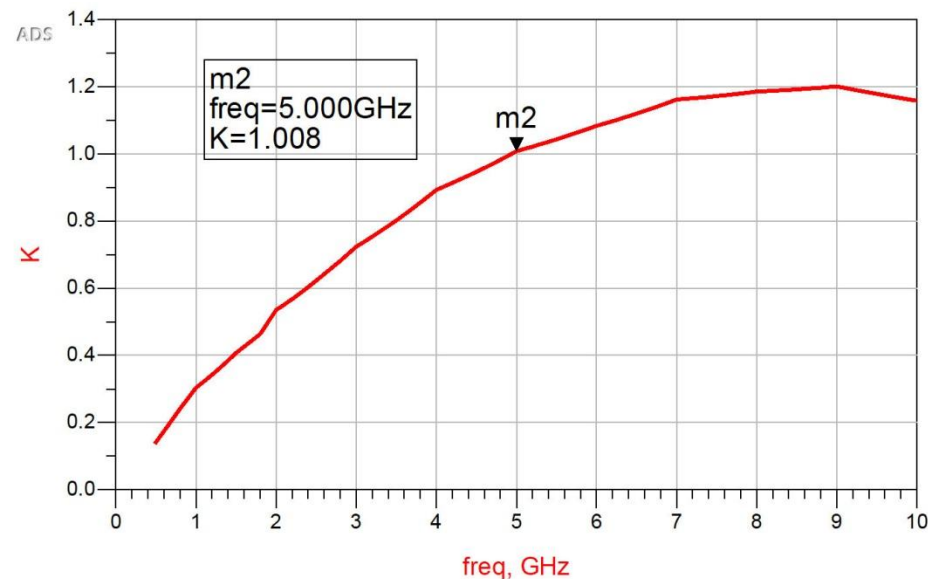- $R_s = 2\Omega$
- $K = 1.008$, $MAG = 13.694\text{dB}$ @ 5GHz
 - no stabilization, $K = 0.886$, $MAG = 14.248\text{dB}$ @ 5GHz



Input shunt resistor

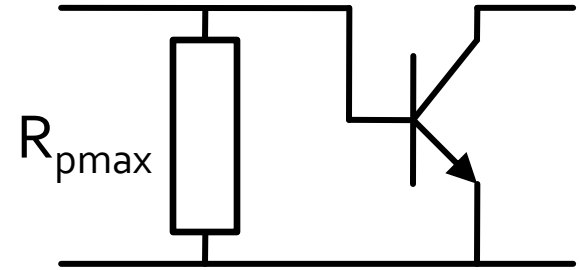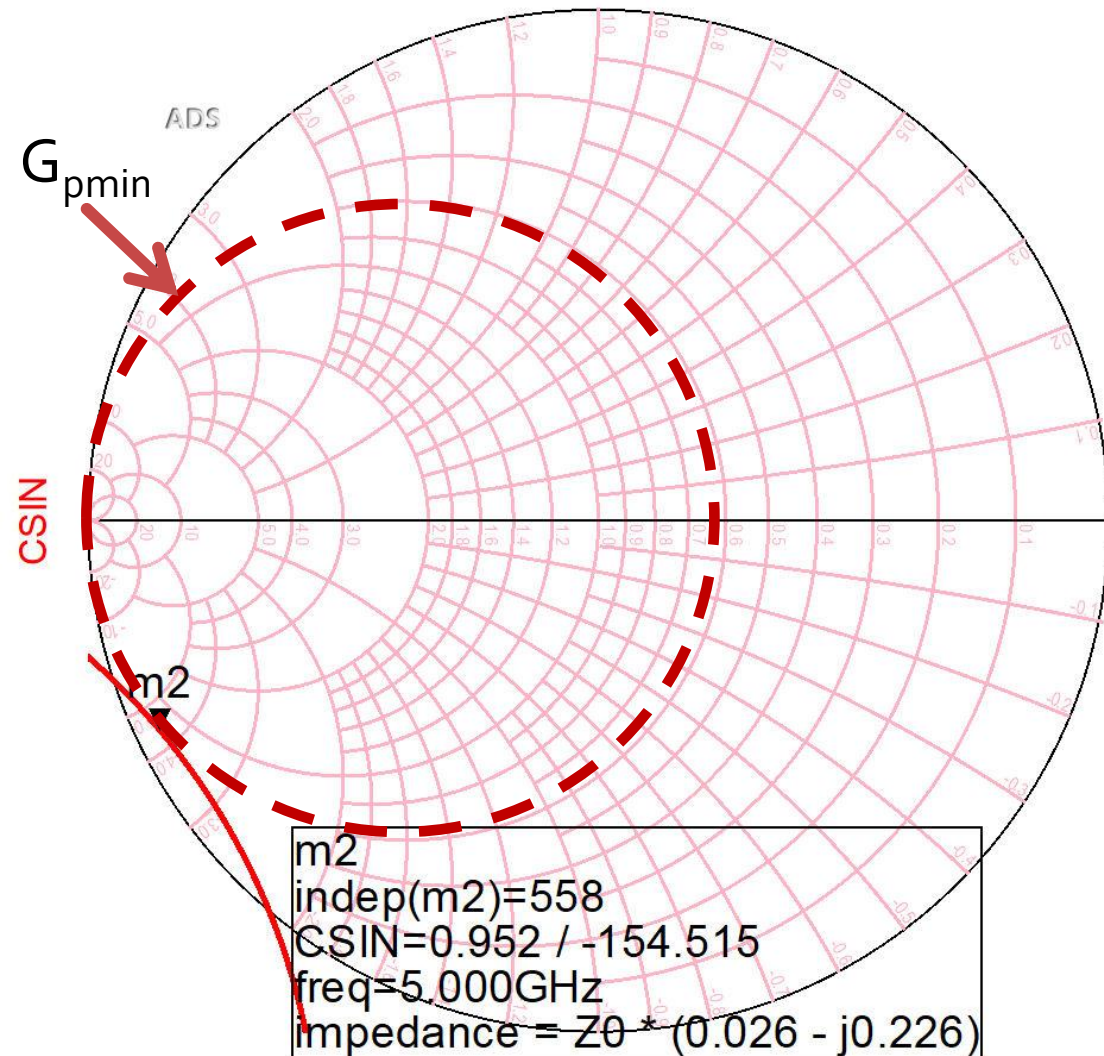


$$R_{p\max} = \frac{1}{G_{p\min}}$$

$$\frac{1}{0.026 - j \cdot 0.226} = 0.502 + j \cdot 4.367$$



$$R_{p\max} = \frac{50\Omega}{0.502} = 99.6\Omega$$

ADS, $R_p = 90\Omega$

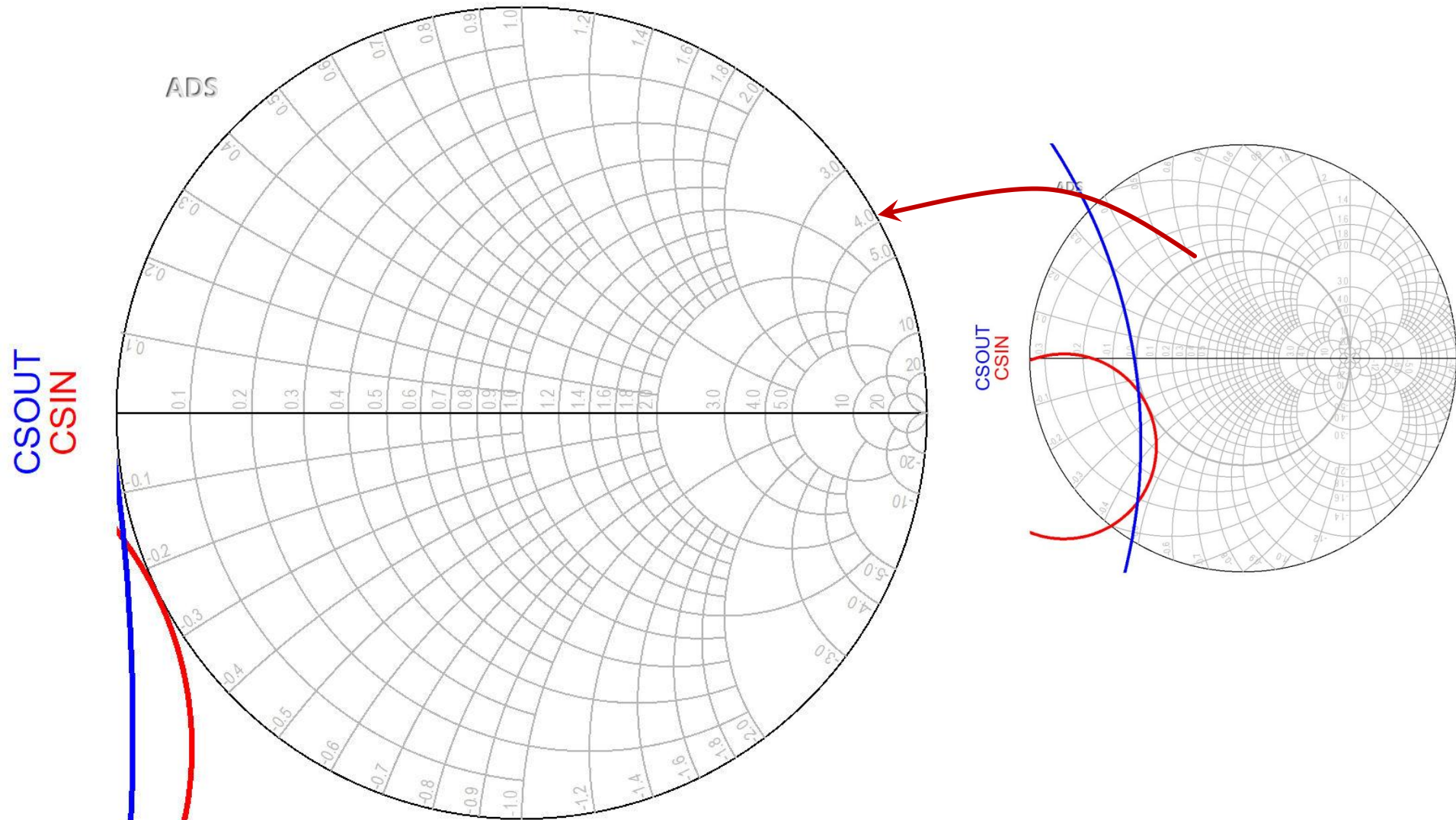



Input shunt resistor

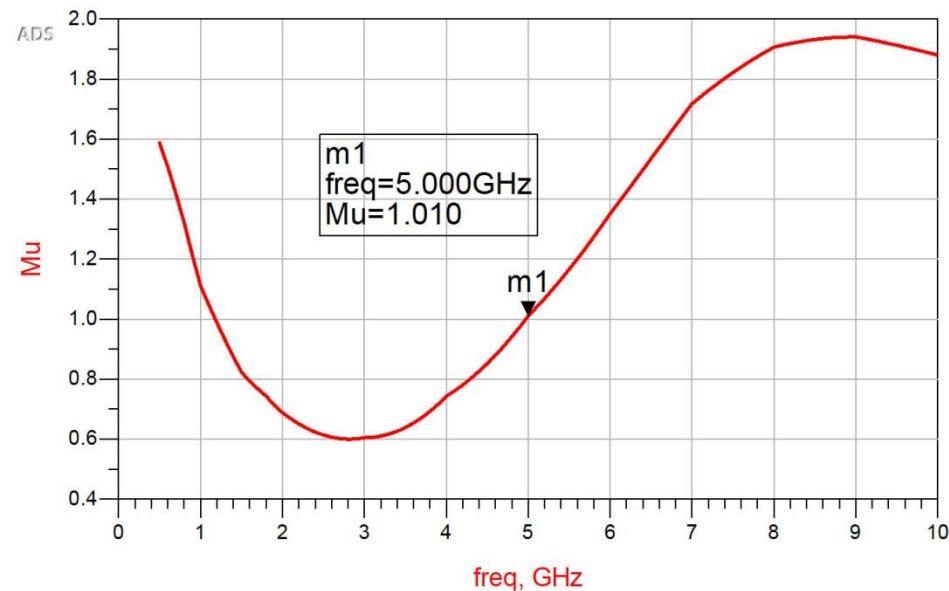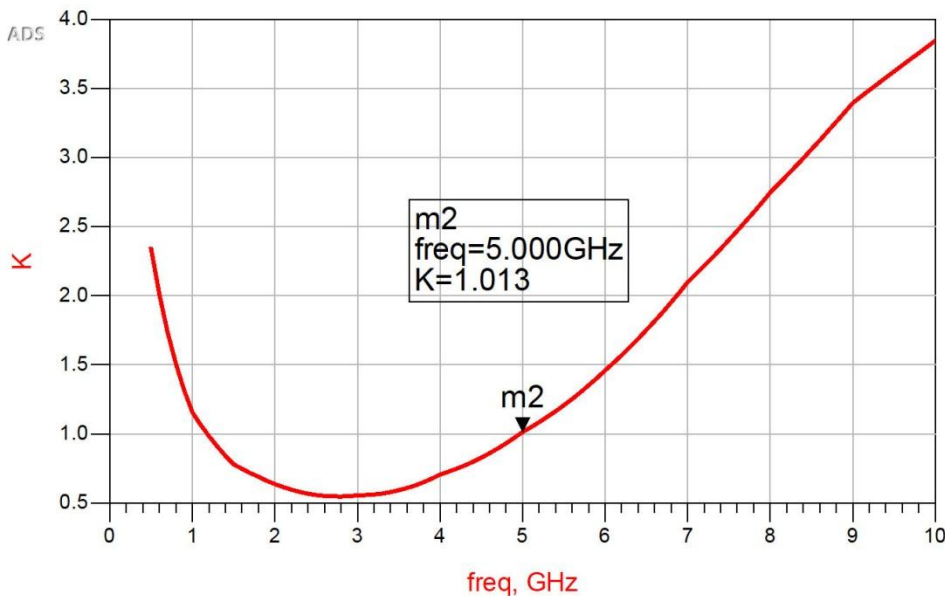- $R_p = 90\Omega$
- $K = 1.013$, $MAG = 13.561\text{dB}$ @ 5GHz
 - no stabilization, $K = 0.886$, $MAG = 14.248\text{dB}$ @ 5GHz



Output series/shunt resistor

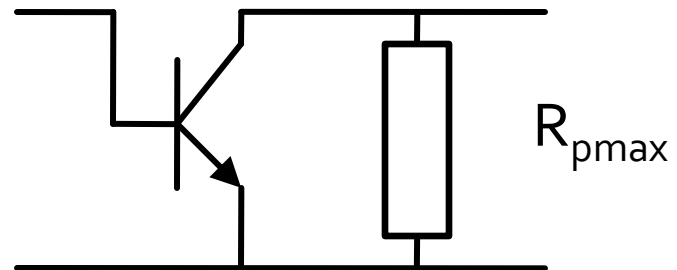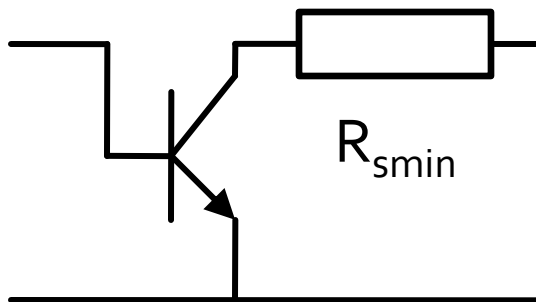
- The procedure can be applied similarly at the output (finding g/r circles tangent to CSOUT)
- From previous examples, resistive loading at the input has a positive effect over output stability and vice versa (resistive loading at the output, effect over input stability)



Stabilization of two-port

- Negative effect over the power gain
 - we must check MAG/MSG while designing resistive loading
- Negative effect over the noise (next lectures)
- We can choose one of the 4 possibilities or a combination which offers better results (depending on transistor, application etc.)
- We can use frequency selective loading
 - Ex: RL, RC circuits which sacrifice performance only when needed to improve stability and have no effect at frequencies where the device is already stable
- It might be possible (and should be checked) that stability is improved as an effect of parasitic elements of biasing circuits (bypass capacitors and RF chokes)

Stabilization of two-port

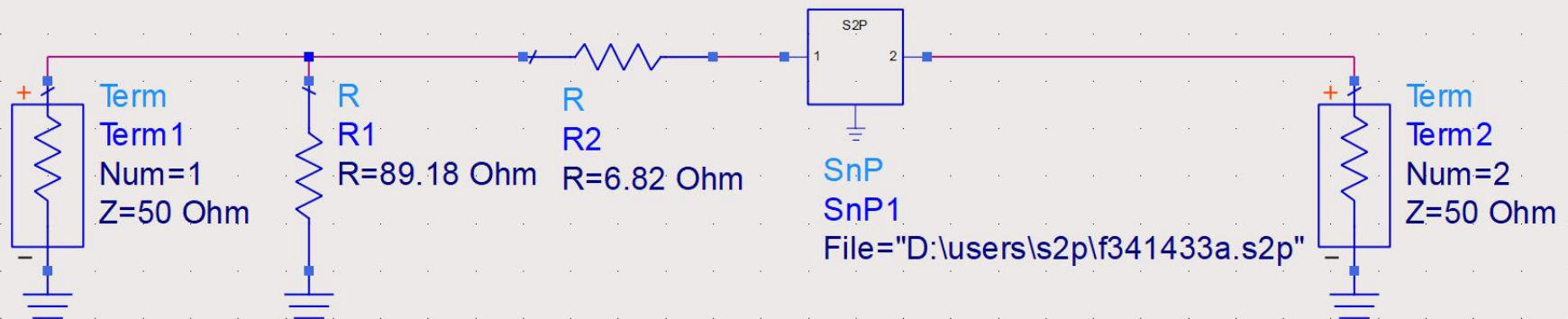

S-PARAMETERS


S_Param

SP1

Start=0.5 GHz

Stop=10.0 GHz

Step=0.1 GHz

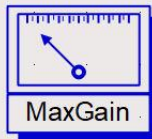


MaxGain

MaxGain

MAG

MAG=max_gain(S)

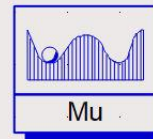


Mu

Mu

Mu1

Mu=mu(S)

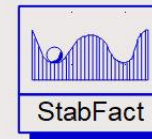



StabFact

StabFact


K

K=stab_fact(S)



Stabilization of two-port

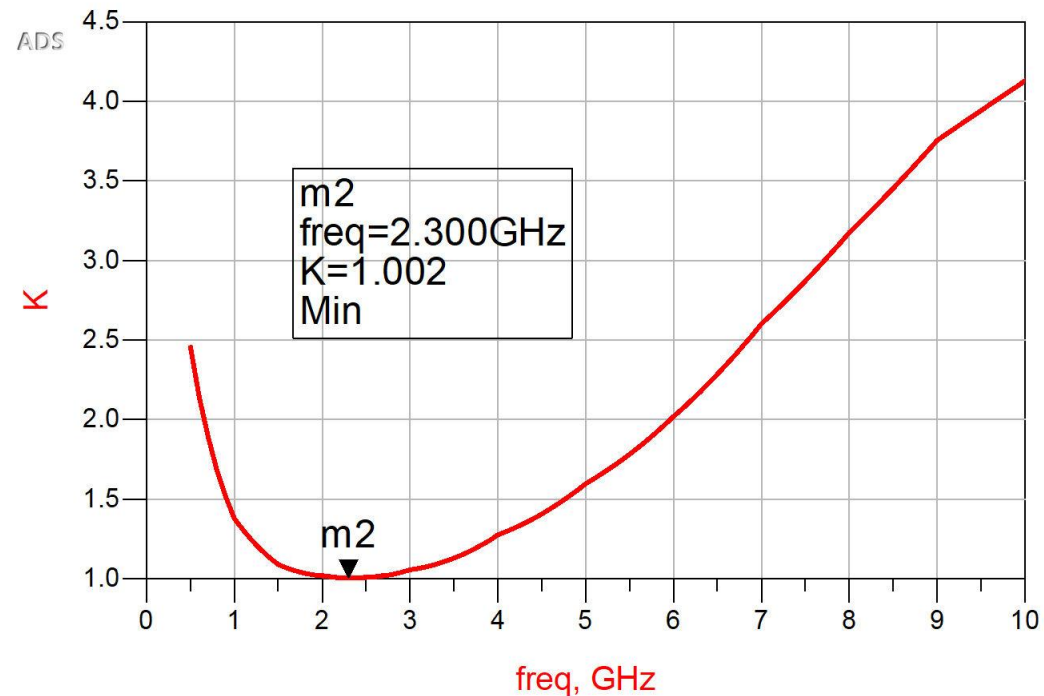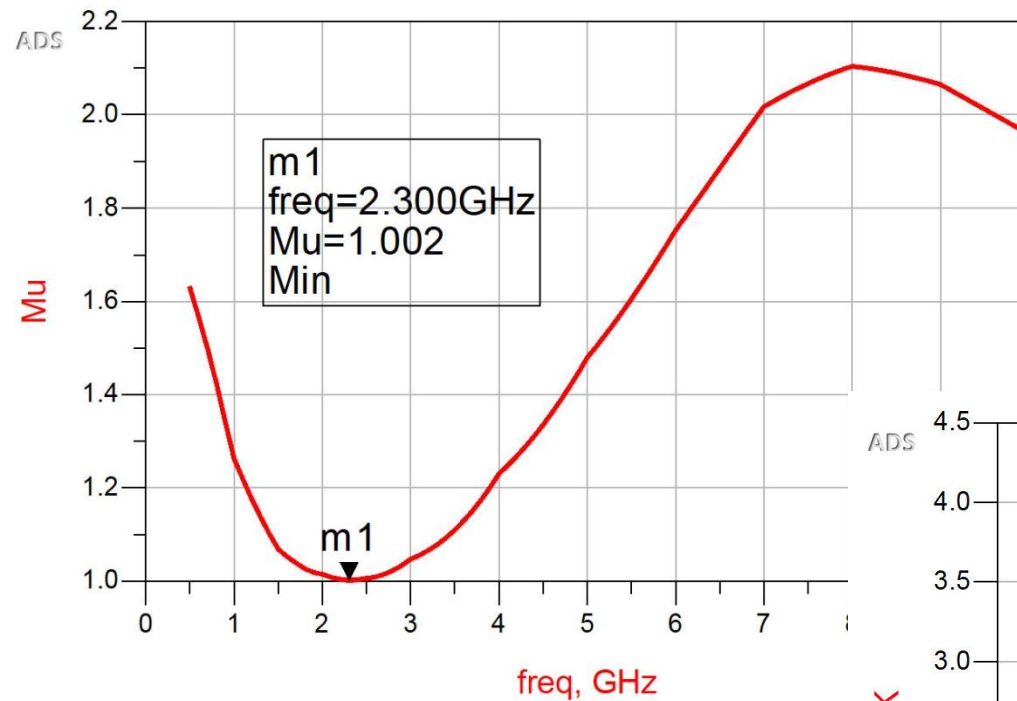

Stabilization of two-port

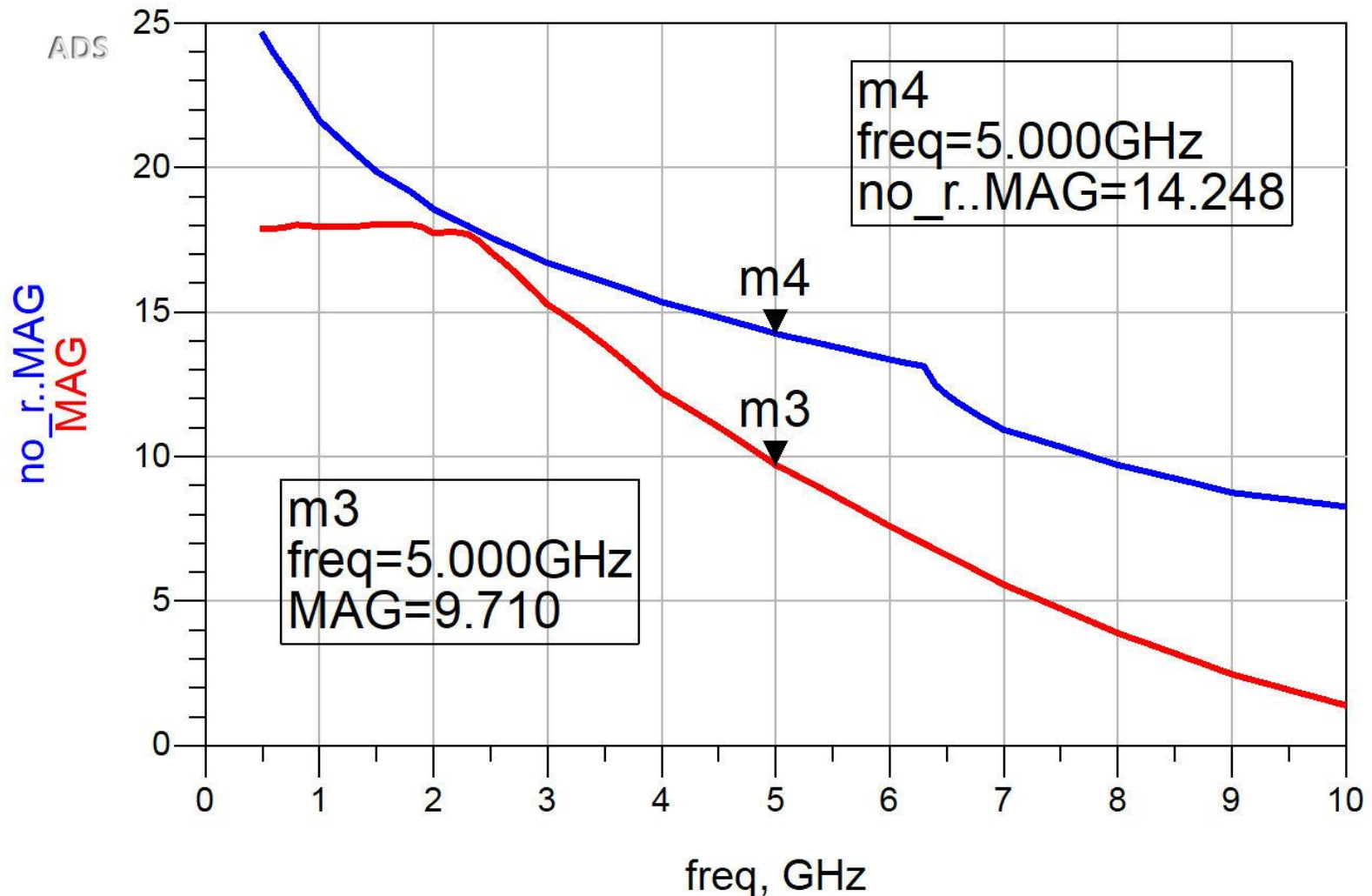

Stabilization of two-port

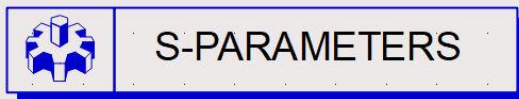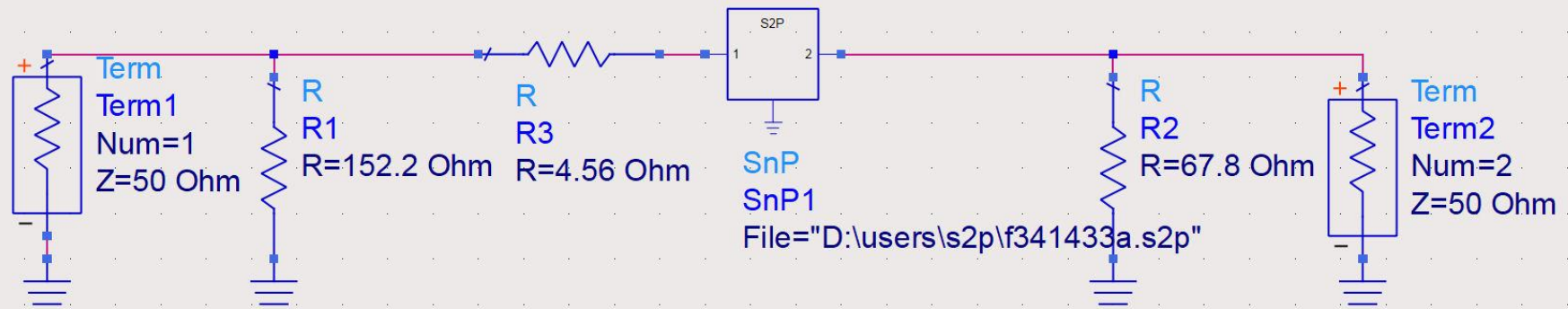


S_Param

SP1

Start=0.5 GHz

Stop=10.0 GHz


Step=0.1 GHz

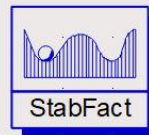

StabFact

K


$K=\text{stab_fact}(S)$

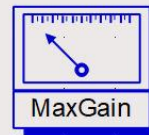

MaxGain

MAG

$\text{MAG}=\text{max_gain}(S)$


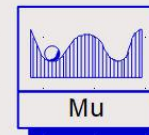


Mu


Mu1

$\text{Mu}=\text{mu}(S)$

Stabilization of two-port

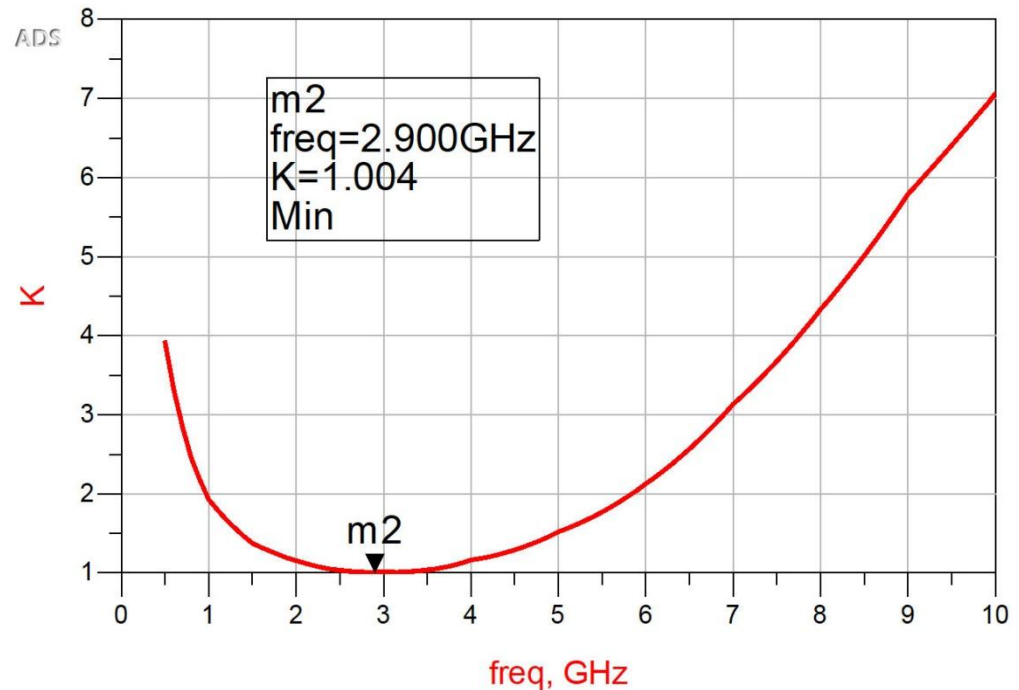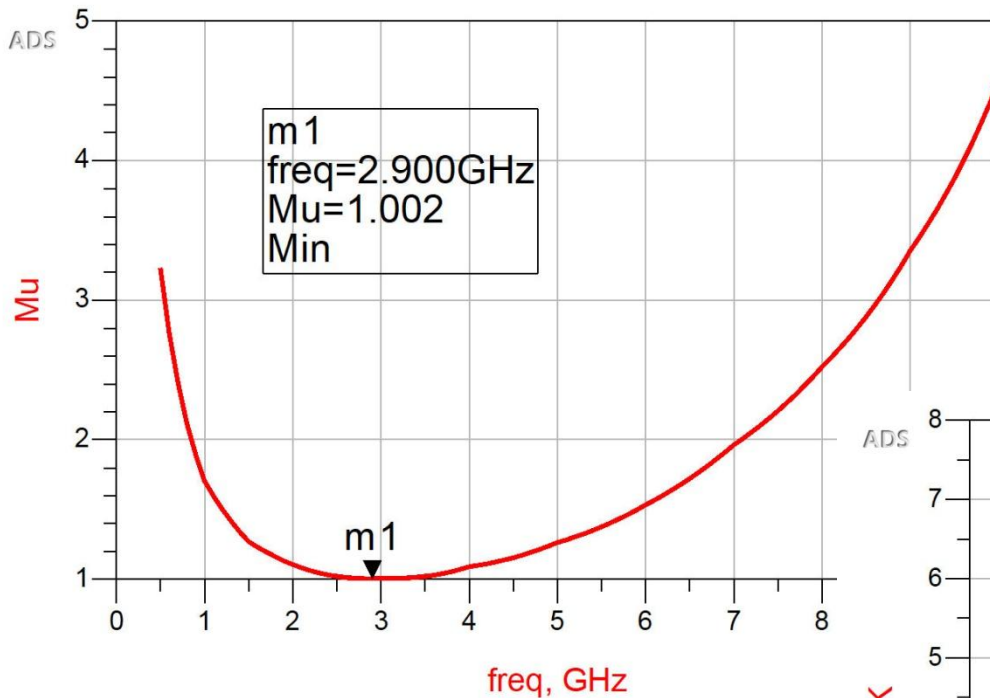


Stabilization of two-port

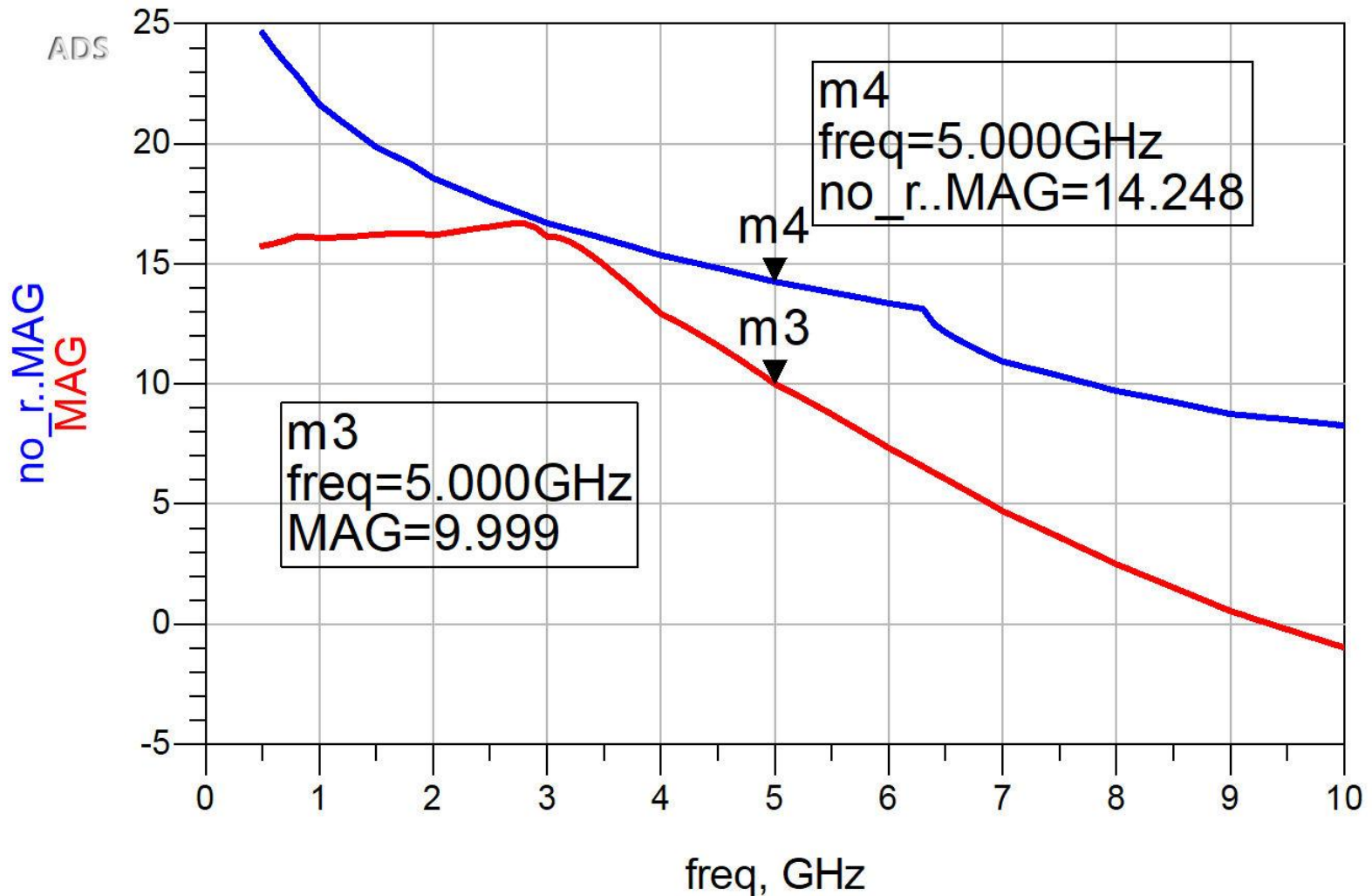

Power Gain of Microwave Amplifiers


Microwave Amplifiers

Amplifier as two-port

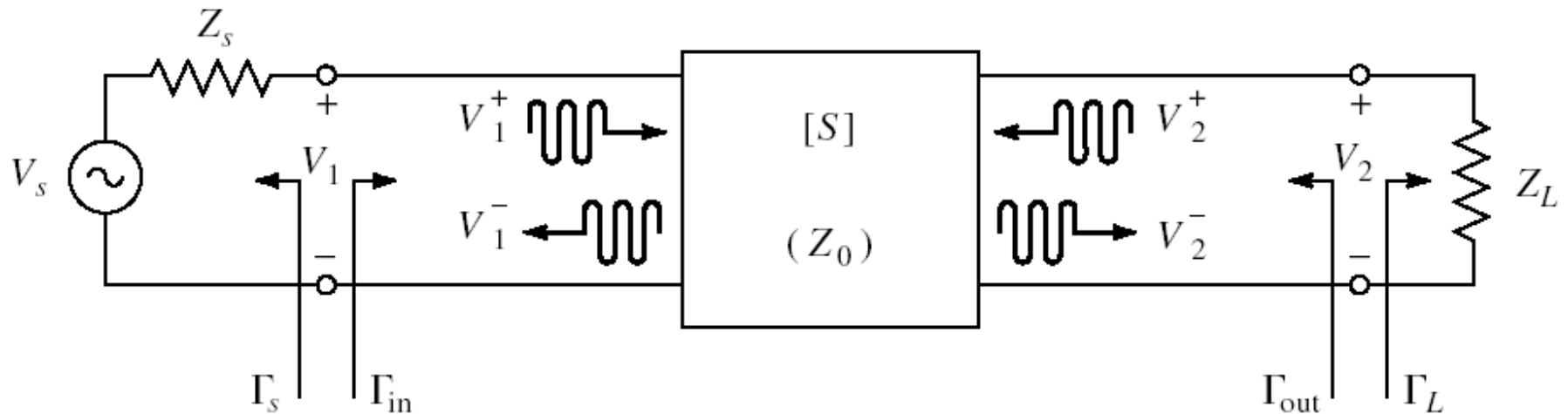

- For an amplifier two-port we are interested in:
 - stability
 - **power gain**
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)

Design for Maximum Gain

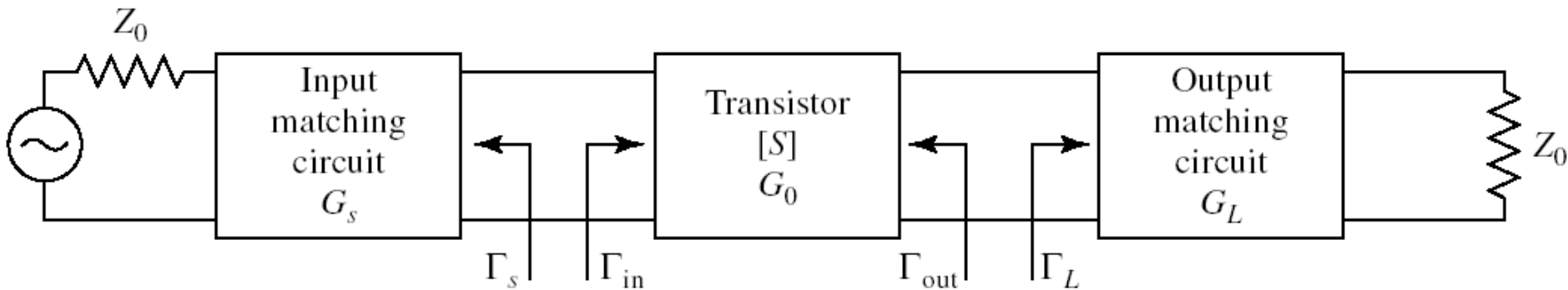

- Maximum power gain (complex conjugate matching):

$$\Gamma_{in} = \Gamma_S^* \quad \Gamma_{out} = \Gamma_L^*$$



- For lossless matching sections

$$G_{T\max} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2} \quad G_{T\max} = \frac{1}{1 - |\Gamma_S|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

- For the general case of the bilateral transistor ($S_{12} \neq 0$)

Γ_{in} and Γ_{out} depend on each other so the input and output sections must be matched simultaneously

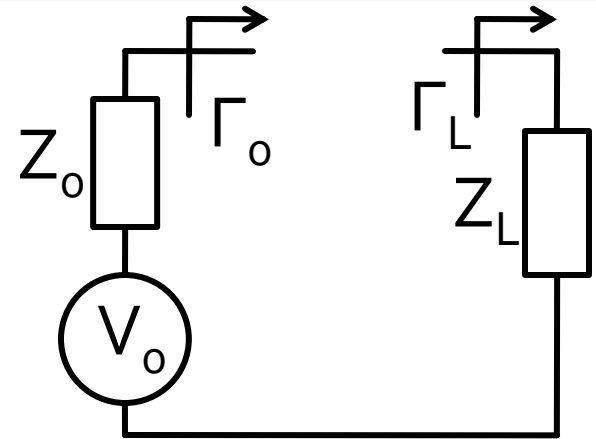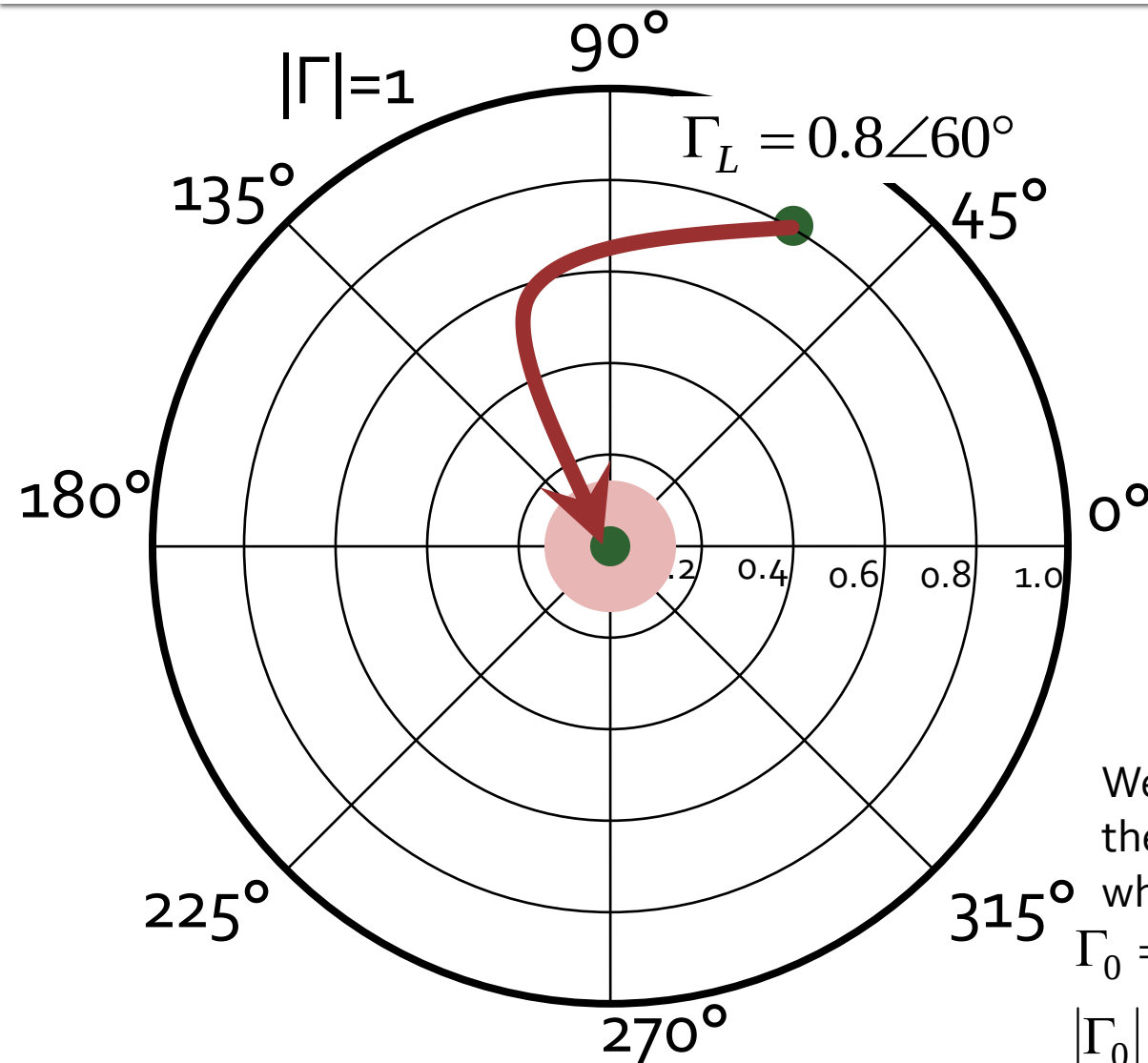The Smith Chart, matching, $Z_L \neq Z_o$



Matching Z_L load to Z_o source.
We normalize Z_L over Z_o

$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

$$z_L = 0.429 + j \cdot 1.65$$



$$\Gamma_L = 0.8 \angle 60^\circ$$

We must move the point denoting the reflection coefficient in the area where with a Z_o source we have:

$$\Gamma_0 = 0 \text{ perfect match}$$

$$|\Gamma_0| \leq \Gamma_m \text{ "good enough" match}$$

The Smith Chart, matching, $Z_L = Z_o$

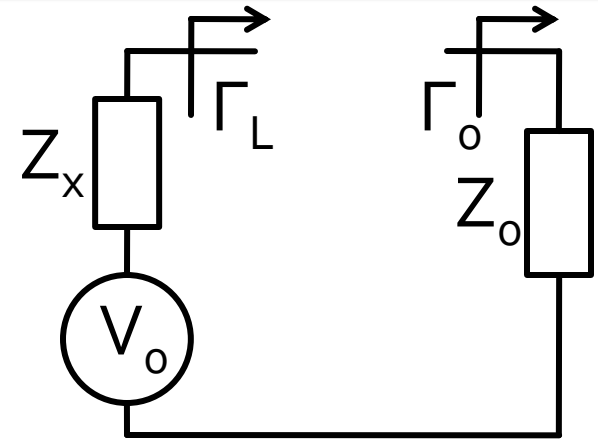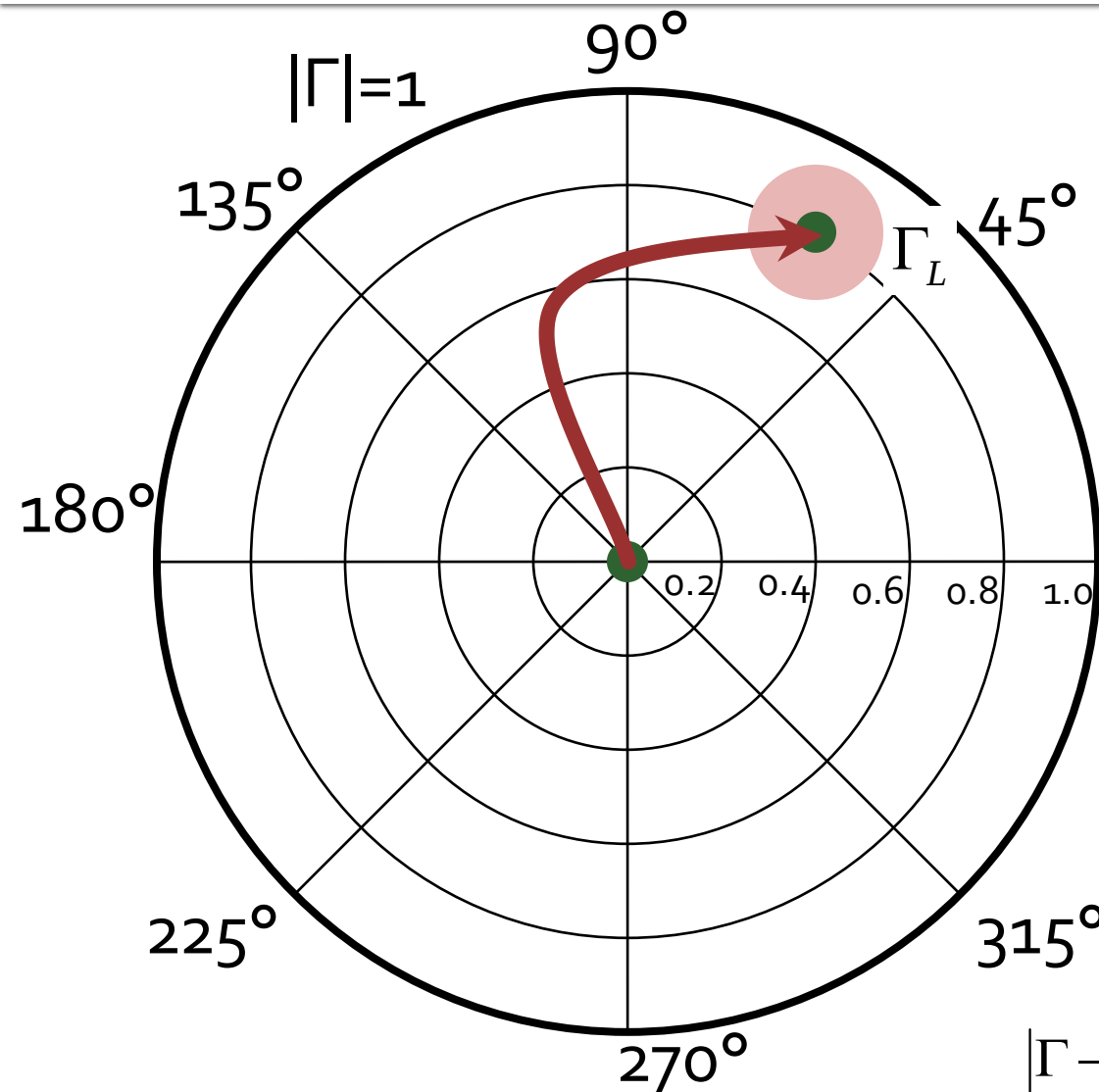

0° The source (eg. the transistor) having Z_x needs to see a certain reflection coefficient Γ_L towards the load Z_o


The matching circuit must move the point denoting the reflection coefficient in the area where for a Z_o load ($\Gamma_o = 0$) we see towards it:

$\Gamma = \Gamma_L$ perfect match

$|\Gamma - \Gamma_L| \leq \Gamma_m$ "good enough" match

The Smith Chart, matching ,

$Z_L \neq Z_o, Z_L = Z_o$

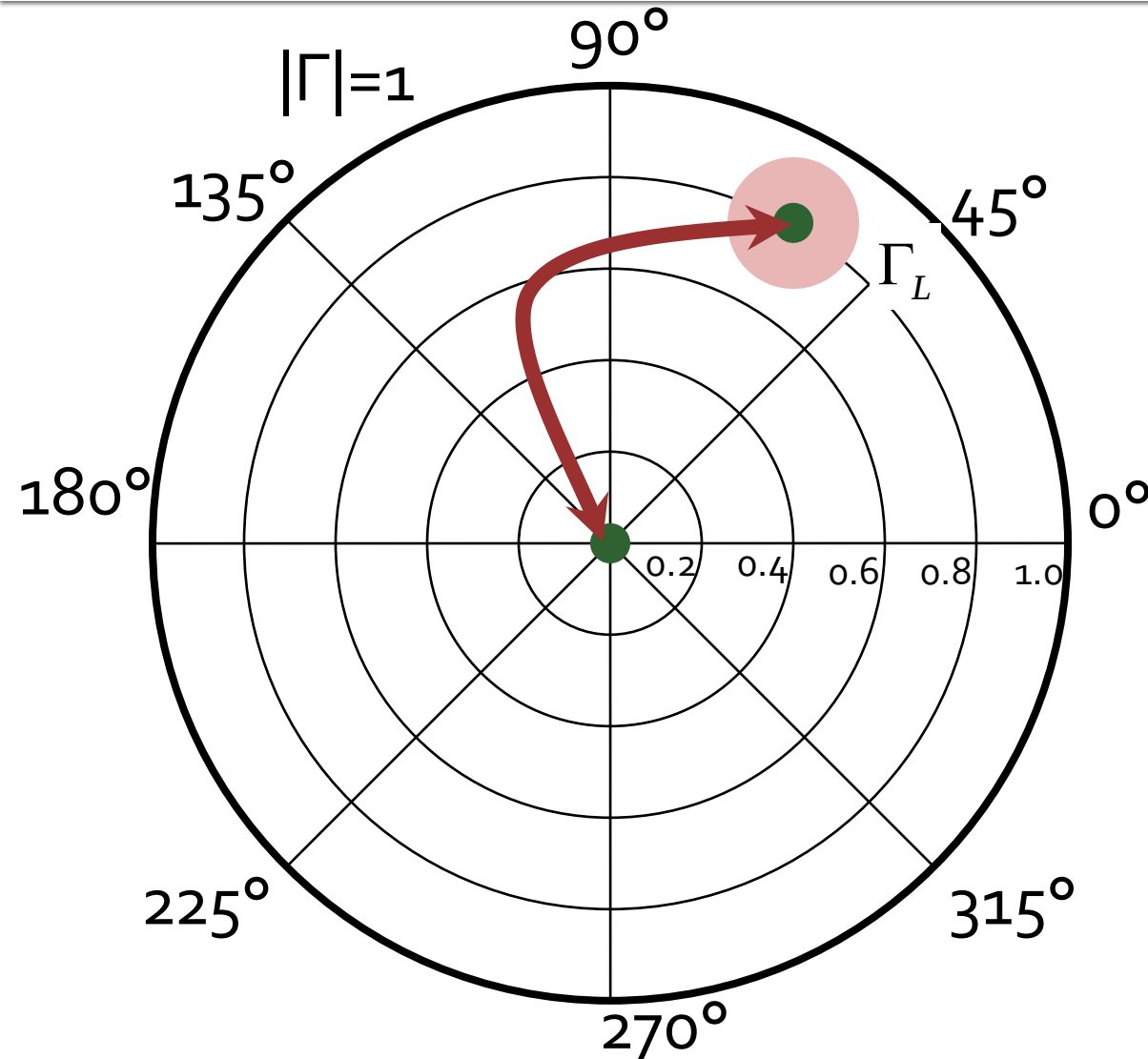

- The matching sections needed to move
 - Γ_L in Γ_o
 - Γ_o in Γ_L
- are **identical**. They differ only by the **order** in which the elements are introduced into the matching circuit
- As a result, we can use in match design the same:
 - **methods**
 - **formulae**

Simultaneous matching

$$\Gamma_{in} = \Gamma_S^*$$

$$\Gamma_{in} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_S^* = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_{out} = \Gamma_L^*$$

$$\Gamma_{out} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

$$\Gamma_L^* = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

- We find Γ_S

$$\Gamma_S = S_{11}^* + \frac{S_{12}^* \cdot S_{21}^*}{1/\Gamma_L^* - S_{22}^*}$$

$$\Gamma_L^* = \frac{S_{22} - \Delta \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

$$\Gamma_S \cdot (1 - |S_{22}|^2) + \Gamma_S^2 \cdot (\Delta \cdot S_{22}^* - S_{11}) = \Gamma_S \cdot (\Delta \cdot S_{11}^* \cdot S_{22}^* - |S_{22}|^2 - \Delta \cdot S_{12}^* \cdot S_{21}^*) + S_{11}^* \cdot (1 - |S_{22}|^2) + S_{12}^* \cdot S_{21}^* \cdot S_{22}$$

Simultaneous matching

$$\Delta \cdot (S_{11}^* \cdot S_{22}^* - S_{12}^* \cdot S_{21}^*) = |\Delta|^2$$

$$\Gamma_S^2 \cdot (S_{11} - \Delta \cdot S_{22}^*) + \Gamma_S \cdot (|\Delta|^2 - |S_{11}|^2 + |S_{22}|^2 - 1) + (S_{11}^* - \Delta^* \cdot S_{22}) = 0$$

- A quadratic equation

$$\Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

- Similarly

$$\Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

- With variables defined as:

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases} \quad \begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

Simultaneous matching

- Simultaneous matching is possible if:

$$B_1^2 - 4 \cdot |C_1|^2 > 0 \quad B_2^2 - 4 \cdot |C_2|^2 > 0$$

$$\Delta \cdot (S_{11}^* \cdot S_{22}^* - S_{12}^* \cdot S_{21}^*) = |\Delta|^2$$

$$|C_1|^2 = |S_{11} - \Delta \cdot S_{22}^*|^2 = |S_{12}|^2 \cdot |S_{21}|^2 + (1 - |S_{22}|^2) \cdot (|S_{11}|^2 - |\Delta|^2)$$

$$B_1^2 - 4 \cdot |C_1|^2 = (1 + |S_{11}|^2)^2 + (|S_{22}|^2 + |\Delta|^2)^2 - \\ - 2 \cdot (1 + |S_{11}|^2) \cdot (|S_{22}|^2 + |\Delta|^2) - 4 \cdot |S_{12} \cdot S_{21}|^2 - 4 \cdot (1 - |S_{22}|^2) \cdot (|S_{22}|^2 - |\Delta|^2)$$

$$B_1^2 - 4 \cdot |C_1|^2 = (1 + |S_{11}|^2)^2 + (|S_{22}|^2 + |\Delta|^2)^2 - \\ - 4 \cdot |S_{11}|^2 - 4 \cdot |S_{22}|^2 \cdot |\Delta|^2 - 2 \cdot (1 - |S_{11}|^2) \cdot (|S_{22}|^2 - |\Delta|^2) - 4 \cdot |S_{12} \cdot S_{21}|^2$$

Simultaneous matching

$$B_1^2 - 4 \cdot |C_1|^2 = \left(1 + |S_{11}|^2\right)^2 + \left(|S_{22}|^2 + |\Delta|^2\right)^2 - 4 \cdot |S_{11}|^2 - 4 \cdot |S_{22}|^2 \cdot |\Delta|^2 - 2 \cdot \left(1 - |S_{11}|^2\right) \cdot \left(|S_{22}|^2 - |\Delta|^2\right) - 4 \cdot |S_{12} \cdot S_{21}|^2$$

$$B_1^2 - 4 \cdot |C_1|^2 = \left(1 - |S_{11}|^2\right)^2 + \left(|S_{22}|^2 - |\Delta|^2\right)^2 - 2 \cdot \left(1 - |S_{11}|^2\right) \cdot \left(|S_{22}|^2 - |\Delta|^2\right) - 4 \cdot |S_{12} \cdot S_{21}|^2$$

$$B_1^2 - 4 \cdot |C_1|^2 = \left(1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2\right)^2 - 4 \cdot |S_{12} \cdot S_{21}|^2$$

$$B_1^2 - 4 \cdot |C_1|^2 = \left(K \cdot 2 \cdot |S_{12} \cdot S_{21}|\right)^2 - 4 \cdot |S_{12} \cdot S_{21}|^2$$

$$B_1^2 - 4 \cdot |C_1|^2 = 4 \cdot |S_{12}|^2 \cdot |S_{21}|^2 \cdot (K^2 - 1)$$

■ Similarly

$$B_2^2 - 4 \cdot |C_2|^2 = 4 \cdot |S_{12}|^2 \cdot |S_{21}|^2 \cdot (K^2 - 1)$$

Simultaneous matching

$$\Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1} \quad \Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

- Solutions must ensure stability:

$$|\Gamma_S| < 1 \quad |\Gamma_L| < 1$$

$$|\Delta| = |S_{11} \cdot S_{22} - S_{12} \cdot S_{21}| < 1$$

$$\begin{cases} B_1 > 0 \\ B_2 > 0 \end{cases}$$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 \cdot |S_{12} \cdot S_{21}|} > 1$$

$$\begin{cases} B_1^2 - 4 \cdot |C_1|^2 = 4 \cdot |S_{12}|^2 \cdot |S_{21}|^2 \cdot (K^2 - 1) > 0 \\ B_2^2 - 4 \cdot |C_2|^2 = 4 \cdot |S_{12}|^2 \cdot |S_{21}|^2 \cdot (K^2 - 1) > 0 \end{cases}$$

Simultaneous matching

- Simultaneous matching can be achieved **if and only if** the amplifier is **unconditionally stable** at the operating frequency, and $|\Gamma| < 1$ solutions are those with “–” sign of quadratic solutions

$$\Gamma_S = \frac{B_1 - \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases}$$

$$\Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

$$\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

Simultaneous matching

- In the case of the simultaneous matching the amplifier achieves the maximum transducer power gain for the bilateral transistor


$$G_{T\max} = \frac{|S_{21}|}{|S_{12}|} \cdot (K - \sqrt{K^2 - 1})$$

- If the device is **not unconditionally stable** at a certain frequency we can use MSG (Maximum Stable Gain) as an indicator of the capability to obtain a power gain in stable conditions

$$G_{MSG} = \frac{|S_{21}|}{|S_{12}|}$$


Maximum Available Gain

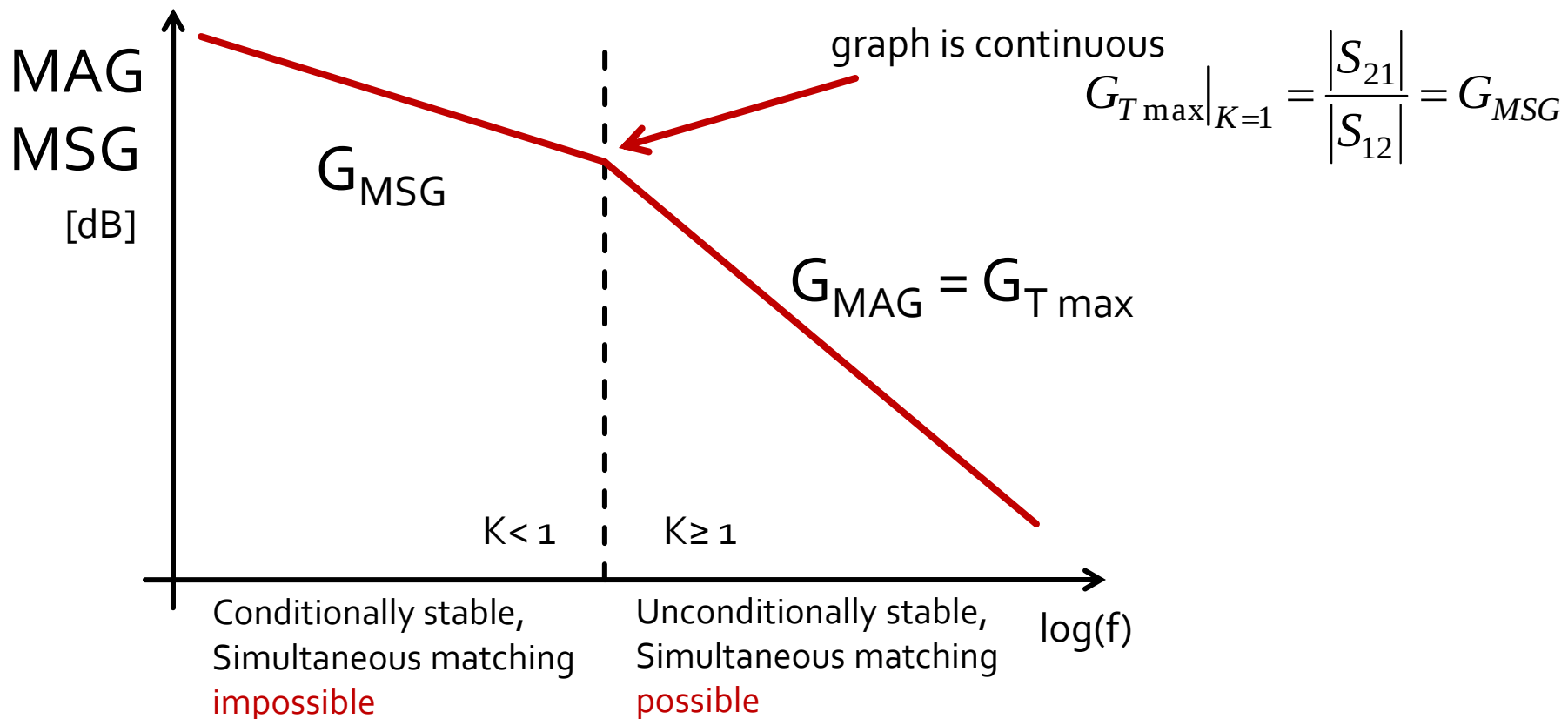- Indicator across full frequency range of the capability to obtain a power gain




Stability

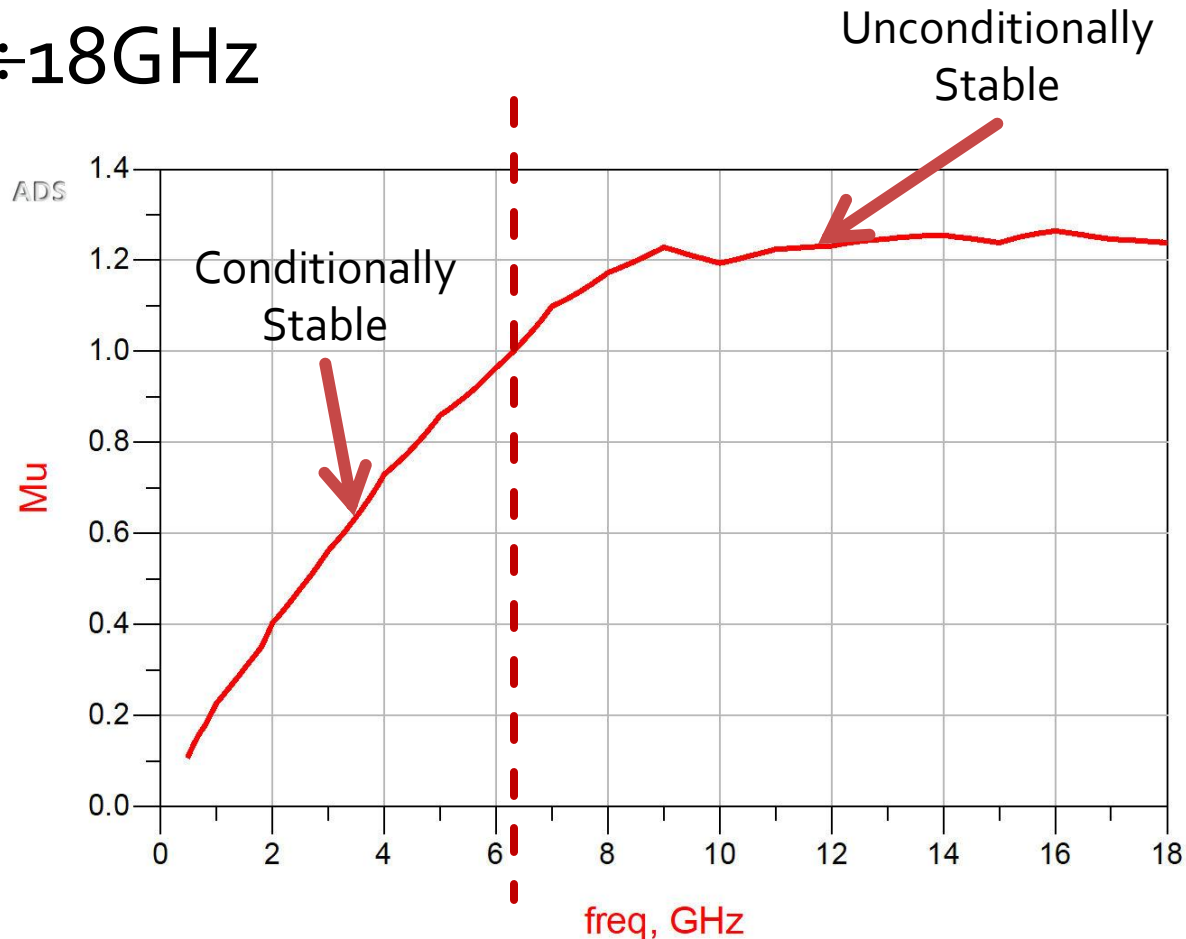- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz




MAG/MSG

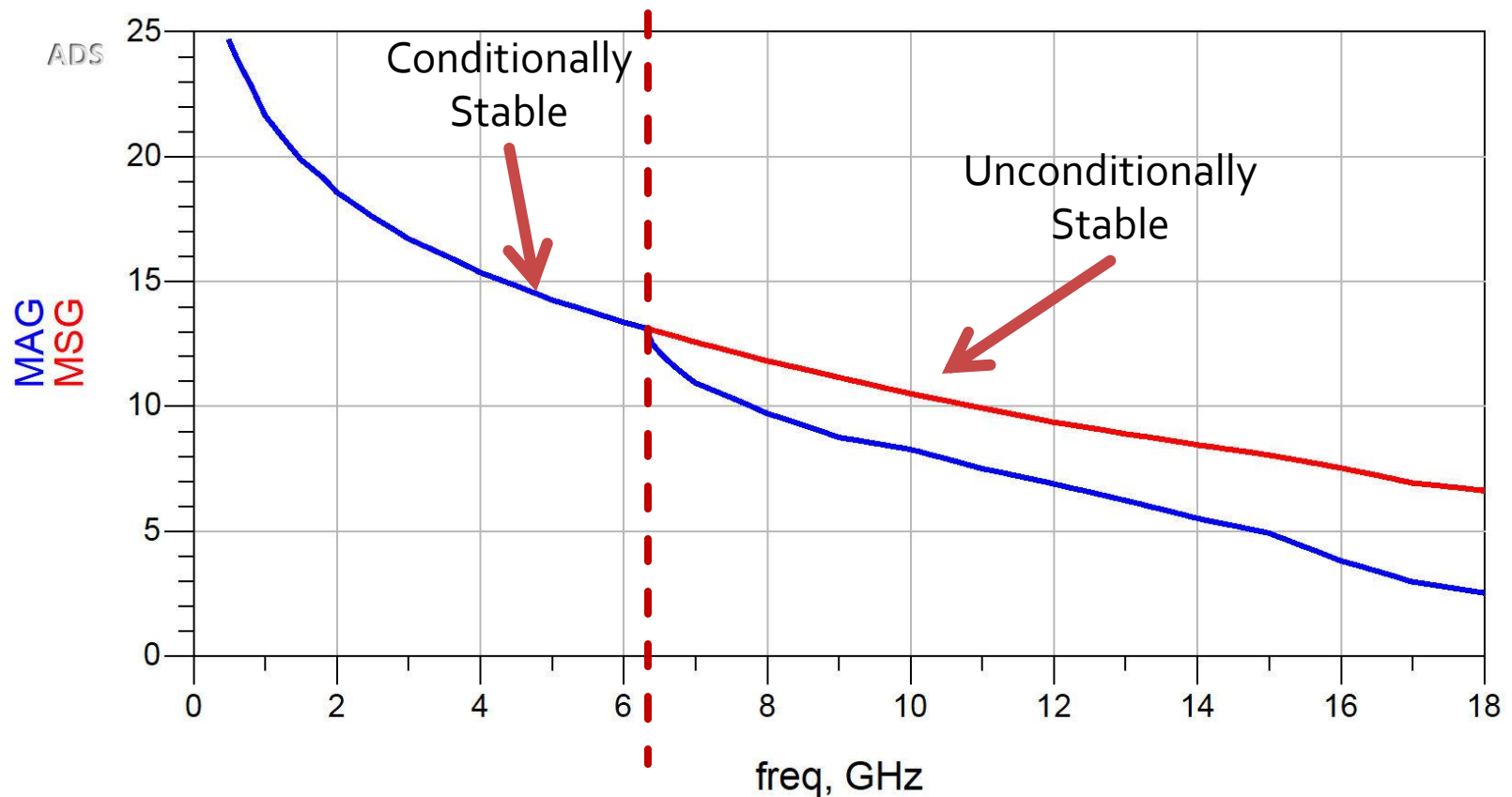- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz



Simultaneous matching, unilateral transistor

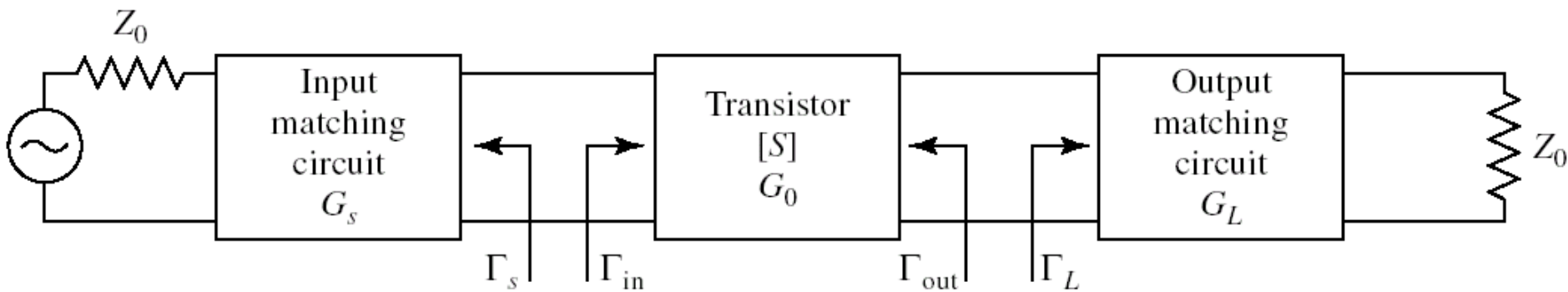- In the case of **unilateral** amplifier/transistor ($S_{12} = 0$) simultaneous matching implies:



$$\Gamma_{in} = S_{11}$$

$$\Gamma_{out} = S_{22}$$

$$\Gamma_s = S_{11}^*$$

$$\Gamma_L = S_{22}^*$$

$$G_{T \max} = \frac{1}{1 - |\Gamma_s|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$G_{TU \max} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2}$$

Example

- ATF-34143 **at $V_{ds}=3V$ $I_d=20mA$.**
 - without stabilization $K = 0.886$, $MAG = 14.248dB$ @ 5GHz
 - cannot be used with this bias conditions
- ATF-34143 **at $V_{ds}=4V$ $I_d=40mA$**
 - without stabilization $K = 1.031$, $MAG = 12.9dB$ @ 5GHz
 - we use this bias conditions for simultaneous matching

Example

- ATF-34143 at $V_{ds}=4V$ $I_d=40mA$.
- @5GHz
 - $S_{11} = 0.64 \angle 111^\circ$
 - $S_{12} = 0.117 \angle -27^\circ$
 - $S_{21} = 2.923 \angle -6^\circ$
 - $S_{22} = 0.21 \angle 111^\circ$

Computations

■ Complex S Parameters

- $S_{11} = -0.229 + 0.597 \cdot j$
- $S_{12} = 0.104 - 0.053 \cdot j$
- $S_{21} = 2.907 - 0.306 \cdot j$
- $S_{22} = -0.075 + 0.196 \cdot j$

$$G_{T \max} = \frac{|S_{21}|}{|S_{12}|} \cdot \left(K - \sqrt{K^2 - 1} \right) = 19.497 = 12.9 \text{ dB}$$

$$G_{TU \max} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2} = 15.139 = 11.8 \text{ dB}$$

Computations

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases}$$

$$\begin{cases} B_1 = ? \\ C_1 = ? \end{cases}$$

$$\Gamma_S = \frac{B_1 - \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

$$\Gamma_S = ?$$

$$\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

$$\begin{cases} B_2 = ? \\ C_2 = ? \end{cases}$$

$$\Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

$$\Gamma_L = ?$$

Computations

$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases}$$

$$\begin{cases} B_1 = 1.207 \\ C_1 = -0.277 + j \cdot 0.529 \end{cases}$$

$$\Gamma_S = \frac{B_1 - \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$

$$\Gamma_S = -0.403 - j \cdot 0.768$$

$$|\Gamma_S| = 0.867 < 1$$

$$\Gamma_S = 0.867 \angle -117.7^\circ$$

$$\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

$$\begin{cases} B_2 = 0.476 \\ C_2 = -0.222 - j \cdot 0.013 \end{cases}$$


$$\Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

$$\Gamma_L = -0.685 + j \cdot 0.04$$

$$|\Gamma_L| = 0.686 < 1$$

$$\Gamma_L = 0.686 \angle 176.7^\circ$$

Shunt stub matching, C6-7

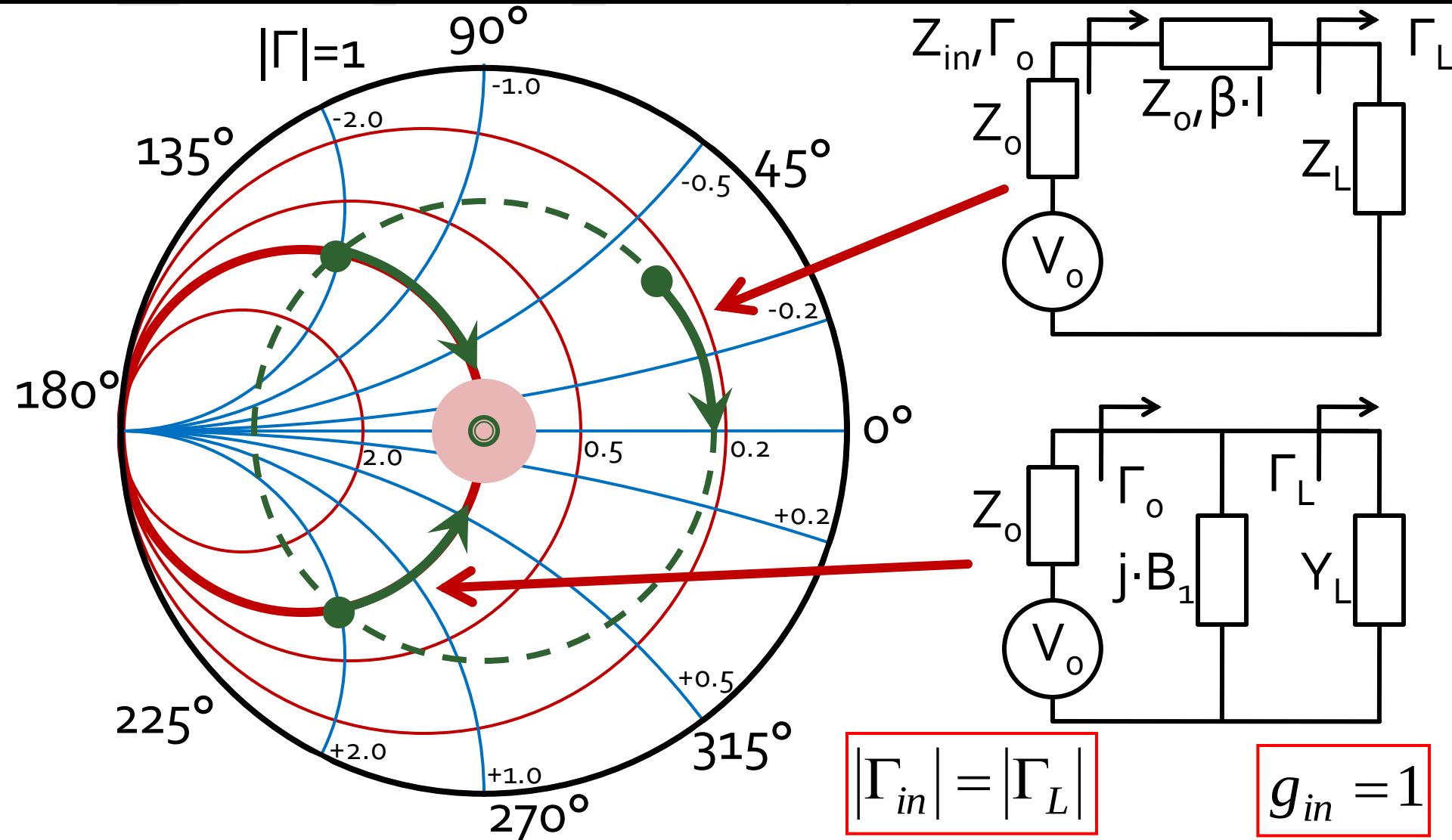

Analytical solution (Γ_S)

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = 0.867 \angle -117.7^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.867; \quad \varphi = -117.7^\circ \quad \cos(\varphi + 2\theta) = -0.867 \Rightarrow (\varphi + 2\theta) = \pm 150.1^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **"+" solution**

$$(-117.7^\circ + 2\theta) = +150.1^\circ$$

$$\theta = 133.9^\circ$$

$$\text{Im } y_s = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -3.477$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_s) = -74^\circ (+180^\circ) \rightarrow \theta_{sp} = 106^\circ$$

- **"-" solution**

$$(-117.7^\circ + 2\theta) = -150.1^\circ$$

$$\theta = -16.2^\circ (+180^\circ) \rightarrow \theta = 163.8^\circ$$

$$\text{Im } y_s = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +3.477$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_s) = 74^\circ$$

Analytical solution (Γ_L)

$$\cos(\varphi + 2\theta) = -|\Gamma_L|$$

$$\Gamma_L = 0.686 \angle 176.7^\circ$$

$$|\Gamma_L| = 0.686; \quad \varphi = 176.7^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}}$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation
 - **“+” solution**
 - **“-” solution**

Analytical solution (Γ_L)

$$\cos(\varphi + 2\theta) = -|\Gamma_L|$$

$$\Gamma_L = 0.686 \angle 176.7^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}}$$

$$|\Gamma_L| = 0.686; \quad \varphi = 176.7^\circ \quad \cos(\varphi + 2\theta) = -0.686 \Rightarrow (\varphi + 2\theta) = \pm 133.3^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **"+" solution**

$$(176.7^\circ + 2\theta) = +133.3^\circ \quad \theta = -21.7^\circ (+180^\circ) \rightarrow \theta = 158.3^\circ $$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_L) = -62.1^\circ (+180^\circ) \rightarrow \theta_{sp} = 117.9^\circ \quad \text{Im } y_L = \frac{-2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}} = -1.885$$

- **"-" solution**

$$(176.7^\circ + 2\theta) = -133.3^\circ \quad \theta = -155^\circ (+180^\circ) \rightarrow \theta = 25^\circ$$

$$\text{Im } y_L =  \frac{+2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}} = +1.885 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_L) = 62.1^\circ$$

Complete analytical solution

- We choose **one** of the two possible solutions for the input matching


$$(\varphi + 2\theta) = \begin{cases} +150.1^\circ \\ -150.1^\circ \end{cases} \quad \theta = \begin{cases} 133.9^\circ \\ 163.8^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -3.477 \\ +3.477 \end{cases} \quad \theta_{sp} = \begin{cases} -74^\circ + 180^\circ = 106^\circ \\ +74^\circ \end{cases}$$

- Similarly for the output matching

$$(\varphi + 2\theta) = \begin{cases} +133.3^\circ \\ -133.3^\circ \end{cases} \quad \theta = \begin{cases} 158.3^\circ \\ 25.0^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -1.885 \\ +1.885 \end{cases} \quad \theta_{sp} = \begin{cases} 117.9^\circ \\ 62.1^\circ \end{cases}$$


- In total there are **4** possible solutions input/output

ADS

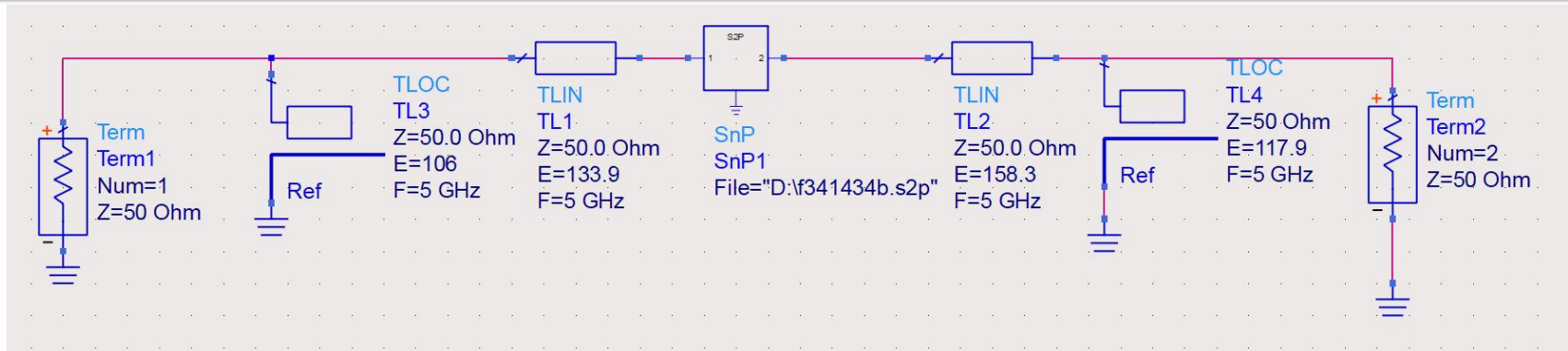



$$EqnGT=10*\log(\text{mag}(S(2,1))^2)$$

freq	S(2,1)	GT	S(1,1)	S(2,2)
5.000 GHz	4.415 / 157.353	12.900	0.004 / 86.088	0.004 / 37.766

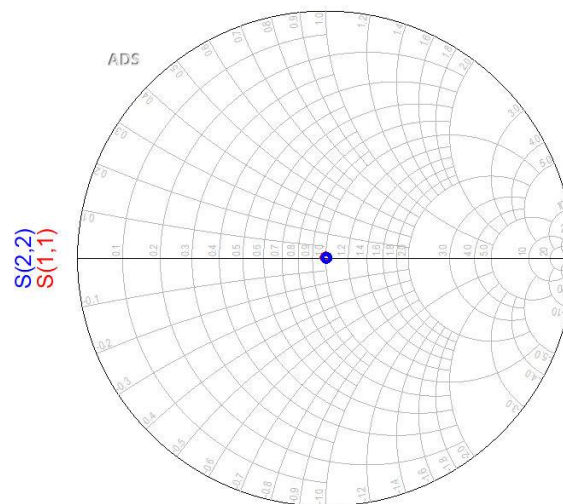

freq (5.000GHz to 5.000GHz)

ADS

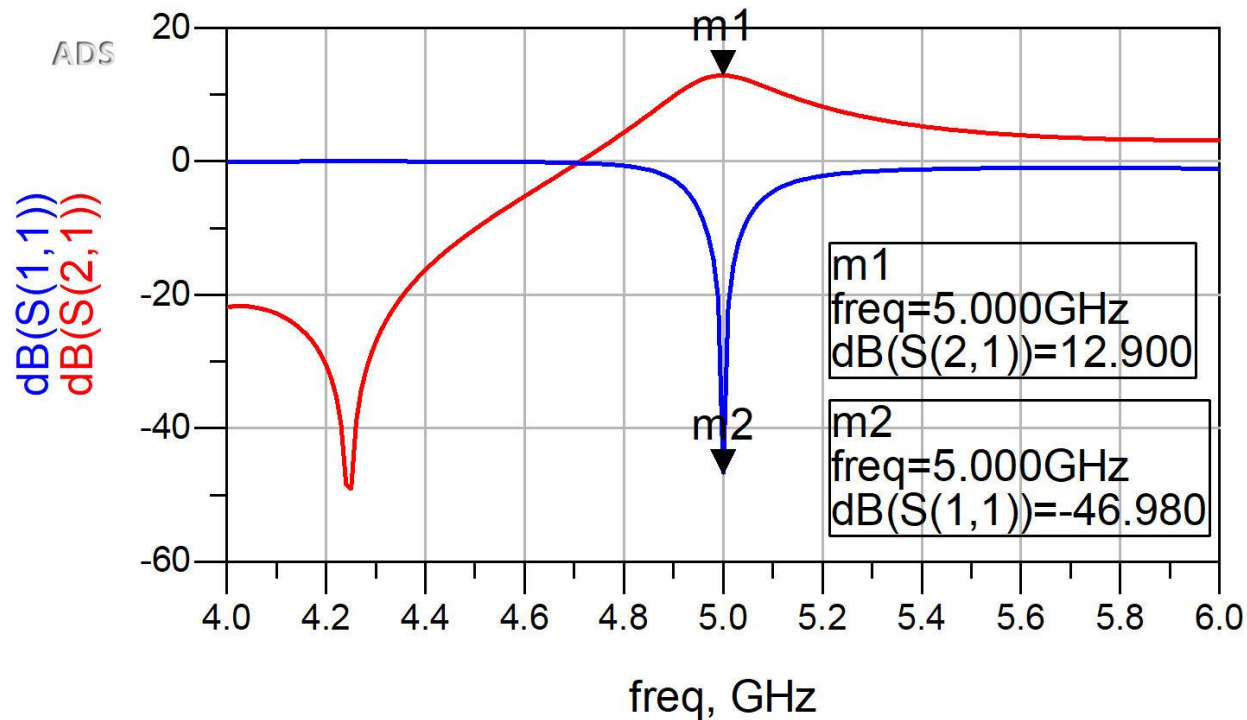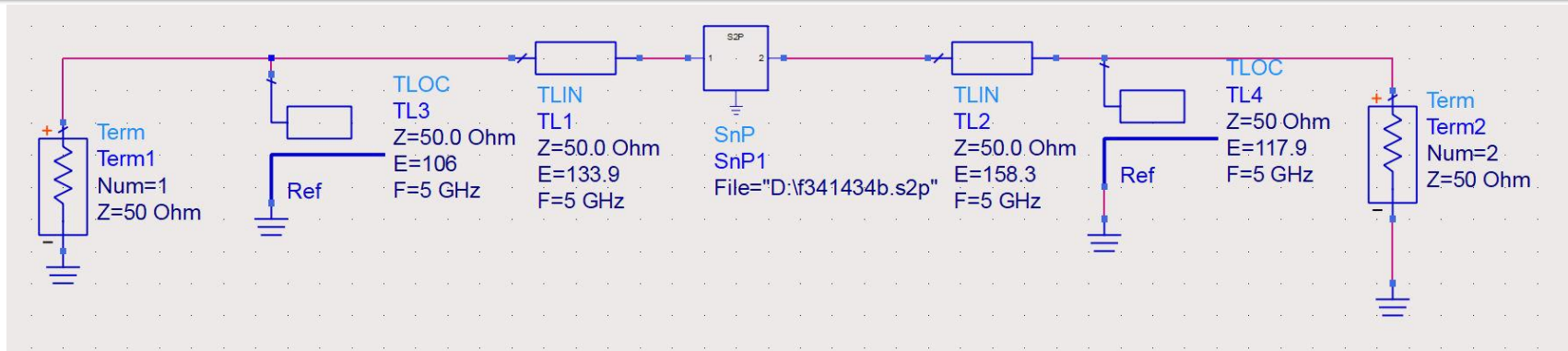

Contact

- Microwave and Optoelectronics Laboratory
- <http://rf-opto.etti.tuiasi.ro>
- rdamian@etti.tuiasi.ro