Lecture 9 2020/2021

# Microwave Devices and Circuits for Radiocommunications

#### 2020/2021

- 2C/1L, MDCR
- Attendance at minimum 7 sessions (course + laboratory)
- Lectures- associate professor Radu Damian
  - Wednesday 15-17, Online, Microsoft Teams
  - E 50% final grade
  - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
    - 3p=+0.5p
  - all materials/equipments authorized

#### Materials

#### RF-OPTO

- http://rf-opto.etti.tuiasi.ro
- David Pozar, "Microwave Engineering", Wiley; 4th edition, 2011

#### Photos

- sent by email/online exam
- used at lectures/laboratory

#### **Profile photo**

#### Profile photo – online "exam"

Examene online: 2020/2021

Disciplina: MDC (Microwave Devices and Circuits (Engleza))

#### Pas 3

| Nr. | Titlu                   | Start             | Stop              | Text                      |
|-----|-------------------------|-------------------|-------------------|---------------------------|
| 1   | Profile photos          | 03/03/2021; 10:00 | 08/04/2021; 08:00 | Online "exam" created f . |
| 2   | Mini Test 1 (lecture 2) | 03/03/2021; 15:35 | 03/03/2021; 15:50 | The current test consis   |

#### Online

#### access to online exams requires the password received by email





#### **Online results submission**

#### many numerical values



#### **Online results submission**

# Grade = Quality of the work + + Quality of the submission

# Important

#### The lossless line

 input impedance of a length *l* of transmission line with characteristic impedance *Z<sub>o</sub>*, loaded with an arbitrary impedance *Z<sub>L</sub>*



#### The lossless line



$$V(z) = V_0^+ e^{-j \cdot \beta \cdot z} + V_0^- e^{j \cdot \beta \cdot z}$$
$$I(z) = \frac{V_0^+}{Z_0} e^{-j \cdot \beta \cdot z} - \frac{V_0^-}{Z_0} e^{j \cdot \beta \cdot z}$$
$$Z_L = \frac{V(0)}{I(0)} \qquad Z_L = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \cdot Z_0$$

 voltage reflection coefficient

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Z<sub>o</sub> real

#### The lossless line

$$V(z) = V_0^+ \cdot \left( e^{-j \cdot \beta \cdot z} + \Gamma \cdot e^{j \cdot \beta \cdot z} \right) \qquad \qquad I(z) = \frac{V_0^+}{Z_0} \cdot \left( e^{-j \cdot \beta \cdot z} - \Gamma \cdot e^{j \cdot \beta \cdot z} \right)$$

time-average Power flow along the line

$$P_{avg} = \frac{1}{2} \cdot \operatorname{Re}\left\{V(z) \cdot I(z)^{*}\right\} = \frac{1}{2} \cdot \frac{\left|V_{0}^{+}\right|^{2}}{Z_{0}} \cdot \operatorname{Re}\left\{1 - \Gamma^{*} \cdot e^{-2j \cdot \beta \cdot z} + \Gamma \cdot e^{2j \cdot \beta \cdot z} - \left|\Gamma\right|^{2}\right\}$$

$$P_{avg} = \frac{1}{2} \cdot \frac{\left|V_{0}^{+}\right|^{2}}{Z_{0}} \cdot \left(1 - \left|\Gamma\right|^{2}\right)$$

- Total power delivered to the load = Incident power – "Reflected" power
   Return "Loss" [dB]
- Return "Loss" [dB]  $RL = -20 \cdot \log |\Gamma|$  [dB]

#### **Reflection and power / Model**



- The source has the ability to sent to the load a certain maximum power (available power) P<sub>a</sub>
- For a particular load the power sent to the load is less than the maximum (mismatch) P<sub>L</sub> < P<sub>a</sub>
- The phenomenon is "as if" (model) some of the power is reflected P<sub>r</sub> = P<sub>a</sub> P<sub>L</sub>
- The power is a scalar !

# Matching , from the point of view of power transmission



#### Scattering matrix – S



- a,b
  - information about signal power AND signal phase
- S<sub>ii</sub>
  - network effect (gain) over signal power including phase information

#### Impedance matching



#### **The Smith Chart**



#### **The Smith Chart**



#### Impedance Matching Impedance Matching with Stubs

#### Smith chart, r=1 and g=1



#### Impedance Matching with Stubs











# **Analytical solutions**

Exam / Project



#### Case 1, Shunt Stub

Shunt Stub



#### Analytical solution, usage

$$\cos(\varphi + 2\theta) = -|\Gamma_{S}|$$
  

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_{S}|}{\sqrt{1 - |\Gamma_{S}|^{2}}}$$

 $|\Gamma_s| = 0.593; \quad \varphi = 46.85^\circ \quad \cos(\varphi + 2\theta) = -0.593 \implies (\varphi + 2\theta) = \pm 126.35^\circ$ 

- The sign (+/-) chosen for the series line equation imposes the sign used for the shunt stub equation
  - "+" solution  $(46.85^{\circ} + 2\theta) = +126.35^{\circ}$   $\theta = +39.7^{\circ}$  Im  $y_s = \frac{-2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} = -1.472$  $\theta_{sp} = \tan^{-1}(\operatorname{Im} y_s) = -55.8^{\circ}(+180^{\circ}) \rightarrow \theta_{sp} = 124.2^{\circ}$

• "-" solution  

$$(46.85^{\circ} + 2\theta) = -126.35^{\circ} \qquad \theta = -86.6^{\circ}(+180^{\circ}) \rightarrow \theta = 93.4^{\circ}$$

$$\operatorname{Im} y_{s} = \frac{+2 \cdot |\Gamma_{s}|}{\sqrt{1 - |\Gamma_{s}|^{2}}} = +1.472 \qquad \theta_{sp} = \tan^{-1}(\operatorname{Im} y_{s}) = 55.8^{\circ}$$

#### Case 2, Series Stub

- Series Stub
- difficult to realize in single conductor line technologies (microstrip)



#### Analytical solution, usage

$$\cos(\varphi + 2\theta) = |\Gamma_s|$$

$$\theta_{ss} = \beta \cdot l = \cot^{-1} \frac{\mp 2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}}$$

 $\Gamma_{\rm s} = 0.555 \angle -29.92^{\circ}$  $|\Gamma_s| = 0.555; \quad \varphi = -29.92^\circ \quad \cos(\varphi + 2\theta) = 0.555 \Rightarrow (\varphi + 2\theta) = \pm 56.28^\circ$ 

- The sign (+/-) chosen for the series line equation imposes the sign used for the series stub equation
  - "+" solution  $\begin{array}{l} \textbf{``+`' Solution} \\ (-29.92^{\circ} + 2\theta) = +56.28^{\circ} \\ \theta = 43.1^{\circ} \\ \textbf{Im} z_{s} = \frac{+2 \cdot |\Gamma_{s}|}{\sqrt{1 - |\Gamma_{s}|^{2}}} = +1.335 \\ \theta_{ss} = -\cot^{-1}(\text{Im} z_{s}) = -36.8^{\circ}(+180^{\circ}) \rightarrow \theta_{ss} = 143.2^{\circ} \end{array}$

  - "-" solution  $(-29.92^\circ + 2\theta) = -56.28^\circ$   $\theta = -13.2^\circ(+180^\circ) \rightarrow \theta = 166.8^\circ$  $\operatorname{Im} z_{s} = \frac{-2 \cdot |\Gamma_{s}|}{\sqrt{1 - |\Gamma_{s}|^{2}}} = -1.335 \qquad \theta_{ss} = -\operatorname{cot}^{-1}(\operatorname{Im} z_{s}) = 36.8^{\circ}$

#### **Amplifier Power / Matching**

 Two ports in which matching influences the power transfer



#### **Amplifier as two-port**



# Input matching circuit



If we can afford a 1.2dB decrease of the input gain for better NF, Q (Gs = 1 dB), position m1 above is better
 We obtain better (smaller) NF

# **Output matching circuit**



output constant gain circles CCCOUT: -0.4dB, -0.2dB, odB, +0.2dB
 the lack of noise restrictions allows optimization for better gain (close to maximum – position m4)

#### **The Smith Chart**



#### **The Smith Chart**



#### **Microwave Filters**

#### **Microwave Filters**

- Two ways of implementing filters in microwave frequency range
  - microwave specific structures (coupled lines, dielectric resonators, periodic structures)
  - filter synthesis with lumped elements followed by implementation with transmission lines
- the first strategy leads to more efficient filters but:
  - has lower generality
  - design is often difficult (lack of analytical relationships)

#### **Filter synthesis**

- Filter is designed with lumped elements (L/C) followed by implementation with distributed elements (transmission lines)
  - general
  - analytical relationships easy to implement on the computer
  - efficient
- The preferred procedure is insertion loss method

#### **Insertion loss method**

$$P_{LR} = \frac{P_S}{P_L} = \frac{1}{1 - \left|\Gamma(\omega)\right|^2}$$

•  $|\Gamma(\omega)|^2$  is an even function of  $\omega$ 

$$\left|\Gamma(\omega)\right|^{2} = \frac{M(\omega^{2})}{M(\omega^{2}) + N(\omega^{2})}$$
$$P_{LR} = 1 + \frac{M(\omega^{2})}{N(\omega^{2})}$$

 Choosing M and N polynomials appropriately leads to a filter with a completely specified frequency response

#### **Insertion loss method**

- We control the power loss ratio/attenuation introduced by the filter:
  - in the passband (pass all frequencies)
  - in the stopband (reject all frequencies)


# **Filter specifications**



#### Insertion loss method

- We choose the right polynomials to design an low-pass filter (prototype)
- The low-pass prototype are then converted to the desired other types of filters
  - low-pass, high-pass, bandpass, or bandstop



#### Practical low-pass prototypes responses

- Maximally flat filters (Butterworth, binomial): provide the flattest possible passband response
- Equal ripple filters (Chebyshev): provide a sharper cutoff but the passband response will have ripples
- Elliptic function filters, they have equal-ripple responses in the passband as well as in the stopband,
- Linear phase filters, offer linear phase response in the passband to avoid signal distortion (important in some applications)

#### Maximally Flat/Equal ripple LPF Prototype



Figure 8.21 © John Wiley & Sons, Inc. All rights reserved.

# **Elliptic function LPF Prototype**



# Maximally Flat LPF Prototype

Polynomial
 (a)<sup>2N</sup>

$$P_{LR} = 1 + k^2 \cdot \left(\frac{\omega}{\omega_c}\right)^2$$

• For  $\omega >> \omega_c$ 

$$P_{LR} \approx k^2 \cdot (\omega/\omega_c)^{2N}$$



- attenuation increases <sup>Figure 8.21</sup>
   John Wiley & Sons, Inc. All rights reserved.
   at a rate of 20-N dB/decade
- k gives the attenuation at cutoff frequency (3dB cutoff imposes k = 1)

# **Equal Ripple LPF Prototype**

Polynomial

$$P_{LR} = 1 + k^2 \cdot T_N^2 \left(\frac{\omega}{\omega_c}\right)$$

- For  $\omega >> \omega_c$   $P_{LR} \approx \frac{k^2}{4} \cdot \left(\frac{2 \cdot \omega}{\omega_c}\right)^{2N}$ 
  - $1 + k^2$ 0.5 1.0
- attenuation increases at a rate of 20-N dB/decade (also)
- attenuation is (2<sup>2N</sup>)/4 greater than the binomial response at any given frequency where  $\omega >> \omega_c$
- the passband ripples:  $1 + k^2$ , k gives the ripple



#### Order (N) of the Maximally Flat filter

$$n \ge \frac{\log \left(\frac{\frac{L_{As}}{10} - 1}{\frac{L_{Ar}}{10} - 1}\right)}{2 \cdot \log \frac{\omega'_s}{\omega'_1}}$$

Iattenuations in dB



# Order (N) of the Equal Ripple filter



# Maximally flat filter prototypes



#### 3 dB Equal-ripple filter prototypes



#### o.5 dB Equal-ripple filter prototypes



# **Prototype Filters**



(a)



# **Prototype Filters**

- Prototype filters are:
  - Low-Pass Filters (LPF)
  - cutoff frequency  $\omega_0 = 1 \text{ rad/s} (f_0 = 0.159 \text{ Hz})$
  - connected to a source with  $R = 1\Omega$
- The number of reactive elements (L/C) is the order of the filter (N)
- Reactive elements are alternated: series L / shunt C
- There two prototypes with the same response, a prototype beginning with a shunt C element, and a prototype beginning with a series L element

#### **Prototype Filters**

We define filter parameters g<sub>i</sub>, i=o,N+1
 g<sub>i</sub> are the element values in the prototype filter

 $g_0 = \begin{cases} \text{generator resistance } R'_0 \text{ if } g_1 = C'_1 \\ \text{generator conductance } G'_0 \text{ if } g_1 = L'_1 \end{cases}$ 

 $g_k|_{k=\overline{1,N}} = \begin{cases} \text{inductance for series inductors} \\ \text{capacitance for shunt capacitors} \end{cases}$ 

$$g_{N+1} = \begin{cases} \text{load resistance } R'_{N+1} \text{ if } g_N = C'_N \\ \text{load conductance } G'_{N+1} \text{ if } g_N = L'_N \end{cases}$$

# Maximally Flat LPF Prototype

Formulas for filter parameters

$$g_{0} = 1$$

$$g_{k} = 2 \cdot \sin \left[ \frac{(2 \cdot k - 1) \cdot \pi}{2 \cdot N} \right] , \quad k = 1, N$$

$$g_{N+1} = 1$$

#### Maximally Flat LPF Prototype

TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ( $g_0 = 1$ ,  $\omega_c = 1$ , N = 1 to 10)

| N  | <i>g</i> <sub>1</sub> | <i>g</i> <sub>2</sub> | <i>g</i> <sub>3</sub> | <i>g</i> 4 | <b>g</b> 5 | <i>8</i> 6 | <b>g</b> 7 | <i>g</i> 8 | <b>g</b> 9 | <i>g</i> <sub>10</sub> | <i>g</i> <sub>11</sub> |
|----|-----------------------|-----------------------|-----------------------|------------|------------|------------|------------|------------|------------|------------------------|------------------------|
| 1  | 2.0000                | 1.0000                |                       |            |            |            |            |            |            |                        |                        |
| 2  | 1.4142                | 1.4142                | 1.0000                |            |            |            |            |            |            |                        |                        |
| 3  | 1.0000                | 2.0000                | 1.0000                | 1.0000     |            |            |            |            |            |                        |                        |
| 4  | 0.7654                | 1.8478                | 1.8478                | 0.7654     | 1.0000     |            |            |            |            |                        |                        |
| 5  | 0.6180                | 1.6180                | 2.0000                | 1.6180     | 0.6180     | 1.0000     |            |            |            |                        |                        |
| 6  | 0.5176                | 1.4142                | 1.9318                | 1.9318     | 1.4142     | 0.5176     | 1.0000     |            |            |                        |                        |
| 7  | 0.4450                | 1.2470                | 1.8019                | 2.0000     | 1.8019     | 1.2470     | 0.4450     | 1.0000     |            |                        |                        |
| 8  | 0.3902                | 1.1111                | 1.6629                | 1.9615     | 1.9615     | 1.6629     | 1.1111     | 0.3902     | 1.0000     |                        |                        |
| 9  | 0.3473                | 1.0000                | 1.5321                | 1.8794     | 2.0000     | 1.8794     | 1.5321     | 1.0000     | 0.3473     | 1.0000                 |                        |
| 10 | 0.3129                | 0.9080                | 1.4142                | 1.7820     | 1.9754     | 1.9754     | 1.7820     | 1.4142     | 0.9080     | 0.3129                 | 1.0000                 |

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

# Equal-ripple LPF Prototype

Formulas for filter parameters (iterative)



| TABLE 8.4        | Element    | Values   | for  | <b>Equal-Ripple</b> | Low-Pass | Filter | Prototypes | $(g_0 = 1, \omega_c =$ |
|------------------|------------|----------|------|---------------------|----------|--------|------------|------------------------|
| 1, N = 1  to  10 | , 0.5 dB a | nd 3.0 d | B ri | ipple)              |          |        |            |                        |

| 0.5 dB Ripple |                       |        |        |            |        |            |            |            |           |                               |                        |
|---------------|-----------------------|--------|--------|------------|--------|------------|------------|------------|-----------|-------------------------------|------------------------|
| N             | <i>g</i> <sub>1</sub> | 82     | 83     | <i>8</i> 4 | 85     | 86         | 87         | <i>g</i> 8 | <u>89</u> | <b><i>g</i></b> <sub>10</sub> | <i>g</i> <sub>11</sub> |
| 1             | 0.6986                | 1.0000 |        |            |        |            |            |            |           |                               |                        |
| 2             | 1.4029                | 0.7071 | 1.9841 |            |        |            |            |            |           |                               |                        |
| 3             | 1.5963                | 1.0967 | 1.5963 | 1.0000     |        |            |            |            |           |                               |                        |
| 4             | 1.6703                | 1.1926 | 2.3661 | 0.8419     | 1.9841 |            |            |            |           |                               |                        |
| 5             | 1.7058                | 1.2296 | 2.5408 | 1.2296     | 1.7058 | 1.0000     |            |            |           |                               |                        |
| 6             | 1.7254                | 1.2479 | 2.6064 | 1.3137     | 2.4758 | 0.8696     | 1.9841     |            |           |                               |                        |
| 7             | 1.7372                | 1.2583 | 2.6381 | 1.3444     | 2.6381 | 1.2583     | 1.7372     | 1.0000     |           |                               |                        |
| 8             | 1.7451                | 1.2647 | 2.6564 | 1.3590     | 2.6964 | 1.3389     | 2.5093     | 0.8796     | 1.9841    |                               |                        |
| 9             | 1.7504                | 1.2690 | 2.6678 | 1.3673     | 2.7239 | 1.3673     | 2.6678     | 1.2690     | 1.7504    | 1.0000                        |                        |
| 10            | 1.7543                | 1.2721 | 2.6754 | 1.3725     | 2.7392 | 1.3806     | 2.7231     | 1.3485     | 2.5239    | 0.8842                        | 1.984                  |
|               | 3.0 dB Ripple         |        |        |            |        |            |            |            |           |                               |                        |
| N             | <b>g</b> 1            | 82     | 83     | <i>8</i> 4 | 85     | <b>g</b> 6 | <b>8</b> 7 | <i>g</i> 8 | <u>89</u> | <b>g10</b>                    | <i>g</i> 11            |
| 1             | 1.9953                | 1.0000 |        |            |        |            |            |            |           |                               |                        |
| 2             | 3.1013                | 0.5339 | 5.8095 |            |        |            |            |            |           |                               |                        |
| 3             | 3.3487                | 0.7117 | 3.3487 | 1.0000     |        |            |            |            |           |                               |                        |
| 4             | 3.4389                | 0.7483 | 4.3471 | 0.5920     | 5.8095 |            |            |            |           |                               |                        |
| 5             | 3.4817                | 0.7618 | 4.5381 | 0.7618     | 3.4817 | 1.0000     |            |            |           |                               |                        |
| 6             | 3.5045                | 0.7685 | 4.6061 | 0.7929     | 4.4641 | 0.6033     | 5.8095     |            |           |                               |                        |
| 7             | 3.5182                | 0.7723 | 4.6386 | 0.8039     | 4.6386 | 0.7723     | 3.5182     | 1.0000     |           |                               |                        |
| 8             | 3.5277                | 0.7745 | 4.6575 | 0.8089     | 4.6990 | 0.8018     | 4.4990     | 0.6073     | 5.8095    |                               |                        |
| 9             | 3.5340                | 0.7760 | 4.6692 | 0.8118     | 4.7272 | 0.8118     | 4.6692     | 0.7760     | 3.5340    | 1.0000                        |                        |
| 10            | 3 5384                | 0 7771 | 4 6768 | 0.8136     | 4 7425 | 0 8164     | 4 7260     | 0.8051     | 1 5142    | 0.6001                        | 5 8004                 |

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

 For even N order of the filter (N = 2, 4, 6, 8 ...) equal-ripple filters must closed by
 a load impedance

 $g_{N+1} \neq 1$ If the application doesn't allow this, supplemental impedance matching is required (quarterwave transformer, binomial ...) to  $g_L = 1$ 

#### Table 8.4

© John Wiley & Sons, Inc. All rights reserved.

#### Example

 Design a 3rd order bandpass filter with 0.5 dB ripples in passband. The center frequency of the filter should be 1 GHz. The fractional bandwidth of the passband should be 10%, and the impedance 50Ω.

# LPF Prototype

o.5dB equal-ripple table or design formulas:

- g1 = 1.5963 = L1/C3,
- g2 = 1.0967 = C2/L4,
- g3 = 1.5963 = L3/C5,
- g4=1.000 = R<sub>L</sub>

|                                   | °~~                         |                                 | • <u>•</u> •••••••••••••••••••••••••••••••••• |                                   |
|-----------------------------------|-----------------------------|---------------------------------|---|-----------------------------------|
| Term<br>Term1<br>Num=1<br>Z=1 Ohm | L<br>L1<br>L=1.5963 H<br>R= | C<br>C2<br>C2<br>C=1.0967 F     | L<br>L3<br>L=1.5963 H<br>R=                   | Term<br>Term2<br>Num=2<br>Z=1 Ohm |
|                                   |                             |                                 |   |                                   |
|                                   |                             |                                 |   |                                   |
| Term<br>Term3<br>Num=3<br>Z=1 Ohm | C<br>C3<br>C=1.5963 F       | <br>L<br>L4<br>L=1.0967 H<br>R= | C<br>C5<br>C=1.5963 F                         | Term<br>Term4<br>Num=4<br>Z=1 Ohm |

#### LPF Prototype

•  $\omega_0 = 1 \text{ rad/s} (f_0 = \omega_0 / 2\pi = 0.159 \text{ Hz})$ 



#### Impedance and Frequency Scaling

- After computing prototype filter's elements:
  - Low-Pass Filters (LPF)
  - cutoff frequency  $\omega_0 = 1 \text{ rad/s} (f_0 = 0.159 \text{ Hz})$
  - connected to a source with  $R = 1\Omega$
- component values can be scaled in terms of impedance and frequency

#### Impedance and Frequency Scaling

- LPF Prototype is only used as an intermediate step
  - Low-Pass Filter (LPF)
  - cutoff frequency  $\omega_0 = 1 \text{ rad/s} (f_0 = 0.159 \text{ Hz})$
  - connected to a source with R = 1Ω



# Impedance Scaling

To design a filter which will work with a source resistance of R<sub>o</sub> we multiplying all the impedances of the prototype design by R<sub>o</sub> (" " denotes scaled values)

$$R'_{s} = R_{0} \cdot (R_{s} = 1) \qquad \qquad R'_{L} = R_{0} \cdot R_{L}$$
$$L' = R_{0} \cdot L \qquad \qquad C' = \frac{C}{R_{0}}$$

# **Frequency Scaling**

changing the cutoff frequency – (fig. b)
 changing the type (for example LPF → HPF – fig. c) requires also conversion



# **Frequency Scaling**

• To change the cutoff frequency of a low-pass prototype from unity to  $\omega_c$  we insert a variable change  $\omega \leftarrow \frac{\omega}{\omega}$ 



# **Frequency Scaling**

To change the cutoff frequency of a low-pass prototype we insert a variable substitution:

$$\omega \leftarrow \frac{\omega}{\omega_c}$$

 Equivalent to the widening of the power loss filter response

$$P_{LR}'(\omega) = P_{LR}\left(\frac{\omega}{\omega_c}\right)$$

$$j \cdot X_k = j \cdot \frac{\omega}{\omega_c} \cdot L_k = j \cdot \omega \cdot L'_k \qquad j \cdot B_k = j \cdot \frac{\omega}{\omega_c} \cdot C_k = j \cdot \omega \cdot C'_k$$

# Frequency Scaling LPF $\rightarrow$ LPF

- New element values for frequency scaling:  $L'_{k} = \frac{L_{k}}{\omega_{c}}$   $C'_{k} = \frac{C_{k}}{\omega_{c}}$
- When both impedance and frequency scaling are required:

$$L'_{k} = \frac{R_{0} \cdot L_{k}}{\omega_{c}} \qquad \qquad C'_{k} = \frac{C_{k}}{R_{0} \cdot \omega_{c}}$$

# Low-pass to high-pass transformation LPF $\rightarrow$ HPF

• Variable substitution for LPF  $\rightarrow$  HPF:

$$\omega \leftarrow -\frac{\omega_c}{\omega}$$



#### High-pass transformation LPF $\rightarrow$ HPF

• Variable substitution for LPF  $\rightarrow$  HPF :

$$j \cdot X_{k} = -j \cdot \frac{\omega_{c}}{\omega} \cdot L_{k} = \frac{1}{j \cdot \omega \cdot C_{k}'} \qquad j \cdot B_{k} = -j \cdot \frac{\omega_{c}}{\omega} \cdot C_{k} = \frac{1}{j \cdot \omega \cdot L_{k}'}$$

Impedance scaling can be included

 $\omega \leftarrow -\frac{\omega_c}{\omega_c}$ 

$$C'_{k} = \frac{1}{R_{0} \cdot \omega_{c} \cdot L_{k}} \qquad L'_{k} = \frac{R_{0}}{\omega_{c} \cdot C_{k}}$$

In the schematic series inductors must be replaced with series capacitors, and shunt capacitors must be replaced with shunt inductors

#### Bandpass Transformation LPF $\rightarrow$ BPF

# ■ Variable substitution for LPF → BPF: $\omega \leftarrow \frac{\omega_0}{\omega_2 - \omega_1} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)$

where we use the fractional bandwidth of the passband and the center frequency

$$\Delta = \frac{\omega_2 - \omega_1}{\omega_0} \qquad \qquad \omega_0 = \sqrt{\omega_1 \cdot \omega_2}$$

#### Bandpass Transformation LPF $\rightarrow$ BPF

$$\omega = \omega_{0} \rightarrow \frac{1}{\Delta} \left( \frac{\omega}{\omega_{0}} - \frac{\omega_{0}}{\omega} \right) = \frac{1}{\Delta} \left( \frac{\omega_{0}}{\omega_{0}} - \frac{\omega_{0}}{\omega_{0}} \right) = 0 \qquad \omega = -\omega_{0} \rightarrow \frac{1}{\Delta} \left( \frac{-\omega_{0}}{\omega_{0}} - \frac{\omega_{0}}{-\omega_{0}} \right) = 0$$
$$\omega = \omega_{1} \rightarrow \frac{1}{\Delta} \left( \frac{\omega}{\omega_{0}} - \frac{\omega_{0}}{\omega} \right) = \frac{1}{\Delta} \left( \frac{\omega_{1}^{2} - \omega_{0}^{2}}{\omega_{0} \cdot \omega_{1}} \right) = -1$$
$$\omega = \omega_{2} \rightarrow \frac{1}{\Delta} \left( \frac{\omega}{\omega_{0}} - \frac{\omega_{0}}{\omega} \right) = \frac{1}{\Delta} \left( \frac{\omega_{2}^{2} - \omega_{0}^{2}}{\omega_{0} \cdot \omega_{2}} \right) = 1$$
$$P_{LR} \qquad \qquad PBF$$



#### Bandpass Transformation LPF $\rightarrow$ BPF

$$j \cdot X_{k} = \frac{j}{\Delta} \left( \frac{\omega}{\omega_{0}} - \frac{\omega_{0}}{\omega} \right) \cdot L_{k} = j \cdot \frac{\omega \cdot L_{k}}{\Delta \cdot \omega_{0}} - j \cdot \frac{\omega_{0} \cdot L_{k}}{\Delta \cdot \omega} = j \cdot \omega \cdot L_{k}' - j \frac{1}{\omega \cdot C_{k}'}$$
$$j \cdot B_{k} = \frac{j}{\Delta} \left( \frac{\omega}{\omega_{0}} - \frac{\omega_{0}}{\omega} \right) \cdot C_{k} = j \cdot \frac{\omega \cdot C_{k}}{\Delta \cdot \omega_{0}} - j \cdot \frac{\omega_{0} \cdot C_{k}}{\Delta \cdot \omega} = j \cdot \omega \cdot C_{k}' - j \frac{1}{\omega \cdot L_{k}'}$$

A series inductor in the prototype filter is transformed to a series LC circuit

$$L'_{k} = \frac{L_{k}}{\Delta \cdot \omega_{0}} \qquad C'_{k} = \frac{\Delta}{\omega_{0} \cdot L_{k}}$$
  
• A shunt **capacitor** in the prototype filter is  
transformed to a **shunt LC** circuit

$$L'_{k} = \frac{\Delta}{C_{k} \cdot \omega_{0}} \qquad C'_{k} = \frac{C_{k}}{\omega_{0} \cdot \Delta}$$

#### Bandstop Transformation LPF $\rightarrow$ BSF

$$\omega \leftarrow -\Delta \cdot \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^{-1} \qquad \omega = \omega_0 \to \frac{-\Delta}{\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)} = \frac{-\Delta}{\left(\frac{\omega_0}{\omega_0} - \frac{\omega_0}{\omega_0}\right)} \to \pm \infty$$



#### Bandstop Transformation LPF $\rightarrow$ BSF

$$\omega \leftarrow -\Delta \cdot \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^{-1}$$

 A series inductor in the prototype filter is transformed to a shunt LC circuit

$$L'_{k} = \frac{\Delta \cdot L_{k}}{\omega_{0}} \qquad C'_{k} = \frac{1}{\omega_{0} \cdot \Delta \cdot L_{k}}$$

A shunt capacitor in the prototype filter is transformed to a series LC circuit

$$L'_{k} = \frac{1}{\Delta \cdot \omega_{0} \cdot C_{k}} \qquad C'_{k} = \frac{\Delta \cdot C_{k}}{\omega_{0}}$$
#### Summary of Prototype Filter Transformations





#### Example

Design a 3rd order bandpass filter with 0.5 dB ripples in passband. The center frequency of the filter should be 1 GHz. The fractional bandwidth of the passband should be 10%, and the impedance 50Ω.

$$\omega_0 = 2 \cdot \pi \cdot 1 GHz = 6.283 \cdot 10^9 \, rad \, / \, s$$

 $\Delta = 0.1$ 

# LPF Prototype

o.5dB equal-ripple table or design formulas:

- g1 = 1.5963 = L1/C3,
- g2 = 1.0967 = C2/L4,
- g3 = 1.5963 = L3/C5,
- g4=1.000 = R<sub>L</sub>

|                                   | °~~                         |                                 | • <u>•</u> •••••••••••••••••••••••••••••••••• |                                   |
|-----------------------------------|-----------------------------|---------------------------------|---|-----------------------------------|
| Term<br>Term1<br>Num=1<br>Z=1 Ohm | L<br>L1<br>L=1.5963 H<br>R= | C<br>C2<br>C2<br>C=1.0967 F     | L<br>L3<br>L=1.5963 H<br>R=                   | Term<br>Term2<br>Num=2<br>Z=1 Ohm |
|                                   |                             |                                 |   |                                   |
|                                   |                             |                                 |   |                                   |
| Term<br>Term3<br>Num=3<br>Z=1 Ohm | C<br>C3<br>C=1.5963 F       | <br>L<br>L4<br>L=1.0967 H<br>R= | C<br>C5<br>C=1.5963 F                         | Term<br>Term4<br>Num=4<br>Z=1 Ohm |

### LPF Prototype

•  $\omega_0 = 1 \text{ rad/s} (f_0 = \omega_0 / 2\pi = 0.159 \text{ Hz})$ 



#### **Bandpass Transformation / BPF**

$$\omega_0 = 2 \cdot \pi \cdot 1 GHz = 6.283 \cdot 10^9 \, rad \, / \, s$$

$$L_1' = \frac{L_1 \cdot R_0}{\Delta \cdot \omega_0} = 127.0 \, nH$$

$$L_2' = \frac{\Delta \cdot R_0}{\omega_0 \cdot C_2} = 0.726 nH$$

$$L_3' = \frac{L_3 \cdot R_0}{\Delta \cdot \omega_0} = 127.0 \, nH$$

$$\Delta = \frac{\Delta \omega}{\omega_0} = \frac{\Delta f}{f_0} = 0.1 \qquad R_0 = 50 \ \Omega$$
  
g3 = 1.5963 = L3,  
g4=1.000 = R<sub>L</sub>

$$C_1' = \frac{\Delta}{\omega_0 \cdot L_1 \cdot R_0} = 0.199 \, pF$$

$$C_2' = \frac{C_2}{\Delta \cdot \omega_0 \cdot R_0} = 34.91 \, pF$$

$$C_3' = \frac{\Delta}{\omega_0 \cdot L_3 \cdot R_0} = 0.199 \, pF$$

#### ADS



freq, GHz

# Microwave Filters Implementation

#### **Microwave Filters Implementation**

- The lumped-element (L, C) filter design generally works well only at low frequencies (RF):
  - lumped-element inductors and capacitors are generally available only for a limited range of values, and can be difficult to implement at microwave frequencies
  - difficulty to obtain the (very low) required tolerance for elements



© John Wiley & Sons, Inc. All rights reserved.

Impedance seen at the input of a line loaded with Z<sub>1</sub>

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

- We prefer the load impedance to be:
  - open circuit ( $Z_1 = \infty$ )  $Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l$
  - short circuit ( $Z_1 = 0$ )  $Z_{in.sc} = j \cdot Z_0 \cdot \tan \beta \cdot l$

 $Z_{in sc} = j \cdot X_L$ 

- Input impedance is:
- capacitive  $Z_{in,oc} = j \cdot X_C = \frac{1}{j \cdot B_C}$
- $Z_0 \leftrightarrow \frac{1}{C} \quad \tan \beta \cdot l \leftrightarrow \omega$

 $Z_0 \leftrightarrow L \quad \tan \beta \cdot l \leftrightarrow \omega$ 

inductive

• Variable substitution  

$$\Omega = \tan \beta \cdot l = \tan \left( \frac{\omega \cdot l}{v_p} \right)$$

- With this variable substitution we define:
  - reactance of an inductor

 $j \cdot X_L = j \cdot \Omega \cdot L = j \cdot L \cdot \tan \beta \cdot l$ 

susceptance of a capacitor

 $j \cdot B_C = j \cdot \Omega \cdot C = j \cdot C \cdot \tan \beta \cdot l$ 

The equivalent filter in Ω has a cutoff frequency at:

$$\Omega = 1 = \tan \beta \cdot l \quad \rightarrow \quad \beta \cdot l = \frac{\pi}{4} \quad \rightarrow \quad l = \frac{\lambda}{8}$$

 allows implementation of the inductors and capacitors with lines after the transformation of the LPF prototype to the required type (LPF/HPF/BPF/BSF)



- By choosing the open-circuited or short-circuited lines to be λ/8 at the desired cutoff frequency (ω<sub>c</sub>) and the corresponding characteristic impedances (L/C from LPF prototype) we will obtain at frequencies around ω<sub>c</sub> a behavior similar to that of the prototype filter.
  - At frequencies far from ω<sub>c</sub> the behavior of the filter will no longer be identical to that of the prototype (in specific situations the correct behavior must be verified)
  - Frequency scaling is simplified: choosing the appropriate physical length of the line to have the electrical length λ/8 at the desired cutoff frequency
- All lines will have equal electrical lengths (λ/8) and thus comparable physical lengths, so the lines are called commensurate lines

- At the frequency  $\omega = 2 \cdot \omega_c$  the lines will be  $\lambda/4$ long  $l = \frac{\lambda}{\Lambda} \implies \beta \cdot l = \frac{\pi}{2} \implies \tan \beta \cdot l \to \infty$
- an supplemental attenuation pole will occur at  $2 \cdot \omega_c$  (LPF):
  - inductances (usually in series)  $Z_{in.sc} = j \cdot Z_0 \cdot \tan \beta \cdot l \rightarrow \infty$
  - capacitances (usually shunt)  $Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l \rightarrow 0$

the periodicity of tan function implies the periodicity of the filter implemented with lines
 the filter response will be repeated every 4·ω<sub>c</sub>

$$\tan(\alpha + \pi) = \tan \alpha$$

 $\beta \cdot l\Big|_{\omega = \omega_c} = \frac{\pi}{4} \implies \frac{\omega_c \cdot l}{v_p} = \frac{\pi}{4} \implies \pi = \frac{(4 \cdot \omega_c) \cdot l}{v_p}$  $Z_{in}(\omega) = Z_{in}(\omega + 4 \cdot \omega_c) \implies P_{LR}(\omega) = P_{LR}(\omega + 4 \cdot \omega_c)$ 

$$P_{LR}(4 \cdot \omega_c) = P_{LR}(0) \qquad P_{LR}(3 \cdot \omega_c) = P_{LR}(-\omega_c) \qquad P_{LR}(5 \cdot \omega_c) = P_{LR}(\omega_c)$$

#### Example

- Low-pass filter 4<sup>th</sup> order, 4 GHz cutoff frequency, maximally flat design (working with 50Ω source and load)
- maximally flat table or formulas:
  - g1 = 0.7654 = L1
  - g2 = 1.8478 = C2
  - g3 = 1.8478 = L3
  - g4 = 0.7654 = C4
  - g5 = 1 (does not need supplemental impedance matching – required only for even order equal-ripple filters)

## LPF Prototype



freq, Hz

#### Lumped elements

$$\omega_{c} = 2 \cdot \pi \cdot 4 GHz = 2.5133 \cdot 10^{10} rad / s$$

$$L_1' = \frac{R_0 \cdot L_1}{\omega_c} = 1.523 nH$$

$$L_3' = \frac{R_0 \cdot L_3}{\omega_c} = 3.676 nH$$

$$C_2' = \frac{C_2}{R_0 \cdot \omega_c} = 1.470 \, pF$$

$$C_4' = \frac{C_4}{R_0 \cdot \omega_c} = 0.609 \, pF$$

#### Lumped elements – ADS



- LPF Prototype parameters:
  - g1 = 0.7654 = L1
  - g2 = 1.8478 = C2
  - g3 = 1.8478 = L3
  - g4 = 0.7654 = C4
- Normalized line impedances
  - z1 = 0.7654 = series / short circuit
  - z2 = 1 / 1.8478 = 0.5412 = shunt / open circuit
  - z<sub>3</sub> = 1.8478 = series / short circuit
  - z4 = 1/ 0.7654 = 1.3065 = shunt / open circuit
- Impedance scaling by multiplying with Zo = 50Ω
   All lines must have the length equal to λ/8 (electrical length E = 45°) at 4GHz

$$Z_0 \leftrightarrow \frac{1}{C}$$

 $Z_0 \leftrightarrow L$ 

#### **Richards' Transformation – ADS**



- Filters implemented with Richards' Transformation
  - beneficiate from the supplemental pole at  $2 \cdot \omega_c$
  - have the major disadvantage of frequency periodicity, a supplemental non-periodic LPF must be inserted if needed



# Equal-ripple prototype

- For even N order of the filter (N = 2, 4, 6, 8 ...) equal-ripple filters must closed by a non-standard load impedance g<sub>N+1</sub> ≠ 1
   If the application doesn't allow this, supplemental impedance matching is
  - required (quarter-wave transformer, binomial ...) to  $g_L = 1$

$$g_{N+1} \neq 1 \longrightarrow R \neq R_0 \quad (50\Omega)$$

#### Observation: even order equal-ripple

- Same filter, 3dB equal-ripple
- 3dB equal-ripple tables or formulas:
  - g1 = 3.4389 = L1
  - g2 = 0.7483 = C2
  - g3 = 4.3471 = L3
  - g4 = 0.5920 = C4
  - g5 = 5.8095 = R<sub>L</sub>
- Line impedances
  - $Z_1 = 3.4389 \cdot 50\Omega = 171.945\Omega = series / short circuit$
  - Z<sub>2</sub> = 50Ω / 0.7483 = 66.818Ω = shunt / open circuit
  - $Z_3 = 4.3471 \cdot 50\Omega = 217.355\Omega = \text{series} / \text{short circuit}$
  - Z<sub>4</sub> = 50Ω / 0.5920 = 84.459Ω = shunt / open circuit
  - RL = 5.8095·50Ω = 295.475Ω = load

#### Even order equal-ripple – ADS



#### **Observation: even order equal-ripple**

 Even order equal-ripple filters need output matching towards 50Ω for precise results.
 Example:



- Filters implemented with the Richards' transformation have certain disadvantages in terms of practical use
   Kuroda's Identities/Transformations can eliminate
  - some of these disadvantages
- We use additional line sections to obtain systems that are easier to implement in practice
- The additional line sections are called unit elements and have lengths of λ / 8 at the desired cutoff frequency (ω<sub>c</sub>) thus being commensurate with the stubs implementing the inductors and capacitors.



- Kuroda's Identities perform any of the following operations:
  - Physically separate transmission line stubs
  - Transform series stubs into shunt stubs, or vice versa
  - Change impractical characteristic impedances into more realizable values (~50Ω)



- 4 circuit equivalents (a,b)
  - each box represents a unit element, or transmission line, of the indicated characteristic impedance and length ( $\lambda/8$  at  $\omega_c$ ). The inductors and capacitors represent short-circuit and open-circuit stubs  $\frac{Z_1}{n^2}$





- 4 circuit equivalents (c,d)
  - each box represents a unit element, or transmission line, of the indicated characteristic impedance and length ( $\lambda/8$  at  $\omega_c$ ). The inductors and capacitors represent short-circuit and open-circuit stubs



#### In all Kuroda's Identities:

n:

$$n^2 = 1 + \frac{Z_2}{Z_1}$$

- The inductors and capacitors represent shortcircuit and open-circuit stubs resulted from Richards' transformation (λ/8 at ω<sub>c</sub>).
- Each box represents a unit element, or transmission line, of the indicated characteristic impedance and length ( $\lambda/8$  at  $\omega_c$ ).

#### **First Kuroda's Identity**



Figure 8.35 © John Wiley & Sons, Inc. All rights reserved.









First circuit

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{1}{\sqrt{1 + \Omega^2}} \cdot \begin{bmatrix} 1 & j \cdot \Omega \cdot Z_1 \\ j \cdot \Omega \cdot \left(\frac{1}{Z_1} + \frac{1}{Z_2}\right) & 1 - \Omega^2 \cdot \frac{Z_1}{Z_2} \end{bmatrix}$$
  
Second circuit

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{1}{\sqrt{1+\Omega^2}} \cdot \begin{bmatrix} 1 & j \cdot \frac{\Omega}{n^2} \cdot (Z_1 + Z_2) \\ \frac{j \cdot \Omega \cdot n^2}{Z_2} & 1 - \Omega^2 \cdot \frac{Z_1}{Z_2} \end{bmatrix}$$

Results are identical if we choose

$$n^2 = 1 + \frac{Z_2}{Z_1}$$

The other 3 identities can be proved in the same way
## (Same) Example

- Low-pass filter 4<sup>th</sup> order, 4 GHz cutoff frequency, maximally flat design (working with 50Ω source and load)
- maximally flat table or formulas:
  - g1 = 0.7654 = L1
  - g2 = 1.8478 = C2
  - g3 = 1.8478 = L3
  - g4 = 0.7654 = C4
  - g5 = 1 (does not need supplemental impedance matching – required only for even order equal-ripple filters)

#### Apply Richards's transformation



- Problems:
  - the series stubs would be very difficult to implement in microstrip line form
  - in microstrip technology it is preferable to have open-circuit stubs (short-circuit requires a viahole to the ground plane)
  - the 4 stubs are physically connected at the same point, an implementation that eliminates/reduces the coupling between these lines is impossible
  - not the case here, but sometimes the normalized impedances are much different from 1. Most circuit technologies are designed for 50Ω lines

- In all 4 Kuroda's Identities we always have a circuit with a series line section (not present in initial circuit):
  - we **add** unit elements (z = 1,  $l = \lambda/8$ ) at the ends of the filter (these redundant elements do not affect filter performance since they are matched to z = 1, both source and load)
  - we **apply** one of the Kuroda's Identities at both ends and **continue** (add unit ...)
  - we can stop the procedure when we have a series line section between all the stubs from Richards' transformation



#### Apply:

- Kuroda 2 (L,Z known  $\rightarrow$  C,Z) on the left side
- Kuroda 1 (C,Z known  $\rightarrow$  L,Z) on the right side



We add another unit element on the right side and apply Kuroda 2 twice





Impedance scaling (multiply by 50Ω)



### Kuroda's Identities – ADS



freq, GHz



Figure 8.55 Courtesy of LNX Corporation, Salem, N.H.



Figure 8.55 Courtesy of LNX Corporation, Salem, N.H.







- Richards' transformation and Kuroda's identities are useful especially for low-pass filters in technologies where the series stubs would be very difficult/ impossible to implement (microstrip)
- In the case of other filters (example 3<sup>rd</sup> order BPF):
  - series inductance can be implemented using K1-K2
  - series capacitance cannot be implemented using shunt stubs



Figure 8.32 © John Wiley & Sons, Inc. All rights reserved.

 For cases where Richards + Kuroda do not offer practical solutions we use circuits called impedance and admittance inverters

$$Z_{in} = \frac{K^2}{Z_L}$$

Impedance inverters



Admittance inverters





© John Wiley & Sons, Inc. All rights reserved.

 The simplest example of impedance and admittance inverter is the quarter-wave transformer (L4)



- Impedance/admittance inverters can be used to change the structure of a designed filter to a realizable form
- For example a 2<sup>nd</sup> order BSF



 The series elements can be eliminated/replaced using an admittance inverter





The equivalence of the two schematics (when looking from the left) is proofed by obtaining the same input admittance





 $L_n \cdot C_n = L'_n \cdot C'_n = \frac{1}{\omega_0^2} \implies \frac{1}{Z_0^2} \cdot \sqrt{\frac{L_1}{C_1}} = \sqrt{\frac{C'_1}{L'_1}} \implies Y = Y' \qquad \text{A similar result can be} \\ \sqrt{\frac{L_2}{C}} = \sqrt{\frac{L'_2}{C'}} \implies Y = Y' \qquad \text{A similar result can be} \\ \text{obtained for a bandpass} \\ \mathbf{f} : \mathbf{I} : \mathbf{I}$ filter

The complete equivalence (when looking from both sides) is obtained by enclosing the series LC circuit between two admittance inverters



- A series LC circuit inserted in series in the circuit can be replaced by a shunt LC circuit inserted in parallel enclosed between 2 admittance inverters
- A shunt LC circuit inserted in series in the circuit can be replaced by a series LC circuit inserted in parallel enclosed between 2 admittance inverters

### Practical implementations of impedance/admittance inverters

 Most often the quarter-wave transformer is used



### Practical implementations of impedance/admittance inverters

# Implementation with transmission lines and reactive elements



## **Prototype filters using inverters**

- Using impedance/admittance inverters we can implement prototype filters using a single type of reactive elements
  - Shunt C replaced by series L enclosed between 2 inverters



## **Prototype filters using inverters**

- Using impedance/admittance inverters we can implement prototype filters using a single type of reactive elements
  - Series L replaced by shunt C enclosed between 2 inverters



# **Prototype filters using inverters**

- For prototype filters using inverters formulas we have 2.N+1 parameters and N+1 equations (to ensure the equivalence of the 2 schematics) so N parameters can be chosen freely
  - convenient values for the reactance can be chosen, and the required inverters will be computed from the equivalence equations or,
  - convenient inverters can be chosen, and the required reactance values will be computed from the equivalence equations

## **BPF and BSF using inverters**

- The same principle can be applied to the BPF and BSF filters, those can be implemented using N+1 inverters and N resonators (series or shunt LC circuits with resonant frequency ω<sub>o</sub>) connected either in series or in parallel enclosed between 2 inverters
  - BPF are implemented with
    - series LC circuits connected in series between inverters
    - shunt LC circuits connected in parallel between inverters
  - BSF are implemented with
    - shunt LC circuits connected in series between inverters
    - series LC circuits connected in parallel between inverters

#### Lines as resonators

 The impedance of short-circuited or opencircuited line (stub) shows a resonant behavior that can be used to implement required resonators

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$



#### Lines as resonators

- Short-circuited line
- For the frequency at which I =  $\lambda/4$  ( $\omega_0$ ) the line behaves as an shunt LC resonator circuit
  - the line shows capacitive behavior for lower frequencies (I>λ/4)
  - the line shows inductive behavior for higher frequencies (I<λ/4)</li>
- Similar discussion for the open circuited line (equivalent to a series LC resonator around the frequency at which I=λ/4)



## **BPF/BSP design formulas**

- When the admittance inverters are implemented with quarter-wave transformers with Zo characteristic impedance
  - BPF short-circuited shunt stubs with I = \lambda/4 Z<sub>0n</sub> \approx \frac{\pi \cdot Z\_0 \cdot \Delta}{4 \cdot g\_n}

    BSF – open-circuited shunt stubs with I = \lambda/4 Z<sub>0n</sub> \approx \frac{4 \cdot Z\_0}{\pi \cdot g\_n \cdot \Delta}

- Similar to a project assignment
- Follows the amplifier designed as in L8
- 4<sup>th</sup> order bandpass filter, fo = 5GHz, fractional bandwidth of the passband 10 %
- maximally flat table or formulas for g<sub>n</sub>:

| n | <b>g</b> <sub>n</sub> | Z <sub>on</sub> (Ω) |   |
|---|-----------------------|---------------------|---|
| 1 | 0.7654                | 5.131               | $Z_{0n} \approx \frac{\pi \cdot Z_0 \cdot \Delta}{4 \cdot g_n}$ |
| 2 | 1.8478                | 2.125               |   |
| 3 | 1.8478                | 2.125               |   |
| 4 | 0.7654                | 5.131               |   |

#### ADS – BPF





freq, GHz

### ADS – BPF



freq, GHz



- Disadvantages of the filters using impedance inverters and lines as resonators:
  - short-circuited stubs (via-hole) for BPF
  - often the characteristic impedances for the stubs have values difficult to implement (2.125Ω)

- A parallel coupled line section model is obtained by even/odd mode analysis
- Even and odd modes are characterized by the characteristic even/odd mode impedances whose required values will impose the lines' geometry (width / distance between lines, depending on the line technology we use)



## **Coupled Lines**



Figure 3.25b © John Wiley & Sons, Inc. All rights reserved

- Even mode characterizes the common mode signal on the two lines
- Odd mode characterizes the differential mode signal between the two lines
- Each of the two modes is characterized by different characteristic impedances



c) ODD MODE ELECTRIC FIELD PATTERN (SCHEMATIC)

b) EVEN MODE ELECTRIC FIELD PATTERN (SCHEMATIC)



Bandpass filter with resonance at  $\theta = \pi/2$  ( $l = \lambda/4$ )



Figure 8.44 © John Wiley & Sons, Inc. All rights reserved.

#### We get a N<sup>th</sup> order filter with N+1 parallel coupled line section



- Equivalent circuits for
  - transmission lines of length 2θ
  - admittance inverters



 We get a 2<sup>nd</sup> order BPF behavior cu 3 coupled lines sections





Figure 8.45def © John Wiley & Sons, Inc. All rights reserved.
## **Coupled Line Filters design formulas**

 Compute the inverters from prototype parameters

$$Z_0 \cdot J_1 = \sqrt{\frac{\pi \cdot \Delta}{2 \cdot g_1}} \qquad \qquad Z_0 \cdot J_n = \frac{\pi \cdot \Delta}{2 \cdot \sqrt{g_{n-1} \cdot g_n}}, n = \overline{2, N} \qquad \qquad Z_0 \cdot J_{N+1} = \sqrt{\frac{\pi \cdot \Delta}{2 \cdot g_N \cdot g_{N+1}}}$$

 Compute coupled line parameters Zoe/Zoo (all of length *l*=λ/4)

$$Z_{0e,n} = Z_0 \cdot \left[ 1 + J_n \cdot Z_0 + (J_n \cdot Z_0)^2 \right]$$
  

$$Z_{0o,n} = Z_0 \cdot \left[ 1 - J_n \cdot Z_0 + (J_n \cdot Z_0)^2 \right]$$
  

$$n = \overline{1, N+1}$$

## Example

- Similar to a project assignment
- Follows the amplifier designed as in L8
- 4<sup>th</sup> order bandpass filter, fo = 5GHz, fractional bandwidth of the passband 10 %
- o.5dB equal-ripple table for g<sub>n</sub> followed by filter design formulas

| n | g      | ZoJn     | Zoe   | Zoo   |
|---|--------|----------|-------|-------|
| 1 | 1.6703 | 0.306664 | 70.04 | 39.37 |
| 2 | 1.1926 | 0.111295 | 56.18 | 45.05 |
| 3 | 2.3661 | 0.09351  | 55.11 | 45.76 |
| 4 | 0.8419 | 0.111294 | 56.18 | 45.05 |
| 5 | 1.9841 | 0.306653 | 70.03 | 39.37 |

## ADS – coupled line BPF



## ADS – coupled line BPF



## Examples



Figure 8.55 Courtesy of LNX Corporation, Salem, N.H.



## Bandpass Filters Using Capacitively Coupled Series Resonators

 The gaps between the resonators (~λ/2) generate a capacitive coupling between two resonators and can be approximated as series capacitors





## Bandpass Filters Using Capacitively Coupled Series Resonators

• From the real physical length of the resonators, some part is used implement a admittance inverter (the remainder  $\phi = \pi$ ,  $l = \lambda/2$ , resonator)



Figure 8.50 © John Wiley & Sons, Inc. All rights reserved.

## Bandpass Filters Using Capacitively Coupled Series Resonators design

Compute the inverters (similar to coupled lines)

$$Z_0 \cdot J_1 = \sqrt{\frac{\pi \cdot \Delta}{2 \cdot g_1}} \qquad \qquad Z_0 \cdot J_n = \frac{\pi \cdot \Delta}{2 \cdot \sqrt{g_{n-1} \cdot g_n}}, n = \overline{2, N} \qquad \qquad Z_0 \cdot J_{N+1} = \sqrt{\frac{\pi \cdot \Delta}{2 \cdot g_N \cdot g_{N+1}}}$$

Compute capacitive susceptances

$$B_n = \frac{J_n}{1 - (Z_0 \cdot J_n)^2}, n = \overline{1, N + 1}$$

 Compute the line lengths that must be "borrowed" to implement the inverters

 $\phi_n = -\tan^{-1}(2 \cdot Z_0 \cdot B_n), n = \overline{1, N+1} \qquad \phi_n < 0, n = \overline{1, N+1}$   $\bullet_n < 0, n = \overline{1, N+1}$ 

# Equivalent circuits for short sections of transmission lines

#### ABCD matrix (L4)

short line , model with lumped elements is valid



# Equivalent circuits for short sections of transmission lines

- The shunt element is capacitive  $Z_3 = \frac{1}{j \cdot Y_0 \cdot \sin \beta \cdot l}$
- Series elements are equal, and inductive

$$\cos\beta \cdot l = 1 + \frac{Z_1}{Z_3} = 1 + \frac{Z_2}{Z_3}$$

$$Z_1 = Z_2 = Z_3 \cdot (\cos\beta \cdot l - 1) = -j \cdot Z_0 \cdot \frac{\cos\beta \cdot l - 1}{\sin\beta \cdot l} = j \cdot Z_0 \cdot \tan\frac{\beta \cdot l}{2}$$
Equivalent circuit
$$j\frac{X}{2}$$

$$\frac{j\frac{X}{2}}{j^B}$$

$$\frac{X}{2} = Z_0 \cdot \tan\frac{\beta \cdot l}{2}$$

$$B = \frac{1}{Z_0} \cdot \sin\beta \cdot l$$

# Equivalent circuits for short sections of transmission lines

- depending on the characteristic impedance:
  - high Zo >>

$$\sum_{X = Z_0 \beta l} X \cong Z_0 \cdot \beta \cdot l \qquad \beta \cdot l < \frac{\pi}{4} \qquad Z_0 = Z_h$$



Iow Zo <<</p>

$$\underbrace{ = }_{0}^{\circ} B = Y_{0}\beta l$$

$$B \cong Y_{0} \cdot \beta \cdot l$$

$$\beta \cdot l < \frac{\pi}{4}$$

$$Z_{0} = Z_{l}$$

## Stepped-impedance low-pass filter

- Series L, shunt C, we realize low-pass filtersWe use
  - lines with high characteristic impedance to implement an series inductor

$$\beta \cdot l = \frac{L \cdot R_0}{Z_h}$$

 lines with low characteristic impedance to implement a shunt capacitor

 $\beta \cdot l = \frac{C \cdot Z_l}{R_0}$ usually the highest and lowest characteristic impedance that can be practically fabricated

## **Stepped-impedance LPF**

 Not all the lines will result with the same length so the filter response is not periodic in frequency



Figure 8.40 © John Wiley & Sons, Inc. All rights reserved.



 LPF with 8GHz cutoff frequency, 6<sup>th</sup> order. Maximum realizable impedance is 150Ω and lowest 15Ω.

| n | <b>g</b> <sub>n</sub> | L/C <sub>n</sub> | Z   | $\theta_n$ [rad] | θ <sub>n</sub> [°] |
|---|-----------------------|------------------|-----|------------------|--------------------|
| 1 | 0.5176                | 0.206pF          | 15  | 0.155            | 8.90               |
| 2 | 1.4142                | 1.407nH          | 150 | 0.471            | 27.01              |
| 3 | 1.9318                | 0.769pF          | 15  | 0.580            | 33.21              |
| 4 | 1.9318                | 1.922nH          | 150 | 0.644            | 36.89              |
| 5 | 1.4142                | 0.563pF          | 15  | 0.424            | 24.31              |
| 6 | 0.5176                | 0.515nH          | 150 | 0.173            | 9.89               |

## ADS – Stepped-impedance LPF



## **ADS – Stepped-impedance LPF**



# ADS – Stepped-impedance LPF – compared with lumped elements



freq, GHz

## Examples



Figure 8.55 Courtesy of LNX Corporation, Salem, N.H.





- Microwave and Optoelectronics Laboratory
- http://rf-opto.etti.tuiasi.ro
- rdamian@etti.tuiasi.ro