

Laboratory 5 (w11-14)

2023/2024

Microwave Devices and Circuits for Radiocommunications

MDCR Project

Assignment


- Design a low-noise multi-stage transistor amplifier required to provide a power gain of **G [dB]** and a noise factor of **F [dB]** at the design frequency **f [GHz]**.
- At the output of the amplifier insert a order **N** bandpass filter with fractional bandwidth of the passband **B [%]** around the design frequency.

Assignment

- The matching networks and filter must be implemented with transmission lines (stubs: L7-L8).
- The use of the transistors we used in lectures and laboratories examples is not permitted (NE 71084, ATF 34143)
- Delivery deadline: last day of the semester (06.06.2021, 23:59:59)


Assignment

 - this structure is frequently encountered in radiocommunication systems




Multistage amplifiers

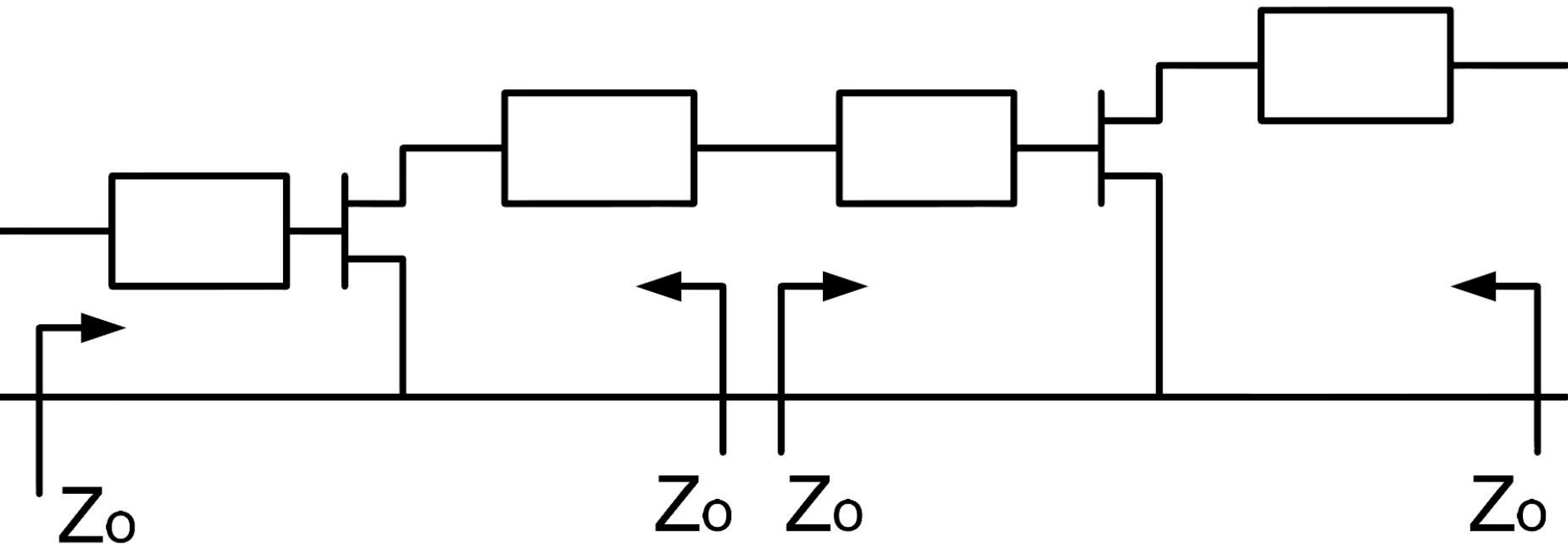- Interstage matching can be designed in two modes:
 - Each stage is matched to a virtual $\Gamma = 0$




Multistage amplifier design

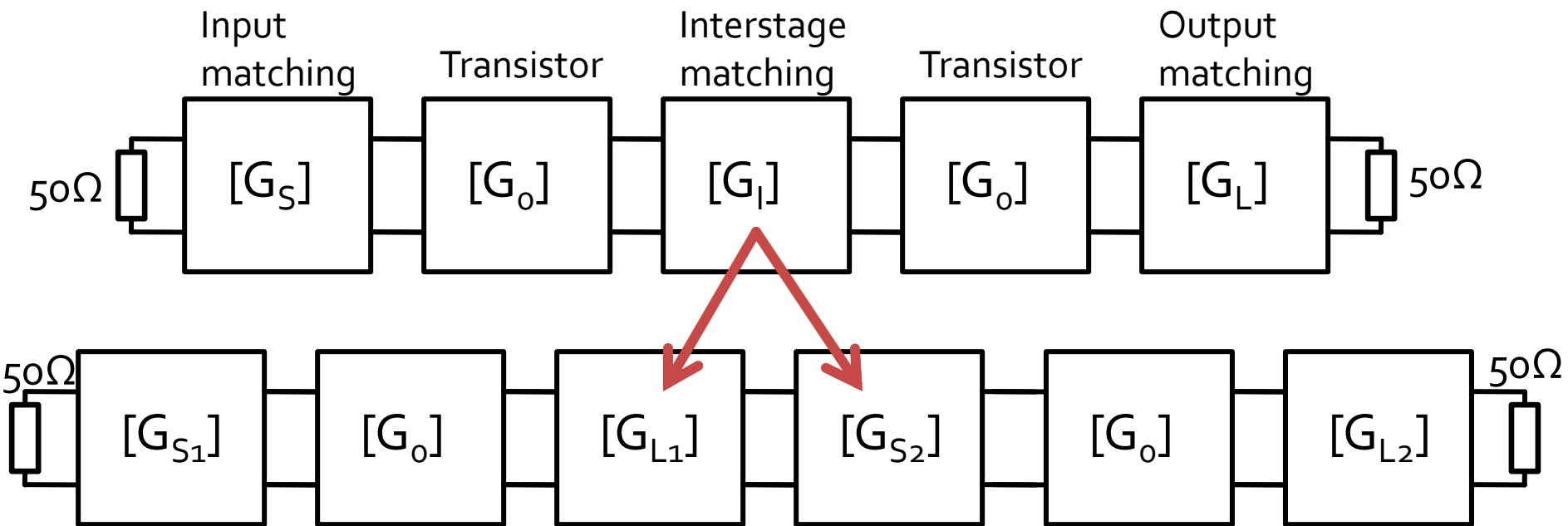

- The design for input and output matching must be achieved on a single transistor schematic (recommended: easier)

Interstage matching

 
- One of the stages creates through its matching network a reflection coefficient $\Gamma=0$ towards which the other stage is matched



The two shunt stubs
combine into a single one

Interstage matching

 - The two shunt stubs combine into a single one



Practical Procedure

Step - 1

- Split performance parameters on the 2 stages
 - G
 - F
- Uses Friis formula
- Pt. 3 example

$$G_{cas} = G_1 \cdot G_2$$

$$F_{cas} = F_1 + \frac{1}{G_1}(F_2 - 1)$$

- 2 equations, 4 unknowns, multiple solutions

Friis Formula (noise)

$$G_{cas} = G_1 \cdot G_2$$

$$F_{cas} = F_1 + \frac{1}{G_1} (F_2 - 1)$$

- Friis formula
 - first stage: low noise factor, probably resulting in a smaller gain
 - second stage: high gain, probably resulting in higher noise factor
- It's essential to introduce a design margin (reserve: ΔF , ΔG)
 - $G = G_{design} + \Delta G$
 - $F = F_{design} - \Delta F$
- Interpretation of the design target
 - $G > G_{design}$, better, but it's not required to sacrifice other parameters to maximize the gain
 - $F < F_{design}$, better, the smaller the better, we must target **the smallest possible noise** factor as long as the other design parameters **are met**

Friis Formula (noise)

- Friis formula
 - first stage: low noise factor, probably resulting in a smaller gain
 - second stage: high gain, probably resulting in higher noise factor
- Division between the two stages (Estimated!)
 - input stage: $F_1 = 0.7$ dB, $G_1 = 9$ dB
 - output stage: $F_2 = 1.2$ dB, $G_2 = 13$ dB
- To verify the result apply Friis formula
- First transform to **linear scale** !

$$F_1 = 10^{\frac{F_1[dB]}{10}} = 10^{0.07} = 1.175$$

$$F_2 = 10^{\frac{F_2[dB]}{10}} = 10^{0.12} = 1.318$$

$$F_{cas} = F_1 + \frac{1}{G_1} (F_2 - 1) = 1.215$$

$$F_{cas} = 10 \cdot \log(1.215) = 0.846 \text{ dB}$$

$$G_1 = 10^{\frac{G_1[dB]}{10}} = 10^{0.9} = 7.943$$

$$G_2 = 10^{\frac{G_2[dB]}{10}} = 10^{1.3} = 19.953$$

$$G_{cas} = G_1 \cdot G_2 = 158.49$$


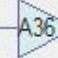
$$G_{cas} = 10 \cdot \log(158.49) = 22 \text{ dB}$$

Friis Formula (noise)

- Avago/Broadcom AppCAD

The screenshot shows the AppCAD - [NoiseCalc] application window. The title bar reads "AppCAD - [NoiseCalc]". The menu bar includes "File", "Calculate", "Application Examples", "Options", and "Help". The main window title is "NoiseCalc". Below the title bar, there is a "Set Number of Stages" field set to "2" and a "Calculate [F4]" button.

The main content area displays a table with the following data:

		Stage 1	Stage 2
Stage Data	Units		
Stage Name:		Avago Duplexer	Avago ATF-36xxx
Noise Figure	dB	0.7	1.2
Gain	dB	9	13
Output IP3	dBm	100	14.5
dNF/dTemp	dB/°C	0	0
dG/dTemp	dB/°C	0	0
Stage Analysis:			
NF (Temp corr)	dB	0.70	1.20
Gain (Temp corr)	dB	9.00	13.00
Input Power	dBm	-50.00	-41.00
Output Power	dBm	-41.00	-28.00
d NF/d NF	dB/dB	0.97	0.15
d NF/d Gain	dB/dB	-0.03	0.00
d IP3/d IP3	dBm/dBm	0.00	1.00

Below the table, there are three sections:

Enter System Parameters:

Input Power	-50	dBm
Analysis Temperature	25	°C
Noise BW	1	MHz
Ref Temperature	25	°C
S/N (for sensitivity)	10	dB
Noise Source (Ref)	290	*K

System Analysis:

Gain =	22.00	dB
Noise Figure =	0.85	dB
Noise Temp =	82.94	*K
SNR =	63.13	dB
MDS =	-113.13	dBm
Sensitivity =	-103.13	dBm
Noise Floor =	-173.13	dBm/Hz

System Analysis (continued):

Input IP3 =	-7.50	dBm
Output IP3 =	14.50	dBm
Input IM level =	-135.00	dBm
Input IM level =	-85.00	dBc
Output IM level =	-113.00	dBm
Output IM level =	-85.00	dBc
SFDR =	70.42	dB

Step - 1

- Result:
 - first amplifier G_1/F_1
 - second amplifier G_2/F_2

Step - 2

- Choose appropriate transistor(**s**) (Gi/Fi)
- Time consuming
- Depending on the design frequency :
 - bipolar
 - unipolar
- Starting from selection guides **recommended**
- Pt. 5 example

Step - 2



- Few selection guides available on rf-opto
- -> Google: microwave/rf transistor, low noise, LNA

Low Noise pHEMTs (Typical Specifications @ 25°C Case Temperature)

Part Number	Gate Width (μm)	Frequency Range (GHz)	Test Freq. (GHz)	V _{dd} (V)	I _{dd} (mA)	NF _o (dB)	G _a (dB)	OIP3 (dBm)	P _{1dB} (dBm)	Package
ATF-33143	1600	0.45 - 6	2	4	80	0.5	15.0	33.5	+22	SOT-343 (SC-70)
ATF-331M4	1600	0.45 - 6	2	4	60	0.6	15.0	31	+19	MiniPak ^[2]
ATF-34143	800	0.45 - 6	2	4	60	0.5	17.5	31.5	+20	SOT-343 (SC-70)
ATF-35143	400	0.45 - 6	2	2	15	0.4	18.0	21	+10	SOT-343 (SC-70)
ATF-38143	800	0.45 - 6	2	2	10	0.4	16.0	22	+12	SOT-343 (SC-70)
ATF-36077	200	1.5 - 18	12	1.5	10	0.5	12.0	—	+5	70 mil SM
ATF-36163	200	1.5 - 18	12	1.5	15	1.2	10.0	—	+5	SOT-363 (SC-70)

Step - 2

  - Take into account the typical variation of the parameters to estimate from test frequency to design frequency
 - Noise factor **increases** with increasing frequency
 - Gain **decreases** with increasing frequency




Step - 2

- Result
 - candidate T1: **ATF34143**
 - candidate T2: **NE71084**

Step - 3

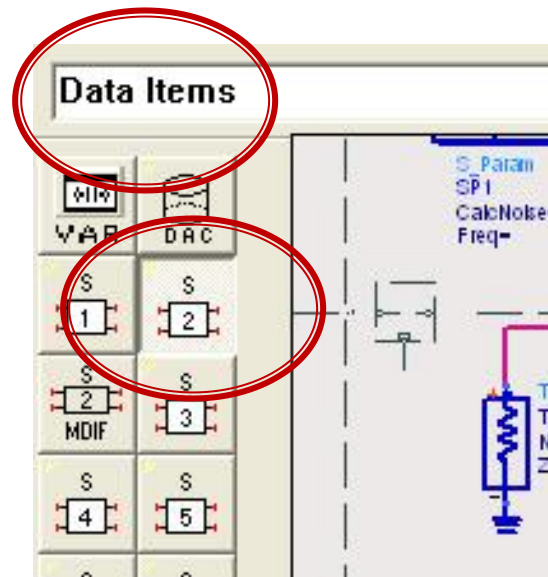- Obtain model data for the candidate transistor(**s**)
- Most often S parameter files (Touchstone)
- Google, manufacturer site: S2p files, S parameters etc.




Step - 4

- Investigate the transistor
 - schematic 1/lab 3-4
 - compute some values (check G/F at design frequency)
 - compute some circles (position, diameter)
 - estimate/choose GS/GL
 - similar to lab3-4
 - for each transistor
- Pt. 7 example

Step - 4

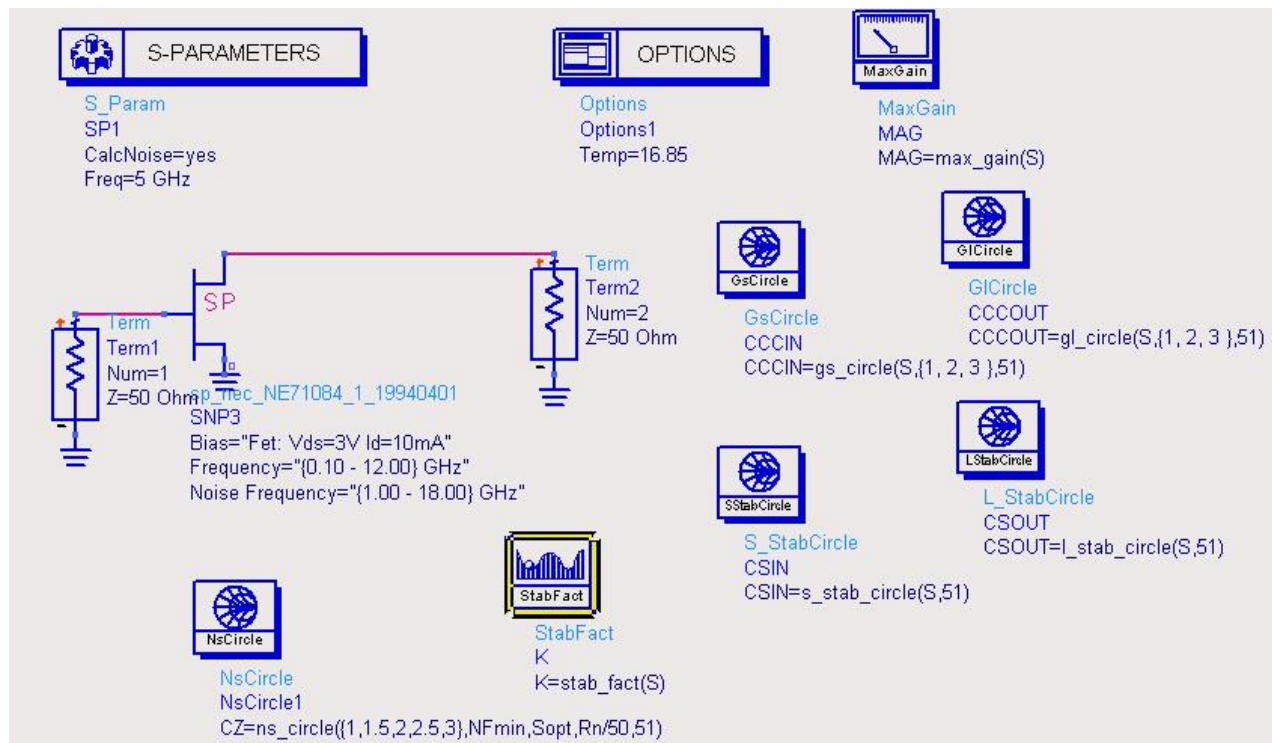- introduce a succession of multiple S parameter files and simulate (**repeatedly**)



Step - 4


- Result
 - candidate T1: **ATF34143** la 3V, 20mA, **GS1 = ~ ... dB, GL1 = ~ ...dB**
 - candidate T2: **NE71084** la 3V, 1mA , **GS2 = ~ ... dB, GL2 = ~ ...dB**

Step - 5

- For each transistor:
- Design of the input matching network
 - schematics 1~2/lab 3-4
- circles on the Smith Chart
 - stability circle
 - noise circle(**s**) (~chosen F)
 - gain circle(**s**) (~chosen GS)
- Pt. 8,9 example

Step - 5

 - Use a marker to get the value of the reflection coefficient Γ_S
 - draw a dummy circle to have a point for the marker



Step - 5

- Calculate the electrical lengths of the two series/parallel lines according to the examples in the course/project
 - write down (on paper) the computation (**!!"andrei" factor**)

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

Step - 5


- Result:
 - electrical length **E_1 , E_2**
 - for each transistor

Step - 6

- For each transistor:
- Design of the output matching network
 - schematics 1~2/lab 3-4
- circles on the Smith Chart
 - stability circle
 - ~~■ noise circle(**s**) (~chosen F)~~
 - gain circle(**s**) (~chosen GL)
- Pt. 8,9 example

Step - 6

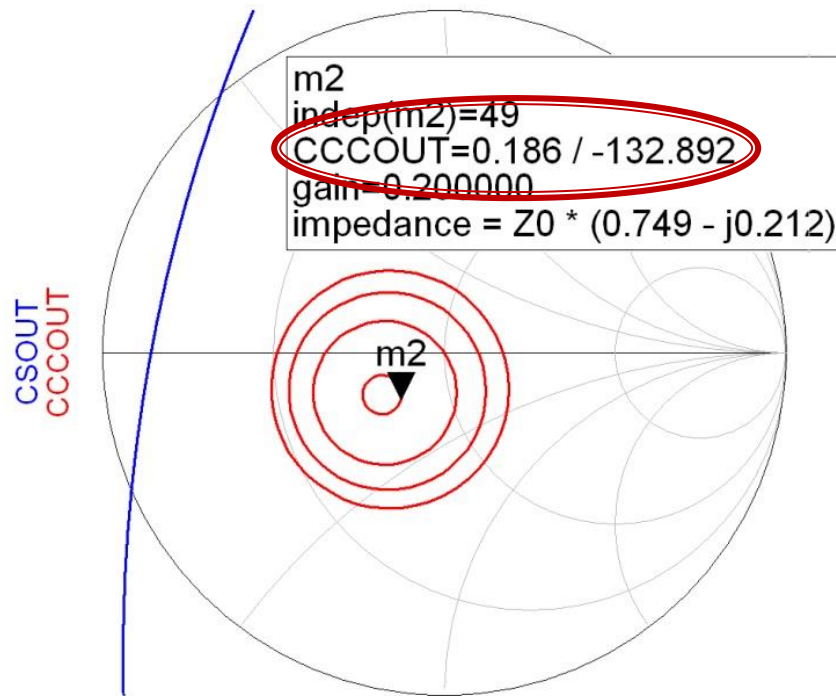- Use a marker to get the value of the reflection coefficient Γ_L



Step - 6

- Calculate the electrical lengths of the two series/parallel lines according to the examples in the course/project
 - write down (on paper) the computation (**!!"andrei" factor**)

$$\cos(\varphi + 2\theta) = -|\Gamma_L|$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}}$$

Step - 6


- Result:
 - electrical length E_3, E_4
 - for each transistor

Step - 7



- For each transistor
- Check E_1, E_2, E_3, E_4
- Insert lines E_1, E_2 as the input network and E_3, E_4 as the output network and check if the proposed G / NF results are obtained.
 - Check and repeat the calculations

- Pt. 8,9 example

Step - 7

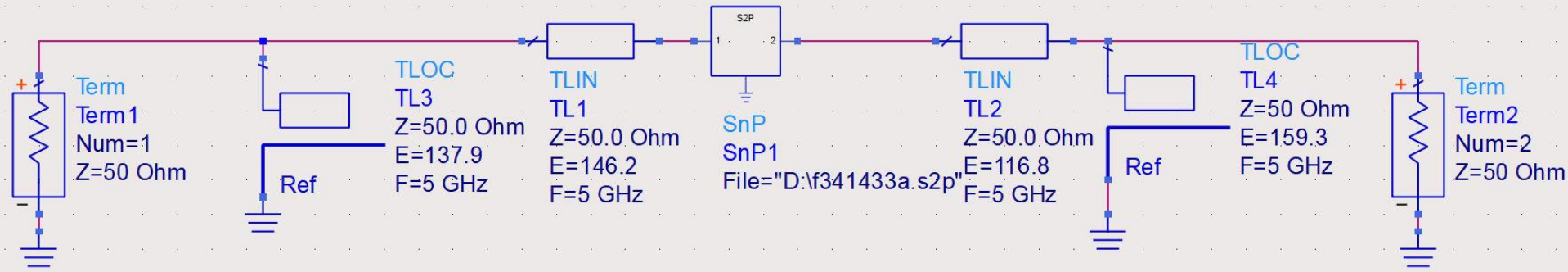

Step - 7

 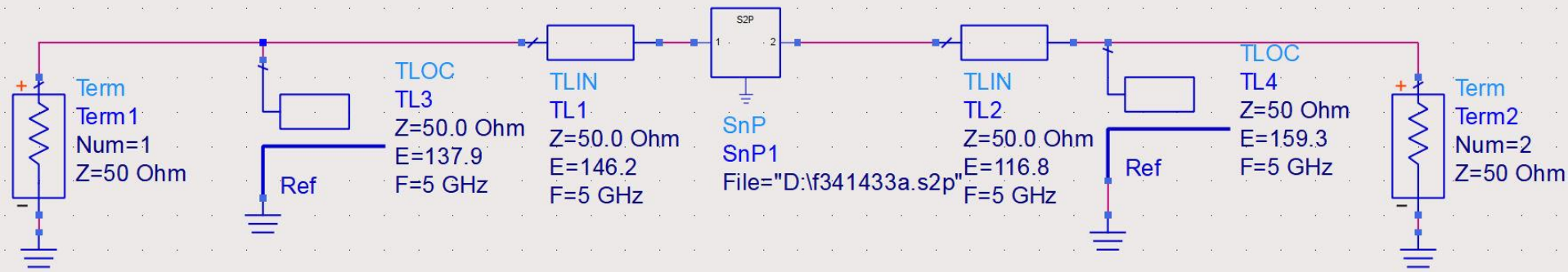

Step - 7

- Result
 - adopted T₁: **ATF34143** I_a 3V, 20mA, GS₁ = ... dB, GL₁ = ...dB
 - adopted T₂: **NE71084** I_a 3V, 1mA, GS₂ = ... dB, GL₂ = ...dB

Step - 8


- Following steps 1-7 we have two functional one transistor amplifier stages which fulfill Friis formulae:

- G_1, G_2 $G_{cas} = G_1 \cdot G_2$ $G_{cas} [dB] = G_{tema} + \Delta G$
- F_1, F_2 $F_{cas} = F_1 + \frac{1}{G_1} (F_2 - 1)$ $F_{cas} [dB] = F_{tema} - \Delta F$

- Cascade connection of the two amplifiers to get a single two stage amplifier
- Pt. 10 example

Step - 8

 - Following steps 5,6 we know the electrical lengths of the lines from the output of first transistor and input of the second transistor







The two shunt stubs will combine into a single shunt stub

Step - 8

- The two series lines keep their previous values
 - **Attention!** solutions are dual +/- for both amplifiers, for every series line any of the two solutions are available (**independently**)
- The two shunt lines combine into a single shunt line
 - **Attention!** admittances are in parallel and add up, not the electrical lengths
 - Recovering $\text{Im}(y_1)$, $\text{Im}(y_2)$ from step 5,6 computations is required
 - Solutions for admittances are also dual, chose (+/-) values corresponding to **already chosen solutions** for the series lines

Step - 8

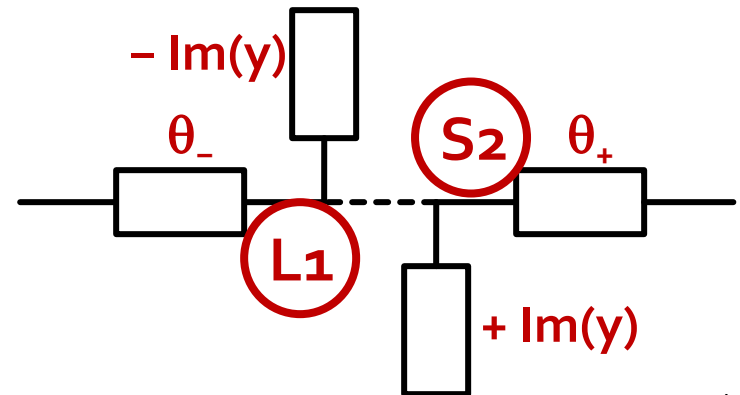 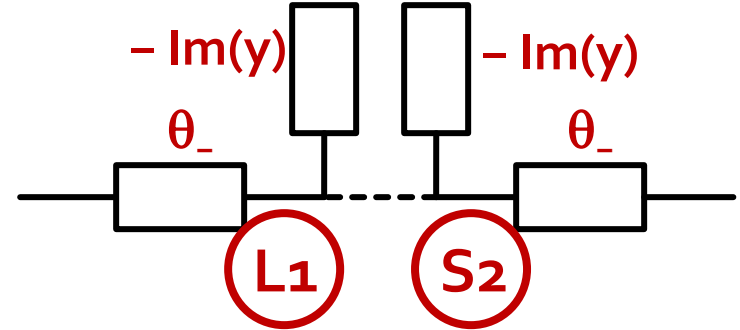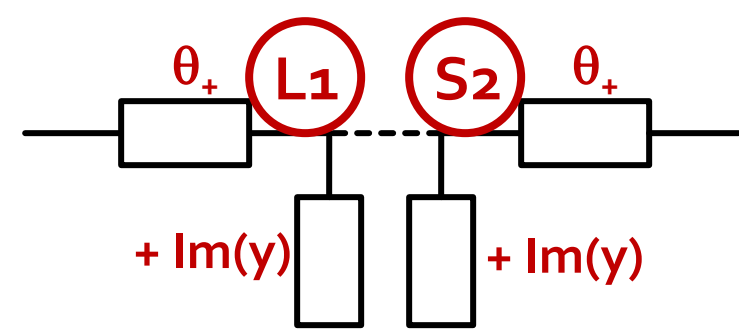- 4 possible combinations
 - admittances** are in parallel and **add up**, not the electrical lengths



$$\text{Im}[y_{sp}] = \text{Im}[y_{L1}(\theta)] + \text{Im}[y_{S2}(\theta)]$$


$$\theta_{sp} = \tan^{-1}(\text{Im}[y_{sp}])$$

Step - 8

- Compute the required admittance of the combined shunt stub
 - $\text{Im}(y) = \text{Im}(y_1) + \text{Im}(y_2)$
- Compute the electrical length that offer this admittance
 - $E = \tan^{-1}(\text{Im}(y))$
- Combine the two amplifiers, keeping the series lines and replacing the interstage shunt stubs with the computed combined shunt stub




Step - 8

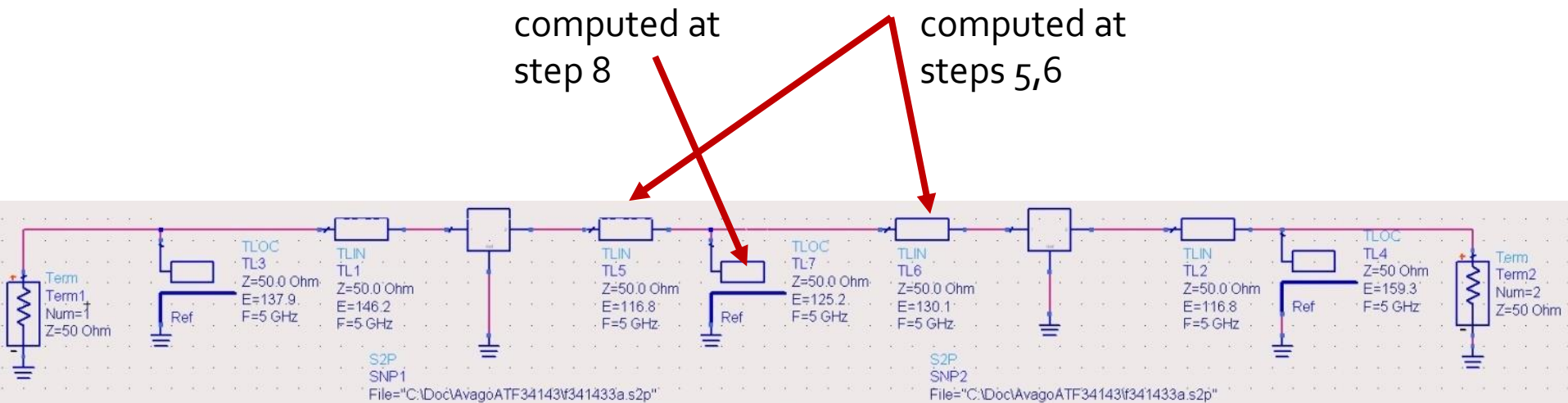- Result
 - final amplifier
- Simulate to verify computations
 - Pt. 11 example



Step - 8

- Simulate to verify computations

  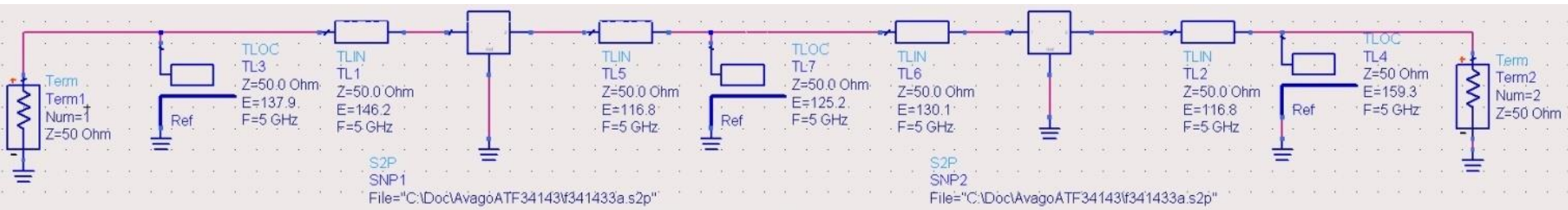

Step - 9

- Design and draw filter schematic
- Pt. 13 example

- Depending on the type of filter formulae and schematic are different
 - other type other than coupled-lines offers bonus point


Step - 9

- **Attention!** Filter design can be done only by computation
 - due to high number of parameters (order 5-6, 12-14 parameters) **it's not possible** to get good results by tuning

n	g_n	$Z_o J_n$	$Z_{oe} [\Omega]$	$Z_{oo} [\Omega]$
1	1.6703	0.306664	70.04	39.37
2	1.1926	0.111295	56.18	45.05
3	2.3661	0.09351	55.11	45.76
4	0.8419	0.111294	56.18	45.05
5	1.9841	0.306653	70.03	39.37


Step - 9

- Simulate to verify filter separately

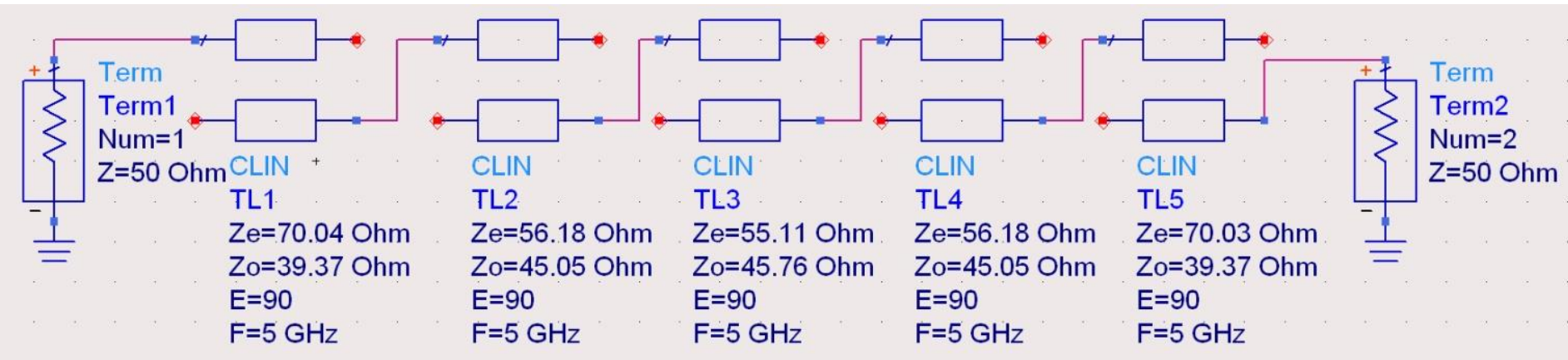

Step - 9

 - Check carefully the passband, and maximum ripple/loss in passband
 - correct passband is **significant** in project grade
 - eventual uncontrolled losses in passband will lower amplifier gain and gain assignment fulfillment might fail



Step - 10

- Follow lab 3 principles for final tune
 - input lines mainly to change noise, output lines only change gain
- Pt. 14 example

Step - 11

- Implement supplemental design for additional points
 - Proving additional points will require submission of archived ADS project (*.zap)

Contact

- Laboratorul de microunde si optoelectronica
- <http://rf-opto.etti.tuiasi.ro>
- rdamian@etti.tuiasi.ro