

Subject no. 1

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (36.0 + j \cdot 42.6)\Omega = 0.579 + j \cdot 0.685$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.579 + j \cdot 0.685)] / (1 + 0.579 + j \cdot 0.685)$
 $\Gamma = (0.066) + j \cdot (0.463) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.467 \angle 81.8^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 7.9\text{dBm} - 5.30\text{dB} = 2.60\text{dBm}$;

b) $P_{in} = 7.9\text{dBm} = 6.166\text{mW}$; $P_c = 2.60\text{dBm} = 1.820\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 6.166\text{mW} - 1.820\text{mW} = 4.346\text{mW} = 6.381\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.543, y_2 = 1.191, y_1 = 0.647, Z_1 = Z_0/y_1 = 77.3 \Omega, Z_2 = Z_0/y_2 = 42.0\Omega$

3. a) $Z = 66.00\Omega + j \cdot (27.22)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.183 + j \cdot (0.192) = 0.265 \angle 46.3^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.265$; $\varphi = \arg(\Gamma) = 46.3^\circ$; Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 29.5^\circ$; $\text{Im}(y_S) = -0.550$; $\theta_{P1} = 151.2^\circ$ **or** $\theta_{S2} = 104.1^\circ$; $\text{Im}(y_S) = 0.550$; $\theta_{P2} = 28.8^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 515\text{MHz} = 3.236 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 53.799\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 4.709\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 70.122\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 4.709\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 53.799\text{nH}$;

b) Draw the schematic:

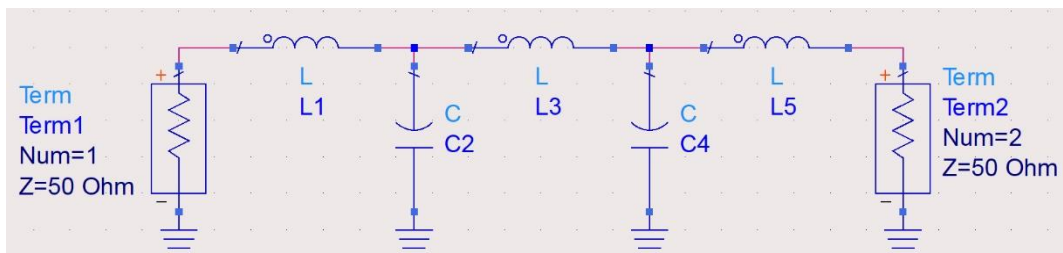

c) In the passband ($f < 515 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 515 \text{ MHz}$; In the stopband ($f > 515 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 1030.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 23.7\text{dB} + 24.8\text{dB} + 21.1\text{dB} = 69.6\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 9,120,108.4$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A1, A3 so: $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1$; $F_1 = 3.90\text{dB} = 2.455, G_1 = 23.7\text{dB} = 234.423, F_2 = 4.23\text{dB} = 2.649, G_2 = 24.8\text{dB} = 301.995, F_3 = 5.65\text{dB} = 3.673, G_3 = 21.1\text{dB} = 128.825$;

$F = 2.649 + (2.455 - 1)/301.995 + (3.673 - 1)/301.995/234.423 = 2.653 = 4.238\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$F = 2.649 + (3.673 - 1)/301.995 + (2.455 - 1)/301.995/128.825 = 2.657 = 4.245\text{dB}$

Subject no. 2

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (56.1 - j \cdot 61.4)\Omega = 0.406 - j \cdot 0.444$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.406 - j \cdot 0.444)] / (1 + 0.406 - j \cdot 0.444)$
 $\Gamma = (0.294) + j \cdot (-0.409) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.503 \angle -54.3^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 7.0\text{dBm} - 5.80\text{dB} = 1.20\text{dBm}$;

b) $P_{in} = 7.0\text{dBm} = 5.012\text{mW}$; $P_c = 1.20\text{dBm} = 1.318\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 5.012\text{mW} - 1.318\text{mW} = 3.694\text{mW} = 5.675\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.513, y_2 = 1.165, y_1 = 0.597, Z_1 = Z_0/y_1 = 83.7 \Omega, Z_2 = Z_0/y_2 = 42.9\Omega$

3. a) $Z = 72.00\Omega + j \cdot (74.08)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.401 + j \cdot (0.364) = 0.541 \angle 42.2^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.541$; $\varphi = \arg(\Gamma) = 42.2^\circ$; Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 40.3^\circ$; $\text{Im}(y_s) = -1.288$; $\theta_{P1} = 127.8^\circ$ **or** $\theta_{S2} = 97.5^\circ$; $\text{Im}(y_s) = 1.288$; $\theta_{P2} = 52.2^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 315\text{MHz} = 1.979 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 5.924\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 20.545\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 3.977\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 20.545\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 5.924\text{pF}$;

b) Draw the schematic:

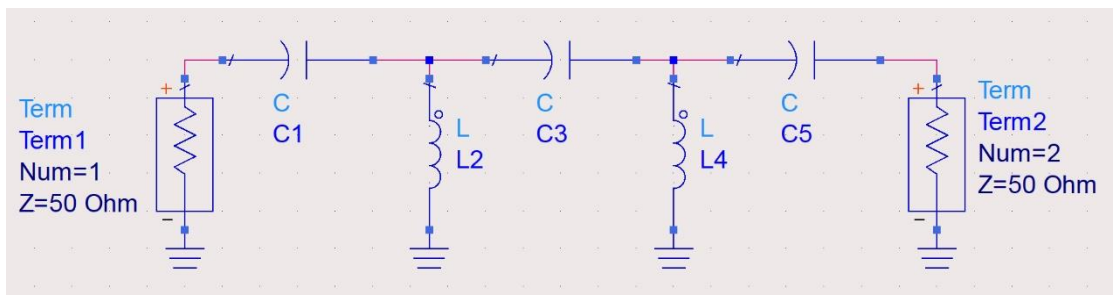

c) In the passband ($f > 315 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 315 \text{ MHz}$; In the stopband ($f < 315 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 157.5 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 18.8\text{dB} + 22.7\text{dB} + 23.4\text{dB} = 64.9\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 3,090,295.4$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A3, A1 so: $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$; $F_1 = 3.17\text{dB} = 2.075$, $G_1 = 18.8\text{dB} = 75.858$, $F_2 = 4.12\text{dB} = 2.582$, $G_2 = 22.7\text{dB} = 186.209$, $F_3 = 5.18\text{dB} = 3.296$, $G_3 = 23.4\text{dB} = 218.776$;

$F = 2.582 + (3.296 - 1)/186.209 + (2.075 - 1)/186.209/218.776 = 2.595 = 4.141\text{dB}$

c) If the order is A1, A2, A3 the gain remains the same but $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$;

$F = 2.075 + (2.582 - 1)/75.858 + (3.296 - 1)/75.858/186.209 = 2.096 = 3.214\text{dB}$

Subject no. 3


1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (45.6 - j \cdot 36.0)\Omega = 0.675 - j \cdot 0.533$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.675 - j \cdot 0.533)] / (1 + 0.675 - j \cdot 0.533)$
 $\Gamma = (0.084) + j \cdot (-0.345) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.355 \angle -76.3^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 4.8\text{dBm} - 4.10\text{dB} = 0.70\text{dBm}$;
 b) $P_{in} = 4.8\text{dBm} = 3.020\text{mW}$; $P_c = 0.70\text{dBm} = 1.175\text{mW}$;
 Lossless coupler $P_{th} = P_{in} - P_c = 3.020\text{mW} - 1.175\text{mW} = 1.845\text{mW} = 2.660\text{dBm}$
 c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.624, y_2 = 1.279, y_1 = 0.798, Z_1 = Z_0/y_1 = 62.7 \Omega, Z_2 = Z_0/y_2 = 39.1\Omega$

3. a) $Z = 60.00\Omega + j \cdot (67.46)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.339 + j \cdot (0.405) = 0.528 \angle 50.0^\circ$;
 b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.
 c) $|\Gamma| = 0.528$; $\varphi = \arg(\Gamma) = 50.0^\circ$; Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 35.9^\circ$; $\text{Im}(y_s) = -1.245$; $\theta_{P1} = 128.8^\circ$ **or** $\theta_{S2} = 94.0^\circ$; $\text{Im}(y_s) = 1.245$; $\theta_{P2} = 51.2^\circ$
 c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 560\text{MHz} = 3.519 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).
 Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:
 g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 49.476\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 4.330\text{pF}$;
 g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 64.488\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 4.330\text{pF}$;
 g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 49.476\text{nH}$;

b) Draw the schematic:

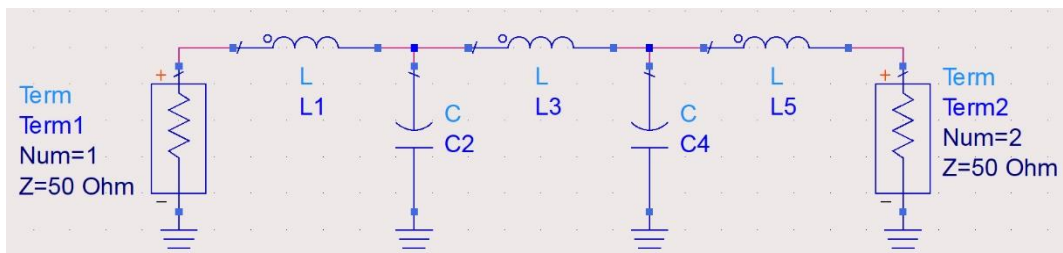

c) In the passband ($f < 560 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 560 \text{ MHz}$; In the stopband ($f > 560 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 1120.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:
 $G[\text{dB}] = G_1 + G_2 + G_3 = 23.4\text{dB} + 24.8\text{dB} + 19.1\text{dB} = 67.3\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 5,370,318.0$
 b) 3 amplifiers Friis formula, $F = F_1 + (F_2-1)/G_1 + (F_3-1)/G_1/G_2$ but the connection order is A3, A1, A2 so: $F = F_3 + (F_1-1)/G_3 + (F_2-1)/G_3/G_1$; $F_1 = 3.81\text{dB} = 2.404, G_1 = 23.4\text{dB} = 218.776, F_2 = 4.83\text{dB} = 3.041, G_2 = 24.8\text{dB} = 301.995, F_3 = 5.30\text{dB} = 3.388, G_3 = 19.1\text{dB} = 81.283$;
 $F = 3.388 + (2.404-1)/81.283 + (3.041-1)/81.283/218.776 = 3.406 = 5.322\text{dB}$
 c) If the order is A1, A3, A2 the gain remains the same but $F = F_1 + (F_3-1)/G_1 + (F_2-1)/G_1/G_3$;
 $F = 2.404 + (3.388-1)/218.776 + (3.041-1)/218.776/81.283 = 2.415 = 3.830\text{dB}$

Subject no. 4

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (32.5 + j \cdot 33.1)\Omega = 0.755 + j \cdot 0.769$;

$\Gamma = (1 - y) / (1 + y) = [1 - (0.755 + j \cdot 0.769)] / (1 + 0.755 + j \cdot 0.769)$

$\Gamma = (-0.044) + j \cdot (0.419) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.421 \angle 96.0^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 5.9\text{dBm} - 7.60\text{dB} = -1.70\text{dBm}$;

b) $P_{in} = 5.9\text{dBm} = 3.890\text{mW}$; $P_c = -1.70\text{dBm} = 0.676\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 3.890\text{mW} - 0.676\text{mW} = 3.214\text{mW} = 5.071\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.417$, $y_2 = 1.100$, $y_1 = 0.459$, $Z_1 = Z_0/y_1 = 109.0\Omega$, $Z_2 = Z_0/y_2 = 45.4\Omega$

3. a) $Z = 18.02\Omega + j \cdot (-31.48)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.211 + j \cdot (-0.560) = 0.599 \angle -110.6^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.599$; $\varphi = \arg(\Gamma) = -110.6^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 118.7^\circ$; $\text{Im}(y_s) = -1.495$; $\theta_{P1} = 123.8^\circ$ **or** $\theta_{S2} = 171.9^\circ$; $\text{Im}(y_s) = 1.495$; $\theta_{P2} = 56.2^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 575\text{MHz} = 3.613 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180$, $g_2 = 1.6180$, $g_3 = 2.0000$, $g_4 = 1.6180$, $g_5 = 0.6180$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 8.958\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 8.553\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 2.768\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 8.553\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 8.958\text{pF}$;

b) Draw the schematic:

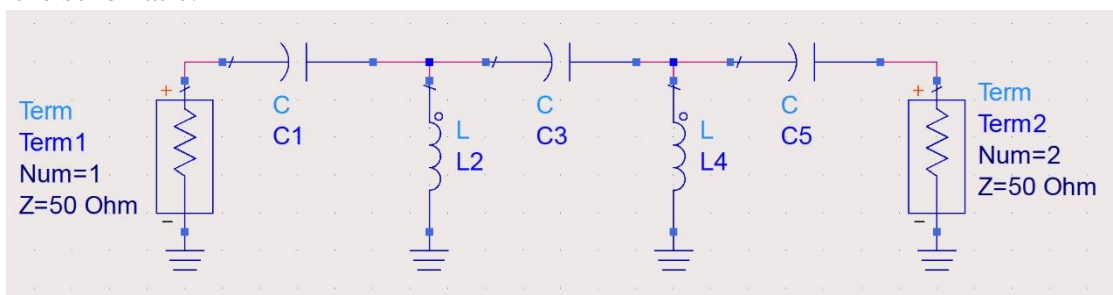

c) In the passband ($f > 575 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 575 \text{ MHz}$; In the stopband ($f < 575 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 287.5 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 19.5\text{dB} + 19.7\text{dB} + 24.6\text{dB} = 63.8\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 2,398,832.9$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A1, A3 so: $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1$; $F_1 = 3.88\text{dB} = 2.443$, $G_1 = 19.5\text{dB} = 89.125$, $F_2 = 4.25\text{dB} = 2.661$, $G_2 = 19.7\text{dB} = 93.325$, $F_3 = 5.46\text{dB} = 3.516$, $G_3 = 24.6\text{dB} = 288.403$;

$F = 2.661 + (2.443 - 1)/93.325 + (3.516 - 1)/93.325/89.125 = 2.676 = 4.276\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$F = 2.661 + (3.516 - 1)/93.325 + (2.443 - 1)/93.325/288.403 = 2.688 = 4.294\text{dB}$

Subject no. 5

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (60.9 + j \cdot 54.2)\Omega = 0.458 + j \cdot 0.408;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.458 + j \cdot 0.408)] / (1 + 0.458 + j \cdot 0.408)$$

$$\Gamma = (0.272) + j \cdot (0.356) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.448 \angle 52.6^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

$$2. a) P_c = P_{in} - C = 8.7\text{dBm} - 4.70\text{dB} = 4.00\text{dBm};$$

$$b) P_{in} = 8.7\text{dBm} = 7.413\text{mW}; P_c = 4.00\text{dBm} = 2.512\text{mW};$$

$$\text{Lossless coupler } P_{th} = P_{in} - P_c = 7.413\text{mW} - 2.512\text{mW} = 4.901\text{mW} = 6.903\text{dBm}$$

$$c) L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.582, y_2 = 1.230, y_1 = 0.716, Z_1 = Z_0/y_1 = 69.8 \Omega, Z_2 = Z_0/y_2 = 40.7\Omega$$

$$3. a) Z = 25.00\Omega + j \cdot (29.48)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.155 + j \cdot (0.454) = 0.480 \angle 108.8^\circ ;$$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

$$c) |\Gamma| = 0.480; \varphi = \arg(\Gamma) = 108.8^\circ; \text{Complex calculus from L8/2024, S114}\div 115, \text{ all lines have } Z_0 = 50\Omega$$

$$\theta_{S1} = 4.9^\circ ; \text{Im}(y_s) = -1.093 ; \theta_{P1} = 132.4^\circ \text{ or } \theta_{S2} = 66.3^\circ ; \text{Im}(y_s) = 1.093 ; \theta_{P2} = 47.6^\circ$$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 325\text{MHz} = 2.042 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180, g_2 = 1.6180, g_3 = 2.0000, g_4 = 1.6180, g_5 = 0.6180, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

$$g_1 : \text{series capacitor } C_1 = 1 / R_0 / g_1 / \omega_c = 15.848\text{pF}; g_2 : \text{shunt inductor } L_2 = R_0 / g_2 / \omega_c = 15.133\text{nH};$$

$$g_3 : \text{series capacitor } C_3 = 1 / R_0 / g_3 / \omega_c = 4.897\text{pF}; g_4 : \text{shunt inductor } L_4 = R_0 / g_4 / \omega_c = 15.133\text{nH};$$

$$g_5 : \text{series capacitor } C_5 = 1 / R_0 / g_5 / \omega_c = 15.848\text{pF};$$

b) Draw the schematic:

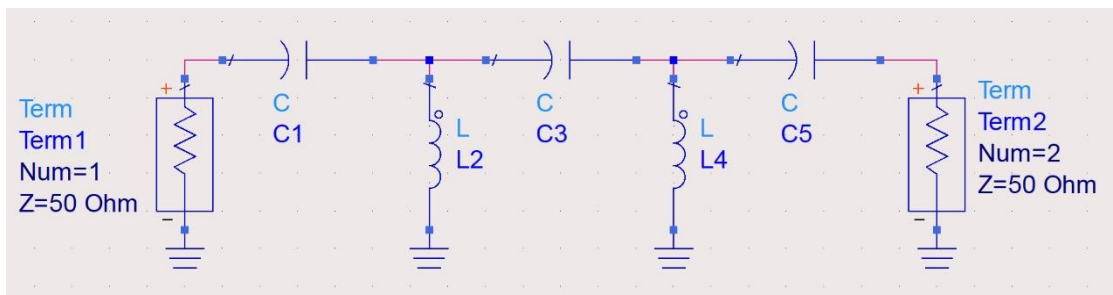

c) In the passband ($f > 325 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 325 \text{ MHz}$; In the stopband ($f < 325 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 162.5 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 24.0\text{dB} + 15.9\text{dB} + 21.8\text{dB} = 61.7\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 1,479,108.4$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A3, A1 so: $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$; $F_1 = 3.01\text{dB} = 2.000, G_1 = 24.0\text{dB} = 251.189, F_2 = 4.20\text{dB} = 2.630, G_2 = 15.9\text{dB} = 38.905, F_3 = 5.64\text{dB} = 3.664, G_3 = 21.8\text{dB} = 151.356$;

$$F = 2.630 + (3.664 - 1)/38.905 + (2.000 - 1)/38.905/151.356 = 2.699 = 4.312\text{dB}$$

c) If the order is A1, A2, A3 the gain remains the same but $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$;

$$F = 2.000 + (2.630 - 1)/251.189 + (3.664 - 1)/251.189/38.905 = 2.007 = 3.025\text{dB}$$

Subject no. 6

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (52.4 + j \cdot 57.7)\Omega = 0.431 + j \cdot 0.475;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.431 + j \cdot 0.475)] / (1 + 0.431 + j \cdot 0.475)$$

$$\Gamma = (0.259) + j \cdot (0.418) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.491 \angle 58.2^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 5.3\text{dBm} - 7.75\text{dB} = -2.45\text{dBm};$

b) $P_{in} = 5.3\text{dBm} = 3.388\text{mW}; P_c = -2.45\text{dBm} = 0.569\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 3.388\text{mW} - 0.569\text{mW} = 2.820\text{mW} = 4.502\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.410, y_2 = 1.096, y_1 = 0.449, Z_1 = Z_0/y_1 = 111.3 \Omega, Z_2 = Z_0/y_2 = 45.6\Omega$

3. a) $Z = 33.38\Omega + j \cdot (26.86)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.087 + j \cdot (0.350) = 0.361 \angle 103.9^\circ ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.361; \varphi = \arg(\Gamma) = 103.9^\circ; \text{Complex calculus from L8/2024, S114}\div\text{115, all lines have } Z_0 = 50\Omega$
 $\theta_{S1} = 3.6^\circ ; \text{Im}(y_S) = -0.773 ; \theta_{P1} = 142.3^\circ \text{ or } \theta_{S2} = 72.5^\circ ; \text{Im}(y_S) = 0.773 ; \theta_{P2} = 37.7^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 455\text{MHz} = 2.859 \cdot 10^9 \text{ rad/s} ; R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180, g_2 = 1.6180, g_3 = 2.0000, g_4 = 1.6180, g_5 = 0.6180, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 10.809\text{nH}; g_2$: shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 11.319\text{pF};$

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 34.979\text{nH}; g_4$: shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 11.319\text{pF};$

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 10.809\text{nH};$

b) Draw the schematic:

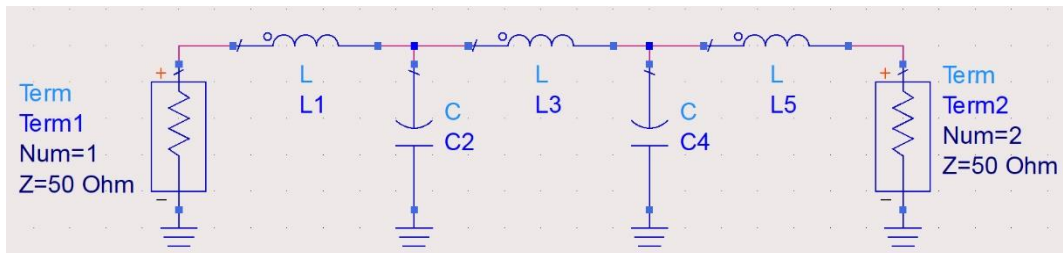

c) In the passband ($f < 455 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 455 \text{ MHz}$; In the stopband ($f > 455 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 910.0 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 17.0\text{dB} + 18.6\text{dB} + 23.6\text{dB} = 59.2\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 831,763.8$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2; F_1 = 3.63\text{dB} = 2.307, G_1 = 17.0\text{dB} = 50.119, F_2 = 4.37\text{dB} = 2.735, G_2 = 18.6\text{dB} = 72.444, F_3 = 5.31\text{dB} = 3.396, G_3 = 23.6\text{dB} = 229.087;$

$F = 2.307 + (2.735 - 1)/50.119 + (3.396 - 1)/50.119/72.444 = 2.342 = 3.696\text{dB}$

c) If the order is A1, A3, A2 the gain remains the same but $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3;$

$F = 2.307 + (3.396 - 1)/50.119 + (2.735 - 1)/50.119/229.087 = 2.355 = 3.719\text{dB}$

Subject no. 7

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (42.4 + j \cdot 55.7)\Omega = 0.433 + j \cdot 0.568;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.433 + j \cdot 0.568)] / (1 + 0.433 + j \cdot 0.568)$$

$$\Gamma = (0.206) + j \cdot (0.479) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.521 \angle 66.7^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 2.4\text{dBm} - 8.05\text{dB} = -5.65\text{dBm};$

b) $P_{in} = 2.4\text{dBm} = 1.738\text{mW}; P_c = -5.65\text{dBm} = 0.272\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 1.738\text{mW} - 0.272\text{mW} = 1.466\text{mW} = 1.660\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.396, y_2 = 1.089, y_1 = 0.431, Z_1 = Z_0/y_1 = 116.0 \Omega, Z_2 = Z_0/y_2 = 45.9\Omega$

3. a) $Z = 63.00\Omega + j \cdot (-67.56)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = 0.348 + j \cdot (-0.390) = 0.523 \angle -48.2^\circ ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.523; \varphi = \arg(\Gamma) = -48.2^\circ; \text{Complex calculus from L8/2024, S114}\div\text{115, all lines have } Z_0 = 50\Omega$
 $\theta_{S1} = 84.9^\circ ; \text{Im}(y_s) = -1.226 ; \theta_{P1} = 129.2^\circ \text{ or } \theta_{S2} = 143.4^\circ ; \text{Im}(y_s) = 1.226 ; \theta_{P2} = 50.8^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 535\text{MHz} = 3.362 \cdot 10^9 \text{ rad/s} ; R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 25.373\text{nH}; g_2$: shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 7.316\text{pF};$

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 37.793\text{nH}; g_4$: shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 7.316\text{pF};$

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 25.373\text{nH};$

b) Draw the schematic:

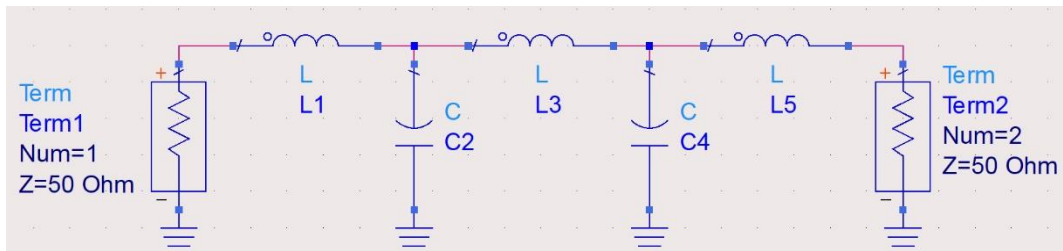

c) In the passband ($f < 535 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 535 \text{ MHz}$; In the stopband ($f > 535 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 1070.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 23.4\text{dB} + 15.3\text{dB} + 16.4\text{dB} = 55.1\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 323,593.7$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A3, A1, A2 so: $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1; F_1 = 3.55\text{dB} = 2.265, G_1 = 23.4\text{dB} = 218.776, F_2 = 4.83\text{dB} = 3.041, G_2 = 15.3\text{dB} = 33.884, F_3 = 5.13\text{dB} = 3.258, G_3 = 16.4\text{dB} = 43.652;$

$F = 3.258 + (2.265 - 1)/43.652 + (3.041 - 1)/43.652/218.776 = 3.288 = 5.169\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3;$

$F = 3.041 + (3.258 - 1)/33.884 + (2.265 - 1)/33.884/43.652 = 3.108 = 4.925\text{dB}$

Subject no. 8

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (48.1 - j \cdot 45.6)\Omega = 0.547 - j \cdot 0.519$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.547 - j \cdot 0.519)] / (1 + 0.547 - j \cdot 0.519)$
 $\Gamma = (0.162) + j \cdot (-0.390) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.422 \angle -67.5^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 2.6\text{dBm} - 7.75\text{dB} = -5.15\text{dBm}$;

b) $P_{in} = 2.6\text{dBm} = 1.820\text{mW}$; $P_c = -5.15\text{dBm} = 0.305\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 1.820\text{mW} - 0.305\text{mW} = 1.514\text{mW} = 1.802\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.410, y_2 = 1.096, y_1 = 0.449, Z_1 = Z_0/y_1 = 111.3 \Omega, Z_2 = Z_0/y_2 = 45.6\Omega$

3. a) $Z = 20.78\Omega + j \cdot (-9.36)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.388 + j \cdot (-0.184) = 0.430 \angle -154.7^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.430$; $\varphi = \arg(\Gamma) = -154.7^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 135.1^\circ$; $\text{Im}(y_s) = -0.952$; $\theta_{P1} = 136.4^\circ$ **or** $\theta_{S2} = 19.6^\circ$; $\text{Im}(y_s) = 0.952$; $\theta_{P2} = 43.6^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 530\text{MHz} = 3.330 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 3.521\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 12.21\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 2.364\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 12.21\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 3.521\text{pF}$;

b) Draw the schematic:

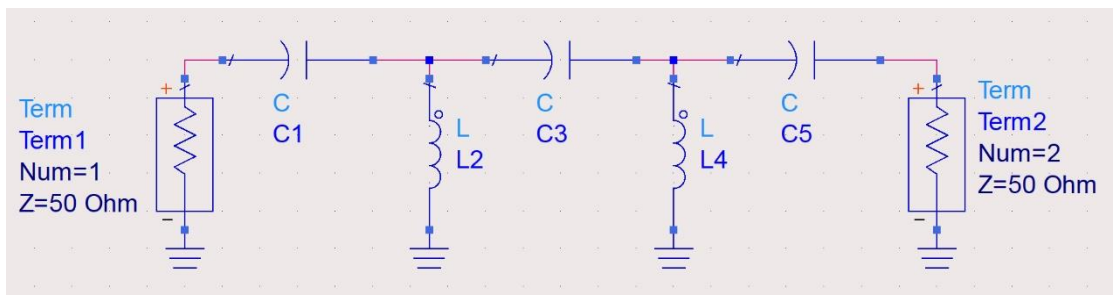

c) In the passband ($f > 530 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 530 \text{ MHz}$; In the stopband ($f < 530 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 265.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 18.4\text{dB} + 18.6\text{dB} + 20.7\text{dB} = 57.7\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 588,843.7$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$; $F_1 = 3.24\text{dB} = 2.109, G_1 = 18.4\text{dB} = 69.183, F_2 = 4.62\text{dB} = 2.897, G_2 = 18.6\text{dB} = 72.444, F_3 = 5.59\text{dB} = 3.622, G_3 = 20.7\text{dB} = 117.490$;

$F = 2.109 + (2.897 - 1)/69.183 + (3.622 - 1)/69.183/72.444 = 2.137 = 3.297\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$F = 2.897 + (3.622 - 1)/72.444 + (2.109 - 1)/72.444/117.490 = 2.934 = 4.674\text{dB}$

Subject no. 9

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (33.6 - j \cdot 58.3)\Omega = 0.371 - j \cdot 0.644;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.371 - j \cdot 0.644)] / (1 + 0.371 - j \cdot 0.644)$$

$$\Gamma = (0.195) + j \cdot (-0.561) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.594 \angle -70.8^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 5.5\text{dBm} - 6.75\text{dB} = -1.25\text{dBm};$

b) $P_{in} = 5.5\text{dBm} = 3.548\text{mW}; P_c = -1.25\text{dBm} = 0.750\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 3.548\text{mW} - 0.750\text{mW} = 2.798\text{mW} = 4.469\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.460, y_2 = 1.126, y_1 = 0.518, Z_1 = Z_0/y_1 = 96.6 \Omega, Z_2 = Z_0/y_2 = 44.4\Omega$

3. a) $Z = 74.00\Omega + j \cdot (-28.69)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = 0.235 + j \cdot (-0.177) = 0.294 \angle -37.1^\circ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.294; \varphi = \arg(\Gamma) = -37.1^\circ;$ Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 72.1^\circ; \text{Im}(y_S) = -0.615; \theta_{P1} = 148.4^\circ$ **or** $\theta_{S2} = 145.0^\circ; \text{Im}(y_S) = 0.615; \theta_{P2} = 31.6^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 400\text{MHz} = 2.513 \cdot 10^9 \text{ rad/s}; R_0 = 50\Omega.$ Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 33.936\text{nH}; g_2$: shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 9.785\text{pF};$

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 50.548\text{nH}; g_4$: shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 9.785\text{pF};$

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 33.936\text{nH};$

b) Draw the schematic:

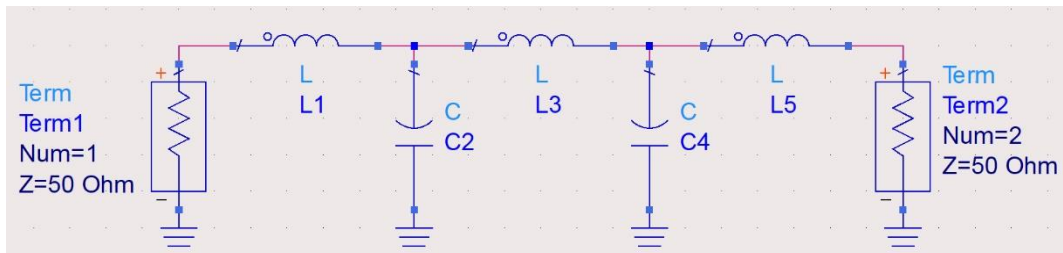

c) In the passband ($f < 400 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 400 \text{ MHz}$; In the stopband ($f > 400 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 800.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 20.7\text{dB} + 19.9\text{dB} + 21.0\text{dB} = 61.6\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 1,445,439.8$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A3, A2 so: $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3; F_1 = 3.52\text{dB} = 2.249, G_1 = 20.7\text{dB} = 117.490, F_2 = 4.29\text{dB} = 2.685, G_2 = 19.9\text{dB} = 97.724, F_3 = 5.86\text{dB} = 3.855, G_3 = 21.0\text{dB} = 125.893;$

$F = 2.249 + (3.855 - 1)/117.490 + (2.685 - 1)/117.490/125.893 = 2.273 = 3.567\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3;$

$F = 2.685 + (3.855 - 1)/97.724 + (2.249 - 1)/97.724/125.893 = 2.715 = 4.337\text{dB}$

Subject no. 10

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (37.8 + j\cdot 44.1)\Omega = 0.560 + j\cdot 0.654$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.560 + j\cdot 0.654)] / (1 + 0.560 + j\cdot 0.654)$
 $\Gamma = (0.090) + j\cdot(0.457) \leftrightarrow \text{Re}\Gamma + j\cdot\text{Im}\Gamma$ or $\Gamma = 0.466\angle 78.8^\circ \leftrightarrow |\Gamma|\angle\arg(\Gamma)$

2. a) $P_c = P_{in} - C = 9.5\text{dBm} - 7.60\text{dB} = 1.90\text{dBm}$;

b) $P_{in} = 9.5\text{dBm} = 8.913\text{mW}$; $P_c = 1.90\text{dBm} = 1.549\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 8.913\text{mW} - 1.549\text{mW} = 7.364\text{mW} = 8.671\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.417, y_2 = 1.100, y_1 = 0.459, Z_1 = Z_0/y_1 = 109.0\Omega, Z_2 = Z_0/y_2 = 45.4\Omega$

3. a) $Z = 22.80\Omega + j\cdot(-27.92)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.197 + j\cdot(-0.459) = 0.500\angle -113.3^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.500$; $\varphi = \arg(\Gamma) = -113.3^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 116.6^\circ$; $\text{Im}(y_s) = -1.155$; $\theta_{P1} = 130.9^\circ$ **or** $\theta_{S2} = 176.6^\circ$; $\text{Im}(y_s) = 1.155$; $\theta_{P2} = 49.1^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2\cdot\pi\cdot f_c = 2\cdot\pi\cdot 370\text{MHz} = 2.325\cdot 10^9$ rad/s ; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180, g_2 = 1.6180, g_3 = 2.0000, g_4 = 1.6180, g_5 = 0.6180, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 13.292\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 13.920\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 43.015\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 13.920\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 13.292\text{nH}$;

b) Draw the schematic:

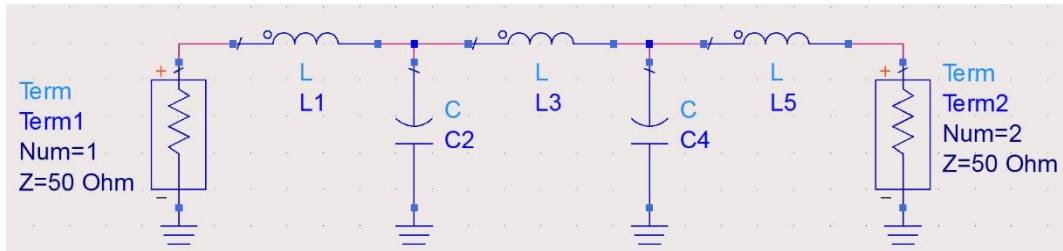

c) In the passband ($f < 370$ MHz) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0$ dB, including at the cutoff frequency $f_1 = 370$ MHz; In the stopband ($f > 370$ MHz) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 740.0$ MHz the attenuation is $L_{As} = 30.107$ dB; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 20.8\text{dB} + 19.2\text{dB} + 16.8\text{dB} = 56.8\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 478,630.1$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$; $F_1 = 3.35\text{dB} = 2.163, G_1 = 20.8\text{dB} = 120.226, F_2 = 4.34\text{dB} = 2.716, G_2 = 19.2\text{dB} = 83.176, F_3 = 5.20\text{dB} = 3.311, G_3 = 16.8\text{dB} = 47.863$;

$F = 2.163 + (2.716 - 1)/120.226 + (3.311 - 1)/120.226/83.176 = 2.177 = 3.379\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$F = 2.716 + (3.311 - 1)/83.176 + (2.163 - 1)/83.176/47.863 = 2.745 = 4.385\text{dB}$

Subject no. 11

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (49.2 - j \cdot 35.9)\Omega = 0.663 - j \cdot 0.484$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.663 - j \cdot 0.484)] / (1 + 0.663 - j \cdot 0.484)$
 $\Gamma = (0.109) + j \cdot (-0.323) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.340 \angle -71.4^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 8.3\text{dBm} - 5.20\text{dB} = 3.10\text{dBm}$;
 b) $P_{in} = 8.3\text{dBm} = 6.761\text{mW}$; $P_c = 3.10\text{dBm} = 2.042\text{mW}$;
 Lossless coupler $P_{th} = P_{in} - P_c = 6.761\text{mW} - 2.042\text{mW} = 4.719\text{mW} = 6.739\text{dBm}$
 c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.550$, $y_2 = 1.197$, $y_1 = 0.658$, $Z_1 = Z_0/y_1 = 76.0\Omega$, $Z_2 = Z_0/y_2 = 41.8\Omega$


3. a) $Z = 50.00\Omega + j \cdot (29.09)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.078 + j \cdot (0.268) = 0.279 \angle 73.8^\circ$;
 b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.
 c) $|\Gamma| = 0.279$; $\varphi = \arg(\Gamma) = 73.8^\circ$; Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 16.2^\circ$; $\text{Im}(y_S) = -0.582$; $\theta_{P1} = 149.8^\circ$ **or** $\theta_{S2} = 90.0^\circ$; $\text{Im}(y_S) = 0.582$; $\theta_{P2} = 30.2^\circ$
 c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 585\text{MHz} = 3.676 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817$, $g_2 = 0.7618$, $g_3 = 4.5381$, $g_4 = 0.7618$, $g_5 = 3.4817$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).

Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 1.563\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 17.856\text{nH}$;
 g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 1.199\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 17.856\text{nH}$;
 g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 1.563\text{pF}$;

b) Draw the schematic:

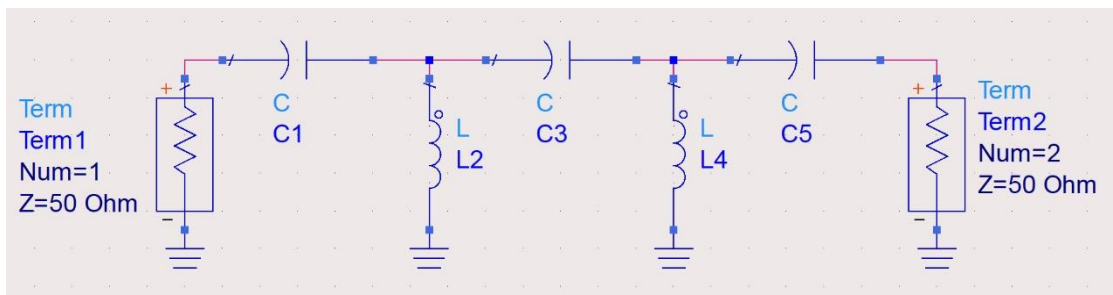

c) In the passband ($f > 585 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 585 \text{ MHz}$; In the stopband ($f < 585 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 292.5 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 18.8\text{dB} + 15.4\text{dB} + 17.9\text{dB} = 52.1\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 162,181.0$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A3, A2 so: $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3$; $F_1 = 3.19\text{dB} = 2.084$, $G_1 = 18.8\text{dB} = 75.858$, $F_2 = 4.57\text{dB} = 2.864$, $G_2 = 15.4\text{dB} = 34.674$, $F_3 = 5.09\text{dB} = 3.228$, $G_3 = 17.9\text{dB} = 61.660$;

$F = 2.084 + (3.228 - 1)/75.858 + (2.864 - 1)/75.858/61.660 = 2.114 = 3.252\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$F = 2.864 + (3.228 - 1)/34.674 + (2.084 - 1)/34.674/61.660 = 2.929 = 4.667\text{dB}$

Subject no. 12

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (42.5 - j \cdot 55.8)\Omega = 0.432 - j \cdot 0.567$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.432 - j \cdot 0.567)] / (1 + 0.432 - j \cdot 0.567)$
 $\Gamma = (0.207) + j \cdot (-0.478) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.521 \angle -66.6^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 8.1\text{dBm} - 6.45\text{dB} = 1.65\text{dBm}$;

b) $P_{in} = 8.1\text{dBm} = 6.457\text{mW}$; $P_c = 1.65\text{dBm} = 1.462\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 6.457\text{mW} - 1.462\text{mW} = 4.994\text{mW} = 6.985\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.476$, $y_2 = 1.137$, $y_1 = 0.541$, $Z_1 = Z_0/y_1 = 92.4 \Omega$, $Z_2 = Z_0/y_2 = 44.0\Omega$

3. a) $Z = 58.00\Omega + j \cdot (-27.76)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.131 + j \cdot (-0.223) = 0.259 \angle -59.5^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.259$; $\varphi = \arg(\Gamma) = -59.5^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 82.3^\circ$; $\text{Im}(y_s) = -0.537$; $\theta_{P1} = 151.8^\circ$ **or** $\theta_{S2} = 157.2^\circ$; $\text{Im}(y_s) = 0.537$; $\theta_{P2} = 28.2^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 300\text{MHz} = 1.885 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180$, $g_2 = 1.6180$, $g_3 = 2.0000$, $g_4 = 1.6180$, $g_5 = 0.6180$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 16.393\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 17.168\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 53.052\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 17.168\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 16.393\text{nH}$;

b) Draw the schematic:

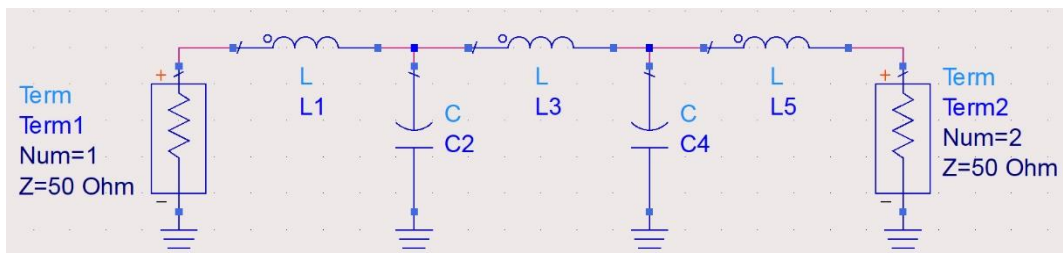

c) In the passband ($f < 300 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 300 \text{ MHz}$; In the stopband ($f > 300 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 600.0 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 16.2\text{dB} + 23.1\text{dB} + 22.0\text{dB} = 61.3\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 1,348,962.9$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2-1)/G_1 + (F_3-1)/G_1/G_2$ but the connection order is A2, A1, A3 so: $F = F_2 + (F_1-1)/G_2 + (F_3-1)/G_2/G_1$; $F_1 = 3.16\text{dB} = 2.070$, $G_1 = 16.2\text{dB} = 41.687$, $F_2 = 4.46\text{dB} = 2.793$, $G_2 = 23.1\text{dB} = 204.174$, $F_3 = 5.80\text{dB} = 3.802$, $G_3 = 22.0\text{dB} = 158.489$;

$F = 2.793 + (2.070-1)/204.174 + (3.802-1)/204.174/41.687 = 2.798 = 4.469\text{dB}$

c) If the order is A1, A2, A3 the gain remains the same but $F = F_1 + (F_2-1)/G_1 + (F_3-1)/G_1/G_2$;

$F = 2.070 + (2.793-1)/41.687 + (3.802-1)/41.687/204.174 = 2.113 = 3.250\text{dB}$

Subject no. 13

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (63.3 - j \cdot 52.3)\Omega = 0.469 - j \cdot 0.388$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.469 - j \cdot 0.388)] / (1 + 0.469 - j \cdot 0.388)$
 $\Gamma = (0.272) + j \cdot (-0.336) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.432 \angle -51.0^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 7.3\text{dBm} - 6.55\text{dB} = 0.75\text{dBm}$;

b) $P_{in} = 7.3\text{dBm} = 5.370\text{mW}$; $P_c = 0.75\text{dBm} = 1.189\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 5.370\text{mW} - 1.189\text{mW} = 4.182\text{mW} = 6.214\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.470$, $y_2 = 1.133$, $y_1 = 0.533$, $Z_1 = Z_0/y_1 = 93.8 \Omega$, $Z_2 = Z_0/y_2 = 44.1\Omega$

3. a) $Z = 23.30\Omega + j \cdot (-15.03)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.309 + j \cdot (-0.269) = 0.410 \angle -139.0^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.410$; $\varphi = \arg(\Gamma) = -139.0^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 126.6^\circ$; $\text{Im}(y_s) = -0.898$; $\theta_{P1} = 138.1^\circ$ **or** $\theta_{S2} = 12.4^\circ$; $\text{Im}(y_s) = 0.898$; $\theta_{P2} = 41.9^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 585\text{MHz} = 3.676 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817$, $g_2 = 0.7618$, $g_3 = 4.5381$, $g_4 = 0.7618$, $g_5 = 3.4817$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 1.563\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 17.856\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 1.199\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 17.856\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 1.563\text{pF}$;

b) Draw the schematic:

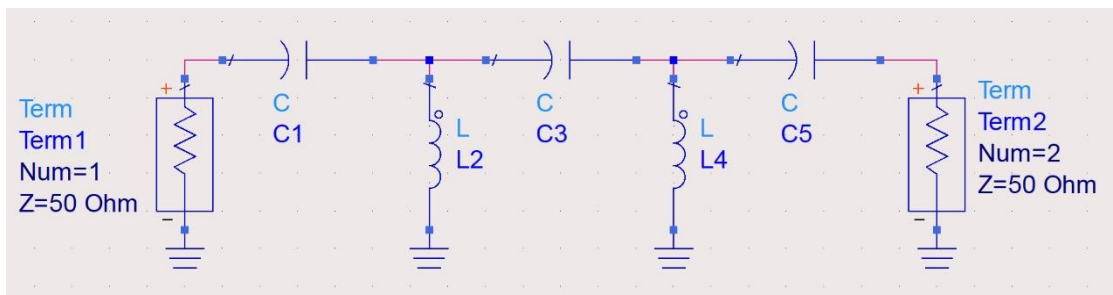

c) In the passband ($f > 585 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 585 \text{ MHz}$; In the stopband ($f < 585 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 292.5 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 15.2\text{dB} + 23.3\text{dB} + 23.1\text{dB} = 61.6\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 1,445,439.8$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A3, A2 so: $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3$; $F_1 = 3.52\text{dB} = 2.249$, $G_1 = 15.2\text{dB} = 33.113$, $F_2 = 4.37\text{dB} = 2.735$, $G_2 = 23.3\text{dB} = 213.796$, $F_3 = 5.49\text{dB} = 3.540$, $G_3 = 23.1\text{dB} = 204.174$;

$F = 2.249 + (3.540 - 1)/33.113 + (2.735 - 1)/33.113/204.174 = 2.326 = 3.666\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$F = 2.735 + (3.540 - 1)/213.796 + (2.249 - 1)/213.796/204.174 = 2.747 = 4.389\text{dB}$

Subject no. 14

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (61.1 - j \cdot 60.9)\Omega = 0.411 - j \cdot 0.409$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.411 - j \cdot 0.409)] / (1 + 0.411 - j \cdot 0.409)$
 $\Gamma = (0.308) + j \cdot (-0.379) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.489 \angle -50.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 7.0\text{dBm} - 5.60\text{dB} = 1.40\text{dBm}$;

b) $P_{in} = 7.0\text{dBm} = 5.012\text{mW}$; $P_c = 1.40\text{dBm} = 1.380\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 5.012\text{mW} - 1.380\text{mW} = 3.631\text{mW} = 5.601\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.525, y_2 = 1.175, y_1 = 0.617, Z_1 = Z_0/y_1 = 81.1 \Omega, Z_2 = Z_0/y_2 = 42.6\Omega$

3. a) $Z = 15.07\Omega + j \cdot (25.14)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.337 + j \cdot (0.517) = 0.617 \angle 123.1^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.617$; $\varphi = \arg(\Gamma) = 123.1^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 2.5^\circ$; $\text{Im}(y_s) = -1.568$; $\theta_{P1} = 122.5^\circ$ **or** $\theta_{S2} = 54.4^\circ$; $\text{Im}(y_s) = 1.568$; $\theta_{P2} = 57.5^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 580\text{MHz} = 3.644 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 47.770\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 4.181\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 62.264\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 4.181\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 47.770\text{nH}$;

b) Draw the schematic:

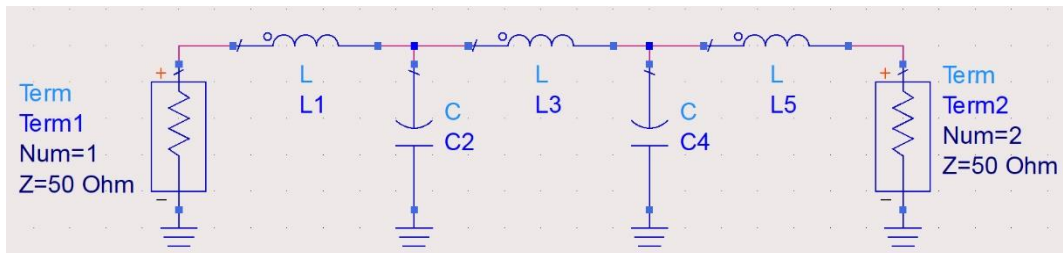

c) In the passband ($f < 580 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 580 \text{ MHz}$; In the stopband ($f > 580 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 1160.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 15.4\text{dB} + 21.5\text{dB} + 21.3\text{dB} = 58.2\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 660,693.4$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A3, A1, A2 so: $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1$; $F_1 = 3.44\text{dB} = 2.208, G_1 = 15.4\text{dB} = 34.674, F_2 = 4.13\text{dB} = 2.588, G_2 = 21.5\text{dB} = 141.254, F_3 = 5.60\text{dB} = 3.631, G_3 = 21.3\text{dB} = 134.896$;

$F = 3.631 + (2.208 - 1)/134.896 + (2.588 - 1)/134.896/34.674 = 3.640 = 5.611\text{dB}$

c) If the order is A3, A2, A1 the gain remains the same but $F = F_3 + (F_2 - 1)/G_3 + (F_1 - 1)/G_3/G_2$;

$F = 3.631 + (2.588 - 1)/134.896 + (2.208 - 1)/134.896/141.254 = 3.643 = 5.614\text{dB}$

Subject no. 15

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (58.5 - j \cdot 51.8)\Omega = 0.479 - j \cdot 0.424;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.479 - j \cdot 0.424)] / (1 + 0.479 - j \cdot 0.424)$$

$$\Gamma = (0.249) + j \cdot (-0.358) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.437 \angle -55.2^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 7.6\text{dBm} - 5.25\text{dB} = 2.35\text{dBm};$

b) $P_{in} = 7.6\text{dBm} = 5.754\text{mW}; P_c = 2.35\text{dBm} = 1.718\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 5.754\text{mW} - 1.718\text{mW} = 4.036\text{mW} = 6.060\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.546, y_2 = 1.194, y_1 = 0.652, Z_1 = Z_0/y_1 = 76.6 \Omega, Z_2 = Z_0/y_2 = 41.9\Omega$

3. a) $Z = 27.00\Omega + j \cdot (-35.77)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.068 + j \cdot (-0.496) = 0.501 \angle -97.8^\circ ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.501; \varphi = \arg(\Gamma) = -97.8^\circ; \text{Complex calculus from L8/2024, S114}\div 115, \text{ all lines have } Z_0 = 50\Omega$
 $\theta_{S1} = 108.9^\circ ; \text{Im}(y_s) = -1.158 ; \theta_{P1} = 130.8^\circ \text{ or } \theta_{S2} = 168.9^\circ ; \text{Im}(y_s) = 1.158 ; \theta_{P2} = 49.2^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 305\text{MHz} = 1.916 \cdot 10^9 \text{ rad/s} ; R_0 = 50\Omega. \text{ Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: } g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1 \text{ (works directly on } 50\Omega \text{ load, no } \lambda/4 \text{ transformer needed).}$


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 2.997\text{pF}; g_2$: shunt inductor $L_2 = R_0 / g_2 / \omega_c = 34.249\text{nH};$

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 2.300\text{pF}; g_4$: shunt inductor $L_4 = R_0 / g_4 / \omega_c = 34.249\text{nH};$

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 2.997\text{pF};$

b) Draw the schematic:

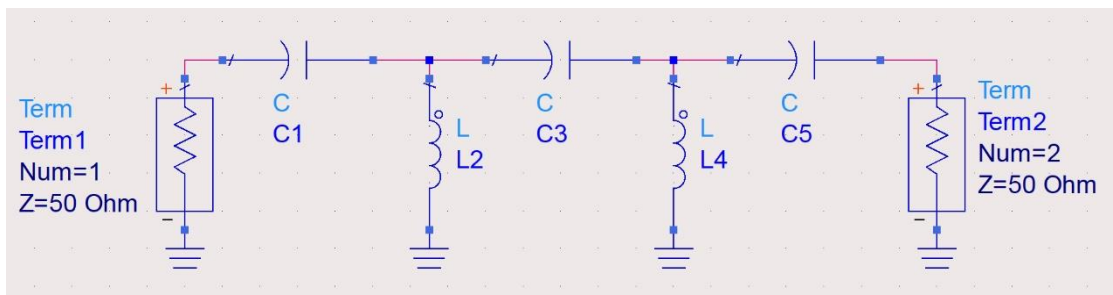

c) In the passband ($f > 305 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 305 \text{ MHz}$; In the stopband ($f < 305 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 152.5 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 24.2\text{dB} + 19.7\text{dB} + 21.0\text{dB} = 64.9\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 3,090,295.4$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A3, A1 so: $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3; F_1 = 3.58\text{dB} = 2.280, G_1 = 24.2\text{dB} = 263.027, F_2 = 4.54\text{dB} = 2.844, G_2 = 19.7\text{dB} = 93.325, F_3 = 5.82\text{dB} = 3.819, G_3 = 21.0\text{dB} = 125.893;$

$$F = 2.844 + (3.819 - 1)/93.325 + (2.280 - 1)/93.325/125.893 = 2.875 = 4.586\text{dB}$$

c) If the order is A1, A2, A3 the gain remains the same but $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2;$

$$F = 2.280 + (2.844 - 1)/263.027 + (3.819 - 1)/263.027/93.325 = 2.287 = 3.594\text{dB}$$

Subject no. 16

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (31.5 + j \cdot 41.3)\Omega = 0.584 + j \cdot 0.765$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.584 + j \cdot 0.765)] / (1 + 0.584 + j \cdot 0.765)$
 $\Gamma = (0.024) + j \cdot (0.495) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.495 \angle 87.3^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 9.5\text{dBm} - 7.55\text{dB} = 1.95\text{dBm}$;

b) $P_{in} = 9.5\text{dBm} = 8.913\text{mW}$; $P_c = 1.95\text{dBm} = 1.567\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 8.913\text{mW} - 1.567\text{mW} = 7.346\text{mW} = 8.660\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.419$, $y_2 = 1.101$, $y_1 = 0.462$, $Z_1 = Z_0/y_1 = 108.3 \Omega$, $Z_2 = Z_0/y_2 = 45.4\Omega$

3. a) $Z = 12.12\Omega + j \cdot (22.53)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.423 + j \cdot (0.516) = 0.667 \angle 129.3^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.667$; $\varphi = \arg(\Gamma) = 129.3^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 1.3^\circ$; $\text{Im}(y_S) = -1.790$; $\theta_{P1} = 119.2^\circ$ **or** $\theta_{S2} = 49.4^\circ$; $\text{Im}(y_S) = 1.790$; $\theta_{P2} = 60.8^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 500\text{MHz} = 3.142 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058$, $g_2 = 1.2296$, $g_3 = 2.5408$, $g_4 = 1.2296$, $g_5 = 1.7058$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 27.149\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 7.828\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 40.438\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 7.828\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 27.149\text{nH}$;

b) Draw the schematic:

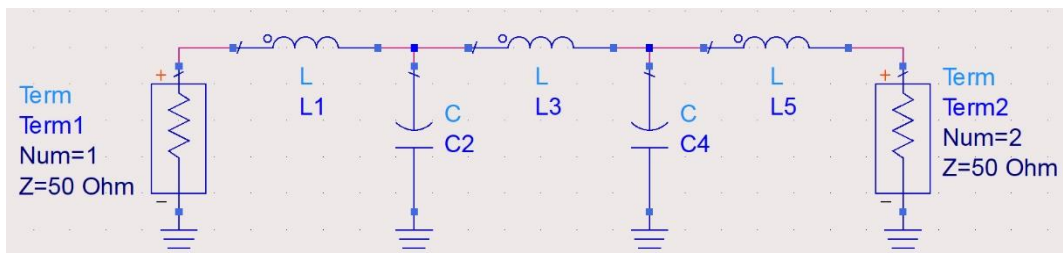

c) In the passband ($f < 500 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 500 \text{ MHz}$; In the stopband ($f > 500 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 1000.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 18.3\text{dB} + 18.7\text{dB} + 24.2\text{dB} = 61.2\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 1,318,256.7$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$; $F_1 = 3.73\text{dB} = 2.360$, $G_1 = 18.3\text{dB} = 67.608$, $F_2 = 4.31\text{dB} = 2.698$, $G_2 = 18.7\text{dB} = 74.131$, $F_3 = 5.33\text{dB} = 3.412$, $G_3 = 24.2\text{dB} = 263.027$;

$F = 2.360 + (2.698 - 1)/67.608 + (3.412 - 1)/67.608/74.131 = 2.386 = 3.777\text{dB}$

c) If the order is A1, A3, A2 the gain remains the same but $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3$;

$F = 2.360 + (3.412 - 1)/67.608 + (2.698 - 1)/67.608/263.027 = 2.396 = 3.795\text{dB}$

Subject no. 17

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (63.9 + j\cdot 40.8)\Omega = 0.556 + j\cdot 0.355$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.556 + j\cdot 0.355)] / (1 + 0.556 + j\cdot 0.355)$
 $\Gamma = (0.222) + j\cdot(0.279) \leftrightarrow \text{Re}\Gamma + j\cdot\text{Im}\Gamma$ or $\Gamma = 0.356\angle 51.5^\circ \leftrightarrow |\Gamma|\angle\arg(\Gamma)$

2. a) $P_c = P_{in} - C = 4.4\text{dBm} - 5.45\text{dB} = -1.05\text{dBm}$;

b) $P_{in} = 4.4\text{dBm} = 2.754\text{mW}$; $P_c = -1.05\text{dBm} = 0.785\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 2.754\text{mW} - 0.785\text{mW} = 1.969\text{mW} = 2.942\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.534$, $y_2 = 1.183$, $y_1 = 0.632$, $Z_1 = Z_0/y_1 = 79.2\Omega$, $Z_2 = Z_0/y_2 = 42.3\Omega$

3. a) $Z = 28.89\Omega + j\cdot(-18.70)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.200 + j\cdot(-0.285) = 0.348\angle -125.1^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.348$; $\varphi = \arg(\Gamma) = -125.1^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 117.7^\circ$; $\text{Im}(y_S) = -0.742$; $\theta_{P1} = 143.4^\circ$ **or** $\theta_{S2} = 7.4^\circ$; $\text{Im}(y_S) = 0.742$; $\theta_{P2} = 36.6^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2\cdot\pi\cdot f_c = 2\cdot\pi\cdot 595\text{MHz} = 3.738\cdot 10^9$ rad/s ; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817$, $g_2 = 0.7618$, $g_3 = 4.5381$, $g_4 = 0.7618$, $g_5 = 3.4817$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 46.566\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 4.075\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 60.694\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 4.075\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 46.566\text{nH}$;

b) Draw the schematic:

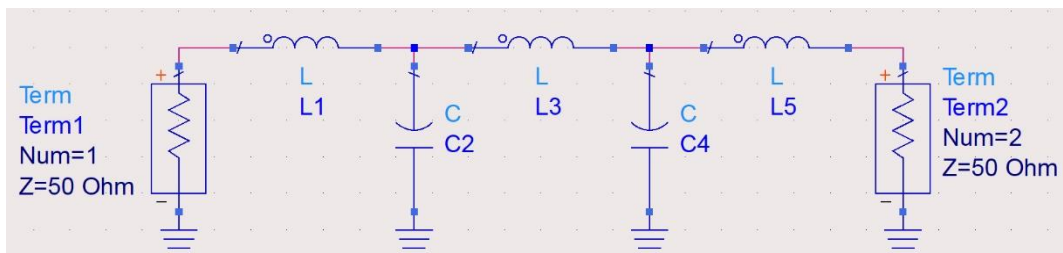

c) In the passband ($f < 595$ MHz) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0$ dB, including at the cutoff frequency $f_1 = 595$ MHz; In the stopband ($f > 595$ MHz) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 1190.0$ MHz the attenuation is $L_{As} = 51.174$ dB; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 24.3\text{dB} + 20.5\text{dB} + 20.0\text{dB} = 64.8\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 3,019,951.7$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2-1)/G_1 + (F_3-1)/G_1/G_2$ but the connection order is A2, A3, A1 so: $F = F_2 + (F_3-1)/G_2 + (F_1-1)/G_2/G_3$; $F_1 = 3.33\text{dB} = 2.153$, $G_1 = 24.3\text{dB} = 269.153$, $F_2 = 4.39\text{dB} = 2.748$, $G_2 = 20.5\text{dB} = 112.202$, $F_3 = 5.90\text{dB} = 3.890$, $G_3 = 20.0\text{dB} = 100.000$;

$F = 2.748 + (3.890-1)/112.202 + (2.153-1)/112.202/100.000 = 2.774 = 4.431\text{dB}$

c) If the order is A3, A1, A2 the gain remains the same but $F = F_3 + (F_1-1)/G_3 + (F_2-1)/G_3/G_1$;

$F = 3.890 + (2.153-1)/100.000 + (2.748-1)/100.000/269.153 = 3.902 = 5.913\text{dB}$

Subject no. 18

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (64.6 + j \cdot 35.5)\Omega = 0.594 + j \cdot 0.327;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.594 + j \cdot 0.327)] / (1 + 0.594 + j \cdot 0.327)$$

$$\Gamma = (0.204) + j \cdot (0.247) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.320 \angle 50.4^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 4.1\text{dBm} - 5.00\text{dB} = -0.90\text{dBm};$

b) $P_{in} = 4.1\text{dBm} = 2.570\text{mW}; P_c = -0.90\text{dBm} = 0.813\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 2.570\text{mW} - 0.813\text{mW} = 1.758\text{mW} = 2.449\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.562, y_2 = 1.209, y_1 = 0.680, Z_1 = Z_0/y_1 = 73.5 \Omega, Z_2 = Z_0/y_2 = 41.3\Omega$

3. a) $Z = 26.58\Omega + j \cdot (15.82)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.252 + j \cdot (0.259) = 0.361 \angle 134.3^\circ ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.361; \varphi = \arg(\Gamma) = 134.3^\circ; \text{Complex calculus from L8/2024, S114}\div\text{115, all lines have } Z_0 = 50\Omega$
 $\theta_{S1} = 168.5^\circ ; \text{Im}(y_S) = -0.775 ; \theta_{P1} = 142.2^\circ \text{ or } \theta_{S2} = 57.3^\circ ; \text{Im}(y_S) = 0.775 ; \theta_{P2} = 37.8^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 345\text{MHz} = 2.168 \cdot 10^9 \text{ rad/s} ; R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180, g_2 = 1.6180, g_3 = 2.0000, g_4 = 1.6180, g_5 = 0.6180, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 14.255\text{nH}; g_2$: shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 14.928\text{pF};$

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 46.132\text{nH}; g_4$: shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 14.928\text{pF};$

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 14.255\text{nH};$

b) Draw the schematic:

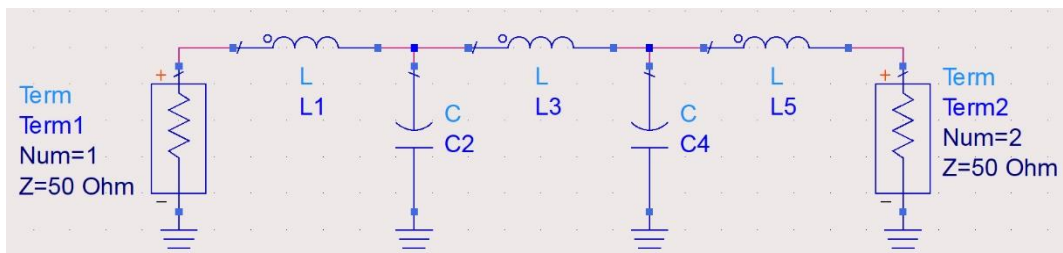

c) In the passband ($f < 345 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 345 \text{ MHz}$; In the stopband ($f > 345 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 690.0 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 21.4\text{dB} + 19.1\text{dB} + 21.6\text{dB} = 62.1\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 1,621,810.1$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A3, A2 so: $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3; F_1 = 3.46\text{dB} = 2.218, G_1 = 21.4\text{dB} = 138.038, F_2 = 4.07\text{dB} = 2.553, G_2 = 19.1\text{dB} = 81.283, F_3 = 5.39\text{dB} = 3.459, G_3 = 21.6\text{dB} = 144.544;$

$F = 2.218 + (3.459 - 1)/138.038 + (2.553 - 1)/138.038/144.544 = 2.236 = 3.495\text{dB}$

c) If the order is A3, A1, A2 the gain remains the same but $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1;$

$F = 3.459 + (2.218 - 1)/144.544 + (2.553 - 1)/144.544/138.038 = 3.468 = 5.401\text{dB}$

Subject no. 19

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (38.2 - j \cdot 33.8)\Omega = 0.734 - j \cdot 0.650$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.734 - j \cdot 0.650)] / (1 + 0.734 - j \cdot 0.650)$
 $\Gamma = (0.011) + j \cdot (-0.379) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.379 \angle -88.3^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 6.3\text{dBm} - 4.25\text{dB} = 2.05\text{dBm}$;

b) $P_{in} = 6.3\text{dBm} = 4.266\text{mW}$; $P_c = 2.05\text{dBm} = 1.603\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 4.266\text{mW} - 1.603\text{mW} = 2.663\text{mW} = 4.253\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.613$, $y_2 = 1.266$, $y_1 = 0.776$, $Z_1 = Z_0/y_1 = 64.4\Omega$, $Z_2 = Z_0/y_2 = 39.5\Omega$

3. a) $Z = 33.33\Omega + j \cdot (-36.82)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.004 + j \cdot (-0.444) = 0.444 \angle -90.5^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.444$; $\varphi = \arg(\Gamma) = -90.5^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 103.4^\circ$; $\text{Im}(y_s) = -0.990$; $\theta_{P1} = 135.3^\circ$ **or** $\theta_{S2} = 167.1^\circ$; $\text{Im}(y_s) = 0.990$; $\theta_{P2} = 44.7^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 565\text{MHz} = 3.550 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058$, $g_2 = 1.2296$, $g_3 = 2.5408$, $g_4 = 1.2296$, $g_5 = 1.7058$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 3.303\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 11.455\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 2.217\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 11.455\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 3.303\text{pF}$;

b) Draw the schematic:

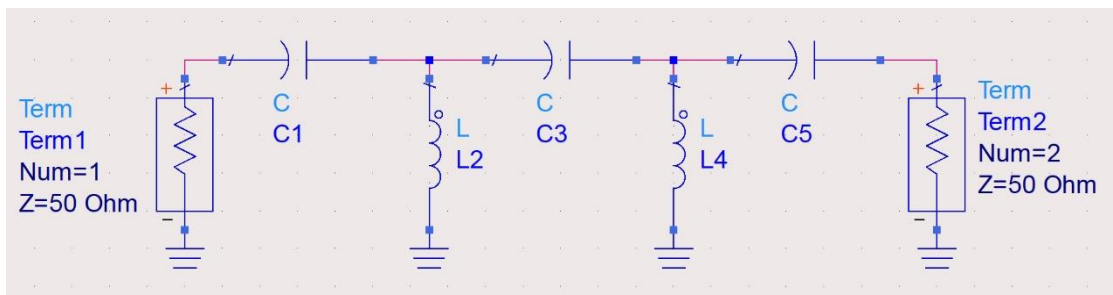

c) In the passband ($f > 565 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 565 \text{ MHz}$; In the stopband ($f < 565 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 282.5 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 20.7\text{dB} + 24.1\text{dB} + 18.5\text{dB} = 63.3\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 2,137,962.1$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$; $F_1 = 3.59\text{dB} = 2.286$, $G_1 = 20.7\text{dB} = 117.490$, $F_2 = 4.41\text{dB} = 2.761$, $G_2 = 24.1\text{dB} = 257.040$, $F_3 = 5.57\text{dB} = 3.606$, $G_3 = 18.5\text{dB} = 70.795$;

$F = 2.286 + (2.761 - 1)/117.490 + (3.606 - 1)/117.490/257.040 = 2.301 = 3.619\text{dB}$

c) If the order is A3, A1, A2 the gain remains the same but $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1$;

$F = 3.606 + (2.286 - 1)/70.795 + (2.761 - 1)/70.795/117.490 = 3.624 = 5.592\text{dB}$

Subject no. 20

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (52.1 + j \cdot 56.6)\Omega = 0.440 + j \cdot 0.478;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.440 + j \cdot 0.478)] / (1 + 0.440 + j \cdot 0.478)$$

$$\Gamma = (0.251) + j \cdot (0.415) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.485 \angle 58.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

$$2. a) P_c = P_{in} - C = 4.2\text{dBm} - 4.05\text{dB} = 0.15\text{dBm};$$

$$b) P_{in} = 4.2\text{dBm} = 2.630\text{mW}; P_c = 0.15\text{dBm} = 1.035\text{mW};$$

$$\text{Lossless coupler } P_{th} = P_{in} - P_c = 2.630\text{mW} - 1.035\text{mW} = 1.595\text{mW} = 2.028\text{dBm}$$

$$c) L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.627, y_2 = 1.284, y_1 = 0.806, Z_1 = Z_0/y_1 = 62.1 \Omega, Z_2 = Z_0/y_2 = 38.9\Omega$$

$$3. a) Z = 37.46\Omega + j \cdot (34.91)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = 0.014 + j \cdot (0.394) = 0.394 \angle 88.0^\circ ;$$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

$$c) |\Gamma| = 0.394; \varphi = \arg(\Gamma) = 88.0^\circ; \text{Complex calculus from L8/2024, S114-115, all lines have } Z_0 = 50\Omega$$

$$\theta_{S1} = 12.6^\circ; \text{Im}(y_S) = -0.857; \theta_{P1} = 139.4^\circ \text{ or } \theta_{S2} = 79.4^\circ; \text{Im}(y_S) = 0.857; \theta_{P2} = 40.6^\circ$$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 595\text{MHz} = 3.738 \cdot 10^9 \text{ rad/s}; R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

$$g_1 : \text{series capacitor } C_1 = 1 / R_0 / g_1 / \omega_c = 1.537\text{pF}; g_2 : \text{shunt inductor } L_2 = R_0 / g_2 / \omega_c = 17.556\text{nH};$$

$$g_3 : \text{series capacitor } C_3 = 1 / R_0 / g_3 / \omega_c = 1.179\text{pF}; g_4 : \text{shunt inductor } L_4 = R_0 / g_4 / \omega_c = 17.556\text{nH};$$

$$g_5 : \text{series capacitor } C_5 = 1 / R_0 / g_5 / \omega_c = 1.537\text{pF};$$

b) Draw the schematic:

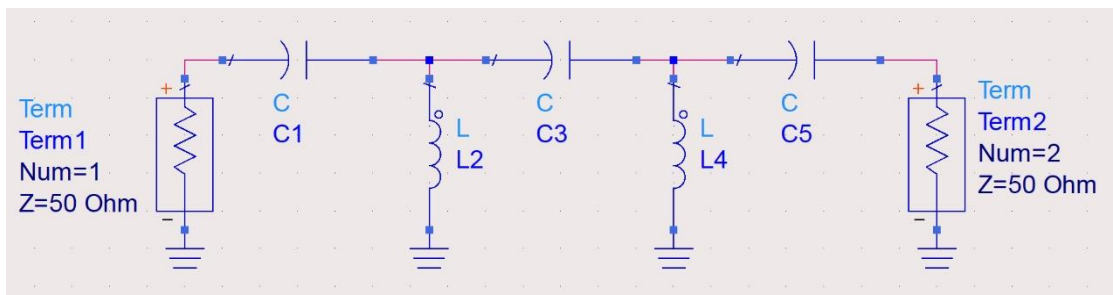

c) In the passband ($f > 595 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 595 \text{ MHz}$; In the stopband ($f < 595 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 297.5 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 16.8\text{dB} + 22.2\text{dB} + 19.5\text{dB} = 58.5\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 707,945.8$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A3, A1, A2 so: $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1$; $F_1 = 3.79\text{dB} = 2.393, G_1 = 16.8\text{dB} = 47.863, F_2 = 4.56\text{dB} = 2.858, G_2 = 22.2\text{dB} = 165.959, F_3 = 5.44\text{dB} = 3.499, G_3 = 19.5\text{dB} = 89.125$;

$$F = 3.499 + (2.393 - 1)/89.125 + (2.858 - 1)/89.125/47.863 = 3.516 = 5.460\text{dB}$$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$$F = 2.858 + (3.499 - 1)/165.959 + (2.393 - 1)/165.959/89.125 = 2.873 = 4.583\text{dB}$$

Subject no. 21

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (46.9 + j \cdot 49.8)\Omega = 0.501 + j \cdot 0.532$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.501 + j \cdot 0.532)] / (1 + 0.501 + j \cdot 0.532)$
 $\Gamma = (0.184) + j \cdot (0.420) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.458 \angle 66.4^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 7.7\text{dBm} - 4.00\text{dB} = 3.70\text{dBm}$;

b) $P_{in} = 7.7\text{dBm} = 5.888\text{mW}$; $P_c = 3.70\text{dBm} = 2.344\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 5.888\text{mW} - 2.344\text{mW} = 3.544\text{mW} = 5.495\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.631$, $y_2 = 1.289$, $y_1 = 0.813$, $Z_1 = Z_0/y_1 = 61.5 \Omega$, $Z_2 = Z_0/y_2 = 38.8\Omega$

3. a) $Z = 14.73\Omega + j \cdot (-13.98)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.476 + j \cdot (-0.319) = 0.573 \angle -146.2^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.573$; $\varphi = \arg(\Gamma) = -146.2^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 135.6^\circ$; $\text{Im}(y_s) = -1.398$; $\theta_{P1} = 125.6^\circ$ **or** $\theta_{S2} = 10.6^\circ$; $\text{Im}(y_s) = 1.398$; $\theta_{P2} = 54.4^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 575\text{MHz} = 3.613 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180$, $g_2 = 1.6180$, $g_3 = 2.0000$, $g_4 = 1.6180$, $g_5 = 0.6180$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 8.958\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 8.553\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 2.768\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 8.553\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 8.958\text{pF}$;

b) Draw the schematic:

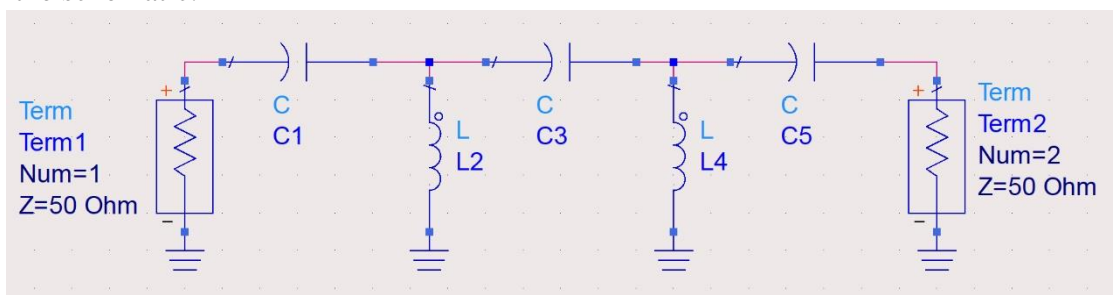

c) In the passband ($f > 575 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 575 \text{ MHz}$; In the stopband ($f < 575 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 287.5 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 20.9\text{dB} + 18.7\text{dB} + 19.8\text{dB} = 59.4\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 870,963.6$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A3, A1 so: $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$; $F_1 = 3.68\text{dB} = 2.333$, $G_1 = 20.9\text{dB} = 123.027$, $F_2 = 4.24\text{dB} = 2.655$, $G_2 = 18.7\text{dB} = 74.131$, $F_3 = 5.98\text{dB} = 3.963$, $G_3 = 19.8\text{dB} = 95.499$;

$F = 2.655 + (3.963 - 1)/74.131 + (2.333 - 1)/74.131/95.499 = 2.695 = 4.305\text{dB}$

c) If the order is A3, A1, A2 the gain remains the same but $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1$;

$F = 3.963 + (2.333 - 1)/95.499 + (2.655 - 1)/95.499/123.027 = 3.977 = 5.995\text{dB}$

Subject no. 22

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (48.4 + j \cdot 35.1)\Omega = 0.677 + j \cdot 0.491;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.677 + j \cdot 0.491)] / (1 + 0.677 + j \cdot 0.491)$$

$$\Gamma = (0.098) + j \cdot (0.322) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.336 \angle 73.0^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 1.7\text{dBm} - 5.95\text{dB} = -4.25\text{dBm}$;

b) $P_{in} = 1.7\text{dBm} = 1.479\text{mW}$; $P_c = -4.25\text{dBm} = 0.376\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 1.479\text{mW} - 0.376\text{mW} = 1.103\text{mW} = 0.427\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.504, y_2 = 1.158, y_1 = 0.584, Z_1 = Z_0/y_1 = 85.7 \Omega, Z_2 = Z_0/y_2 = 43.2\Omega$

3. a) $Z = 31.00\Omega + j \cdot (-73.09)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.320 + j \cdot (-0.614) = 0.692 \angle -62.5^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.692$; $\varphi = \arg(\Gamma) = -62.5^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 98.2^\circ$; $\text{Im}(y_s) = -1.918$; $\theta_{P1} = 117.5^\circ$ **or** $\theta_{S2} = 144.4^\circ$; $\text{Im}(y_s) = 1.918$; $\theta_{P2} = 62.5^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 500\text{MHz} = 3.142 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 55.413\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 4.850\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 72.226\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 4.850\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 55.413\text{nH}$;

b) Draw the schematic:

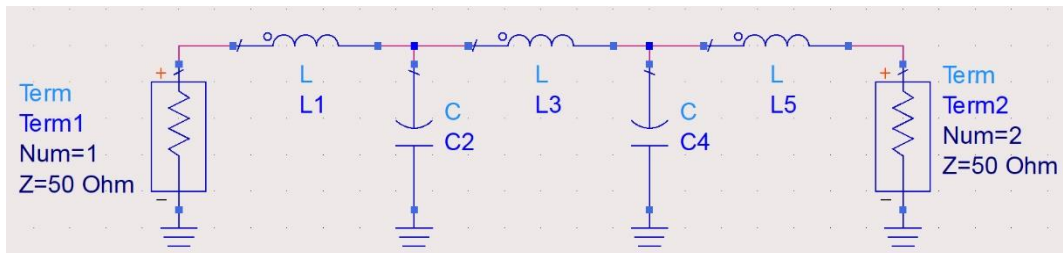

c) In the passband ($f < 500 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 500 \text{ MHz}$; In the stopband ($f > 500 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 1000.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 24.9\text{dB} + 15.7\text{dB} + 16.8\text{dB} = 57.4\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 549,540.9$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A1, A3 so: $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1$; $F_1 = 3.97\text{dB} = 2.495, G_1 = 24.9\text{dB} = 309.030, F_2 = 4.95\text{dB} = 3.126, G_2 = 15.7\text{dB} = 37.154, F_3 = 5.84\text{dB} = 3.837, G_3 = 16.8\text{dB} = 47.863$;

$$F = 3.126 + (2.495 - 1)/37.154 + (3.837 - 1)/37.154/309.030 = 3.167 = 5.006\text{dB}$$

c) If the order is A3, A1, A2 the gain remains the same but $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1$;

$$F = 3.837 + (2.495 - 1)/47.863 + (3.126 - 1)/47.863/309.030 = 3.868 = 5.875\text{dB}$$

Subject no. 23

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (33.4 + j \cdot 31.0)\Omega = 0.804 + j \cdot 0.746$;

$\Gamma = (1 - y) / (1 + y) = [1 - (0.804 + j \cdot 0.746)] / (1 + 0.804 + j \cdot 0.746)$

$\Gamma = (-0.053) + j \cdot (0.392) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.395 \angle 97.8^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 9.8\text{dBm} - 5.35\text{dB} = 4.45\text{dBm}$;

b) $P_{in} = 9.8\text{dBm} = 9.550\text{mW}$; $P_c = 4.45\text{dBm} = 2.786\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 9.550\text{mW} - 2.786\text{mW} = 6.764\text{mW} = 8.302\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.540, y_2 = 1.188, y_1 = 0.642, Z_1 = Z_0/y_1 = 77.9 \Omega, Z_2 = Z_0/y_2 = 42.1\Omega$

3. a) $Z = 69.00\Omega + j \cdot (31.10)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.213 + j \cdot (0.206) = 0.296 \angle 43.9^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.296$; $\varphi = \arg(\Gamma) = 43.9^\circ$; Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 31.7^\circ$; $\text{Im}(y_s) = -0.621$; $\theta_{P1} = 148.2^\circ$ **or** $\theta_{S2} = 104.4^\circ$; $\text{Im}(y_s) = 0.621$; $\theta_{P2} = 31.8^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 335\text{MHz} = 2.105 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 40.520\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 11.683\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 60.355\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 11.683\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 40.520\text{nH}$;

b) Draw the schematic:

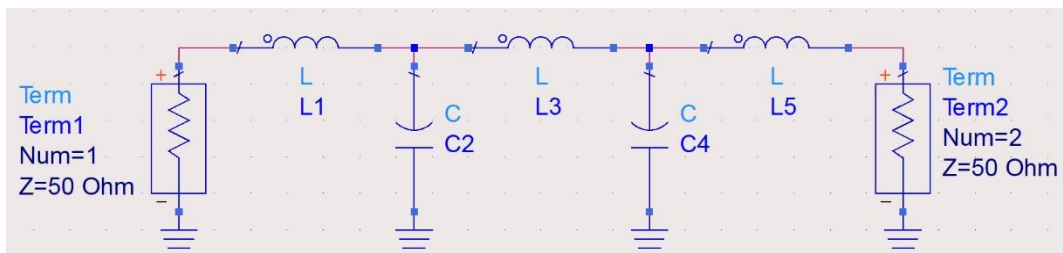

c) In the passband ($f < 335 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 335 \text{ MHz}$; In the stopband ($f > 335 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 670.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 19.2\text{dB} + 19.2\text{dB} + 21.3\text{dB} = 59.7\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 933,254.3$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A1, A3 so: $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1$; $F_1 = 3.32\text{dB} = 2.148, G_1 = 19.2\text{dB} = 83.176, F_2 = 4.63\text{dB} = 2.904, G_2 = 19.2\text{dB} = 83.176, F_3 = 5.94\text{dB} = 3.926, G_3 = 21.3\text{dB} = 134.896$;

$F = 2.904 + (2.148 - 1)/83.176 + (3.926 - 1)/83.176/83.176 = 2.918 = 4.651\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$F = 2.904 + (3.926 - 1)/83.176 + (2.148 - 1)/83.176/134.896 = 2.939 = 4.682\text{dB}$

Subject no. 24

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (36.1 - j \cdot 64.3)\Omega = 0.332 - j \cdot 0.591;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.332 - j \cdot 0.591)] / (1 + 0.332 - j \cdot 0.591)$$

$$\Gamma = (0.254) + j \cdot (-0.557) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.612 \angle -65.4^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

$$2. a) P_c = P_{in} - C = 7.5\text{dBm} - 5.40\text{dB} = 2.10\text{dBm};$$

$$b) P_{in} = 7.5\text{dBm} = 5.623\text{mW}; P_c = 2.10\text{dBm} = 1.622\text{mW};$$

$$\text{Lossless coupler } P_{th} = P_{in} - P_c = 5.623\text{mW} - 1.622\text{mW} = 4.002\text{mW} = 6.022\text{dBm}$$

$$c) L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.537, y_2 = 1.185, y_1 = 0.637, Z_1 = Z_0/y_1 = 78.5 \Omega, Z_2 = Z_0/y_2 = 42.2\Omega$$

$$3. a) Z = 26.97\Omega + j \cdot (11.64)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.270 + j \cdot (0.192) = 0.331 \angle 144.6^\circ;$$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

$$c) |\Gamma| = 0.331; \varphi = \arg(\Gamma) = 144.6^\circ; \text{Complex calculus from L8/2024, S114}\div\text{115, all lines have } Z_0 = 50\Omega$$

$$\theta_{S1} = 162.4^\circ; \text{Im}(y_S) = -0.703; \theta_{P1} = 144.9^\circ \text{ or } \theta_{S2} = 53.0^\circ; \text{Im}(y_S) = 0.703; \theta_{P2} = 35.1^\circ$$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 315\text{MHz} = 1.979 \cdot 10^9 \text{ rad/s}; R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180, g_2 = 1.6180, g_3 = 2.0000, g_4 = 1.6180, g_5 = 0.6180, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

$$g_1 : \text{series inductor } L_1 = g_1 \cdot R_0 / \omega_c = 15.612\text{nH}; g_2 : \text{shunt capacitor } C_2 = g_2 / R_0 / \omega_c = 16.350\text{pF};$$

$$g_3 : \text{series inductor } L_3 = g_3 \cdot R_0 / \omega_c = 50.525\text{nH}; g_4 : \text{shunt capacitor } C_4 = g_4 / R_0 / \omega_c = 16.350\text{pF};$$

$$g_5 : \text{series inductor } L_5 = g_5 \cdot R_0 / \omega_c = 15.612\text{nH};$$

b) Draw the schematic:

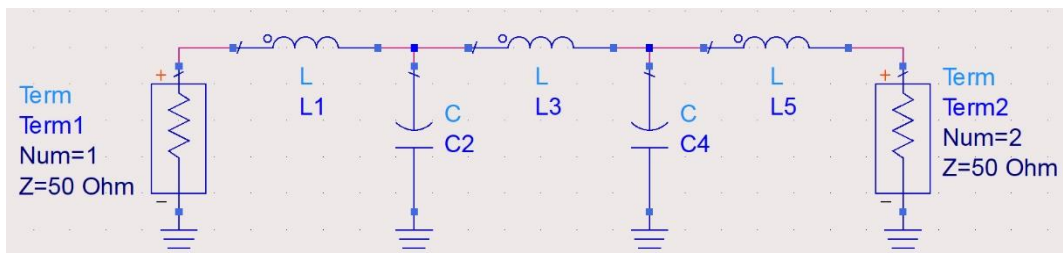

c) In the passband ($f < 315 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 315 \text{ MHz}$; In the stopband ($f > 315 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 630.0 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 21.3\text{dB} + 18.1\text{dB} + 22.2\text{dB} = 61.6\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 1,445,439.8$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2-1)/G_1 + (F_3-1)/G_1/G_2$ but the connection order is A3, A1, A2 so: $F = F_3 + (F_1-1)/G_3 + (F_2-1)/G_3/G_1$; $F_1 = 3.68\text{dB} = 2.333, G_1 = 21.3\text{dB} = 134.896, F_2 = 4.64\text{dB} = 2.911, G_2 = 18.1\text{dB} = 64.565, F_3 = 5.93\text{dB} = 3.917, G_3 = 22.2\text{dB} = 165.959$;

$$F = 3.917 + (2.333-1)/165.959 + (2.911-1)/165.959/134.896 = 3.926 = 5.939\text{dB}$$

c) If the order is A1, A3, A2 the gain remains the same but $F = F_1 + (F_3-1)/G_1 + (F_2-1)/G_1/G_3$;

$$F = 2.333 + (3.917-1)/134.896 + (2.911-1)/134.896/165.959 = 2.355 = 3.720\text{dB}$$

Subject no. 25

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (37.7 - j \cdot 39.9)\Omega = 0.626 - j \cdot 0.662$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.626 - j \cdot 0.662)] / (1 + 0.626 - j \cdot 0.662)$
 $\Gamma = (0.055) + j \cdot (-0.430) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.433 \angle -82.7^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 9.7\text{dBm} - 6.10\text{dB} = 3.60\text{dBm}$;

b) $P_{in} = 9.7\text{dBm} = 9.333\text{mW}$; $P_c = 3.60\text{dBm} = 2.291\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 9.333\text{mW} - 2.291\text{mW} = 7.042\text{mW} = 8.477\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.495, y_2 = 1.151, y_1 = 0.570, Z_1 = Z_0/y_1 = 87.7 \Omega, Z_2 = Z_0/y_2 = 43.4\Omega$

3. a) $Z = 66.00\Omega + j \cdot (45.00)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.251 + j \cdot (0.291) = 0.384 \angle 49.2^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.384$; $\varphi = \arg(\Gamma) = 49.2^\circ$; Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 31.7^\circ$; $\text{Im}(y_s) = -0.831$; $\theta_{P1} = 140.3^\circ$ **or** $\theta_{S2} = 99.1^\circ$; $\text{Im}(y_s) = 0.831$; $\theta_{P2} = 39.7^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 380\text{MHz} = 2.388 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 35.722\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 10.300\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 53.208\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 10.300\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 35.722\text{nH}$;

b) Draw the schematic:

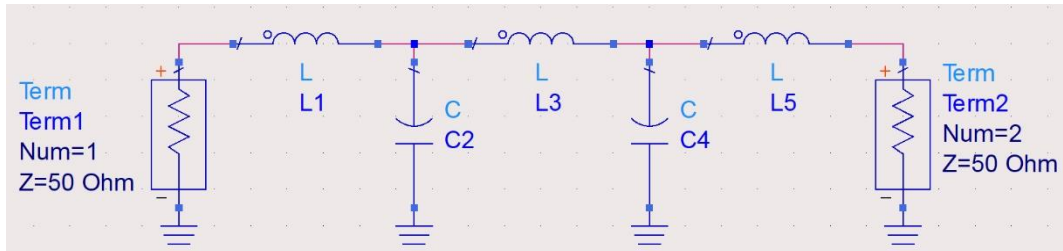

c) In the passband ($f < 380 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 380 \text{ MHz}$; In the stopband ($f > 380 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 760.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 24.7\text{dB} + 17.1\text{dB} + 20.2\text{dB} = 62.0\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 1,584,893.2$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2-1)/G_1 + (F_3-1)/G_1/G_2$ but the connection order is A2, A1, A3 so: $F = F_2 + (F_1-1)/G_2 + (F_3-1)/G_2/G_1$; $F_1 = 3.79\text{dB} = 2.393, G_1 = 24.7\text{dB} = 295.121, F_2 = 4.89\text{dB} = 3.083, G_2 = 17.1\text{dB} = 51.286, F_3 = 5.23\text{dB} = 3.334, G_3 = 20.2\text{dB} = 104.713$;

$F = 3.083 + (2.393-1)/51.286 + (3.334-1)/51.286/295.121 = 3.111 = 4.928\text{dB}$

c) If the order is A3, A1, A2 the gain remains the same but $F = F_3 + (F_1-1)/G_3 + (F_2-1)/G_3/G_1$;

$F = 3.334 + (2.393-1)/104.713 + (3.083-1)/104.713/295.121 = 3.348 = 5.247\text{dB}$

Subject no. 26

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (61.2 + j \cdot 49.5)\Omega = 0.494 + j \cdot 0.399;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.494 + j \cdot 0.399)] / (1 + 0.494 + j \cdot 0.399)$$

$$\Gamma = (0.249) + j \cdot (0.334) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.417 \angle 53.3^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 3.3\text{dBm} - 5.55\text{dB} = -2.25\text{dBm};$

b) $P_{in} = 3.3\text{dBm} = 2.138\text{mW}; P_c = -2.25\text{dBm} = 0.596\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 2.138\text{mW} - 0.596\text{mW} = 1.542\text{mW} = 1.882\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.528, y_2 = 1.177, y_1 = 0.621, Z_1 = Z_0/y_1 = 80.5 \Omega, Z_2 = Z_0/y_2 = 42.5\Omega$

3. a) $Z = 58.00\Omega + j \cdot (-52.82)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = 0.253 + j \cdot (-0.365) = 0.444 \angle -55.3^\circ ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.444; \varphi = \arg(\Gamma) = -55.3^\circ; \text{Complex calculus from L8/2024, S114}\div\text{115, all lines have } Z_0 = 50\Omega$
 $\theta_{S1} = 85.9^\circ ; \text{Im}(y_S) = -0.992 ; \theta_{P1} = 135.2^\circ \text{ or } \theta_{S2} = 149.5^\circ ; \text{Im}(y_S) = 0.992 ; \theta_{P2} = 44.8^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 315\text{MHz} = 1.979 \cdot 10^9 \text{ rad/s} ; R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 43.093\text{nH}; g_2$: shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 12.425\text{pF};$

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 64.187\text{nH}; g_4$: shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 12.425\text{pF};$

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 43.093\text{nH};$

b) Draw the schematic:

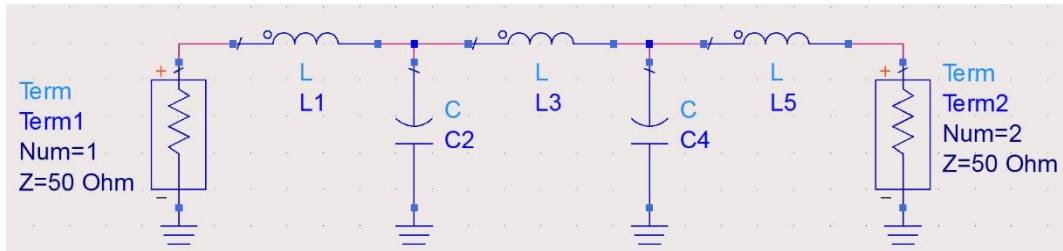

c) In the passband ($f < 315 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 315 \text{ MHz}$; In the stopband ($f > 315 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 630.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 20.0\text{dB} + 15.9\text{dB} + 15.4\text{dB} = 51.3\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 134,896.3$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2-1)/G_1 + (F_3-1)/G_1/G_2$ but the connection order is A2, A1, A3 so: $F = F_2 + (F_1-1)/G_2 + (F_3-1)/G_2/G_1; F_1 = 3.55\text{dB} = 2.265, G_1 = 20.0\text{dB} = 100.000, F_2 = 4.97\text{dB} = 3.141, G_2 = 15.9\text{dB} = 38.905, F_3 = 5.43\text{dB} = 3.491, G_3 = 15.4\text{dB} = 34.674;$

$F = 3.141 + (2.265-1)/38.905 + (3.491-1)/38.905/100.000 = 3.174 = 5.016\text{dB}$

c) If the order is A1, A2, A3 the gain remains the same but $F = F_1 + (F_2-1)/G_1 + (F_3-1)/G_1/G_2;$

$F = 2.265 + (3.141-1)/100.000 + (3.491-1)/100.000/38.905 = 2.287 = 3.592\text{dB}$

Subject no. 27

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (51.4 + j \cdot 31.3)\Omega = 0.710 + j \cdot 0.432;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.710 + j \cdot 0.432)] / (1 + 0.710 + j \cdot 0.432)$$

$$\Gamma = (0.100) + j \cdot (0.278) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.295 \angle 70.3^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 8.0\text{dBm} - 7.70\text{dB} = 0.30\text{dBm};$

b) $P_{in} = 8.0\text{dBm} = 6.310\text{mW}; P_c = 0.30\text{dBm} = 1.072\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 6.310\text{mW} - 1.072\text{mW} = 5.238\text{mW} = 7.192\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.412, y_2 = 1.098, y_1 = 0.452, Z_1 = Z_0/y_1 = 110.5 \Omega, Z_2 = Z_0/y_2 = 45.6\Omega$

3. a) $Z = 14.39\Omega + j \cdot (26.99)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.321 + j \cdot (0.554) = 0.640 \angle 120.1^\circ ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.640; \varphi = \arg(\Gamma) = 120.1^\circ; \text{Complex calculus from L8/2024, S114}\div\text{115, all lines have } Z_0 = 50\Omega$
 $\theta_{S1} = 4.8^\circ ; \text{Im}(y_s) = -1.666 ; \theta_{P1} = 121.0^\circ \text{ or } \theta_{S2} = 55.1^\circ ; \text{Im}(y_s) = 1.666 ; \theta_{P2} = 59.0^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 520\text{MHz} = 3.267 \cdot 10^9 \text{ rad/s} ; R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 3.589\text{pF}; g_2$: shunt inductor $L_2 = R_0 / g_2 / \omega_c = 12.446\text{nH};$

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 2.409\text{pF}; g_4$: shunt inductor $L_4 = R_0 / g_4 / \omega_c = 12.446\text{nH};$

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 3.589\text{pF};$

b) Draw the schematic:

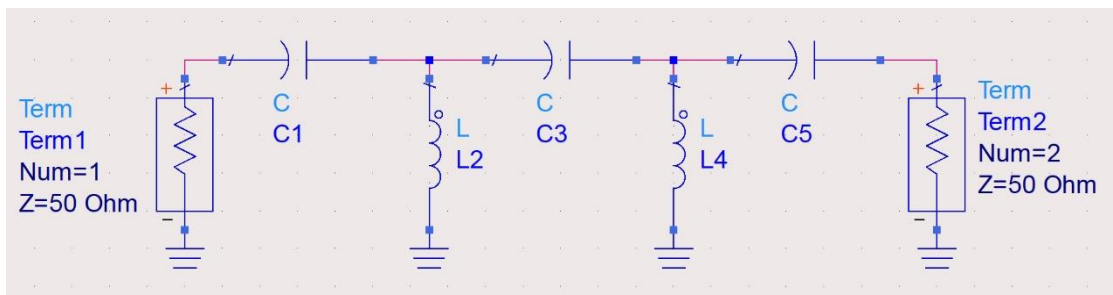

c) In the passband ($f > 520 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{At} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 520 \text{ MHz}$; In the stopband ($f < 520 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 260.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 17.8\text{dB} + 23.7\text{dB} + 20.7\text{dB} = 62.2\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 1,659,586.9$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A3, A1 so: $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3; F_1 = 3.22\text{dB} = 2.099, G_1 = 17.8\text{dB} = 60.256, F_2 = 4.64\text{dB} = 2.911, G_2 = 23.7\text{dB} = 234.423, F_3 = 5.59\text{dB} = 3.622, G_3 = 20.7\text{dB} = 117.490;$

$$F = 2.911 + (3.622 - 1)/234.423 + (2.099 - 1)/234.423/117.490 = 2.922 = 4.657\text{dB}$$

c) If the order is A2, A1, A3 the gain remains the same but $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1;$

$$F = 2.911 + (2.099 - 1)/234.423 + (3.622 - 1)/234.423/60.256 = 2.916 = 4.647\text{dB}$$

Subject no. 28

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (54.6 + j \cdot 50.8)\Omega = 0.491 + j \cdot 0.457$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.491 + j \cdot 0.457)] / (1 + 0.491 + j \cdot 0.457)$
 $\Gamma = (0.226) + j \cdot (0.376) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.439 \angle 58.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 4.8\text{dBm} - 4.85\text{dB} = -0.05\text{dBm}$;

b) $P_{in} = 4.8\text{dBm} = 3.020\text{mW}$; $P_c = -0.05\text{dBm} = 0.989\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 3.020\text{mW} - 0.989\text{mW} = 2.031\text{mW} = 3.078\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.572, y_2 = 1.219, y_1 = 0.698, Z_1 = Z_0/y_1 = 71.7 \Omega, Z_2 = Z_0/y_2 = 41.0\Omega$

3. a) $Z = 30.00\Omega + j \cdot (64.94)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.247 + j \cdot (0.612) = 0.659 \angle 68.0^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.659$; $\varphi = \arg(\Gamma) = 68.0^\circ$; Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 31.6^\circ$; $\text{Im}(y_s) = -1.755$; $\theta_{P1} = 119.7^\circ$ or $\theta_{S2} = 80.3^\circ$; $\text{Im}(y_s) = 1.755$; $\theta_{P2} = 60.3^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 330\text{MHz} = 2.073 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 41.134\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 11.860\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 61.270\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 11.860\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 41.134\text{nH}$;

b) Draw the schematic:

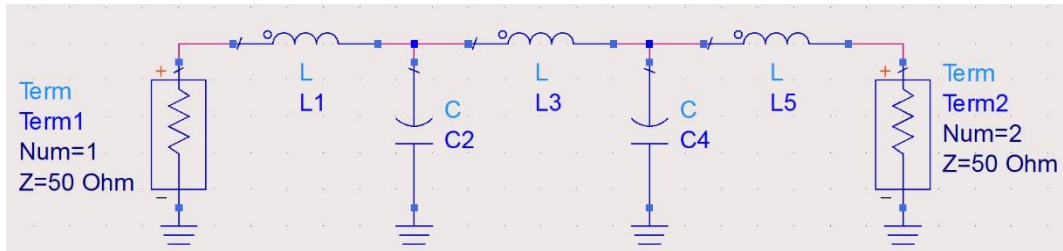

c) In the passband ($f < 330 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 330 \text{ MHz}$; In the stopband ($f > 330 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 660.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 17.0\text{dB} + 21.9\text{dB} + 15.2\text{dB} = 54.1\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 257,039.6$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$; $F_1 = 3.95\text{dB} = 2.483$, $G_1 = 17.0\text{dB} = 50.119$, $F_2 = 4.10\text{dB} = 2.570$, $G_2 = 21.9\text{dB} = 154.882$, $F_3 = 5.64\text{dB} = 3.664$, $G_3 = 15.2\text{dB} = 33.113$;

$F = 2.483 + (2.570 - 1)/50.119 + (3.664 - 1)/50.119/154.882 = 2.515 = 4.005\text{dB}$

c) If the order is A1, A3, A2 the gain remains the same but $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3$;

$F = 2.483 + (3.664 - 1)/50.119 + (2.570 - 1)/50.119/33.113 = 2.537 = 4.044\text{dB}$

Subject no. 29

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (56.5 - j \cdot 59.6)\Omega = 0.419 - j \cdot 0.442$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.419 - j \cdot 0.442)] / (1 + 0.419 - j \cdot 0.442)$
 $\Gamma = (0.285) + j \cdot (-0.400) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.491 \angle -54.5^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 5.6\text{dBm} - 6.65\text{dB} = -1.05\text{dBm}$;

b) $P_{in} = 5.6\text{dBm} = 3.631\text{mW}$; $P_c = -1.05\text{dBm} = 0.785\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 3.631\text{mW} - 0.785\text{mW} = 2.846\text{mW} = 4.542\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.465, y_2 = 1.130, y_1 = 0.525, Z_1 = Z_0/y_1 = 95.2 \Omega, Z_2 = Z_0/y_2 = 44.3\Omega$

3. a) $Z = 24.52\Omega + j \cdot (12.60)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.305 + j \cdot (0.221) = 0.376 \angle 144.1^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.376$; $\varphi = \arg(\Gamma) = 144.1^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 164.0^\circ$; $\text{Im}(y_s) = -0.812$; $\theta_{P1} = 140.9^\circ$ **or** $\theta_{S2} = 51.9^\circ$; $\text{Im}(y_s) = 0.812$; $\theta_{P2} = 39.1^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 560\text{MHz} = 3.519 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 49.476\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 4.330\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 64.488\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 4.330\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 49.476\text{nH}$;

b) Draw the schematic:

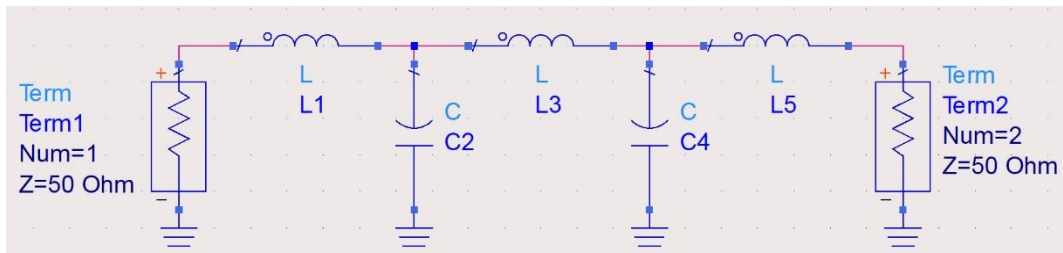

c) In the passband ($f < 560 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 560 \text{ MHz}$; In the stopband ($f > 560 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 1120.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 17.0\text{dB} + 18.6\text{dB} + 15.7\text{dB} = 51.3\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 134,896.3$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$; $F_1 = 3.10\text{dB} = 2.042, G_1 = 17.0\text{dB} = 50.119, F_2 = 4.83\text{dB} = 3.041, G_2 = 18.6\text{dB} = 72.444, F_3 = 5.24\text{dB} = 3.342, G_3 = 15.7\text{dB} = 37.154$;

$F = 2.042 + (3.041 - 1)/50.119 + (3.342 - 1)/50.119/72.444 = 2.083 = 3.187\text{dB}$

c) If the order is A3, A1, A2 the gain remains the same but $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1$;

$F = 3.342 + (2.042 - 1)/37.154 + (3.041 - 1)/37.154/50.119 = 3.371 = 5.278\text{dB}$

Subject no. 30

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (60.9 + j \cdot 63.7)\Omega = 0.392 + j \cdot 0.410$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.392 + j \cdot 0.410)] / (1 + 0.392 + j \cdot 0.410)$
 $\Gamma = (0.322) + j \cdot (0.389) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.505 \angle 50.4^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 6.4\text{dBm} - 4.70\text{dB} = 1.70\text{dBm}$;

b) $P_{in} = 6.4\text{dBm} = 4.365\text{mW}$; $P_c = 1.70\text{dBm} = 1.479\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 4.365\text{mW} - 1.479\text{mW} = 2.886\text{mW} = 4.603\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.582, y_2 = 1.230, y_1 = 0.716, Z_1 = Z_0/y_1 = 69.8 \Omega, Z_2 = Z_0/y_2 = 40.7\Omega$

3. a) $Z = 11.14\Omega + j \cdot (23.57)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.424 + j \cdot (0.549) = 0.694 \angle 127.7^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.694$; $\varphi = \arg(\Gamma) = 127.7^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 3.1^\circ$; $\text{Im}(y_s) = -1.926$; $\theta_{P1} = 117.4^\circ$ **or** $\theta_{S2} = 49.2^\circ$; $\text{Im}(y_s) = 1.926$; $\theta_{P2} = 62.6^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 590\text{MHz} = 3.707 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 23.007\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 6.634\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 34.270\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 6.634\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 23.007\text{nH}$;

b) Draw the schematic:

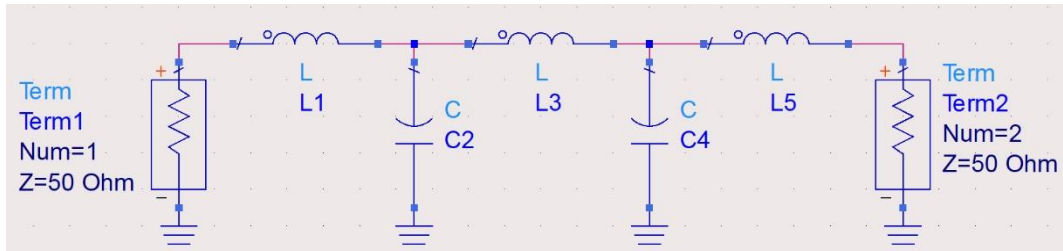

c) In the passband ($f < 590 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 590 \text{ MHz}$; In the stopband ($f > 590 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 1180.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 20.9\text{dB} + 23.8\text{dB} + 19.7\text{dB} = 64.4\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 2,754,228.7$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A3, A2 so: $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3$; $F_1 = 3.90\text{dB} = 2.455, G_1 = 20.9\text{dB} = 123.027, F_2 = 4.84\text{dB} = 3.048, G_2 = 23.8\text{dB} = 239.883, F_3 = 5.16\text{dB} = 3.281, G_3 = 19.7\text{dB} = 93.325$;

$F = 2.455 + (3.281 - 1)/123.027 + (3.048 - 1)/123.027/93.325 = 2.473 = 3.933\text{dB}$

c) If the order is A3, A2, A1 the gain remains the same but $F = F_3 + (F_2 - 1)/G_3 + (F_1 - 1)/G_3/G_2$;

$F = 3.281 + (3.048 - 1)/93.325 + (2.455 - 1)/93.325/239.883 = 3.303 = 5.189\text{dB}$

Subject no. 31

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (36.1 + j \cdot 63.8)\Omega = 0.336 + j \cdot 0.594;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.336 + j \cdot 0.594)] / (1 + 0.336 + j \cdot 0.594)$$

$$\Gamma = (0.250) + j \cdot (0.556) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.609 \angle 65.8^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 7.9\text{dBm} - 7.25\text{dB} = 0.65\text{dBm};$

b) $P_{in} = 7.9\text{dBm} = 6.166\text{mW}; P_c = 0.65\text{dBm} = 1.161\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 6.166\text{mW} - 1.161\text{mW} = 5.005\text{mW} = 6.994\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.434, y_2 = 1.110, y_1 = 0.482, Z_1 = Z_0/y_1 = 103.8 \Omega, Z_2 = Z_0/y_2 = 45.0\Omega$

3. a) $Z = 62.00\Omega + j \cdot (67.54)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = 0.345 + j \cdot (0.395) = 0.525 \angle 48.8^\circ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.525; \varphi = \arg(\Gamma) = 48.8^\circ;$ Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 36.4^\circ; \text{Im}(y_s) = -1.232; \theta_{P1} = 129.1^\circ$ **or** $\theta_{S2} = 94.8^\circ; \text{Im}(y_s) = 1.232; \theta_{P2} = 50.9^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 380\text{MHz} = 2.388 \cdot 10^9 \text{ rad/s}; R_0 = 50\Omega.$ Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 4.911\text{pF}; g_2$: shunt inductor $L_2 = R_0 / g_2 / \omega_c = 17.031\text{nH};$

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 3.297\text{pF}; g_4$: shunt inductor $L_4 = R_0 / g_4 / \omega_c = 17.031\text{nH};$

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 4.911\text{pF};$

b) Draw the schematic:

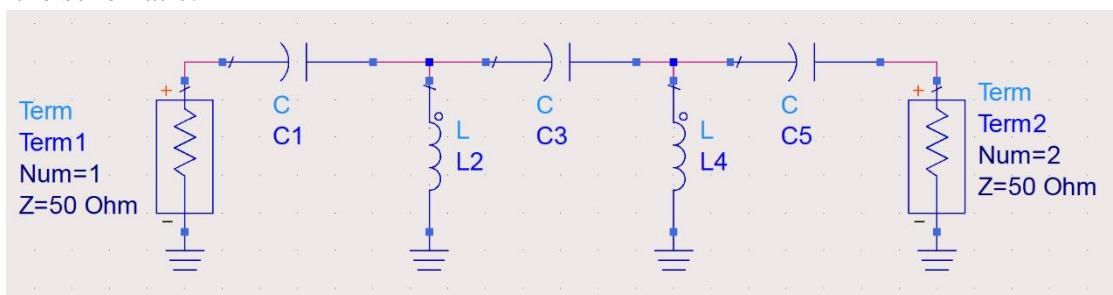

c) In the passband ($f > 380 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 380 \text{ MHz}$; In the stopband ($f < 380 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 190.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 18.4\text{dB} + 20.1\text{dB} + 16.6\text{dB} = 55.1\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 323,593.7$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A3, A2, A1 so: $F = F_3 + (F_2 - 1)/G_3 + (F_1 - 1)/G_3/G_2; F_1 = 3.42\text{dB} = 2.198, G_1 = 18.4\text{dB} = 69.183, F_2 = 4.10\text{dB} = 2.570, G_2 = 20.1\text{dB} = 102.329, F_3 = 5.53\text{dB} = 3.573, G_3 = 16.6\text{dB} = 45.709;$

$$F = 3.573 + (2.570 - 1)/45.709 + (2.198 - 1)/45.709/102.329 = 3.607 = 5.572\text{dB}$$

c) If the order is A1, A2, A3 the gain remains the same but $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2;$

$$F = 2.198 + (2.570 - 1)/69.183 + (3.573 - 1)/69.183/102.329 = 2.221 = 3.465\text{dB}$$

Subject no. 32

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (45.1 - j \cdot 60.5)\Omega = 0.396 - j \cdot 0.531;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.396 - j \cdot 0.531)] / (1 + 0.396 - j \cdot 0.531)$$

$$\Gamma = (0.251) + j \cdot (-0.476) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.539 \angle -62.2^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 8.6\text{dBm} - 7.15\text{dB} = 1.45\text{dBm};$

b) $P_{in} = 8.6\text{dBm} = 7.244\text{mW}; P_c = 1.45\text{dBm} = 1.396\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 7.244\text{mW} - 1.396\text{mW} = 5.848\text{mW} = 7.670\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.439, y_2 = 1.113, y_1 = 0.489, Z_1 = Z_0/y_1 = 102.3 \Omega, Z_2 = Z_0/y_2 = 44.9\Omega$

3. a) $Z = 23.88\Omega + j \cdot (-23.50)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.229 + j \cdot (-0.391) = 0.453 \angle -120.4^\circ ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.453; \varphi = \arg(\Gamma) = -120.4^\circ; \text{Complex calculus from L8/2024, S114} \div 115, \text{ all lines have } Z_0 = 50\Omega$
 $\theta_{S1} = 118.7^\circ; \text{Im}(y_s) = -1.017; \theta_{P1} = 134.5^\circ \text{ or } \theta_{S2} = 1.7^\circ; \text{Im}(y_s) = 1.017; \theta_{P2} = 45.5^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 320\text{MHz} = 2.011 \cdot 10^9 \text{ rad/s}; R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 42.420\text{nH}; g_2$: shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 12.231\text{pF};$

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 63.185\text{nH}; g_4$: shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 12.231\text{pF};$

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 42.420\text{nH};$

b) Draw the schematic:

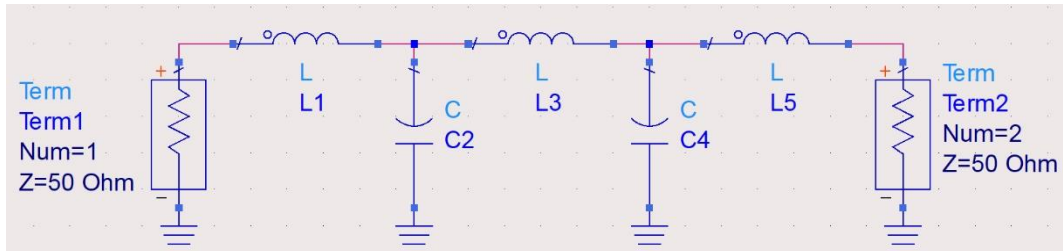

c) In the passband ($f < 320 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 320 \text{ MHz}$; In the stopband ($f > 320 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 640.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 18.9\text{dB} + 19.7\text{dB} + 15.2\text{dB} = 53.8\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 239,883.3$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2; F_1 = 3.81\text{dB} = 2.404, G_1 = 18.9\text{dB} = 77.625, F_2 = 4.09\text{dB} = 2.564, G_2 = 19.7\text{dB} = 93.325, F_3 = 5.40\text{dB} = 3.467, G_3 = 15.2\text{dB} = 33.113;$

$$F = 2.404 + (2.564 - 1)/77.625 + (3.467 - 1)/77.625/93.325 = 2.425 = 3.847\text{dB}$$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3;$

$$F = 2.564 + (3.467 - 1)/93.325 + (2.404 - 1)/93.325/33.113 = 2.591 = 4.135\text{dB}$$

Subject no. 33

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (52.8 - j \cdot 49.4)\Omega = 0.505 - j \cdot 0.472;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.505 - j \cdot 0.472)] / (1 + 0.505 - j \cdot 0.472)$$

$$\Gamma = (0.210) + j \cdot (-0.380) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.434 \angle -61.1^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 3.0\text{dBm} - 5.90\text{dB} = -2.90\text{dBm};$

b) $P_{in} = 3.0\text{dBm} = 1.995\text{mW}; P_c = -2.90\text{dBm} = 0.513\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 1.995\text{mW} - 0.513\text{mW} = 1.482\text{mW} = 1.710\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.507, y_2 = 1.160, y_1 = 0.588, Z_1 = Z_0/y_1 = 85.0 \Omega, Z_2 = Z_0/y_2 = 43.1\Omega$

3. a) $Z = 13.72\Omega + j \cdot (18.62)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.446 + j \cdot (0.423) = 0.614 \angle 136.5^\circ ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.614; \varphi = \arg(\Gamma) = 136.5^\circ; \text{Complex calculus from L8/2024, S114}\div\text{115, all lines have } Z_0 = 50\Omega$
 $\theta_{S1} = 175.7^\circ ; \text{Im}(y_S) = -1.557 ; \theta_{P1} = 122.7^\circ \text{ or } \theta_{S2} = 47.8^\circ ; \text{Im}(y_S) = 1.557 ; \theta_{P2} = 57.3^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 330\text{MHz} = 2.073 \cdot 10^9 \text{ rad/s} ; R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 41.134\text{nH}; g_2$: shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 11.860\text{pF};$

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 61.270\text{nH}; g_4$: shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 11.860\text{pF};$

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 41.134\text{nH};$

b) Draw the schematic:

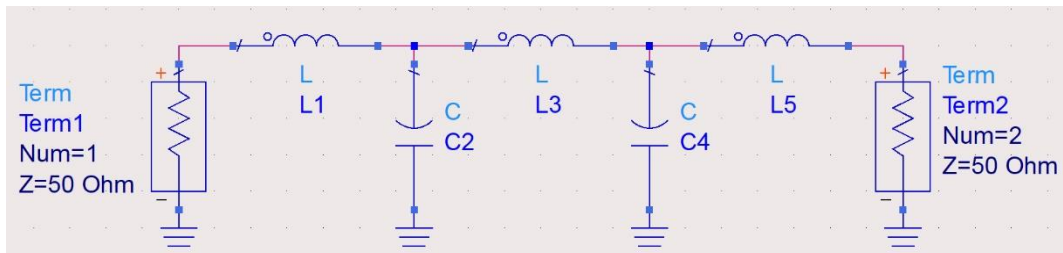

c) In the passband ($f < 330 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 330 \text{ MHz}$; In the stopband ($f > 330 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 660.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 21.6\text{dB} + 22.1\text{dB} + 21.2\text{dB} = 64.9\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 3,090,295.4$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2; F_1 = 3.80\text{dB} = 2.399, G_1 = 21.6\text{dB} = 144.544, F_2 = 4.99\text{dB} = 3.155, G_2 = 22.1\text{dB} = 162.181, F_3 = 5.59\text{dB} = 3.622, G_3 = 21.2\text{dB} = 131.826;$

$F = 2.399 + (3.155 - 1)/144.544 + (3.622 - 1)/144.544/162.181 = 2.414 = 3.827\text{dB}$

c) If the order is A2, A1, A3 the gain remains the same but $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1;$

$F = 3.155 + (2.399 - 1)/162.181 + (3.622 - 1)/162.181/144.544 = 3.164 = 5.002\text{dB}$

Subject no. 34

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (43.2 + j \cdot 62.3)\Omega = 0.376 + j \cdot 0.542;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.376 + j \cdot 0.542)] / (1 + 0.376 + j \cdot 0.542)$$

$$\Gamma = (0.258) + j \cdot (0.496) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.559 \angle 62.5^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 5.8\text{dBm} - 8.45\text{dB} = -2.65\text{dBm};$

b) $P_{in} = 5.8\text{dBm} = 3.802\text{mW}; P_c = -2.65\text{dBm} = 0.543\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 3.802\text{mW} - 0.543\text{mW} = 3.259\text{mW} = 5.130\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.378, y_2 = 1.080, y_1 = 0.408, Z_1 = Z_0/y_1 = 122.5 \Omega, Z_2 = Z_0/y_2 = 46.3\Omega$

3. a) $Z = 31.00\Omega + j \cdot (-70.12)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = 0.294 + j \cdot (-0.611) = 0.678 \angle -64.3^\circ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.678; \varphi = \arg(\Gamma) = -64.3^\circ;$ Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 98.5^\circ; \text{Im}(y_s) = -1.845; \theta_{P1} = 118.5^\circ$ **or** $\theta_{S2} = 145.8^\circ; \text{Im}(y_s) = 1.845; \theta_{P2} = 61.5^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 505\text{MHz} = 3.173 \cdot 10^9 \text{ rad/s}; R_0 = 50\Omega.$ Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 1.810\text{pF}; g_2$: shunt inductor $L_2 = R_0 / g_2 / \omega_c = 20.685\text{nH};$

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 1.389\text{pF}; g_4$: shunt inductor $L_4 = R_0 / g_4 / \omega_c = 20.685\text{nH};$

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 1.810\text{pF};$

b) Draw the schematic:

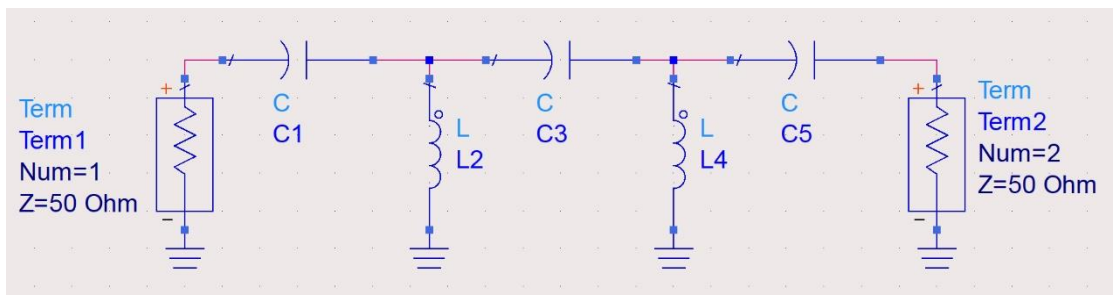

c) In the passband ($f > 505 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 505 \text{ MHz}$; In the stopband ($f < 505 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 252.5 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 24.5\text{dB} + 24.4\text{dB} + 20.2\text{dB} = 69.1\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 8,128,305.2$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A3, A1, A2 so: $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1; F_1 = 3.09\text{dB} = 2.037, G_1 = 24.5\text{dB} = 281.838, F_2 = 4.11\text{dB} = 2.576, G_2 = 24.4\text{dB} = 275.423, F_3 = 5.47\text{dB} = 3.524, G_3 = 20.2\text{dB} = 104.713;$

$$F = 3.524 + (2.037 - 1)/104.713 + (2.576 - 1)/104.713/281.838 = 3.534 = 5.482\text{dB}$$

c) If the order is A1, A3, A2 the gain remains the same but $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3;$

$$F = 2.037 + (3.524 - 1)/281.838 + (2.576 - 1)/281.838/104.713 = 2.046 = 3.109\text{dB}$$

Subject no. 35

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (36.0 - j \cdot 36.8)\Omega = 0.679 - j \cdot 0.694;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.679 - j \cdot 0.694)] / (1 + 0.679 - j \cdot 0.694)$$

$$\Gamma = (0.017) + j \cdot (-0.421) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.421 \angle -87.7^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

$$2. a) P_c = P_{in} - C = 4.7\text{dBm} - 7.05\text{dB} = -2.35\text{dBm};$$

$$b) P_{in} = 4.7\text{dBm} = 2.951\text{mW}; P_c = -2.35\text{dBm} = 0.582\text{mW};$$

$$\text{Lossless coupler } P_{th} = P_{in} - P_c = 2.951\text{mW} - 0.582\text{mW} = 2.369\text{mW} = 3.746\text{dBm}$$

$$c) L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.444, y_2 = 1.116, y_1 = 0.496, Z_1 = Z_0/y_1 = 100.9 \Omega, Z_2 = Z_0/y_2 = 44.8\Omega$$

$$3. a) Z = 34.03\Omega + j \cdot (29.73)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.058 + j \cdot (0.374) = 0.379 \angle 98.8^\circ;$$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

$$c) |\Gamma| = 0.379; \varphi = \arg(\Gamma) = 98.8^\circ; \text{Complex calculus from L8/2024, S114-115, all lines have } Z_0 = 50\Omega$$

$$\theta_{S1} = 6.7^\circ; \text{Im}(y_S) = -0.818; \theta_{P1} = 140.7^\circ \text{ or } \theta_{S2} = 74.5^\circ; \text{Im}(y_S) = 0.818; \theta_{P2} = 39.3^\circ$$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 475\text{MHz} = 2.985 \cdot 10^9 \text{ rad/s}; R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180, g_2 = 1.6180, g_3 = 2.0000, g_4 = 1.6180, g_5 = 0.6180, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

$$g_1 : \text{series capacitor } C_1 = 1 / R_0 / g_1 / \omega_c = 10.843\text{pF}; g_2 : \text{shunt inductor } L_2 = R_0 / g_2 / \omega_c = 10.354\text{nH};$$

$$g_3 : \text{series capacitor } C_3 = 1 / R_0 / g_3 / \omega_c = 3.351\text{pF}; g_4 : \text{shunt inductor } L_4 = R_0 / g_4 / \omega_c = 10.354\text{nH};$$

$$g_5 : \text{series capacitor } C_5 = 1 / R_0 / g_5 / \omega_c = 10.843\text{pF};$$

b) Draw the schematic:

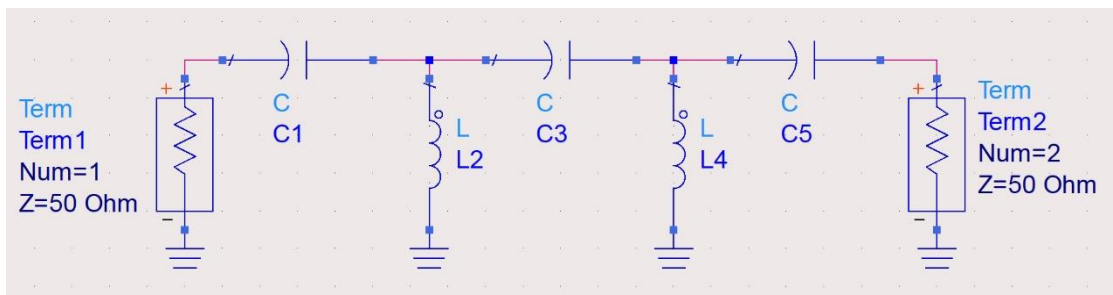

c) In the passband ($f > 475 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 475 \text{ MHz}$; In the stopband ($f < 475 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 237.5 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 24.4\text{dB} + 22.1\text{dB} + 21.3\text{dB} = 67.8\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 6,025,595.9$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A3, A2, A1 so: $F = F_3 + (F_2 - 1)/G_3 + (F_1 - 1)/G_3/G_2$; $F_1 = 3.44\text{dB} = 2.208, G_1 = 24.4\text{dB} = 275.423, F_2 = 4.12\text{dB} = 2.582, G_2 = 22.1\text{dB} = 162.181, F_3 = 5.50\text{dB} = 3.548, G_3 = 21.3\text{dB} = 134.896$;

$$F = 3.548 + (2.582 - 1)/134.896 + (2.208 - 1)/134.896/162.181 = 3.560 = 5.514\text{dB}$$

c) If the order is A2, A1, A3 the gain remains the same but $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1$;

$$F = 2.582 + (2.208 - 1)/162.181 + (3.548 - 1)/162.181/275.423 = 2.590 = 4.133\text{dB}$$

Subject no. 36

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (61.2 - j \cdot 51.4)\Omega = 0.479 - j \cdot 0.402$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.479 - j \cdot 0.402)] / (1 + 0.479 - j \cdot 0.402)$
 $\Gamma = (0.259) + j \cdot (-0.342) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.429 \angle -52.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 6.5\text{dBm} - 7.75\text{dB} = -1.25\text{dBm}$;

b) $P_{in} = 6.5\text{dBm} = 4.467\text{mW}$; $P_c = -1.25\text{dBm} = 0.750\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 4.467\text{mW} - 0.750\text{mW} = 3.717\text{mW} = 5.702\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.410$, $y_2 = 1.096$, $y_1 = 0.449$, $Z_1 = Z_0/y_1 = 111.3 \Omega$, $Z_2 = Z_0/y_2 = 45.6 \Omega$

3. a) $Z = 44.00\Omega + j \cdot (64.14)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.274 + j \cdot (0.495) = 0.566 \angle 61.0^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.566$; $\varphi = \arg(\Gamma) = 61.0^\circ$; Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 31.7^\circ$; $\text{Im}(y_s) = -1.373$; $\theta_{P1} = 126.1^\circ$ **or** $\theta_{S2} = 87.2^\circ$; $\text{Im}(y_s) = 1.373$; $\theta_{P2} = 53.9^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 370\text{MHz} = 2.325 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817$, $g_2 = 0.7618$, $g_3 = 4.5381$, $g_4 = 0.7618$, $g_5 = 3.4817$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 74.882\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 6.554\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 97.603\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 6.554\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 74.882\text{nH}$;

b) Draw the schematic:

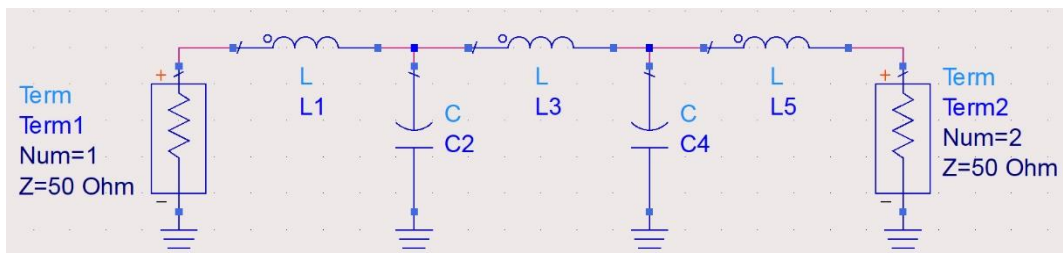

c) In the passband ($f < 370 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 370 \text{ MHz}$; In the stopband ($f > 370 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 740.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 16.6\text{dB} + 20.3\text{dB} + 16.4\text{dB} = 53.3\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 213,796.2$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A3, A2 so: $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3$; $F_1 = 3.38\text{dB} = 2.178$, $G_1 = 16.6\text{dB} = 45.709$, $F_2 = 4.60\text{dB} = 2.884$, $G_2 = 20.3\text{dB} = 107.152$, $F_3 = 5.10\text{dB} = 3.236$, $G_3 = 16.4\text{dB} = 43.652$;

$F = 2.178 + (3.236 - 1)/45.709 + (2.884 - 1)/45.709/43.652 = 2.228 = 3.478\text{dB}$

c) If the order is A2, A1, A3 the gain remains the same but $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1$;

$F = 2.884 + (2.178 - 1)/107.152 + (3.236 - 1)/107.152/45.709 = 2.895 = 4.617\text{dB}$

Subject no. 37

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (34.8 - j \cdot 50.8)\Omega = 0.459 - j \cdot 0.670;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.459 - j \cdot 0.670)] / (1 + 0.459 - j \cdot 0.670)$$

$$\Gamma = (0.132) + j \cdot (-0.520) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.536 \angle -75.7^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

$$2. a) P_c = P_{in} - C = 9.4\text{dBm} - 7.55\text{dB} = 1.85\text{dBm};$$

$$b) P_{in} = 9.4\text{dBm} = 8.710\text{mW}; P_c = 1.85\text{dBm} = 1.531\text{mW};$$

$$\text{Lossless coupler } P_{th} = P_{in} - P_c = 8.710\text{mW} - 1.531\text{mW} = 7.179\text{mW} = 8.560\text{dBm}$$

$$c) L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.419, y_2 = 1.101, y_1 = 0.462, Z_1 = Z_0/y_1 = 108.3 \Omega, Z_2 = Z_0/y_2 = 45.4\Omega$$

$$3. a) Z = 61.00\Omega + j \cdot (-49.24)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = 0.247 + j \cdot (-0.334) = 0.415 \angle -53.5^\circ;$$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

$$c) |\Gamma| = 0.415; \varphi = \arg(\Gamma) = -53.5^\circ; \text{Complex calculus from L8/2024, S114}\div\text{115, all lines have } Z_0 = 50\Omega$$

$$\theta_{S1} = 84.0^\circ; \text{Im}(y_S) = -0.913; \theta_{P1} = 137.6^\circ \text{ or } \theta_{S2} = 149.5^\circ; \text{Im}(y_S) = 0.913; \theta_{P2} = 42.4^\circ$$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + capacitor

$$4. a) \text{Cutoff frequency } \omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 460\text{MHz} = 2.890 \cdot 10^9 \text{ rad/s}; R_0 = 50\Omega. \text{ Filter coefficients from}$$

$$\text{tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: } g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381,$$

$$g_4 = 0.7618, g_5 = 3.4817, g_6 = 1 \text{ (works directly on } 50\Omega \text{ load, no } \lambda/4 \text{ transformer needed).}$$


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

$$g_1 : \text{series capacitor } C_1 = 1 / R_0 / g_1 / \omega_c = 1.987\text{pF}; g_2 : \text{shunt inductor } L_2 = R_0 / g_2 / \omega_c = 22.709\text{nH};$$

$$g_3 : \text{series capacitor } C_3 = 1 / R_0 / g_3 / \omega_c = 1.525\text{pF}; g_4 : \text{shunt inductor } L_4 = R_0 / g_4 / \omega_c = 22.709\text{nH};$$

$$g_5 : \text{series capacitor } C_5 = 1 / R_0 / g_5 / \omega_c = 1.987\text{pF};$$

b) Draw the schematic:

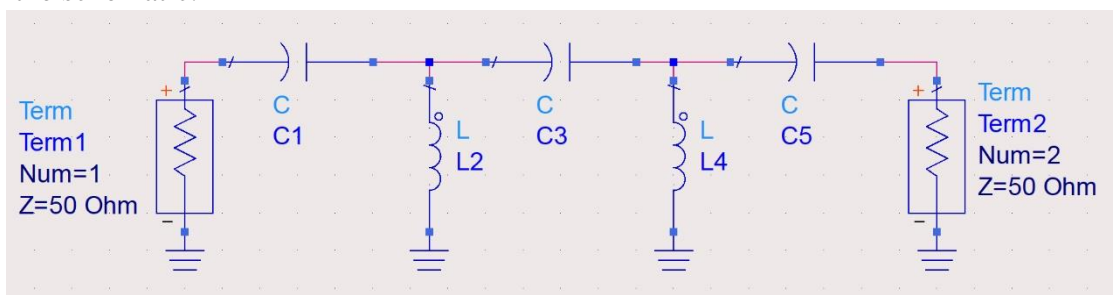

c) In the passband ($f > 460 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 460 \text{ MHz}$; In the stopband ($f < 460 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 230.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 24.0\text{dB} + 20.4\text{dB} + 18.4\text{dB} = 62.8\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 1,905,460.7$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A3, A2, A1 so: $F = F_3 + (F_2 - 1)/G_3 + (F_1 - 1)/G_3/G_2$; $F_1 = 3.08\text{dB} = 2.032, G_1 = 24.0\text{dB} = 251.189, F_2 = 4.28\text{dB} = 2.679, G_2 = 20.4\text{dB} = 109.648, F_3 = 5.26\text{dB} = 3.357, G_3 = 18.4\text{dB} = 69.183$;

$$F = 3.357 + (2.679 - 1)/69.183 + (2.032 - 1)/69.183/109.648 = 3.382 = 5.291\text{dB}$$

c) If the order is A1, A3, A2 the gain remains the same but $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3$;

$$F = 2.032 + (3.357 - 1)/251.189 + (2.679 - 1)/251.189/69.183 = 2.042 = 3.100\text{dB}$$

Subject no. 38

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (68.8 - j \cdot 48.6)\Omega = 0.485 - j \cdot 0.342$;

$\Gamma = (1 - y) / (1 + y) = [1 - (0.485 - j \cdot 0.342)] / (1 + 0.485 - j \cdot 0.342)$

$\Gamma = (0.279) + j \cdot (-0.295) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.406 \angle -46.6^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 9.0\text{dBm} - 7.60\text{dB} = 1.40\text{dBm}$;

b) $P_{in} = 9.0\text{dBm} = 7.943\text{mW}$; $P_c = 1.40\text{dBm} = 1.380\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 7.943\text{mW} - 1.380\text{mW} = 6.563\text{mW} = 8.171\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.417, y_2 = 1.100, y_1 = 0.459, Z_1 = Z_0/y_1 = 109.0 \Omega, Z_2 = Z_0/y_2 = 45.4 \Omega$

3. a) $Z = 22.59\Omega + j \cdot (-8.77)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.358 + j \cdot (-0.164) = 0.394 \angle -155.4^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.394$; $\varphi = \arg(\Gamma) = -155.4^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 134.3^\circ$; $\text{Im}(y_S) = -0.856$; $\theta_{P1} = 139.4^\circ$ **or** $\theta_{S2} = 21.1^\circ$; $\text{Im}(y_S) = 0.856$; $\theta_{P2} = 40.6^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 515\text{MHz} = 3.236 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 53.799\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 4.709\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 70.122\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 4.709\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 53.799\text{nH}$;

b) Draw the schematic:

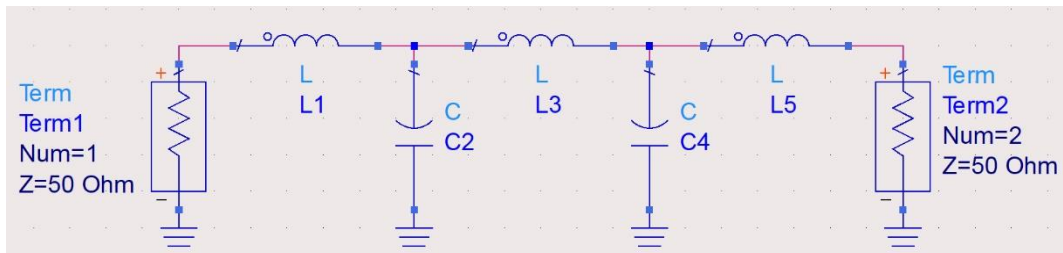

c) In the passband ($f < 515 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 515 \text{ MHz}$; In the stopband ($f > 515 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 1030.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 17.3\text{dB} + 19.4\text{dB} + 19.0\text{dB} = 55.7\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 371,535.2$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A3, A1, A2 so: $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1$; $F_1 = 3.77\text{dB} = 2.382$, $G_1 = 17.3\text{dB} = 53.703$, $F_2 = 4.78\text{dB} = 3.006$, $G_2 = 19.4\text{dB} = 87.096$, $F_3 = 5.56\text{dB} = 3.597$, $G_3 = 19.0\text{dB} = 79.433$;

$F = 3.597 + (2.382 - 1)/79.433 + (3.006 - 1)/79.433/53.703 = 3.615 = 5.582\text{dB}$

c) If the order is A1, A2, A3 the gain remains the same but $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$;

$F = 2.382 + (3.006 - 1)/53.703 + (3.597 - 1)/53.703/87.096 = 2.420 = 3.839\text{dB}$

Subject no. 39

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (46.1 - j \cdot 32.3)\Omega = 0.727 - j \cdot 0.510$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.727 - j \cdot 0.510)] / (1 + 0.727 - j \cdot 0.510)$
 $\Gamma = (0.065) + j \cdot (-0.314) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.321 \angle -78.3^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 8.0\text{dBm} - 6.55\text{dB} = 1.45\text{dBm}$;

b) $P_{in} = 8.0\text{dBm} = 6.310\text{mW}$; $P_c = 1.45\text{dBm} = 1.396\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 6.310\text{mW} - 1.396\text{mW} = 4.913\text{mW} = 6.914\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.470$, $y_2 = 1.133$, $y_1 = 0.533$, $Z_1 = Z_0/y_1 = 93.8 \Omega$, $Z_2 = Z_0/y_2 = 44.1\Omega$

3. a) $Z = 27.00\Omega + j \cdot (-72.42)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.311 + j \cdot (-0.648) = 0.719 \angle -64.4^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.719$; $\varphi = \arg(\Gamma) = -64.4^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 100.2^\circ$; $\text{Im}(y_s) = -2.068$; $\theta_{P1} = 115.8^\circ$ **or** $\theta_{S2} = 144.2^\circ$; $\text{Im}(y_s) = 2.068$; $\theta_{P2} = 64.2^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 370\text{MHz} = 2.325 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058$, $g_2 = 1.2296$, $g_3 = 2.5408$, $g_4 = 1.2296$, $g_5 = 1.7058$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 5.043\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 17.491\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 3.386\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 17.491\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 5.043\text{pF}$;

b) Draw the schematic:

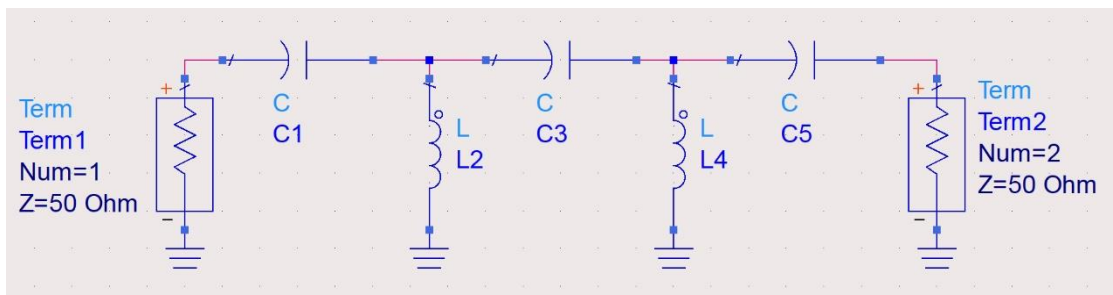

c) In the passband ($f > 370 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 370 \text{ MHz}$; In the stopband ($f < 370 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 185.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 21.0\text{dB} + 19.1\text{dB} + 19.0\text{dB} = 59.1\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 812,830.5$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A3, A1 so: $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$; $F_1 = 3.70\text{dB} = 2.344$, $G_1 = 21.0\text{dB} = 125.893$, $F_2 = 4.55\text{dB} = 2.851$, $G_2 = 19.1\text{dB} = 81.283$, $F_3 = 5.51\text{dB} = 3.556$, $G_3 = 19.0\text{dB} = 79.433$;

$F = 2.851 + (3.556 - 1)/81.283 + (2.344 - 1)/81.283/79.433 = 2.883 = 4.598\text{dB}$

c) If the order is A3, A2, A1 the gain remains the same but $F = F_3 + (F_2 - 1)/G_3 + (F_1 - 1)/G_3/G_2$;

$F = 3.556 + (2.851 - 1)/79.433 + (2.344 - 1)/79.433/81.283 = 3.580 = 5.539\text{dB}$

Subject no. 40

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (64.9 + j \cdot 54.7)\Omega = 0.450 + j \cdot 0.380$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.450 + j \cdot 0.380)] / (1 + 0.450 + j \cdot 0.380)$
 $\Gamma = (0.290) + j \cdot (0.338) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.446 \angle 49.3^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 3.9\text{dBm} - 5.35\text{dB} = -1.45\text{dBm}$;

b) $P_{in} = 3.9\text{dBm} = 2.455\text{mW}$; $P_c = -1.45\text{dBm} = 0.716\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 2.455\text{mW} - 0.716\text{mW} = 1.739\text{mW} = 2.402\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.540$, $y_2 = 1.188$, $y_1 = 0.642$, $Z_1 = Z_0/y_1 = 77.9 \Omega$, $Z_2 = Z_0/y_2 = 42.1\Omega$

3. a) $Z = 19.11\Omega + j \cdot (-18.49)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.350 + j \cdot (-0.361) = 0.503 \angle -134.1^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.503$; $\varphi = \arg(\Gamma) = -134.1^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 127.2^\circ$; $\text{Im}(y_s) = -1.165$; $\theta_{P1} = 130.6^\circ$ **or** $\theta_{S2} = 7.0^\circ$; $\text{Im}(y_s) = 1.165$; $\theta_{P2} = 49.4^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 540\text{MHz} = 3.393 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058$, $g_2 = 1.2296$, $g_3 = 2.5408$, $g_4 = 1.2296$, $g_5 = 1.7058$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 3.456\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 11.985\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 2.320\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 11.985\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 3.456\text{pF}$;

b) Draw the schematic:

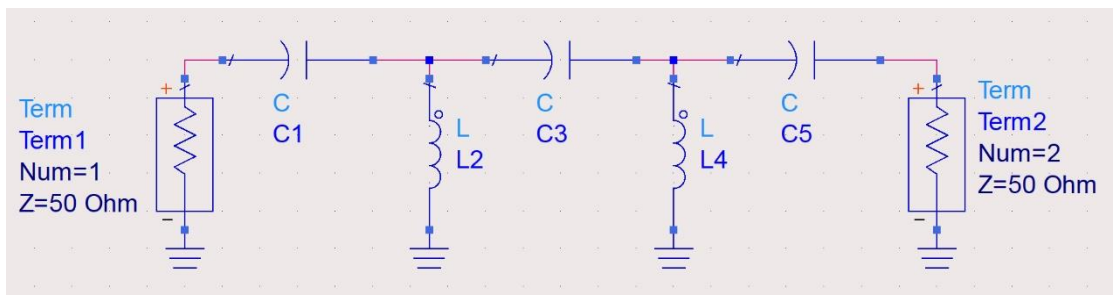

c) In the passband ($f > 540 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 540 \text{ MHz}$; In the stopband ($f < 540 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 270.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 22.4\text{dB} + 16.4\text{dB} + 19.9\text{dB} = 58.7\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 741,310.2$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A3, A2 so: $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3$; $F_1 = 3.18\text{dB} = 2.080$, $G_1 = 22.4\text{dB} = 173.780$, $F_2 = 4.47\text{dB} = 2.799$, $G_2 = 16.4\text{dB} = 43.652$, $F_3 = 5.09\text{dB} = 3.228$, $G_3 = 19.9\text{dB} = 97.724$;

$F = 2.080 + (3.228 - 1)/173.780 + (2.799 - 1)/173.780/97.724 = 2.093 = 3.207\text{dB}$

c) If the order is A2, A1, A3 the gain remains the same but $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1$;

$F = 2.799 + (2.080 - 1)/43.652 + (3.228 - 1)/43.652/173.780 = 2.824 = 4.509\text{dB}$

Subject no. 41

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (50.1 + j \cdot 64.9)\Omega = 0.373 + j \cdot 0.483$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.373 + j \cdot 0.483)] / (1 + 0.373 + j \cdot 0.483)$
 $\Gamma = (0.297) + j \cdot (0.456) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.544 \angle 57.0^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 7.1\text{dBm} - 7.55\text{dB} = -0.45\text{dBm}$;

b) $P_{in} = 7.1\text{dBm} = 5.129\text{mW}$; $P_c = -0.45\text{dBm} = 0.902\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 5.129\text{mW} - 0.902\text{mW} = 4.227\text{mW} = 6.260\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.419$, $y_2 = 1.101$, $y_1 = 0.462$, $Z_1 = Z_0/y_1 = 108.3 \Omega$, $Z_2 = Z_0/y_2 = 45.4\Omega$

3. a) $Z = 56.00\Omega + j \cdot (-71.41)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.351 + j \cdot (-0.437) = 0.561 \angle -51.2^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.561$; $\varphi = \arg(\Gamma) = -51.2^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 87.7^\circ$; $\text{Im}(y_S) = -1.354$; $\theta_{P1} = 126.4^\circ$ **or** $\theta_{S2} = 143.6^\circ$; $\text{Im}(y_S) = 1.354$; $\theta_{P2} = 53.6^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 495\text{MHz} = 3.110 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180$, $g_2 = 1.6180$, $g_3 = 2.0000$, $g_4 = 1.6180$, $g_5 = 0.6180$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 10.405\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 9.936\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 3.215\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 9.936\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 10.405\text{pF}$;

b) Draw the schematic:

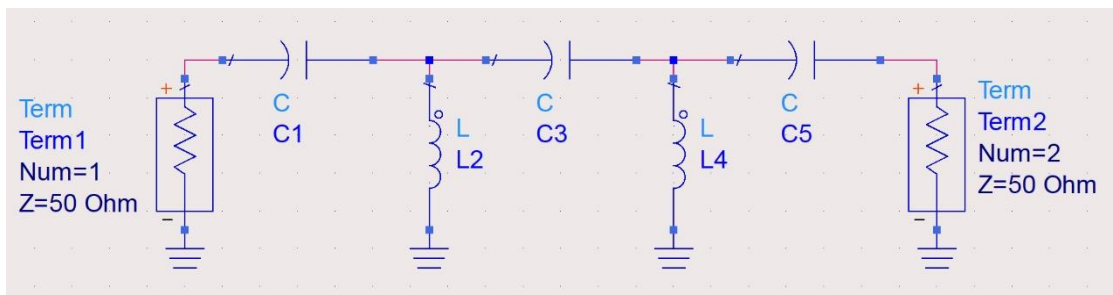

c) In the passband ($f > 495 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 495 \text{ MHz}$; In the stopband ($f < 495 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 247.5 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 15.9\text{dB} + 18.3\text{dB} + 15.1\text{dB} = 49.3\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 85,113.8$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A3, A1 so: $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$; $F_1 = 3.86\text{dB} = 2.432$, $G_1 = 15.9\text{dB} = 38.905$, $F_2 = 4.59\text{dB} = 2.877$, $G_2 = 18.3\text{dB} = 67.608$, $F_3 = 5.52\text{dB} = 3.565$, $G_3 = 15.1\text{dB} = 32.359$;

$F = 2.877 + (3.565 - 1)/67.608 + (2.432 - 1)/67.608/32.359 = 2.916 = 4.648\text{dB}$

c) If the order is A3, A2, A1 the gain remains the same but $F = F_3 + (F_2 - 1)/G_3 + (F_1 - 1)/G_3/G_2$;

$F = 3.565 + (2.877 - 1)/32.359 + (2.432 - 1)/32.359/67.608 = 3.623 = 5.591\text{dB}$

Subject no. 42

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (32.3 + j \cdot 68.4)\Omega = 0.282 + j \cdot 0.598;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.282 + j \cdot 0.598)] / (1 + 0.282 + j \cdot 0.598)$$

$$\Gamma = (0.281) + j \cdot (0.597) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.660 \angle 64.8^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 1.1\text{dBm} - 7.85\text{dB} = -6.75\text{dBm};$

b) $P_{in} = 1.1\text{dBm} = 1.288\text{mW}; P_c = -6.75\text{dBm} = 0.211\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 1.288\text{mW} - 0.211\text{mW} = 1.077\text{mW} = 0.322\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.405, y_2 = 1.094, y_1 = 0.443, Z_1 = Z_0/y_1 = 112.9 \Omega, Z_2 = Z_0/y_2 = 45.7\Omega$

3. a) $Z = 61.00\Omega + j \cdot (49.17)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = 0.247 + j \cdot (0.334) = 0.415 \angle 53.5^\circ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.415; \varphi = \arg(\Gamma) = 53.5^\circ;$ Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 30.5^\circ; \text{Im}(y_s) = -0.912; \theta_{P1} = 137.6^\circ$ **or** $\theta_{S2} = 96.0^\circ; \text{Im}(y_s) = 0.912; \theta_{P2} = 42.4^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 330\text{MHz} = 2.073 \cdot 10^9 \text{ rad/s}; R_0 = 50\Omega.$ Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 41.134\text{nH}; g_2$: shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 11.860\text{pF};$

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 61.270\text{nH}; g_4$: shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 11.860\text{pF};$

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 41.134\text{nH};$

b) Draw the schematic:

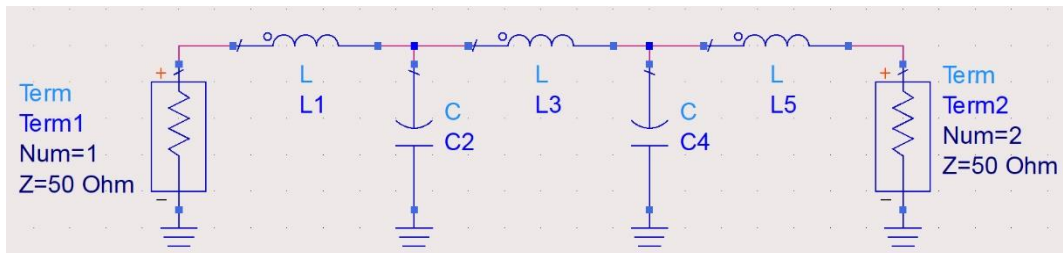

c) In the passband ($f < 330 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 330 \text{ MHz}$; In the stopband ($f > 330 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 660.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 17.7\text{dB} + 17.9\text{dB} + 19.1\text{dB} = 54.7\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 295,120.9$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A3, A1 so: $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3; F_1 = 3.93\text{dB} = 2.472, G_1 = 17.7\text{dB} = 58.884, F_2 = 4.72\text{dB} = 2.965, G_2 = 17.9\text{dB} = 61.660, F_3 = 5.74\text{dB} = 3.750, G_3 = 19.1\text{dB} = 81.283;$

$F = 2.965 + (3.750 - 1)/61.660 + (2.472 - 1)/61.660/81.283 = 3.010 = 4.785\text{dB}$

c) If the order is A3, A1, A2 the gain remains the same but $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1;$

$F = 3.750 + (2.472 - 1)/81.283 + (2.965 - 1)/81.283/58.884 = 3.768 = 5.761\text{dB}$

Subject no. 43

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (50.9 + j\cdot 41.4)\Omega = 0.591 + j\cdot 0.481;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.591 + j\cdot 0.481)] / (1 + 0.591 + j\cdot 0.481)$$

$$\Gamma = (0.152) + j\cdot(0.348) \leftrightarrow \text{Re}\Gamma + j\cdot\text{Im}\Gamma \text{ or } \Gamma = 0.380\angle 66.4^\circ \leftrightarrow |\Gamma|\angle\arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 3.4\text{dBm} - 4.20\text{dB} = -0.80\text{dBm};$

b) $P_{in} = 3.4\text{dBm} = 2.188\text{mW}; P_c = -0.80\text{dBm} = 0.832\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 2.188\text{mW} - 0.832\text{mW} = 1.356\text{mW} = 1.323\text{dBm}$

c) $L_2, C_{12}/2017, \beta = 10^{-C/20} = 0.617, y_2 = 1.270, y_1 = 0.783, Z_1 = Z_0/y_1 = 63.8\Omega, Z_2 = Z_0/y_2 = 39.4\Omega$

3. a) $Z = 22.13\Omega + j\cdot(14.78)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.331 + j\cdot(0.273) = 0.429\angle 140.5^\circ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.429; \varphi = \arg(\Gamma) = 140.5^\circ;$ Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 167.4^\circ; \text{Im}(y_s) = -0.949; \theta_{P1} = 136.5^\circ$ **or** $\theta_{S2} = 52.1^\circ; \text{Im}(y_s) = 0.949; \theta_{P2} = 43.5^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2\cdot\pi\cdot f_c = 2\cdot\pi\cdot 530\text{MHz} = 3.330\cdot 10^9 \text{ rad/s}; R_0 = 50\Omega.$ Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 1.725\text{pF}; g_2$: shunt inductor $L_2 = R_0 / g_2 / \omega_c = 19.709\text{nH};$

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 1.323\text{pF}; g_4$: shunt inductor $L_4 = R_0 / g_4 / \omega_c = 19.709\text{nH};$

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 1.725\text{pF};$

b) Draw the schematic:

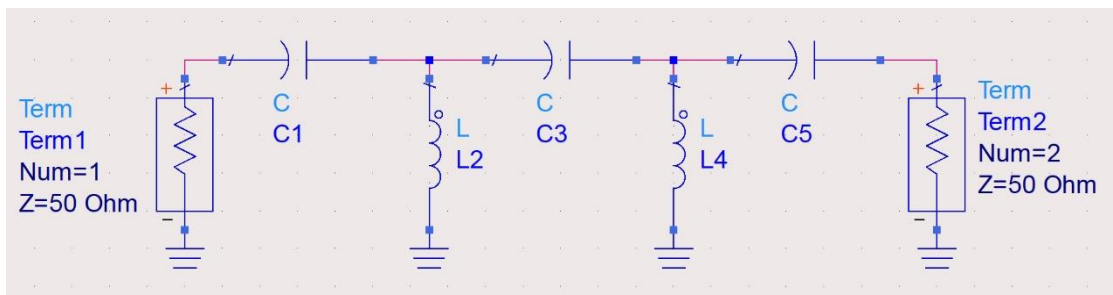

c) In the passband ($f > 530 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 530 \text{ MHz}$; In the stopband ($f < 530 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 265.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 20.8\text{dB} + 23.3\text{dB} + 24.8\text{dB} = 68.9\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 7,762,471.2$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A3, A1 so: $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3; F_1 = 3.06\text{dB} = 2.023, G_1 = 20.8\text{dB} = 120.226, F_2 = 4.76\text{dB} = 2.992, G_2 = 23.3\text{dB} = 213.796, F_3 = 5.96\text{dB} = 3.945, G_3 = 24.8\text{dB} = 301.995;$

$$F = 2.992 + (3.945 - 1)/213.796 + (2.023 - 1)/213.796/301.995 = 3.006 = 4.780\text{dB}$$

c) If the order is A3, A1, A2 the gain remains the same but $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1;$

$$F = 3.945 + (2.023 - 1)/301.995 + (2.992 - 1)/301.995/120.226 = 3.948 = 5.964\text{dB}$$

Subject no. 44

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (53.2 + j \cdot 68.3)\Omega = 0.355 + j \cdot 0.456$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.355 + j \cdot 0.456)] / (1 + 0.355 + j \cdot 0.456)$
 $\Gamma = (0.326) + j \cdot (0.446) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.553 \angle 53.8^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 7.3\text{dBm} - 4.90\text{dB} = 2.40\text{dBm}$;

b) $P_{in} = 7.3\text{dBm} = 5.370\text{mW}$; $P_c = 2.40\text{dBm} = 1.738\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 5.370\text{mW} - 1.738\text{mW} = 3.633\text{mW} = 5.602\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.569, y_2 = 1.216, y_1 = 0.692, Z_1 = Z_0/y_1 = 72.3 \Omega, Z_2 = Z_0/y_2 = 41.1\Omega$

3. a) $Z = 35.00\Omega + j \cdot (-32.02)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.030 + j \cdot (-0.388) = 0.389 \angle -94.5^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.389$; $\varphi = \arg(\Gamma) = -94.5^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 103.7^\circ$; $\text{Im}(y_s) = -0.845$; $\theta_{P1} = 139.8^\circ$ **or** $\theta_{S2} = 170.8^\circ$; $\text{Im}(y_s) = 0.845$; $\theta_{P2} = 40.2^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 410\text{MHz} = 2.576 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180, g_2 = 1.6180, g_3 = 2.0000, g_4 = 1.6180, g_5 = 0.6180, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 12.563\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 11.996\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 3.882\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 11.996\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 12.563\text{pF}$;

b) Draw the schematic:

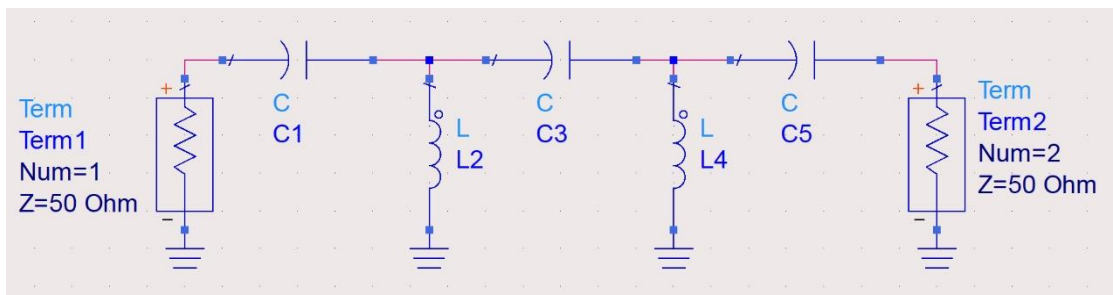

c) In the passband ($f > 410 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 410 \text{ MHz}$; In the stopband ($f < 410 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 205.0 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 19.3\text{dB} + 18.3\text{dB} + 20.0\text{dB} = 57.6\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 575,439.9$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$; $F_1 = 3.53\text{dB} = 2.254, G_1 = 19.3\text{dB} = 85.114, F_2 = 4.47\text{dB} = 2.799, G_2 = 18.3\text{dB} = 67.608, F_3 = 5.91\text{dB} = 3.899, G_3 = 20.0\text{dB} = 100.000$;

$F = 2.254 + (2.799 - 1)/85.114 + (3.899 - 1)/85.114/67.608 = 2.276 = 3.571\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$F = 2.799 + (3.899 - 1)/67.608 + (2.254 - 1)/67.608/100.000 = 2.842 = 4.536\text{dB}$

Subject no. 45

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (61.0 + j \cdot 64.9)\Omega = 0.384 + j \cdot 0.409;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.384 + j \cdot 0.409)] / (1 + 0.384 + j \cdot 0.409)$$

$$\Gamma = (0.329) + j \cdot (0.393) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.512 \angle 50.1^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 8.1\text{dBm} - 6.25\text{dB} = 1.85\text{dBm};$

b) $P_{in} = 8.1\text{dBm} = 6.457\text{mW}; P_c = 1.85\text{dBm} = 1.531\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 6.457\text{mW} - 1.531\text{mW} = 4.925\text{mW} = 6.924\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.487, y_2 = 1.145, y_1 = 0.558, Z_1 = Z_0/y_1 = 89.7 \Omega, Z_2 = Z_0/y_2 = 43.7\Omega$

3. a) $Z = 47.00\Omega + j \cdot (-54.96)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = 0.220 + j \cdot (-0.442) = 0.494 \angle -63.6^\circ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.494; \varphi = \arg(\Gamma) = -63.6^\circ;$ Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 91.6^\circ; \text{Im}(y_s) = -1.135; \theta_{P1} = 131.4^\circ$ **or** $\theta_{S2} = 152.0^\circ; \text{Im}(y_s) = 1.135; \theta_{P2} = 48.6^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 395\text{MHz} = 2.482 \cdot 10^9 \text{ rad/s}; R_0 = 50\Omega.$ Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 2.315\text{pF}; g_2$: shunt inductor $L_2 = R_0 / g_2 / \omega_c = 26.446\text{nH};$

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 1.776\text{pF}; g_4$: shunt inductor $L_4 = R_0 / g_4 / \omega_c = 26.446\text{nH};$

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 2.315\text{pF};$

b) Draw the schematic:

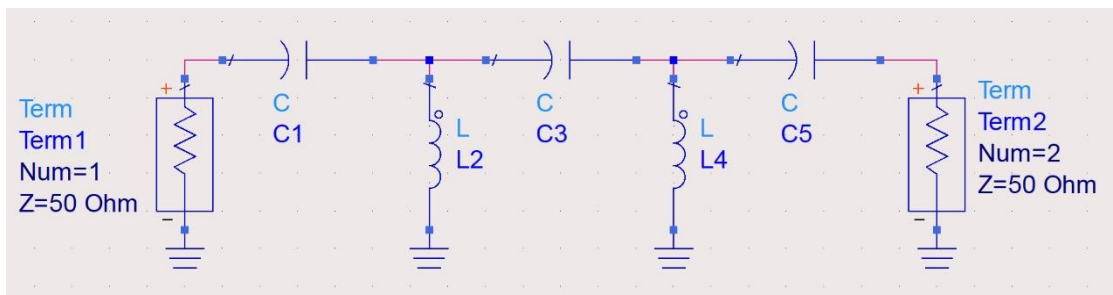

c) In the passband ($f > 395 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 395 \text{ MHz}$; In the stopband ($f < 395 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 197.5 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 21.5\text{dB} + 18.2\text{dB} + 22.8\text{dB} = 62.5\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 1,778,279.4$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2; F_1 = 3.63\text{dB} = 2.307, G_1 = 21.5\text{dB} = 141.254, F_2 = 4.41\text{dB} = 2.761, G_2 = 18.2\text{dB} = 66.069, F_3 = 5.97\text{dB} = 3.954, G_3 = 22.8\text{dB} = 190.546;$

$$F = 2.307 + (2.761 - 1)/141.254 + (3.954 - 1)/141.254/66.069 = 2.320 = 3.654\text{dB}$$

c) If the order is A2, A1, A3 the gain remains the same but $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1;$

$$F = 2.761 + (2.307 - 1)/66.069 + (3.954 - 1)/66.069/141.254 = 2.781 = 4.441\text{dB}$$

Subject no. 46

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (53.7 - j \cdot 35.3)\Omega = 0.650 - j \cdot 0.427;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.650 - j \cdot 0.427)] / (1 + 0.650 - j \cdot 0.427)$$

$$\Gamma = (0.136) + j \cdot (-0.294) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.324 \angle -65.2^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 6.6\text{dBm} - 5.40\text{dB} = 1.20\text{dBm};$

b) $P_{in} = 6.6\text{dBm} = 4.571\text{mW}; P_c = 1.20\text{dBm} = 1.318\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 4.571\text{mW} - 1.318\text{mW} = 3.253\text{mW} = 5.122\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.537, y_2 = 1.185, y_1 = 0.637, Z_1 = Z_0/y_1 = 78.5 \Omega, Z_2 = Z_0/y_2 = 42.2\Omega$

3. a) $Z = 67.00\Omega + j \cdot (75.22)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = 0.395 + j \cdot (0.389) = 0.554 \angle 44.5^\circ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.554; \varphi = \arg(\Gamma) = 44.5^\circ;$ Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 39.6^\circ; \text{Im}(y_s) = -1.332; \theta_{P1} = 126.9^\circ$ **or** $\theta_{S2} = 95.9^\circ; \text{Im}(y_s) = 1.332; \theta_{P2} = 53.1^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 405\text{MHz} = 2.545 \cdot 10^9 \text{ rad/s}; R_0 = 50\Omega.$ Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 68.41\text{ nH}; g_2$: shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 5.987\text{ pF};$

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 89.168\text{ nH}; g_4$: shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 5.987\text{ pF};$

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 68.41\text{ nH};$

b) Draw the schematic:

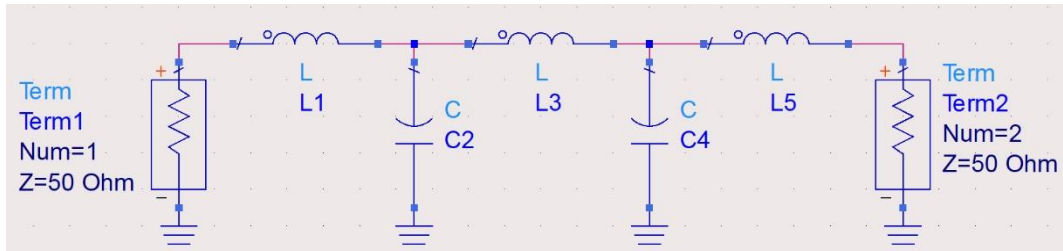

c) In the passband ($f < 405 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 405 \text{ MHz}$; In the stopband ($f > 405 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 810.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 24.5\text{dB} + 24.6\text{dB} + 23.1\text{dB} = 72.2\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 16,595,869.1$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2; F_1 = 3.28\text{dB} = 2.128, G_1 = 24.5\text{dB} = 281.838, F_2 = 4.64\text{dB} = 2.911, G_2 = 24.6\text{dB} = 288.403, F_3 = 5.25\text{dB} = 3.350, G_3 = 23.1\text{dB} = 204.174;$

$F = 2.128 + (2.911 - 1)/281.838 + (3.350 - 1)/281.838/288.403 = 2.135 = 3.294\text{dB}$

c) If the order is A2, A1, A3 the gain remains the same but $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1;$

$F = 2.911 + (2.128 - 1)/288.403 + (3.350 - 1)/288.403/281.838 = 2.915 = 4.646\text{dB}$

Subject no. 47

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (52.8 + j \cdot 56.0)\Omega = 0.446 + j \cdot 0.473$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.446 + j \cdot 0.473)] / (1 + 0.446 + j \cdot 0.473)$
 $\Gamma = (0.250) + j \cdot (0.409) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.479 \angle 58.6^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 2.2\text{dBm} - 6.25\text{dB} = -4.05\text{dBm}$;

b) $P_{in} = 2.2\text{dBm} = 1.660\text{mW}$; $P_c = -4.05\text{dBm} = 0.394\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 1.660\text{mW} - 0.394\text{mW} = 1.266\text{mW} = 1.024\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.487, y_2 = 1.145, y_1 = 0.558, Z_1 = Z_0/y_1 = 89.7 \Omega, Z_2 = Z_0/y_2 = 43.7\Omega$

3. a) $Z = 28.00\Omega + j \cdot (67.33)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.265 + j \cdot (0.634) = 0.687 \angle 67.3^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.687$; $\varphi = \arg(\Gamma) = 67.3^\circ$; Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 33.1^\circ$; $\text{Im}(y_s) = -1.893$; $\theta_{P1} = 117.8^\circ$ **or** $\theta_{S2} = 79.6^\circ$; $\text{Im}(y_s) = 1.893$; $\theta_{P2} = 62.2^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 450\text{MHz} = 2.827 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 61.570\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 5.389\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 80.251\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 5.389\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 61.570\text{nH}$;

b) Draw the schematic:

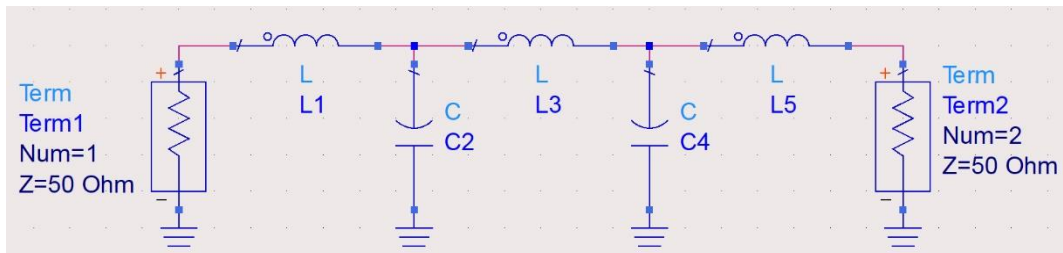

c) In the passband ($f < 450 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 450 \text{ MHz}$; In the stopband ($f > 450 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 900.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 21.8\text{dB} + 15.3\text{dB} + 18.1\text{dB} = 55.2\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 331,131.1$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$; $F_1 = 3.27\text{dB} = 2.123, G_1 = 21.8\text{dB} = 151.356, F_2 = 4.49\text{dB} = 2.812, G_2 = 15.3\text{dB} = 33.884, F_3 = 5.87\text{dB} = 3.864, G_3 = 18.1\text{dB} = 64.565$;

$F = 2.123 + (2.812 - 1)/151.356 + (3.864 - 1)/151.356/33.884 = 2.136 = 3.296\text{dB}$

c) If the order is A2, A1, A3 the gain remains the same but $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1$;

$F = 2.812 + (2.123 - 1)/33.884 + (3.864 - 1)/33.884/151.356 = 2.846 = 4.542\text{dB}$

Subject no. 48

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (49.6 + j \cdot 68.3)\Omega = 0.348 + j \cdot 0.479$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.348 + j \cdot 0.479)] / (1 + 0.348 + j \cdot 0.479)$
 $\Gamma = (0.317) + j \cdot (0.468) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.566 \angle 55.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 8.1\text{dBm} - 5.70\text{dB} = 2.40\text{dBm}$;

b) $P_{in} = 8.1\text{dBm} = 6.457\text{mW}$; $P_c = 2.40\text{dBm} = 1.738\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 6.457\text{mW} - 1.738\text{mW} = 4.719\text{mW} = 6.738\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.519, y_2 = 1.170, y_1 = 0.607, Z_1 = Z_0/y_1 = 82.4 \Omega, Z_2 = Z_0/y_2 = 42.7\Omega$

3. a) $Z = 24.54\Omega + j \cdot (-33.76)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.113 + j \cdot (-0.504) = 0.517 \angle -102.7^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.517$; $\varphi = \arg(\Gamma) = -102.7^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 111.9^\circ$; $\text{Im}(y_s) = -1.207$; $\theta_{P1} = 129.6^\circ$ **or** $\theta_{S2} = 170.8^\circ$; $\text{Im}(y_s) = 1.207$; $\theta_{P2} = 50.4^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 335\text{MHz} = 2.105 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 82.706\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 7.238\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 107.800\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 7.238\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 82.706\text{nH}$;

b) Draw the schematic:

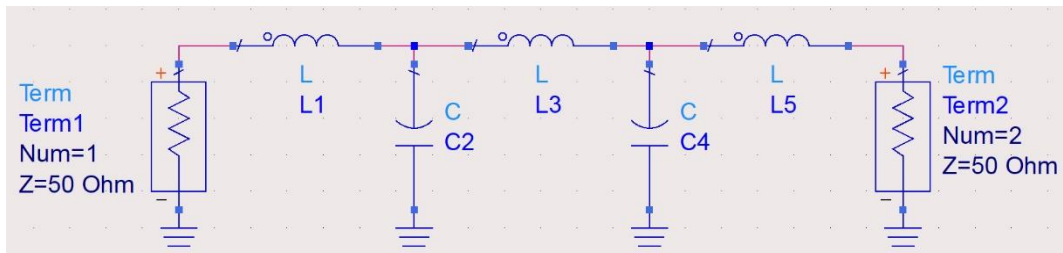

c) In the passband ($f < 335 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 335 \text{ MHz}$; In the stopband ($f > 335 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 670.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 17.8\text{dB} + 16.8\text{dB} + 20.4\text{dB} = 55.0\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 316,227.8$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A3, A1 so: $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$; $F_1 = 3.03\text{dB} = 2.009, G_1 = 17.8\text{dB} = 60.256, F_2 = 4.22\text{dB} = 2.642, G_2 = 16.8\text{dB} = 47.863, F_3 = 5.76\text{dB} = 3.767, G_3 = 20.4\text{dB} = 109.648$;

$F = 2.642 + (3.767 - 1)/47.863 + (2.009 - 1)/47.863/109.648 = 2.700 = 4.314\text{dB}$

c) If the order is A1, A2, A3 the gain remains the same but $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$;

$F = 2.009 + (2.642 - 1)/60.256 + (3.767 - 1)/60.256/47.863 = 2.037 = 3.091\text{dB}$

Subject no. 49

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (57.2 - j \cdot 62.1)\Omega = 0.401 - j \cdot 0.436$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.401 - j \cdot 0.436)] / (1 + 0.401 - j \cdot 0.436)$
 $\Gamma = (0.302) + j \cdot (-0.405) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.505 \angle -53.3^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 1.0\text{dBm} - 7.40\text{dB} = -6.40\text{dBm}$;

b) $P_{in} = 1.0\text{dBm} = 1.259\text{mW}$; $P_c = -6.40\text{dBm} = 0.229\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 1.259\text{mW} - 0.229\text{mW} = 1.030\text{mW} = 0.128\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.427$, $y_2 = 1.106$, $y_1 = 0.472$, $Z_1 = Z_0/y_1 = 106.0\Omega$, $Z_2 = Z_0/y_2 = 45.2\Omega$

3. a) $Z = 28.97\Omega + j \cdot (-35.71)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.051 + j \cdot (-0.475) = 0.478 \angle -96.2^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.478$; $\varphi = \arg(\Gamma) = -96.2^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 107.4^\circ$; $\text{Im}(y_s) = -1.089$; $\theta_{P1} = 132.6^\circ$ **or** $\theta_{S2} = 168.8^\circ$; $\text{Im}(y_s) = 1.089$; $\theta_{P2} = 47.4^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 365\text{MHz} = 2.293 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058$, $g_2 = 1.2296$, $g_3 = 2.5408$, $g_4 = 1.2296$, $g_5 = 1.7058$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 5.112\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 17.731\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 3.432\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 17.731\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 5.112\text{pF}$;

b) Draw the schematic:

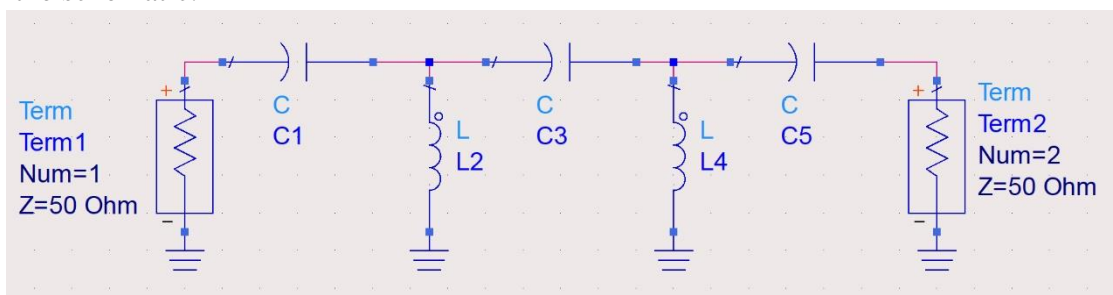

c) In the passband ($f > 365 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 365 \text{ MHz}$; In the stopband ($f < 365 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 182.5 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 21.8\text{dB} + 15.3\text{dB} + 15.3\text{dB} = 52.4\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 173,780.1$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A3, A2 so: $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3$; $F_1 = 3.20\text{dB} = 2.089$, $G_1 = 21.8\text{dB} = 151.356$, $F_2 = 4.02\text{dB} = 2.523$, $G_2 = 15.3\text{dB} = 33.884$, $F_3 = 5.96\text{dB} = 3.945$, $G_3 = 15.3\text{dB} = 33.884$;

$F = 2.089 + (3.945 - 1)/151.356 + (2.523 - 1)/151.356/33.884 = 2.109 = 3.241\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$F = 2.523 + (3.945 - 1)/33.884 + (2.089 - 1)/33.884/33.884 = 2.611 = 4.169\text{dB}$

Subject no. 50

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (30.8 + j \cdot 63.5)\Omega = 0.309 + j \cdot 0.637$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.309 + j \cdot 0.637)] / (1 + 0.309 + j \cdot 0.637)$
 $\Gamma = (0.235) + j \cdot (0.601) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.646 \angle 68.7^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 4.4\text{dBm} - 5.10\text{dB} = -0.70\text{dBm}$;

b) $P_{in} = 4.4\text{dBm} = 2.754\text{mW}$; $P_c = -0.70\text{dBm} = 0.851\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 2.754\text{mW} - 0.851\text{mW} = 1.903\text{mW} = 2.795\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.556$, $y_2 = 1.203$, $y_1 = 0.669$, $Z_1 = Z_0/y_1 = 74.8 \Omega$, $Z_2 = Z_0/y_2 = 41.6\Omega$

3. a) $Z = 69.00\Omega + j \cdot (-50.85)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.289 + j \cdot (-0.304) = 0.420 \angle -46.4^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.420$; $\varphi = \arg(\Gamma) = -46.4^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 80.6^\circ$; $\text{Im}(y_s) = -0.924$; $\theta_{P1} = 137.3^\circ$ **or** $\theta_{S2} = 145.8^\circ$; $\text{Im}(y_s) = 0.924$; $\theta_{P2} = 42.7^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 515\text{MHz} = 3.236 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817$, $g_2 = 0.7618$, $g_3 = 4.5381$, $g_4 = 0.7618$, $g_5 = 3.4817$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 53.799\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 4.709\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 70.122\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 4.709\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 53.799\text{nH}$;

b) Draw the schematic:

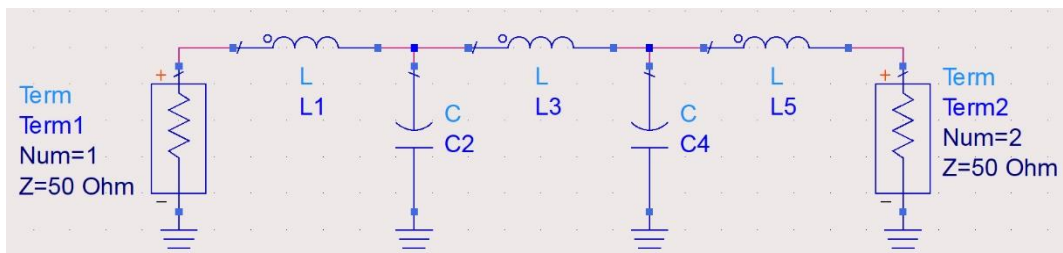

c) In the passband ($f < 515 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 515 \text{ MHz}$; In the stopband ($f > 515 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 1030.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 19.4\text{dB} + 24.9\text{dB} + 20.6\text{dB} = 64.9\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 3,090,295.4$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A3, A1, A2 so: $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1$; $F_1 = 3.88\text{dB} = 2.443$, $G_1 = 19.4\text{dB} = 87.096$, $F_2 = 4.68\text{dB} = 2.938$, $G_2 = 24.9\text{dB} = 309.030$, $F_3 = 5.59\text{dB} = 3.622$, $G_3 = 20.6\text{dB} = 114.815$;

$F = 3.622 + (2.443 - 1)/114.815 + (2.938 - 1)/114.815/87.096 = 3.635 = 5.605\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$F = 2.938 + (3.622 - 1)/309.030 + (2.443 - 1)/309.030/114.815 = 2.946 = 4.693\text{dB}$

Subject no. 51

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (68.3 + j \cdot 52.0)\Omega = 0.463 + j \cdot 0.353$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.463 + j \cdot 0.353)] / (1 + 0.463 + j \cdot 0.353)$
 $\Gamma = (0.292) + j \cdot (0.311) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.427 \angle 46.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 3.0\text{dBm} - 6.20\text{dB} = -3.20\text{dBm}$;

b) $P_{in} = 3.0\text{dBm} = 1.995\text{mW}$; $P_c = -3.20\text{dBm} = 0.479\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 1.995\text{mW} - 0.479\text{mW} = 1.517\text{mW} = 1.809\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.490$, $y_2 = 1.147$, $y_1 = 0.562$, $Z_1 = Z_0/y_1 = 89.0 \Omega$, $Z_2 = Z_0/y_2 = 43.6\Omega$

3. a) $Z = 73.00\Omega + j \cdot (54.43)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = 0.320 + j \cdot (0.301) = 0.439 \angle 43.2^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.439$; $\varphi = \arg(\Gamma) = 43.2^\circ$; Complex calculus from L8/2024, S114-115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 36.4^\circ$; $\text{Im}(y_s) = -0.978$; $\theta_{P1} = 135.6^\circ$ **or** $\theta_{S2} = 100.4^\circ$; $\text{Im}(y_s) = 0.978$; $\theta_{P2} = 44.4^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 440\text{MHz} = 2.765 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180$, $g_2 = 1.6180$, $g_3 = 2.0000$, $g_4 = 1.6180$, $g_5 = 0.6180$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 11.706\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 11.178\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 3.617\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 11.178\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 11.706\text{pF}$;

b) Draw the schematic:

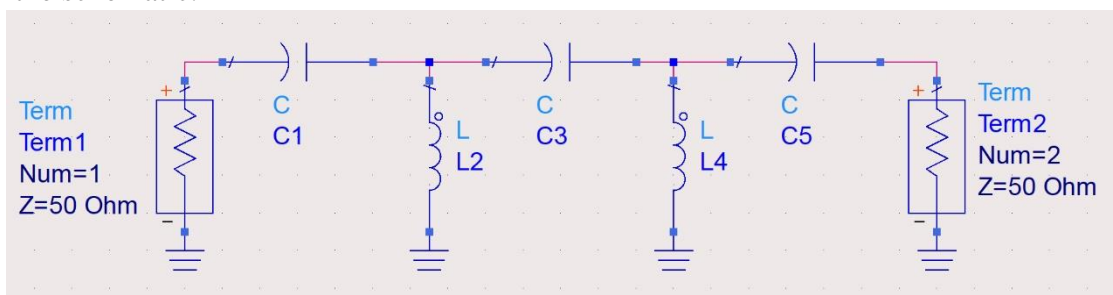

c) In the passband ($f > 440 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 440 \text{ MHz}$; In the stopband ($f < 440 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 220.0 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 23.8\text{dB} + 21.4\text{dB} + 24.5\text{dB} = 69.7\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 9,332,543.0$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$; $F_1 = 3.50\text{dB} = 2.239$, $G_1 = 23.8\text{dB} = 239.883$, $F_2 = 4.00\text{dB} = 2.512$, $G_2 = 21.4\text{dB} = 138.038$, $F_3 = 5.07\text{dB} = 3.214$, $G_3 = 24.5\text{dB} = 281.838$;

$F = 2.239 + (2.512 - 1)/239.883 + (3.214 - 1)/239.883/138.038 = 2.245 = 3.512\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$F = 2.512 + (3.214 - 1)/138.038 + (2.239 - 1)/138.038/281.838 = 2.528 = 4.028\text{dB}$

Subject no. 52

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (69.4 - j \cdot 64.6)\Omega = 0.386 - j \cdot 0.359;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.386 - j \cdot 0.359)] / (1 + 0.386 - j \cdot 0.359)$$

$$\Gamma = (0.352) + j \cdot (-0.351) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.497 \angle -44.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

$$2. a) P_c = P_{in} - C = 2.7\text{dBm} - 4.40\text{dB} = -1.70\text{dBm};$$

$$b) P_{in} = 2.7\text{dBm} = 1.862\text{mW}; P_c = -1.70\text{dBm} = 0.676\text{mW};$$

$$\text{Lossless coupler } P_{th} = P_{in} - P_c = 1.862\text{mW} - 0.676\text{mW} = 1.186\text{mW} = 0.741\text{dBm}$$

$$c) L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.603, y_2 = 1.253, y_1 = 0.755, Z_1 = Z_0/y_1 = 66.2 \Omega, Z_2 = Z_0/y_2 = 39.9\Omega$$

$$3. a) Z = 26.57\Omega + j \cdot (-20.89)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.216 + j \cdot (-0.332) = 0.396 \angle -123.0^\circ ;$$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

$$c) |\Gamma| = 0.396; \varphi = \arg(\Gamma) = -123.0^\circ; \text{Complex calculus from L8/2024, S114}\div\text{115, all lines have } Z_0 = 50\Omega$$

$$\theta_{S1} = 118.2^\circ ; \text{Im}(y_S) = -0.861 ; \theta_{P1} = 139.3^\circ \text{ or } \theta_{S2} = 4.9^\circ ; \text{Im}(y_S) = 0.861 ; \theta_{P2} = 40.7^\circ$$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + capacitor

$$4. a) \text{Cutoff frequency } \omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 500\text{MHz} = 3.142 \cdot 10^9 \text{ rad/s} ; R_0 = 50\Omega. \text{ Filter coefficients from}$$

$$\text{tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: } g_1 = 1.7058, g_2 = 1.2296, g_3 =$$

$$2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1 \text{ (works directly on } 50\Omega \text{ load, no } \lambda/4 \text{ transformer needed).}$$


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

$$g_1 : \text{series capacitor } C_1 = 1 / R_0 / g_1 / \omega_c = 3.732\text{pF}; g_2 : \text{shunt inductor } L_2 = R_0 / g_2 / \omega_c = 12.944\text{nH};$$

$$g_3 : \text{series capacitor } C_3 = 1 / R_0 / g_3 / \omega_c = 2.506\text{pF}; g_4 : \text{shunt inductor } L_4 = R_0 / g_4 / \omega_c = 12.944\text{nH};$$

$$g_5 : \text{series capacitor } C_5 = 1 / R_0 / g_5 / \omega_c = 3.732\text{pF};$$

b) Draw the schematic:

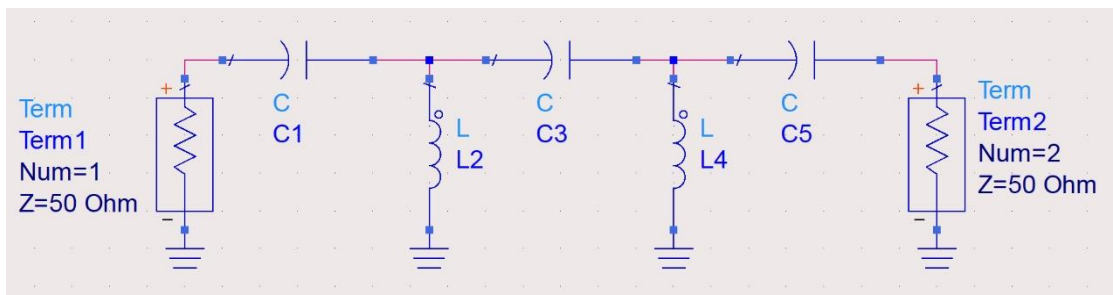

c) In the passband ($f > 500 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 500 \text{ MHz}$; In the stopband ($f < 500 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 250.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 22.8\text{dB} + 21.3\text{dB} + 23.5\text{dB} = 67.6\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 5,754,399.4$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A1, A3 so: $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1$; $F_1 = 3.49\text{dB} = 2.234, G_1 = 22.8\text{dB} = 190.546, F_2 = 4.36\text{dB} = 2.729, G_2 = 21.3\text{dB} = 134.896, F_3 = 5.42\text{dB} = 3.483, G_3 = 23.5\text{dB} = 223.872$;

$$F = 2.729 + (2.234 - 1)/134.896 + (3.483 - 1)/134.896/190.546 = 2.738 = 4.375\text{dB}$$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$$F = 2.729 + (3.483 - 1)/134.896 + (2.234 - 1)/134.896/223.872 = 2.747 = 4.389\text{dB}$$

Subject no. 53

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (53.4 - j \cdot 67.9)\Omega = 0.358 - j \cdot 0.455$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.358 - j \cdot 0.455)] / (1 + 0.358 - j \cdot 0.455)$
 $\Gamma = (0.324) + j \cdot (-0.444) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.550 \angle -53.8^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 8.2\text{dBm} - 6.90\text{dB} = 1.30\text{dBm}$;

b) $P_{in} = 8.2\text{dBm} = 6.607\text{mW}$; $P_c = 1.30\text{dBm} = 1.349\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 6.607\text{mW} - 1.349\text{mW} = 5.258\text{mW} = 7.208\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.452, y_2 = 1.121, y_1 = 0.507, Z_1 = Z_0/y_1 = 98.7 \Omega, Z_2 = Z_0/y_2 = 44.6\Omega$

3. a) $Z = 34.99\Omega + j \cdot (35.00)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.006 + j \cdot (0.414) = 0.414 \angle 90.8^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.414$; $\varphi = \arg(\Gamma) = 90.8^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 11.8^\circ$; $\text{Im}(y_s) = -0.910$; $\theta_{P1} = 137.7^\circ$ **or** $\theta_{S2} = 77.3^\circ$; $\text{Im}(y_s) = 0.910$; $\theta_{P2} = 42.3^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 315\text{MHz} = 1.979 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series inductor $L_1 = g_1 \cdot R_0 / \omega_c = 43.093\text{nH}$; g_2 : shunt capacitor $C_2 = g_2 / R_0 / \omega_c = 12.425\text{pF}$;

g_3 : series inductor $L_3 = g_3 \cdot R_0 / \omega_c = 64.187\text{nH}$; g_4 : shunt capacitor $C_4 = g_4 / R_0 / \omega_c = 12.425\text{pF}$;

g_5 : series inductor $L_5 = g_5 \cdot R_0 / \omega_c = 43.093\text{nH}$;

b) Draw the schematic:

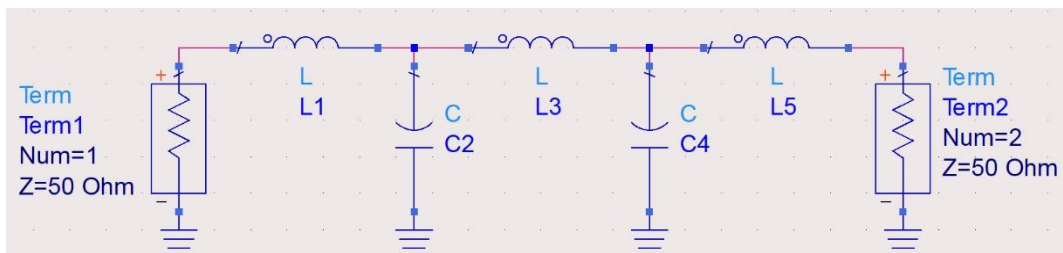

c) In the passband ($f < 315 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{Ar} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 315 \text{ MHz}$; In the stopband ($f > 315 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 630.0 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 23.5\text{dB} + 16.2\text{dB} + 16.9\text{dB} = 56.6\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 457,088.2$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A1, A3 so: $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1$; $F_1 = 3.81\text{dB} = 2.404, G_1 = 23.5\text{dB} = 223.872, F_2 = 4.65\text{dB} = 2.917, G_2 = 16.2\text{dB} = 41.687, F_3 = 5.29\text{dB} = 3.381, G_3 = 16.9\text{dB} = 48.978$;

$F = 2.917 + (2.404 - 1)/41.687 + (3.381 - 1)/41.687/223.872 = 2.951 = 4.700\text{dB}$

c) If the order is A1, A2, A3 the gain remains the same but $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$;

$F = 2.404 + (2.917 - 1)/223.872 + (3.381 - 1)/223.872/41.687 = 2.413 = 3.826\text{dB}$

Subject no. 54

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (62.8 + j \cdot 47.4)\Omega = 0.507 + j \cdot 0.383;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.507 + j \cdot 0.383)] / (1 + 0.507 + j \cdot 0.383)$$

$$\Gamma = (0.247) + j \cdot (0.317) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.401 \angle 52.1^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 3.0\text{dBm} - 7.05\text{dB} = -4.05\text{dBm};$

b) $P_{in} = 3.0\text{dBm} = 1.995\text{mW}; P_c = -4.05\text{dBm} = 0.394\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 1.995\text{mW} - 0.394\text{mW} = 1.602\text{mW} = 2.046\text{dBm}$

c) $L_2, C_{12}/2017, \beta = 10^{-C/20} = 0.444, y_2 = 1.116, y_1 = 0.496, Z_1 = Z_0/y_1 = 100.9 \Omega, Z_2 = Z_0/y_2 = 44.8\Omega$

3. a) $Z = 59.00\Omega + j \cdot (-74.51)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = 0.375 + j \cdot (-0.427) = 0.568 \angle -48.8^\circ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.568; \varphi = \arg(\Gamma) = -48.8^\circ;$ Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 86.7^\circ; \text{Im}(y_s) = -1.382; \theta_{P1} = 125.9^\circ$ **or** $\theta_{S2} = 142.1^\circ; \text{Im}(y_s) = 1.382; \theta_{P2} = 54.1^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 595\text{MHz} = 3.738 \cdot 10^9 \text{ rad/s}; R_0 = 50\Omega.$ Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180, g_2 = 1.6180, g_3 = 2.0000, g_4 = 1.6180, g_5 = 0.6180, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 8.657\text{pF}; g_2$: shunt inductor $L_2 = R_0 / g_2 / \omega_c = 8.266\text{nH};$

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 2.675\text{pF}; g_4$: shunt inductor $L_4 = R_0 / g_4 / \omega_c = 8.266\text{nH};$

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 8.657\text{pF};$

b) Draw the schematic:

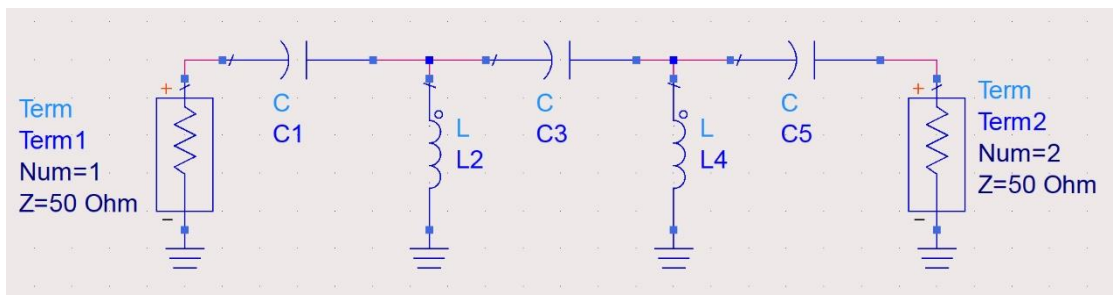

c) In the passband ($f > 595 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 595 \text{ MHz}$; In the stopband ($f < 595 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 297.5 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 15.0\text{dB} + 18.2\text{dB} + 16.9\text{dB} = 50.1\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 102,329.3$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A3, A1, A2 so: $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1; F_1 = 3.06\text{dB} = 2.023, G_1 = 15.0\text{dB} = 31.623, F_2 = 4.84\text{dB} = 3.048, G_2 = 18.2\text{dB} = 66.069, F_3 = 5.83\text{dB} = 3.828, G_3 = 16.9\text{dB} = 48.978;$

$$F = 3.828 + (2.023 - 1)/48.978 + (3.048 - 1)/48.978/31.623 = 3.850 = 5.855\text{dB}$$

c) If the order is A2, A1, A3 the gain remains the same but $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1;$

$$F = 3.048 + (2.023 - 1)/66.069 + (3.828 - 1)/66.069/31.623 = 3.065 = 4.864\text{dB}$$

Subject no. 55

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (43.7 + j \cdot 30.0)\Omega = 0.778 + j \cdot 0.534;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.778 + j \cdot 0.534)] / (1 + 0.778 + j \cdot 0.534)$$

$$\Gamma = (0.032) + j \cdot (0.310) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.312 \angle 84.1^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 6.2\text{dBm} - 5.80\text{dB} = 0.40\text{dBm};$

b) $P_{in} = 6.2\text{dBm} = 4.169\text{mW}; P_c = 0.40\text{dBm} = 1.096\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 4.169\text{mW} - 1.096\text{mW} = 3.072\text{mW} = 4.875\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.513, y_2 = 1.165, y_1 = 0.597, Z_1 = Z_0/y_1 = 83.7 \Omega, Z_2 = Z_0/y_2 = 42.9\Omega$

3. a) $Z = 60.00\Omega + j \cdot (68.89)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = 0.347 + j \cdot (0.409) = 0.536 \angle 49.7^\circ ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.536; \varphi = \arg(\Gamma) = 49.7^\circ; \text{Complex calculus from L8/2024, S114-115, all lines have } Z_0 = 50\Omega$
 $\theta_{S1} = 36.4^\circ ; \text{Im}(y_s) = -1.271 ; \theta_{P1} = 128.2^\circ \text{ or } \theta_{S2} = 93.9^\circ ; \text{Im}(y_s) = 1.271 ; \theta_{P2} = 51.8^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), series circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 540\text{MHz} = 3.393 \cdot 10^9 \text{ rad/s} ; R_0 = 50\Omega. \text{ Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: } g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381, g_4 = 0.7618, g_5 = 3.4817, g_6 = 1 \text{ (works directly on } 50\Omega \text{ load, no } \lambda/4 \text{ transformer needed).}$


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 1.693\text{pF}; g_2$: shunt inductor $L_2 = R_0 / g_2 / \omega_c = 19.344\text{nH};$

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 1.299\text{pF}; g_4$: shunt inductor $L_4 = R_0 / g_4 / \omega_c = 19.344\text{nH};$

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 1.693\text{pF};$

b) Draw the schematic:

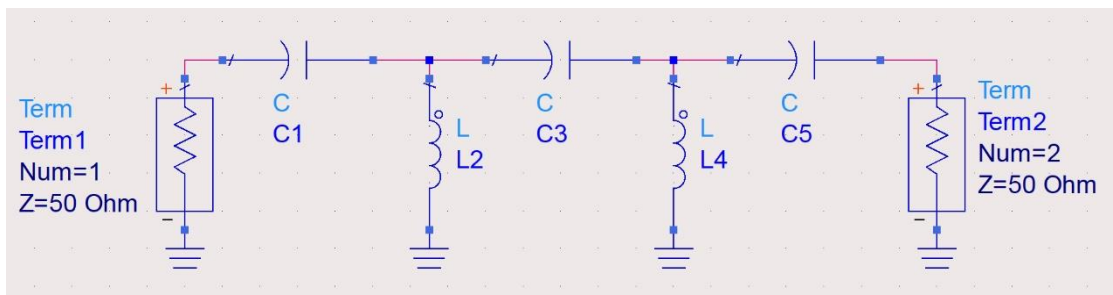

c) In the passband ($f > 540 \text{ MHz}$) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 540 \text{ MHz}$; In the stopband ($f < 540 \text{ MHz}$) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 270.0 \text{ MHz}$ the attenuation is $L_{As} = 51.174 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 23.8\text{dB} + 24.9\text{dB} + 20.4\text{dB} = 69.1\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 8,128,305.2$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A3, A2 so: $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3; F_1 = 3.47\text{dB} = 2.223, G_1 = 23.8\text{dB} = 239.883, F_2 = 4.11\text{dB} = 2.576, G_2 = 24.9\text{dB} = 309.030, F_3 = 5.23\text{dB} = 3.334, G_3 = 20.4\text{dB} = 109.648;$

$F = 2.223 + (3.334 - 1)/239.883 + (2.576 - 1)/239.883/109.648 = 2.233 = 3.489\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3;$

$F = 2.576 + (3.334 - 1)/309.030 + (2.223 - 1)/309.030/109.648 = 2.584 = 4.123\text{dB}$

Subject no. 56

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (58.1 + j \cdot 38.9)\Omega = 0.594 + j \cdot 0.398$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.594 + j \cdot 0.398)] / (1 + 0.594 + j \cdot 0.398)$
 $\Gamma = (0.181) + j \cdot (0.295) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.346 \angle 58.4^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 6.2\text{dBm} - 8.00\text{dB} = -1.80\text{dBm}$;

b) $P_{in} = 6.2\text{dBm} = 4.169\text{mW}$; $P_c = -1.80\text{dBm} = 0.661\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 4.169\text{mW} - 0.661\text{mW} = 3.508\text{mW} = 5.451\text{dBm}$

c) L_2 , C12/2017, $\beta = 10^{-C/20} = 0.398$, $y_2 = 1.090$, $y_1 = 0.434$, $Z_1 = Z_0/y_1 = 115.2 \Omega$, $Z_2 = Z_0/y_2 = 45.9\Omega$

3. a) $Z = 8.67\Omega + j \cdot (-21.70)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.499 + j \cdot (-0.555) = 0.746 \angle -132.0^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.746$; $\varphi = \arg(\Gamma) = -132.0^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 135.1^\circ$; $\text{Im}(y_s) = -2.242$; $\theta_{P1} = 114.0^\circ$ **or** $\theta_{S2} = 176.9^\circ$; $\text{Im}(y_s) = 2.242$; $\theta_{P2} = 66.0^\circ$

c) source (50Ω), shunt stub (50Ω , $\theta_{P1/2}$), series line (50Ω , $\theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 405\text{MHz} = 2.545 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058$, $g_2 = 1.2296$, $g_3 = 2.5408$, $g_4 = 1.2296$, $g_5 = 1.7058$, $g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 4.608\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 15.980\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 3.093\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 15.980\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 4.608\text{pF}$;

b) Draw the schematic:

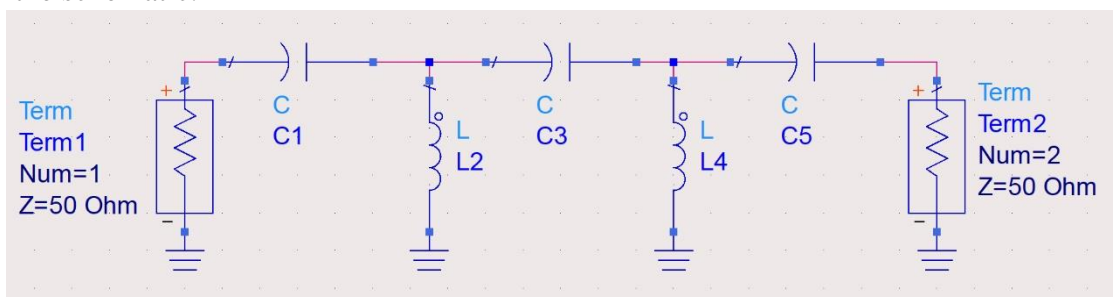

c) In the passband ($f > 405 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{At} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 405 \text{ MHz}$; In the stopband ($f < 405 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 202.5 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 24.1\text{dB} + 20.2\text{dB} + 15.2\text{dB} = 59.5\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 891,250.9$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A3, A2 so: $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3$; $F_1 = 3.81\text{dB} = 2.404$, $G_1 = 24.1\text{dB} = 257.040$, $F_2 = 4.84\text{dB} = 3.048$, $G_2 = 20.2\text{dB} = 104.713$, $F_3 = 5.92\text{dB} = 3.908$, $G_3 = 15.2\text{dB} = 33.113$;

$F = 2.404 + (3.908 - 1)/257.040 + (3.048 - 1)/257.040/33.113 = 2.416 = 3.831\text{dB}$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$F = 3.048 + (3.908 - 1)/104.713 + (2.404 - 1)/104.713/33.113 = 3.076 = 4.880\text{dB}$

Subject no. 57

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (45.7 + j \cdot 60.6)\Omega = 0.397 + j \cdot 0.526;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.397 + j \cdot 0.526)] / (1 + 0.397 + j \cdot 0.526)$$

$$\Gamma = (0.254) + j \cdot (0.472) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.536 \angle 61.7^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

$$2. a) P_c = P_{in} - C = 5.3\text{dBm} - 7.80\text{dB} = -2.50\text{dBm};$$

$$b) P_{in} = 5.3\text{dBm} = 3.388\text{mW}; P_c = -2.50\text{dBm} = 0.562\text{mW};$$

$$\text{Lossless coupler } P_{th} = P_{in} - P_c = 3.388\text{mW} - 0.562\text{mW} = 2.826\text{mW} = 4.512\text{dBm}$$

$$c) L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.407, y_2 = 1.095, y_1 = 0.446, Z_1 = Z_0/y_1 = 112.1 \Omega, Z_2 = Z_0/y_2 = 45.7\Omega$$

$$3. a) Z = 13.52\Omega + j \cdot (15.81)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.482 + j \cdot (0.369) = 0.607 \angle 142.6^\circ ;$$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

$$c) |\Gamma| = 0.607; \varphi = \arg(\Gamma) = 142.6^\circ; \text{Complex calculus from L8/2024, S114}\div\text{115, all lines have } Z_0 = 50\Omega$$

$$\theta_{S1} = 172.4^\circ; \text{Im}(y_s) = -1.529; \theta_{P1} = 123.2^\circ \text{ or } \theta_{S2} = 45.0^\circ; \text{Im}(y_s) = 1.529; \theta_{P2} = 56.8^\circ$$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + inductor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 395\text{MHz} = 2.482 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an equal ripple (0.5dB) filter: $g_1 = 1.7058, g_2 = 1.2296, g_3 = 2.5408, g_4 = 1.2296, g_5 = 1.7058, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

$$g_1 : \text{series capacitor } C_1 = 1 / R_0 / g_1 / \omega_c = 4.724\text{pF}; g_2 : \text{shunt inductor } L_2 = R_0 / g_2 / \omega_c = 16.384\text{nH};$$

$$g_3 : \text{series capacitor } C_3 = 1 / R_0 / g_3 / \omega_c = 3.172\text{pF}; g_4 : \text{shunt inductor } L_4 = R_0 / g_4 / \omega_c = 16.384\text{nH};$$

$$g_5 : \text{series capacitor } C_5 = 1 / R_0 / g_5 / \omega_c = 4.724\text{pF};$$

b) Draw the schematic:

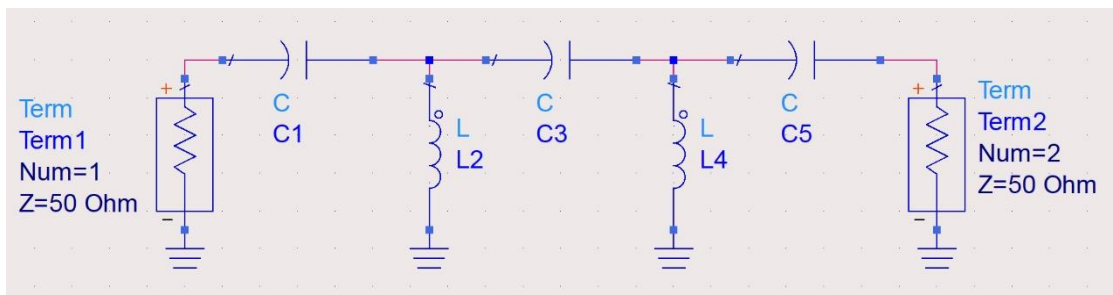

c) In the passband ($f > 395 \text{ MHz}$) we have equal ripple (0.5dB) behavior, maximum attenuation $L_{At} = 0.5 \text{ dB}$, including at the cutoff frequency $f_1 = 395 \text{ MHz}$; In the stopband ($f < 395 \text{ MHz}$) the attenuation for 5th order, equal ripple (0.5dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 197.5 \text{ MHz}$ the attenuation is $L_{As} = 42.039 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 18.1\text{dB} + 15.2\text{dB} + 21.9\text{dB} = 55.2\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 331,131.1$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A1, A3 so: $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1$; $F_1 = 3.80\text{dB} = 2.399, G_1 = 18.1\text{dB} = 64.565, F_2 = 4.42\text{dB} = 2.767, G_2 = 15.2\text{dB} = 33.113, F_3 = 5.52\text{dB} = 3.565, G_3 = 21.9\text{dB} = 154.882$;

$$F = 2.767 + (2.399 - 1)/33.113 + (3.565 - 1)/33.113/64.565 = 2.810 = 4.488\text{dB}$$

c) If the order is A2, A3, A1 the gain remains the same but $F = F_2 + (F_3 - 1)/G_2 + (F_1 - 1)/G_2/G_3$;

$$F = 2.767 + (3.565 - 1)/33.113 + (2.399 - 1)/33.113/154.882 = 2.845 = 4.540\text{dB}$$

Subject no. 58

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (48.2 - j \cdot 43.0)\Omega = 0.578 - j \cdot 0.515;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.578 - j \cdot 0.515)] / (1 + 0.578 - j \cdot 0.515)$$

$$\Gamma = (0.146) + j \cdot (-0.374) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.401 \angle -68.7^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

$$2. a) P_c = P_{in} - C = 5.3\text{dBm} - 4.45\text{dB} = 0.85\text{dBm};$$

$$b) P_{in} = 5.3\text{dBm} = 3.388\text{mW}; P_c = 0.85\text{dBm} = 1.216\text{mW};$$

$$\text{Lossless coupler } P_{th} = P_{in} - P_c = 3.388\text{mW} - 1.216\text{mW} = 2.172\text{mW} = 3.369\text{dBm}$$

$$c) L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.599, y_2 = 1.249, y_1 = 0.748, Z_1 = Z_0/y_1 = 66.8 \Omega, Z_2 = Z_0/y_2 = 40.0\Omega$$

$$3. a) Z = 29.74\Omega + j \cdot (-35.03)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.051 + j \cdot (-0.462) = 0.465 \angle -96.3^\circ ;$$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

$$c) |\Gamma| = 0.465; \varphi = \arg(\Gamma) = -96.3^\circ; \text{Complex calculus from L8/2024, S114}\div\text{115, all lines have } Z_0 = 50\Omega$$

$$\theta_{S1} = 107.0^\circ ; \text{Im}(y_s) = -1.049 ; \theta_{P1} = 133.6^\circ \text{ or } \theta_{S2} = 169.3^\circ ; \text{Im}(y_s) = 1.049 ; \theta_{P2} = 46.4^\circ$$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + capacitor

$$4. a) \text{Cutoff frequency } \omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 445\text{MHz} = 2.796 \cdot 10^9 \text{ rad/s} ; R_0 = 50\Omega. \text{ Filter coefficients from}$$

tables in Lect.11/2024, Sd. 120,122, for an equal ripple (3dB) filter: $g_1 = 3.4817, g_2 = 0.7618, g_3 = 4.5381,$
 $g_4 = 0.7618, g_5 = 3.4817, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**low-pass filter (LPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

$$g_1 : \text{series inductor } L_1 = g_1 \cdot R_0 / \omega_c = 62.262\text{nH}; g_2 : \text{shunt capacitor } C_2 = g_2 / R_0 / \omega_c = 5.449\text{pF};$$

$$g_3 : \text{series inductor } L_3 = g_3 \cdot R_0 / \omega_c = 81.153\text{nH}; g_4 : \text{shunt capacitor } C_4 = g_4 / R_0 / \omega_c = 5.449\text{pF};$$

$$g_5 : \text{series inductor } L_5 = g_5 \cdot R_0 / \omega_c = 62.262\text{nH};$$

b) Draw the schematic:

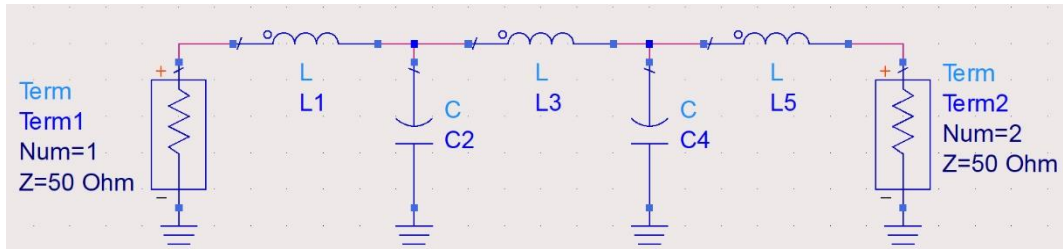

c) In the passband ($f < 445$ MHz) we have equal ripple (3dB) behavior, maximum attenuation $L_{Ar} = 3.0$ dB, including at the cutoff frequency $f_1 = 445$ MHz; In the stopband ($f > 445$ MHz) the attenuation for 5th order, equal ripple (3dB) filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c \cdot 2$) so at $f_s = 890.0$ MHz the attenuation is $L_{As} = 51.174$ dB; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 24.8\text{dB} + 18.9\text{dB} + 16.9\text{dB} = 60.6\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 1,148,153.6$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A2, A3 so: $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$; $F_1 = 3.12\text{dB} = 2.051, G_1 = 24.8\text{dB} = 301.995, F_2 = 4.36\text{dB} = 2.729, G_2 = 18.9\text{dB} = 77.625, F_3 = 5.17\text{dB} = 3.289, G_3 = 16.9\text{dB} = 48.978$;

$$F = 2.051 + (2.729 - 1)/301.995 + (3.289 - 1)/301.995/77.625 = 2.057 = 3.132\text{dB}$$

c) If the order is A1, A3, A2 the gain remains the same but $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3$;

$$F = 2.051 + (3.289 - 1)/301.995 + (2.729 - 1)/301.995/48.978 = 2.059 = 3.136\text{dB}$$

Subject no. 59

$$1. y = Y/Y_0 = Z_0/Z = 50\Omega / (37.9 + j \cdot 33.6)\Omega = 0.739 + j \cdot 0.655;$$

$$\Gamma = (1 - y) / (1 + y) = [1 - (0.739 + j \cdot 0.655)] / (1 + 0.739 + j \cdot 0.655)$$

$$\Gamma = (0.007) + j \cdot (0.379) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma \text{ or } \Gamma = 0.380 \angle 88.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$$

2. a) $P_c = P_{in} - C = 4.4\text{dBm} - 5.50\text{dB} = -1.10\text{dBm};$

b) $P_{in} = 4.4\text{dBm} = 2.754\text{mW}; P_c = -1.10\text{dBm} = 0.776\text{mW};$

Lossless coupler $P_{th} = P_{in} - P_c = 2.754\text{mW} - 0.776\text{mW} = 1.978\text{mW} = 2.962\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.531, y_2 = 1.180, y_1 = 0.626, Z_1 = Z_0/y_1 = 79.8 \Omega, Z_2 = Z_0/y_2 = 42.4\Omega$

3. a) $Z = 19.51\Omega + j \cdot (-28.10)\Omega; \Gamma = (Z - Z_0)/(Z + Z_0) = -0.237 + j \cdot (-0.500) = 0.553 \angle -115.3^\circ ;$

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.553; \varphi = \arg(\Gamma) = -115.3^\circ; \text{Complex calculus from L8/2024, S114} \div 115, \text{ all lines have } Z_0 = 50\Omega$
 $\theta_{S1} = 119.5^\circ ; \text{Im}(y_s) = -1.328 ; \theta_{P1} = 127.0^\circ \text{ or } \theta_{S2} = 175.9^\circ ; \text{Im}(y_s) = 1.328 ; \theta_{P2} = 53.0^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 315\text{MHz} = 1.979 \cdot 10^9 \text{ rad/s} ; R_0 = 50\Omega. \text{ Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: } g_1 = 0.6180, g_2 = 1.6180, g_3 = 2.0000, g_4 = 1.6180, g_5 = 0.6180, g_6 = 1 \text{ (works directly on } 50\Omega \text{ load, no } \lambda/4 \text{ transformer needed).}$


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 16.351\text{pF}; g_2$: shunt inductor $L_2 = R_0 / g_2 / \omega_c = 15.614\text{nH};$

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 5.053\text{pF}; g_4$: shunt inductor $L_4 = R_0 / g_4 / \omega_c = 15.614\text{nH};$

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 16.351\text{pF};$

b) Draw the schematic:

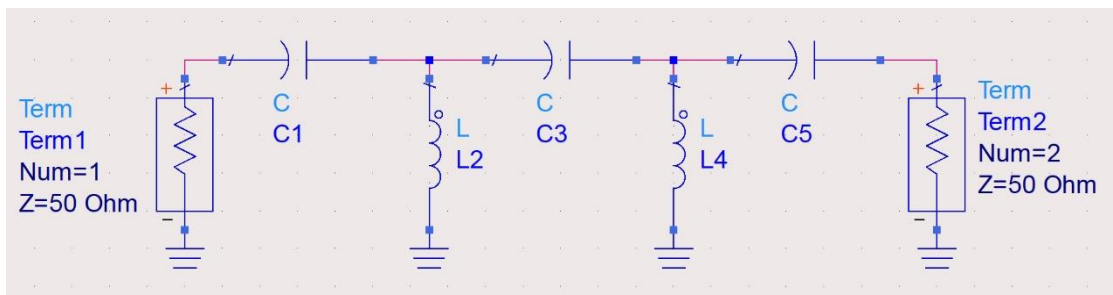

c) In the passband ($f > 315 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 315 \text{ MHz}$; In the stopband ($f < 315 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 157.5 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$$G[\text{dB}] = G_1 + G_2 + G_3 = 19.3\text{dB} + 19.2\text{dB} + 16.5\text{dB} = 55.0\text{dB}; G[\text{lin}] = 10^{G[\text{dB}]/10} = 316,227.8$$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A2, A1, A3 so: $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1; F_1 = 3.19\text{dB} = 2.084, G_1 = 19.3\text{dB} = 85.114, F_2 = 4.02\text{dB} = 2.523, G_2 = 19.2\text{dB} = 83.176, F_3 = 5.91\text{dB} = 3.899, G_3 = 16.5\text{dB} = 44.668;$

$$F = 2.523 + (2.084 - 1)/83.176 + (3.899 - 1)/83.176/85.114 = 2.537 = 4.043\text{dB}$$

c) If the order is A3, A1, A2 the gain remains the same but $F = F_3 + (F_1 - 1)/G_3 + (F_2 - 1)/G_3/G_1;$

$$F = 3.899 + (2.084 - 1)/44.668 + (2.523 - 1)/44.668/85.114 = 3.924 = 5.937\text{dB}$$

Subject no. 60

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (63.0 - j \cdot 59.6)\Omega = 0.419 - j \cdot 0.396$;
 $\Gamma = (1 - y) / (1 + y) = [1 - (0.419 - j \cdot 0.396)] / (1 + 0.419 - j \cdot 0.396)$
 $\Gamma = (0.308) + j \cdot (-0.365) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.477 \angle -49.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

2. a) $P_c = P_{in} - C = 2.4\text{dBm} - 4.75\text{dB} = -2.35\text{dBm}$;

b) $P_{in} = 2.4\text{dBm} = 1.738\text{mW}$; $P_c = -2.35\text{dBm} = 0.582\text{mW}$;

Lossless coupler $P_{th} = P_{in} - P_c = 1.738\text{mW} - 0.582\text{mW} = 1.156\text{mW} = 0.628\text{dBm}$

c) $L_2, C_{12/2017}, \beta = 10^{-C/20} = 0.579, y_2 = 1.226, y_1 = 0.710, Z_1 = Z_0/y_1 = 70.5 \Omega, Z_2 = Z_0/y_2 = 40.8\Omega$

3. a) $Z = 24.51\Omega + j \cdot (-33.02)\Omega$; $\Gamma = (Z - Z_0)/(Z + Z_0) = -0.122 + j \cdot (-0.497) = 0.512 \angle -103.8^\circ$;

b) plot point (Γ) in complex plane either with rectangular coordinates or polar coordinates.

c) $|\Gamma| = 0.512$; $\varphi = \arg(\Gamma) = -103.8^\circ$; Complex calculus from L8/2024, S114÷115, all lines have $Z_0 = 50\Omega$
 $\theta_{S1} = 112.3^\circ$; $\text{Im}(y_s) = -1.192$; $\theta_{P1} = 130.0^\circ$ **or** $\theta_{S2} = 171.5^\circ$; $\text{Im}(y_s) = 1.192$; $\theta_{P2} = 50.0^\circ$

c) source (50Ω), shunt stub ($50\Omega, \theta_{P1/2}$), series line ($50\Omega, \theta_{S1/2}$), parallel circuit: resistor + capacitor

4. a) Cutoff frequency $\omega_c = 2 \cdot \pi \cdot f_c = 2 \cdot \pi \cdot 575\text{MHz} = 3.613 \cdot 10^9 \text{ rad/s}$; $R_0 = 50\Omega$. Filter coefficients from tables in Lect.11/2024, Sd. 120,122, for an maximally flat filter: $g_1 = 0.6180, g_2 = 1.6180, g_3 = 2.0000, g_4 = 1.6180, g_5 = 0.6180, g_6 = 1$ (works directly on 50Ω load, no $\lambda/4$ transformer needed).


Element equations depend on filter type (**high-pass filter (HPF)**) and on choice between starting the prototype filter with series inductor or shunt capacitor. If we choose to start with series inductor:

g_1 : series capacitor $C_1 = 1 / R_0 / g_1 / \omega_c = 8.958\text{pF}$; g_2 : shunt inductor $L_2 = R_0 / g_2 / \omega_c = 8.553\text{nH}$;

g_3 : series capacitor $C_3 = 1 / R_0 / g_3 / \omega_c = 2.768\text{pF}$; g_4 : shunt inductor $L_4 = R_0 / g_4 / \omega_c = 8.553\text{nH}$;

g_5 : series capacitor $C_5 = 1 / R_0 / g_5 / \omega_c = 8.958\text{pF}$;

b) Draw the schematic:

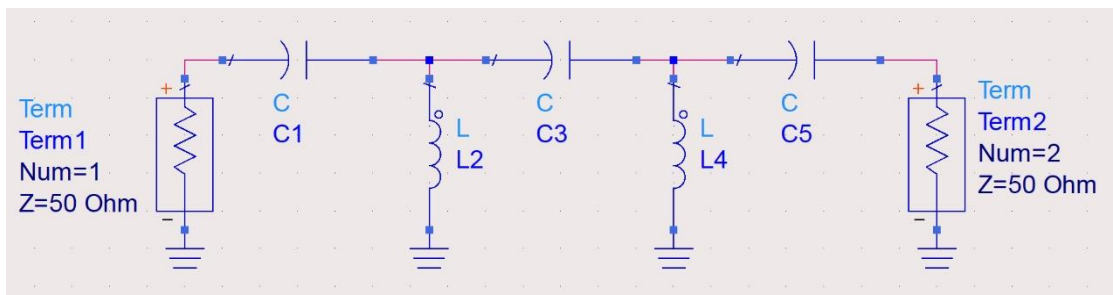

c) In the passband ($f > 575 \text{ MHz}$) we have maximally flat behavior, maximum attenuation $L_{Ar} = 3.0 \text{ dB}$, including at the cutoff frequency $f_1 = 575 \text{ MHz}$; In the stopband ($f < 575 \text{ MHz}$) the attenuation for 5th order, maximally flat filter can be estimated from Lect.11/2024, equations in Sd. 109-110 or plots in Sd. 113-115, for $|\omega / \omega_c| - 1 = 1$ (equivalent to: $\omega = \omega_c / 2$) so at $f_s = 287.5 \text{ MHz}$ the attenuation is $L_{As} = 30.107 \text{ dB}$; Draw a plot similar to Lect. 11 Sd. 104.

5. a) Whatever the order in which the amplifiers are connected:

$G[\text{dB}] = G_1 + G_2 + G_3 = 16.5\text{dB} + 24.4\text{dB} + 23.7\text{dB} = 64.6\text{dB}$; $G[\text{lin}] = 10^{G[\text{dB}]/10} = 2,884,031.5$

b) 3 amplifiers Friis formula, $F = F_1 + (F_2 - 1)/G_1 + (F_3 - 1)/G_1/G_2$ but the connection order is A1, A3, A2 so: $F = F_1 + (F_3 - 1)/G_1 + (F_2 - 1)/G_1/G_3$; $F_1 = 3.42\text{dB} = 2.198, G_1 = 16.5\text{dB} = 44.668, F_2 = 4.13\text{dB} = 2.588, G_2 = 24.4\text{dB} = 275.423, F_3 = 5.94\text{dB} = 3.926, G_3 = 23.7\text{dB} = 234.423$;

$F = 2.198 + (3.926 - 1)/44.668 + (2.588 - 1)/44.668/234.423 = 2.264 = 3.548\text{dB}$

c) If the order is A2, A1, A3 the gain remains the same but $F = F_2 + (F_1 - 1)/G_2 + (F_3 - 1)/G_2/G_1$;

$F = 2.588 + (2.198 - 1)/275.423 + (3.926 - 1)/275.423/44.668 = 2.593 = 4.138\text{dB}$

