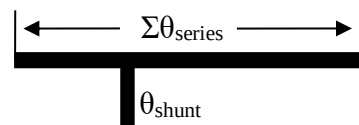


Subject no. 1

1. $y = Y/Y_0 = Z_0/Z = 55\Omega / (46.4 + j \cdot 34.3)\Omega = 0.766 - j \cdot 0.567$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0310 + j \cdot 0.0119)] / (0.02 + 0.0310 + j \cdot 0.0119)$
 $\Gamma = (-0.256) + j \cdot (-0.174) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.309 \angle -145.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless quadrature coupler, matched at the input; Isolation $I = D + C = 29.10\text{dB}$
 $P_{\text{in}} = 3.75\text{mW} = 5.740\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 5.740\text{dBm} - 29.10\text{dB} = -23.36\text{dBm} = 4.614\mu\text{W}$
 b) L2, C5/2025, $\beta = 10^{-C/20} = 0.531$, $y_2 = 1.180$, $y_1 = 0.626$, $Z_1 = Z_0/y_1 = 79.8\Omega$, $Z_2 = Z_0/y_2 = 42.4\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 66)\Omega} = 57.45\Omega$
 b) $Z_L = 66\Omega$ series with 0.73nH inductor at $10.0\text{GHz} = 66.00\Omega + j \cdot (45.87)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 33.72\Omega + j \cdot (-23.43)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 15.80\text{dB}$): $G = G_1 + G_4 = 5.9 + 11.6 = 17.5\text{dB}$; $G = G_2 + G_3 = 7.7 + 9.0 = 16.7\text{dB}$; $G = G_2 + G_4 = 7.7 + 11.6 = 19.3\text{dB}$; $G = G_3 + G_4 = 9.0 + 11.6 = 20.6\text{dB}$;
 b) Friis Formula (C10/2025, S50), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.69\text{dB} = 1.172$, $F_2 = 0.87\text{dB} = 1.222$, $F_3 = 1.03\text{dB} = 1.268$, $F_4 = 1.29\text{dB} = 1.346$, $G_1 = 5.9\text{dB} = 3.890$, $G_2 = 7.7\text{dB} = 5.888$; $F(1,4) = 1.172 + (1.346 - 1)/3.890 = 1.261 = 1.01\text{dB}$; $F(2,3) = 1.222 + (1.268 - 1)/5.888 = 1.281 = 1.07\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.530 < 1$; $|S_{22}| = 0.263 < 1$; $K = 1.312 > 1$; $|\Delta| = |(-0.094) + j \cdot (-0.070)| = 0.117 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 11.71 = 10.69\text{dB}$
 b_2) Complex calculus from C9/2025, S70:
 $B_1 = 1.198$; $C_1 = (-0.547) + j \cdot (0.117)$; $\Gamma_S = (-0.672) + j \cdot (-0.144) = 0.687 \angle -167.9^\circ$
 $B_2 = 0.775$; $C_2 = (-0.143) + j \cdot (-0.289)$; $\Gamma_L = (-0.237) + j \cdot (0.480) = 0.535 \angle 116.3^\circ$
 c) Complex calculus from C7/2025, S112, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 150.7^\circ$; $\text{Im}(y_S) = -1.892$; $\theta_{p1} = 117.9^\circ$ or $\theta_{S2} = 17.3^\circ$; $\text{Im}(y_S) = 1.892$; $\theta_{p2} = 62.1^\circ$
 output: $\theta_{L1} = 3.0^\circ$; $\text{Im}(y_L) = -1.268$; $\theta_{p1} = 128.3^\circ$ or $\theta_{L2} = 60.7^\circ$; $\text{Im}(y_L) = 1.268$; $\theta_{p2} = 51.7^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, C12/2025, S140÷156):
 d1) $\theta_{L1} = 3.0^\circ$; $\text{Im}(y_L) = -1.268 + (-1.892) = -3.159$; $\theta_{p1} = 107.6^\circ$; $\theta_{S1} = 150.7^\circ$;
 d2) $\theta_{L2} = 60.7^\circ$; $\text{Im}(y_L) = 1.268 + (-1.892) = -0.624$; $\theta_{p2} = 148.0^\circ$; $\theta_{S1} = 150.7^\circ$;
 d3) $\theta_{L1} = 3.0^\circ$; $\text{Im}(y_L) = -1.268 + (1.892) = 0.624$; $\theta_{p3} = 32.0^\circ$; $\theta_{S2} = 17.3^\circ$;
 d4) $\theta_{L2} = 60.7^\circ$; $\text{Im}(y_L) = 1.268 + (1.892) = 3.159$; $\theta_{p4} = 72.4^\circ$; $\theta_{S2} = 17.3^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 3.0 + 150.7 = 153.7$; $\theta_p = 107.6$; $A \sim 16534.0$
 e2) $\Sigma\theta_s = 60.7 + 150.7 = 211.3$; $\theta_p = 148.0$; $A \sim 31285.5$
 e3) $\Sigma\theta_s = 3.0 + 17.3 = 20.3$; $\theta_p = 32.0$; $A \sim 649.2$
 e4) $\Sigma\theta_s = 60.7 + 17.3 = 77.9$; $\theta_p = 72.4$; $A \sim 5645.7$
 Smallest substrate area is occupied by solution e3 (d3)



Subject no. 2

1. $y = Y/Y_0 = Z_0/Z = 65\Omega / (44.8 - j \cdot 45.0)\Omega = 0.722 + j \cdot 0.725$

2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0345 + j \cdot 0.0370)] / (0.02 + 0.0345 + j \cdot 0.0370)$
 $\Gamma = (-0.498) + j \cdot (-0.341) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.603 \angle -145.6^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

3. a) Lossless coupled line coupler, matched at the input; Isolation $I = 20.20\text{dB}$

$P_{\text{in}} = 2.95\text{mW} = 4.698\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 4.698\text{dBm} - 20.20\text{dB} = -15.50\text{dBm} = 28.172\mu\text{W}$

b) $L_2, C_5/2025$, $\beta = 10^{-C/20} = 0.528$, $Z_{\text{CE}} = 89.94\Omega$, $Z_{\text{CO}} = 27.80\Omega$

4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 61)\Omega} = 55.23\Omega$

b) $Z_L = 61\Omega$ parallel with 0.97nH inductor at $7.3\text{GHz} = 21.18\Omega + j \cdot (29.04)\Omega$

$\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (-68.55)\Omega$

5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).

Valid combinations ($G > 14.30\text{dB}$): $G = G_1 + G_4 = 5.8 + 11.4 = 17.2\text{dB}$; $G = G_2 + G_3 = 7.4 + 8.4 = 15.8\text{dB}$; $G = G_2 + G_4 = 7.4 + 11.4 = 18.8\text{dB}$; $G = G_3 + G_4 = 8.4 + 11.4 = 19.8\text{dB}$;

b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;

From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$

$F_1 = 0.60\text{dB} = 1.148$, $F_2 = 0.75\text{dB} = 1.189$, $F_3 = 0.97\text{dB} = 1.250$, $F_4 = 1.20\text{dB} = 1.318$, $G_1 = 5.8\text{dB} = 3.802$, $G_2 = 7.4\text{dB} = 5.495$; $F(1,4) = 1.148 + (1.318 - 1)/3.802 = 1.232 = 0.91\text{dB}$; $F(2,3) = 1.189 + (1.250 - 1)/5.495 = 1.246 = 0.96\text{dB}$;

$F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4

6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:

$|S_{11}| = 0.536 < 1$; $|S_{22}| = 0.251 < 1$; $K = 1.315 > 1$; $|\Delta| = |(-0.090) + j \cdot (-0.076)| = 0.118 < 1$

b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 10.97 = 10.40\text{dB}$

b_2) Complex calculus from $C9/2025$, $S70$:

$B_1 = 1.210$; $C_1 = (-0.536) + j \cdot (0.180)$; $\Gamma_S = (-0.654) + j \cdot (-0.219) = 0.689 \angle -161.5^\circ$

$B_2 = 0.762$; $C_2 = (-0.156) + j \cdot (-0.273)$; $\Gamma_L = (-0.262) + j \cdot (0.457) = 0.527 \angle 119.8^\circ$

c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines

input: $\theta_{S1} = 147.5^\circ$; $\text{Im}(y_S) = -1.902$; $\theta_{p1} = 117.7^\circ$ or $\theta_{S2} = 14.0^\circ$; $\text{Im}(y_S) = 1.902$; $\theta_{p2} = 62.3^\circ$

output: $\theta_{L1} = 1.0^\circ$; $\text{Im}(y_L) = -1.239$; $\theta_{p1} = 128.9^\circ$ or $\theta_{L2} = 59.2^\circ$; $\text{Im}(y_L) = 1.239$; $\theta_{p2} = 51.1^\circ$

d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):

d1) $\theta_{L1} = 1.0^\circ$; $\text{Im}(y_L) = -1.239 + (-1.902) = -3.142$; $\theta_{p1} = 107.7^\circ$; $\theta_{S1} = 147.5^\circ$;

d2) $\theta_{L2} = 59.2^\circ$; $\text{Im}(y_L) = 1.239 + (-1.902) = -0.663$; $\theta_{p2} = 146.5^\circ$; $\theta_{S1} = 147.5^\circ$;

d3) $\theta_{L1} = 1.0^\circ$; $\text{Im}(y_L) = -1.239 + (1.902) = 0.663$; $\theta_{p3} = 33.5^\circ$; $\theta_{S2} = 14.0^\circ$;

d4) $\theta_{L2} = 59.2^\circ$; $\text{Im}(y_L) = 1.239 + (1.902) = 3.142$; $\theta_{p4} = 72.3^\circ$; $\theta_{S2} = 14.0^\circ$;

e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.


e1) $\Sigma\theta_s = 1.0 + 147.5 = 148.5$; $\theta_p = 107.7$; $A \sim 15987.5$

e2) $\Sigma\theta_s = 59.2 + 147.5 = 206.7$; $\theta_p = 146.5$; $A \sim 30276.6$

e3) $\Sigma\theta_s = 1.0 + 14.0 = 15.0$; $\theta_p = 33.5$; $A \sim 501.0$


e4) $\Sigma\theta_s = 59.2 + 14.0 = 73.2$; $\theta_p = 72.3$; $A \sim 5292.1$

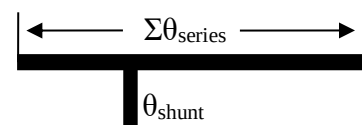Smallest substrate area is occupied by solution e3 (d3)




Subject no. 3

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (69.0 - j \cdot 43.2)\Omega = 0.521 + j \cdot 0.326$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0198 - j \cdot 0.0238)] / (0.02 + 0.0198 - j \cdot 0.0238)$
 $\Gamma = (-0.260) + j \cdot (0.443) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.513 \angle 120.4^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless quadrature coupler, matched at the input; Isolation $I = 23.70\text{dB}$
 $P_{\text{in}} = 3.50\text{mW} = 5.441\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 5.441\text{dBm} - 23.70\text{dB} = -18.26\text{dBm} = 14.930\mu\text{W}$
 b) L_2 , C5/2025, $\beta = 10^{-C/20} = 0.490$, $y_2 = 1.147$, $y_1 = 0.562$, $Z_1 = Z_0/y_1 = 89.0\Omega$, $Z_2 = Z_0/y_2 = 43.6\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 59)\Omega} = 54.31\Omega$
 b) $Z_L = 59\Omega$ parallel with 1.18nH inductor at $8.9\text{GHz} = 32.79\Omega + j \cdot (29.32)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (-44.71)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 16.80\text{dB}$): $G = G_1 + G_4 = 5.7 + 11.3 = 17.0\text{dB}$; $G = G_2 + G_3 = 8.9 + 9.3 = 18.2\text{dB}$; $G = G_2 + G_4 = 8.9 + 11.3 = 20.2\text{dB}$; $G = G_3 + G_4 = 9.3 + 11.3 = 20.6\text{dB}$;
 b) Friis Formula (C10/2025, S50), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.62\text{dB} = 1.153$, $F_2 = 0.74\text{dB} = 1.186$, $F_3 = 0.92\text{dB} = 1.236$, $F_4 = 1.25\text{dB} = 1.334$, $G_1 = 5.7\text{dB} = 3.715$, $G_2 = 8.9\text{dB} = 7.762$; $F(1,4) = 1.153 + (1.334 - 1)/3.715 = 1.243 = 0.95\text{dB}$; $F(2,3) = 1.186 + (1.236 - 1)/7.762 = 1.229 = 0.89\text{dB}$;
 $F(1,4) > F(2,3) \rightarrow$ For minimal noise factor we must use devices 2,3
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.553 < 1$; $|S_{22}| = 0.230 < 1$; $K = 1.308 > 1$; $|\Delta| = |(-0.098) + j \cdot (-0.091)| = 0.134 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 9.67 = 9.86\text{dB}$
 b_2) Complex calculus from C9/2025, S70:
 $B_1 = 1.235$; $C_1 = (-0.497) + j \cdot (0.299)$; $\Gamma_S = (-0.598) + j \cdot (-0.361) = 0.699 \angle -148.9^\circ$
 $B_2 = 0.729$; $C_2 = (-0.179) + j \cdot (-0.236)$; $\Gamma_L = (-0.310) + j \cdot (0.409) = 0.513 \angle 127.2^\circ$
 c) Complex calculus from C7/2025, S112, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 141.6^\circ$; $\text{Im}(y_S) = -1.953$; $\theta_{p1} = 117.1^\circ$ or $\theta_{S2} = 7.3^\circ$; $\text{Im}(y_S) = 1.953$; $\theta_{p2} = 62.9^\circ$
 output: $\theta_{L1} = 176.9^\circ$; $\text{Im}(y_L) = -1.197$; $\theta_{p1} = 129.9^\circ$ or $\theta_{L2} = 56.0^\circ$; $\text{Im}(y_L) = 1.197$; $\theta_{p2} = 50.1^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, C12/2025, S140÷156):
 d1) $\theta_{L1} = 176.9^\circ$; $\text{Im}(y_L) = -1.197 + (-1.953) = -3.149$; $\theta_{p1} = 107.6^\circ$; $\theta_{S1} = 141.6^\circ$;
 d2) $\theta_{L2} = 56.0^\circ$; $\text{Im}(y_L) = 1.197 + (-1.953) = -0.756$; $\theta_{p2} = 142.9^\circ$; $\theta_{S1} = 141.6^\circ$;
 d3) $\theta_{L1} = 176.9^\circ$; $\text{Im}(y_L) = -1.197 + (1.953) = 0.756$; $\theta_{p3} = 37.1^\circ$; $\theta_{S2} = 7.3^\circ$;
 d4) $\theta_{L2} = 56.0^\circ$; $\text{Im}(y_L) = 1.197 + (1.953) = 3.149$; $\theta_{p4} = 72.4^\circ$; $\theta_{S2} = 7.3^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 176.9 + 141.6 = 318.5$; $\theta_p = 107.6$; $A \sim 34272.9$
 e2) $\Sigma\theta_s = 56.0 + 141.6 = 197.6$; $\theta_p = 142.9$; $A \sim 28236.8$
 e3) $\Sigma\theta_s = 176.9 + 7.3 = 184.2$; $\theta_p = 37.1$; $A \sim 6829.5$
 e4) $\Sigma\theta_s = 56.0 + 7.3 = 63.3$; $\theta_p = 72.4$; $A \sim 4579.4$
 Smallest substrate area is occupied by solution e4 (d4)

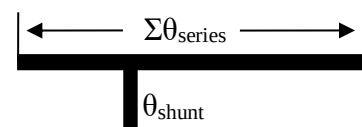

Subject no. 4

1. $y = Y/Y_0 = Z_0/Z = 65\Omega / (62.1 + j \cdot 66.7)\Omega = 0.486 - j \cdot 0.522$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0290 + j \cdot 0.0380)] / (0.02 + 0.0290 + j \cdot 0.0380)$
 $\Gamma = (-0.490) + j \cdot (-0.395) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.630 \angle -141.1^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless coupled line coupler, matched at the input; Isolation $I = 24.60\text{dB}$
 $P_{\text{in}} = 3.35\text{mW} = 5.250\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 5.250\text{dBm} - 24.60\text{dB} = -19.35\text{dBm} = 11.616\mu\text{W}$
 b) $L_2, C_5/2025$, $\beta = 10^{-C/20} = 0.534$, $Z_{\text{CE}} = 90.71\Omega$, $Z_{\text{CO}} = 27.56\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 51)\Omega} = 50.50\Omega$
 b) $Z_L = 51\Omega$ series with 0.73nH inductor at $9.8\text{GHz} = 51.00\Omega + j \cdot (44.95)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 28.14\Omega + j \cdot (-24.80)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 15.15\text{dB}$): $G = G_1 + G_4 = 6.1 + 11.0 = 17.1\text{dB}$; $G = G_2 + G_3 = 7.0 + 8.9 = 15.9\text{dB}$; $G = G_2 + G_4 = 7.0 + 11.0 = 18.0\text{dB}$; $G = G_3 + G_4 = 8.9 + 11.0 = 19.9\text{dB}$;
 b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.64\text{dB} = 1.159$, $F_2 = 0.76\text{dB} = 1.191$, $F_3 = 0.94\text{dB} = 1.242$, $F_4 = 1.24\text{dB} = 1.330$, $G_1 = 6.1\text{dB} = 4.074$, $G_2 = 7.0\text{dB} = 5.012$; $F(1,4) = 1.159 + (1.330 - 1)/4.074 = 1.240 = 0.93\text{dB}$; $F(2,3) = 1.191 + (1.242 - 1)/5.012 = 1.257 = 0.99\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.540 < 1$; $|S_{22}| = 0.245 < 1$; $K = 1.310 > 1$; $|\Delta| = |(-0.091) + j \cdot (-0.080)| = 0.121 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 10.64 = 10.27\text{dB}$
 b_2) Complex calculus from $C9/2025$, $S70$:
 $B_1 = 1.217$; $C_1 = (-0.529) + j \cdot (0.210)$; $\Gamma_S = (-0.643) + j \cdot (-0.256) = 0.692 \angle -158.3^\circ$
 $B_2 = 0.754$; $C_2 = (-0.163) + j \cdot (-0.264)$; $\Gamma_L = (-0.276) + j \cdot (0.446) = 0.525 \angle 121.7^\circ$
 c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 146.1^\circ$; $\text{Im}(y_S) = -1.919$; $\theta_{p1} = 117.5^\circ$ or $\theta_{S2} = 12.3^\circ$; $\text{Im}(y_S) = 1.919$; $\theta_{p2} = 62.5^\circ$
 output: $\theta_{L1} = 180.0^\circ$; $\text{Im}(y_L) = -1.233$; $\theta_{p1} = 129.1^\circ$ or $\theta_{L2} = 58.3^\circ$; $\text{Im}(y_L) = 1.233$; $\theta_{p2} = 50.9^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):
 d1) $\theta_{L1} = 180.0^\circ$; $\text{Im}(y_L) = -1.233 + (-1.919) = -3.151$; $\theta_{p1} = 107.6^\circ$; $\theta_{S1} = 146.1^\circ$;
 d2) $\theta_{L2} = 58.3^\circ$; $\text{Im}(y_L) = 1.233 + (-1.919) = -0.686$; $\theta_{p2} = 145.5^\circ$; $\theta_{S1} = 146.1^\circ$;
 d3) $\theta_{L1} = 180.0^\circ$; $\text{Im}(y_L) = -1.233 + (1.919) = 0.686$; $\theta_{p3} = 34.5^\circ$; $\theta_{S2} = 12.3^\circ$;
 d4) $\theta_{L2} = 58.3^\circ$; $\text{Im}(y_L) = 1.233 + (1.919) = 3.151$; $\theta_{p4} = 72.4^\circ$; $\theta_{S2} = 12.3^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 180.0 + 146.1 = 326.1$; $\theta_p = 107.6$; $A \sim 35085.1$
 e2) $\Sigma\theta_s = 58.3 + 146.1 = 204.4$; $\theta_p = 145.5$; $A \sim 29750.0$
 e3) $\Sigma\theta_s = 180.0 + 12.3 = 192.2$; $\theta_p = 34.5$; $A \sim 6624.1$
 e4) $\Sigma\theta_s = 58.3 + 12.3 = 70.6$; $\theta_p = 72.4$; $A \sim 5110.7$
 Smallest substrate area is occupied by solution e4 (d4)

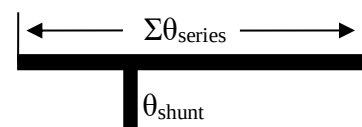

Subject no. 5

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (37.8 - j \cdot 31.0)\Omega = 0.791 + j \cdot 0.649$

2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0244 + j \cdot 0.0340)] / (0.02 + 0.0244 + j \cdot 0.0340)$
 $\Gamma = (-0.432) + j \cdot (-0.435) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.613 \angle -134.8^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

3. a) Lossless coupled line coupler, matched at the input; Isolation $I = 21.70\text{dB}$

$P_{\text{in}} = 1.25\text{mW} = 0.969\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 0.969\text{dBm} - 21.70\text{dB} = -20.73\text{dBm} = 8.451\mu\text{W}$

b) $L_2, C_5/2025$, $\beta = 10^{-C/20} = 0.613$, $Z_{\text{CE}} = 102.09\Omega$, $Z_{\text{CO}} = 24.49\Omega$

4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 72)\Omega} = 60.00\Omega$

b) $Z_L = 72\Omega$ parallel with 1.22nH inductor at $8.8\text{GHz} = 33.66\Omega + j \cdot (35.92)\Omega$

$\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (-53.37)\Omega$

5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).

Valid combinations ($G > 15.75\text{dB}$): $G = G_1 + G_4 = 6.2 + 10.2 = 16.4\text{dB}$; $G = G_2 + G_3 = 8.4 + 9.3 = 17.7\text{dB}$; $G = G_2 + G_4 = 8.4 + 10.2 = 18.6\text{dB}$; $G = G_3 + G_4 = 9.3 + 10.2 = 19.5\text{dB}$;

b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;

From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$

$F_1 = 0.66\text{dB} = 1.164$, $F_2 = 0.81\text{dB} = 1.205$, $F_3 = 1.08\text{dB} = 1.282$, $F_4 = 1.11\text{dB} = 1.291$, $G_1 = 6.2\text{dB} = 4.169$, $G_2 = 8.4\text{dB} = 6.918$; $F(1,4) = 1.164 + (1.291 - 1)/4.169 = 1.234 = 0.91\text{dB}$; $F(2,3) = 1.205 + (1.282 - 1)/6.918 = 1.247 = 0.96\text{dB}$;

$F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4

6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:

$|S_{11}| = 0.530 < 1$; $|S_{22}| = 0.287 < 1$; $K = 1.222 > 1$; $|\Delta| = |(-0.120) + j \cdot (-0.081)| = 0.144 < 1$

b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 13.98 = 11.45\text{dB}$

b_2) Complex calculus from $C9/2025$, $S70$:

$B_1 = 1.178$; $C_1 = (-0.557) + j \cdot (-0.017)$; $\Gamma_S = (-0.717) + j \cdot (0.022) = 0.717 \angle 178.2^\circ$

$B_2 = 0.781$; $C_2 = (-0.124) + j \cdot (-0.318)$; $\Gamma_L = (-0.213) + j \cdot (0.550) = 0.589 \angle 111.2^\circ$

c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines

input: $\theta_{S1} = 158.8^\circ$; $\text{Im}(y_S) = -2.057$; $\theta_{p1} = 115.9^\circ$ or $\theta_{S2} = 23.0^\circ$; $\text{Im}(y_S) = 2.057$; $\theta_{p2} = 64.1^\circ$

output: $\theta_{L1} = 7.5^\circ$; $\text{Im}(y_L) = -1.460$; $\theta_{p1} = 124.4^\circ$ or $\theta_{L2} = 61.3^\circ$; $\text{Im}(y_L) = 1.460$; $\theta_{p2} = 55.6^\circ$

d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):

d1) $\theta_{L1} = 7.5^\circ$; $\text{Im}(y_L) = -1.460 + (-2.057) = -3.517$; $\theta_{p1} = 105.9^\circ$; $\theta_{S1} = 158.8^\circ$;

d2) $\theta_{L2} = 61.3^\circ$; $\text{Im}(y_L) = 1.460 + (-2.057) = -0.597$; $\theta_{p2} = 149.1^\circ$; $\theta_{S1} = 158.8^\circ$;

d3) $\theta_{L1} = 7.5^\circ$; $\text{Im}(y_L) = -1.460 + (2.057) = 0.597$; $\theta_{p3} = 30.9^\circ$; $\theta_{S2} = 23.0^\circ$;

d4) $\theta_{L2} = 61.3^\circ$; $\text{Im}(y_L) = 1.460 + (2.057) = 3.517$; $\theta_{p4} = 74.1^\circ$; $\theta_{S2} = 23.0^\circ$;

e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.


e1) $\Sigma\theta_s = 7.5 + 158.8 = 166.2$; $\theta_p = 105.9$; $A \sim 17600.1$

e2) $\Sigma\theta_s = 61.3 + 158.8 = 220.1$; $\theta_p = 149.1$; $A \sim 32829.2$

e3) $\Sigma\theta_s = 7.5 + 23.0 = 30.4$; $\theta_p = 30.9$; $A \sim 938.9$

e4) $\Sigma\theta_s = 61.3 + 23.0 = 84.3$; $\theta_p = 74.1$; $A \sim 6249.5$

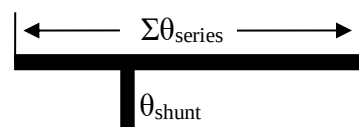Smallest substrate area is occupied by solution e3 (d3)



Subject no. 6

1. $y = Y/Y_0 = Z_0/Z = 65\Omega / (65.1 - j \cdot 61.9)\Omega = 0.524 + j \cdot 0.499$

2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0263 + j \cdot 0.0351)] / (0.02 + 0.0263 + j \cdot 0.0351)$
 $\Gamma = (-0.451) + j \cdot (-0.416) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.614 \angle -137.3^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

3. a) Lossless coupled line coupler, matched at the input; Isolation $I = D + C = 25.55\text{dB}$
 $P_{\text{in}} = 1.20\text{mW} = 0.792\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 0.792\text{dBm} - 25.55\text{dB} = -24.76\text{dBm} = 3.343\mu\text{W}$

b) $L2, C5/2025$, $\beta = 10^{-C/20} = 0.528$, $Z_{\text{CE}} = 89.94\Omega$, $Z_{\text{CO}} = 27.80\Omega$

4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 62)\Omega} = 55.68\Omega$

b) $Z_L = 62\Omega$ parallel with 0.30pF capacitor at $8.2\text{GHz} = 32.32\Omega + j \cdot (-30.97)\Omega$

$\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (47.92)\Omega$

5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).

Valid combinations ($G > 16.70\text{dB}$): $G = G_1 + G_4 = 6.7 + 11.3 = 18.0\text{dB}$; $G = G_2 + G_3 = 7.6 + 9.4 = 17.0\text{dB}$; $G = G_2 + G_4 = 7.6 + 11.3 = 18.9\text{dB}$; $G = G_3 + G_4 = 9.4 + 11.3 = 20.7\text{dB}$;

b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;

From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$

$F_1 = 0.58\text{dB} = 1.143$, $F_2 = 0.83\text{dB} = 1.211$, $F_3 = 0.98\text{dB} = 1.253$, $F_4 = 1.29\text{dB} = 1.346$, $G_1 = 6.7\text{dB} = 4.677$, $G_2 = 7.6\text{dB} = 5.754$; $F(1,4) = 1.143 + (1.346 - 1)/4.677 = 1.217 = 0.85\text{dB}$; $F(2,3) = 1.211 + (1.253 - 1)/5.754 = 1.271 = 1.04\text{dB}$;

$F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4

6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:

$|S_{11}| = 0.532 < 1$; $|S_{22}| = 0.257 < 1$; $K = 1.321 > 1$; $|\Delta| = |(-0.091) + j \cdot (-0.072)| = 0.116 < 1$

b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 11.29 = 10.53\text{dB}$

b_2) Complex calculus from $C9/2025$, $S70$:

$B_1 = 1.204$; $C_1 = (-0.541) + j \cdot (0.149)$; $\Gamma_S = (-0.661) + j \cdot (-0.182) = 0.685 \angle -164.6^\circ$

$B_2 = 0.770$; $C_2 = (-0.149) + j \cdot (-0.281)$; $\Gamma_L = (-0.247) + j \cdot (0.467) = 0.528 \angle 117.9^\circ$

c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines

input: $\theta_{S1} = 148.9^\circ$; $\text{Im}(y_S) = -1.883$; $\theta_{p1} = 118.0^\circ$ or $\theta_{S2} = 15.7^\circ$; $\text{Im}(y_S) = 1.883$; $\theta_{p2} = 62.0^\circ$

output: $\theta_{L1} = 2.0^\circ$; $\text{Im}(y_L) = -1.243$; $\theta_{p1} = 128.8^\circ$ or $\theta_{L2} = 60.1^\circ$; $\text{Im}(y_L) = 1.243$; $\theta_{p2} = 51.2^\circ$

d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):

d1) $\theta_{L1} = 2.0^\circ$; $\text{Im}(y_L) = -1.243 + (-1.883) = -3.127$; $\theta_{p1} = 107.7^\circ$; $\theta_{S1} = 148.9^\circ$;

d2) $\theta_{L2} = 60.1^\circ$; $\text{Im}(y_L) = 1.243 + (-1.883) = -0.640$; $\theta_{p2} = 147.4^\circ$; $\theta_{S1} = 148.9^\circ$;

d3) $\theta_{L1} = 2.0^\circ$; $\text{Im}(y_L) = -1.243 + (1.883) = 0.640$; $\theta_{p3} = 32.6^\circ$; $\theta_{S2} = 15.7^\circ$;

d4) $\theta_{L2} = 60.1^\circ$; $\text{Im}(y_L) = 1.243 + (1.883) = 3.127$; $\theta_{p4} = 72.3^\circ$; $\theta_{S2} = 15.7^\circ$;

e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.


e1) $\Sigma\theta_s = 2.0 + 148.9 = 150.9$; $\theta_p = 107.7$; $A \sim 16261.1$

e2) $\Sigma\theta_s = 60.1 + 148.9 = 209.1$; $\theta_p = 147.4$; $A \sim 30815.5$

e3) $\Sigma\theta_s = 2.0 + 15.7 = 17.7$; $\theta_p = 32.6$; $A \sim 575.7$


e4) $\Sigma\theta_s = 60.1 + 15.7 = 75.8$; $\theta_p = 72.3$; $A \sim 5476.7$

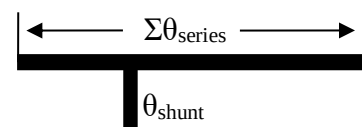Smallest substrate area is occupied by solution e3 (d3)




Subject no. 7

1. $y = Y/Y_0 = Z_0/Z = 95\Omega / (62.7 - j \cdot 64.4)\Omega = 0.737 + j \cdot 0.757$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0295 + j \cdot 0.0280)] / (0.02 + 0.0295 + j \cdot 0.0280)$
 $\Gamma = (-0.388) + j \cdot (-0.346) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.520 \angle -138.2^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless quadrature coupler, matched at the input; Isolation $I = 23.90\text{dB}$
 $P_{\text{in}} = 2.00\text{mW} = 3.010\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 3.010\text{dBm} - 23.90\text{dB} = -20.89\text{dBm} = 8.148\mu\text{W}$
 b) L_2 , C5/2025, $\beta = 10^{-C/20} = 0.546$, $y_2 = 1.194$, $y_1 = 0.652$, $Z_1 = Z_0/y_1 = 76.6\Omega$, $Z_2 = Z_0/y_2 = 41.9\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 44)\Omega} = 46.90\Omega$
 b) $Z_L = 44\Omega$ parallel with 0.35pF capacitor at $7.2\text{GHz} = 29.62\Omega + j \cdot (-20.64)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (34.83)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 15.60\text{dB}$): $G = G_1 + G_4 = 5.5 + 10.6 = 16.1\text{dB}$; $G = G_2 + G_3 = 8.9 + 9.6 = 18.5\text{dB}$; $G = G_2 + G_4 = 8.9 + 10.6 = 19.5\text{dB}$; $G = G_3 + G_4 = 9.6 + 10.6 = 20.2\text{dB}$;
 b) Friis Formula (C10/2025, S50), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.65\text{dB} = 1.161$, $F_2 = 0.86\text{dB} = 1.219$, $F_3 = 0.91\text{dB} = 1.233$, $F_4 = 1.20\text{dB} = 1.318$, $G_1 = 5.5\text{dB} = 3.548$, $G_2 = 8.9\text{dB} = 7.762$; $F(1,4) = 1.161 + (1.318 - 1)/3.548 = 1.251 = 0.97\text{dB}$; $F(2,3) = 1.219 + (1.233 - 1)/7.762 = 1.260 = 1.00\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.615 < 1$; $|S_{22}| = 0.237 < 1$; $K = 1.287 > 1$; $|\Delta| = |(-0.133) + j \cdot (-0.127)| = 0.184 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 8.12 = 9.09\text{dB}$
 b_2) Complex calculus from C9/2025, S70:
 $B_1 = 1.288$; $C_1 = (-0.379) + j \cdot (0.486)$; $\Gamma_S = (-0.455) + j \cdot (-0.583) = 0.740 \angle -128.0^\circ$
 $B_2 = 0.644$; $C_2 = (-0.215) + j \cdot (-0.148)$; $\Gamma_L = (-0.421) + j \cdot (0.290) = 0.511 \angle 145.4^\circ$
 c) Complex calculus from C7/2025, S112, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 132.8^\circ$; $\text{Im}(y_S) = -2.198$; $\theta_{p1} = 114.5^\circ$ or $\theta_{S2} = 175.1^\circ$; $\text{Im}(y_S) = 2.198$; $\theta_{p2} = 65.5^\circ$
 output: $\theta_{L1} = 167.7^\circ$; $\text{Im}(y_L) = -1.190$; $\theta_{p1} = 130.0^\circ$ or $\theta_{L2} = 46.9^\circ$; $\text{Im}(y_L) = 1.190$; $\theta_{p2} = 50.0^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, C12/2025, S140÷156):
 d1) $\theta_{L1} = 167.7^\circ$; $\text{Im}(y_L) = -1.190 + (-2.198) = -3.388$; $\theta_{p1} = 106.4^\circ$; $\theta_{S1} = 132.8^\circ$;
 d2) $\theta_{L2} = 46.9^\circ$; $\text{Im}(y_L) = 1.190 + (-2.198) = -1.008$; $\theta_{p2} = 134.8^\circ$; $\theta_{S1} = 132.8^\circ$;
 d3) $\theta_{L1} = 167.7^\circ$; $\text{Im}(y_L) = -1.190 + (2.198) = 1.008$; $\theta_{p3} = 45.2^\circ$; $\theta_{S2} = 175.1^\circ$;
 d4) $\theta_{L2} = 46.9^\circ$; $\text{Im}(y_L) = 1.190 + (2.198) = 3.388$; $\theta_{p4} = 73.6^\circ$; $\theta_{S2} = 175.1^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 167.7 + 132.8 = 300.5$; $\theta_p = 106.4$; $A \sim 31984.5$
 e2) $\Sigma\theta_s = 46.9 + 132.8 = 179.7$; $\theta_p = 134.8$; $A \sim 24221.7$
 e3) $\Sigma\theta_s = 167.7 + 175.1 = 342.8$; $\theta_p = 45.2$; $A \sim 15505.1$
 e4) $\Sigma\theta_s = 46.9 + 175.1 = 222.0$; $\theta_p = 73.6$; $A \sim 16331.6$
 Smallest substrate area is occupied by solution e3 (d3)

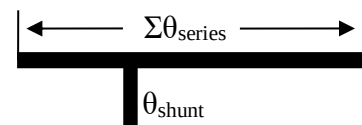


Subject no. 8

1. $y = Y/Y_0 = Z_0/Z = 30\Omega / (51.3 + j \cdot 64.0)\Omega = 0.229 - j \cdot 0.285$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0216 + j \cdot 0.0125)] / (0.02 + 0.0216 + j \cdot 0.0125)$
 $\Gamma = (-0.118) + j \cdot (-0.265) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.290 \angle -114.0^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless ring coupler, matched at the input; Isolation $I = D + C = 27.95\text{dB}$
 $P_{\text{in}} = 1.15\text{mW} = 0.607\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 0.607\text{dBm} - 27.95\text{dB} = -27.34\text{dBm} = 1.844\mu\text{W}$
 b) $L2, C5/2025$, $\beta = 10^{-C/20} = 0.449$, $y_1 = 0.449$, $y_2 = 0.893$, $Z_1 = Z_0/y_1 = 111.3\Omega$, $Z_2 = Z_0/y_2 = 56.0\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 48)\Omega} = 48.99\Omega$
 b) $Z_L = 48\Omega$ series with 0.31pF capacitor at $8.4\text{GHz} = 48.00\Omega + j \cdot (-61.12)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 19.07\Omega + j \cdot (24.29)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 15.30\text{dB}$): $G = G_1 + G_4 = 5.1 + 11.0 = 16.1\text{dB}$; $G = G_2 + G_3 = 7.4 + 9.8 = 17.2\text{dB}$; $G = G_2 + G_4 = 7.4 + 11.0 = 18.4\text{dB}$; $G = G_3 + G_4 = 9.8 + 11.0 = 20.8\text{dB}$;
 b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.57\text{dB} = 1.140$, $F_2 = 0.74\text{dB} = 1.186$, $F_3 = 1.00\text{dB} = 1.259$, $F_4 = 1.12\text{dB} = 1.294$, $G_1 = 5.1\text{dB} = 3.236$, $G_2 = 7.4\text{dB} = 5.495$; $F(1,4) = 1.140 + (1.294 - 1)/3.236 = 1.231 = 0.90\text{dB}$; $F(2,3) = 1.186 + (1.259 - 1)/5.495 = 1.239 = 0.93\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.559 < 1$; $|S_{22}| = 0.230 < 1$; $K = 1.318 > 1$; $|\Delta| = |(-0.096) + j \cdot (-0.094)| = 0.134 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 9.39 = 9.73\text{dB}$
 b_2) Complex calculus from $C9/2025$, $S70$:
 $B_1 = 1.242$; $C_1 = (-0.484) + j \cdot (0.325)$; $\Gamma_S = (-0.581) + j \cdot (-0.390) = 0.700 \angle -146.1^\circ$
 $B_2 = 0.722$; $C_2 = (-0.186) + j \cdot (-0.225)$; $\Gamma_L = (-0.325) + j \cdot (0.392) = 0.509 \angle 129.6^\circ$
 c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 140.3^\circ$; $\text{Im}(y_S) = -1.960$; $\theta_{p1} = 117.0^\circ$ or $\theta_{S2} = 5.8^\circ$; $\text{Im}(y_S) = 1.960$; $\theta_{p2} = 63.0^\circ$
 output: $\theta_{L1} = 175.5^\circ$; $\text{Im}(y_L) = -1.182$; $\theta_{p1} = 130.2^\circ$ or $\theta_{L2} = 54.9^\circ$; $\text{Im}(y_L) = 1.182$; $\theta_{p2} = 49.8^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):
 d1) $\theta_{L1} = 175.5^\circ$; $\text{Im}(y_L) = -1.182 + (-1.960) = -3.142$; $\theta_{p1} = 107.7^\circ$; $\theta_{S1} = 140.3^\circ$;
 d2) $\theta_{L2} = 54.9^\circ$; $\text{Im}(y_L) = 1.182 + (-1.960) = -0.777$; $\theta_{p2} = 142.1^\circ$; $\theta_{S1} = 140.3^\circ$;
 d3) $\theta_{L1} = 175.5^\circ$; $\text{Im}(y_L) = -1.182 + (1.960) = 0.777$; $\theta_{p3} = 37.9^\circ$; $\theta_{S2} = 5.8^\circ$;
 d4) $\theta_{L2} = 54.9^\circ$; $\text{Im}(y_L) = 1.182 + (1.960) = 3.142$; $\theta_{p4} = 72.3^\circ$; $\theta_{S2} = 5.8^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 175.5 + 140.3 = 315.7$; $\theta_p = 107.7$; $A \sim 33991.4$
 e2) $\Sigma\theta_s = 54.9 + 140.3 = 195.2$; $\theta_p = 142.1$; $A \sim 27740.4$
 e3) $\Sigma\theta_s = 175.5 + 5.8 = 181.3$; $\theta_p = 37.9$; $A \sim 6863.9$
 e4) $\Sigma\theta_s = 54.9 + 5.8 = 60.7$; $\theta_p = 72.3$; $A \sim 4394.1$
 Smallest substrate area is occupied by solution e4 (d4)

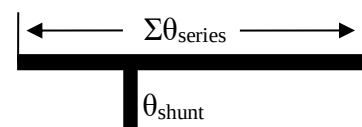

Subject no. 9

1. $y = Y/Y_0 = Z_0/Z = 85\Omega / (67.7 - j \cdot 54.8)\Omega = 0.759 + j \cdot 0.614$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0369 - j \cdot 0.0295)] / (0.02 + 0.0369 - j \cdot 0.0295)$
 $\Gamma = (-0.446) + j \cdot (0.287) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.530 \angle 147.2^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless ring coupler, matched at the input; Isolation $I = D + C = 26.05\text{dB}$
 $P_{\text{in}} = 1.95\text{mW} = 2.900\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 2.900\text{dBm} - 26.05\text{dB} = -23.15\text{dBm} = 4.842\mu\text{W}$
 b) $L_2, C_5/2025$, $\beta = 10^{-C/20} = 0.627$, $y_1 = 0.627$, $y_2 = 0.779$, $Z_1 = Z_0/y_1 = 79.7\Omega$, $Z_2 = Z_0/y_2 = 64.2\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 64)}\Omega = 56.57\Omega$
 b) $Z_L = 64\Omega$ parallel with 1.17nH inductor at $8.9\text{GHz} = 32.71\Omega + j \cdot (31.99)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (-48.91)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 15.15\text{dB}$): $G = G_1 + G_4 = 5.4 + 10.3 = 15.7\text{dB}$; $G = G_2 + G_3 = 8.2 + 9.4 = 17.6\text{dB}$; $G = G_2 + G_4 = 8.2 + 10.3 = 18.5\text{dB}$; $G = G_3 + G_4 = 9.4 + 10.3 = 19.7\text{dB}$;
 b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.54\text{dB} = 1.132$, $F_2 = 0.84\text{dB} = 1.213$, $F_3 = 0.91\text{dB} = 1.233$, $F_4 = 1.25\text{dB} = 1.334$, $G_1 = 5.4\text{dB} = 3.467$, $G_2 = 8.2\text{dB} = 6.607$; $F(1,4) = 1.132 + (1.334 - 1)/3.467 = 1.229 = 0.89\text{dB}$; $F(2,3) = 1.213 + (1.233 - 1)/6.607 = 1.264 = 1.02\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.530 < 1$; $|S_{22}| = 0.290 < 1$; $K = 1.213 > 1$; $|\Delta| = |(-0.123) + j \cdot (-0.084)| = 0.149 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 14.28 = 11.55\text{dB}$
 b_2) Complex calculus from $C9/2025$, $S70$:
 $B_1 = 1.175$; $C_1 = (-0.556) + j \cdot (-0.034)$; $\Gamma_S = (-0.719) + j \cdot (0.043) = 0.721 \angle 176.5^\circ$
 $B_2 = 0.781$; $C_2 = (-0.121) + j \cdot (-0.322)$; $\Gamma_L = (-0.209) + j \cdot (0.558) = 0.596 \angle 110.6^\circ$
 c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 159.8^\circ$; $\text{Im}(y_S) = -2.079$; $\theta_{p1} = 115.7^\circ$ or $\theta_{S2} = 23.7^\circ$; $\text{Im}(y_S) = 2.079$; $\theta_{p2} = 64.3^\circ$
 output: $\theta_{L1} = 8.0^\circ$; $\text{Im}(y_L) = -1.484$; $\theta_{p1} = 124.0^\circ$ or $\theta_{L2} = 61.4^\circ$; $\text{Im}(y_L) = 1.484$; $\theta_{p2} = 56.0^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):
 d1) $\theta_{L1} = 8.0^\circ$; $\text{Im}(y_L) = -1.484 + (-2.079) = -3.563$; $\theta_{p1} = 105.7^\circ$; $\theta_{S1} = 159.8^\circ$;
 d2) $\theta_{L2} = 61.4^\circ$; $\text{Im}(y_L) = 1.484 + (-2.079) = -0.594$; $\theta_{p2} = 149.3^\circ$; $\theta_{S1} = 159.8^\circ$;
 d3) $\theta_{L1} = 8.0^\circ$; $\text{Im}(y_L) = -1.484 + (2.079) = 0.594$; $\theta_{p3} = 30.7^\circ$; $\theta_{S2} = 23.7^\circ$;
 d4) $\theta_{L2} = 61.4^\circ$; $\text{Im}(y_L) = 1.484 + (2.079) = 3.563$; $\theta_{p4} = 74.3^\circ$; $\theta_{S2} = 23.7^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 8.0 + 159.8 = 167.8$; $\theta_p = 105.7$; $A \sim 17731.5$
 e2) $\Sigma\theta_s = 61.4 + 159.8 = 221.2$; $\theta_p = 149.3$; $A \sim 33019.7$
 e3) $\Sigma\theta_s = 8.0 + 23.7 = 31.7$; $\theta_p = 30.7$; $A \sim 973.6$
 e4) $\Sigma\theta_s = 61.4 + 23.7 = 85.1$; $\theta_p = 74.3$; $A \sim 6325.1$
 Smallest substrate area is occupied by solution e3 (d3)

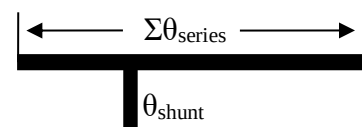

Subject no. 10

1. $y = Y/Y_0 = Z_0/Z = 95\Omega / (52.5 - j \cdot 67.4)\Omega = 0.683 + j \cdot 0.877$

2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0355 + j \cdot 0.0217)] / (0.02 + 0.0355 + j \cdot 0.0217)$
 $\Gamma = (-0.375) + j \cdot (-0.244) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.448\angle -146.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

3. a) Lossless coupled line coupler, matched at the input; Isolation $I = 24.90\text{dB}$

$P_{\text{in}} = 3.80\text{mW} = 5.798\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 5.798\text{dBm} - 24.90\text{dB} = -19.10\text{dBm} = 12.297\mu\text{W}$

b) $L_2, C_5/2025$, $\beta = 10^{-C/20} = 0.572$, $Z_{\text{CE}} = 95.84\Omega$, $Z_{\text{CO}} = 26.08\Omega$

4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 29)\Omega} = 38.08\Omega$

b) $Z_L = 29\Omega$ parallel with 1.16nH inductor at $6.9\text{GHz} = 21.76\Omega + j \cdot (12.55)\Omega$

$\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (-28.83)\Omega$

5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).

Valid combinations ($G > 15.35\text{dB}$): $G = G_1 + G_4 = 5.3 + 10.8 = 16.1\text{dB}$; $G = G_2 + G_3 = 8.0 + 9.4 = 17.4\text{dB}$; $G = G_2 + G_4 = 8.0 + 10.8 = 18.8\text{dB}$; $G = G_3 + G_4 = 9.4 + 10.8 = 20.2\text{dB}$;

b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;

From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$

$F_1 = 0.65\text{dB} = 1.161$, $F_2 = 0.86\text{dB} = 1.219$, $F_3 = 1.00\text{dB} = 1.259$, $F_4 = 1.16\text{dB} = 1.306$, $G_1 = 5.3\text{dB} = 3.388$, $G_2 = 8.0\text{dB} = 6.310$; $F(1,4) = 1.161 + (1.306 - 1)/3.388 = 1.252 = 0.98\text{dB}$; $F(2,3) = 1.219 + (1.259 - 1)/6.310 = 1.268 = 1.03\text{dB}$;

$F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4

6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:

$|S_{11}| = 0.550 < 1$; $|S_{22}| = 0.320 < 1$; $K = 1.191 > 1$; $|\Delta| = |(-0.137) + j \cdot (-0.101)| = 0.170 < 1$

b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 17.58 = 12.45\text{dB}$

b_2) Complex calculus from $C9/2025$, $S70$:

$B_1 = 1.171$; $C_1 = (-0.525) + j \cdot (-0.196)$; $\Gamma_S = (-0.695) + j \cdot (0.260) = 0.742\angle 159.5^\circ$

$B_2 = 0.771$; $C_2 = (-0.081) + j \cdot (-0.337)$; $\Gamma_L = (-0.146) + j \cdot (0.606) = 0.624\angle 103.5^\circ$

c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines

input: $\theta_{S1} = 169.2^\circ$; $\text{Im}(y_S) = -2.215$; $\theta_{p1} = 114.3^\circ$ or $\theta_{S2} = 31.3^\circ$; $\text{Im}(y_S) = 2.215$; $\theta_{p2} = 65.7^\circ$

output: $\theta_{L1} = 12.5^\circ$; $\text{Im}(y_L) = -1.595$; $\theta_{p1} = 122.1^\circ$ or $\theta_{L2} = 64.0^\circ$; $\text{Im}(y_L) = 1.595$; $\theta_{p2} = 57.9^\circ$

d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025$, $S140 \div 156$):

d1) $\theta_{L1} = 12.5^\circ$; $\text{Im}(y_L) = -1.595 + (-2.215) = -3.810$; $\theta_{p1} = 104.7^\circ$; $\theta_{S1} = 169.2^\circ$;

d2) $\theta_{L2} = 64.0^\circ$; $\text{Im}(y_L) = 1.595 + (-2.215) = -0.619$; $\theta_{p2} = 148.2^\circ$; $\theta_{S1} = 169.2^\circ$;

d3) $\theta_{L1} = 12.5^\circ$; $\text{Im}(y_L) = -1.595 + (2.215) = 0.619$; $\theta_{p3} = 31.8^\circ$; $\theta_{S2} = 31.3^\circ$;

d4) $\theta_{L2} = 64.0^\circ$; $\text{Im}(y_L) = 1.595 + (2.215) = 3.810$; $\theta_{p4} = 75.3^\circ$; $\theta_{S2} = 31.3^\circ$;

e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.


e1) $\Sigma\theta_s = 12.5 + 169.2 = 181.7$; $\theta_p = 104.7$; $A \sim 19028.6$

e2) $\Sigma\theta_s = 64.0 + 169.2 = 233.2$; $\theta_p = 148.2$; $A \sim 34560.6$

e3) $\Sigma\theta_s = 12.5 + 31.3 = 43.8$; $\theta_p = 31.8$; $A \sim 1392.0$

e4) $\Sigma\theta_s = 64.0 + 31.3 = 95.2$; $\theta_p = 75.3$; $A \sim 7170.8$

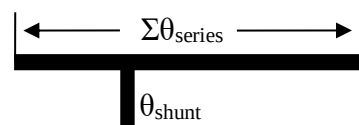Smallest substrate area is occupied by solution e3 (d3)



Subject no. 11

1. $y = Y/Y_0 = Z_0/Z = 60\Omega / (41.2 - j \cdot 46.1)\Omega = 0.647 + j \cdot 0.724$

2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0399 + j \cdot 0.0125)] / (0.02 + 0.0399 + j \cdot 0.0125)$
 $\Gamma = (-0.360) + j \cdot (-0.134) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.384 \angle -159.7^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

3. a) Lossless coupled line coupler, matched at the input; Isolation $I = 21.10\text{dB}$

$P_{\text{in}} = 4.05\text{mW} = 6.075\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 6.075\text{dBm} - 21.10\text{dB} = -15.03\text{dBm} = 31.438\mu\text{W}$

b) $L2, C5/2025$, $\beta = 10^{-C/20} = 0.550$, $Z_{\text{CE}} = 92.74\Omega$, $Z_{\text{CO}} = 26.96\Omega$

4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 62)\Omega} = 55.68\Omega$

b) $Z_L = 62\Omega$ parallel with 0.26pF capacitor at $9.9\text{GHz} = 30.92\Omega + j \cdot (-31.00)\Omega$

$\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (50.14)\Omega$

5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).

Valid combinations ($G > 16.70\text{dB}$): $G = G_1 + G_4 = 5.5 + 11.6 = 17.1\text{dB}$; $G = G_2 + G_3 = 8.5 + 9.8 = 18.3\text{dB}$; $G = G_2 + G_4 = 8.5 + 11.6 = 20.1\text{dB}$; $G = G_3 + G_4 = 9.8 + 11.6 = 21.4\text{dB}$;

b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;

From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$

$F_1 = 0.68\text{dB} = 1.169$, $F_2 = 0.70\text{dB} = 1.175$, $F_3 = 1.01\text{dB} = 1.262$, $F_4 = 1.20\text{dB} = 1.318$, $G_1 = 5.5\text{dB} = 3.548$, $G_2 = 8.5\text{dB} = 7.079$; $F(1,4) = 1.169 + (1.318 - 1)/3.548 = 1.259 = 1.00\text{dB}$; $F(2,3) = 1.175 + (1.262 - 1)/7.079 = 1.220 = 0.86\text{dB}$;

$F(1,4) > F(2,3) \rightarrow$ For minimal noise factor we must use devices 2,3

6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:

$|S_{11}| = 0.542 < 1$; $|S_{22}| = 0.308 < 1$; $K = 1.197 > 1$; $|\Delta| = |(-0.131) + j \cdot (-0.091)| = 0.159 < 1$

b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 16.24 = 12.11\text{dB}$

b_2) Complex calculus from $C9/2025$, $S70$:

$B_1 = 1.174$; $C_1 = (-0.544) + j \cdot (-0.132)$; $\Gamma_S = (-0.715) + j \cdot (0.174) = 0.735 \angle 166.3^\circ$

$B_2 = 0.776$; $C_2 = (-0.098) + j \cdot (-0.332)$; $\Gamma_L = (-0.174) + j \cdot (0.590) = 0.615 \angle 106.4^\circ$

c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines

input: $\theta_{S1} = 165.5^\circ$; $\text{Im}(y_S) = -2.170$; $\theta_{p1} = 114.7^\circ$ or $\theta_{S2} = 28.2^\circ$; $\text{Im}(y_S) = 2.170$; $\theta_{p2} = 65.3^\circ$

output: $\theta_{L1} = 10.8^\circ$; $\text{Im}(y_L) = -1.561$; $\theta_{p1} = 122.7^\circ$ or $\theta_{L2} = 62.8^\circ$; $\text{Im}(y_L) = 1.561$; $\theta_{p2} = 57.3^\circ$

d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025$, $S140 \div 156$):

d1) $\theta_{L1} = 10.8^\circ$; $\text{Im}(y_L) = -1.561 + (-2.170) = -3.731$; $\theta_{p1} = 105.0^\circ$; $\theta_{S1} = 165.5^\circ$;

d2) $\theta_{L2} = 62.8^\circ$; $\text{Im}(y_L) = 1.561 + (-2.170) = -0.610$; $\theta_{p2} = 148.6^\circ$; $\theta_{S1} = 165.5^\circ$;

d3) $\theta_{L1} = 10.8^\circ$; $\text{Im}(y_L) = -1.561 + (2.170) = 0.610$; $\theta_{p3} = 31.4^\circ$; $\theta_{S2} = 28.2^\circ$;

d4) $\theta_{L2} = 62.8^\circ$; $\text{Im}(y_L) = 1.561 + (2.170) = 3.731$; $\theta_{p4} = 75.0^\circ$; $\theta_{S2} = 28.2^\circ$;

e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.


e1) $\Sigma\theta_s = 10.8 + 165.5 = 176.3$; $\theta_p = 105.0$; $A \sim 18509.9$

e2) $\Sigma\theta_s = 62.8 + 165.5 = 228.3$; $\theta_p = 148.6$; $A \sim 33934.3$

e3) $\Sigma\theta_s = 10.8 + 28.2 = 38.9$; $\theta_p = 31.4$; $A \sim 1221.5$


e4) $\Sigma\theta_s = 62.8 + 28.2 = 91.0$; $\theta_p = 75.0$; $A \sim 6822.6$

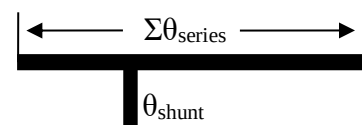Smallest substrate area is occupied by solution e3 (d3)




Subject no. 12

1. $y = Y/Y_0 = Z_0/Z = 35\Omega / (34.3 + j \cdot 39.1)\Omega = 0.444 - j \cdot 0.506$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0131 - j \cdot 0.0240)] / (0.02 + 0.0131 - j \cdot 0.0240)$
 $\Gamma = (-0.208) + j \cdot (0.574) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.611 \angle 109.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless ring coupler, matched at the input; Isolation $I = D + C = 25.15\text{dB}$
 $P_{\text{in}} = 2.65\text{mW} = 4.232\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 4.232\text{dBm} - 25.15\text{dB} = -20.92\text{dBm} = 8.096\mu\text{W}$
 b) $L2, C5/2025$, $\beta = 10^{-C/20} = 0.599$, $y_1 = 0.599$, $y_2 = 0.801$, $Z_1 = Z_0/y_1 = 83.5\Omega$, $Z_2 = Z_0/y_2 = 62.4\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 73)}\Omega = 60.42\Omega$
 b) $Z_L = 73\Omega$ series with 0.90nH inductor at $7.6\text{GHz} = 73.00\Omega + j \cdot (42.98)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 37.13\Omega + j \cdot (-21.86)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 15.95\text{dB}$): $G = G_1 + G_4 = 6.6 + 11.7 = 18.3\text{dB}$; $G = G_2 + G_3 = 8.8 + 8.9 = 17.7\text{dB}$; $G = G_2 + G_4 = 8.8 + 11.7 = 20.5\text{dB}$; $G = G_3 + G_4 = 8.9 + 11.7 = 20.6\text{dB}$;
 b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.50\text{dB} = 1.122$, $F_2 = 0.73\text{dB} = 1.183$, $F_3 = 0.99\text{dB} = 1.256$, $F_4 = 1.26\text{dB} = 1.337$, $G_1 = 6.6\text{dB} = 4.571$, $G_2 = 8.8\text{dB} = 7.586$; $F(1,4) = 1.122 + (1.337 - 1)/4.571 = 1.196 = 0.78\text{dB}$; $F(2,3) = 1.183 + (1.256 - 1)/7.586 = 1.227 = 0.89\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.590 < 1$; $|S_{22}| = 0.232 < 1$; $K = 1.339 > 1$; $|\Delta| = |(-0.108) + j \cdot (-0.113)| = 0.156 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 8.32 = 9.20\text{dB}$
 b_2) Complex calculus from $C9/2025$, $S70$:
 $B_1 = 1.270$; $C_1 = (-0.415) + j \cdot (0.434)$; $\Gamma_S = (-0.493) + j \cdot (-0.515) = 0.713 \angle -133.8^\circ$
 $B_2 = 0.681$; $C_2 = (-0.208) + j \cdot (-0.173)$; $\Gamma_L = (-0.380) + j \cdot (0.315) = 0.494 \angle 140.3^\circ$
 c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 134.6^\circ$; $\text{Im}(y_S) = -2.034$; $\theta_{p1} = 116.2^\circ$ or $\theta_{S2} = 179.1^\circ$; $\text{Im}(y_S) = 2.034$; $\theta_{p2} = 63.8^\circ$
 output: $\theta_{L1} = 169.6^\circ$; $\text{Im}(y_L) = -1.137$; $\theta_{p1} = 131.3^\circ$ or $\theta_{L2} = 50.0^\circ$; $\text{Im}(y_L) = 1.137$; $\theta_{p2} = 48.7^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):
 d1) $\theta_{L1} = 169.6^\circ$; $\text{Im}(y_L) = -1.137 + (-2.034) = -3.170$; $\theta_{p1} = 107.5^\circ$; $\theta_{S1} = 134.6^\circ$;
 d2) $\theta_{L2} = 50.0^\circ$; $\text{Im}(y_L) = 1.137 + (-2.034) = -0.897$; $\theta_{p2} = 138.1^\circ$; $\theta_{S1} = 134.6^\circ$;
 d3) $\theta_{L1} = 169.6^\circ$; $\text{Im}(y_L) = -1.137 + (2.034) = 0.897$; $\theta_{p3} = 41.9^\circ$; $\theta_{S2} = 179.1^\circ$;
 d4) $\theta_{L2} = 50.0^\circ$; $\text{Im}(y_L) = 1.137 + (2.034) = 3.170$; $\theta_{p4} = 72.5^\circ$; $\theta_{S2} = 179.1^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 169.6 + 134.6 = 304.3$; $\theta_p = 107.5$; $A \sim 32709.4$
 e2) $\Sigma\theta_s = 50.0 + 134.6 = 184.6$; $\theta_p = 138.1$; $A \sim 25500.5$
 e3) $\Sigma\theta_s = 169.6 + 179.1 = 348.8$; $\theta_p = 41.9$; $A \sim 14611.6$
 e4) $\Sigma\theta_s = 50.0 + 179.1 = 229.2$; $\theta_p = 72.5$; $A \sim 16613.0$
 Smallest substrate area is occupied by solution e3 (d3)

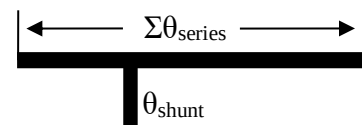


Subject no. 13

1. $y = Y/Y_0 = Z_0/Z = 55\Omega / (36.5 + j \cdot 58.2)\Omega = 0.425 - j \cdot 0.678$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0387 + j \cdot 0.0282)] / (0.02 + 0.0387 + j \cdot 0.0282)$
 $\Gamma = (-0.446) + j \cdot (-0.266) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.520 \angle -149.2^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless coupled line coupler, matched at the input; Isolation $I = D + C = 28.55\text{dB}$
 $P_{\text{in}} = 3.20\text{mW} = 5.051\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 5.051\text{dBm} - 28.55\text{dB} = -23.50\text{dBm} = 4.468\mu\text{W}$
 b) $L_2, C_5/2025$, $\beta = 10^{-C/20} = 0.540$, $Z_{\text{CE}} = 91.50\Omega$, $Z_{\text{CO}} = 27.32\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 72)\Omega} = 60.00\Omega$
 b) $Z_L = 72\Omega$ parallel with 1.11nH inductor at $7.1\text{GHz} = 23.12\Omega + j \cdot (33.62)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (-72.70)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 15.05\text{dB}$): $G = G_1 + G_4 = 5.2 + 11.2 = 16.4\text{dB}$; $G = G_2 + G_3 = 7.3 + 8.4 = 15.7\text{dB}$; $G = G_2 + G_4 = 7.3 + 11.2 = 18.5\text{dB}$; $G = G_3 + G_4 = 8.4 + 11.2 = 19.6\text{dB}$;
 b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.67\text{dB} = 1.167$, $F_2 = 0.79\text{dB} = 1.199$, $F_3 = 1.01\text{dB} = 1.262$, $F_4 = 1.12\text{dB} = 1.294$, $G_1 = 5.2\text{dB} = 3.311$, $G_2 = 7.3\text{dB} = 5.370$; $F(1,4) = 1.167 + (1.294 - 1)/3.311 = 1.256 = 0.99\text{dB}$; $F(2,3) = 1.199 + (1.262 - 1)/5.370 = 1.254 = 0.98\text{dB}$;
 $F(1,4) > F(2,3) \rightarrow$ For minimal noise factor we must use devices 2,3
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.532 < 1$; $|S_{22}| = 0.293 < 1$; $K = 1.209 > 1$; $|\Delta| = |(-0.124) + j \cdot (-0.084)| = 0.150 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 14.60 = 11.64\text{dB}$
 b_2) Complex calculus from $C9/2025$, $S70$:
 $B_1 = 1.175$; $C_1 = (-0.556) + j \cdot (-0.050)$; $\Gamma_S = (-0.720) + j \cdot (0.065) = 0.723 \angle 174.8^\circ$
 $B_2 = 0.780$; $C_2 = (-0.117) + j \cdot (-0.324)$; $\Gamma_L = (-0.204) + j \cdot (0.564) = 0.600 \angle 109.9^\circ$
 c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 160.7^\circ$; $\text{Im}(y_S) = -2.096$; $\theta_{p1} = 115.5^\circ$ or $\theta_{S2} = 24.4^\circ$; $\text{Im}(y_S) = 2.096$; $\theta_{p2} = 64.5^\circ$
 output: $\theta_{L1} = 8.5^\circ$; $\text{Im}(y_L) = -1.499$; $\theta_{p1} = 123.7^\circ$ or $\theta_{L2} = 61.6^\circ$; $\text{Im}(y_L) = 1.499$; $\theta_{p2} = 56.3^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):
 d1) $\theta_{L1} = 8.5^\circ$; $\text{Im}(y_L) = -1.499 + (-2.096) = -3.594$; $\theta_{p1} = 105.5^\circ$; $\theta_{S1} = 160.7^\circ$;
 d2) $\theta_{L2} = 61.6^\circ$; $\text{Im}(y_L) = 1.499 + (-2.096) = -0.597$; $\theta_{p2} = 149.2^\circ$; $\theta_{S1} = 160.7^\circ$;
 d3) $\theta_{L1} = 8.5^\circ$; $\text{Im}(y_L) = -1.499 + (2.096) = 0.597$; $\theta_{p3} = 30.8^\circ$; $\theta_{S2} = 24.4^\circ$;
 d4) $\theta_{L2} = 61.6^\circ$; $\text{Im}(y_L) = 1.499 + (2.096) = 3.594$; $\theta_{p4} = 74.5^\circ$; $\theta_{S2} = 24.4^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 8.5 + 160.7 = 169.2$; $\theta_p = 105.5$; $A \sim 17861.4$
 e2) $\Sigma\theta_s = 61.6 + 160.7 = 222.4$; $\theta_p = 149.2$; $A \sim 33170.8$
 e3) $\Sigma\theta_s = 8.5 + 24.4 = 32.9$; $\theta_p = 30.8$; $A \sim 1014.2$
 e4) $\Sigma\theta_s = 61.6 + 24.4 = 86.0$; $\theta_p = 74.5$; $A \sim 6406.1$
 Smallest substrate area is occupied by solution e3 (d3)

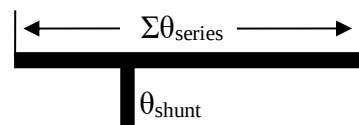


Subject no. 14

1. $y = Y/Y_0 = Z_0/Z = 65\Omega / (50.9 + j \cdot 56.6)\Omega = 0.571 - j \cdot 0.635$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0364 - j \cdot 0.0144)] / (0.02 + 0.0364 - j \cdot 0.0144)$
 $\Gamma = (-0.334) + j \cdot (0.170) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.375 \angle 153.0^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless quadrature coupler, matched at the input; Isolation $I = D + C = 29.25\text{dB}$
 $P_{\text{in}} = 2.45\text{mW} = 3.892\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 3.892\text{dBm} - 29.25\text{dB} = -25.36\text{dBm} = 2.912\mu\text{W}$
 b) L_2 , C5/2025, $\beta = 10^{-C/20} = 0.528$, $y_2 = 1.177$, $y_1 = 0.621$, $Z_1 = Z_0/y_1 = 80.5\Omega$, $Z_2 = Z_0/y_2 = 42.5\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 54)\Omega} = 51.96\Omega$
 b) $Z_L = 54\Omega$ parallel with 0.87nH inductor at $9.6\text{GHz} = 26.23\Omega + j \cdot (26.99)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (-51.45)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 14.15\text{dB}$): $G = G_1 + G_4 = 5.1 + 11.1 = 16.2\text{dB}$; $G = G_2 + G_3 = 7.4 + 9.0 = 16.4\text{dB}$; $G = G_2 + G_4 = 7.4 + 11.1 = 18.5\text{dB}$; $G = G_3 + G_4 = 9.0 + 11.1 = 20.1\text{dB}$;
 b) Friis Formula (C10/2025, S50), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.55\text{dB} = 1.135$, $F_2 = 0.83\text{dB} = 1.211$, $F_3 = 0.91\text{dB} = 1.233$, $F_4 = 1.18\text{dB} = 1.312$, $G_1 = 5.1\text{dB} = 3.236$, $G_2 = 7.4\text{dB} = 5.495$; $F(1,4) = 1.135 + (1.312 - 1)/3.236 = 1.231 = 0.90\text{dB}$; $F(2,3) = 1.211 + (1.233 - 1)/5.495 = 1.267 = 1.03\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.544 < 1$; $|S_{22}| = 0.239 < 1$; $K = 1.307 > 1$; $|\Delta| = |(-0.093) + j \cdot (-0.084)| = 0.126 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 10.31 = 10.13\text{dB}$
 b_2) Complex calculus from C9/2025, S70:
 $B_1 = 1.223$; $C_1 = (-0.520) + j \cdot (0.241)$; $\Gamma_S = (-0.630) + j \cdot (-0.292) = 0.695 \angle -155.1^\circ$
 $B_2 = 0.745$; $C_2 = (-0.168) + j \cdot (-0.255)$; $\Gamma_L = (-0.287) + j \cdot (0.435) = 0.522 \angle 123.4^\circ$
 c) Complex calculus from C7/2025, S112, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 144.6^\circ$; $\text{Im}(y_S) = -1.933$; $\theta_{p1} = 117.4^\circ$ or $\theta_{S2} = 10.6^\circ$; $\text{Im}(y_S) = 1.933$; $\theta_{p2} = 62.6^\circ$
 output: $\theta_{L1} = 179.0^\circ$; $\text{Im}(y_L) = -1.223$; $\theta_{p1} = 129.3^\circ$ or $\theta_{L2} = 57.6^\circ$; $\text{Im}(y_L) = 1.223$; $\theta_{p2} = 50.7^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, C12/2025, S140÷156):
 d1) $\theta_{L1} = 179.0^\circ$; $\text{Im}(y_L) = -1.223 + (-1.933) = -3.155$; $\theta_{p1} = 107.6^\circ$; $\theta_{S1} = 144.6^\circ$;
 d2) $\theta_{L2} = 57.6^\circ$; $\text{Im}(y_L) = 1.223 + (-1.933) = -0.710$; $\theta_{p2} = 144.6^\circ$; $\theta_{S1} = 144.6^\circ$;
 d3) $\theta_{L1} = 179.0^\circ$; $\text{Im}(y_L) = -1.223 + (1.933) = 0.710$; $\theta_{p3} = 35.4^\circ$; $\theta_{S2} = 10.6^\circ$;
 d4) $\theta_{L2} = 57.6^\circ$; $\text{Im}(y_L) = 1.223 + (1.933) = 3.155$; $\theta_{p4} = 72.4^\circ$; $\theta_{S2} = 10.6^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 179.0 + 144.6 = 323.6$; $\theta_p = 107.6$; $A \sim 34811.8$
 e2) $\Sigma\theta_s = 57.6 + 144.6 = 202.1$; $\theta_p = 144.6$; $A \sim 29235.5$
 e3) $\Sigma\theta_s = 179.0 + 10.6 = 189.6$; $\theta_p = 35.4$; $A \sim 6703.9$
 e4) $\Sigma\theta_s = 57.6 + 10.6 = 68.1$; $\theta_p = 72.4$; $A \sim 4932.7$
 Smallest substrate area is occupied by solution e4 (d4)

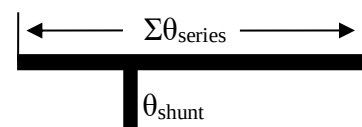


Subject no. 15

1. $y = Y/Y_0 = Z_0/Z = 65\Omega / (67.0 + j \cdot 55.1)\Omega = 0.579 - j \cdot 0.476$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0289 - j \cdot 0.0185)] / (0.02 + 0.0289 - j \cdot 0.0185)$
 $\Gamma = (-0.284) + j \cdot (0.271) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.393 \angle 136.4^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless coupled line coupler, matched at the input; Isolation $I = 24.20\text{dB}$
 $P_{\text{in}} = 2.65\text{mW} = 4.232\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 4.232\text{dBm} - 24.20\text{dB} = -19.97\text{dBm} = 10.075\mu\text{W}$
 b) $L2, C5/2025$, $\beta = 10^{-C/20} = 0.449$, $Z_{\text{CE}} = 81.11\Omega$, $Z_{\text{CO}} = 30.82\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 43)\Omega} = 46.37\Omega$
 b) $Z_L = 43\Omega$ series with 1.12nH inductor at $8.4\text{GHz} = 43.00\Omega + j \cdot (59.11)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 17.30\Omega + j \cdot (-23.79)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 15.15\text{dB}$): $G = G_1 + G_4 = 6.2 + 11.1 = 17.3\text{dB}$; $G = G_2 + G_3 = 8.8 + 8.3 = 17.1\text{dB}$; $G = G_2 + G_4 = 8.8 + 11.1 = 19.9\text{dB}$; $G = G_3 + G_4 = 8.3 + 11.1 = 19.4\text{dB}$;
 b) Friis Formula (C10/2025, S50), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.69\text{dB} = 1.172$, $F_2 = 0.82\text{dB} = 1.208$, $F_3 = 0.96\text{dB} = 1.247$, $F_4 = 1.26\text{dB} = 1.337$, $G_1 = 6.2\text{dB} = 4.169$, $G_2 = 8.8\text{dB} = 7.586$; $F(1,4) = 1.172 + (1.337 - 1)/4.169 = 1.253 = 0.98\text{dB}$; $F(2,3) = 1.208 + (1.247 - 1)/7.586 = 1.252 = 0.98\text{dB}$;
 $F(1,4) > F(2,3) \rightarrow$ For minimal noise factor we must use devices 2,3
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.548 < 1$; $|S_{22}| = 0.317 < 1$; $K = 1.192 > 1$; $|\Delta| = |(-0.135) + j \cdot (-0.098)| = 0.167 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 17.24 = 12.37\text{dB}$
 b_2) Complex calculus from C9/2025, S70:
 $B_1 = 1.172$; $C_1 = (-0.531) + j \cdot (-0.180)$; $\Gamma_S = (-0.701) + j \cdot (0.238) = 0.741 \angle 161.2^\circ$
 $B_2 = 0.772$; $C_2 = (-0.085) + j \cdot (-0.336)$; $\Gamma_L = (-0.153) + j \cdot (0.603) = 0.622 \angle 104.2^\circ$
 c) Complex calculus from C7/2025, S112, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 168.3^\circ$; $\text{Im}(y_S) = -2.205$; $\theta_{p1} = 114.4^\circ$ or $\theta_{S2} = 30.5^\circ$; $\text{Im}(y_S) = 2.205$; $\theta_{p2} = 65.6^\circ$
 output: $\theta_{L1} = 12.1^\circ$; $\text{Im}(y_L) = -1.588$; $\theta_{p1} = 122.2^\circ$ or $\theta_{L2} = 63.6^\circ$; $\text{Im}(y_L) = 1.588$; $\theta_{p2} = 57.8^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, C12/2025, S140÷156):
 d1) $\theta_{L1} = 12.1^\circ$; $\text{Im}(y_L) = -1.588 + (-2.205) = -3.793$; $\theta_{p1} = 104.8^\circ$; $\theta_{S1} = 168.3^\circ$;
 d2) $\theta_{L2} = 63.6^\circ$; $\text{Im}(y_L) = 1.588 + (-2.205) = -0.617$; $\theta_{p2} = 148.3^\circ$; $\theta_{S1} = 168.3^\circ$;
 d3) $\theta_{L1} = 12.1^\circ$; $\text{Im}(y_L) = -1.588 + (2.205) = 0.617$; $\theta_{p3} = 31.7^\circ$; $\theta_{S2} = 30.5^\circ$;
 d4) $\theta_{L2} = 63.6^\circ$; $\text{Im}(y_L) = 1.588 + (2.205) = 3.793$; $\theta_{p4} = 75.2^\circ$; $\theta_{S2} = 30.5^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 12.1 + 168.3 = 180.4$; $\theta_p = 104.8$; $A \sim 18898.8$
 e2) $\Sigma\theta_s = 63.6 + 168.3 = 231.9$; $\theta_p = 148.3$; $A \sim 34402.3$
 e3) $\Sigma\theta_s = 12.1 + 30.5 = 42.6$; $\theta_p = 31.7$; $A \sim 1349.0$
 e4) $\Sigma\theta_s = 63.6 + 30.5 = 94.1$; $\theta_p = 75.2$; $A \sim 7082.4$
 Smallest substrate area is occupied by solution e3 (d3)

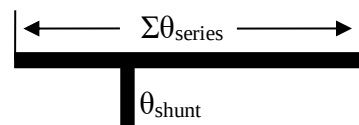

Subject no. 16

1. $y = Y/Y_0 = Z_0/Z = 35\Omega / (38.2 - j \cdot 42.7)\Omega = 0.407 + j \cdot 0.455$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0129 + j \cdot 0.0127)] / (0.02 + 0.0129 + j \cdot 0.0127)$
 $\Gamma = (0.058) + j \cdot (-0.408) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.413 \angle -81.9^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless coupled line coupler, matched at the input; Isolation $I = 24.20\text{dB}$
 $P_{\text{in}} = 1.70\text{mW} = 2.304\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 2.304\text{dBm} - 24.20\text{dB} = -21.90\text{dBm} = 6.463\mu\text{W}$
 b) $L2, C5/2025$, $\beta = 10^{-C/20} = 0.566$, $Z_{\text{CE}} = 94.92\Omega$, $Z_{\text{CO}} = 26.34\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 72)\Omega} = 60.00\Omega$
 b) $Z_L = 72\Omega$ series with 0.41pF capacitor at $7.6\text{GHz} = 72.00\Omega + j \cdot (-51.08)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 33.26\Omega + j \cdot (23.60)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 17.15\text{dB}$): $G = G_1 + G_4 = 6.7 + 11.0 = 17.7\text{dB}$; $G = G_2 + G_3 = 8.8 + 9.0 = 17.8\text{dB}$; $G = G_2 + G_4 = 8.8 + 11.0 = 19.8\text{dB}$; $G = G_3 + G_4 = 9.0 + 11.0 = 20.0\text{dB}$;
 b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.58\text{dB} = 1.143$, $F_2 = 0.89\text{dB} = 1.227$, $F_3 = 1.06\text{dB} = 1.276$, $F_4 = 1.21\text{dB} = 1.321$, $G_1 = 6.7\text{dB} = 4.677$, $G_2 = 8.8\text{dB} = 7.586$; $F(1,4) = 1.143 + (1.321 - 1)/4.677 = 1.212 = 0.83\text{dB}$; $F(2,3) = 1.227 + (1.276 - 1)/7.586 = 1.270 = 1.04\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.585 < 1$; $|S_{22}| = 0.231 < 1$; $K = 1.350 > 1$; $|\Delta| = |(-0.105) + j \cdot (-0.109)| = 0.152 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 8.35 = 9.22\text{dB}$
 b_2) Complex calculus from $C9/2025$, $S70$:
 $B_1 = 1.266$; $C_1 = (-0.421) + j \cdot (0.423)$; $\Gamma_S = (-0.499) + j \cdot (-0.501) = 0.707 \angle -134.9^\circ$
 $B_2 = 0.688$; $C_2 = (-0.206) + j \cdot (-0.178)$; $\Gamma_L = (-0.371) + j \cdot (0.320) = 0.490 \angle 139.3^\circ$
 c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 135.0^\circ$; $\text{Im}(y_S) = -2.001$; $\theta_{p1} = 116.5^\circ$ or $\theta_{S2} = 179.9^\circ$; $\text{Im}(y_S) = 2.001$; $\theta_{p2} = 63.5^\circ$
 output: $\theta_{L1} = 170.0^\circ$; $\text{Im}(y_L) = -1.125$; $\theta_{p1} = 131.6^\circ$ or $\theta_{L2} = 50.7^\circ$; $\text{Im}(y_L) = 1.125$; $\theta_{p2} = 48.4^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025$, $S140 \div 156$):
 d1) $\theta_{L1} = 170.0^\circ$; $\text{Im}(y_L) = -1.125 + (-2.001) = -3.126$; $\theta_{p1} = 107.7^\circ$; $\theta_{S1} = 135.0^\circ$;
 d2) $\theta_{L2} = 50.7^\circ$; $\text{Im}(y_L) = 1.125 + (-2.001) = -0.877$; $\theta_{p2} = 138.8^\circ$; $\theta_{S1} = 135.0^\circ$;
 d3) $\theta_{L1} = 170.0^\circ$; $\text{Im}(y_L) = -1.125 + (2.001) = 0.877$; $\theta_{p3} = 41.2^\circ$; $\theta_{S2} = 179.9^\circ$;
 d4) $\theta_{L2} = 50.7^\circ$; $\text{Im}(y_L) = 1.125 + (2.001) = 3.126$; $\theta_{p4} = 72.3^\circ$; $\theta_{S2} = 179.9^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 170.0 + 135.0 = 305.0$; $\theta_p = 107.7$; $A \sim 32860.7$
 e2) $\Sigma\theta_s = 50.7 + 135.0 = 185.7$; $\theta_p = 138.8$; $A \sim 25760.6$
 e3) $\Sigma\theta_s = 170.0 + 179.9 = 350.0$; $\theta_p = 41.2$; $A \sim 14434.5$
 e4) $\Sigma\theta_s = 50.7 + 179.9 = 230.6$; $\theta_p = 72.3$; $A \sim 16665.9$
 Smallest substrate area is occupied by solution e3 (d3)

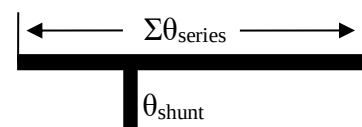

Subject no. 17

1. $y = Y/Y_0 = Z_0/Z = 45\Omega / (66.4 + j \cdot 60.6)\Omega = 0.370 - j \cdot 0.337$

2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0346 + j \cdot 0.0275)] / (0.02 + 0.0346 + j \cdot 0.0275)$
 $\Gamma = (-0.416) + j \cdot (-0.294) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.509 \angle -144.7^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

3. a) Lossless coupled line coupler, matched at the input; Isolation $I = 20.10\text{dB}$

$P_{\text{in}} = 1.85\text{mW} = 2.672\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 2.672\text{dBm} - 20.10\text{dB} = -17.43\text{dBm} = 18.079\mu\text{W}$

b) $L2, C5/2025$, $\beta = 10^{-C/20} = 0.507$, $Z_{\text{CE}} = 87.42\Omega$, $Z_{\text{CO}} = 28.60\Omega$

4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 42)\Omega} = 45.83\Omega$

b) $Z_L = 42\Omega$ parallel with 0.44pF capacitor at $10.0\text{GHz} = 17.89\Omega + j \cdot (-20.77)\Omega$

$\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (58.06)\Omega$

5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).

Valid combinations ($G > 15.80\text{dB}$): $G = G_1 + G_4 = 6.4 + 11.5 = 17.9\text{dB}$; $G = G_2 + G_3 = 8.1 + 9.3 = 17.4\text{dB}$; $G = G_2 + G_4 = 8.1 + 11.5 = 19.6\text{dB}$; $G = G_3 + G_4 = 9.3 + 11.5 = 20.8\text{dB}$;

b) Friis Formula (C10/2025, S50), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;

From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$

$F_1 = 0.59\text{dB} = 1.146$, $F_2 = 0.89\text{dB} = 1.227$, $F_3 = 0.90\text{dB} = 1.230$, $F_4 = 1.29\text{dB} = 1.346$, $G_1 = 6.4\text{dB} = 4.365$, $G_2 = 8.1\text{dB} = 6.457$; $F(1,4) = 1.146 + (1.346 - 1)/4.365 = 1.225 = 0.88\text{dB}$; $F(2,3) = 1.227 + (1.230 - 1)/6.457 = 1.281 = 1.08\text{dB}$;

$F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4

6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:

$|S_{11}| = 0.534 < 1$; $|S_{22}| = 0.254 < 1$; $K = 1.318 > 1$; $|\Delta| = |(-0.090) + j \cdot (-0.074)| = 0.117 < 1$

b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 11.13 = 10.46\text{dB}$

b_2) Complex calculus from C9/2025, S70:

$B_1 = 1.207$; $C_1 = (-0.539) + j \cdot (0.164)$; $\Gamma_S = (-0.658) + j \cdot (-0.200) = 0.687 \angle -163.1^\circ$

$B_2 = 0.766$; $C_2 = (-0.153) + j \cdot (-0.277)$; $\Gamma_L = (-0.255) + j \cdot (0.462) = 0.528 \angle 118.9^\circ$

c) Complex calculus from C7/2025, S112, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines

input: $\theta_{S1} = 148.2^\circ$; $\text{Im}(y_S) = -1.893$; $\theta_{p1} = 117.8^\circ$ or $\theta_{S2} = 14.8^\circ$; $\text{Im}(y_S) = 1.893$; $\theta_{p2} = 62.2^\circ$

output: $\theta_{L1} = 1.5^\circ$; $\text{Im}(y_L) = -1.242$; $\theta_{p1} = 128.8^\circ$ or $\theta_{L2} = 59.6^\circ$; $\text{Im}(y_L) = 1.242$; $\theta_{p2} = 51.2^\circ$

d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, C12/2025, S140÷156):

d1) $\theta_{L1} = 1.5^\circ$; $\text{Im}(y_L) = -1.242 + (-1.893) = -3.135$; $\theta_{p1} = 107.7^\circ$; $\theta_{S1} = 148.2^\circ$;

d2) $\theta_{L2} = 59.6^\circ$; $\text{Im}(y_L) = 1.242 + (-1.893) = -0.651$; $\theta_{p2} = 146.9^\circ$; $\theta_{S1} = 148.2^\circ$;

d3) $\theta_{L1} = 1.5^\circ$; $\text{Im}(y_L) = -1.242 + (1.893) = 0.651$; $\theta_{p3} = 33.1^\circ$; $\theta_{S2} = 14.8^\circ$;

d4) $\theta_{L2} = 59.6^\circ$; $\text{Im}(y_L) = 1.242 + (1.893) = 3.135$; $\theta_{p4} = 72.3^\circ$; $\theta_{S2} = 14.8^\circ$;

e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.


e1) $\Sigma\theta_s = 1.5 + 148.2 = 149.7$; $\theta_p = 107.7$; $A \sim 16124.0$

e2) $\Sigma\theta_s = 59.6 + 148.2 = 207.9$; $\theta_p = 146.9$; $A \sim 30544.5$

e3) $\Sigma\theta_s = 1.5 + 14.8 = 16.3$; $\theta_p = 33.1$; $A \sim 539.0$


e4) $\Sigma\theta_s = 59.6 + 14.8 = 74.5$; $\theta_p = 72.3$; $A \sim 5384.0$

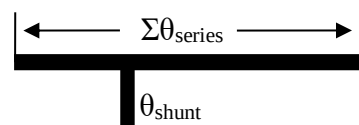Smallest substrate area is occupied by solution e3 (d3)




Subject no. 18

1. $y = Y/Y_0 = Z_0/Z = 40\Omega / (45.8 - j \cdot 64.4)\Omega = 0.293 + j \cdot 0.412$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0182 + j \cdot 0.0306)] / (0.02 + 0.0182 + j \cdot 0.0306)$
 $\Gamma = (-0.362) + j \cdot (-0.511) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.626 \angle -125.3^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless ring coupler, matched at the input; Isolation $I = D + C = 27.10\text{dB}$
 $P_{\text{in}} = 1.15\text{mW} = 0.607\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 0.607\text{dBm} - 27.10\text{dB} = -26.49\text{dBm} = 2.242\mu\text{W}$
 b) $L_2, C_5/2025$, $\beta = 10^{-C/20} = 0.519$, $y_1 = 0.519$, $y_2 = 0.855$, $Z_1 = Z_0/y_1 = 96.4\Omega$, $Z_2 = Z_0/y_2 = 58.5\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 45)}\Omega = 47.43\Omega$
 b) $Z_L = 45\Omega$ parallel with 1.16nH inductor at $9.5\text{GHz} = 31.64\Omega + j \cdot (20.56)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (-32.50)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 16.50\text{dB}$): $G = G_1 + G_4 = 6.5 + 10.4 = 16.9\text{dB}$; $G = G_2 + G_3 = 7.0 + 9.8 = 16.8\text{dB}$; $G = G_2 + G_4 = 7.0 + 10.4 = 17.4\text{dB}$; $G = G_3 + G_4 = 9.8 + 10.4 = 20.2\text{dB}$;
 b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.67\text{dB} = 1.167$, $F_2 = 0.89\text{dB} = 1.227$, $F_3 = 0.94\text{dB} = 1.242$, $F_4 = 1.11\text{dB} = 1.291$, $G_1 = 6.5\text{dB} = 4.467$, $G_2 = 7.0\text{dB} = 5.012$; $F(1,4) = 1.167 + (1.291 - 1)/4.467 = 1.232 = 0.91\text{dB}$; $F(2,3) = 1.227 + (1.242 - 1)/5.012 = 1.286 = 1.09\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.574 < 1$; $|S_{22}| = 0.230 < 1$; $K = 1.348 > 1$; $|\Delta| = |(-0.098) + j \cdot (-0.102)| = 0.142 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 8.68 = 9.38\text{dB}$
 b_2) Complex calculus from $C9/2025$, $S70$:
 $B_1 = 1.257$; $C_1 = (-0.446) + j \cdot (0.388)$; $\Gamma_S = (-0.529) + j \cdot (-0.461) = 0.702 \angle -138.9^\circ$
 $B_2 = 0.703$; $C_2 = (-0.200) + j \cdot (-0.195)$; $\Gamma_L = (-0.353) + j \cdot (0.345) = 0.494 \angle 135.7^\circ$
 c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 136.7^\circ$; $\text{Im}(y_S) = -1.969$; $\theta_{p1} = 116.9^\circ$ or $\theta_{S2} = 2.2^\circ$; $\text{Im}(y_S) = 1.969$; $\theta_{p2} = 63.1^\circ$
 output: $\theta_{L1} = 171.9^\circ$; $\text{Im}(y_L) = -1.135$; $\theta_{p1} = 131.4^\circ$ or $\theta_{L2} = 52.3^\circ$; $\text{Im}(y_L) = 1.135$; $\theta_{p2} = 48.6^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):
 d1) $\theta_{L1} = 171.9^\circ$; $\text{Im}(y_L) = -1.135 + (-1.969) = -3.104$; $\theta_{p1} = 107.9^\circ$; $\theta_{S1} = 136.7^\circ$;
 d2) $\theta_{L2} = 52.3^\circ$; $\text{Im}(y_L) = 1.135 + (-1.969) = -0.833$; $\theta_{p2} = 140.2^\circ$; $\theta_{S1} = 136.7^\circ$;
 d3) $\theta_{L1} = 171.9^\circ$; $\text{Im}(y_L) = -1.135 + (1.969) = 0.833$; $\theta_{p3} = 39.8^\circ$; $\theta_{S2} = 2.2^\circ$;
 d4) $\theta_{L2} = 52.3^\circ$; $\text{Im}(y_L) = 1.135 + (1.969) = 3.104$; $\theta_{p4} = 72.1^\circ$; $\theta_{S2} = 2.2^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 171.9 + 136.7 = 308.7$; $\theta_p = 107.9$; $A \sim 33292.9$
 e2) $\Sigma\theta_s = 52.3 + 136.7 = 189.1$; $\theta_p = 140.2$; $A \sim 26510.1$
 e3) $\Sigma\theta_s = 171.9 + 2.2 = 174.1$; $\theta_p = 39.8$; $A \sim 6931.2$
 e4) $\Sigma\theta_s = 52.3 + 2.2 = 54.5$; $\theta_p = 72.1$; $A \sim 3935.1$
 Smallest substrate area is occupied by solution e4 (d4)

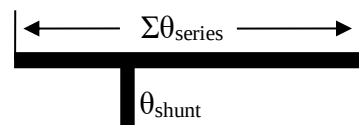

Subject no. 19

1. $y = Y/Y_0 = Z_0/Z = 55\Omega / (58.5 + j \cdot 50.5)\Omega = 0.539 - j \cdot 0.465$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0136 - j \cdot 0.0295)] / (0.02 + 0.0136 - j \cdot 0.0295)$
 $\Gamma = (-0.328) + j \cdot (0.590) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.675 \angle 119.0^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless quadrature coupler, matched at the input; Isolation $I = D + C = 27.10\text{dB}$
 $P_{\text{in}} = 3.15\text{mW} = 4.983\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 4.983\text{dBm} - 27.10\text{dB} = -22.12\text{dBm} = 6.142\mu\text{W}$
 b) L2, C5/2025, $\beta = 10^{-C/20} = 0.569$, $y_2 = 1.216$, $y_1 = 0.692$, $Z_1 = Z_0/y_1 = 72.3\Omega$, $Z_2 = Z_0/y_2 = 41.1\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 38)\Omega} = 43.59\Omega$
 b) $Z_L = 38\Omega$ parallel with 0.71nH inductor at $9.2\text{GHz} = 20.46\Omega + j \cdot (18.94)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (-46.29)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 15.15\text{dB}$): $G = G_1 + G_4 = 5.3 + 10.1 = 15.4\text{dB}$; $G = G_2 + G_3 = 7.2 + 9.6 = 16.8\text{dB}$; $G = G_2 + G_4 = 7.2 + 10.1 = 17.3\text{dB}$; $G = G_3 + G_4 = 9.6 + 10.1 = 19.7\text{dB}$;
 b) Friis Formula (C10/2025, S50), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.53\text{dB} = 1.130$, $F_2 = 0.71\text{dB} = 1.178$, $F_3 = 1.00\text{dB} = 1.259$, $F_4 = 1.11\text{dB} = 1.291$, $G_1 = 5.3\text{dB} = 3.388$, $G_2 = 7.2\text{dB} = 5.248$; $F(1,4) = 1.130 + (1.291 - 1)/3.388 = 1.216 = 0.85\text{dB}$; $F(2,3) = 1.178 + (1.259 - 1)/5.248 = 1.233 = 0.91\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.562 < 1$; $|S_{22}| = 0.230 < 1$; $K = 1.324 > 1$; $|\Delta| = |(-0.096) + j \cdot (-0.095)| = 0.135 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 9.25 = 9.66\text{dB}$
 b_2) Complex calculus from C9/2025, S70:
 $B_1 = 1.245$; $C_1 = (-0.477) + j \cdot (0.338)$; $\Gamma_S = (-0.572) + j \cdot (-0.405) = 0.700 \angle -144.7^\circ$
 $B_2 = 0.719$; $C_2 = (-0.189) + j \cdot (-0.219)$; $\Gamma_L = (-0.331) + j \cdot (0.383) = 0.506 \angle 130.8^\circ$
 c) Complex calculus from C7/2025, S112, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 139.6^\circ$; $\text{Im}(y_S) = -1.962$; $\theta_{p1} = 117.0^\circ$ or $\theta_{S2} = 5.1^\circ$; $\text{Im}(y_S) = 1.962$; $\theta_{p2} = 63.0^\circ$
 output: $\theta_{L1} = 174.8^\circ$; $\text{Im}(y_L) = -1.174$; $\theta_{p1} = 130.4^\circ$ or $\theta_{L2} = 54.4^\circ$; $\text{Im}(y_L) = 1.174$; $\theta_{p2} = 49.6^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, C12/2025, S140÷156):
 d1) $\theta_{L1} = 174.8^\circ$; $\text{Im}(y_L) = -1.174 + (-1.962) = -3.137$; $\theta_{p1} = 107.7^\circ$; $\theta_{S1} = 139.6^\circ$;
 d2) $\theta_{L2} = 54.4^\circ$; $\text{Im}(y_L) = 1.174 + (-1.962) = -0.788$; $\theta_{p2} = 141.8^\circ$; $\theta_{S1} = 139.6^\circ$;
 d3) $\theta_{L1} = 174.8^\circ$; $\text{Im}(y_L) = -1.174 + (1.962) = 0.788$; $\theta_{p3} = 38.2^\circ$; $\theta_{S2} = 5.1^\circ$;
 d4) $\theta_{L2} = 54.4^\circ$; $\text{Im}(y_L) = 1.174 + (1.962) = 3.137$; $\theta_{p4} = 72.3^\circ$; $\theta_{S2} = 5.1^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 174.8 + 139.6 = 314.4$; $\theta_p = 107.7$; $A \sim 33851.3$
 e2) $\Sigma\theta_s = 54.4 + 139.6 = 193.9$; $\theta_p = 141.8$; $A \sim 27493.2$
 e3) $\Sigma\theta_s = 174.8 + 5.1 = 179.9$; $\theta_p = 38.2$; $A \sim 6879.5$
 e4) $\Sigma\theta_s = 54.4 + 5.1 = 59.5$; $\theta_p = 72.3$; $A \sim 4301.8$
 Smallest substrate area is occupied by solution e4 (d4)

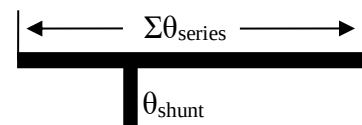

Subject no. 20

1. $y = Y/Y_0 = Z_0/Z = 90\Omega / (36.8 - j \cdot 34.7)\Omega = 1.295 + j \cdot 1.221$

2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0180 - j \cdot 0.0333)] / (0.02 + 0.0180 - j \cdot 0.0333)$
 $\Gamma = (-0.405) + j \cdot (0.522) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.660 \angle 127.8^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$

3. a) Lossless coupled line coupler, matched at the input; Isolation $I = D + C = 27.30\text{dB}$

$P_{\text{in}} = 1.55\text{mW} = 1.903\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 1.903\text{dBm} - 27.30\text{dB} = -25.40\text{dBm} = 2.886\mu\text{W}$

b) $L_2, C_5/2025$, $\beta = 10^{-C/20} = 0.631$, $Z_{\text{CE}} = 105.11\Omega$, $Z_{\text{CO}} = 23.78\Omega$

4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 51)\Omega} = 50.50\Omega$

b) $Z_L = 51\Omega$ series with 1.12nH inductor at $6.7\text{GHz} = 51.00\Omega + j \cdot (47.15)\Omega$

$\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 26.96\Omega + j \cdot (-24.92)\Omega$

5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).

Valid combinations ($G > 16.00\text{dB}$): $G = G_1 + G_4 = 6.4 + 10.9 = 17.3\text{dB}$; $G = G_2 + G_3 = 8.5 + 8.1 = 16.6\text{dB}$; $G = G_2 + G_4 = 8.5 + 10.9 = 19.4\text{dB}$; $G = G_3 + G_4 = 8.1 + 10.9 = 19.0\text{dB}$;

b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;

From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$

$F_1 = 0.56\text{dB} = 1.138$, $F_2 = 0.79\text{dB} = 1.199$, $F_3 = 1.07\text{dB} = 1.279$, $F_4 = 1.20\text{dB} = 1.318$, $G_1 = 6.4\text{dB} = 4.365$, $G_2 = 8.5\text{dB} = 7.079$; $F(1,4) = 1.138 + (1.318 - 1)/4.365 = 1.211 = 0.83\text{dB}$; $F(2,3) = 1.199 + (1.279 - 1)/7.079 = 1.244 = 0.95\text{dB}$;

$F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4

6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:

$|S_{11}| = 0.530 < 1$; $|S_{22}| = 0.266 < 1$; $K = 1.299 > 1$; $|\Delta| = |(-0.096) + j \cdot (-0.071)| = 0.119 < 1$

b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 11.98 = 10.78\text{dB}$

b_2) Complex calculus from $C9/2025$, $S70$:

$B_1 = 1.196$; $C_1 = (-0.550) + j \cdot (0.100)$; $\Gamma_S = (-0.680) + j \cdot (-0.124) = 0.691 \angle -169.7^\circ$

$B_2 = 0.776$; $C_2 = (-0.141) + j \cdot (-0.293)$; $\Gamma_L = (-0.235) + j \cdot (0.489) = 0.542 \angle 115.7^\circ$

c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines

input: $\theta_{S1} = 151.7^\circ$; $\text{Im}(y_S) = -1.911$; $\theta_{p1} = 117.6^\circ$ or $\theta_{S2} = 18.0^\circ$; $\text{Im}(y_S) = 1.911$; $\theta_{p2} = 62.4^\circ$

output: $\theta_{L1} = 3.6^\circ$; $\text{Im}(y_L) = -1.291$; $\theta_{p1} = 127.8^\circ$ or $\theta_{L2} = 60.7^\circ$; $\text{Im}(y_L) = 1.291$; $\theta_{p2} = 52.2^\circ$

d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):

d1) $\theta_{L1} = 3.6^\circ$; $\text{Im}(y_L) = -1.291 + (-1.911) = -3.202$; $\theta_{p1} = 107.3^\circ$; $\theta_{S1} = 151.7^\circ$;

d2) $\theta_{L2} = 60.7^\circ$; $\text{Im}(y_L) = 1.291 + (-1.911) = -0.620$; $\theta_{p2} = 148.2^\circ$; $\theta_{S1} = 151.7^\circ$;

d3) $\theta_{L1} = 3.6^\circ$; $\text{Im}(y_L) = -1.291 + (1.911) = 0.620$; $\theta_{p3} = 31.8^\circ$; $\theta_{S2} = 18.0^\circ$;

d4) $\theta_{L2} = 60.7^\circ$; $\text{Im}(y_L) = 1.291 + (1.911) = 3.202$; $\theta_{p4} = 72.7^\circ$; $\theta_{S2} = 18.0^\circ$;

e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.


e1) $\Sigma\theta_s = 3.6 + 151.7 = 155.3$; $\theta_p = 107.3$; $A \sim 16668.8$

e2) $\Sigma\theta_s = 60.7 + 151.7 = 212.4$; $\theta_p = 148.2$; $A \sim 31480.6$

e3) $\Sigma\theta_s = 3.6 + 18.0 = 21.6$; $\theta_p = 31.8$; $A \sim 686.8$


e4) $\Sigma\theta_s = 60.7 + 18.0 = 78.7$; $\theta_p = 72.7$; $A \sim 5721.3$

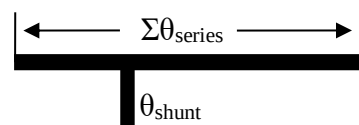Smallest substrate area is occupied by solution e3 (d3)




Subject no. 21

1. $y = Y/Y_0 = Z_0/Z = 50\Omega / (30.3 - j \cdot 52.1)\Omega = 0.417 + j \cdot 0.717$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0348 + j \cdot 0.0132)] / (0.02 + 0.0348 + j \cdot 0.0132)$
 $\Gamma = (-0.310) + j \cdot (-0.166) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.352 \angle -151.8^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless coupled line coupler, matched at the input; Isolation $I = 24.00\text{dB}$
 $P_{\text{in}} = 1.25\text{mW} = 0.969\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 0.969\text{dBm} - 24.00\text{dB} = -23.03\text{dBm} = 4.976\mu\text{W}$
 b) $L2, C5/2025$, $\beta = 10^{-C/20} = 0.562$, $Z_{\text{CE}} = 94.47\Omega$, $Z_{\text{CO}} = 26.46\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 48)\Omega} = 48.99\Omega$
 b) $Z_L = 48\Omega$ series with 0.30pF capacitor at $8.9\text{GHz} = 48.00\Omega + j \cdot (-59.61)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 19.67\Omega + j \cdot (24.42)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 15.80\text{dB}$): $G = G_1 + G_4 = 6.9 + 11.1 = 18.0\text{dB}$; $G = G_2 + G_3 = 7.3 + 8.7 = 16.0\text{dB}$; $G = G_2 + G_4 = 7.3 + 11.1 = 18.4\text{dB}$; $G = G_3 + G_4 = 8.7 + 11.1 = 19.8\text{dB}$;
 b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.59\text{dB} = 1.146$, $F_2 = 0.84\text{dB} = 1.213$, $F_3 = 0.96\text{dB} = 1.247$, $F_4 = 1.12\text{dB} = 1.294$, $G_1 = 6.9\text{dB} = 4.898$, $G_2 = 7.3\text{dB} = 5.370$; $F(1,4) = 1.146 + (1.294 - 1)/4.898 = 1.206 = 0.81\text{dB}$; $F(2,3) = 1.213 + (1.247 - 1)/5.370 = 1.268 = 1.03\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.620 < 1$; $|S_{22}| = 0.238 < 1$; $K = 1.277 > 1$; $|\Delta| = |(-0.139) + j \cdot (-0.129)| = 0.190 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 8.08 = 9.07\text{dB}$
 b_2) Complex calculus from $C9/2025$, $S70$:
 $B_1 = 1.292$; $C_1 = (-0.370) + j \cdot (0.496)$; $\Gamma_S = (-0.446) + j \cdot (-0.596) = 0.745 \angle -126.8^\circ$
 $B_2 = 0.636$; $C_2 = (-0.216) + j \cdot (-0.143)$; $\Gamma_L = (-0.428) + j \cdot (0.285) = 0.514 \angle 146.4^\circ$
 c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 132.5^\circ$; $\text{Im}(y_S) = -2.232$; $\theta_{p1} = 114.1^\circ$ or $\theta_{S2} = 174.3^\circ$; $\text{Im}(y_S) = 2.232$; $\theta_{p2} = 65.9^\circ$
 output: $\theta_{L1} = 167.3^\circ$; $\text{Im}(y_L) = -1.199$; $\theta_{p1} = 129.8^\circ$ or $\theta_{L2} = 46.3^\circ$; $\text{Im}(y_L) = 1.199$; $\theta_{p2} = 50.2^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):
 d1) $\theta_{L1} = 167.3^\circ$; $\text{Im}(y_L) = -1.199 + (-2.232) = -3.431$; $\theta_{p1} = 106.2^\circ$; $\theta_{S1} = 132.5^\circ$;
 d2) $\theta_{L2} = 46.3^\circ$; $\text{Im}(y_L) = 1.199 + (-2.232) = -1.032$; $\theta_{p2} = 134.1^\circ$; $\theta_{S1} = 132.5^\circ$;
 d3) $\theta_{L1} = 167.3^\circ$; $\text{Im}(y_L) = -1.199 + (2.232) = 1.032$; $\theta_{p3} = 45.9^\circ$; $\theta_{S2} = 174.3^\circ$;
 d4) $\theta_{L2} = 46.3^\circ$; $\text{Im}(y_L) = 1.199 + (2.232) = 3.431$; $\theta_{p4} = 73.8^\circ$; $\theta_{S2} = 174.3^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 167.3 + 132.5 = 299.7$; $\theta_p = 106.2$; $A \sim 31845.4$
 e2) $\Sigma\theta_s = 46.3 + 132.5 = 178.8$; $\theta_p = 134.1$; $A \sim 23971.0$
 e3) $\Sigma\theta_s = 167.3 + 174.3 = 341.6$; $\theta_p = 45.9$; $A \sim 15684.3$
 e4) $\Sigma\theta_s = 46.3 + 174.3 = 220.6$; $\theta_p = 73.8$; $A \sim 16272.5$
 Smallest substrate area is occupied by solution e3 (d3)

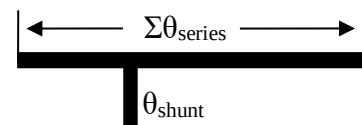


Subject no. 22

1. $y = Y/Y_0 = Z_0/Z = 85\Omega / (55.5 + j \cdot 68.6)\Omega = 0.606 - j \cdot 0.749$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0311 + j \cdot 0.0283)] / (0.02 + 0.0311 + j \cdot 0.0283)$
 $\Gamma = (-0.401) + j \cdot (-0.332) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.520 \angle -140.4^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless ring coupler, matched at the input; Isolation $I = 21.80\text{dB}$
 $P_{\text{in}} = 3.65\text{mW} = 5.623\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 5.623\text{dBm} - 21.80\text{dB} = -16.18\text{dBm} = 24.115\mu\text{W}$
 b) $L2, C5/2025$, $\beta = 10^{-C/20} = 0.507$, $y_1 = 0.507$, $y_2 = 0.862$, $Z_1 = Z_0/y_1 = 98.6\Omega$, $Z_2 = Z_0/y_2 = 58.0\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 39)\Omega} = 44.16\Omega$
 b) $Z_L = 39\Omega$ series with 0.28pF capacitor at $8.1\text{GHz} = 39.00\Omega + j \cdot (-70.17)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 11.80\Omega + j \cdot (21.23)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 14.50\text{dB}$): $G = G_1 + G_4 = 5.6 + 10.7 = 16.3\text{dB}$; $G = G_2 + G_3 = 7.5 + 8.2 = 15.7\text{dB}$; $G = G_2 + G_4 = 7.5 + 10.7 = 18.2\text{dB}$; $G = G_3 + G_4 = 8.2 + 10.7 = 18.9\text{dB}$;
 b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.60\text{dB} = 1.148$, $F_2 = 0.75\text{dB} = 1.189$, $F_3 = 0.91\text{dB} = 1.233$, $F_4 = 1.18\text{dB} = 1.312$, $G_1 = 5.6\text{dB} = 3.631$, $G_2 = 7.5\text{dB} = 5.623$; $F(1,4) = 1.148 + (1.312 - 1)/3.631 = 1.234 = 0.91\text{dB}$; $F(2,3) = 1.189 + (1.233 - 1)/5.623 = 1.244 = 0.95\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.530 < 1$; $|S_{22}| = 0.275 < 1$; $K = 1.264 > 1$; $|\Delta| = |(-0.105) + j \cdot (-0.073)| = 0.128 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 12.81 = 11.08\text{dB}$
 b_2) Complex calculus from $C9/2025$, $S70$:
 $B_1 = 1.189$; $C_1 = (-0.557) + j \cdot (0.050)$; $\Gamma_S = (-0.699) + j \cdot (-0.062) = 0.702 \angle -174.9^\circ$
 $B_2 = 0.778$; $C_2 = (-0.134) + j \cdot (-0.304)$; $\Gamma_L = (-0.227) + j \cdot (0.515) = 0.563 \angle 113.8^\circ$
 c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 154.8^\circ$; $\text{Im}(y_S) = -1.972$; $\theta_{p1} = 116.9^\circ$ or $\theta_{S2} = 20.2^\circ$; $\text{Im}(y_S) = 1.972$; $\theta_{p2} = 63.1^\circ$
 output: $\theta_{L1} = 5.2^\circ$; $\text{Im}(y_L) = -1.362$; $\theta_{p1} = 126.3^\circ$ or $\theta_{L2} = 61.0^\circ$; $\text{Im}(y_L) = 1.362$; $\theta_{p2} = 53.7^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):
 d1) $\theta_{L1} = 5.2^\circ$; $\text{Im}(y_L) = -1.362 + (-1.972) = -3.335$; $\theta_{p1} = 106.7^\circ$; $\theta_{S1} = 154.8^\circ$;
 d2) $\theta_{L2} = 61.0^\circ$; $\text{Im}(y_L) = 1.362 + (-1.972) = -0.610$; $\theta_{p2} = 148.6^\circ$; $\theta_{S1} = 154.8^\circ$;
 d3) $\theta_{L1} = 5.2^\circ$; $\text{Im}(y_L) = -1.362 + (1.972) = 0.610$; $\theta_{p3} = 31.4^\circ$; $\theta_{S2} = 20.2^\circ$;
 d4) $\theta_{L2} = 61.0^\circ$; $\text{Im}(y_L) = 1.362 + (1.972) = 3.335$; $\theta_{p4} = 73.3^\circ$; $\theta_{S2} = 20.2^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 5.2 + 154.8 = 160.0$; $\theta_p = 106.7$; $A \sim 17070.4$
 e2) $\Sigma\theta_s = 61.0 + 154.8 = 215.7$; $\theta_p = 148.6$; $A \sim 32062.1$
 e3) $\Sigma\theta_s = 5.2 + 20.2 = 25.4$; $\theta_p = 31.4$; $A \sim 796.9$
 e4) $\Sigma\theta_s = 61.0 + 20.2 = 81.1$; $\theta_p = 73.3$; $A \sim 5947.7$
 Smallest substrate area is occupied by solution e3 (d3)

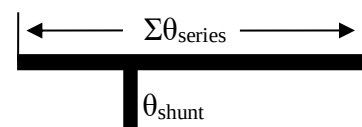


Subject no. 23

1. $y = Y/Y_0 = Z_0/Z = 60\Omega / (38.4 + j \cdot 31.5)\Omega = 0.934 - j \cdot 0.766$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0127 - j \cdot 0.0374)] / (0.02 + 0.0127 - j \cdot 0.0374)$
 $\Gamma = (-0.470) + j \cdot (0.606) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.767 \angle 127.8^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless coupled line coupler, matched at the input; Isolation $I = 22.60\text{dB}$
 $P_{\text{in}} = 3.40\text{mW} = 5.315\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 5.315\text{dBm} - 22.60\text{dB} = -17.29\text{dBm} = 18.684\mu\text{W}$
 b) $L2, C5/2025$, $\beta = 10^{-C/20} = 0.473$, $Z_{\text{CE}} = 83.61\Omega$, $Z_{\text{CO}} = 29.90\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 60)\Omega} = 54.77\Omega$
 b) $Z_L = 60\Omega$ parallel with 0.37pF capacitor at $7.9\text{GHz} = 27.10\Omega + j \cdot (-29.86)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (55.10)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 15.25\text{dB}$): $G = G_1 + G_4 = 6.7 + 11.5 = 18.2\text{dB}$; $G = G_2 + G_3 = 8.4 + 8.0 = 16.4\text{dB}$; $G = G_2 + G_4 = 8.4 + 11.5 = 19.9\text{dB}$; $G = G_3 + G_4 = 8.0 + 11.5 = 19.5\text{dB}$;
 b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.68\text{dB} = 1.169$, $F_2 = 0.75\text{dB} = 1.189$, $F_3 = 1.02\text{dB} = 1.265$, $F_4 = 1.20\text{dB} = 1.318$, $G_1 = 6.7\text{dB} = 4.677$, $G_2 = 8.4\text{dB} = 6.918$; $F(1,4) = 1.169 + (1.318 - 1)/4.677 = 1.238 = 0.93\text{dB}$; $F(2,3) = 1.189 + (1.265 - 1)/6.918 = 1.235 = 0.91\text{dB}$;
 $F(1,4) > F(2,3) \rightarrow$ For minimal noise factor we must use devices 2,3
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.580 < 1$; $|S_{22}| = 0.230 < 1$; $K = 1.362 > 1$; $|\Delta| = |(-0.102) + j \cdot (-0.106)| = 0.147 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 8.39 = 9.24\text{dB}$
 b_2) Complex calculus from $C9/2025$, $S70$:
 $B_1 = 1.262$; $C_1 = (-0.427) + j \cdot (0.412)$; $\Gamma_S = (-0.505) + j \cdot (-0.487) = 0.702 \angle -136.0^\circ$
 $B_2 = 0.695$; $C_2 = (-0.204) + j \cdot (-0.182)$; $\Gamma_L = (-0.362) + j \cdot (0.324) = 0.486 \angle 138.2^\circ$
 c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 135.3^\circ$; $\text{Im}(y_S) = -1.970$; $\theta_{p1} = 116.9^\circ$ or $\theta_{S2} = 0.7^\circ$; $\text{Im}(y_S) = 1.970$; $\theta_{p2} = 63.1^\circ$
 output: $\theta_{L1} = 170.5^\circ$; $\text{Im}(y_L) = -1.113$; $\theta_{p1} = 132.0^\circ$ or $\theta_{L2} = 51.4^\circ$; $\text{Im}(y_L) = 1.113$; $\theta_{p2} = 48.0^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):
 d1) $\theta_{L1} = 170.5^\circ$; $\text{Im}(y_L) = -1.113 + (-1.970) = -3.082$; $\theta_{p1} = 108.0^\circ$; $\theta_{S1} = 135.3^\circ$;
 d2) $\theta_{L2} = 51.4^\circ$; $\text{Im}(y_L) = 1.113 + (-1.970) = -0.857$; $\theta_{p2} = 139.4^\circ$; $\theta_{S1} = 135.3^\circ$;
 d3) $\theta_{L1} = 170.5^\circ$; $\text{Im}(y_L) = -1.113 + (1.970) = 0.857$; $\theta_{p3} = 40.6^\circ$; $\theta_{S2} = 0.7^\circ$;
 d4) $\theta_{L2} = 51.4^\circ$; $\text{Im}(y_L) = 1.113 + (1.970) = 3.082$; $\theta_{p4} = 72.0^\circ$; $\theta_{S2} = 0.7^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 170.5 + 135.3 = 305.8$; $\theta_p = 108.0$; $A \sim 33014.2$
 e2) $\Sigma\theta_s = 51.4 + 135.3 = 186.7$; $\theta_p = 139.4$; $A \sim 26021.9$
 e3) $\Sigma\theta_s = 170.5 + 0.7 = 171.2$; $\theta_p = 40.6$; $A \sim 6950.4$
 e4) $\Sigma\theta_s = 51.4 + 0.7 = 52.1$; $\theta_p = 72.0$; $A \sim 3753.1$
 Smallest substrate area is occupied by solution e4 (d4)

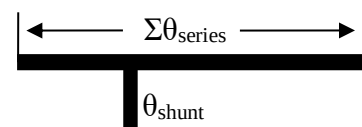

Subject no. 24

1. $y = Y/Y_0 = Z_0/Z = 45\Omega / (34.5 + j \cdot 50.1)\Omega = 0.420 - j \cdot 0.609$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0134 + j \cdot 0.0273)] / (0.02 + 0.0134 + j \cdot 0.0273)$
 $\Gamma = (-0.282) + j \cdot (-0.587) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.651 \angle -115.7^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless coupled line coupler, matched at the input; Isolation $I = D + C = 30.20\text{dB}$
 $P_{\text{in}} = 1.85\text{mW} = 2.672\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 2.672\text{dBm} - 30.20\text{dB} = -27.53\text{dBm} = 1.767\mu\text{W}$
 b) $L_2, C_5/2025$, $\beta = 10^{-C/20} = 0.490$, $Z_{\text{CE}} = 85.44\Omega$, $Z_{\text{CO}} = 29.26\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 36)\Omega} = 42.43\Omega$
 b) $Z_L = 36\Omega$ parallel with 1.50nH inductor at $7.4\text{GHz} = 28.43\Omega + j \cdot (14.67)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (-25.81)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 16.70\text{dB}$): $G = G_1 + G_4 = 5.7 + 11.2 = 16.9\text{dB}$; $G = G_2 + G_3 = 7.2 + 9.8 = 17.0\text{dB}$; $G = G_2 + G_4 = 7.2 + 11.2 = 18.4\text{dB}$; $G = G_3 + G_4 = 9.8 + 11.2 = 21.0\text{dB}$;
 b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.57\text{dB} = 1.140$, $F_2 = 0.80\text{dB} = 1.202$, $F_3 = 0.95\text{dB} = 1.245$, $F_4 = 1.26\text{dB} = 1.337$, $G_1 = 5.7\text{dB} = 3.715$, $G_2 = 7.2\text{dB} = 5.248$;
 $F(1,4) = 1.140 + (1.337 - 1)/3.715 = 1.231 = 0.90\text{dB}$; $F(2,3) = 1.202 + (1.245 - 1)/5.248 = 1.266 = 1.03\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.546 < 1$; $|S_{22}| = 0.314 < 1$; $K = 1.194 > 1$; $|\Delta| = |(-0.134) + j \cdot (-0.095)| = 0.164 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 16.91 = 12.28\text{dB}$
 b_2) Complex calculus from $C9/2025$, $S70$:
 $B_1 = 1.173$; $C_1 = (-0.536) + j \cdot (-0.165)$; $\Gamma_S = (-0.707) + j \cdot (0.217) = 0.739 \angle 162.9^\circ$
 $B_2 = 0.773$; $C_2 = (-0.090) + j \cdot (-0.335)$; $\Gamma_L = (-0.160) + j \cdot (0.599) = 0.620 \angle 105.0^\circ$
 c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 167.4^\circ$; $\text{Im}(y_S) = -2.194$; $\theta_{p1} = 114.5^\circ$ or $\theta_{S2} = 29.7^\circ$; $\text{Im}(y_S) = 2.194$; $\theta_{p2} = 65.5^\circ$
 output: $\theta_{L1} = 11.7^\circ$; $\text{Im}(y_L) = -1.580$; $\theta_{p1} = 122.3^\circ$ or $\theta_{L2} = 63.4^\circ$; $\text{Im}(y_L) = 1.580$; $\theta_{p2} = 57.7^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025$, $S140 \div 156$):
 d1) $\theta_{L1} = 11.7^\circ$; $\text{Im}(y_L) = -1.580 + (-2.194) = -3.774$; $\theta_{p1} = 104.8^\circ$; $\theta_{S1} = 167.4^\circ$;
 d2) $\theta_{L2} = 63.4^\circ$; $\text{Im}(y_L) = 1.580 + (-2.194) = -0.615$; $\theta_{p2} = 148.4^\circ$; $\theta_{S1} = 167.4^\circ$;
 d3) $\theta_{L1} = 11.7^\circ$; $\text{Im}(y_L) = -1.580 + (2.194) = 0.615$; $\theta_{p3} = 31.6^\circ$; $\theta_{S2} = 29.7^\circ$;
 d4) $\theta_{L2} = 63.4^\circ$; $\text{Im}(y_L) = 1.580 + (2.194) = 3.774$; $\theta_{p4} = 75.2^\circ$; $\theta_{S2} = 29.7^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 11.7 + 167.4 = 179.0$; $\theta_p = 104.8$; $A \sim 18769.1$
 e2) $\Sigma\theta_s = 63.4 + 167.4 = 230.7$; $\theta_p = 148.4$; $A \sim 34245.2$
 e3) $\Sigma\theta_s = 11.7 + 29.7 = 41.4$; $\theta_p = 31.6$; $A \sim 1306.3$
 e4) $\Sigma\theta_s = 63.4 + 29.7 = 93.1$; $\theta_p = 75.2$; $A \sim 6994.9$
 Smallest substrate area is occupied by solution e3 (d3)

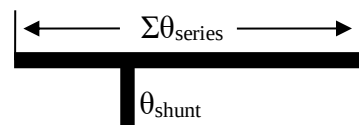

Subject no. 25

1. $y = Y/Y_0 = Z_0/Z = 60\Omega / (46.5 - j \cdot 58.2)\Omega = 0.503 + j \cdot 0.629$
2. $Y_0 = 0.02S$; $\Gamma = (Y_0 - Y) / (Y_0 + Y) = [0.02 - (0.0176 + j \cdot 0.0391)] / (0.02 + 0.0176 + j \cdot 0.0391)$
 $\Gamma = (-0.489) + j \cdot (-0.532) \leftrightarrow \text{Re}\Gamma + j \cdot \text{Im}\Gamma$ or $\Gamma = 0.722 \angle -132.6^\circ \leftrightarrow |\Gamma| \angle \arg(\Gamma)$
3. a) Lossless ring coupler, matched at the input; Isolation $I = D + C = 27.20\text{dB}$
 $P_{\text{in}} = 1.20\text{mW} = 0.792\text{dBm}$; $P_{\text{is}} = P_{\text{in}} - I = 0.792\text{dBm} - 27.20\text{dB} = -26.41\text{dBm} = 2.287\mu\text{W}$
 b) $L2, C5/2025$, $\beta = 10^{-C/20} = 0.562$, $y_1 = 0.562$, $y_2 = 0.827$, $Z_1 = Z_0/y_1 = 88.9\Omega$, $Z_2 = Z_0/y_2 = 60.5\Omega$
4. a) $Z_1 = \sqrt{(Z_0 \cdot R_L)} = \sqrt{(50 \cdot 43)\Omega} = 46.37\Omega$
 b) $Z_L = 43\Omega$ parallel with 0.38pF capacitor at $8.0\text{GHz} = 25.68\Omega + j \cdot (-21.09)\Omega$
 $\theta = \pi/4$, $\tan(\beta \cdot l) \rightarrow \infty$, $Z_{\text{in}} = Z_1^2/Z_L = Z_0 \cdot R_L/Z_L = 50.00\Omega + j \cdot (41.07)\Omega$
5. a) From the 6 possible combinations, 2 don't meet the required gain (1,2 ; 1,3).
 Valid combinations ($G > 17.35\text{dB}$): $G = G_1 + G_4 = 6.9 + 11.6 = 18.5\text{dB}$; $G = G_2 + G_3 = 8.9 + 9.1 = 18.0\text{dB}$; $G = G_2 + G_4 = 8.9 + 11.6 = 20.5\text{dB}$; $G = G_3 + G_4 = 9.1 + 11.6 = 20.7\text{dB}$;
 b) Friis Formula ($C10/2025$, $S50$), $F = F_a + (F_b - 1)/G_a$; We note that $F_1 < F_2 < F_3 < F_4$;
 From the 4 combinations that meet the gain requirement, we must compare only (1,4) and (2,3) because
 $F_2 + (F_3 - 1)/G_2 < F_2 + (F_4 - 1)/G_2$ and $F_2 + (F_3 - 1)/G_2 < F_3 + (F_4 - 1)/G_3$
 $F_1 = 0.62\text{dB} = 1.153$, $F_2 = 0.76\text{dB} = 1.191$, $F_3 = 1.00\text{dB} = 1.259$, $F_4 = 1.12\text{dB} = 1.294$, $G_1 = 6.9\text{dB} = 4.898$, $G_2 = 8.9\text{dB} = 7.762$; $F(1,4) = 1.153 + (1.294 - 1)/4.898 = 1.214 = 0.84\text{dB}$; $F(2,3) = 1.191 + (1.259 - 1)/7.762 = 1.229 = 0.90\text{dB}$;
 $F(1,4) < F(2,3) \rightarrow$ For minimal noise factor we must use devices 1,4
6. a) The transistor can be conjugately matched for maximum gain only if it is unconditionally stable:
 $|S_{11}| = 0.536 < 1$; $|S_{22}| = 0.299 < 1$; $K = 1.204 > 1$; $|\Delta| = |(-0.126) + j \cdot (-0.086)| = 0.153 < 1$
 b_1) $G_{\text{Tmax}} = |S_{21}|/|S_{12}| \cdot [K - \sqrt{(K^2 - 1)}] = 15.24 = 11.83\text{dB}$
 b_2) Complex calculus from $C9/2025$, $S70$:
 $B_1 = 1.174$; $C_1 = (-0.553) + j \cdot (-0.083)$; $\Gamma_S = (-0.721) + j \cdot (0.108) = 0.729 \angle 171.4^\circ$
 $B_2 = 0.779$; $C_2 = (-0.110) + j \cdot (-0.327)$; $\Gamma_L = (-0.193) + j \cdot (0.575) = 0.606 \angle 108.5^\circ$
 c) Complex calculus from $C7/2025$, $S112$, 2 solutions for the input/output match, $Z_0 = 50\Omega$ lines
 input: $\theta_{S1} = 162.7^\circ$; $\text{Im}(y_S) = -2.128$; $\theta_{p1} = 115.2^\circ$ or $\theta_{S2} = 25.9^\circ$; $\text{Im}(y_S) = 2.128$; $\theta_{p2} = 64.8^\circ$
 output: $\theta_{L1} = 9.4^\circ$; $\text{Im}(y_L) = -1.526$; $\theta_{p1} = 123.2^\circ$ or $\theta_{L2} = 62.1^\circ$; $\text{Im}(y_L) = 1.526$; $\theta_{p2} = 56.8^\circ$
 d) Second stage is identical to the first one, we can reuse c) results. There are 4 solutions (any offers the points) from the first stage output towards the second stage input (Pr.2025, $C12/2025, S140 \div 156$):
 d1) $\theta_{L1} = 9.4^\circ$; $\text{Im}(y_L) = -1.526 + (-2.128) = -3.653$; $\theta_{p1} = 105.3^\circ$; $\theta_{S1} = 162.7^\circ$;
 d2) $\theta_{L2} = 62.1^\circ$; $\text{Im}(y_L) = 1.526 + (-2.128) = -0.602$; $\theta_{p2} = 148.9^\circ$; $\theta_{S1} = 162.7^\circ$;
 d3) $\theta_{L1} = 9.4^\circ$; $\text{Im}(y_L) = -1.526 + (2.128) = 0.602$; $\theta_{p3} = 31.1^\circ$; $\theta_{S2} = 25.9^\circ$;
 d4) $\theta_{L2} = 62.1^\circ$; $\text{Im}(y_L) = 1.526 + (2.128) = 3.653$; $\theta_{p4} = 74.7^\circ$; $\theta_{S2} = 25.9^\circ$;
 e) We note that the electrical length $\theta = \beta \cdot l$ is proportional to the physical length and the layout is T shaped (series lines are perpendicular to the shunt stub), $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}} \sim \text{Substrate Area}$. We must compute all solutions for d) and compare individual products $\Sigma\theta_{\text{series}} \times \theta_{\text{shunt}}$.
 e1) $\Sigma\theta_s = 9.4 + 162.7 = 172.1$; $\theta_p = 105.3$; $A \sim 18120.9$
 e2) $\Sigma\theta_s = 62.1 + 162.7 = 224.7$; $\theta_p = 148.9$; $A \sim 33474.4$
 e3) $\Sigma\theta_s = 9.4 + 25.9 = 35.3$; $\theta_p = 31.1$; $A \sim 1096.2$
 e4) $\Sigma\theta_s = 62.1 + 25.9 = 88.0$; $\theta_p = 74.7$; $A \sim 6570.4$
 Smallest substrate area is occupied by solution e3 (d3)

