

Lecture 11

2025/2026

Microwave Devices and Circuits for Radiocommunications

2025/2026

- 2C/1L, **MDCR**
- Attendance at minimum 7 sessions (course or laboratory)
- Lectures- **associate professor Radu Damian**
 - Tuesday **12-14, P2**
 - E – 50% final grade
 - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
 - first test L1: 24.02.2026 (t2 and t3 not announced, lecture)
 - 3att.=+0.5p
 - all materials/equipments authorized


2025/2026

- Laboratory – **associate professor Radu Damian**
 - Monday 14-16, II.13 / (even weeks)
 - L – 25% final grade
 - ADS, 4 sessions
 - Attendance + **personal results**
 - P – 25% final grade
 - ADS, 3 sessions (-1? 24.02.2026)
 - personal homework

Impedance Matching


Impedance Matching with Stubs

Smith chart, $r=1$ and $g=1$

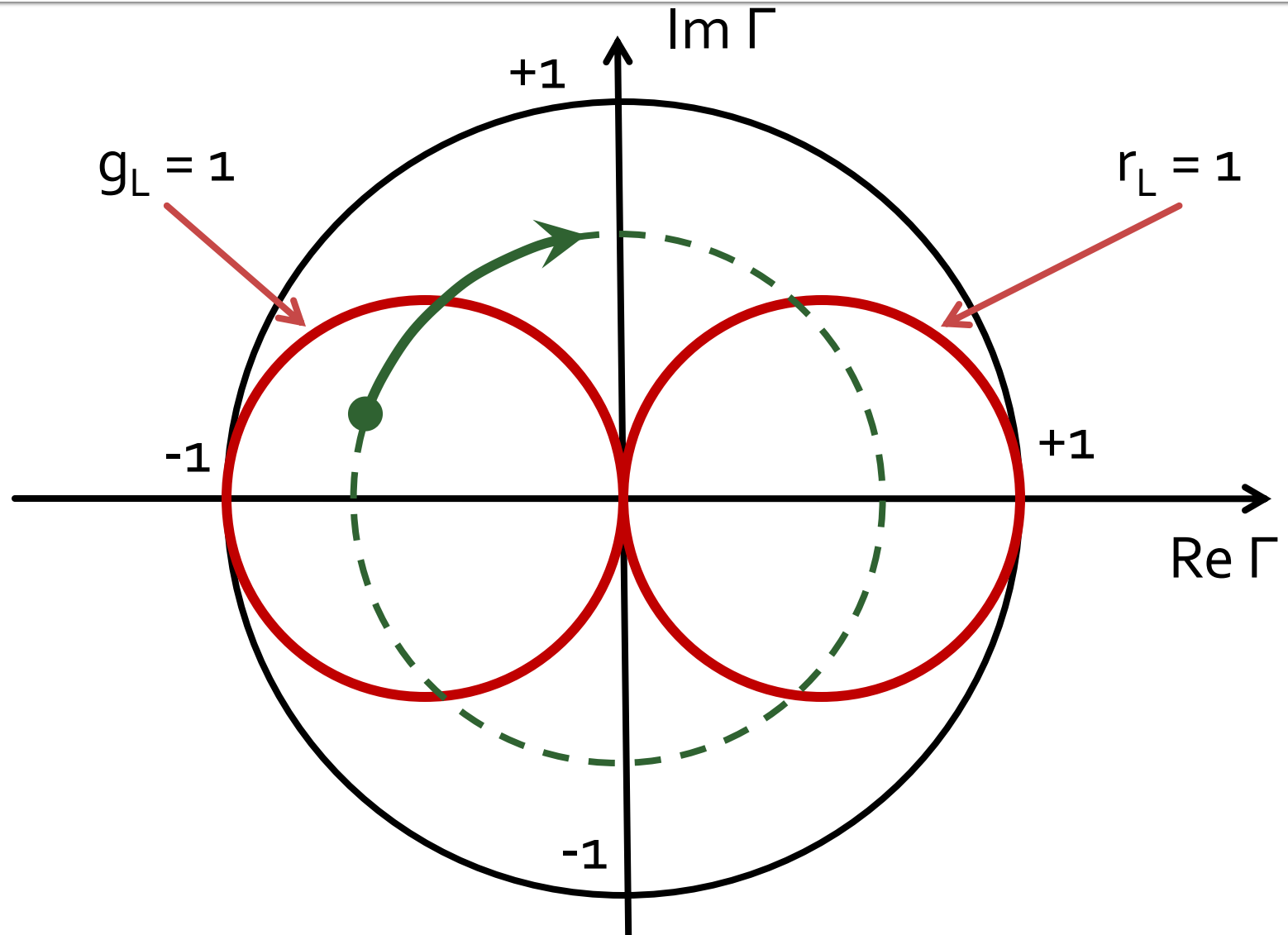


Single stub tuning

- Shunt Stub

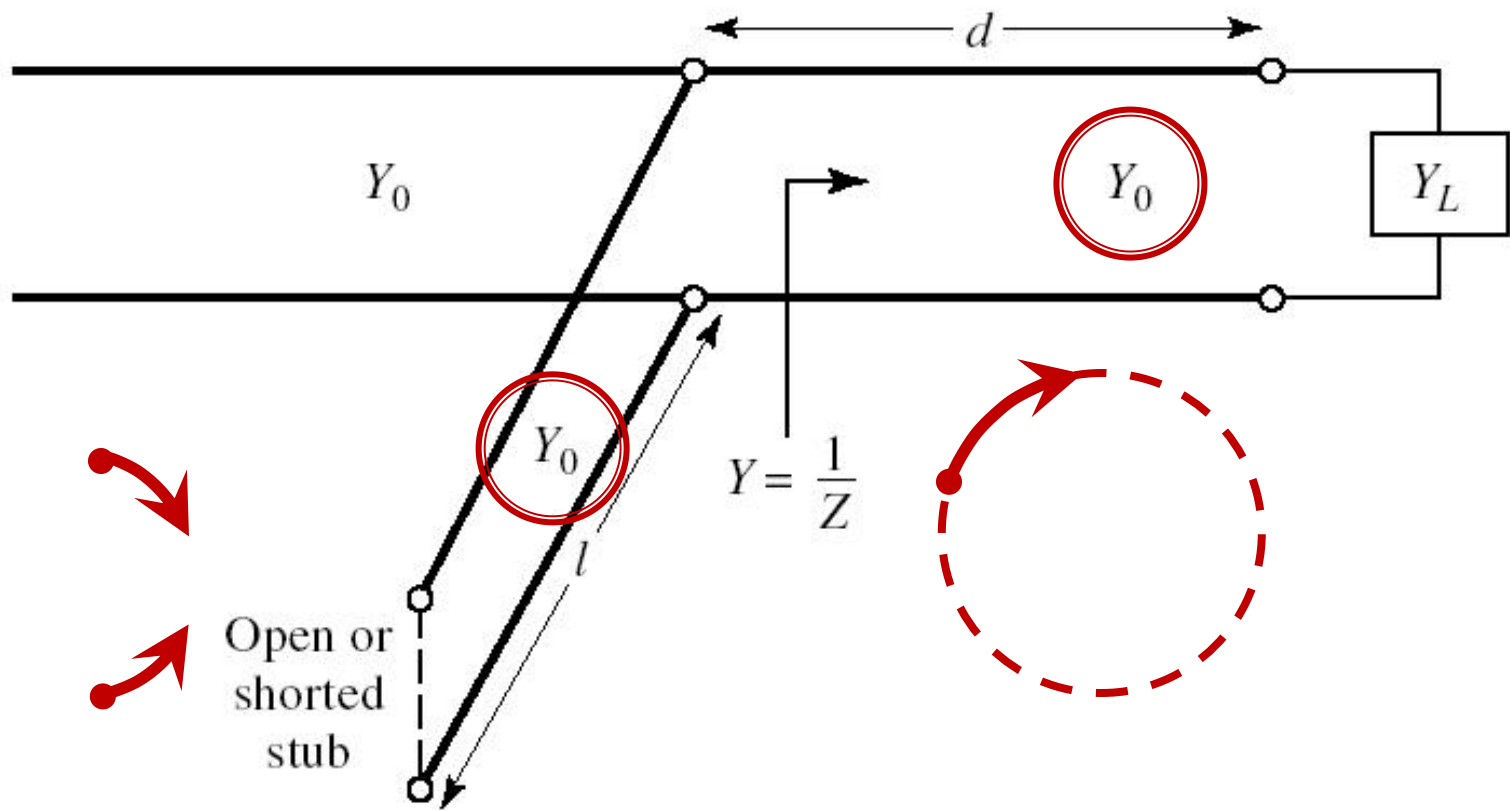

Single stub tuning

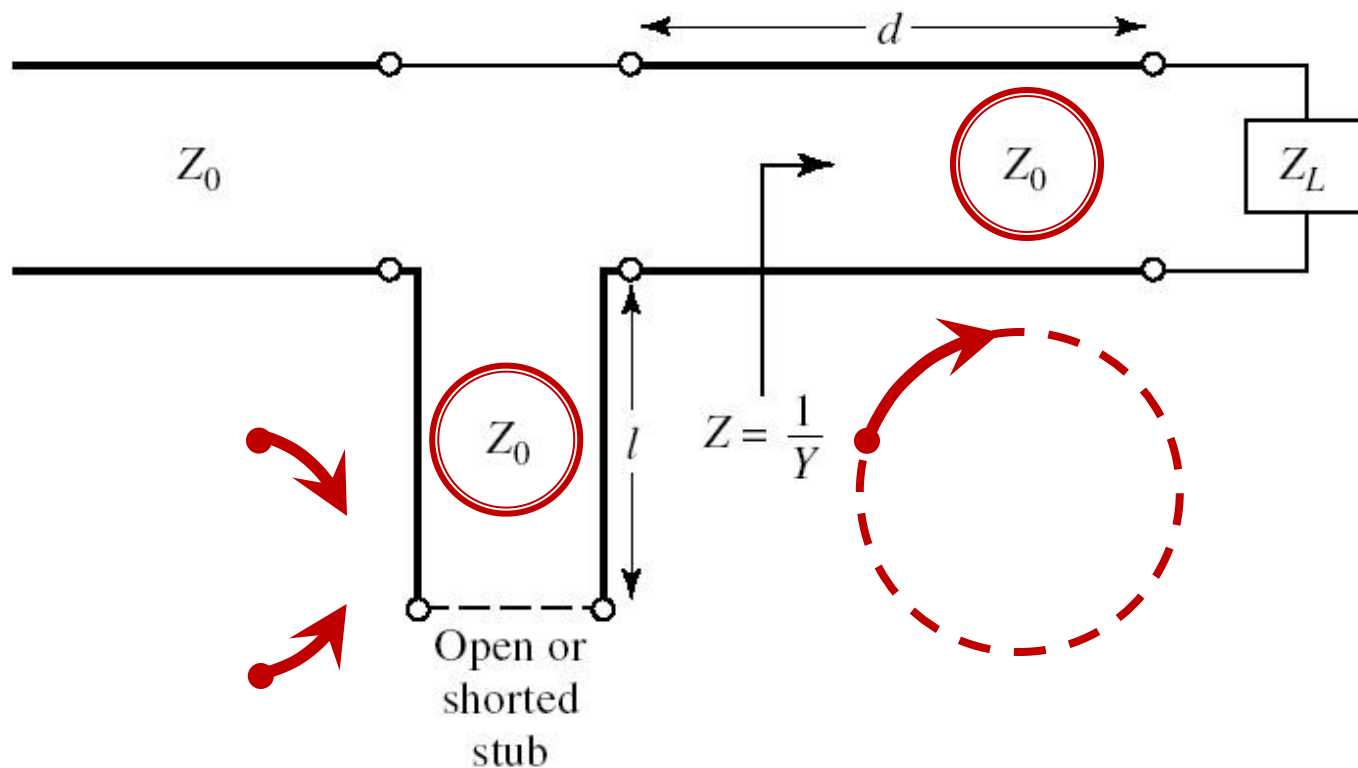- Series Stub
- difficult to realize in single conductor line technologies (microstrip)




Analytical solutions


Exam / Project

Case 1, Shunt Stub

- Shunt Stub

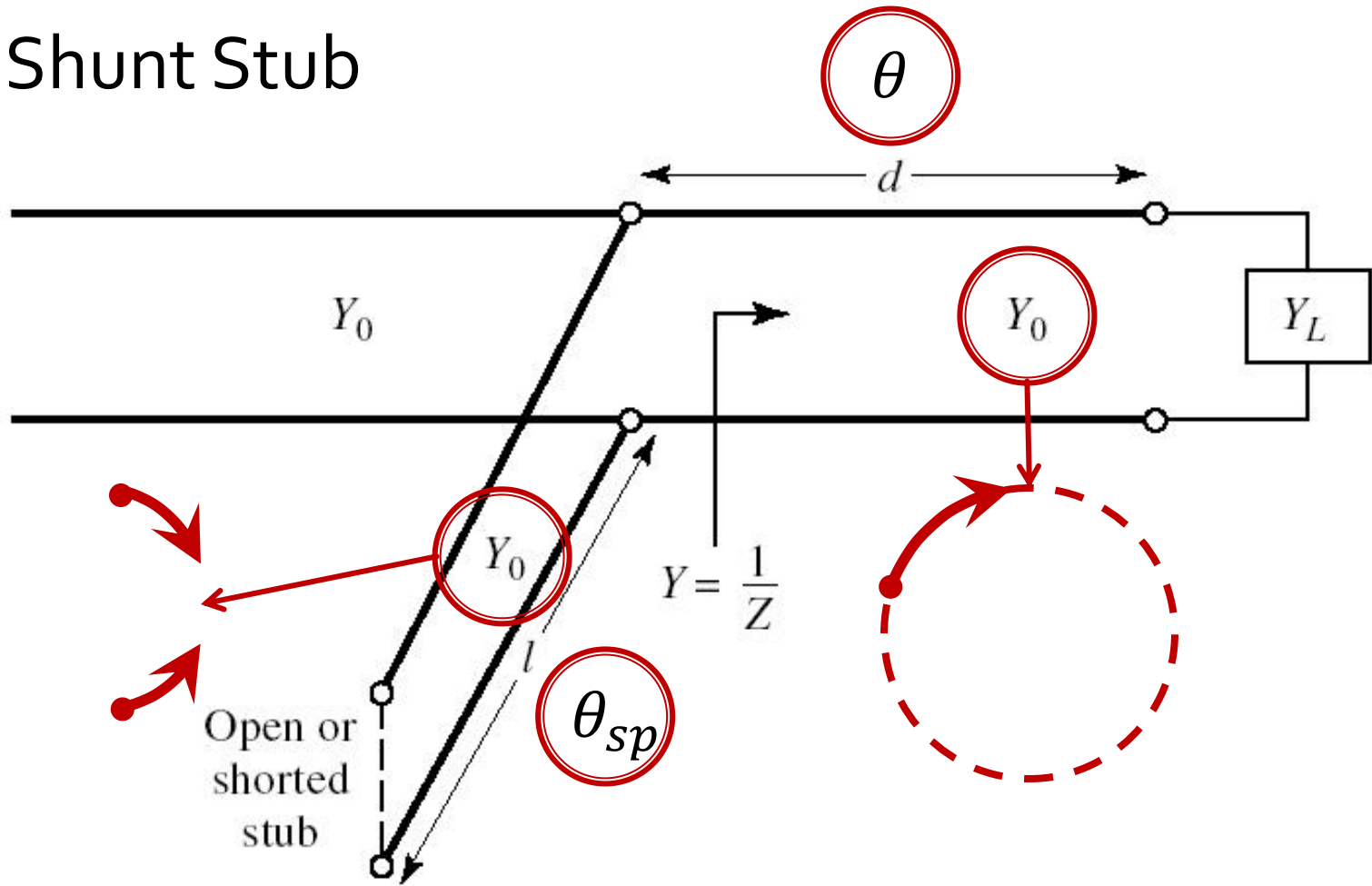

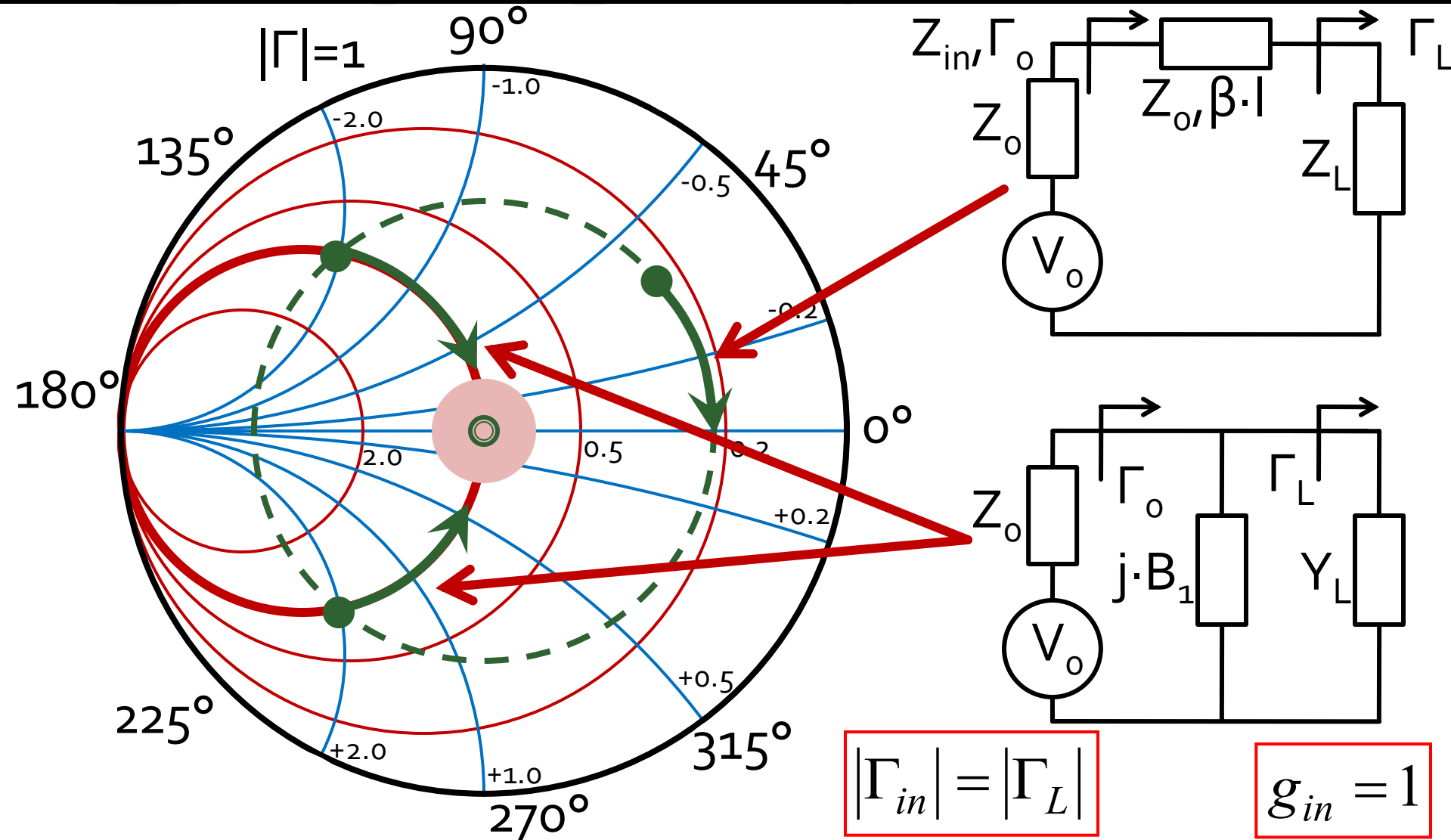Matching, series line + shunt susceptance



Analytical solution, usage

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = 0.593 \angle 46.85^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ \quad \cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- “+” solution ↓

$$(46.85^\circ + 2\theta) = +126.35^\circ \quad \theta = +39.7^\circ \quad \text{Im } y_S = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.472$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_S) = -55.8^\circ (+180^\circ) \rightarrow \theta_{sp} = 124.2^\circ$$

- “-” solution ↓

$$(46.85^\circ + 2\theta) = -126.35^\circ \quad \theta = -86.6^\circ (+180^\circ) \rightarrow \theta = 93.4^\circ$$

$$\text{Im } y_S = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +1.472 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_S) = 55.8^\circ$$

Analytical solution, usage

$$(\varphi + 2\theta) = \begin{cases} +126.35^\circ \\ -126.35^\circ \end{cases} \quad \theta = \begin{cases} 39.7^\circ \\ 93.4^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -1.472 \\ +1.472 \end{cases} \quad \theta_{sp} = \begin{cases} -55.8^\circ + 180^\circ = 124.2^\circ \\ +55.8^\circ \end{cases}$$



- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

$$l_1 = \frac{39.7^\circ}{360^\circ} \cdot \lambda = 0.110 \cdot \lambda$$

$$l_2 = \frac{124.2^\circ}{360^\circ} \cdot \lambda = 0.345 \cdot \lambda$$


$$l_1 = \frac{93.4^\circ}{360^\circ} \cdot \lambda = 0.259 \cdot \lambda$$
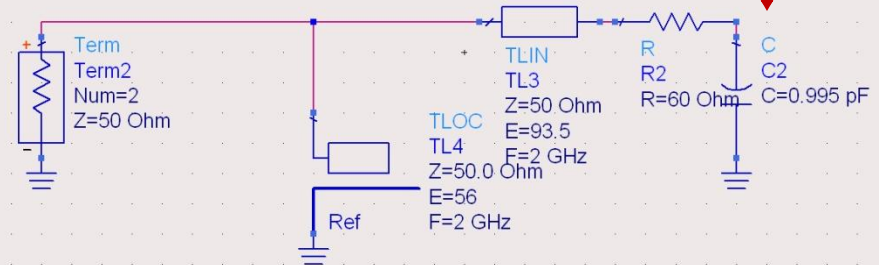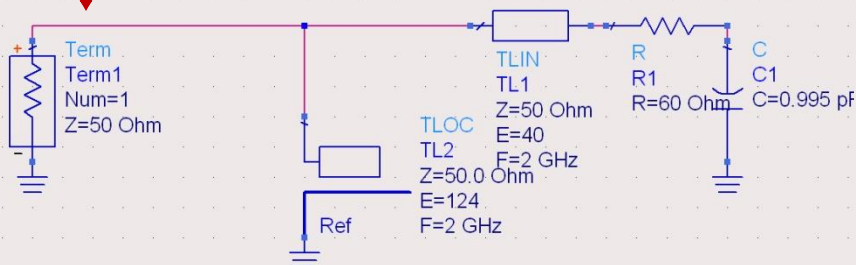
$$l_2 = \frac{55.8^\circ}{360^\circ} \cdot \lambda = 0.155 \cdot \lambda$$






Case 2, Series Stub

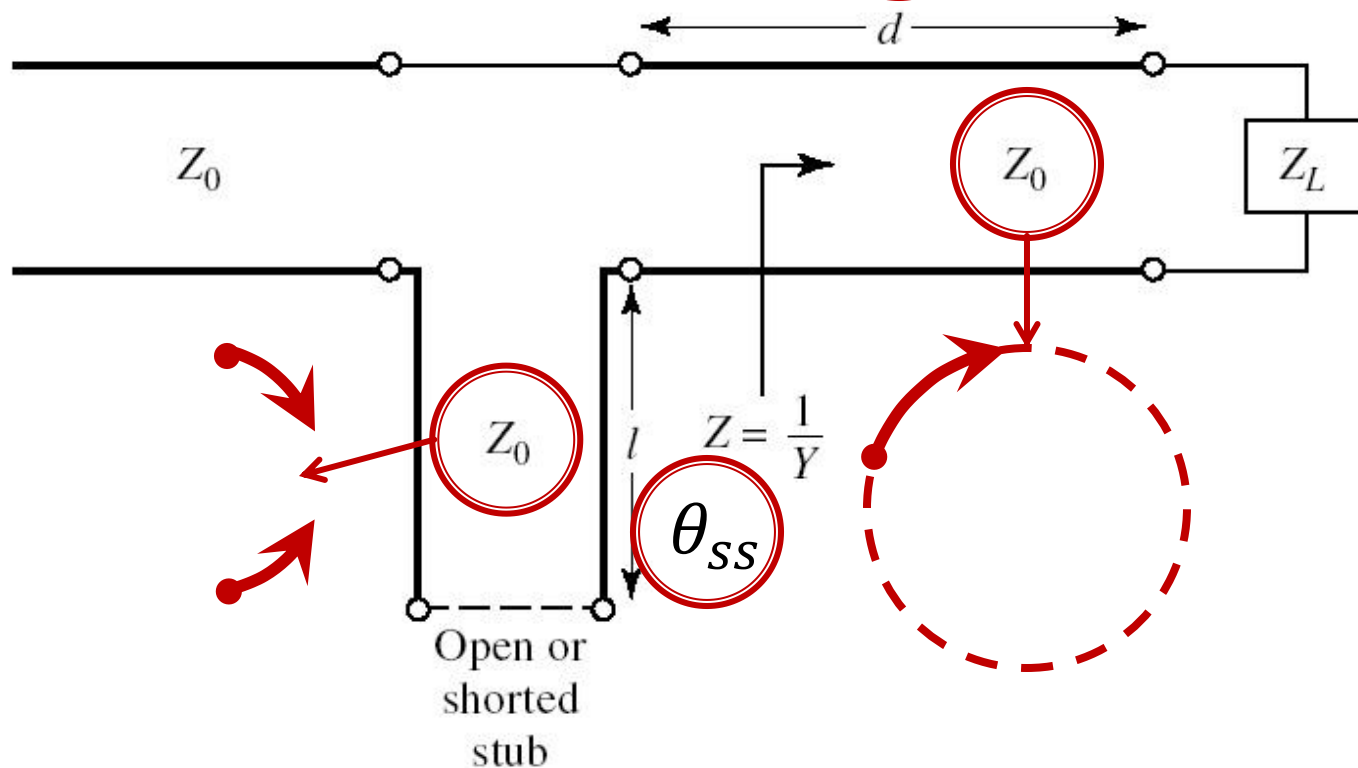- Series Stub
- difficult to realize in single conductor line technologies (microstrip) θ



Matching, series line + series reactance

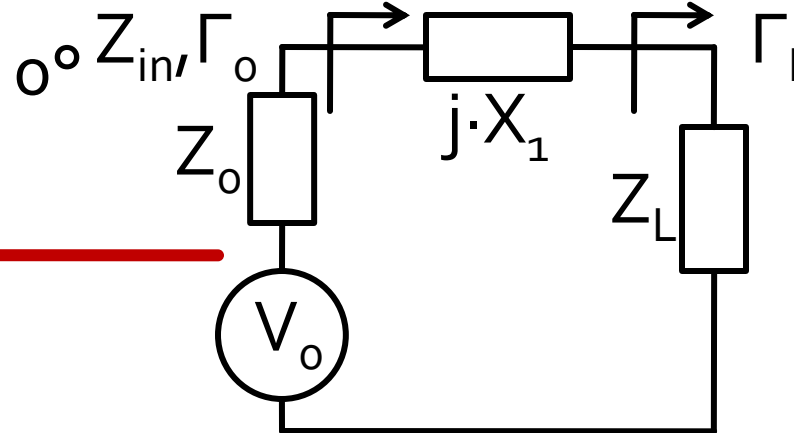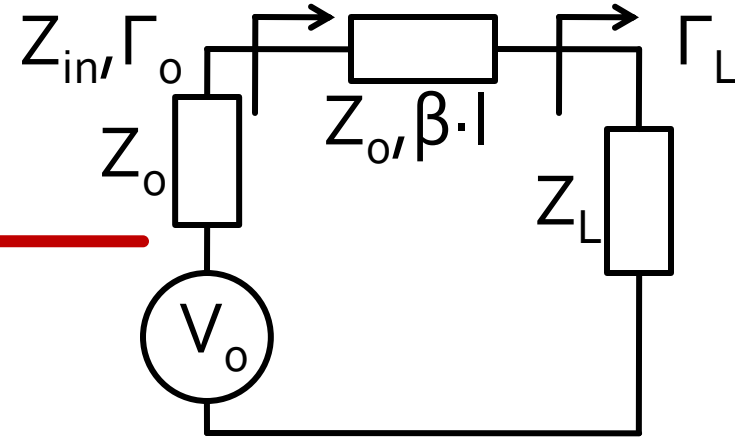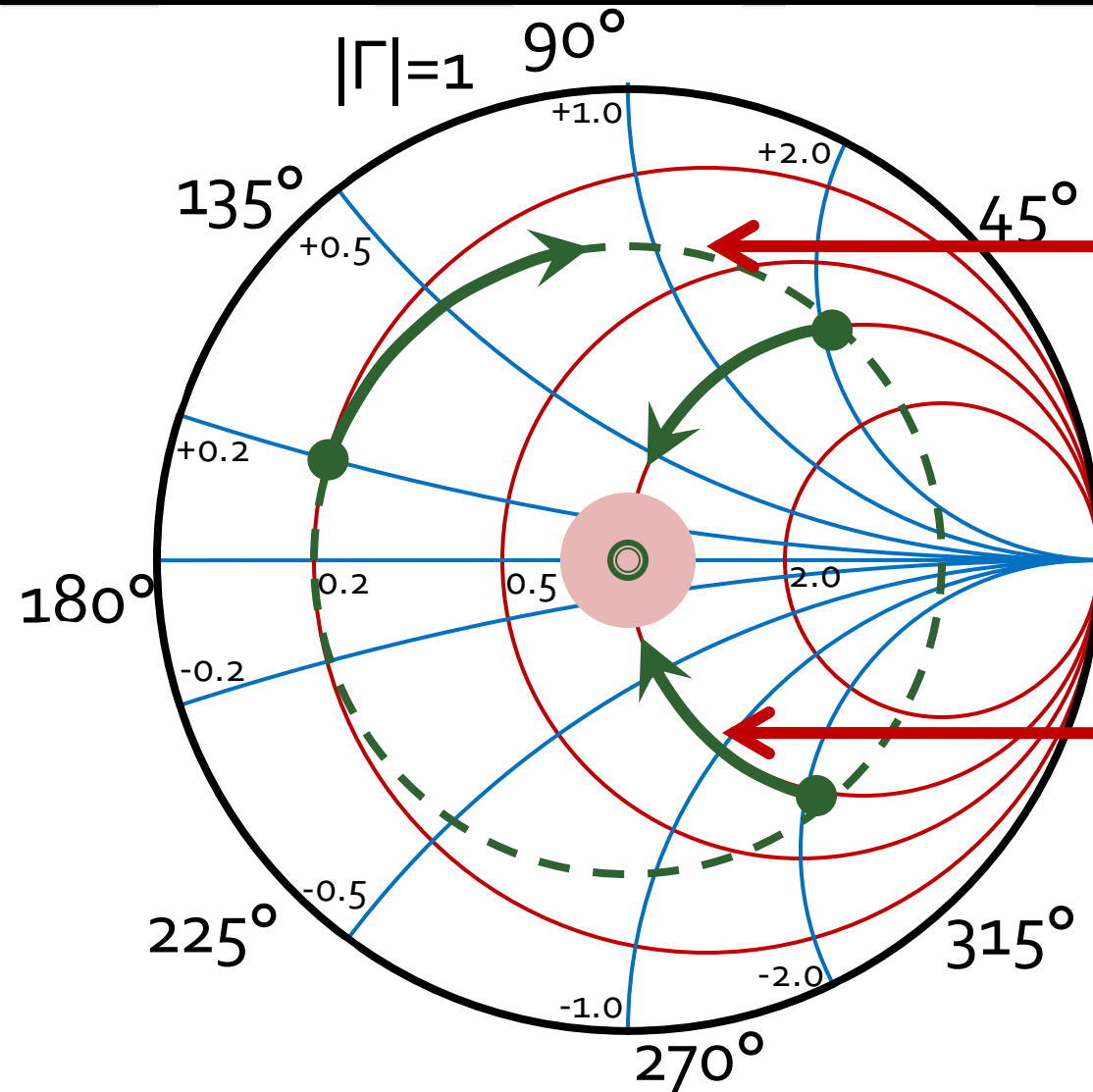

$$|\Gamma_{in}| = |\Gamma_L|$$

$$r_{in} = 1$$

Analytical solution, usage

$$\cos(\varphi + 2\theta) = |\Gamma_S|$$

$$\theta_{ss} = \beta \cdot l = \cot^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$\Gamma_S = 0.555 \angle -29.92^\circ$$

$$|\Gamma_S| = 0.555; \quad \varphi = -29.92^\circ \quad \cos(\varphi + 2\theta) = 0.555 \Rightarrow (\varphi + 2\theta) = \pm 56.28^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

- **"+" solution** ↓

$$(-29.92^\circ + 2\theta) = +56.28^\circ \quad \theta = 43.1^\circ \quad \text{Im } z_S = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +1.335$$

$$\theta_{ss} = -\cot^{-1}(\text{Im } z_S) = -36.8^\circ (+180^\circ) \rightarrow \theta_{ss} = 143.2^\circ$$

- **"-" solution** ↓

$$(-29.92^\circ + 2\theta) = -56.28^\circ \quad \theta = -13.2^\circ (+180^\circ) \rightarrow \theta = 166.8^\circ$$

$$\text{Im } z_S = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.335 \quad \theta_{ss} = -\cot^{-1}(\text{Im } z_S) = 36.8^\circ$$

Analytical solution, usage

$$(\varphi + 2\theta) = \begin{cases} +56.28^\circ \\ -56.28^\circ \end{cases} \quad \theta = \begin{cases} 43.1^\circ \\ 166.8^\circ \end{cases} \quad \text{Im}[z_s(\theta)] = \begin{cases} +1.335 \\ -1.335 \end{cases} \quad \theta_{ss} = \begin{cases} -36.8^\circ + 180^\circ = 143.2^\circ \\ +36.8^\circ \end{cases}$$

- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

$$l_1 = \frac{43.1^\circ}{360^\circ} \cdot \lambda = 0.120 \cdot \lambda$$

$$l_2 = \frac{143.2^\circ}{360^\circ} \cdot \lambda = 0.398 \cdot \lambda$$

$$l_1 = \frac{166.8^\circ}{360^\circ} \cdot \lambda = 0.463 \cdot \lambda$$

$$l_2 = \frac{36.8^\circ}{360^\circ} \cdot \lambda = 0.102 \cdot \lambda$$



Stub, observations

- adding or subtracting **180°** ($\lambda/2$) doesn't change the result (full rotation around the Smith Chart)

$$E = \beta \cdot l = \pi = 180^\circ \quad l = k \cdot \frac{\lambda}{2}, \forall k \in \mathbf{N}$$

- if the lines/stubs result with **negative** "length"/ "electrical length" we add $\lambda/2$ / 180° to obtain physically realizable lines
- adding or subtracting **90°** ($\lambda/4$) change the stub impedance:

$$Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l \quad \Leftrightarrow \quad Z_{in,g} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$


- for the stub we can add or subtract 90° ($\lambda/4$) while in the same time changing **open-circuit** \Leftrightarrow **short-circuit**

Microwave Amplifiers

Course Topics

- Transmission lines
- Impedance matching and tuning
- Directional couplers
- Power dividers
- **Microwave amplifier design**
- Microwave filters
- ~~Oscillators and mixers?~~


Amplifier as two-port

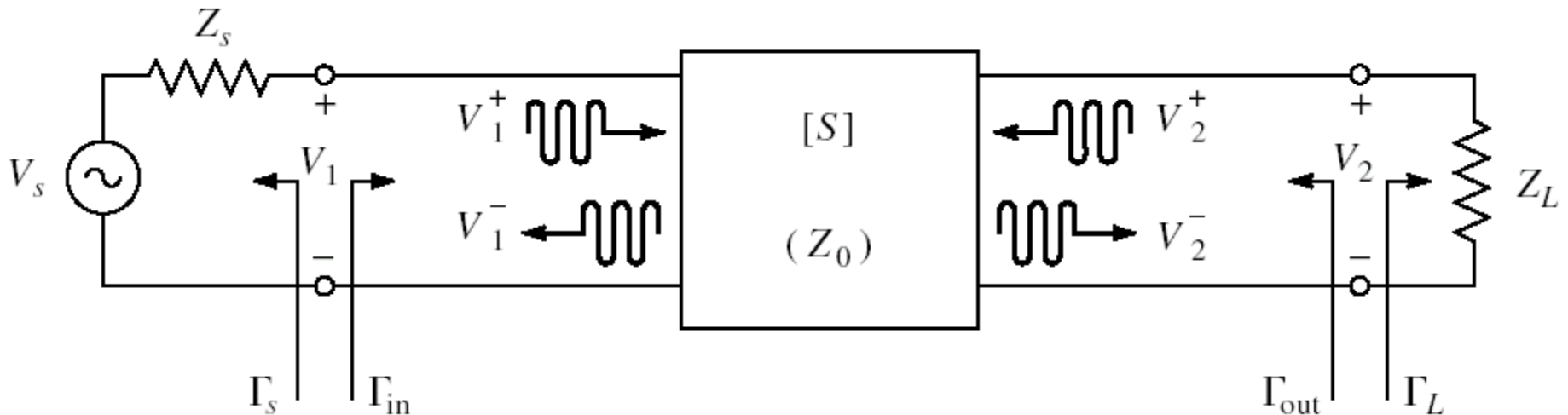

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_s}{1 - S_{11} \cdot \Gamma_s}$$

Amplifier as two-port

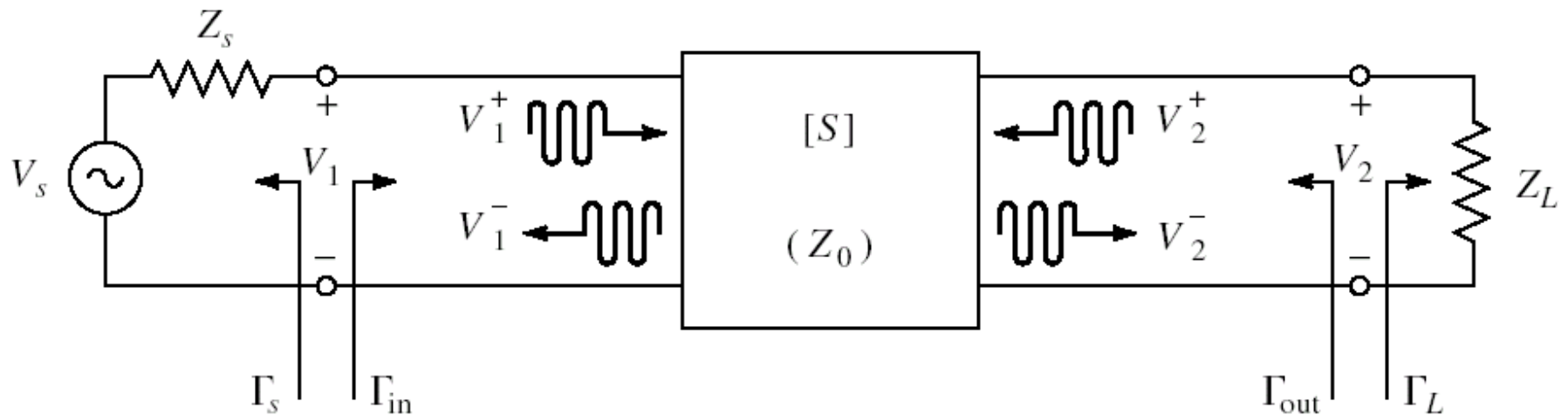

- For an amplifier two-port we are interested in:
 - **stability**
 - power gain
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)

Output stability circle (CSOUT)

$$\left| \Gamma_L - \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12} \cdot S_{21}}{|S_{22}|^2 - |\Delta|^2} \right| \quad |\Gamma_L - C_L| = R_L$$


- We obtain the equation of a circle in the complex plane, which represents the locus of Γ_L for the **limit between stability and instability** ($|\Gamma_{in}| = 1$)
- This circle is the **output stability circle** (Γ_L)

$$C_L = \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \quad R_L = \frac{|S_{12} \cdot S_{21}|}{\left| |S_{22}|^2 - |\Delta|^2 \right|}$$


3D representation of $|\Gamma_{in}|$, $|\Gamma_{out}|$, $|\Gamma|=1$

- $|\Gamma| = 1 \rightarrow \log_{10}|\Gamma| = 0$, the intersection with the plane $z = 0$ is a circle

$\log(\Gamma_{in}(\Gamma_L))$

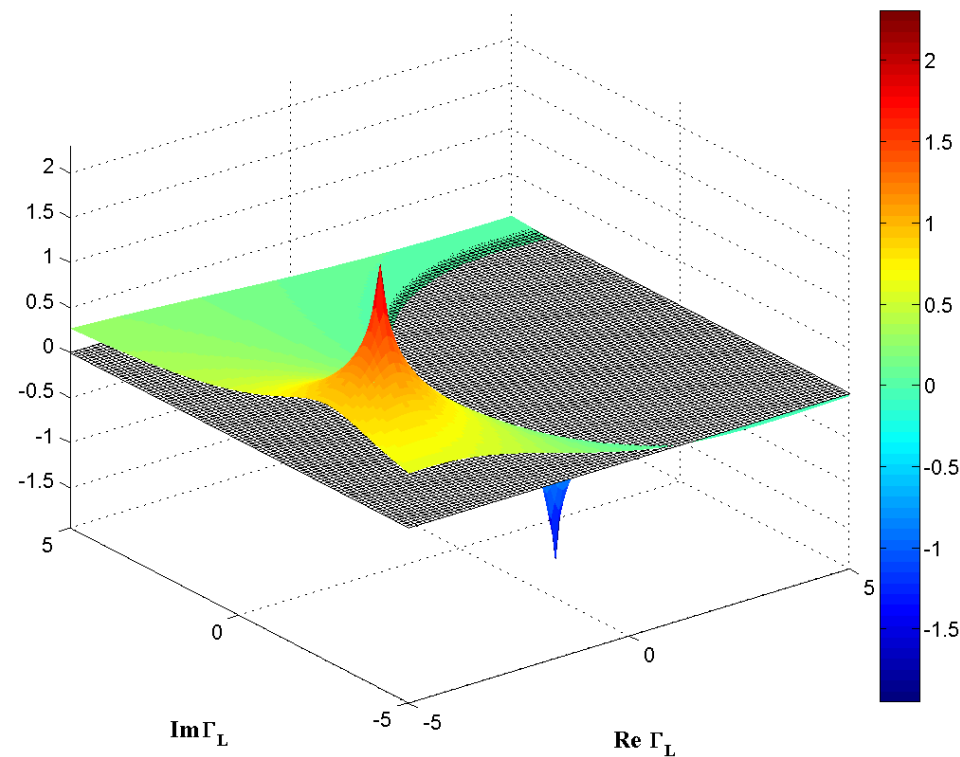


$\log(\Gamma_{out}(\Gamma_S))$


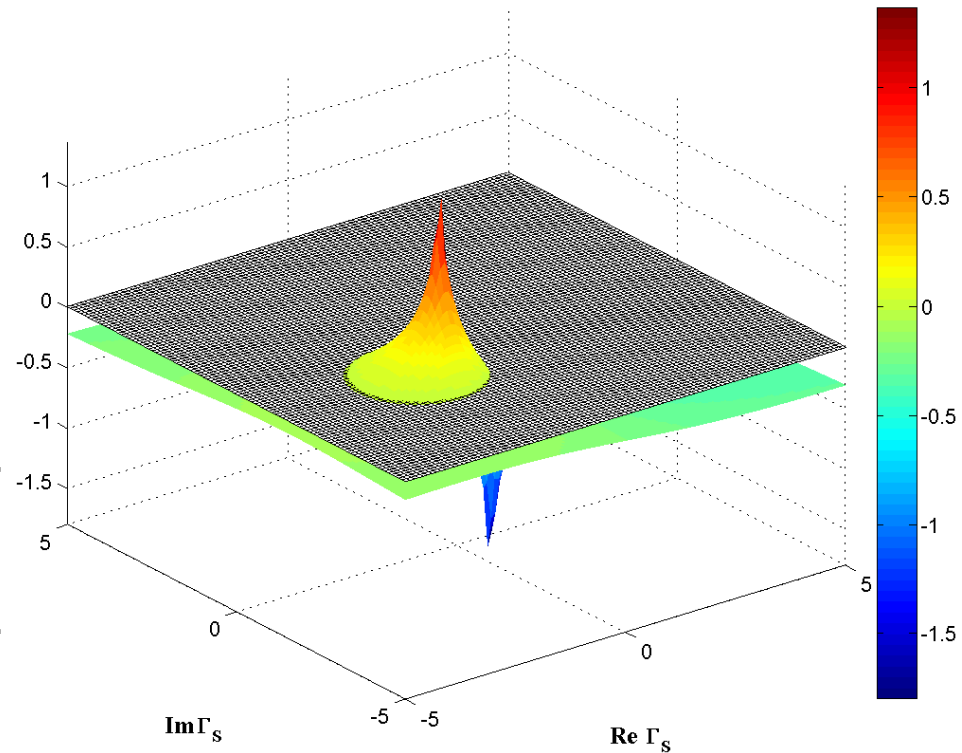


Contour map/lines


contoured peak
(side view)

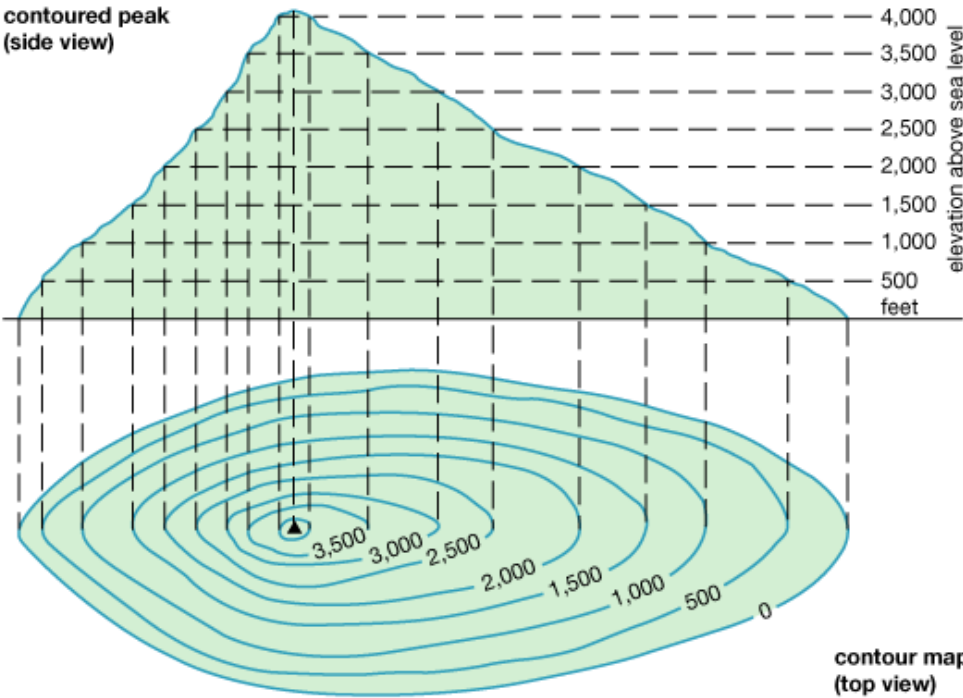



© 2011 Encyclopædia Britannica, Inc.

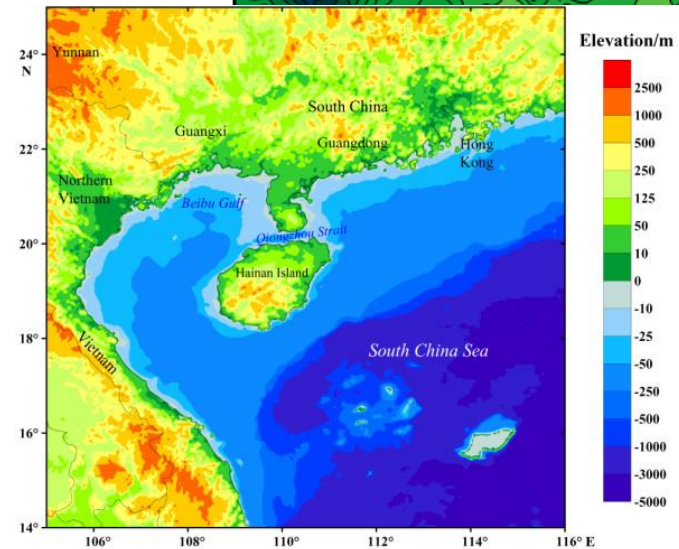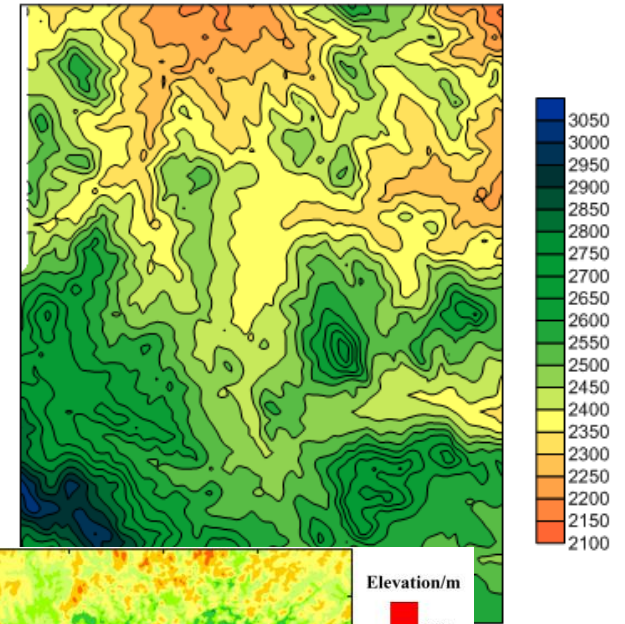

Several possible positioning


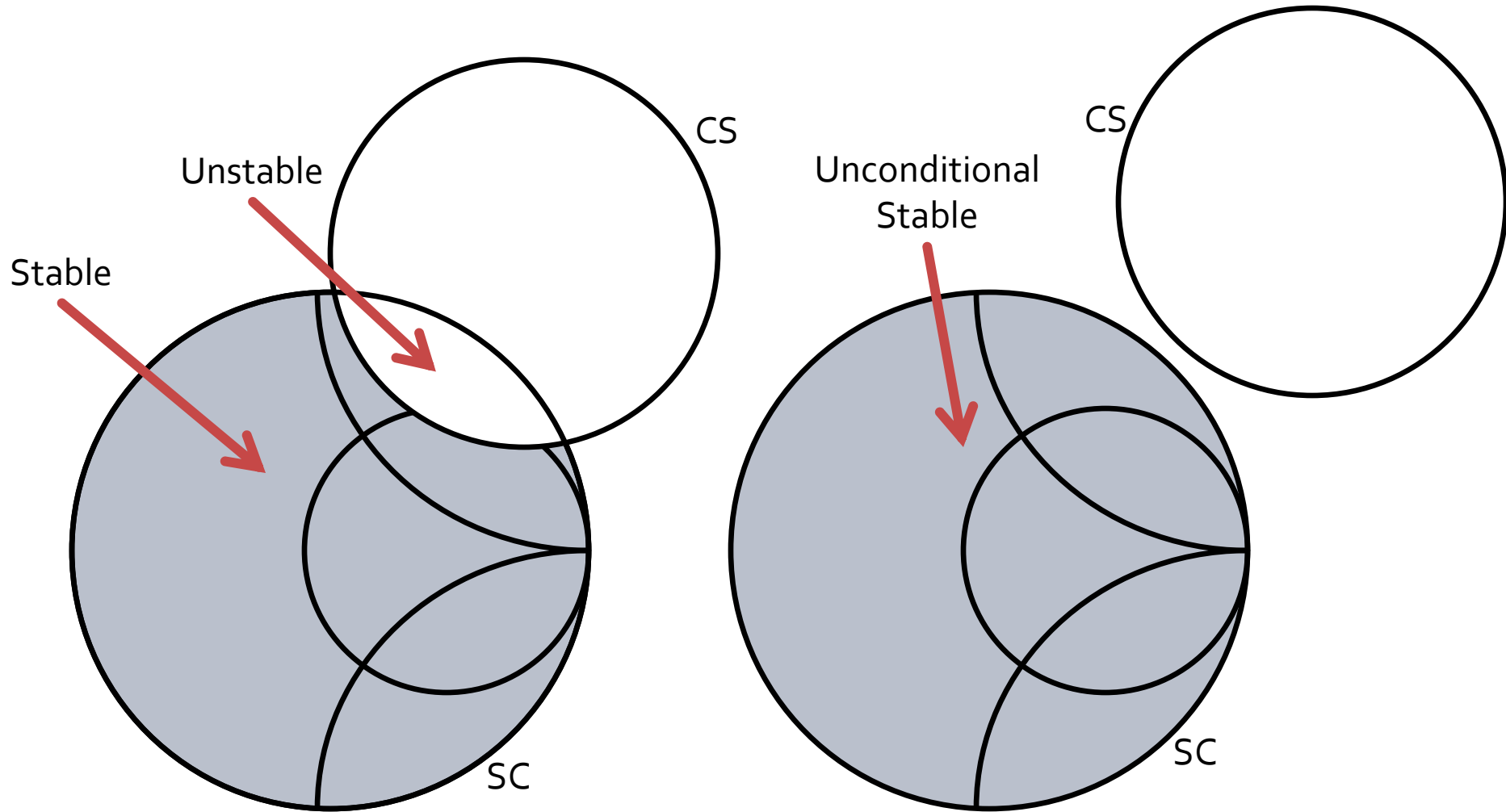


Several possible positioning

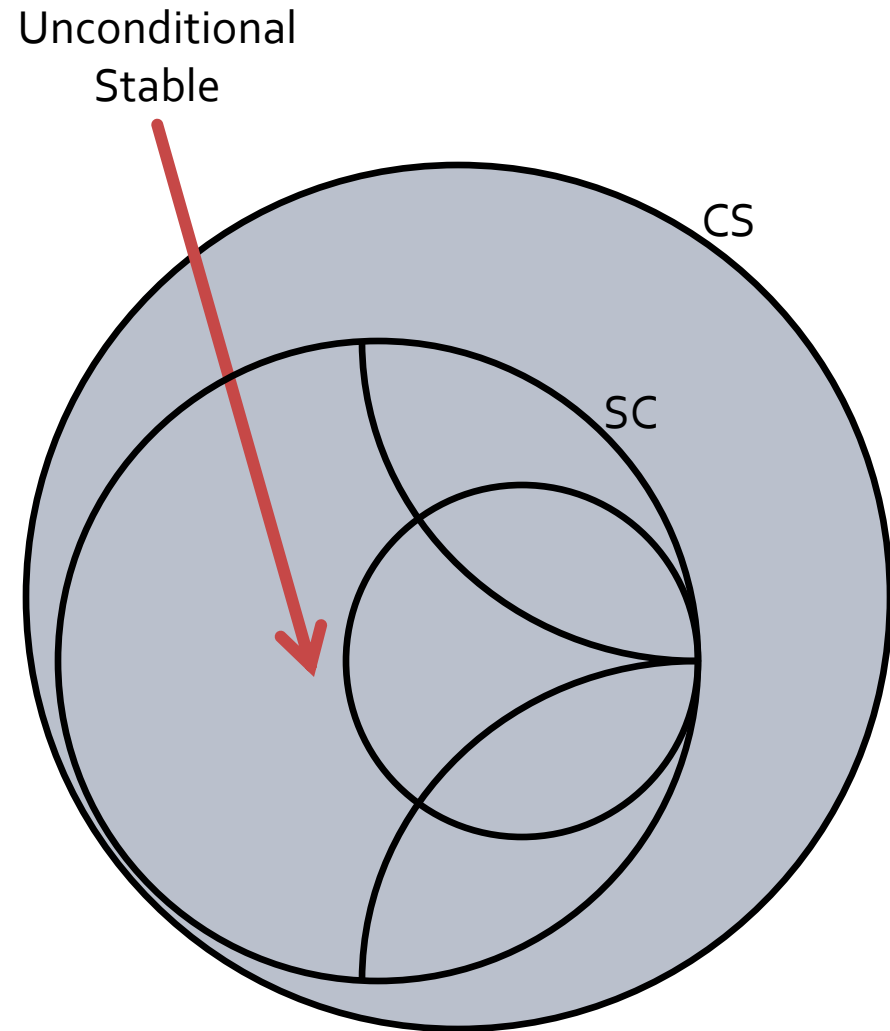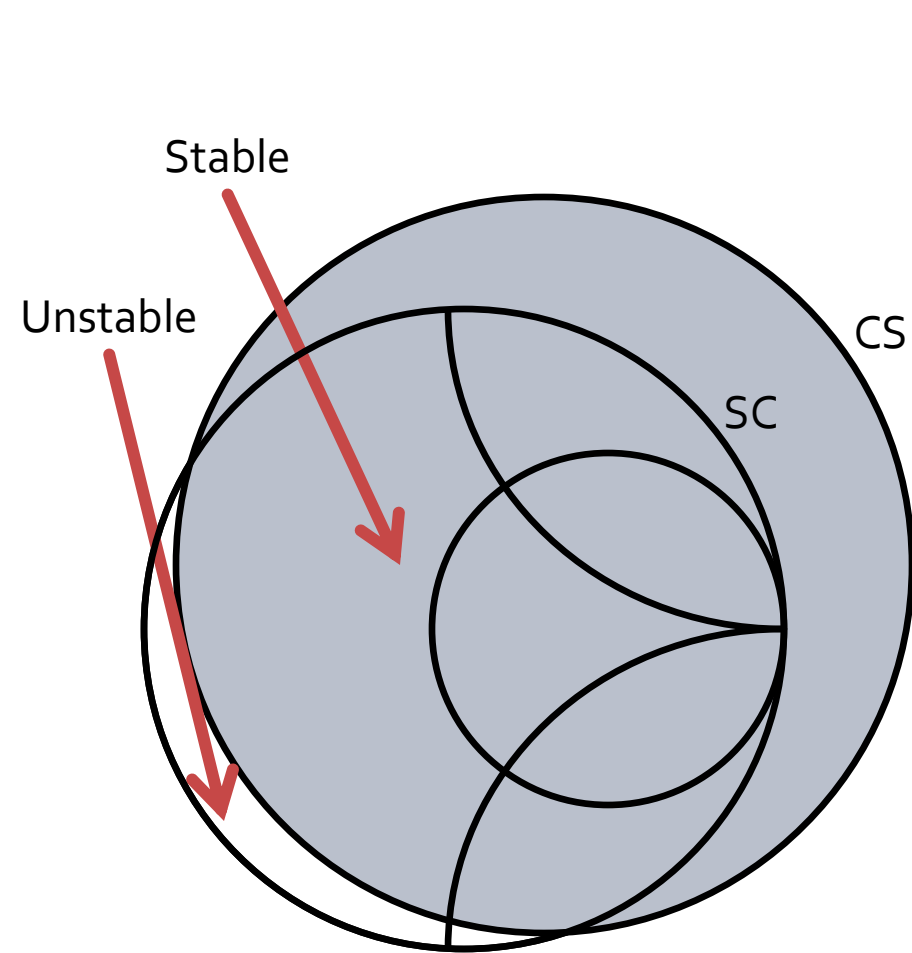


Stability

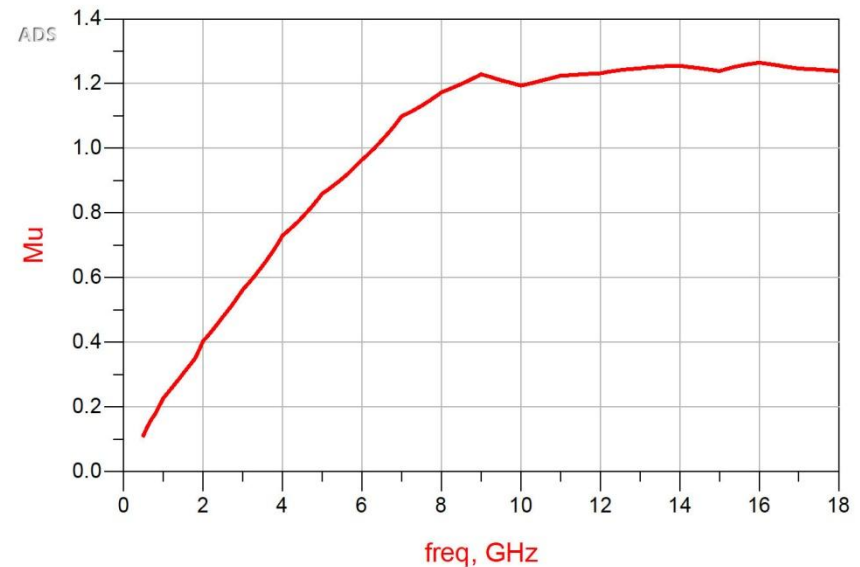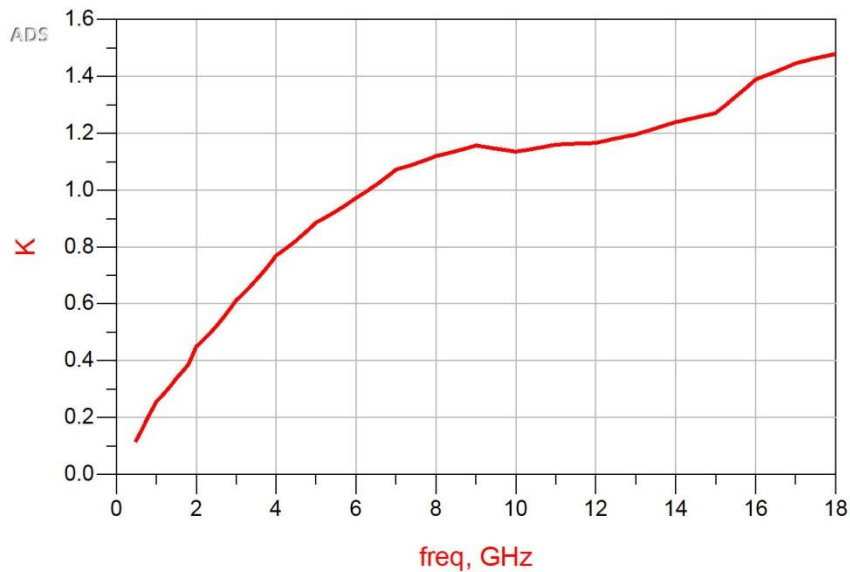- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz
- unconditionally stable for $f > 6.31GHz$




Amplifier as two-port

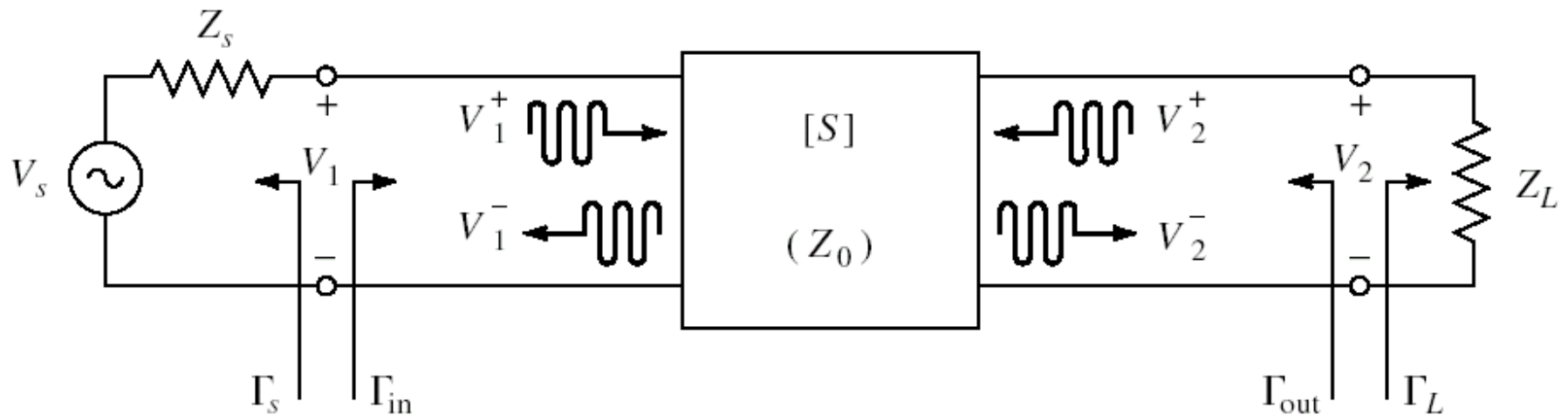

- For an amplifier two-port we are interested in:
 - stability
 - **power gain**
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)

Power / Matching

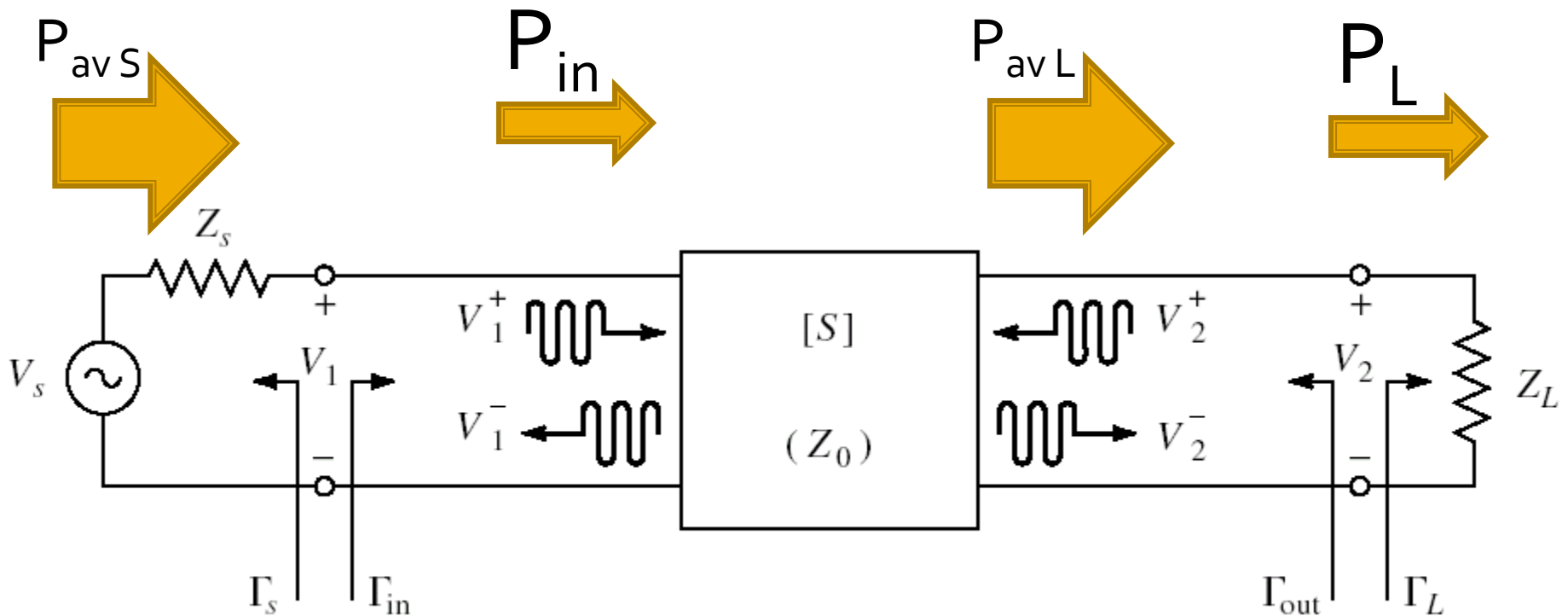- Two ports in which matching influences the power transfer



Two-Port Power Gains

- **Available** power gain

$$G_A = \frac{P_{av L}}{P_{av S}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2)}{|1 - S_{22} \cdot \Gamma_L|^2 \cdot (1 - |\Gamma_{out}|^2)}$$

- **Transducer** power gain

$$G_T = \frac{P_L}{P_{av S}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2}$$

$$\Gamma_{in} = \Gamma_{in}(\Gamma_L)$$

- **Unilateral transducer** power gain


$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$S_{12} \cong 0$$

$$\Gamma_{in} = S_{11}$$

Input and output can be treated independently

Design for Maximum Gain

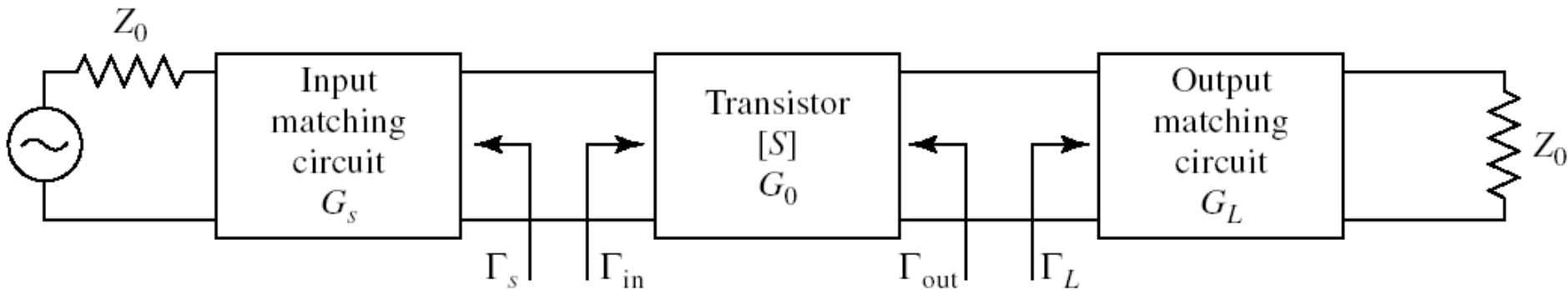

- Maximum power gain (complex conjugate matching):

$$\Gamma_{in} = \Gamma_S^* \quad \Gamma_{out} = \Gamma_L^*$$

- For lossless matching sections

$$G_{T \max} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2} \quad G_{T \max} = \frac{1}{1 - |\Gamma_S|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

- For the general case of the bilateral transistor ($S_{12} \neq 0$)

Γ_{in} and Γ_{out} depend on each other so the input and output sections must be matched simultaneously

Simultaneous matching

- Simultaneous matching can be achieved **if and only if** the amplifier is **unconditionally stable** at the operating frequency, and $|\Gamma| < 1$ solutions are those with “–” sign of quadratic solutions

$$\Gamma_S = \frac{B_1 - \sqrt{B_1^2 - 4 \cdot |C_1|^2}}{2 \cdot C_1}$$


$$\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta \cdot S_{22}^* \end{cases}$$

$$\Gamma_L = \frac{B_2 - \sqrt{B_2^2 - 4 \cdot |C_2|^2}}{2 \cdot C_2}$$

$$\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta \cdot S_{11}^* \end{cases}$$

Design for Specified Gain

- Assumes the amplifier device **unilateral**

$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$


Input and output can be treated independently

$$S_{12} \cong 0$$

$$\Gamma_{in} = S_{11}$$

- Maximum power gain

$$\Gamma_S = S_{11}^*$$

$$\Gamma_L = S_{22}^*$$

$$G_{TU \max} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2}$$

Unilateral figure of merit


- Allows estimation of the error introduced by the unilateral assumption

$$\frac{1}{(1+U)^2} < \frac{G_T}{G_{TU}} < \frac{1}{(1-U)^2} \quad U = \frac{|S_{12}| \cdot |S_{21}| \cdot |S_{11}| \cdot |S_{22}|}{(1-|S_{11}|^2) \cdot (1-|S_{22}|^2)}$$

- We compute U then the maximum and minimum deviation of G_{TU} from G_T
 - this deviation must be accounted in the design as a reserve gain against the target gain

$$-20 \cdot \log(1+U) < G_T [dB] - G_{TU} [dB] < -20 \cdot \log(1-U)$$

Design for Specified Gain

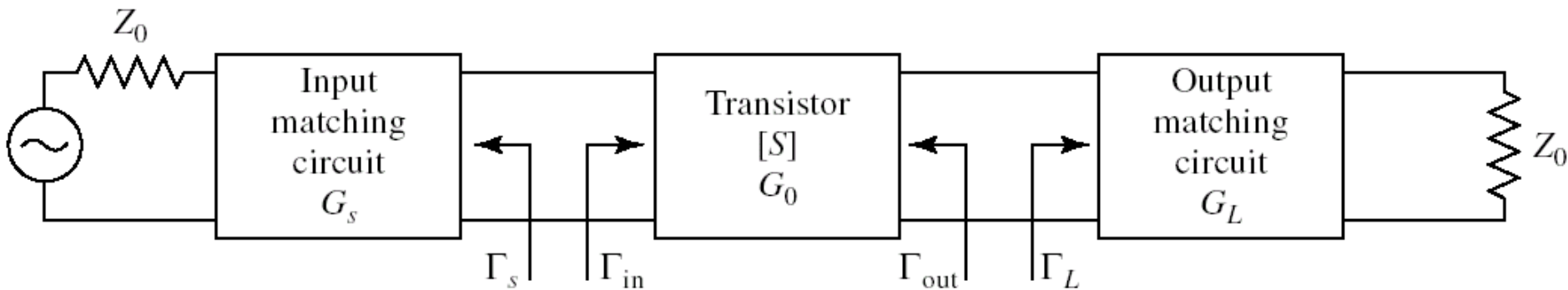

- In the unilateral assumption:

$$G_{TU} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2}$$


$$G_S = G_S(\Gamma_S)$$

$$G_0 = |S_{21}|^2$$

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$


$$G_L = G_L(\Gamma_L)$$

$G_S(\Gamma_S)$

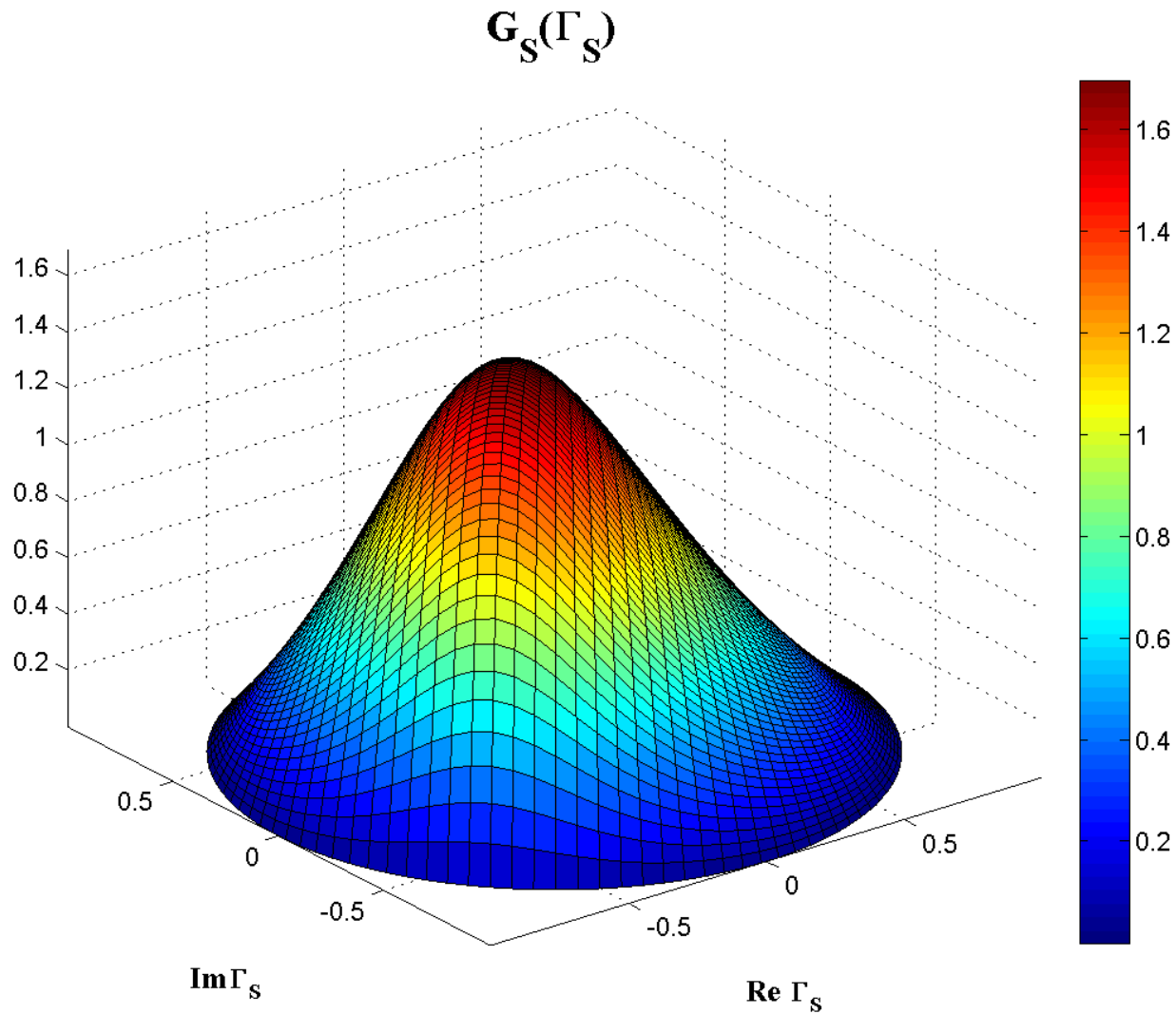


$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2}$$


Contour map/lines

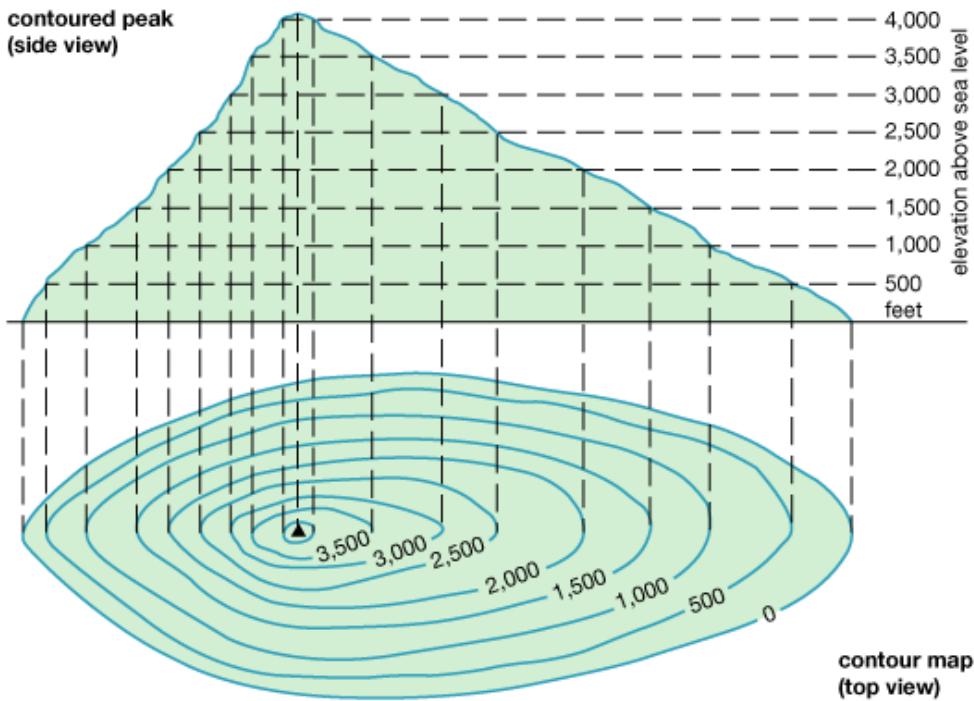

© 2011 Encyclopædia Britannica, Inc.

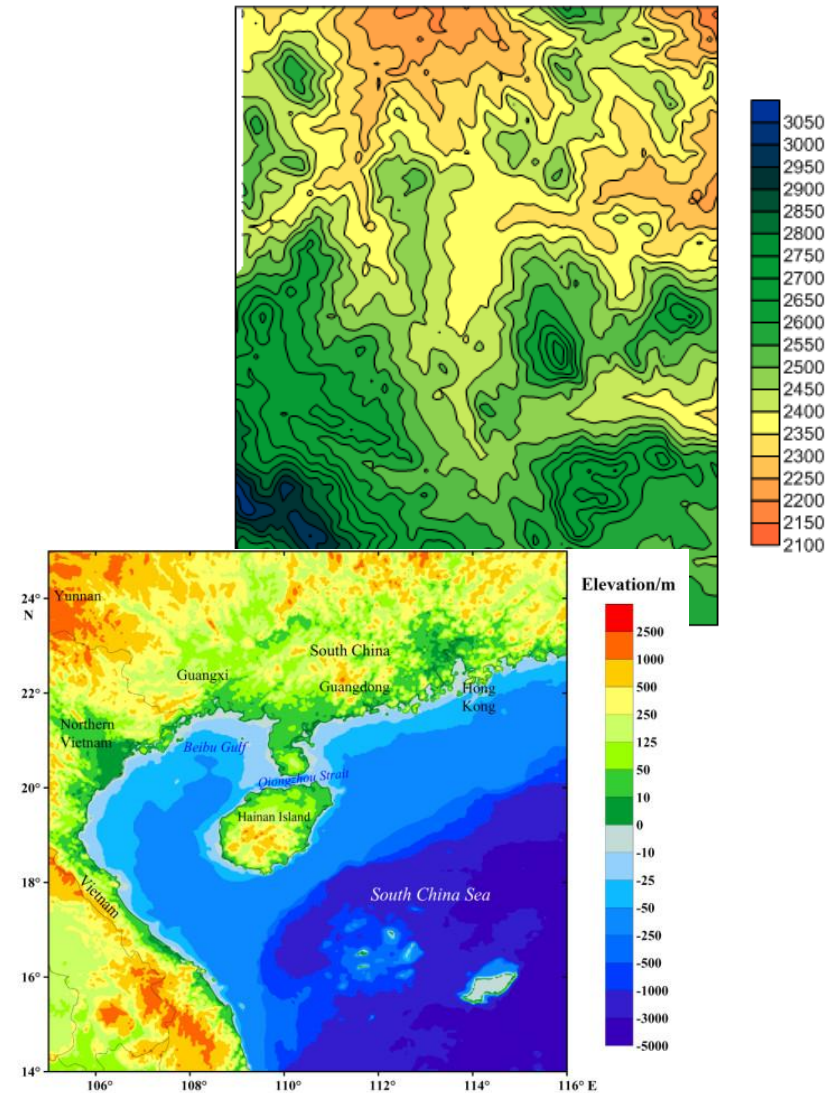

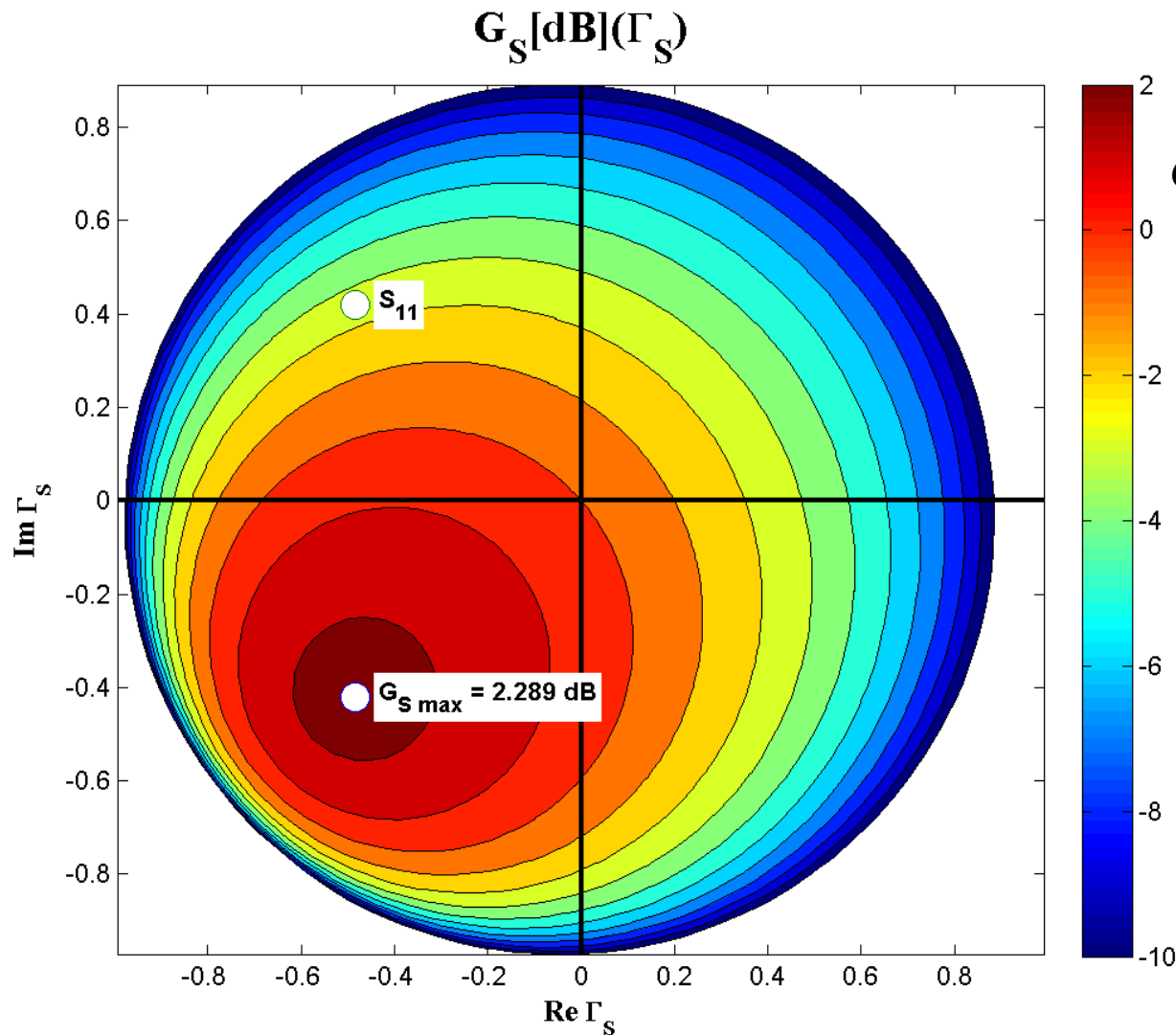$G_S[\text{dB}](\Gamma_S)$, constant value contours



$$G_S[\text{dB}] = 10 \cdot \log \left(\frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \right)$$

$$G_{S \text{ max}} = G_S \Big|_{\Gamma_S = S_{11}^*}$$


Input section constant gain circles

$$\left| \Gamma_S - \frac{g_S \cdot S_{11}^*}{1 - (1 - g_S) \cdot |S_{11}|^2} \right| = \frac{\sqrt{1 - g_S} \cdot (1 - |S_{11}|^2)}{1 - (1 - g_S) \cdot |S_{11}|^2} \quad |\Gamma_S - C_S| = R_S$$

$$C_S = \frac{g_S \cdot S_{11}^*}{1 - (1 - g_S) \cdot |S_{11}|^2} \quad R_S = \frac{\sqrt{1 - g_S} \cdot (1 - |S_{11}|^2)}{1 - (1 - g_S) \cdot |S_{11}|^2}$$


- Equation of a circle in the complex plane where Γ_S is plotted
- **Interpretation:** Any reflection coefficient Γ_S which plotted in the complex plane lies **on** the circle drawn for $g_{\text{circle}} = G_{\text{circle}}/G_{S_{\text{max}}}$ will lead to a gain $G_S = G_{\text{circle}}$
 - Any reflection coefficient Γ_S plotted **outside** this circle will lead to a gain $G_S < G_{\text{circle}}$
 - Any reflection coefficient Γ_S plotted **inside** this circle will lead to a gain $G_S > G_{\text{circle}}$

Amplifier as two-port

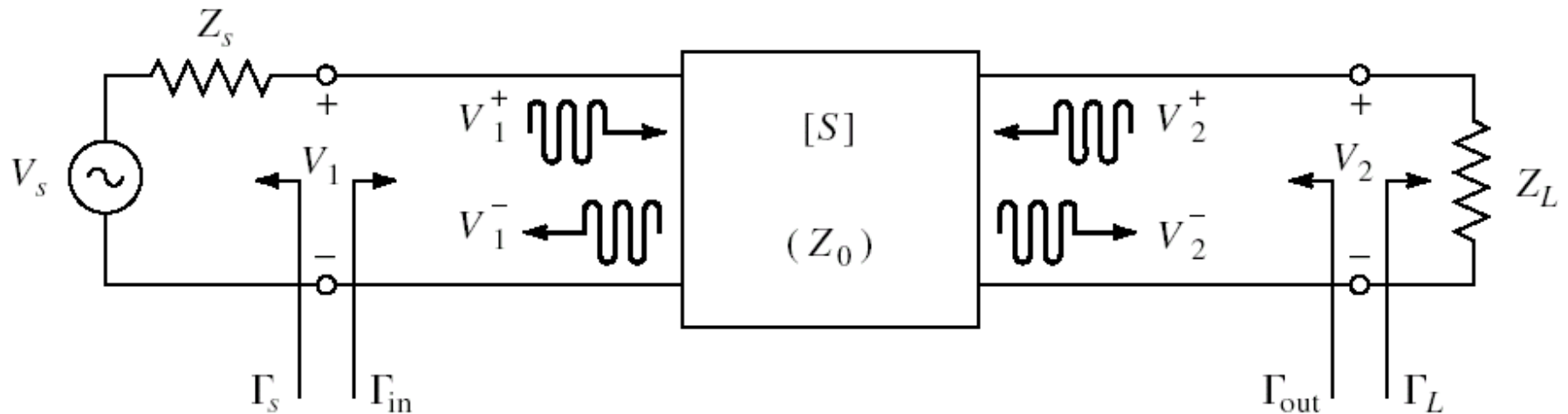

- For an amplifier two-port we are interested in:
 - stability
 - power gain
 - **noise** (sometimes – **small signals**)
 - linearity (sometimes – large signals)

Noise Figure F

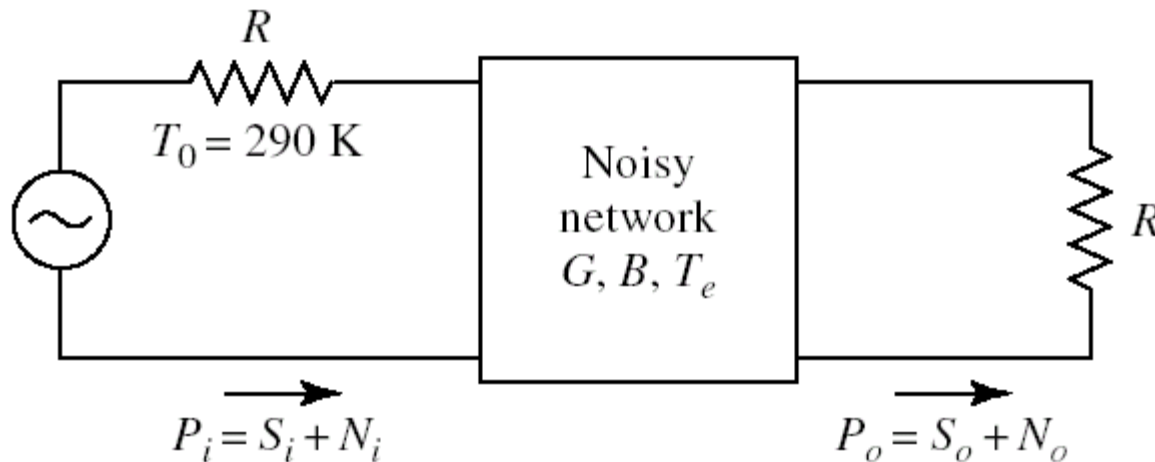


- The noise figure F , is a measure of the reduction in signal-to-noise ratio between the input and output of a device, when (by definition) the input noise power is assumed to be the noise power resulting from a matched resistor at $T_0 = 290\text{ K}$ (reference noise conditions)

$$F = \frac{S_i/N_i}{S_o/N_o} \Big|_{T_0=290K}$$


$$V_{n(e\text{f})} = \sqrt{4kTBR}$$

$$P_n = kTB$$

Noise figure of a cascaded system

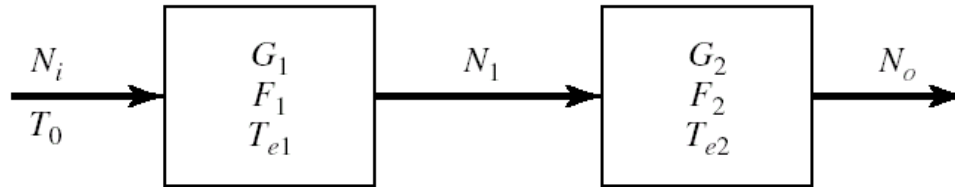

(a)

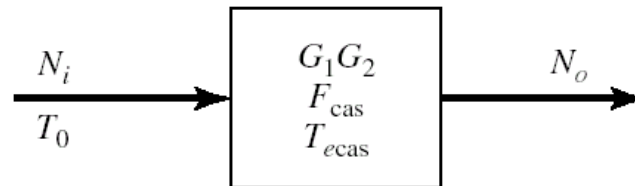


(b)

$$G_{cas} = G_1 \cdot G_2 \qquad F_{cas} = F_1 + \frac{1}{G_1} (F_2 - 1)$$


- Friis Formula (!linear scale)

$$F_{cas} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 \cdot G_2} + \frac{F_4 - 1}{G_1 \cdot G_2 \cdot G_3} + \dots$$


$F[\text{dB}](\Gamma_S)$

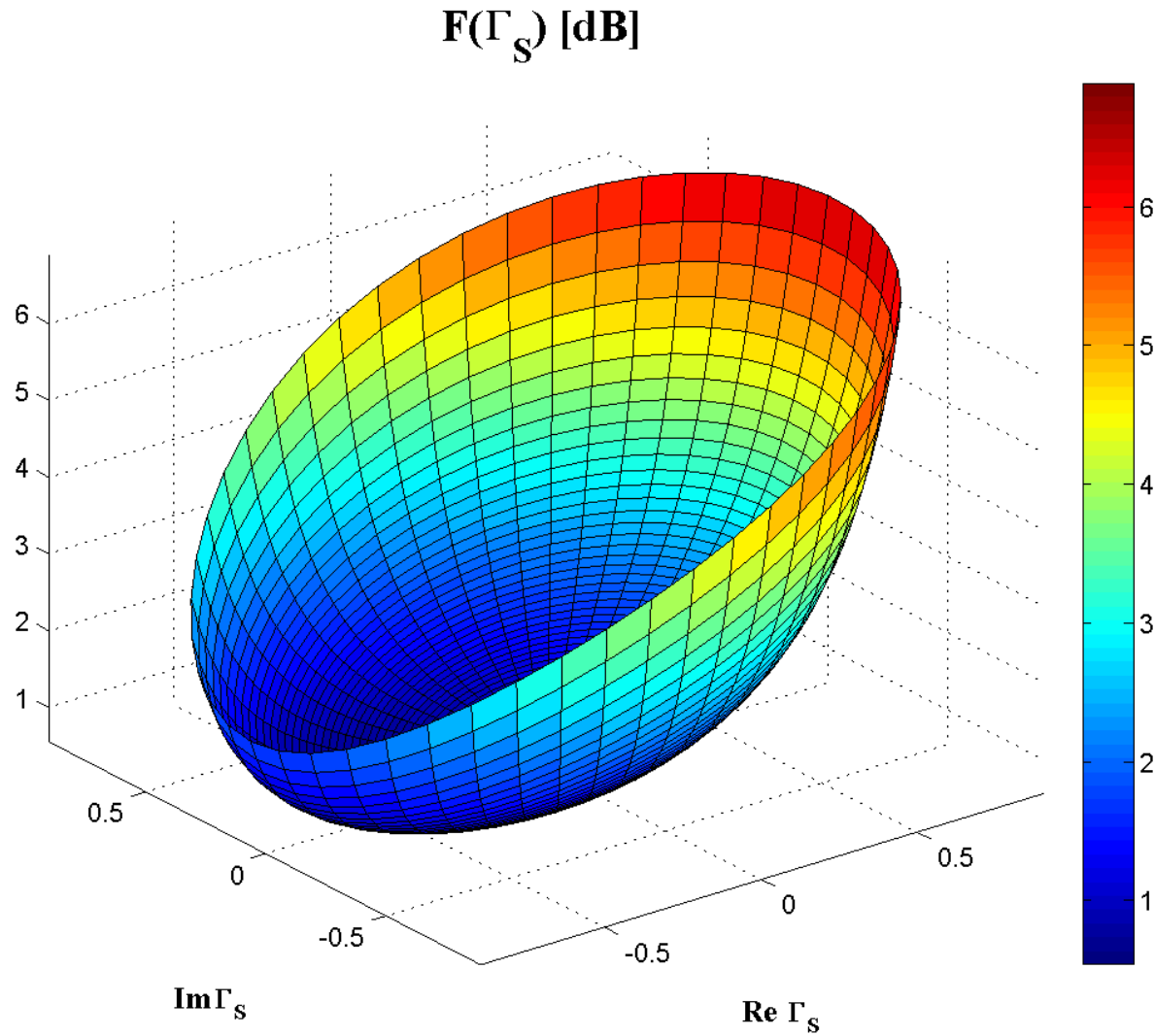

Contour map/lines

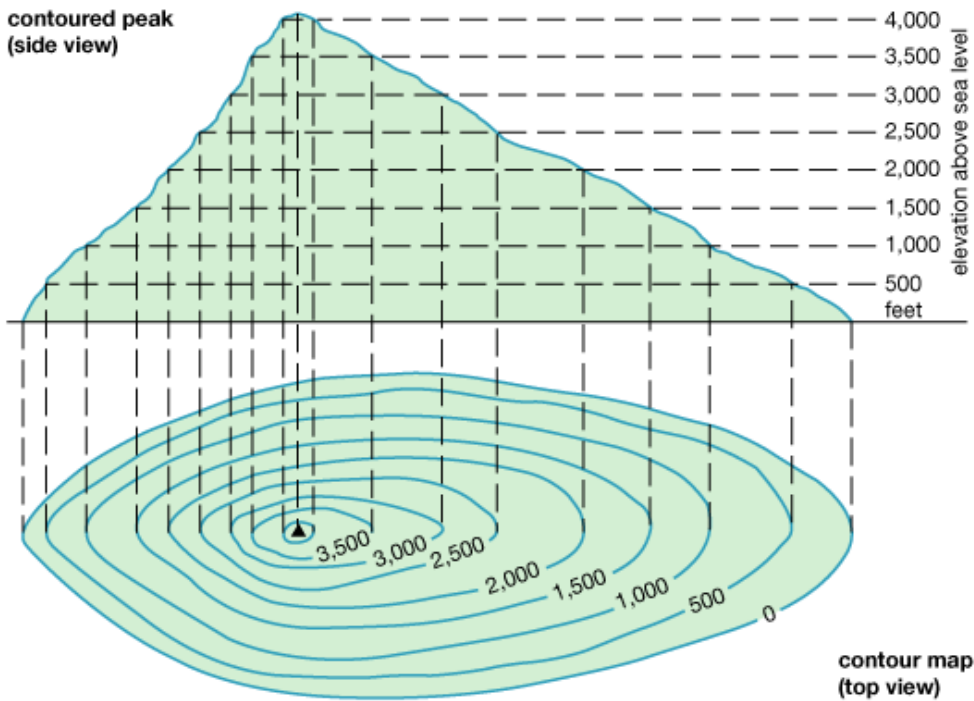

© 2011 Encyclopædia Britannica, Inc.

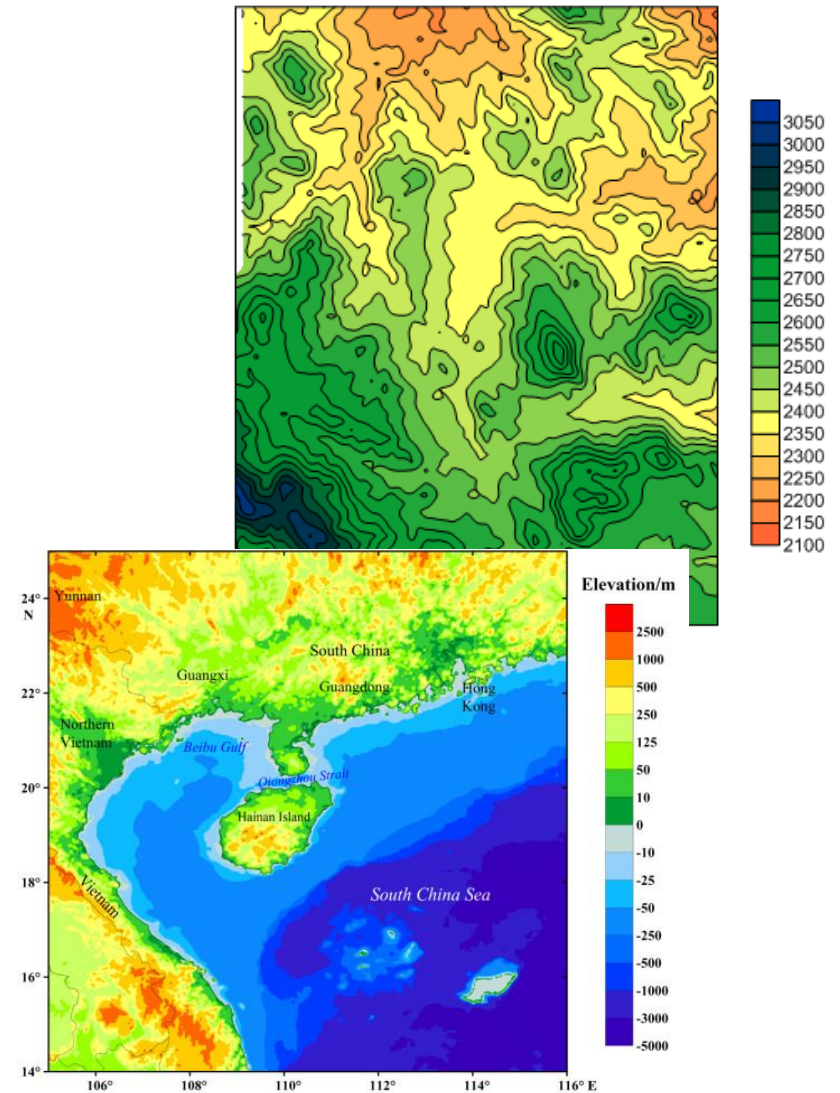

Circles of constant noise figure


$$N = \frac{F - F_{\min}}{4 \cdot r_n} \cdot |1 + \Gamma_{opt}|^2 \quad \left| \Gamma_S - \frac{\Gamma_{opt}}{N+1} \right| = \frac{\sqrt{N \cdot (N+1 - |\Gamma_{opt}|^2)}}{N+1}$$

$$|\Gamma_S - C_F| = R_F \quad C_F = \frac{\Gamma_{opt}}{N+1} \quad R_F = \frac{\sqrt{N \cdot (N+1 - |\Gamma_{opt}|^2)}}{N+1}$$

- The locus in the complex plane Γ_S of the points with constant noise figure is a circle
- **Interpretation:** Any reflection coefficient Γ_S which plotted in the complex plane lies **on** the circle drawn for F_{circle} will lead to a noise factor $F = F_{\text{circle}}$
 - Any reflection coefficient Γ_S plotted **outside** this circle will lead to a noise factor $F > F_{\text{circle}}$
 - Any reflection coefficient Γ_S plotted **inside** this circle will lead to a noise factor $F < F_{\text{circle}}$

LNA – Low Noise Amplifier

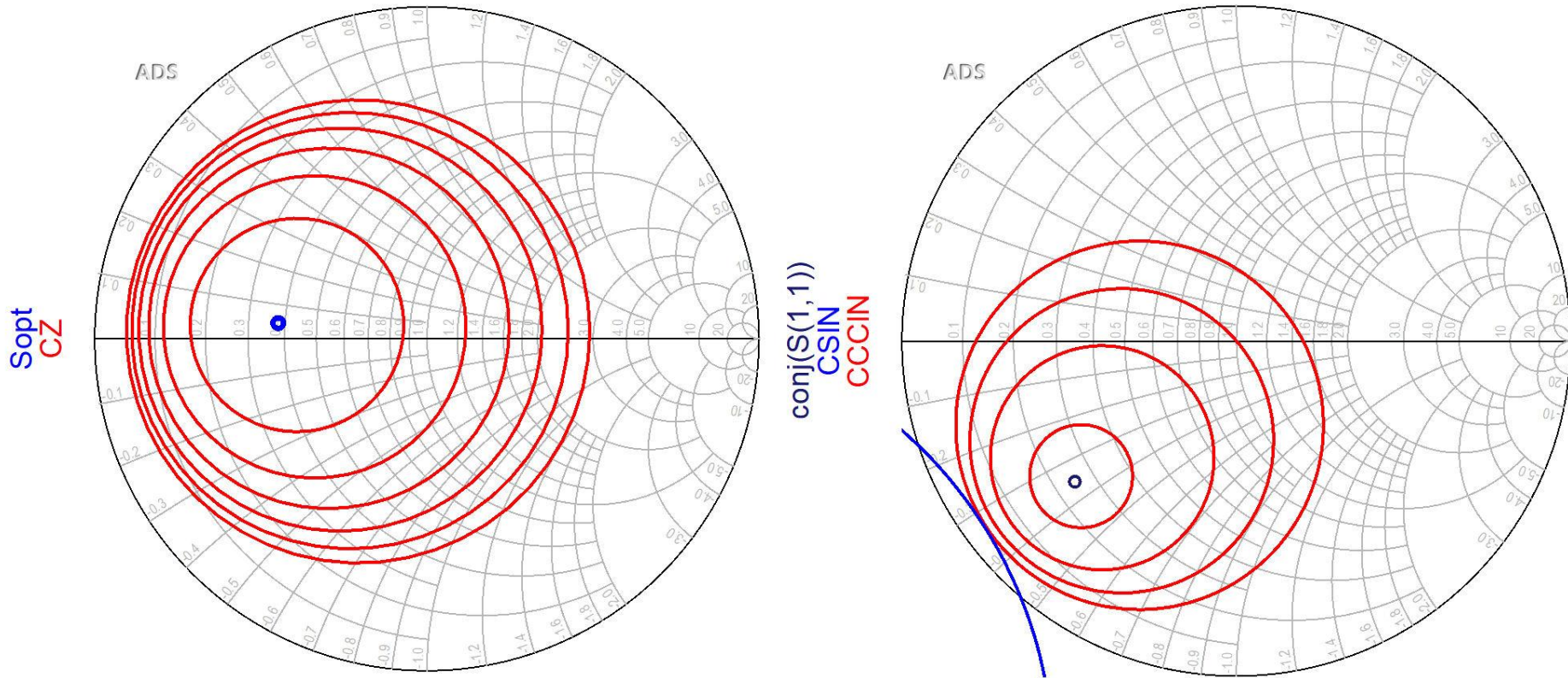
- Usually a transistor suitable for implementing an LNA at a certain frequency will have input gain circles and noise circles in the same area for Γ_S



Matching – 2

- We plot on the complex plane (Smith Chart) the stability/gain/noise circles (depending on the particular application)
- We choose a point with a suitable position relative to these circles (also application dependent)
- We determine the input reflection coefficient corresponding to this point, Γ_S
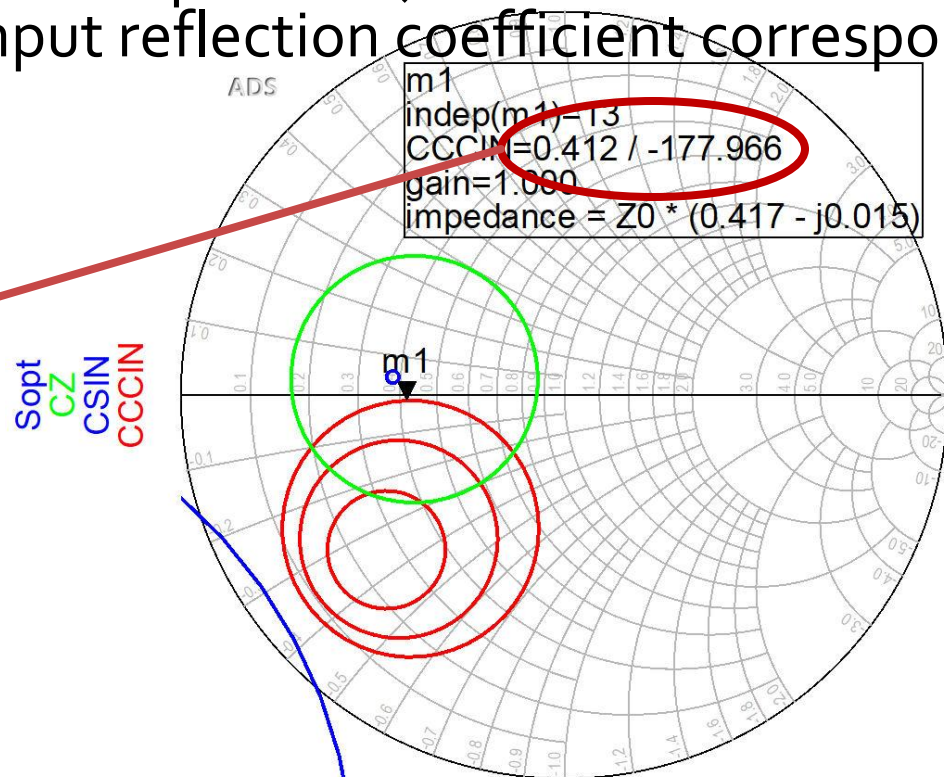
$$\Gamma_S = 0.412 \angle -177.966^\circ$$




Continue

Microwave Filters

Assignment

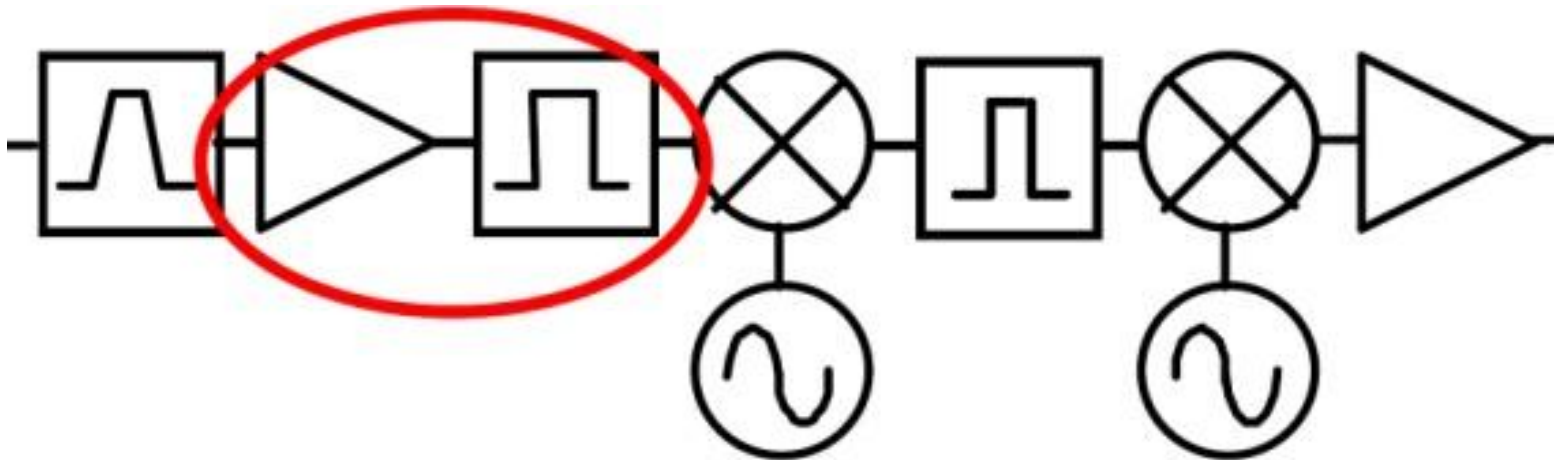- this structure is frequently encountered in radiocommunication systems



$$P_n = kTB$$

Microwave Filters

- Two ways of implementing filters in microwave frequency range
 - microwave specific structures (coupled lines, dielectric resonators, periodic structures)
 - **filter synthesis** with lumped elements followed by implementation with transmission lines
- the first strategy leads to more efficient filters but:
 - has lower generality
 - design is often difficult (lack of analytical relationships)

Filter synthesis

- Filter is designed with lumped elements (L/C) followed by implementation with distributed elements (transmission lines)
 - general
 - analytical relationships easy to implement on the computer
 - efficient
- The preferred procedure is **insertion loss method**

Insertion loss method

- In the insertion loss method, we are passing an intermediate stage (low pass prototype) in order to obtain any type of filter, with controlled specifications

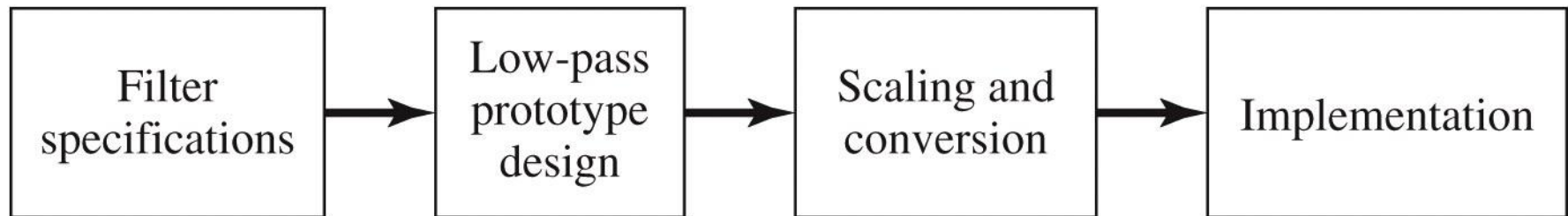


Figure 8.23

© John Wiley & Sons, Inc. All rights reserved.

Insertion loss method

- We control the power loss ratio/attenuation introduced by the filter:
 - in the passband (pass all frequencies)
 - in the stopband (reject all frequencies)

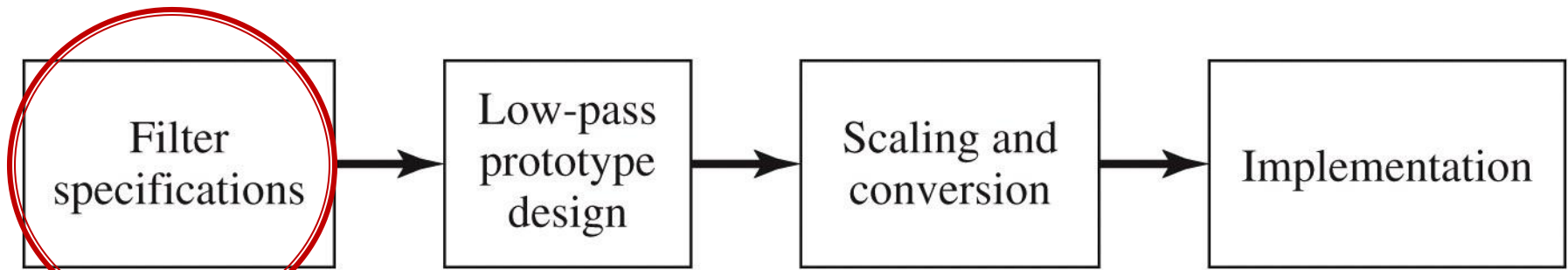


Figure 8.23

Insertion loss method

$$P_{LR} = \frac{P_S}{P_L} = \frac{1}{1 - |\Gamma(\omega)|^2}$$

- $|\Gamma(\omega)|^2$ is an even function of ω


$$|\Gamma(\omega)|^2 = \frac{M(\omega^2)}{M(\omega^2) + N(\omega^2)}$$

$$P_{LR} = 1 + \frac{M(\omega^2)}{N(\omega^2)}$$

- Choosing M and N polynomials appropriately leads to a filter with a completely specified frequency response

Filter specifications

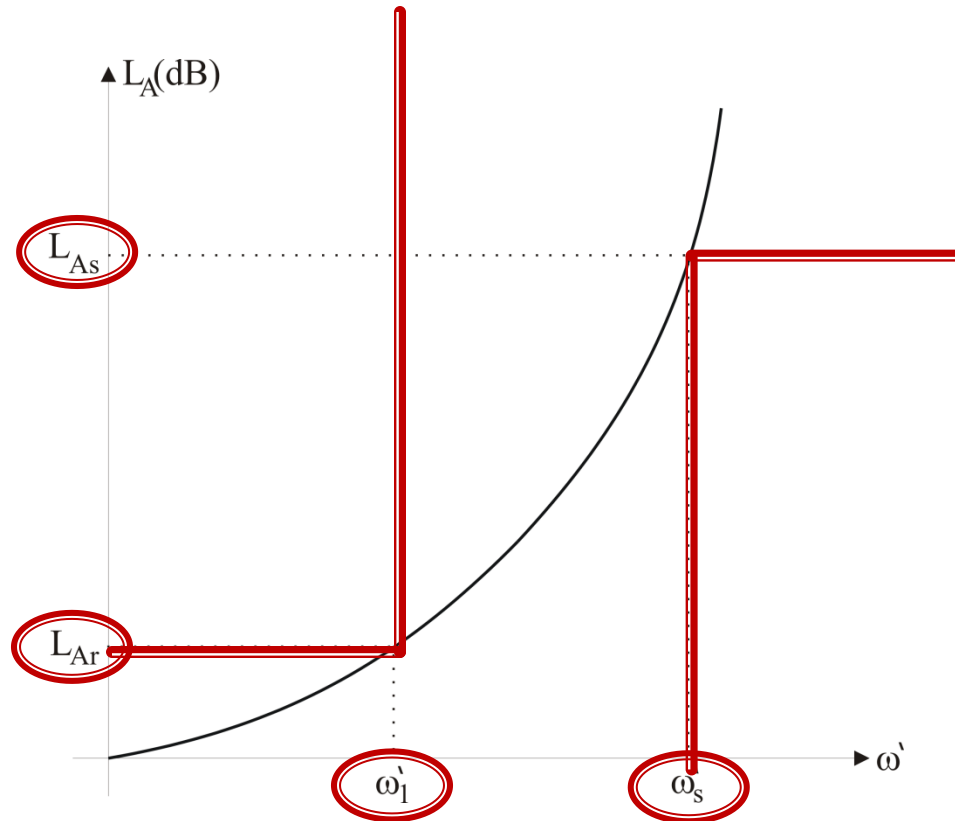- Attenuation
 - in passband
 - in stopband
 - most often in **dB**
- Frequency range
 - passband
 - stopband
 - cutoff frequency ω_1'
usually normalized
(= **1**)



Insertion loss method

- We choose the right polynomials to design an **low-pass** filter (prototype)
- The low-pass prototype are then converted to the desired other types of filters
 - low-pass, high-pass, bandpass, or bandstop

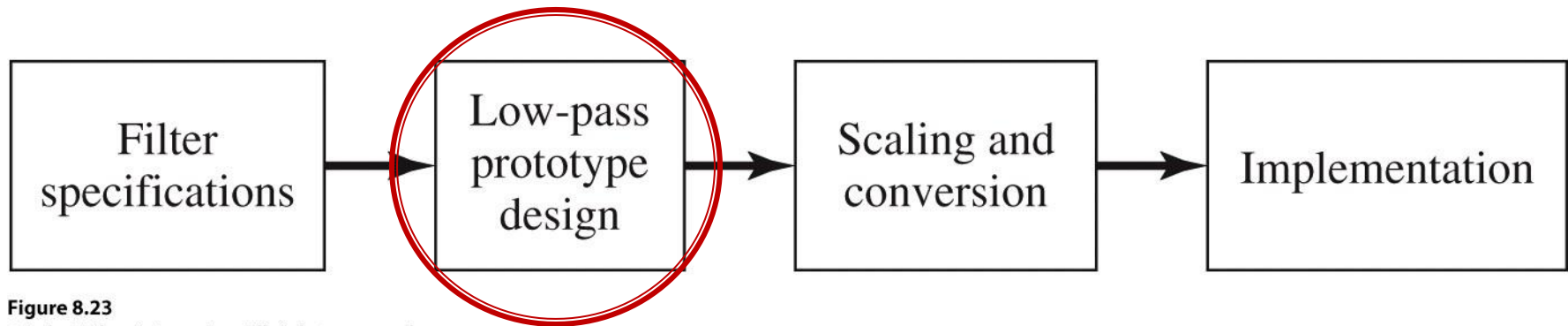


Figure 8.23

Practical low-pass prototypes responses

- **Maximally flat filters** (Butterworth, binomial): provide the flattest possible passband response
- **Equal ripple filters** (Chebyshev): provide a sharper cutoff but the passband response will have ripples
- **Elliptic function filters**, they have equal-ripple responses in the passband as well as in the stopband,
- **Linear phase filters**, offer linear phase response in the passband to avoid signal distortion (important in some applications)

Maximally Flat/Equal ripple LPF Prototype

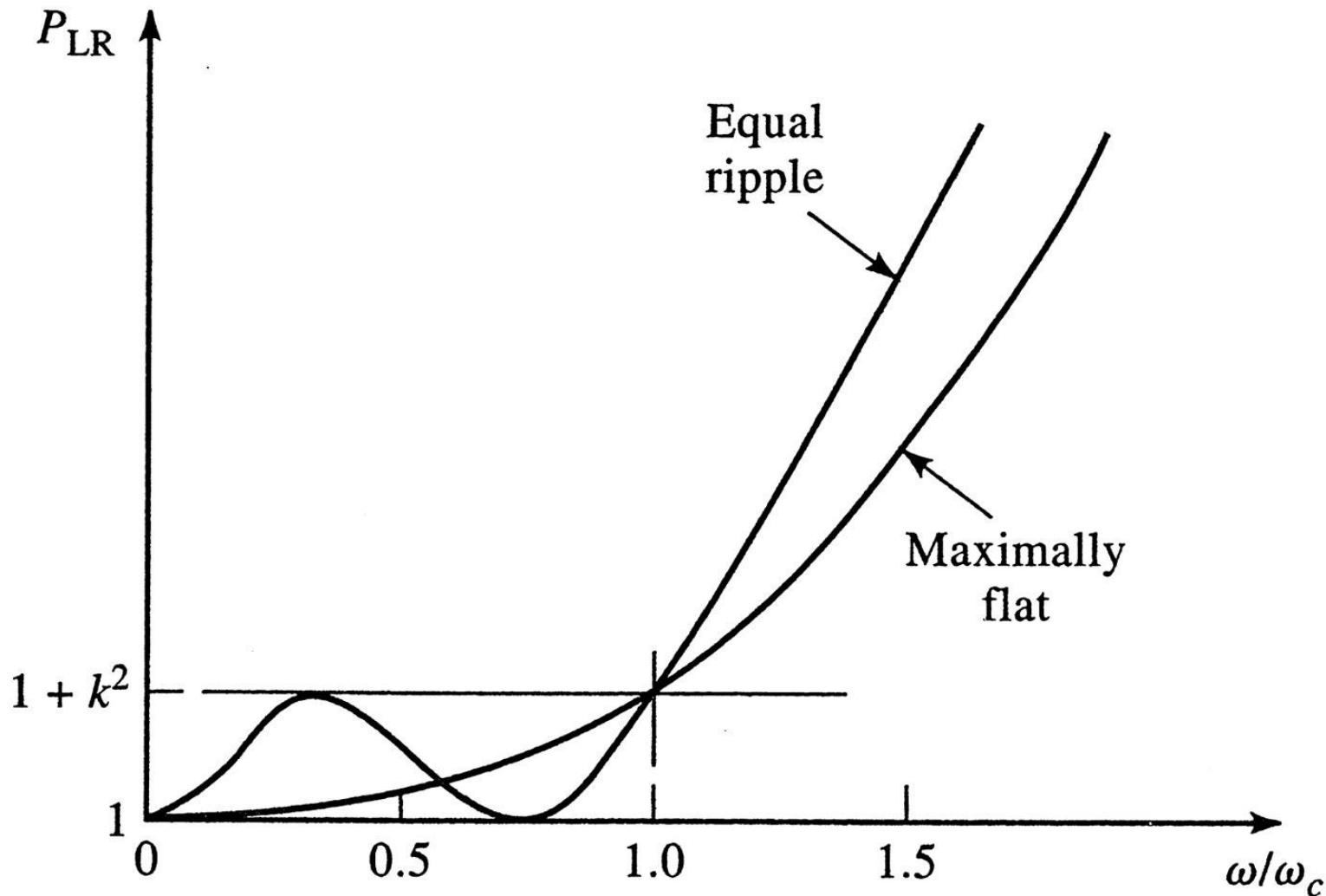


Figure 8.21
© John Wiley & Sons, Inc. All rights reserved.

Elliptic function LPF Prototype

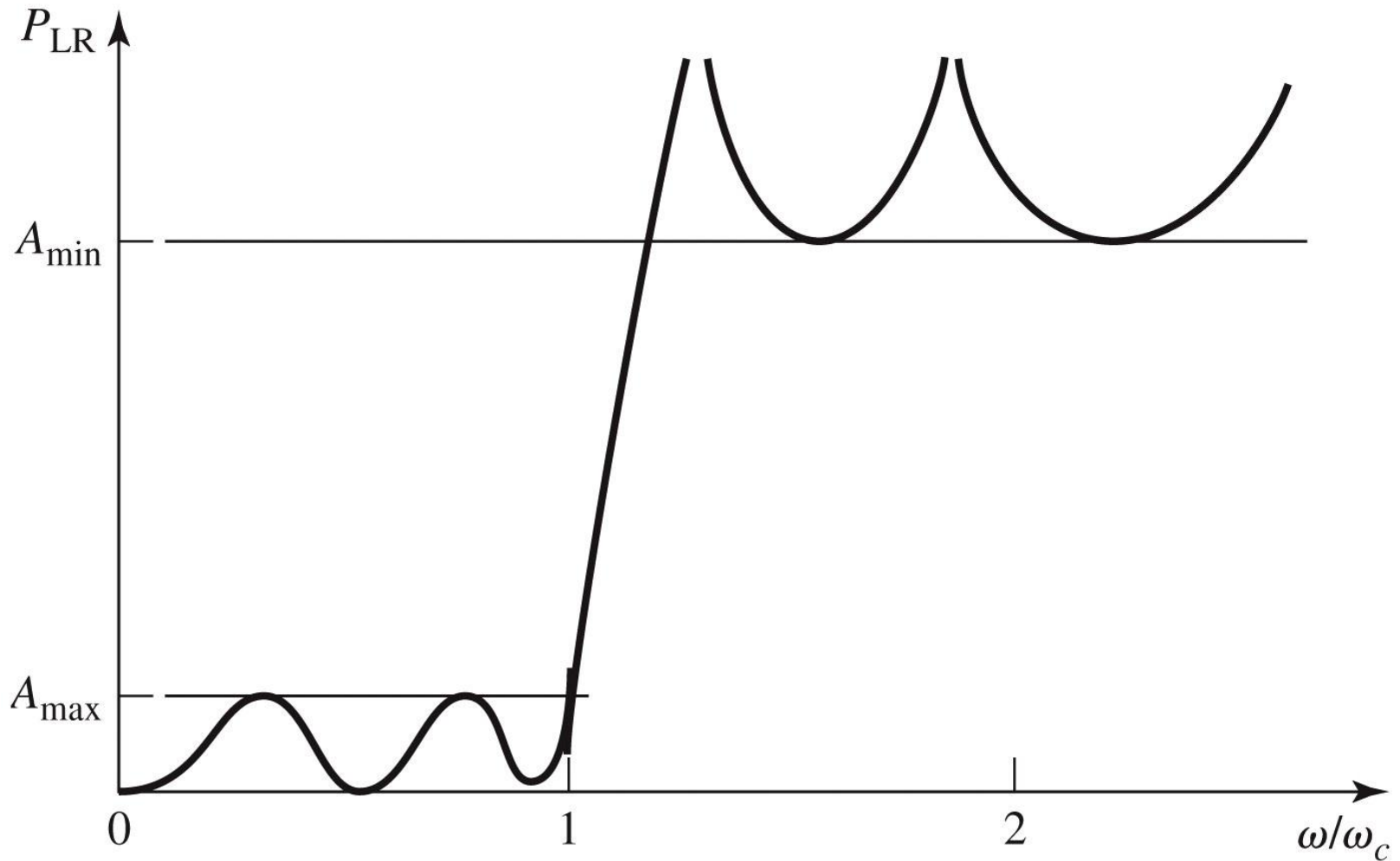


Figure 8.22
© John Wiley & Sons, Inc. All rights reserved.

Maximally Flat LPF Prototype

- Polynomial

$$P_{LR} = 1 + k^2 \cdot \left(\frac{\omega}{\omega_c} \right)^{2N}$$

- For $\omega \gg \omega_c$

$$P_{LR} \approx k^2 \cdot (\omega/\omega_c)^{2N}$$

- attenuation increases at a rate of $20 \cdot N$ dB/decade
- k gives the attenuation at cutoff frequency (3dB cutoff imposes $k = 1$)

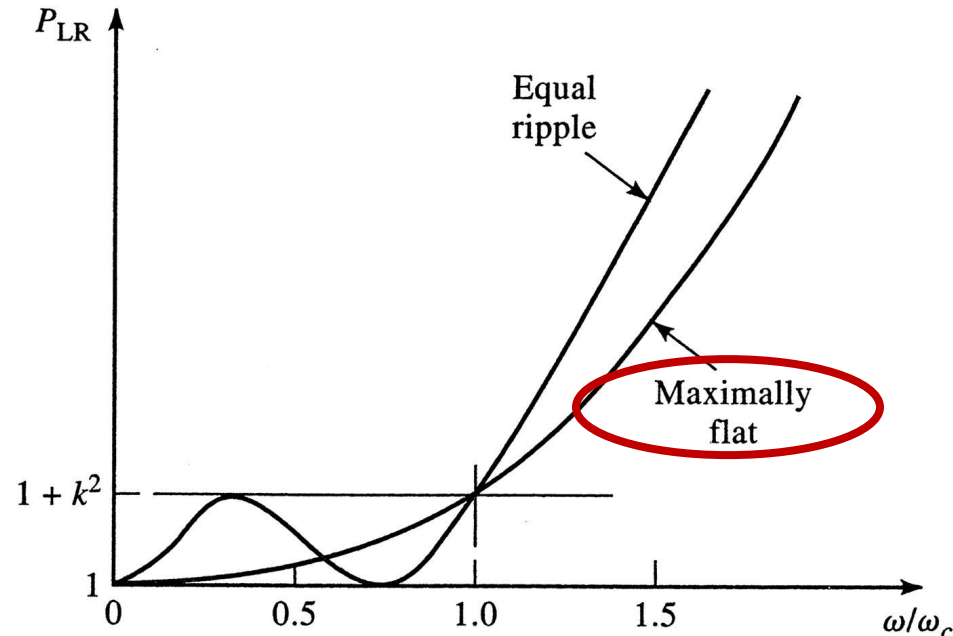


Figure 8.21
© John Wiley & Sons, Inc. All rights reserved.

Equal Ripple LPF Prototype

- Polynomial

$$P_{LR} = 1 + k^2 \cdot T_N^2\left(\frac{\omega}{\omega_c}\right)$$

- For $\omega \gg \omega_c$

$$P_{LR} \approx \frac{k^2}{4} \cdot \left(\frac{2 \cdot \omega}{\omega_c}\right)^{2N}$$

- attenuation increases

at a rate of $20 \cdot N$ dB/decade (**also**)

- attenuation is $(2^{2N})/4$ greater than the binomial response at any given frequency where $\omega \gg \omega_c$

- the passband ripples: $1 + k^2$, k gives the ripple


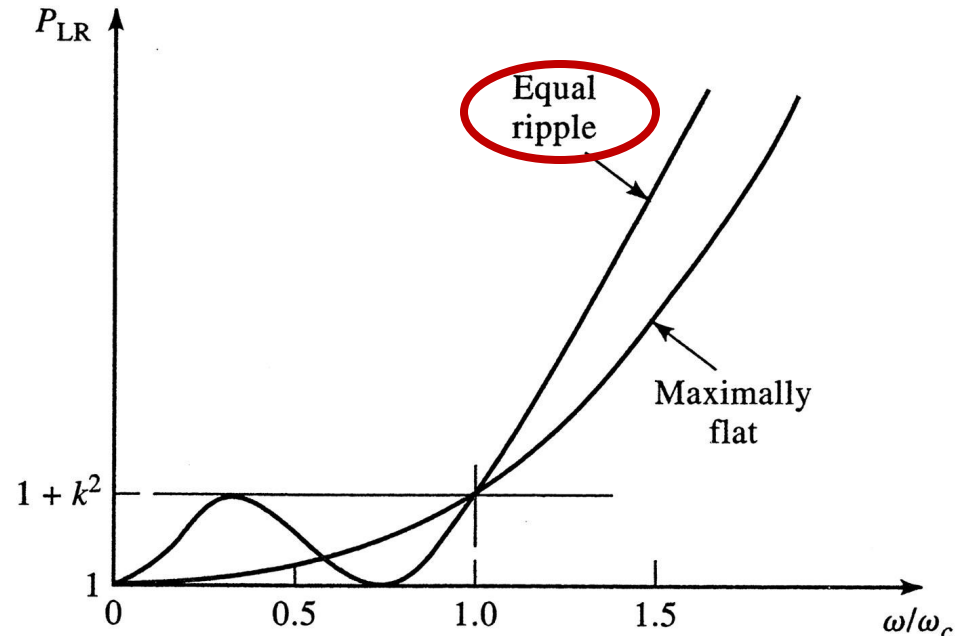


Figure 8.21
© John Wiley & Sons, Inc. All rights reserved.

Order (N) of the Maximally Flat filter

$$n \geq \frac{\log \left(\frac{10^{\frac{L_{As}}{10}} - 1}{10^{\frac{L_{Ar}}{10}} - 1} \right)}{2 \cdot \log \frac{\omega'_s}{\omega'_1}}$$


- !attenuations in **dB**

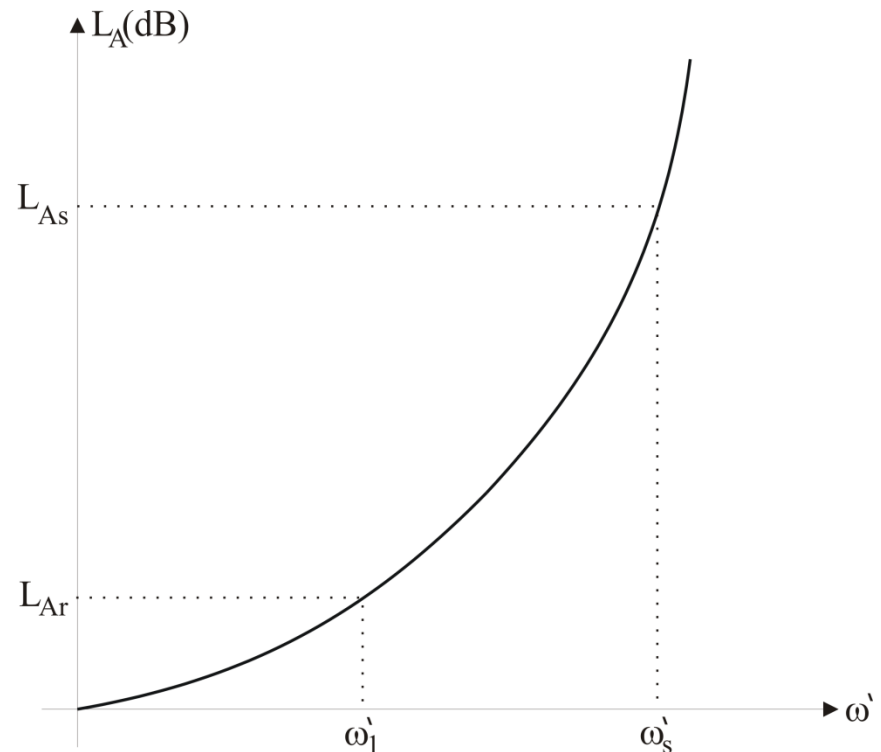


Order (N) of the Equal Ripple filter

$$n \geq \frac{\cosh^{-1} \left(\sqrt{\frac{10^{\frac{L_{As}}{10}} - 1}{10^{\frac{L_{Ar}}{10}} - 1}} \right)}{\cosh^{-1} \left(\frac{\omega'_s}{\omega'_1} \right)}$$

- !attenuations in **dB**

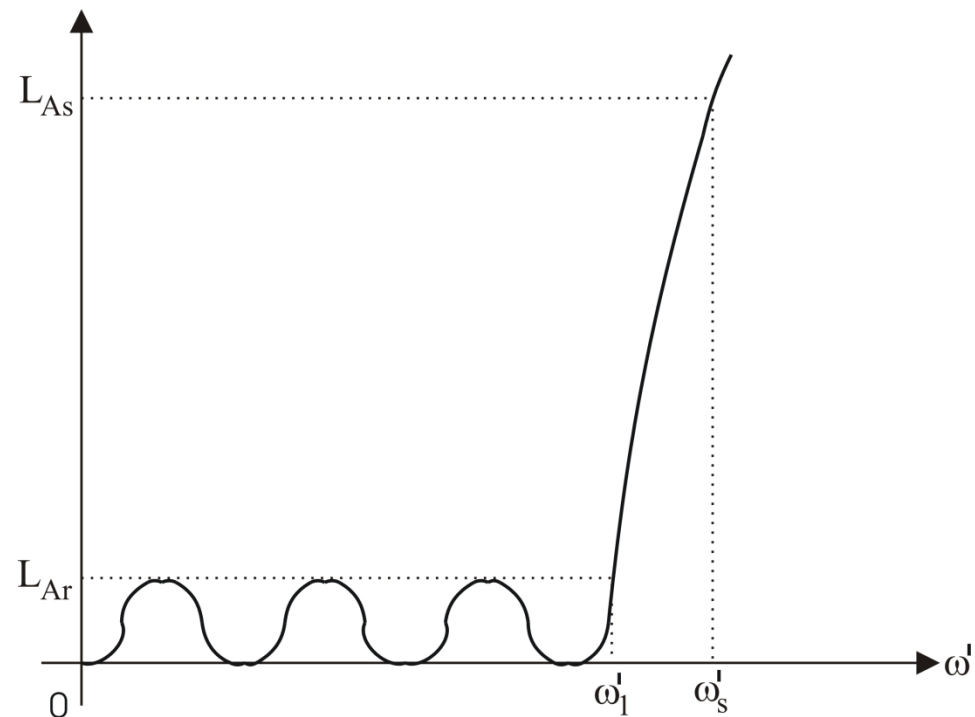


Maximally flat filter prototypes

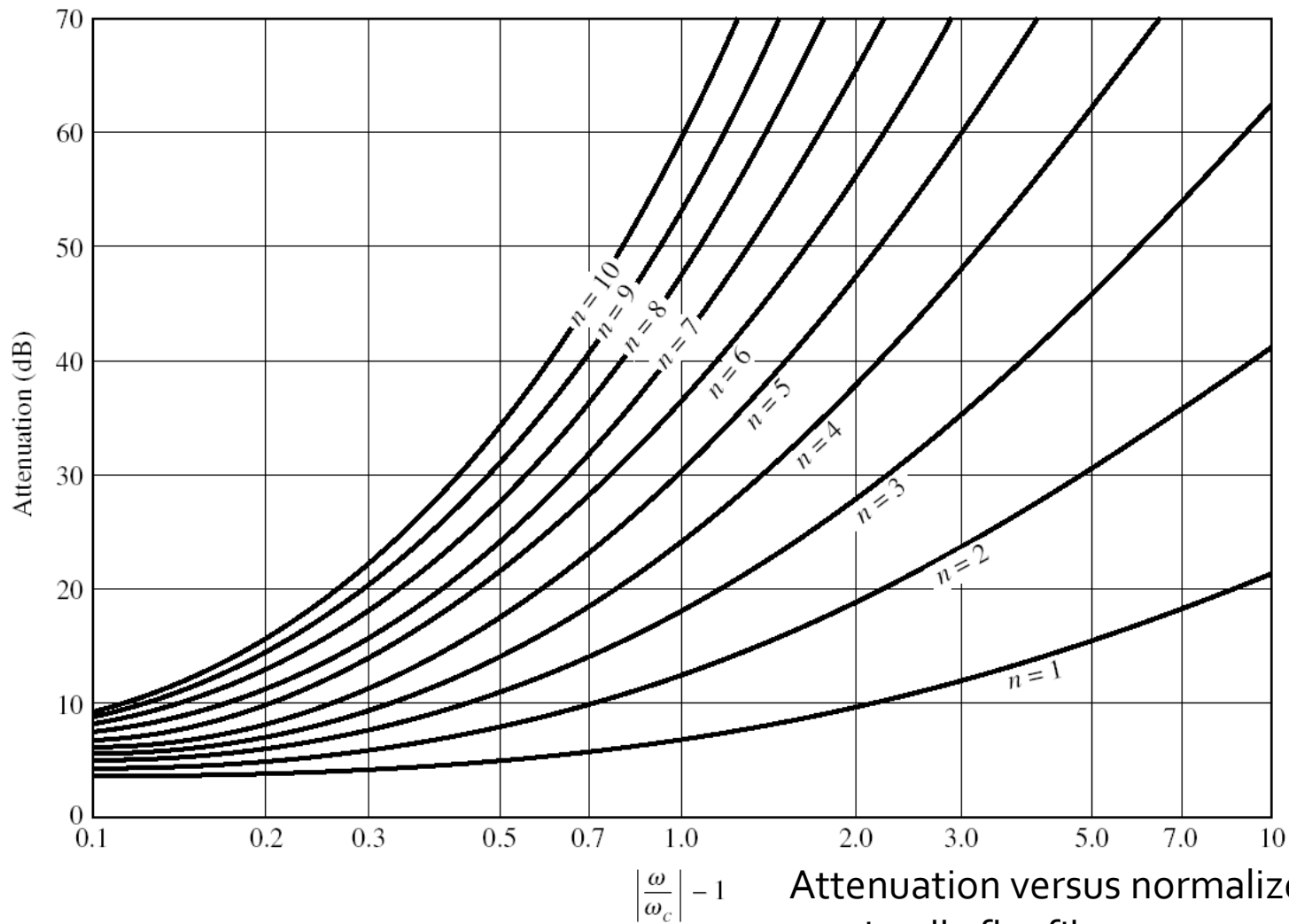

Attenuation versus normalized frequency for maximally flat filter prototypes


3 dB Equal-ripple filter prototypes

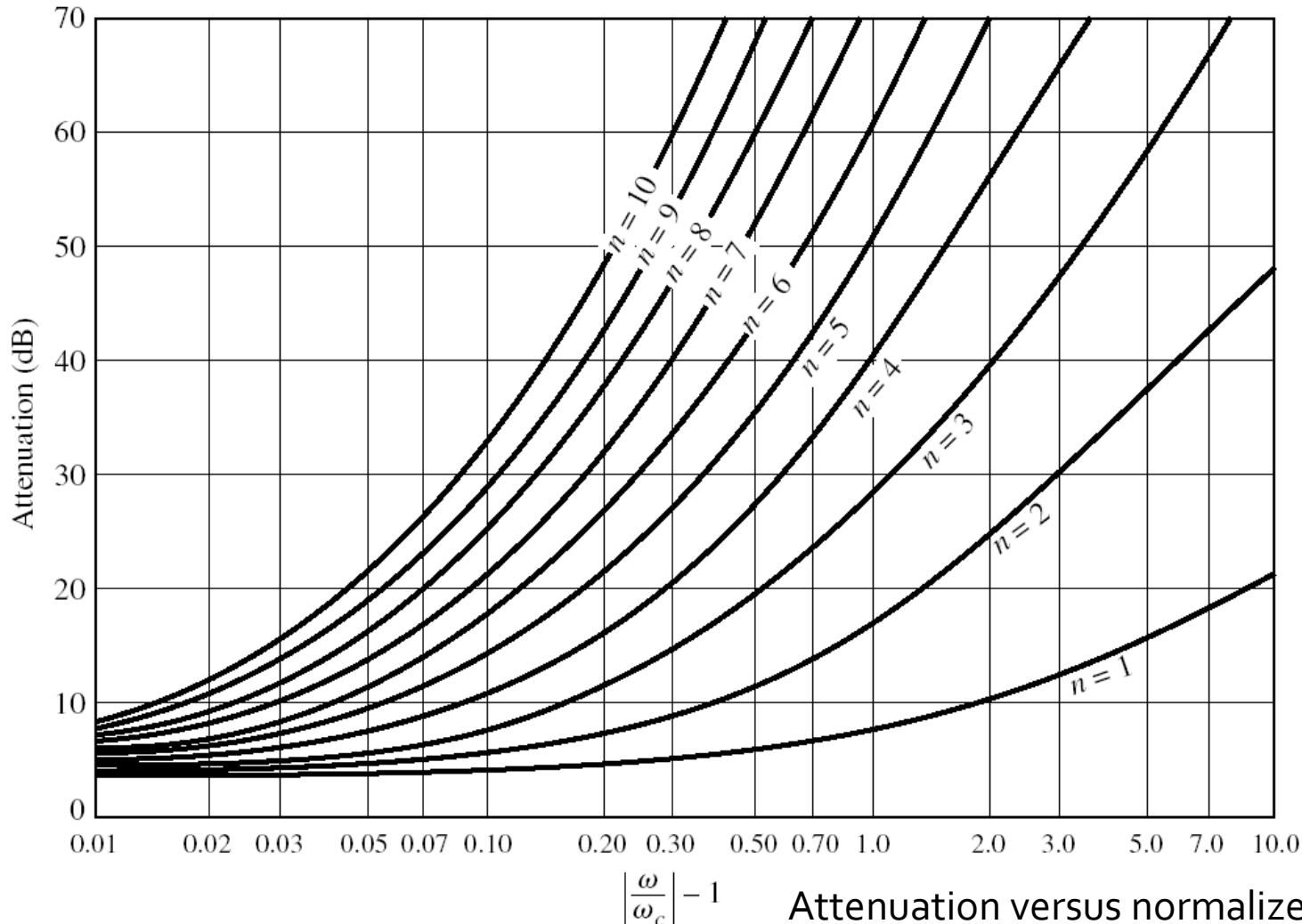

(b)

Attenuation versus normalized frequency for equal-ripple filter prototypes (3dB)


0.5 dB Equal-ripple filter prototypes

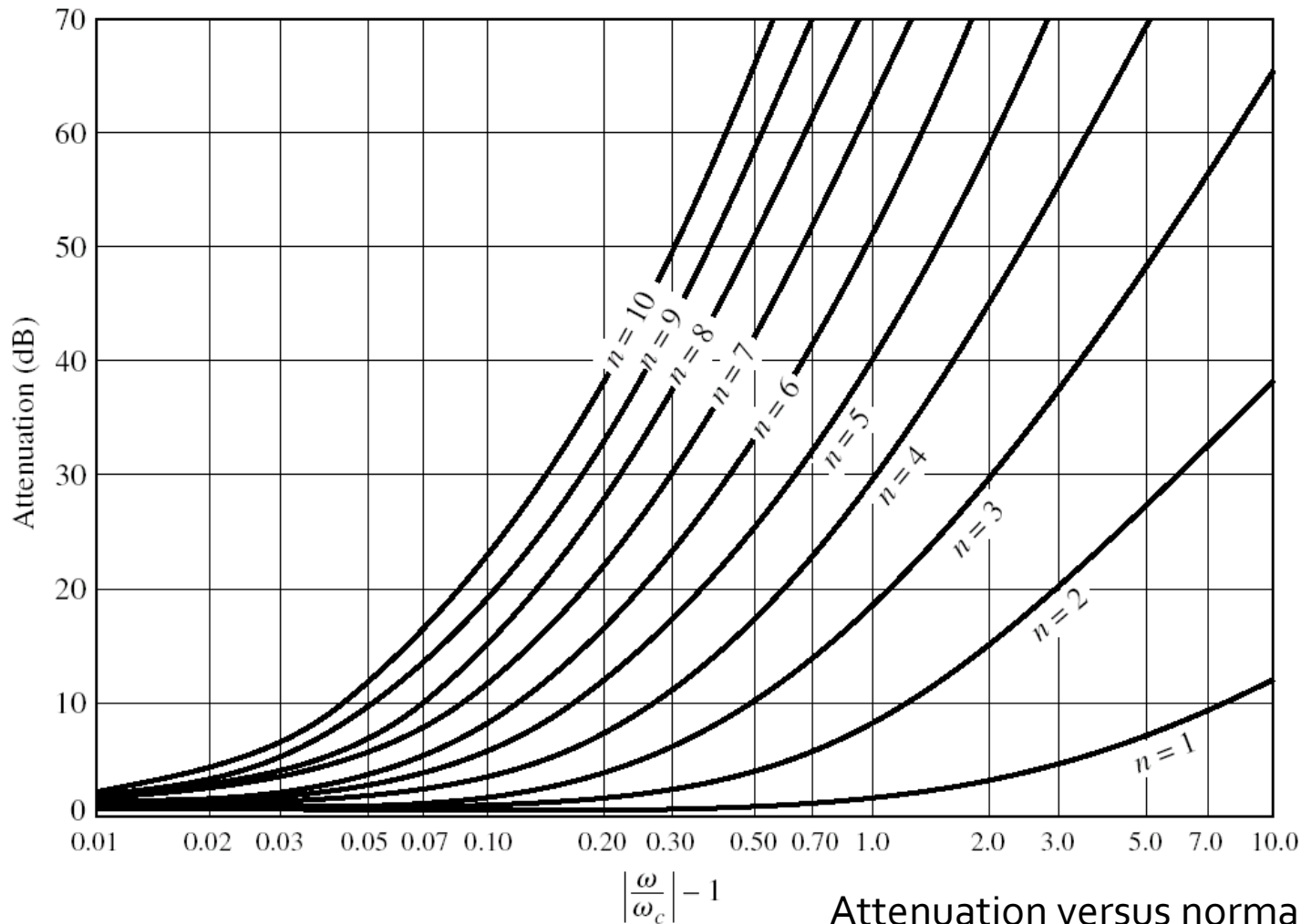


(a)

Attenuation versus normalized frequency for equal-ripple filter prototypes (0.5dB)

Prototype Filters

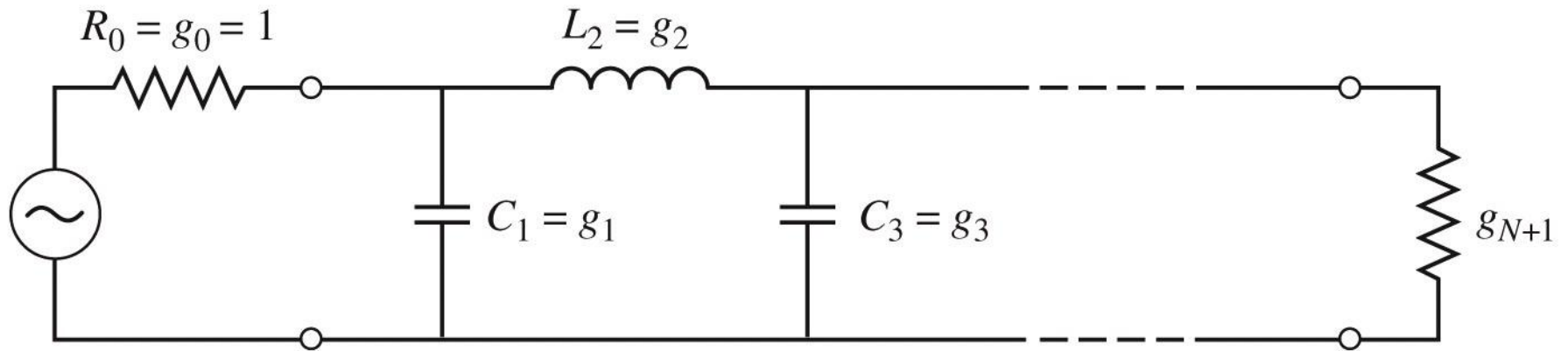

(a)

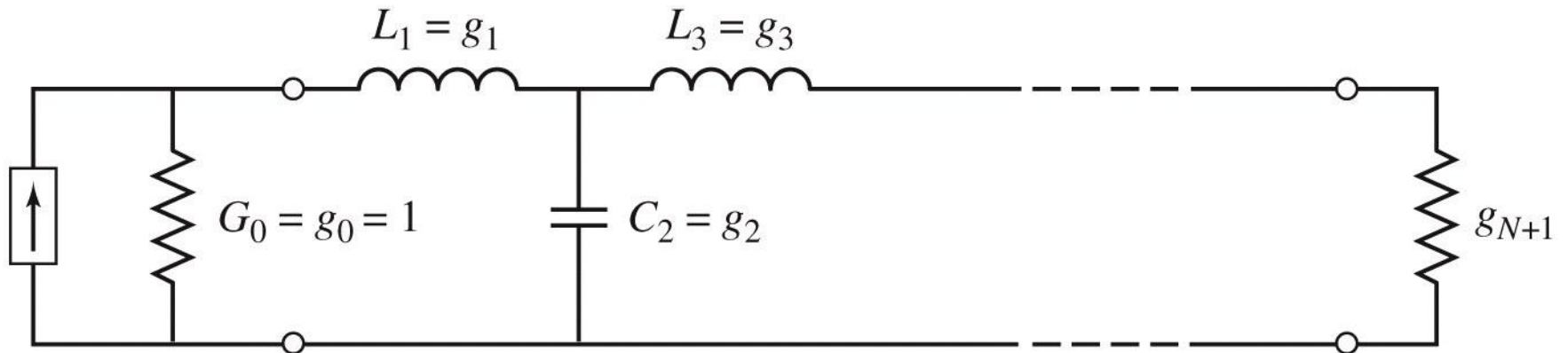

(b)

Prototype Filters

- Prototype filters are:
 - Low-Pass Filters (**LPF**)
 - cutoff frequency **$\omega_o = 1 \text{ rad/s}$** ($f_o = 0.159 \text{ Hz}$)
 - connected to a source with **$R = 1\Omega$**
- The number of reactive elements (L/C) is the order of the filter (N)
- Reactive elements are alternated: series L / shunt C
- There two prototypes with the same response, a prototype beginning with a shunt C element, and a prototype beginning with a series L element

Prototype Filters

- We define filter parameters g_i , $i=0, N+1$
- g_i are the element values in the prototype filter

$$g_0 = \begin{cases} \text{generator resistance } R'_0 & \text{if } g_1 = C'_1 \\ \text{generator conductance } G'_0 & \text{if } g_1 = L'_1 \end{cases}$$

$$g_k \Big|_{k=1, \overline{N}} = \begin{cases} \text{inductance for series inductors} \\ \text{capacitance for shunt capacitors} \end{cases}$$

$$g_{N+1} = \begin{cases} \text{load resistance } R'_{N+1} & \text{if } g_N = C'_N \\ \text{load conductance } G'_{N+1} & \text{if } g_N = L'_N \end{cases}$$

Maximally Flat LPF Prototype

- Formulas for filter parameters

$$g_0 = 1$$

$$g_k = 2 \cdot \sin \left[\frac{(2 \cdot k - 1) \cdot \pi}{2 \cdot N} \right], \quad k = 1, N$$

$$g_{N+1} = 1$$

Maximally Flat LPF Prototype

TABLE 8.3 Element Values for Maximally Flat Low-Pass Filter Prototypes ($g_0 = 1$, $\omega_c = 1$, $N = 1$ to 10)

N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

Equal-ripple LPF Prototype

- Formulas for filter parameters (iterative)

$$a_k = \sin\left[\frac{(2 \cdot k - 1) \cdot \pi}{2 \cdot N}\right], \quad k = 1, N \qquad \beta = \ln\left(\coth \frac{L_{Ar}}{17.37}\right)$$

$$\gamma = \sinh\left(\frac{\beta}{2 \cdot N}\right) \qquad b_k = \gamma^2 + \sin^2\left(\frac{k \cdot \pi}{N}\right), \quad k = 1, N$$

$$g_1 = \frac{2 \cdot a_1}{\gamma}$$

$$g_k = \frac{4 \cdot a_{k-1} \cdot a_k}{b_{k-1} \cdot g_{k-1}}, \quad k = 2, N$$

$$g_{N+1} = \begin{cases} 1 & \text{for odd } N \\ \coth^2\left(\frac{\beta}{4}\right) & \text{for even } N \end{cases}$$

TABLE 8.4 Element Values for Equal-Ripple Low-Pass Filter Prototypes ($g_0 = 1, \omega_c = 1, N = 1$ to 10, 0.5 dB and 3.0 dB ripple)

0.5 dB Ripple											
N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	0.6986	1.0000									
2	1.4029	0.7071	1.9841								
3	1.5963	1.0967	1.5963	1.0000							
4	1.6703	1.1926	2.3661	0.8419	1.9841						
5	1.7058	1.2296	2.5408	1.2296	1.7058	1.0000					
6	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841				
7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.0000			
8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841		
9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6678	1.2690	1.7504	1.0000	
10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841

3.0 dB Ripple											
N	g_1	g_2	g_3	g_4	g_5	g_6	g_7	g_8	g_9	g_{10}	g_{11}
1	1.9953	1.0000									
2	3.1013	0.5339	5.8095								
3	3.3487	0.7117	3.3487	1.0000							
4	3.4389	0.7483	4.3471	0.5920	5.8095						
5	3.4817	0.7618	4.5381	0.7618	3.4817	1.0000					
6	3.5045	0.7685	4.6061	0.7929	4.4641	0.6033	5.8095				
7	3.5182	0.7723	4.6386	0.8039	4.6386	0.7723	3.5182	1.0000			
8	3.5277	0.7745	4.6575	0.8089	4.6990	0.8018	4.4990	0.6073	5.8095		
9	3.5340	0.7760	4.6692	0.8118	4.7272	0.8118	4.6692	0.7760	3.5340	1.0000	
10	3.5384	0.7771	4.6768	0.8136	4.7425	0.8164	4.7260	0.8051	4.5142	0.6091	5.8095

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures*, Artech House, Dedham, Mass., 1980, with permission.

- For even N order of the filter (N = 2, 4, 6, 8 ...) equal-ripple filters **must** closed by a load impedance

$g_{N+1} \neq 1$

- If the application doesn't allow this, supplemental impedance matching is required (quarter-wave transformer, binomial ...) to $g_L = 1$

Example

- Design a **3rd order** ~~bandpass~~ filter with **0.5 dB ripples** in passband. ~~The center frequency of the filter should be 1 GHz. The fractional bandwidth of the passband should be 10%, and the impedance 50Ω.~~

LPF Prototype


- 0.5dB equal-ripple table or design formulas:

- $g_1 = 1.5963 = L_1/C_3,$

- $g_2 = 1.0967 = C_2/L_4,$



- $g_3 = 1.5963 = L_3/C_5,$

- $g_4 = 1.000 = R_L$

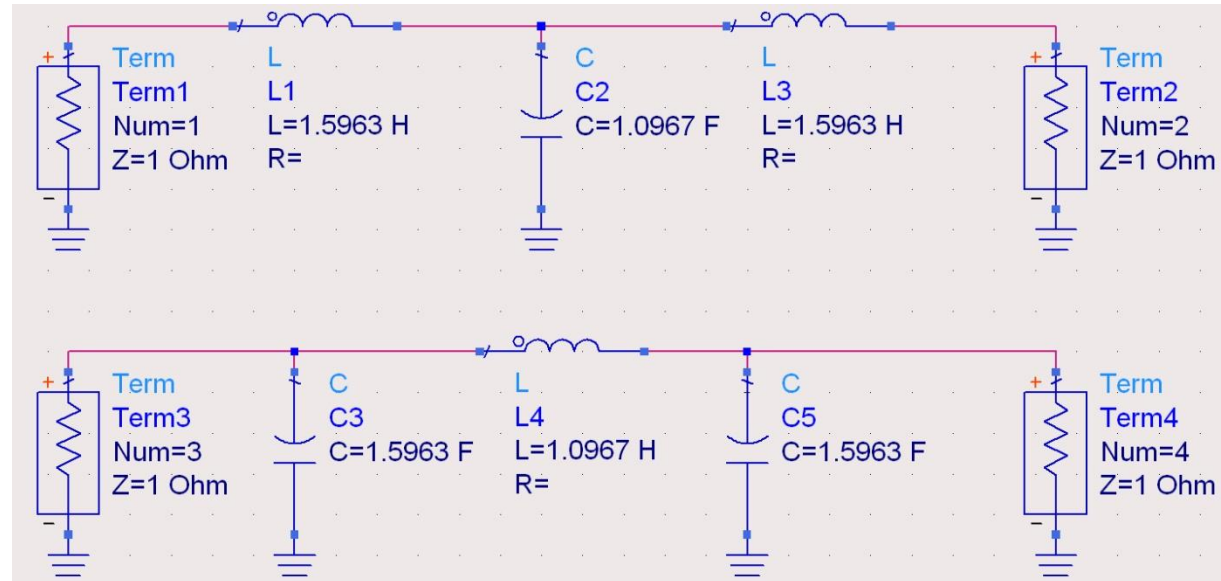

LPF Prototype

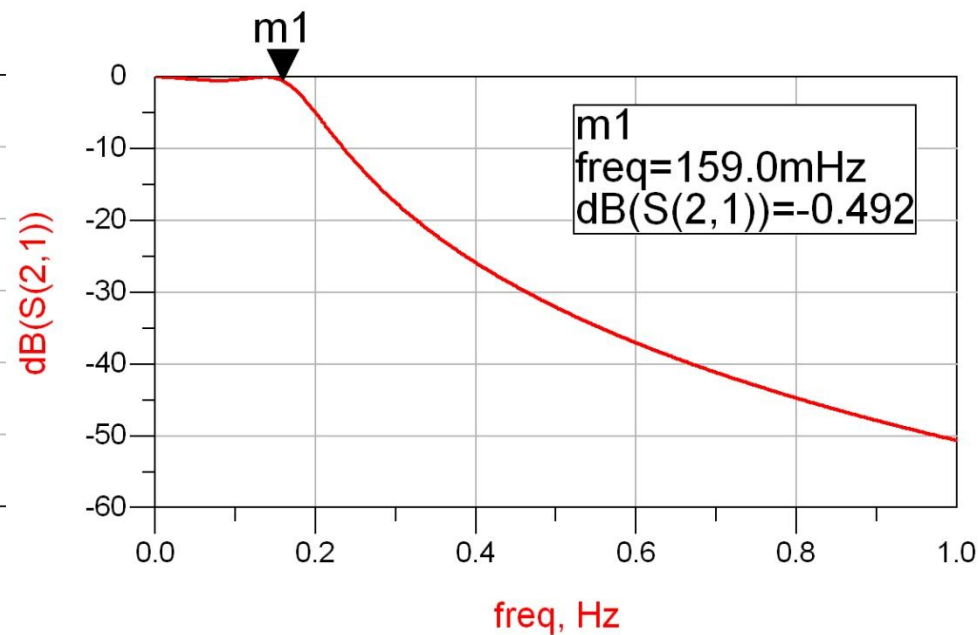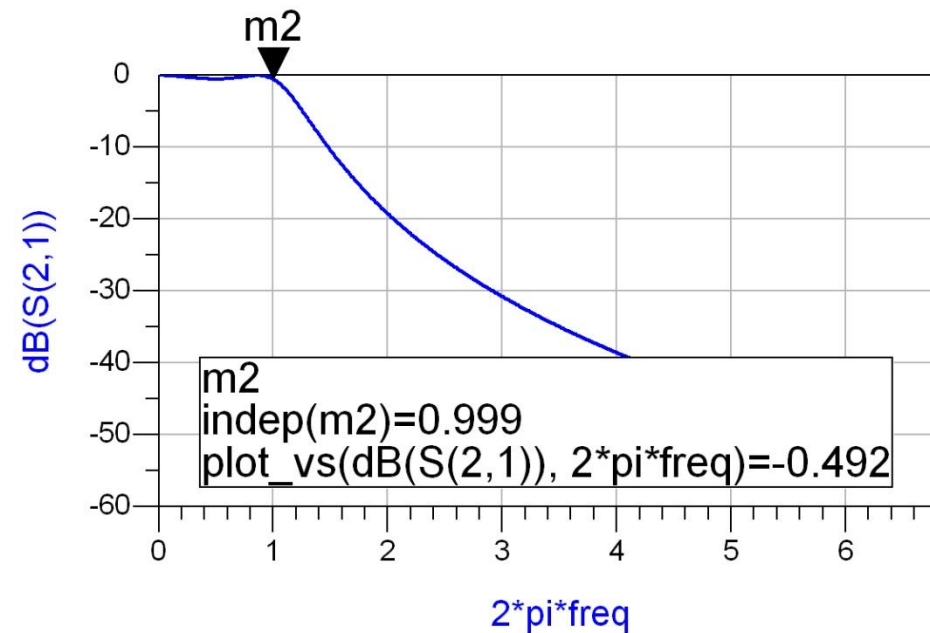- $\omega_o = 1 \text{ rad/s}$ ($f_o = \omega_o / 2\pi = 0.159 \text{ Hz}$)



Impedance and Frequency Scaling

- After computing prototype filter's elements:
 - Low-Pass Filters (**LPF**)
 - cutoff frequency **$\omega_o = 1 \text{ rad/s}$** ($f_o = 0.159 \text{ Hz}$)
 - connected to a source with **$R = 1\Omega$**
- component values can be scaled in terms of impedance and frequency

Impedance and Frequency Scaling

- LPF Prototype is only used as an intermediate step
 - Low-Pass Filter (LPF)
 - cutoff frequency $\omega_o = 1 \text{ rad/s}$ ($f_o = 0.159 \text{ Hz}$)
 - connected to a source with $R = 1\Omega$

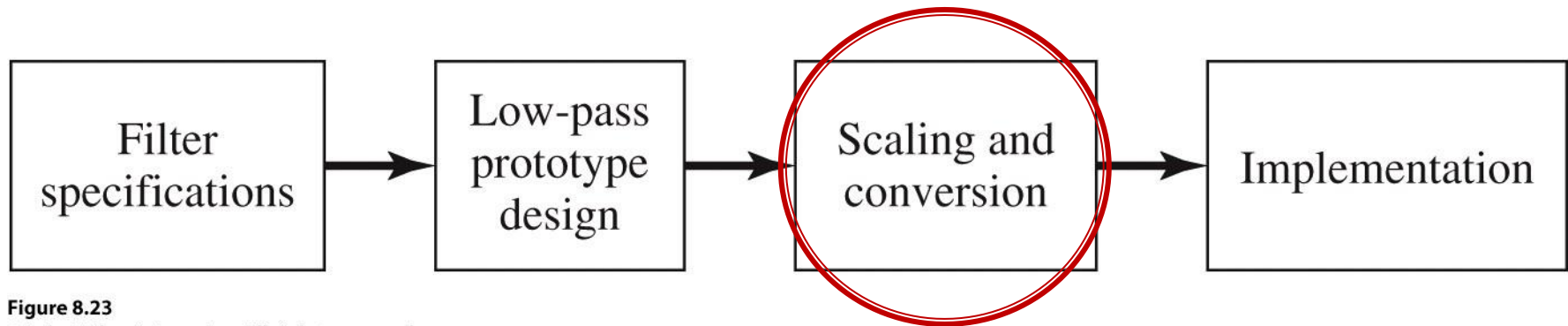


Figure 8.23

Impedance Scaling

- To design a filter which will work with a source resistance of R_0 we multiply all the impedances of the prototype design by R_0 (" $'$ " denotes scaled values)

$$R'_s = R_0 \cdot (R_s = 1)$$


$$R'_L = R_0 \cdot R_L$$

$$L' = R_0 \cdot L$$

$$C' = \frac{C}{R_0}$$


Frequency Scaling

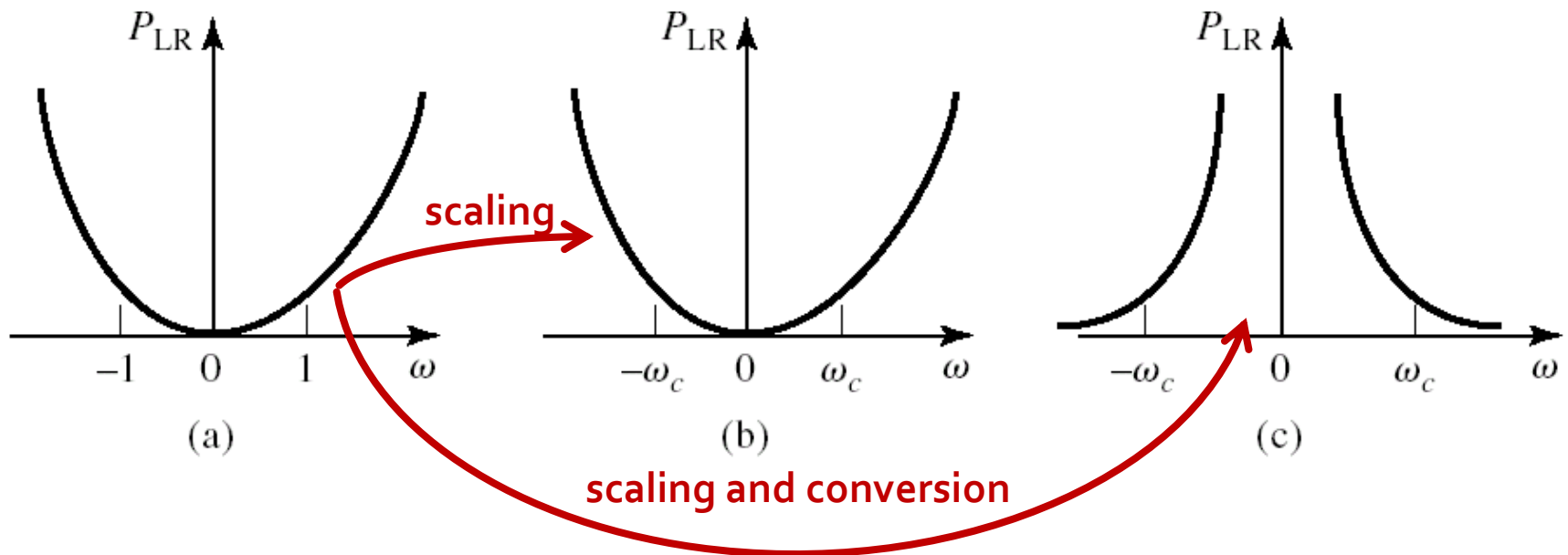- changing the cutoff frequency – (fig. b)
- changing the type (for example LPF \rightarrow HPF – fig. c) requires also conversion



Frequency Scaling

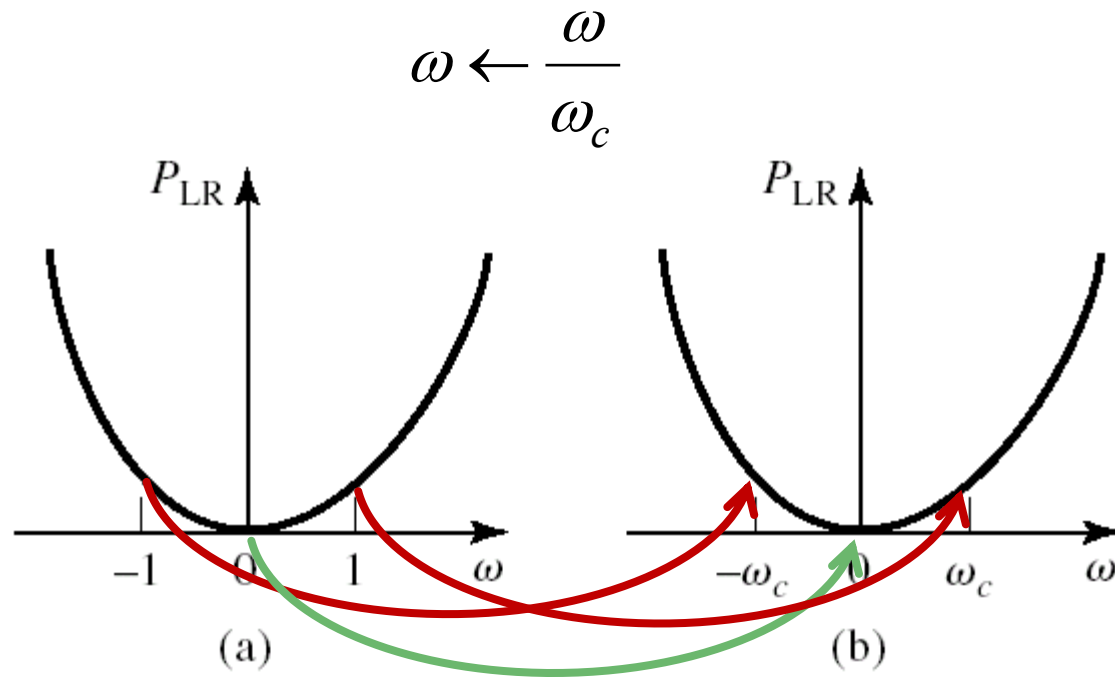- To change the cutoff frequency of a low-pass prototype from unity to ω_c we apply a variable substitution



Frequency Scaling

- To change the cutoff frequency of a low-pass prototype we apply a variable substitution:

$$\omega \leftarrow \frac{\omega}{\omega_c}$$

- Equivalent to the widening of the power loss filter response

$$P'_{LR}(\omega) = P_{LR}\left(\frac{\omega}{\omega_c}\right)$$

$$j \cdot X_k = j \cdot \frac{\omega}{\omega_c} \cdot L_k = j \cdot \omega \cdot L'_k$$

$$j \cdot B_k = j \cdot \frac{\omega}{\omega_c} \cdot C_k = j \cdot \omega \cdot C'_k$$

Frequency Scaling LPF \rightarrow LPF

- New element values for frequency scaling:

$$L'_k = \frac{L_k}{\omega_c} \quad C'_k = \frac{C_k}{\omega_c}$$


- When both impedance and frequency scaling are required:

$$L'_k = \frac{R_0 \cdot L_k}{\omega_c} \quad C'_k = \frac{C_k}{R_0 \cdot \omega_c}$$

Low-pass to high-pass transformation LPF \rightarrow HPF

- Variable substitution for LPF \rightarrow HPF:
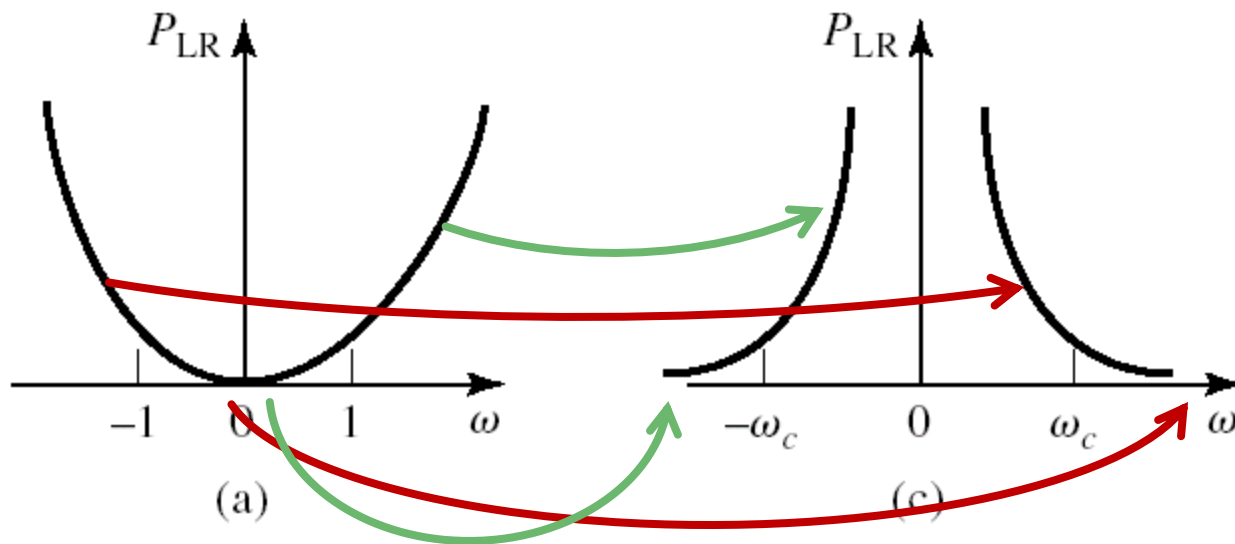
$$\omega \leftarrow -\frac{\omega_c}{\omega}$$



High-pass transformation LPF \rightarrow HPF

- Variable substitution for LPF \rightarrow HPF :

$$\omega \leftarrow -\frac{\omega_c}{\omega}$$
$$j \cdot X_k = -j \cdot \frac{\omega_c}{\omega} \cdot L_k = \frac{1}{j \cdot \omega \cdot C'_k} \quad j \cdot B_k = -j \cdot \frac{\omega_c}{\omega} \cdot C_k = \frac{1}{j \cdot \omega \cdot L'_k}$$

- Impedance scaling can be included

$$C'_k = \frac{1}{R_0 \cdot \omega_c \cdot L_k} \quad L'_k = \frac{R_0}{\omega_c \cdot C_k}$$

- In the schematic series **inductors** must be replaced with series **capacitors**, and shunt **capacitors** must be replaced with shunt **inductors**

Bandpass Transformation LPF \rightarrow BPF

- Variable substitution for LPF \rightarrow BPF:

$$\omega \leftarrow \frac{\omega_0}{\omega_2 - \omega_1} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)$$

- where we use the fractional bandwidth of the passband and the center frequency

$$\Delta = \frac{\omega_2 - \omega_1}{\omega_0} \qquad \omega_0 = \sqrt{\omega_1 \cdot \omega_2}$$


Bandpass Transformation LPF \rightarrow BPF

$$\omega = \omega_0 \rightarrow \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega_0}{\omega_0} - \frac{\omega_0}{\omega_0} \right) = 0$$

$$\omega = -\omega_0 \rightarrow \frac{1}{\Delta} \left(\frac{-\omega_0}{\omega_0} - \frac{\omega_0}{-\omega_0} \right) = 0$$

$$\omega = \omega_1 \rightarrow \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega_1^2 - \omega_0^2}{\omega_0 \cdot \omega_1} \right) = -1$$
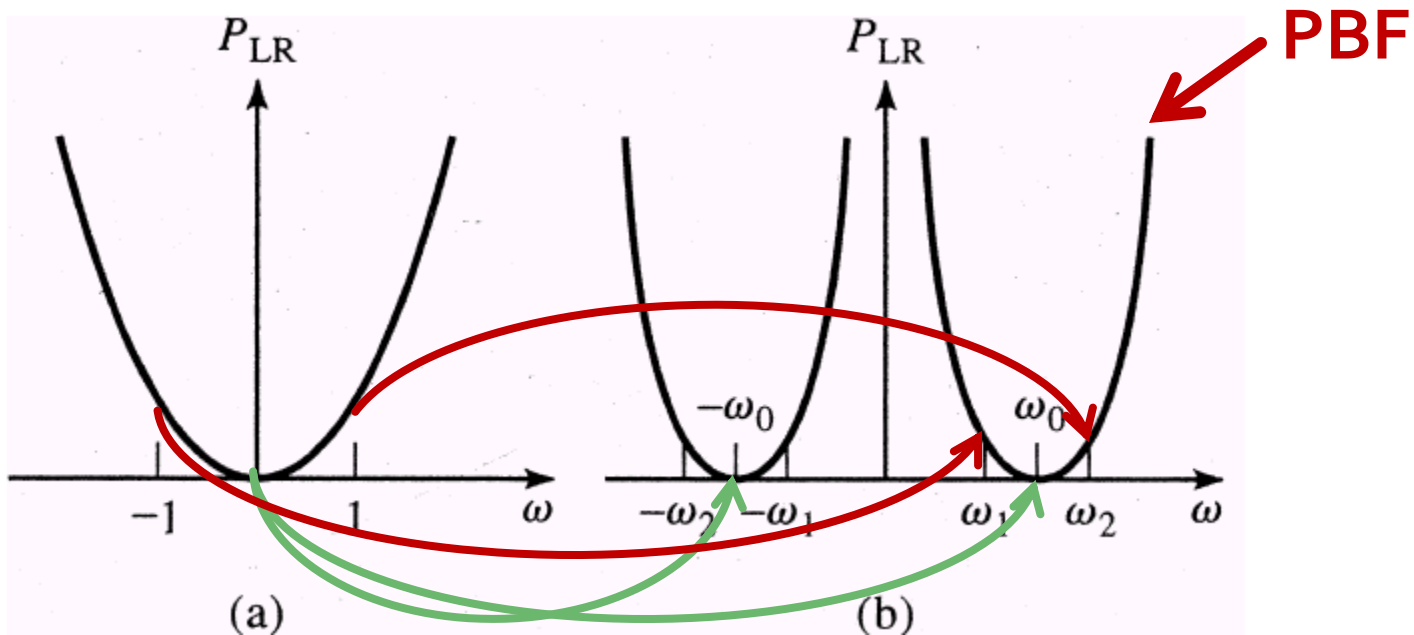
$$\omega = \omega_2 \rightarrow \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega_2^2 - \omega_0^2}{\omega_0 \cdot \omega_2} \right) = 1$$



Bandpass Transformation LPF \rightarrow BPF

$$j \cdot X_k = \frac{j}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \cdot L_k = j \cdot \frac{\omega \cdot L_k}{\Delta \cdot \omega_0} - j \cdot \frac{\omega_0 \cdot L_k}{\Delta \cdot \omega} = j \cdot \omega \cdot L'_k - j \frac{1}{\omega \cdot C'_k}$$
$$j \cdot B_k = \frac{j}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \cdot C_k = j \cdot \frac{\omega \cdot C_k}{\Delta \cdot \omega_0} - j \cdot \frac{\omega_0 \cdot C_k}{\Delta \cdot \omega} = j \cdot \omega \cdot C'_k - j \frac{1}{\omega \cdot L'_k}$$

- A series **inductor** in the prototype filter is transformed to a **series LC circuit in series**



$$L'_k = \frac{L_k}{\Delta \cdot \omega_0} \quad C'_k = \frac{\Delta}{\omega_0 \cdot L_k}$$

- A shunt **capacitor** in the prototype filter is transformed to a **shunt LC circuit in parallel**

$$L'_k = \frac{\Delta}{C_k \cdot \omega_0} \quad C'_k = \frac{C_k}{\omega_0 \cdot \Delta}$$

Bandstop Transformation LPF \rightarrow BSF
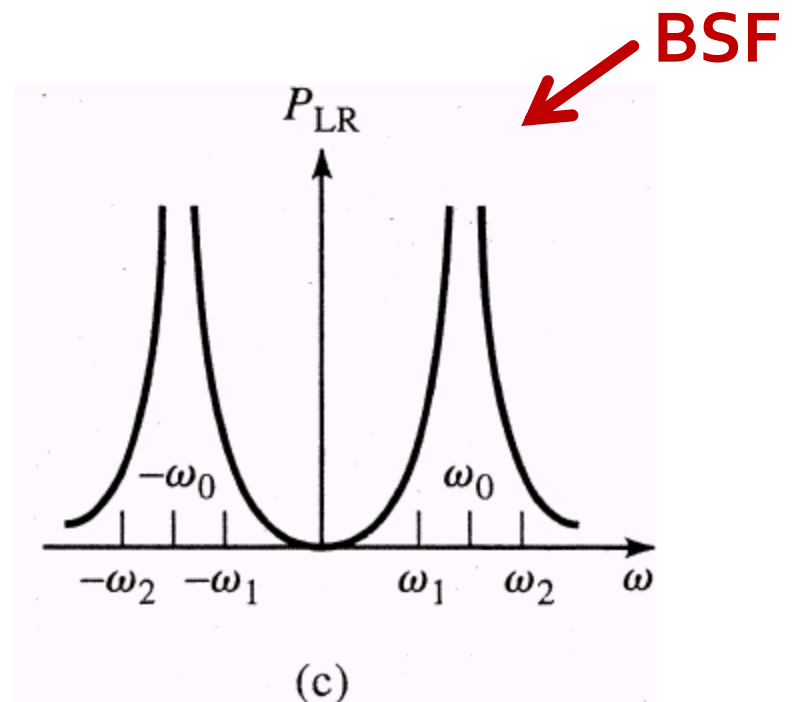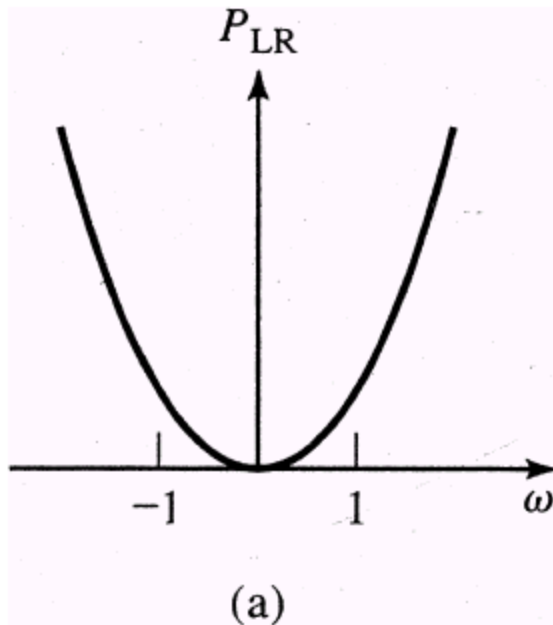
$$\omega \leftarrow -\Delta \cdot \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^{-1} \quad \omega = \omega_0 \rightarrow \frac{-\Delta}{\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)} = \frac{-\Delta}{\left(\frac{\omega_0}{\omega_0} - \frac{\omega_0}{\omega_0} \right)} \rightarrow \pm\infty$$



Bandstop Transformation LPF \rightarrow BSF

$$\omega \leftarrow -\Delta \cdot \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^{-1}$$


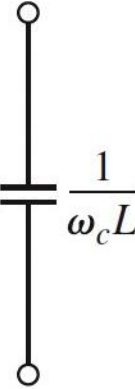
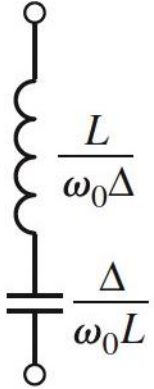
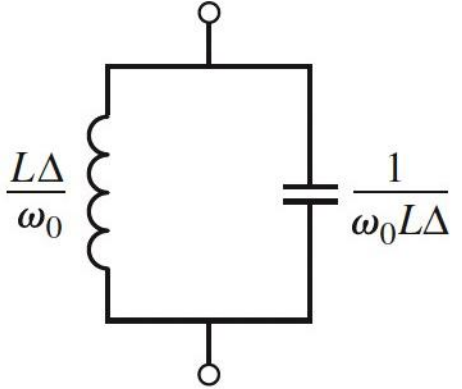
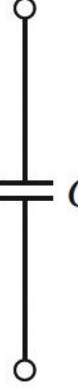
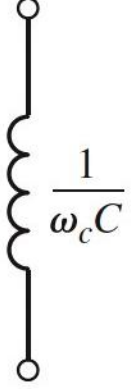
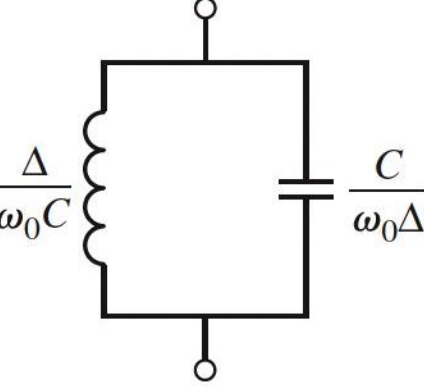
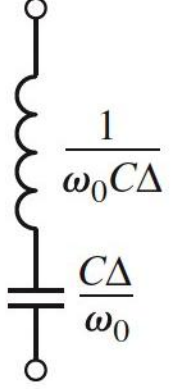
- A series **inductor** in the prototype filter is transformed to a **shunt LC circuit in series**

$$L'_k = \frac{\Delta \cdot L_k}{\omega_0} \quad C'_k = \frac{1}{\omega_0 \cdot \Delta \cdot L_k}$$

- A shunt **capacitor** in the prototype filter is transformed to a **series LC circuit in parallel**

$$L'_k = \frac{1}{\Delta \cdot \omega_0 \cdot C_k} \quad C'_k = \frac{\Delta \cdot C_k}{\omega_0}$$

Summary of Prototype Filter Transformations

Low-pass	High-pass	Bandpass	Bandstop
 <p style="text-align: center;">L</p>	 <p style="text-align: center;">$\frac{1}{\omega_c L}$</p>	 <p style="text-align: center;">$\frac{L}{\omega_0 \Delta}$ $\frac{\Delta}{\omega_0 L}$</p>	 <p style="text-align: center;">$\frac{L \Delta}{\omega_0}$ $\frac{1}{\omega_0 L \Delta}$</p>
 <p style="text-align: center;">C</p>	 <p style="text-align: center;">$\frac{1}{\omega_c C}$</p>	 <p style="text-align: center;">$\frac{\Delta}{\omega_0 C}$ $\frac{C}{\omega_0 \Delta}$</p>	 <p style="text-align: center;">$\frac{1}{\omega_0 C \Delta}$ $\frac{C \Delta}{\omega_0}$</p>

Example

- Design a 3rd order **bandpass** filter with 0.5 dB ripples in passband. The **center frequency** of the filter should be 1 GHz. The **fractional bandwidth** of the passband should be 10%, and the **impedance** 50Ω.

$$\omega_0 = 2 \cdot \pi \cdot 1 \text{ GHz} = 6.283 \cdot 10^9 \text{ rad / s}$$

$$\Delta = 0.1$$

LPF Prototype


- 0.5dB equal-ripple table or design formulas:

- $g_1 = 1.5963 = L_1/C_3,$

- $g_2 = 1.0967 = C_2/L_4,$



- $g_3 = 1.5963 = L_3/C_5,$

- $g_4 = 1.000 = R_L$

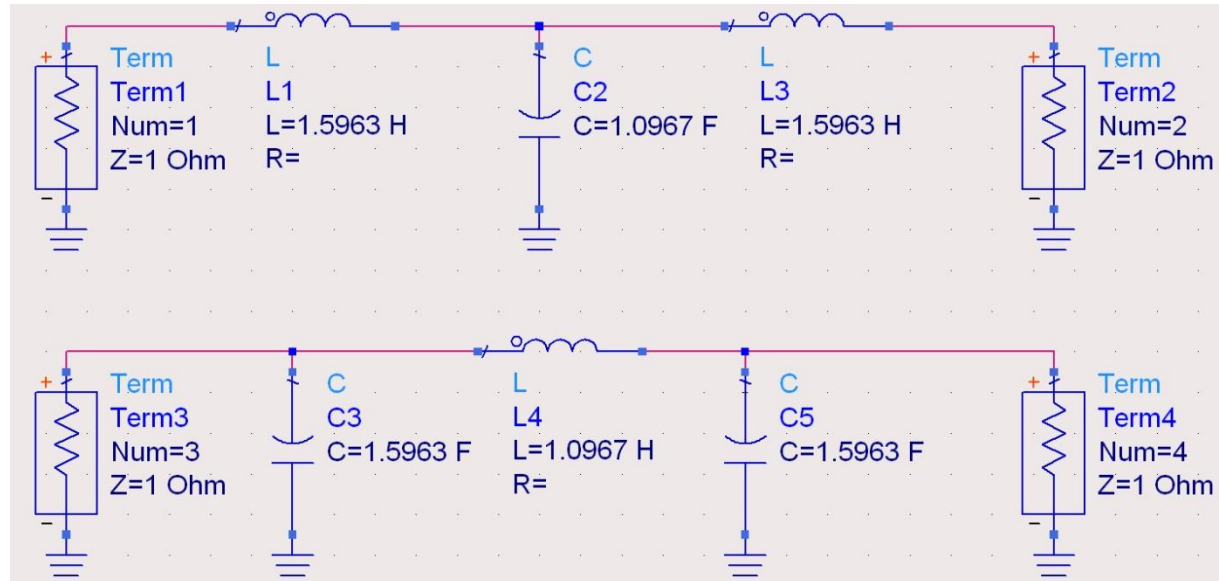

LPF Prototype

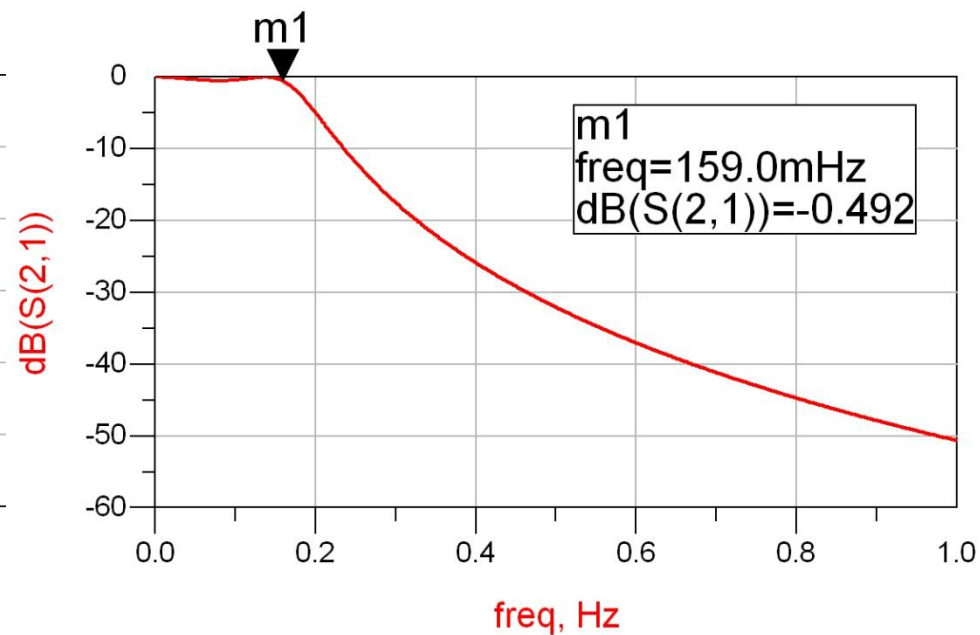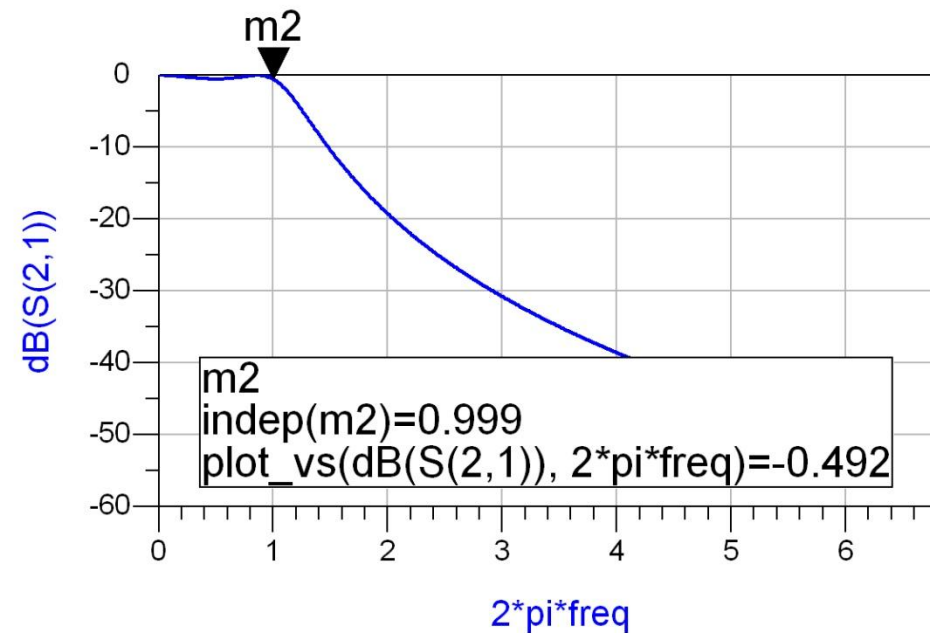- $\omega_o = 1 \text{ rad/s}$ ($f_o = \omega_o / 2\pi = 0.159 \text{ Hz}$)



Bandpass Transformation / BPF

$$\omega_0 = 2 \cdot \pi \cdot 1 \text{ GHz} = 6.283 \cdot 10^9 \text{ rad/s} \quad \Delta = \frac{\Delta\omega}{\omega_0} = \frac{\Delta f}{f_0} = 0.1 \quad R_0 = 50 \Omega$$

$$g_1 = 1.5963 = L_1,$$

$$g_3 = 1.5963 = L_3,$$

$$g_2 = 1.0967 = C_2,$$

$$g_4 = 1.000 = R_L$$

$$L'_1 = \frac{L_1 \cdot R_0}{\Delta \cdot \omega_0} = 127.0 \text{ nH}$$

$$C'_1 = \frac{\Delta}{\omega_0 \cdot L_1 \cdot R_0} = 0.199 \text{ pF}$$



$$L'_2 = \frac{\Delta \cdot R_0}{\omega_0 \cdot C_2} = 0.726 \text{ nH}$$

$$C'_2 = \frac{C_2}{\Delta \cdot \omega_0 \cdot R_0} = 34.91 \text{ pF}$$

$$L'_3 = \frac{L_3 \cdot R_0}{\Delta \cdot \omega_0} = 127.0 \text{ nH}$$

$$C'_3 = \frac{\Delta}{\omega_0 \cdot L_3 \cdot R_0} = 0.199 \text{ pF}$$

ADS

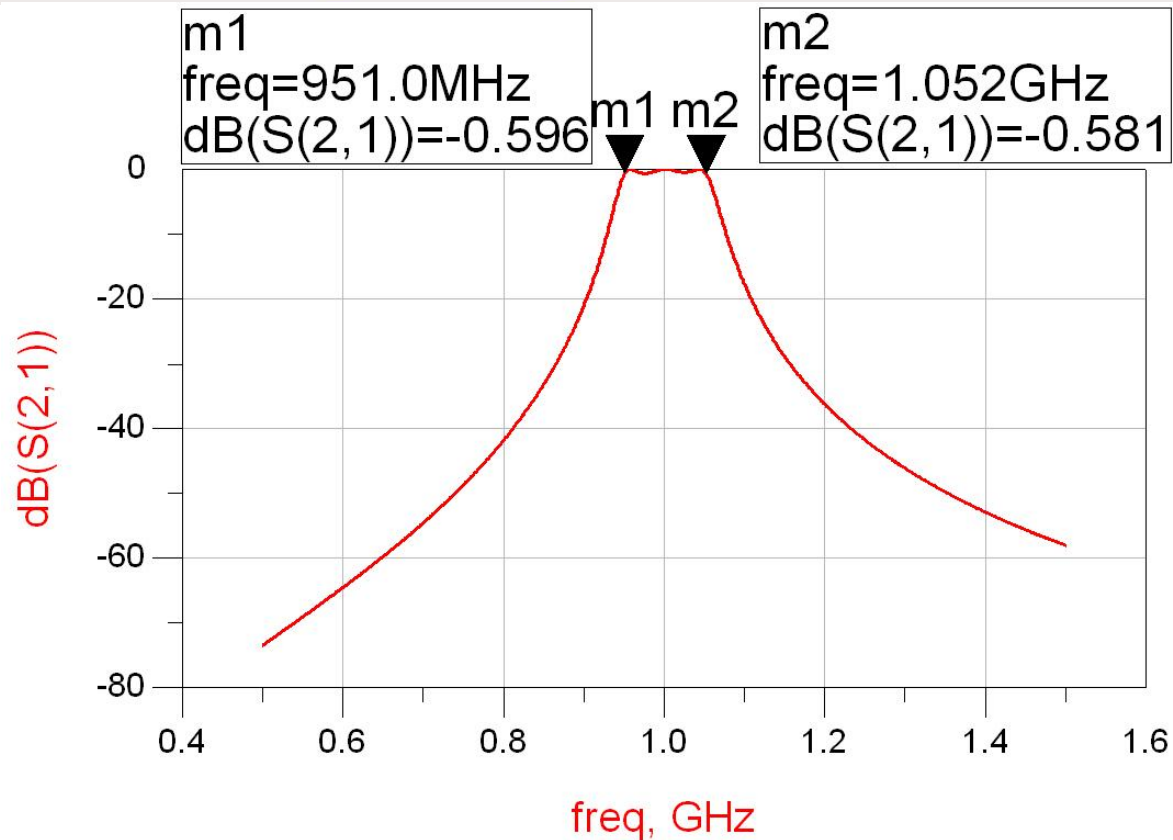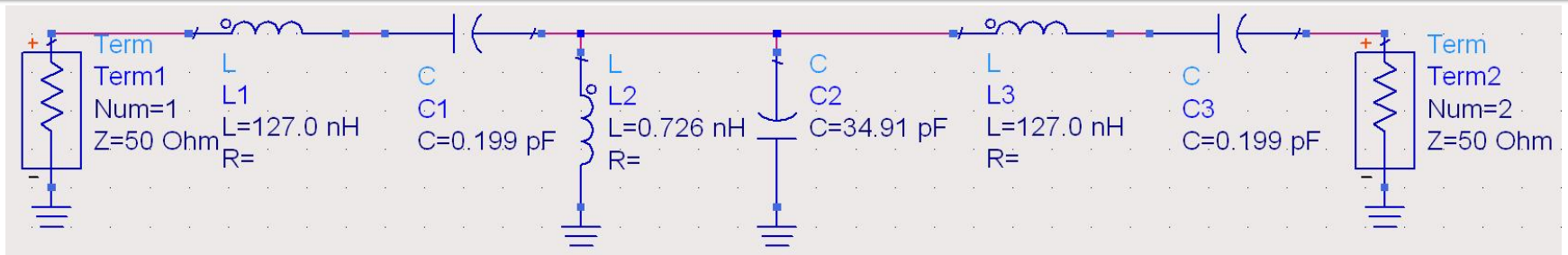

Microwave Filters Implementation

Microwave Filters Implementation

- The lumped-element (L, C) filter design generally works well **only** at low frequencies (RF):
 - lumped-element inductors and capacitors are generally available only for a limited range of values, and can be difficult to implement at microwave frequencies
 - difficulty to obtain the (very low) required tolerance for elements

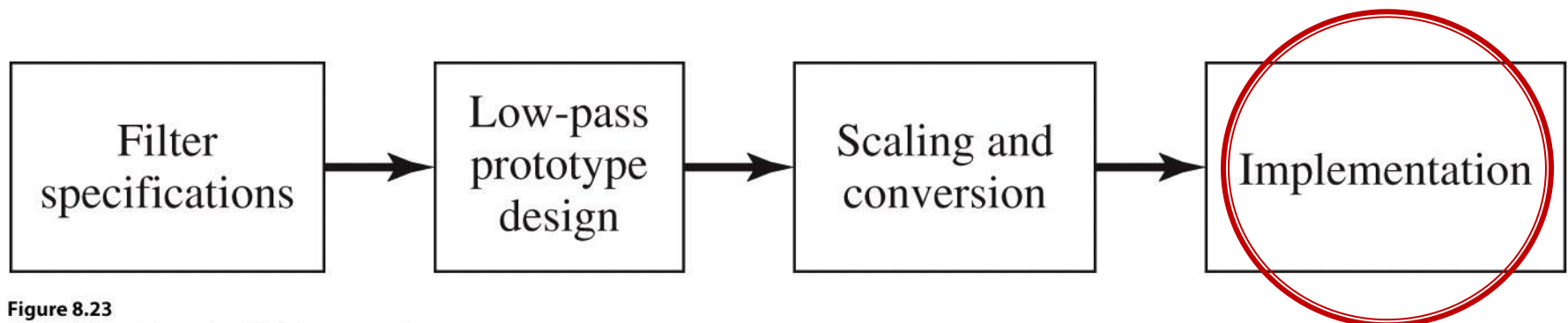


Figure 8.23

Richards' Transformation

- Impedance seen at the input of a line loaded with Z_L

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

- We prefer the load impedance to be:

- open circuit ($Z_L = \infty$) $Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l$

- short circuit ($Z_L = 0$) $Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l$

- Input impedance is:

- capacitive $Z_{in,oc} = j \cdot X_C = \frac{1}{j \cdot B_C}$ $Z_0 \leftrightarrow \frac{1}{C}$ $\tan \beta \cdot l \leftrightarrow \omega$

- inductive $Z_{in,sc} = j \cdot X_L$ $Z_0 \leftrightarrow L$ $\tan \beta \cdot l \leftrightarrow \omega$

Richards' Transformation

- Variable substitution

$$\Omega = \tan \beta \cdot l = \tan \left(\frac{\omega \cdot l}{v_p} \right)$$

- With this variable substitution we define:
 - reactance of an inductor

$$j \cdot X_L = j \cdot \Omega \cdot L = j \cdot L \cdot \tan \beta \cdot l$$

- susceptance of a capacitor



$$j \cdot B_C = j \cdot \Omega \cdot C = j \cdot C \cdot \tan \beta \cdot l$$

- The equivalent filter in Ω has a cutoff frequency at:

$$\Omega = 1 = \tan \beta \cdot l \quad \rightarrow \quad \beta \cdot l = \frac{\pi}{4} \quad \rightarrow \quad l = \frac{\lambda}{8}$$

Richards' Transformation

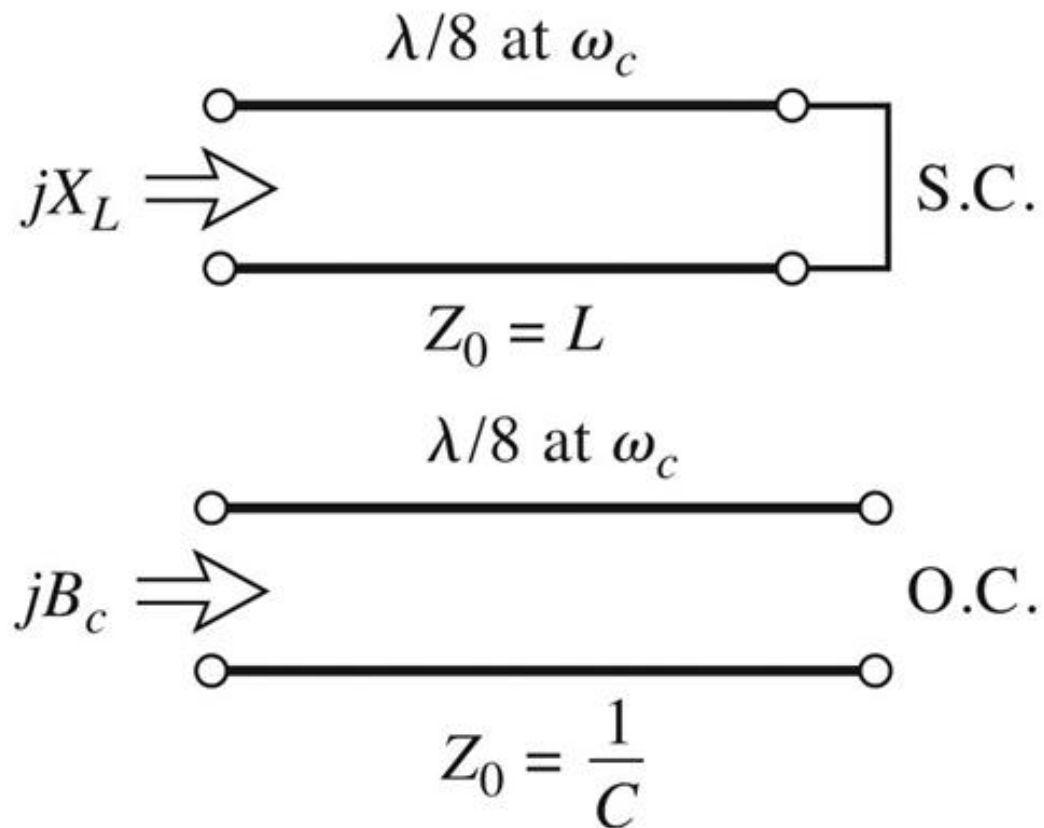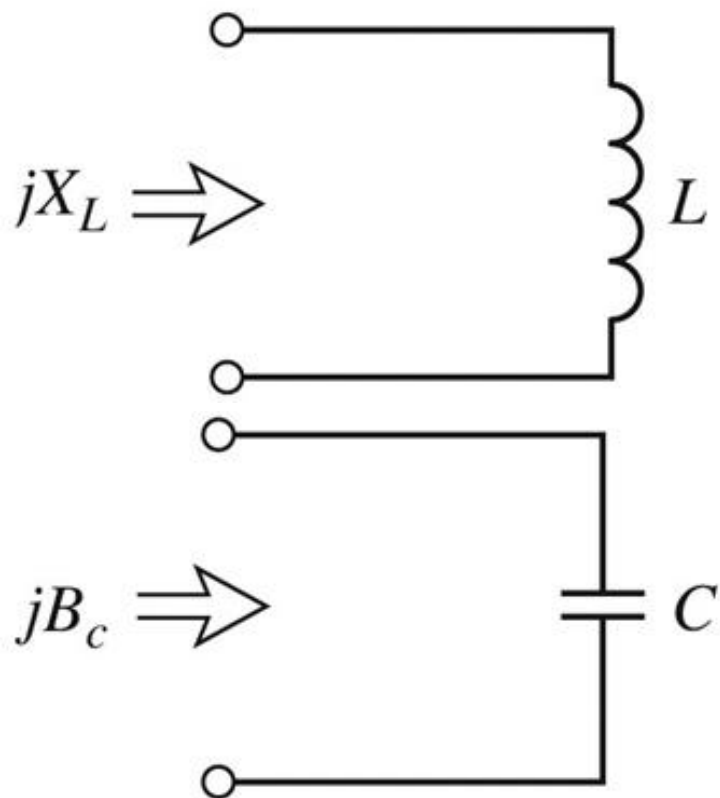- allows implementation of the inductors and capacitors with lines **after** the transformation of the LPF prototype to the required type (LPF/HPF/BPF/BSF)



Richards' Transformation

- By choosing the open-circuited or short-circuited lines to be $\lambda/8$ at the desired cutoff frequency (ω_c) and the corresponding characteristic impedances (L/C from LPF prototype) we will obtain at frequencies around ω_c a behavior similar to that of the prototype filter.
 - At frequencies far from ω_c the behavior of the filter will no longer be identical to that of the prototype (in specific situations the correct behavior must be **verified**)
 - Frequency scaling is simplified: choosing the appropriate physical length of the line to have the electrical length $\lambda/8$ at the desired cutoff frequency
- All lines will have equal electrical lengths ($\lambda/8$) and thus comparable physical lengths, so the lines are called **commensurate** lines

Richards' Transformation

- At the frequency $\omega = 2 \cdot \omega_c$ the lines will be $\lambda/4$ long

$$l = \frac{\lambda}{4} \Rightarrow \beta \cdot l = \frac{\pi}{2} \Rightarrow \tan \beta \cdot l \rightarrow \infty$$

- an supplemental attenuation pole will occur at $2 \cdot \omega_c$ (LPF):
 - inductances (usually in series) $Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l \rightarrow \infty$
 - capacitances (usually shunt) $Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l \rightarrow 0$

Richards' Transformation

- the periodicity of tan function implies the periodicity of the filter implemented with lines
 - the filter response will be repeated every $4 \cdot \omega_c$

$$\tan(\alpha + \pi) = \tan \alpha$$

$$\beta \cdot l \Big|_{\omega=\omega_c} = \frac{\pi}{4} \quad \Rightarrow \quad \frac{\omega_c \cdot l}{v_p} = \frac{\pi}{4} \quad \Rightarrow \quad \pi = \frac{(4 \cdot \omega_c) \cdot l}{v_p}$$



$$Z_{in}(\omega) = Z_{in}(\omega + 4 \cdot \omega_c) \quad \Rightarrow \quad P_{LR}(\omega) = P_{LR}(\omega + 4 \cdot \omega_c)$$

$$P_{LR}(4 \cdot \omega_c) = P_{LR}(0) \quad P_{LR}(3 \cdot \omega_c) = P_{LR}(-\omega_c) \quad P_{LR}(5 \cdot \omega_c) = P_{LR}(\omega_c)$$

Example

- Low-pass filter 4th order, 4 GHz cutoff frequency, maximally flat design (working with 50Ω source and load)
- maximally flat table or formulas:
 - $g_1 = 0.7654 = L_1$
 - $g_2 = 1.8478 = C_2$
 - $g_3 = 1.8478 = L_3$
 - $g_4 = 0.7654 = C_4$
 - $g_5 = 1$ (**does not** need supplemental impedance matching – required only for even order equal-ripple filters)

LPF Prototype

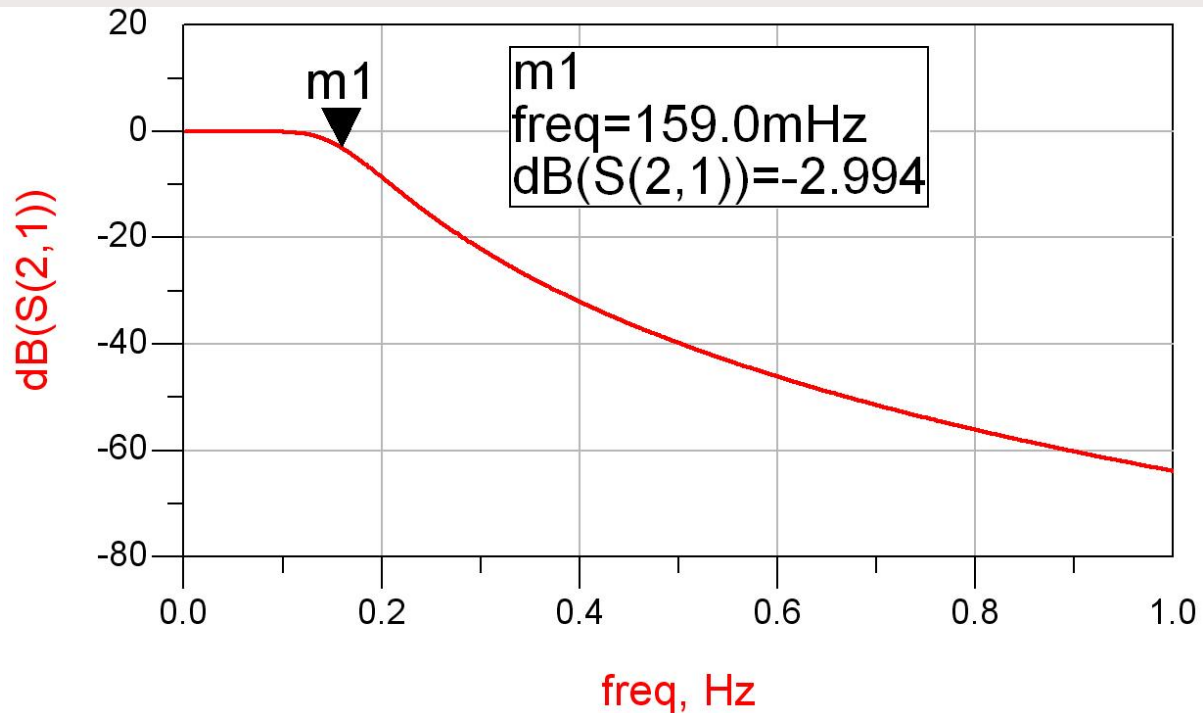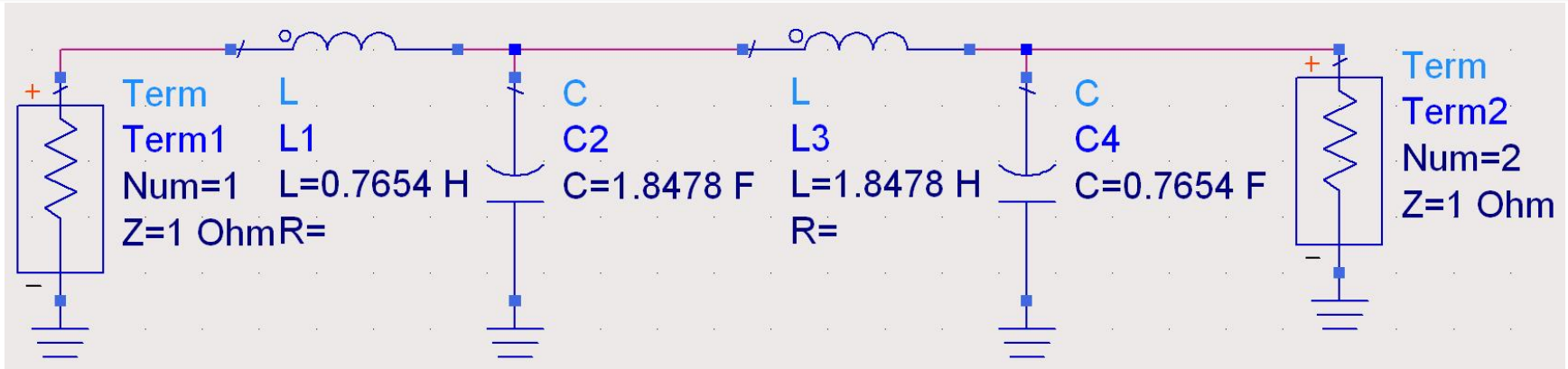

Lumped elements

$$\omega_c = 2 \cdot \pi \cdot 4\text{GHz} = 2.5133 \cdot 10^{10} \text{rad/s}$$

$$g_1 = 0.7654 = L_1,$$

$$g_2 = 1.8478 = C_2,$$

$$g_3 = 1.8478 = L_3,$$

$$g_4 = 0.7654 = C_4,$$

$$g_5 = 1 = RL$$



$$L'_1 = \frac{R_0 \cdot L_1}{\omega_c} = 1.523 \text{nH}$$

$$C'_2 = \frac{C_2}{R_0 \cdot \omega_c} = 1.470 \text{pF}$$

$$L'_3 = \frac{R_0 \cdot L_3}{\omega_c} = 3.676 \text{nH}$$

$$C'_4 = \frac{C_4}{R_0 \cdot \omega_c} = 0.609 \text{pF}$$



Lumped elements – ADS

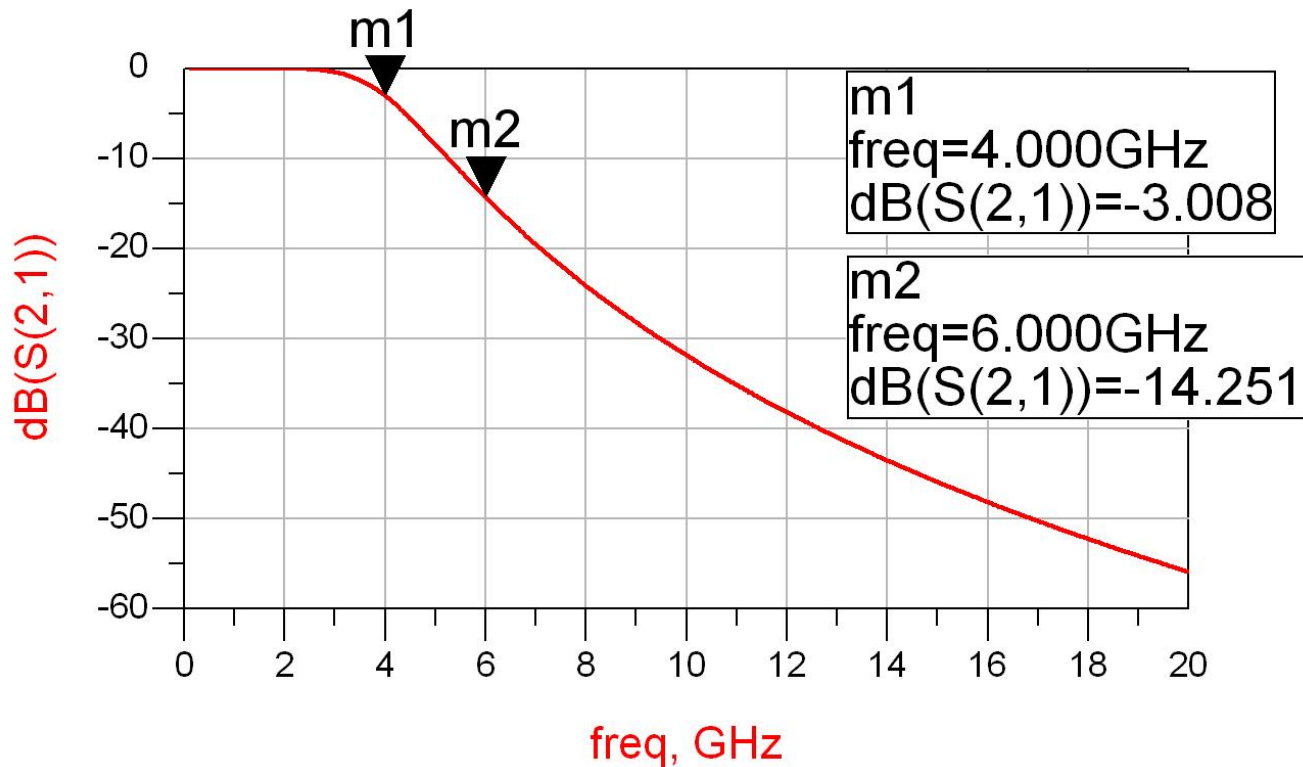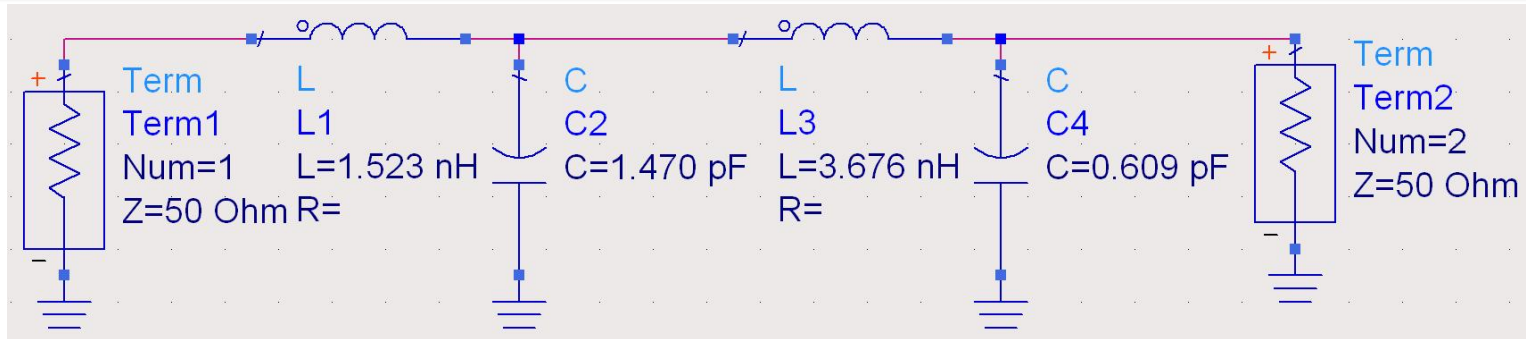

Richards' Transformation


- LPF Prototype parameters:
 - $g_1 = 0.7654 = L_1$
 - $g_2 = 1.8478 = C_2$
 - $g_3 = 1.8478 = L_3$
 - $g_4 = 0.7654 = C_4$
- Normalized line impedances
 - $z_1 = 0.7654 = \text{series / short circuit}$ $Z_0 \leftrightarrow \frac{1}{C}$
 - $z_2 = 1 / 1.8478 = 0.5412 = \text{shunt / open circuit}$
 - $z_3 = 1.8478 = \text{series / short circuit}$ $Z_0 \leftrightarrow L$
 - $z_4 = 1 / 0.7654 = 1.3065 = \text{shunt / open circuit}$
- Impedance scaling by multiplying with $Z_0 = 50\Omega$
- All lines must have the length equal to $\lambda/8$ (electrical length $E = 45^\circ$) at 4GHz

Richards' Transformation – ADS

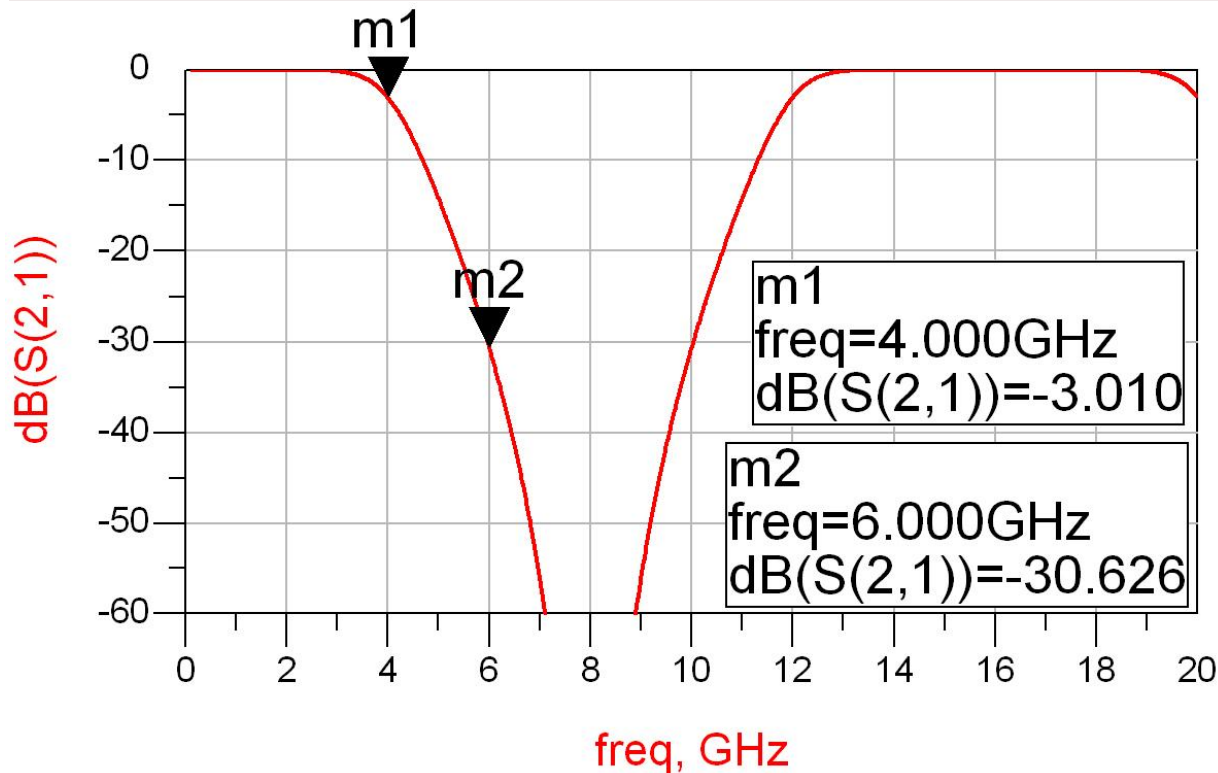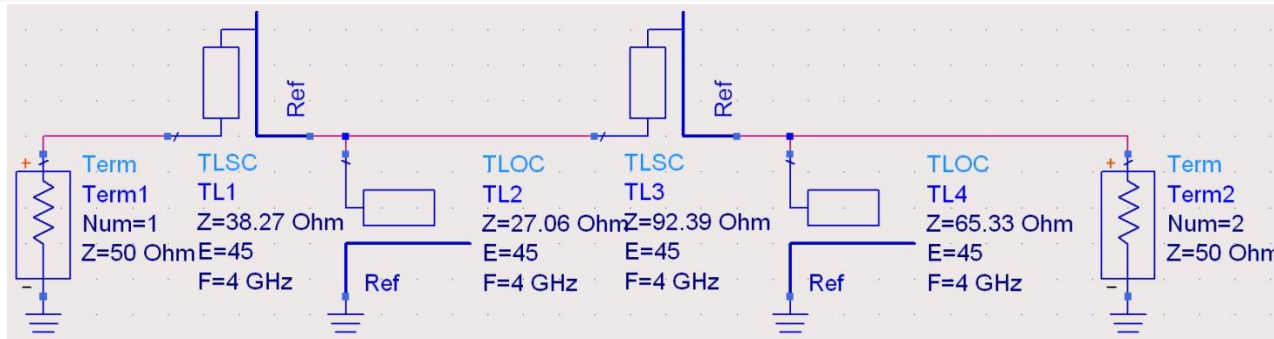

Richards' Transformation

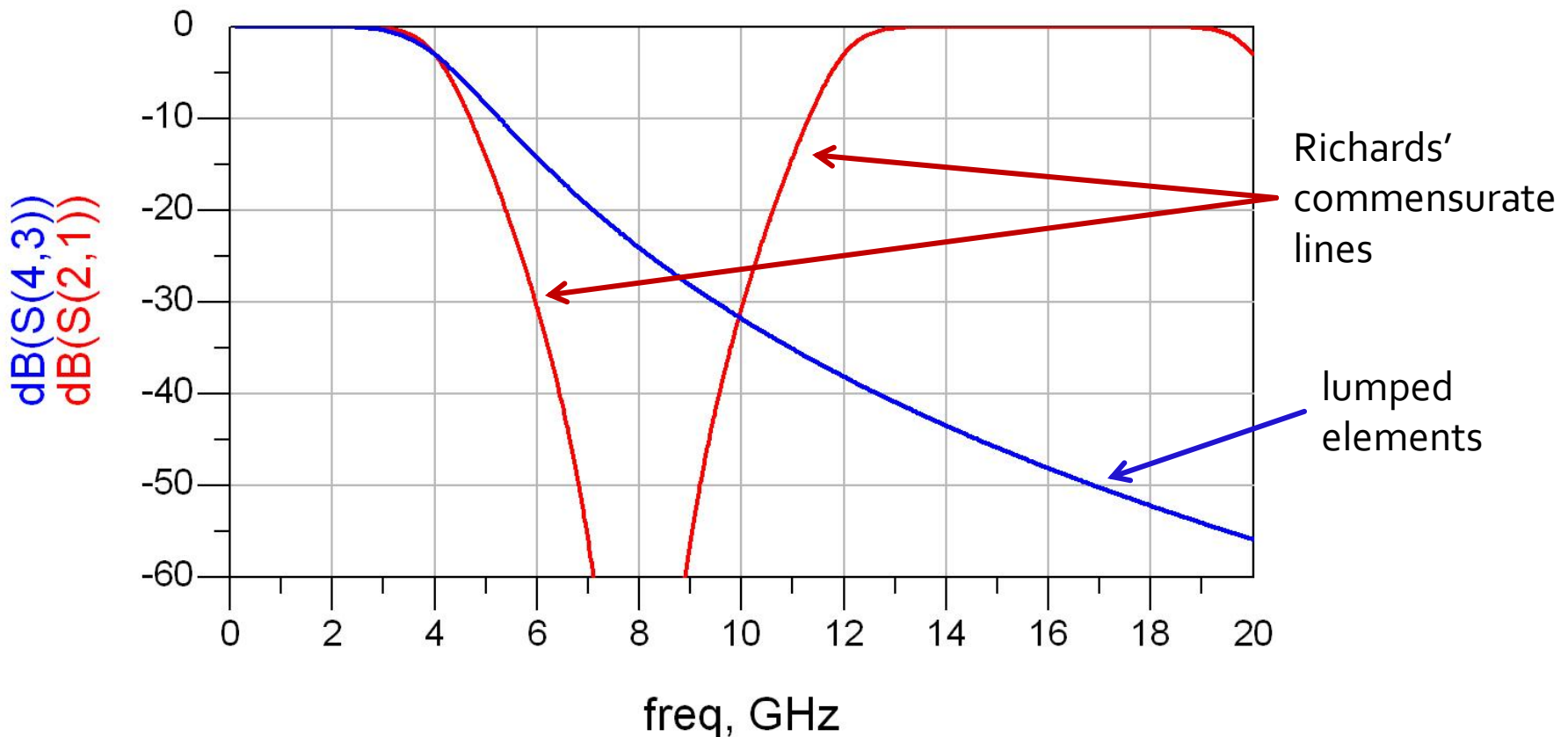- Filters implemented with Richards' Transformation
 - beneficiate from the supplemental pole at $2 \cdot \omega_c$
 - have the major disadvantage of frequency periodicity, a supplemental non-periodic LPF must be inserted if needed



Equal-ripple prototype



- For even N order of the filter (N = 2, 4, 6, 8 ...) equal-ripple filters **must** closed by a non-standard load impedance **$g_{N+1} \neq 1$**
- If the application doesn't allow this, supplemental impedance matching is required (quarter-wave transformer, binomial ...) to **$g_L = 1$**

$$g_{N+1} \neq 1 \rightarrow R \neq R_0 \quad (50\Omega)$$

Observation: even order equal-ripple


- Same filter, 3dB equal-ripple
- 3dB equal-ripple tables or formulas:
 - $g_1 = 3.4389 = L_1$
 - $g_2 = 0.7483 = C_2$
 - $g_3 = 4.3471 = L_3$
 - $g_4 = 0.5920 = C_4$
 - $g_5 = 5.8095 = R_L$
- Line impedances
 - $Z_1 = 3.4389 \cdot 50\Omega = 171.945\Omega = \text{series / short circuit}$
 - $Z_2 = 50\Omega / 0.7483 = 66.818\Omega = \text{shunt / open circuit}$
 - $Z_3 = 4.3471 \cdot 50\Omega = 217.355\Omega = \text{series / short circuit}$
 - $Z_4 = 50\Omega / 0.5920 = 84.459\Omega = \text{shunt / open circuit}$
 - $R_L = 5.8095 \cdot 50\Omega = 295.475\Omega = \text{load}$

Even order equal-ripple – ADS

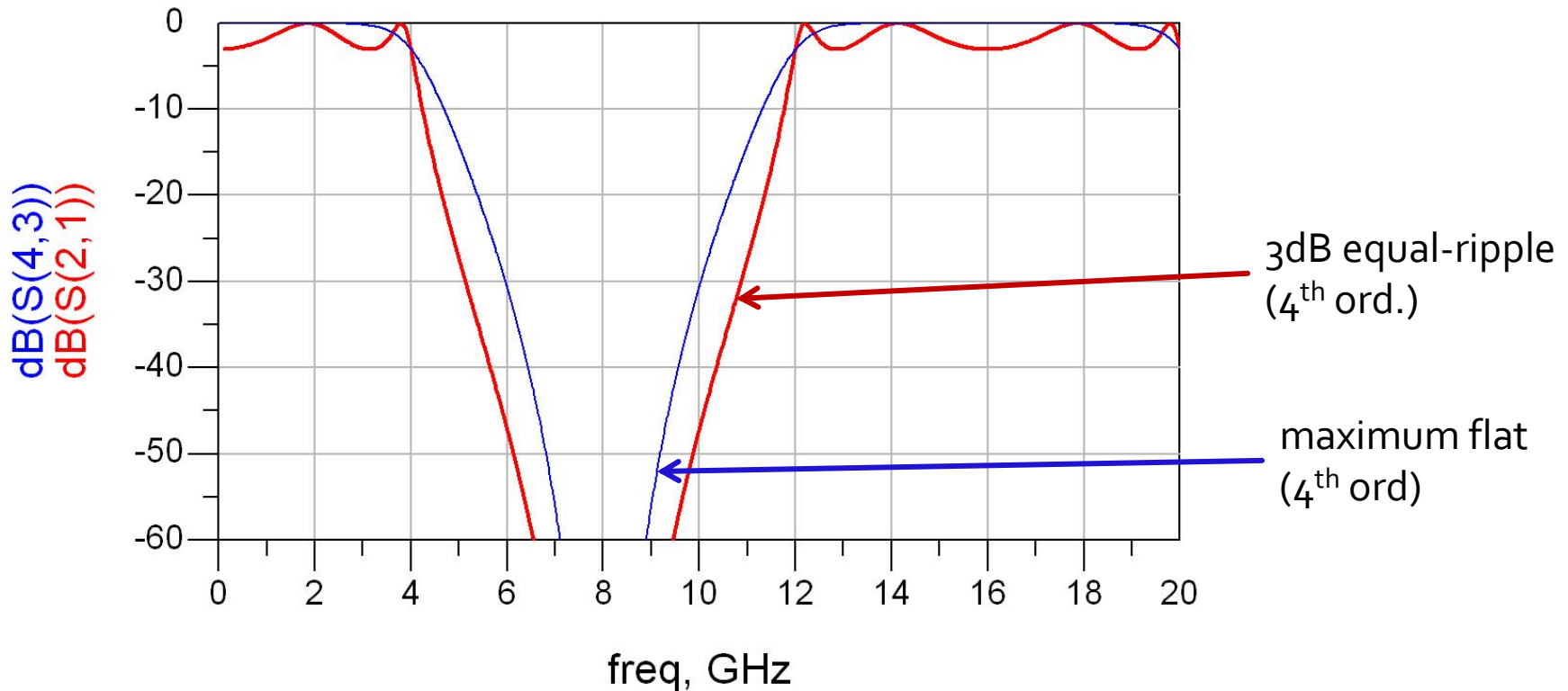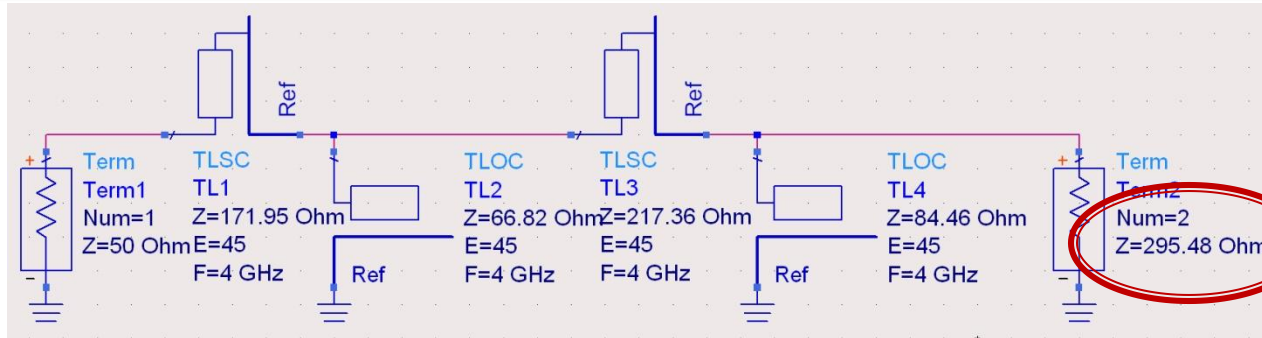

Observation: even order equal-ripple

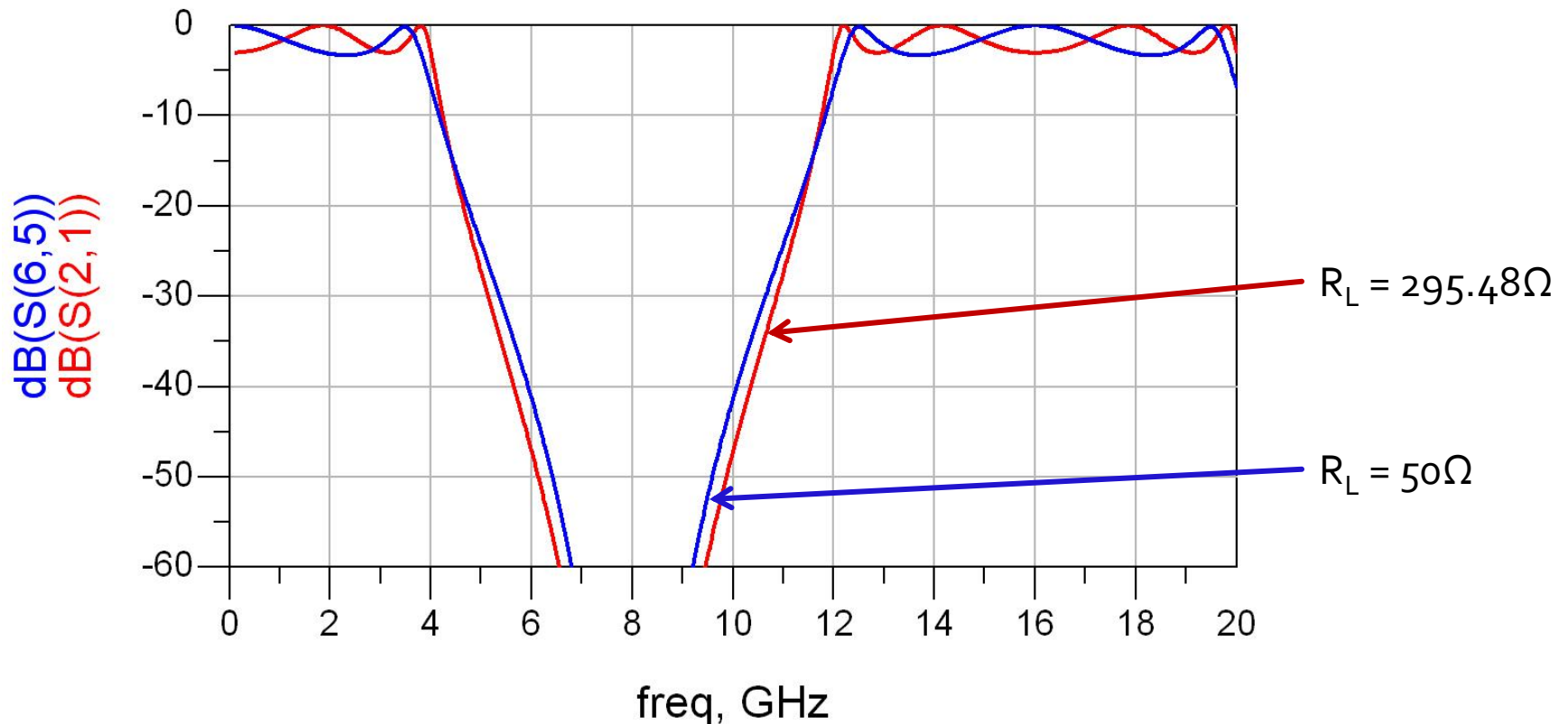- Even order equal-ripple filters need output matching towards 50Ω for precise results.
Example:



Contact

- Microwave and Optoelectronics Laboratory
- <https://rf-opto.etti.tuiasi.ro>
- rdamian@etti.tuiasi.ro