

Lecture 3  
2025/2026

# Microwave Devices and Circuits for Radiocommunications

# 2025/2026

- 2C/1L, **MDCR**
- Attendance at minimum 7 sessions (course or laboratory)
- Lectures- **associate professor Radu Damian**
  - Tuesday **12-14, P2**
  - E – 50% final grade
  - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
    - first test L1: 24.02.2026 (t2 and t3 not announced, lecture)
    - 3att.=+0.5p
  - all materials/equipments authorized

# 2025/2026

- Laboratory – **associate professor Radu Damian**
  - Monday 14-16, II.13 / (even weeks)
  - L – 25% final grade
    - ADS, 4 sessions
    - Attendance + **personal results**
  - P – 25% final grade
    - ADS, 3 sessions (-1? 24.02.2026)
    - personal homework

# Materials

■ <https://rf-opto.etti.tuiasi.ro>

The screenshot shows a web browser window with the URL [https://rf-opto.etti.tuiasi.ro/microwave\\_cd.php?chg\\_lang=0](https://rf-opto.etti.tuiasi.ro/microwave_cd.php?chg_lang=0). The page features a dark blue navigation bar with links for Main, Courses, Master, Staff, Research, Students, and Admin. Below this is a secondary navigation bar with links for Microwave CD, Optical Communications, Optoelectronics, Internet, Antennas, Practica, Networks, and Educational software. The main content area is titled "Microwave Devices and Circuits for Radiocommunications (English)".

**Course: MDCR (2017-2018)**

Course Coordinator: Assoc.P. Dr. Radu-Florin Damian  
Code: EDOS412T  
Discipline Type: DOS; Alternative, Specialty  
Credits: 4  
Enrollment Year: 4, Sem. 7

**Activities**

Course: Instructor: Assoc.P. Dr. Radu-Florin Damian, 2 Hours/Week, Specialization Section, Timetable:  
Laboratory: Instructor: Assoc.P. Dr. Radu-Florin Damian, 1 Hours/Week, Group, Timetable:

**Evaluation**

Type: Examen

A: 50%, (Test/Colloquium)  
B: 25%, (Seminary/Laboratory/Project Activity)  
D: 25%, (Homework/Specialty papers)

**Grades**

[Aggregate Results](#)

**Attendance**

[Course](#)  
[Laboratory](#)

**Lists**

[Bonus-uri acumulate \(final\)](#)  
[Studenti care nu pot intra in examen](#)

**Materials**

Course Slides

- [MDCR Lecture 1](#) (pdf, 5.43 MB, en, [🔗](#))
- [MDCR Lecture 2](#) (pdf, 3.67 MB, en, [🔗](#))
- [MDCR Lecture 3](#) (pdf, 4.76 MB, en, [🔗](#))
- [MDCR Lecture 4](#) (pdf, 5.58 MB, en, [🔗](#))

On the right side of the screenshot, there is a dark blue banner for "RF-OPTO" with the ETTI logo and the University of Tuiasi logo. Below the banner, there are language selection options: "English" (with a UK flag icon) and "Romana" (with a Romanian flag icon). The "English" option is circled in red. Below the banner is another navigation bar with links for Main, Courses, Master, Staff, and Research. Below that is a third navigation bar with links for Grades, Student List, Exams, and Photos. The main content area on the right is titled "Online Exams" and contains the text "In order to participate at online exams you must get ready following".

# Materials

- RF-OPTO
  - <https://rf-opto.etti.tuiasi.ro>
- **David Pozar, “Microwave Engineering”,**  
Wiley; 4th edition , 2011
  - 1 exam problem ← Pozar
- Photos
  - sent by **online exam**
  - used at lectures/laboratory

# Examen: Logarithmic scales

$$\text{dB} = 10 \cdot \log_{10} (P_2 / P_1)$$

0 dB	= 1
+ 0.1 dB	= 1.023 (+2.3%)
+ 3 dB	= 2
+ 5 dB	= 3
+ 10 dB	= 10
-3 dB	= 0.5
-10 dB	= 0.1
-20 dB	= 0.01
-30 dB	= 0.001

$$\text{dBm} = 10 \cdot \log_{10} (P / 1 \text{ mW})$$

0 dBm	= 1 mW
3 dBm	= 2 mW
5 dBm	= 3 mW
10 dBm	= 10 mW
20 dBm	= 100 mW
-3 dBm	= 0.5 mW
-10 dBm	= 100 $\mu$ W
-30 dBm	= 1 $\mu$ W
-60 dBm	= 1 nW

$$[\text{dBm}] + [\text{dB}] = [\text{dBm}]$$

$$[\text{dBm/Hz}] + [\text{dB}] = [\text{dBm/Hz}]$$


$$[x] + [\text{dB}] = [x]$$

# Exam

- Complex numbers arithmetic!!!!
- $z = a + j \cdot b ; j^2 = -1$
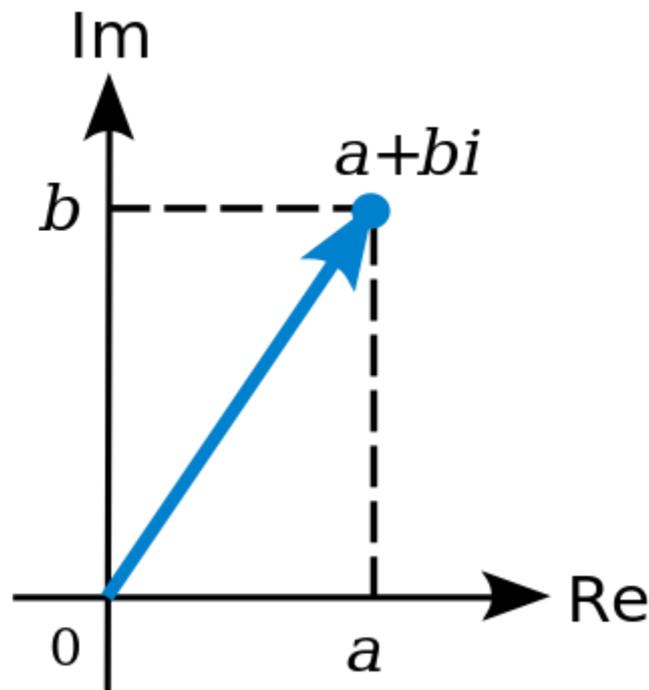
# Complex plane

- abscissa – real part
- ordinate – imaginary part
- any of them can be negative, whole plane, 4 quadrants




# Polar representation

- Polar representation
  - modulus
  - phase relative to the real axis

$$z = a + j \cdot b = |z| \cdot (\cos \varphi + j \cdot \sin \varphi)$$

$$|z| = \sqrt{a^2 + b^2}$$
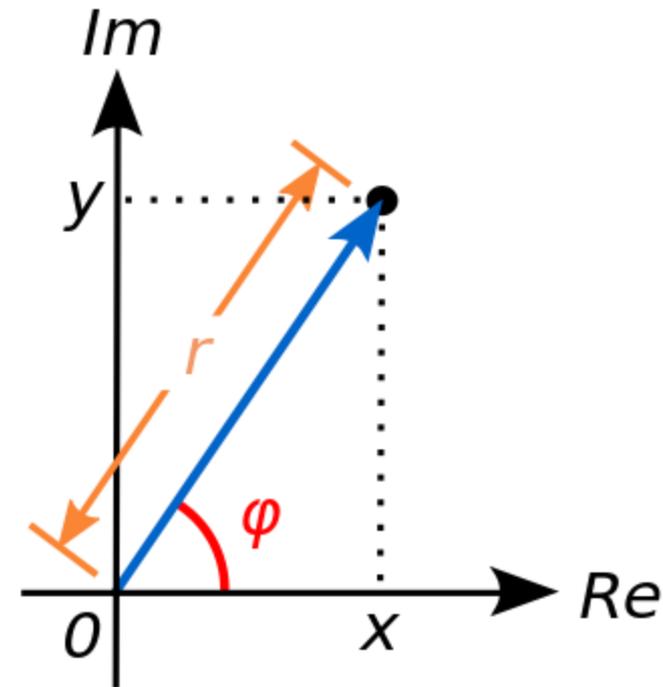
$$\varphi = \arg(z) = \begin{cases} \arctan\left(\frac{b}{a}\right), & a > 0 \\ \arctan\left(\frac{b}{a}\right) + \pi, & a < 0, b \geq 0 \\ \arctan\left(\frac{b}{a}\right) - \pi, & a < 0, b < 0 \\ \frac{\pi}{2}, -\frac{\pi}{2}, \text{nedefinit} & a = 0 \end{cases}$$



# Polar representation

- Euler's formula

$$e^{j \cdot x} = \cos x + j \cdot \sin x; \forall x \in R$$

- Polar representation

$$z = a + j \cdot b = |z| \cdot e^{j \cdot \varphi}$$


$$z = a + j \cdot b = |z| \cdot (\cos \varphi + j \cdot \sin \varphi)$$

$$z^n = (|z| \cdot e^{j \cdot \varphi})^n = |z|^n \cdot e^{j \cdot n \cdot \varphi} = |z|^n \cdot [\cos(n \cdot \varphi) + j \cdot \sin(n \cdot \varphi)]$$

→ 
$$\sqrt{z} = (|z| \cdot e^{j \cdot \varphi})^{1/2} = \sqrt{|z|} \cdot e^{j \cdot \frac{\varphi}{2}} = \sqrt{|z|} \cdot \left( \cos \frac{\varphi}{2} + j \cdot \sin \frac{\varphi}{2} \right)$$

$$z \cdot w = |z| \cdot e^{j \cdot \varphi} \cdot |w| \cdot e^{j \cdot \theta} = |z| \cdot |w| \cdot e^{j \cdot (\varphi + \theta)} = |z| \cdot |w| \cdot [\cos(\varphi + \theta) + j \cdot \sin(\varphi + \theta)]$$

$$z/w = \frac{|z| \cdot e^{j \cdot \varphi}}{|w| \cdot e^{j \cdot \theta}} = \frac{|z|}{|w|} \cdot e^{j \cdot \varphi} \cdot e^{-j \cdot \theta} = \frac{|z|}{|w|} \cdot [\cos(\varphi - \theta) + j \cdot \sin(\varphi - \theta)]$$

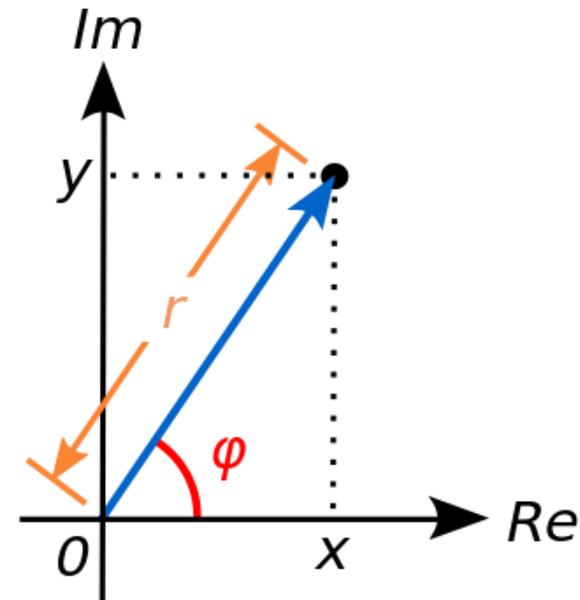

# Polar representation

- Polar representation

$$|z| = \sqrt{a^2 + b^2}$$


$$|z|^2 = z \cdot z^*$$

⇒ ⇒

$$|e^{j \cdot x}| = |\cos x + j \cdot \sin x| = \sqrt{\cos^2 x + \sin^2 x} = 1$$

$$|e^{j \cdot x}| = 1; \quad \forall x \in R$$

$$\begin{aligned} z^* &= (|z| \cdot e^{j \cdot \varphi})^* = |z| \cdot (\cos \varphi + j \cdot \sin \varphi)^* = |z| \cdot (\cos \varphi - j \cdot \sin \varphi) = \\ &= |z| \cdot [\cos(-\varphi) + j \cdot \sin(-\varphi)] = |z| \cdot e^{-j \cdot \varphi} \end{aligned}$$

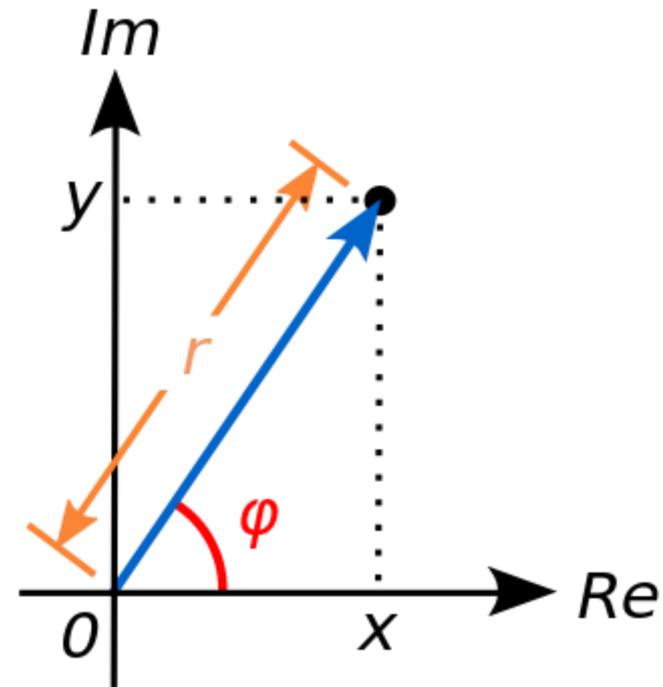


# Polar representation

- standard unit for angles – radians
- microwaves traditional unit for angles – **degrees in decimal form** ( $55.89^\circ$ )

$$\varphi = \arg(z) = \begin{cases} \arctan\left(\frac{b}{a}\right), & a > 0 \\ \arctan\left(\frac{b}{a}\right) + \pi, & a < 0, b \geq 0 \\ \arctan\left(\frac{b}{a}\right) - \pi, & a < 0, b < 0 \\ \frac{\pi}{2}, -\frac{\pi}{2}, \text{nedefinit} & a = 0 \end{cases}$$


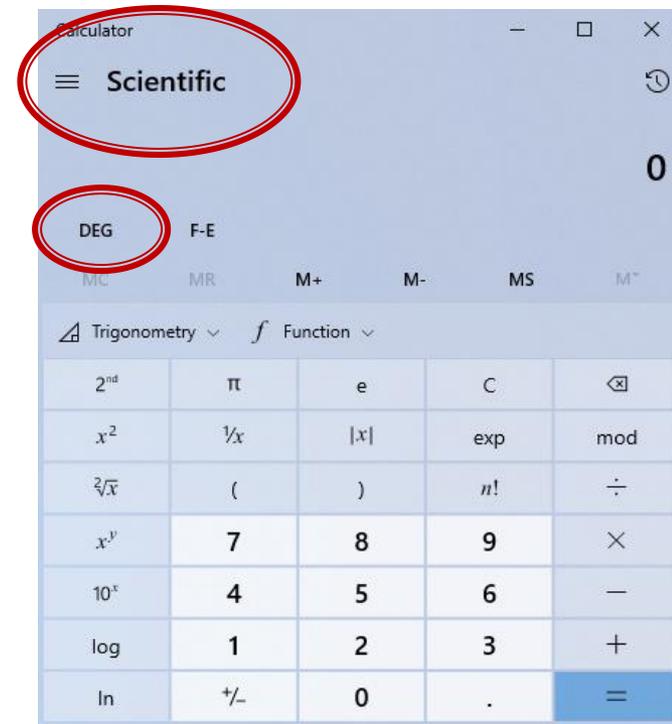
$$\varphi[^\circ] = 180^\circ \cdot \frac{\varphi[\text{rad}]}{\pi} \qquad \varphi[\text{rad}] = \pi \cdot \frac{\varphi[^\circ]}{180^\circ}$$


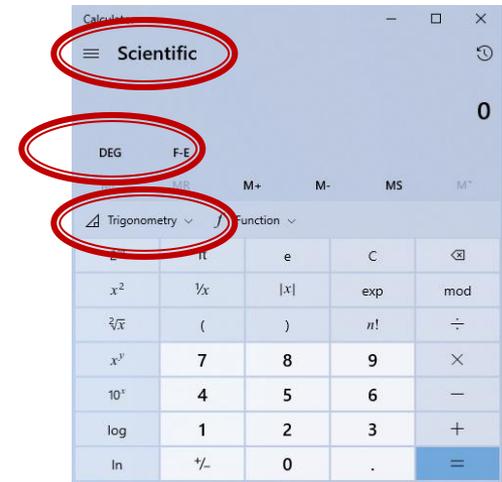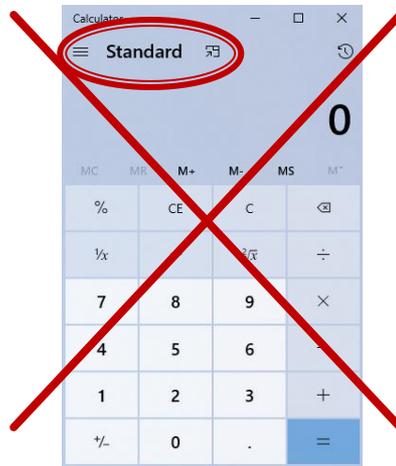
# Polar representation

- **Attention to angle numerical values!!**
  - math software – work in standard unit: radians
    - a **conversion** is necessary before and after using a trigonometric function (sin, cos, tan, atan, tanh)
  - scientific calculators have the built-in option of choosing the angle unit
    - always **double check** current working unit

$$\varphi[^\circ] = 180^\circ \cdot \frac{\varphi[rad]}{\pi}$$
$$\varphi[rad] = \pi \cdot \frac{\varphi[^\circ]}{180^\circ}$$



# Introduction

---

# ~ Microwaves

- Electrical Length (Phase Length)
  - $l$  – physical length
  - $E = \beta \cdot l$  – electrical Length

$$E = \beta \cdot l = \frac{2\pi}{\lambda} \cdot l = 2\pi \cdot \left( \frac{l}{\lambda} \right)$$

$$E = \beta \cdot l = \frac{2\pi}{c_0} \cdot (l \cdot f \cdot \sqrt{\epsilon_r})$$

V, I vary  
~ useless


- Dependency
  - antenna gain
  - radar cross-section

# Electrical Length

- Behavior (and description) of any circuit depends on his electrical length at the particular frequency of interest

- $E \approx 0 \rightarrow$  Kirchhoff
- $E > 0 \rightarrow$  wave propagation
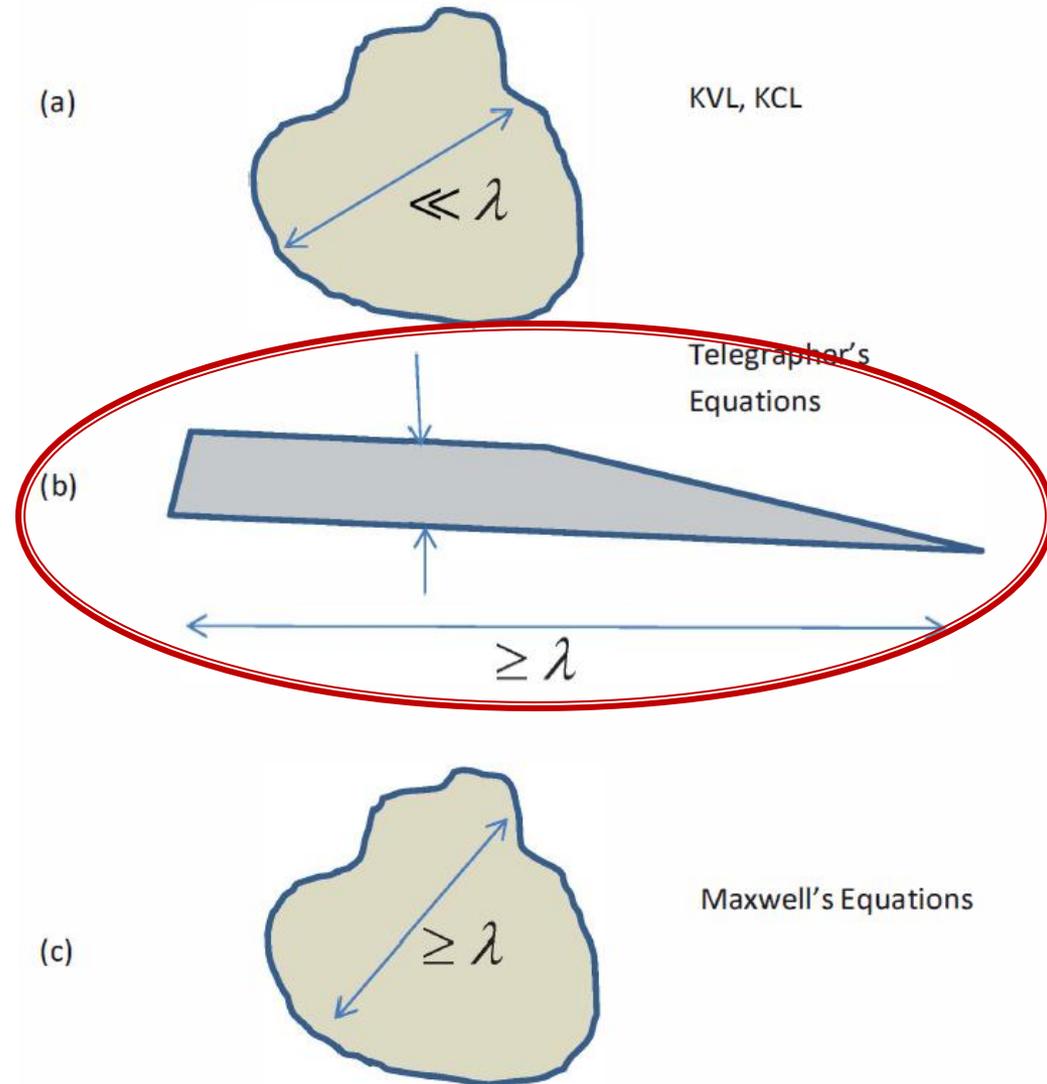
$$E = \beta \cdot l = \frac{2\pi}{\lambda} \cdot l = 2\pi \cdot \left( \frac{l}{\lambda} \right)$$



# TEM transmission lines

# Course Topics

- **Transmission lines**
- Impedance matching and tuning
- Directional couplers
- Power dividers
- Microwave amplifier design
- Microwave filters
- ~~Oscillators and mixers?~~




# Transmission line

- TEM wave propagation, at least two conductors

$$I(z,t)$$




$$V(z,t)$$

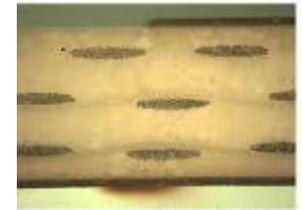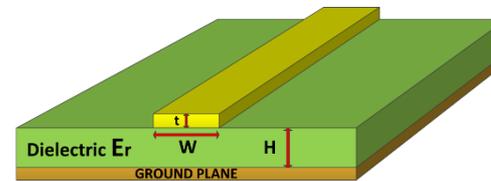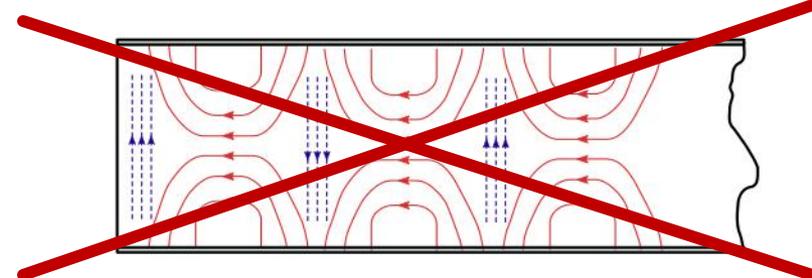
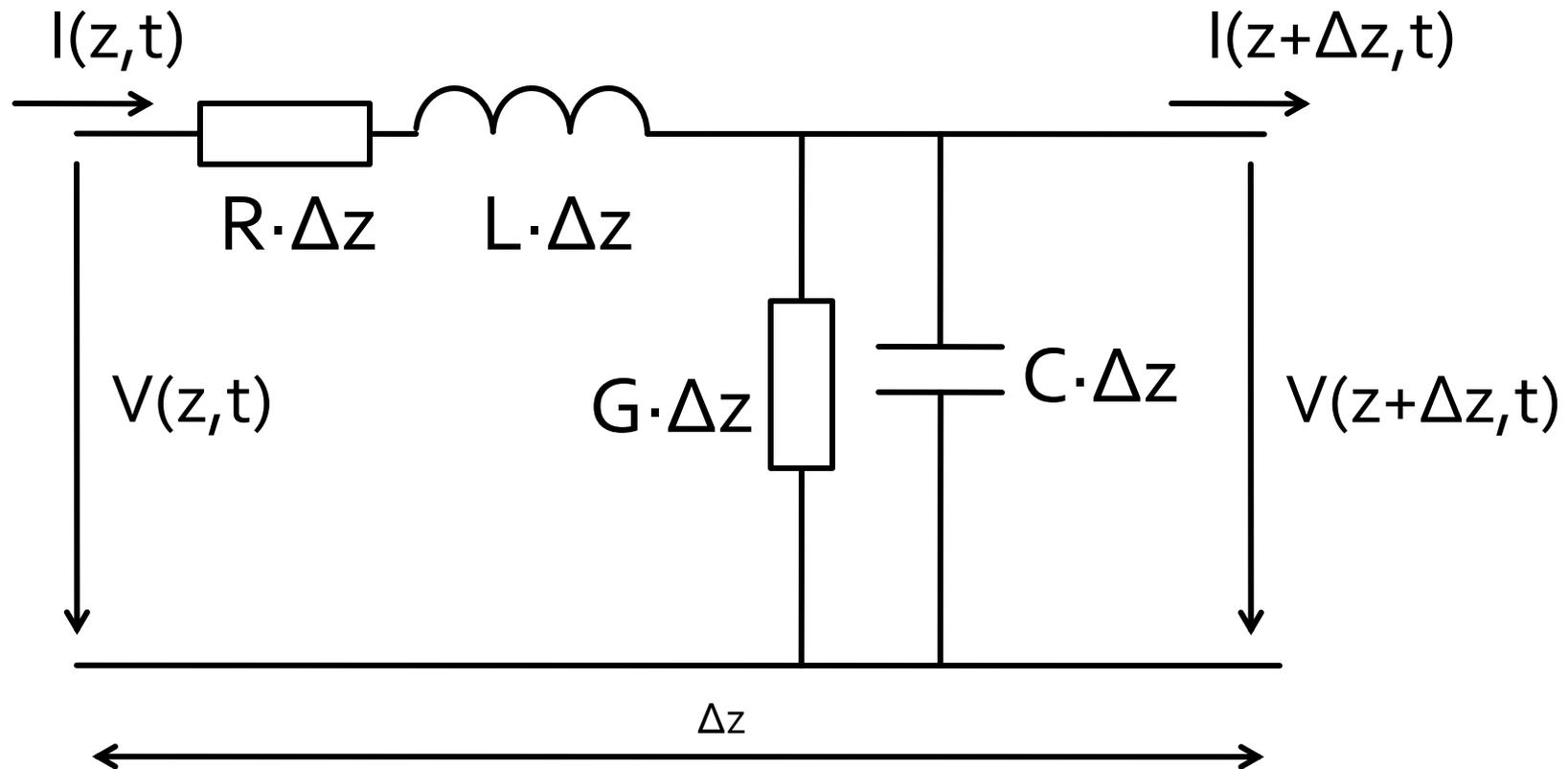
# Transmission line equivalent model

- TEM wave propagation, at least two conductors



- **distributed** (line) parameters  $R$ ,  $L$ ,  $G$ ,  $C$  (eg.  $\Omega/\text{m}$ )

# Telegrapher's equations

- time domain

$$\frac{\partial v(z,t)}{\partial z} = -R \cdot i(z,t) - L \cdot \frac{\partial i(z,t)}{\partial t} \quad \text{K II}$$

$$\frac{\partial i(z,t)}{\partial z} = -G \cdot v(z,t) - C \cdot \frac{\partial v(z,t)}{\partial t} \quad \text{K I}$$

- armonic signals (frequency domain)

$$\frac{dV(z)}{dz} = -(R + j \cdot \omega \cdot L) \cdot I(z)$$
$$\frac{dI(z)}{dz} = -(G + j \cdot \omega \cdot C) \cdot V(z)$$

$\left/ \frac{d}{dz} (\dots) \right.$

# Solving T's E

$$\frac{d^2 V(z)}{dz^2} - \gamma^2 \cdot V(z) = 0$$

$$\frac{d^2 I(z)}{dz^2} - \gamma^2 \cdot I(z) = 0$$

$$\gamma = \alpha + j \cdot \beta = \sqrt{(R + j \cdot \omega \cdot L) \cdot (G + j \cdot \omega \cdot C)}$$


$$\nabla^2 E - \gamma^2 E = 0$$

$$\nabla^2 H - \gamma^2 H = 0$$

$$E_y = E_+ e^{-\gamma \cdot z} + E_- e^{\gamma \cdot z}$$

$$\gamma^2 = -\omega^2 \epsilon \mu + j \omega \mu \sigma$$

# Solutions

$$\left\{ \begin{array}{l} V(z) = V_0^+ e^{-\gamma \cdot z} + V_0^- e^{\gamma \cdot z} \\ I(z) = I_0^+ e^{-\gamma \cdot z} + I_0^- e^{\gamma \cdot z} \end{array} \right. \quad \gamma = \alpha + j \cdot \beta = \sqrt{(R + j \cdot \omega \cdot L) \cdot (G + j \cdot \omega \cdot C)}$$

$$V(z) = V_0^+ e^{-\gamma \cdot z} + V_0^- e^{\gamma \cdot z}$$

$$\frac{dV(z)}{dz} = -(R + j \cdot \omega \cdot L) \cdot I(z)$$

$$Z_0 \equiv \frac{R + j \cdot \omega \cdot L}{\gamma} = \sqrt{\frac{R + j \cdot \omega \cdot L}{G + j \cdot \omega \cdot C}}$$

$$I(z) = \frac{\gamma}{R + j \cdot \omega \cdot L} (V_0^+ e^{-\gamma \cdot z} - V_0^- e^{\gamma \cdot z})$$

- Characteristic impedance of the line

$$\frac{V_0^+}{I_0^+} = Z_0 = -\frac{V_0^-}{I_0^-}$$

$$\lambda = \frac{2\pi}{\beta} \quad v_f = \frac{\omega}{\beta} = \lambda \cdot f$$

# The lossless line

- **Lossless:**  $R=G=0$

$$\gamma = \alpha + j \cdot \beta = \sqrt{(R + j \cdot \omega \cdot L) \cdot (G + j \cdot \omega \cdot C)} = j \cdot \omega \cdot \sqrt{L \cdot C}$$

$$\alpha = 0 \quad ; \quad \beta = \omega \cdot \sqrt{L \cdot C}$$

$$Z_0 = \sqrt{\frac{R + j \cdot \omega \cdot L}{G + j \cdot \omega \cdot C}} = \sqrt{\frac{L}{C}}$$

- $Z_0$  is **real**


$$V(z) = V_0^+ e^{-j \cdot \beta \cdot z} + V_0^- e^{j \cdot \beta \cdot z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j \cdot \beta \cdot z} - \frac{V_0^-}{Z_0} e^{j \cdot \beta \cdot z}$$

$$\lambda = \frac{2\pi}{\omega \cdot \sqrt{LC}}$$

$$v_f = \frac{1}{\sqrt{LC}}$$

# The lossless line

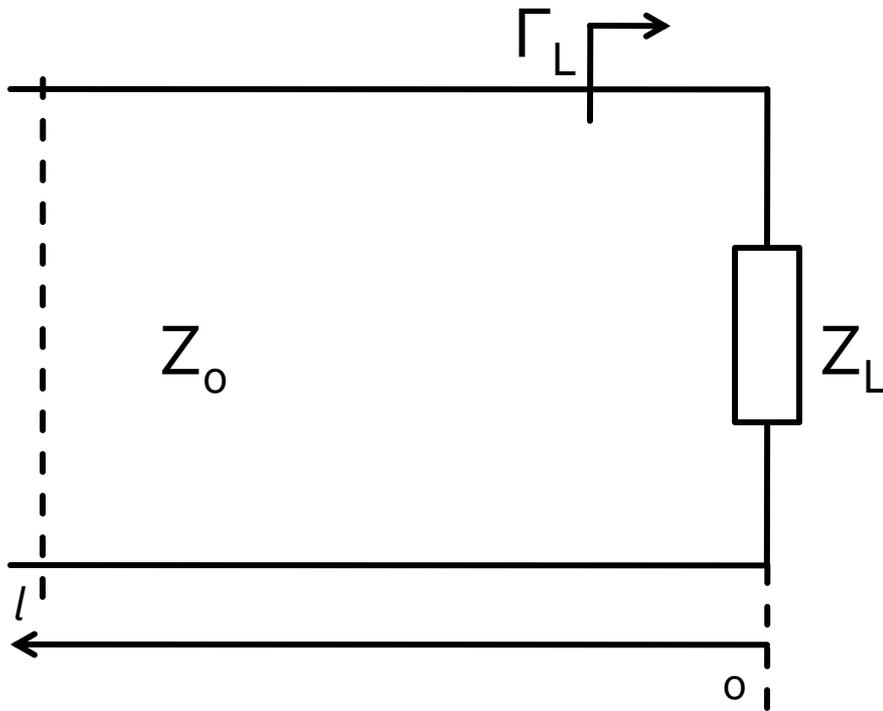

$$V(z) = V_0^+ e^{-j\beta \cdot z} + V_0^- e^{j\beta \cdot z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta \cdot z} - \frac{V_0^-}{Z_0} e^{j\beta \cdot z}$$

$$Z_L = \frac{V(0)}{I(0)} \quad Z_L = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \cdot Z_0$$

- voltage reflection coefficient

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

- $Z_0$  real

# The lossless line

- voltage reflection coefficient seen at the input of the line

$$V(z) = V_0^+ e^{-j\beta \cdot z} + V_0^- e^{j\beta \cdot z}$$

$$\Gamma = \Gamma(z) = \frac{V_0^-(z)}{V_0^+(z)}$$

$$V(0) = V_0^+ + V_0^- \quad \Gamma(0) = \Gamma_L = \frac{V_0^-}{V_0^+}$$


$$V(-l) = V_0^+ e^{j\beta \cdot l} + V_0^- e^{-j\beta \cdot l}$$

$$\Gamma(-l) = \Gamma_{IN} = \frac{V_0^- \cdot e^{-j\beta \cdot l}}{V_0^+ \cdot e^{j\beta \cdot l}} = \Gamma(0) \cdot e^{-2j\beta \cdot l}$$

$$|\Gamma(-l)| = |\Gamma(0)| \cdot |e^{-2j\beta \cdot l}| = |\Gamma(0)|$$

$$\Gamma_{IN} = \Gamma_L \cdot e^{-2j\beta \cdot l}$$

$$|\Gamma_{IN}| = |\Gamma_L|$$

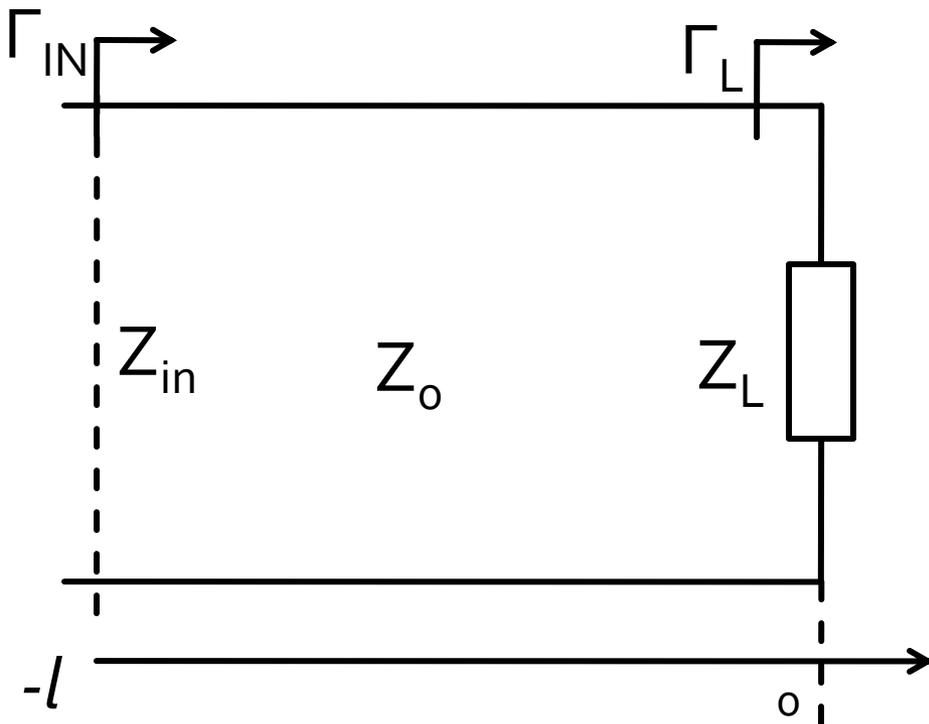

# The lossless line

$$V(z) = V_0^+ \cdot (e^{-j\beta \cdot z} + \Gamma \cdot e^{j\beta \cdot z})$$

$$I(z) = \frac{V_0^+}{Z_0} \cdot (e^{-j\beta \cdot z} - \Gamma \cdot e^{j\beta \cdot z})$$

- time-average Power flow along the line

$$P_{avg} = \frac{1}{2} \cdot \text{Re}\{V(z) \cdot I(z)^*\} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot \text{Re}\{1 - \Gamma^* \cdot e^{-2j\beta \cdot z} + \Gamma \cdot e^{2j\beta \cdot z} - |\Gamma|^2\}$$

$$P_{avg} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot (1 - |\Gamma|^2)$$

$$(z - z^*) = \text{Im}$$

- Total power delivered to the load = Incident power – “Reflected” power
- Return “Loss” [dB]  $\text{RL} = -20 \cdot \log|\Gamma|$  [dB]

# The lossless line

$$P_{avg} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot (1 - |\Gamma|^2)$$

- Average power flow is constant along the line
  - ( **no**  $P_{avg}(\mathbf{z})$  )
  - can be measured
- We can use the power to characterize the amplitude of a signal
  - a very “energetic” (basic physics) point of view
  - more power = “more” signal

# Polar representation

## ■ Euler's formula

$$e^{j \cdot x} = \cos x + j \cdot \sin x; \forall x \in R$$

## ■ Polar representation

$$z = a + j \cdot b = |z| \cdot e^{j \cdot \varphi}$$


$$z = a + j \cdot b = |z| \cdot (\cos \varphi + j \cdot \sin \varphi)$$

$$z^n = (|z| \cdot e^{j \cdot \varphi})^n = |z|^n \cdot e^{j \cdot n \cdot \varphi} = |z|^n \cdot [\cos(n \cdot \varphi) + j \cdot \sin(n \cdot \varphi)]$$

$$\sqrt{z} = (|z| \cdot e^{j \cdot \varphi})^{1/2} = \sqrt{|z|} \cdot e^{j \cdot \frac{\varphi}{2}} = \sqrt{|z|} \cdot \left( \cos \frac{\varphi}{2} + j \cdot \sin \frac{\varphi}{2} \right)$$

$$z \cdot w = |z| \cdot e^{j \cdot \varphi} \cdot |w| \cdot e^{j \cdot \theta} = |z| \cdot |w| \cdot e^{j \cdot (\varphi + \theta)} = |z| \cdot |w| \cdot [\cos(\varphi + \theta) + j \cdot \sin(\varphi + \theta)]$$

$$z/w = \frac{|z| \cdot e^{j \cdot \varphi}}{|w| \cdot e^{j \cdot \theta}} = \frac{|z|}{|w|} \cdot e^{j \cdot \varphi} \cdot e^{-j \cdot \theta} = \frac{|z|}{|w|} \cdot [\cos(\varphi - \theta) + j \cdot \sin(\varphi - \theta)]$$

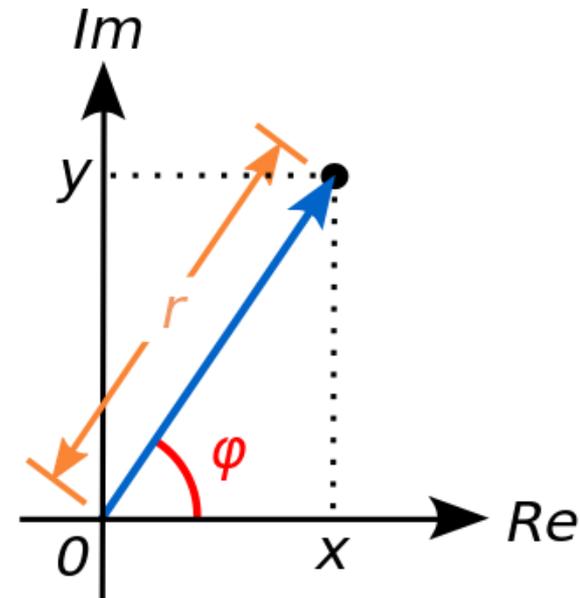

# Polar representation

- Euler's formula

$$e^{j \cdot x} = \cos x + j \cdot \sin x; \forall x \in R$$

$$e^{j \cdot x} + e^{-j \cdot x} = \cos x + j \cdot \sin x + \cos(-x) + j \cdot \sin(-x)$$

$$e^{j \cdot x} + e^{-j \cdot x} = \cos x + j \cdot \sin x + \cos x - j \cdot \sin x = 2 \cdot \cos x$$

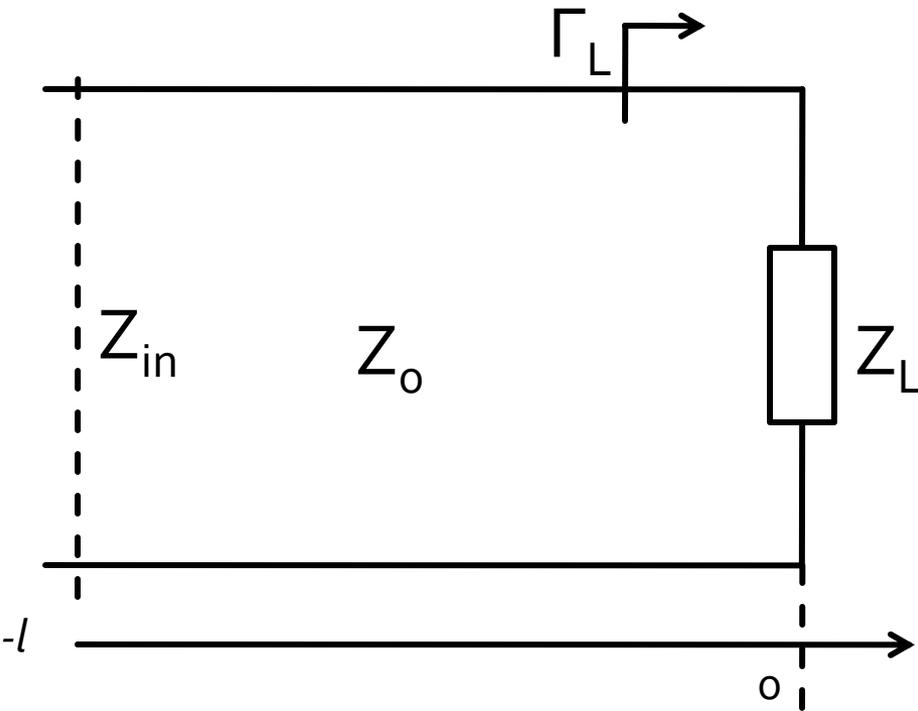

$$\cos x = \frac{e^{j \cdot x} + e^{-j \cdot x}}{2}$$

$$e^{j \cdot x} - e^{-j \cdot x} = \cos x + j \cdot \sin x - \cos(-x) - j \cdot \sin(-x)$$

$$e^{j \cdot x} - e^{-j \cdot x} = \cos x + j \cdot \sin x - \cos x + j \cdot \sin x = 2j \cdot \sin x$$


$$\sin x = \frac{e^{j \cdot x} - e^{-j \cdot x}}{2j}$$

# The lossless line



$$V(-l) = V_0^+ e^{j\beta \cdot l} + V_0^- e^{-j\beta \cdot l}$$

$$I(-l) = \frac{V_0^+}{Z_0} e^{j\beta \cdot l} - \frac{V_0^-}{Z_0} e^{-j\beta \cdot l}$$

$$Z_{in} = \frac{V(-l)}{I(-l)} \quad Z_{in} = Z_0 \cdot \frac{1 + \Gamma \cdot e^{-2j\beta \cdot l}}{1 - \Gamma \cdot e^{-2j\beta \cdot l}}$$

- the **input impedance** seen looking toward the load

$$Z_{in} = Z_0 \cdot \frac{(Z_L + Z_0) \cdot e^{j\beta \cdot l} + (Z_L - Z_0) \cdot e^{-j\beta \cdot l}}{(Z_L + Z_0) \cdot e^{j\beta \cdot l} - (Z_L - Z_0) \cdot e^{-j\beta \cdot l}}$$

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan(\beta \cdot l)}{Z_0 + j \cdot Z_L \cdot \tan(\beta \cdot l)}$$


# The lossless line

- the **input impedance** seen looking toward the load

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$
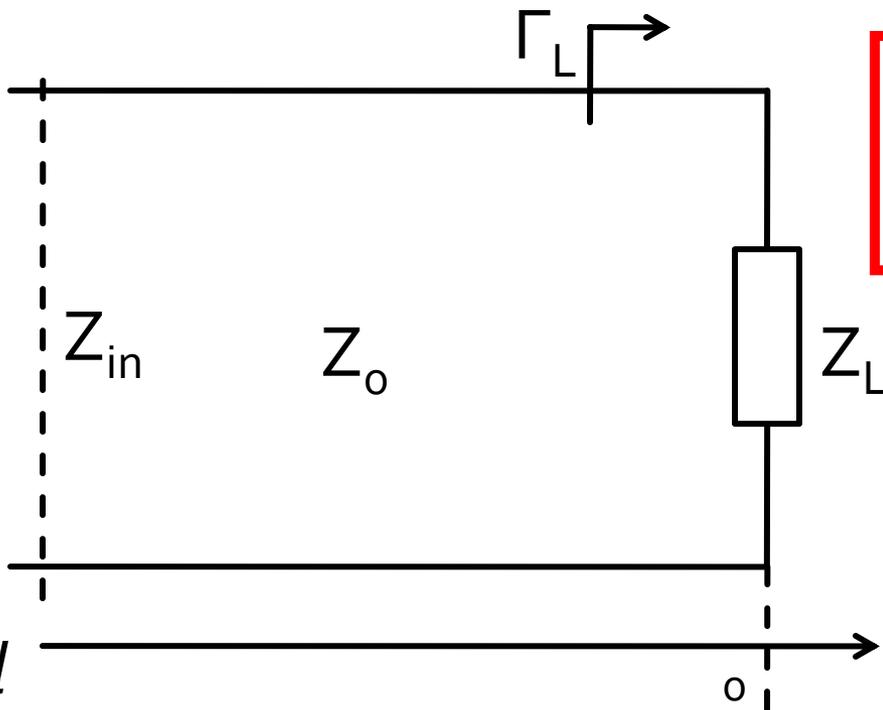
# The lossless line


- input impedance of a length  $l$  of transmission line with characteristic impedance  $Z_0$ , loaded with an arbitrary impedance  $Z_L$



$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$
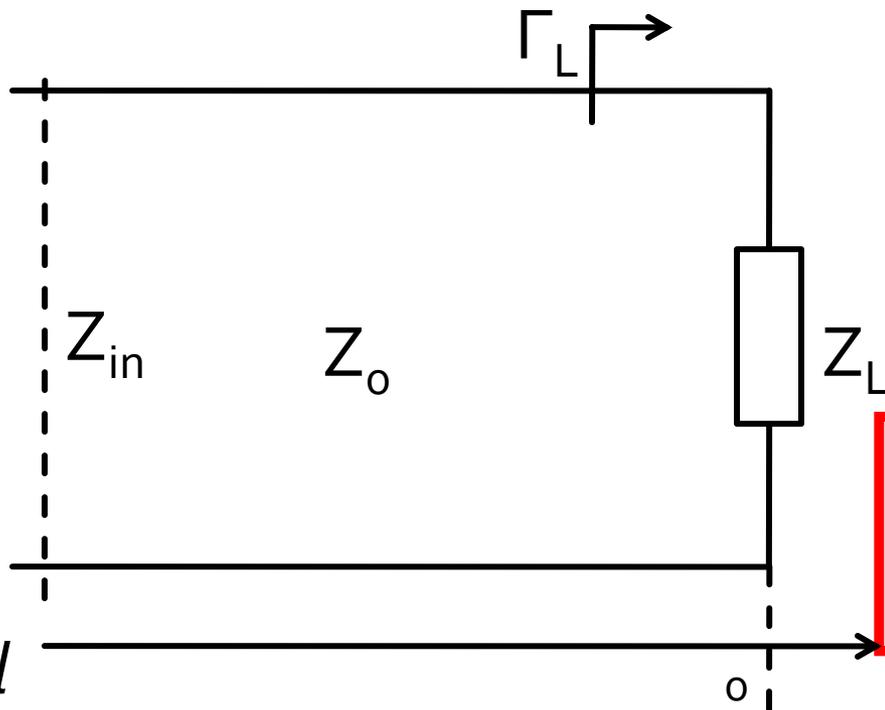
# The lossless line

- input impedance is **frequency dependent** through  $\beta \cdot l$



$$v_f = \frac{\omega}{\beta} = \lambda \cdot f \quad \lambda = \frac{2\pi}{\beta}$$

$$\beta \cdot l = \frac{2\pi}{\lambda} \cdot l = \frac{2\pi \cdot f}{v_f} \cdot l = \frac{2\pi \cdot l}{v_f} \cdot f$$

frequency dependence is **periodical**, imposed by the tan trigonometric function

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$


# The lossless line, special cases

- $l = k \cdot \lambda / 2$ 
 $\beta \cdot l = \frac{2\pi}{\lambda} \cdot l = k \cdot \pi$ 
 $\tan \beta \cdot l = 0$

$$Z_{in} = Z_L$$

- $l = \lambda / 4 + k \cdot \lambda / 2$ 
 $\beta \cdot l = \frac{\pi}{2} + k \cdot \pi$ 
 $\tan \beta \cdot l \rightarrow \infty$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

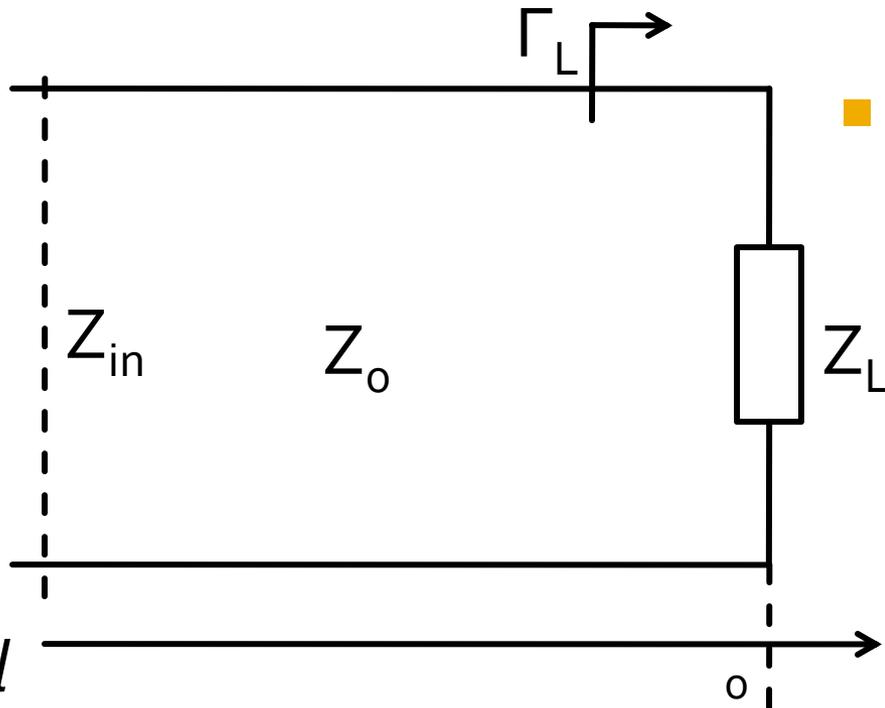

- quarter-wave transformer
  - $E = 90^\circ$




$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

# Short-circuited transmission line

- $Z_L = 0$
- input purely **imaginary** for any length  $l$ 
  - +/-  $\rightarrow$  depending on  $l$  value

$$Z_{in} = j \cdot Z_0 \cdot \tan \beta \cdot l$$
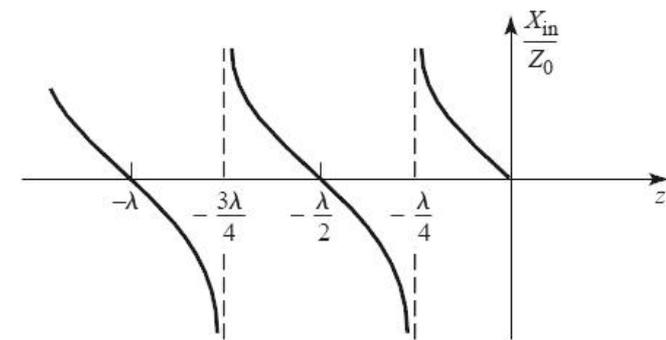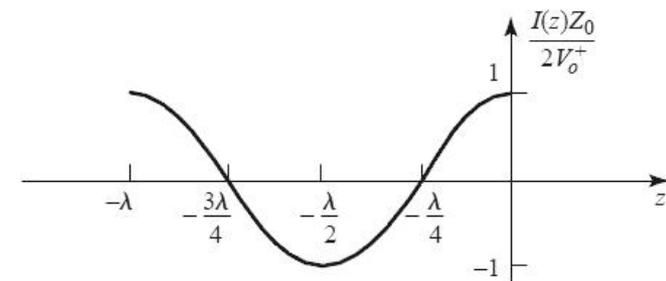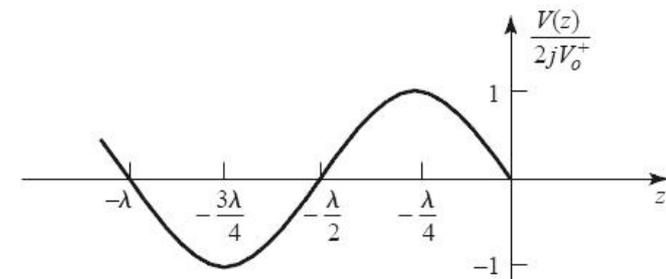
$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan(\beta \cdot l)}{Z_0 + j \cdot Z_L \cdot \tan(\beta \cdot l)}$$






# Open-circuited transmission line


- $Z_L = \infty \rightarrow 1/Z_L = 0$
- input purely **imaginary** for any length  $l$ 
  - +/-  $\rightarrow$  depending on  $l$  value

$$Z_{in} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$

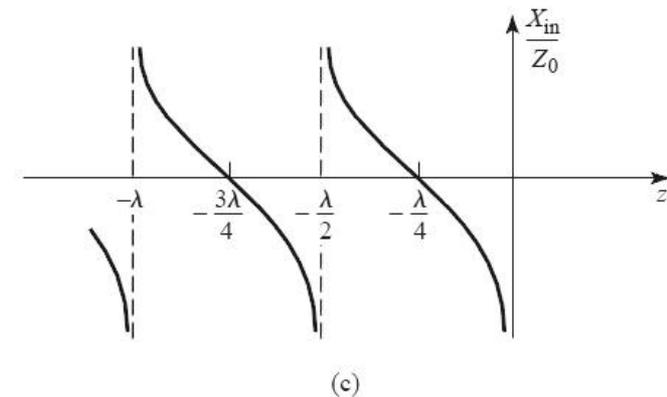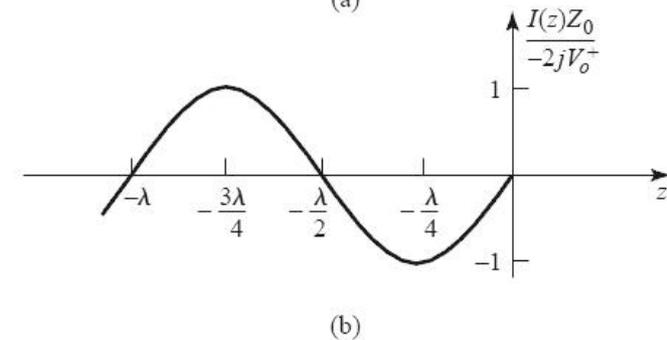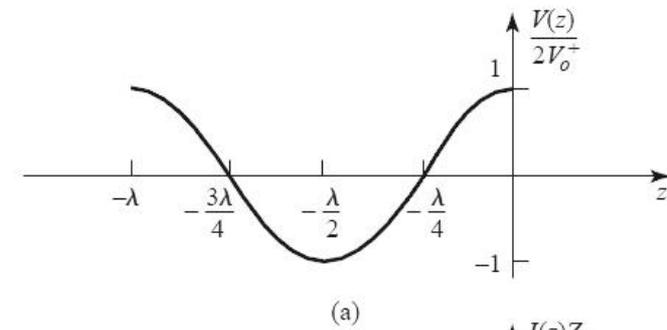
$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan(\beta \cdot l)}{Z_0 + j \cdot Z_L \cdot \tan(\beta \cdot l)}$$




# Examples

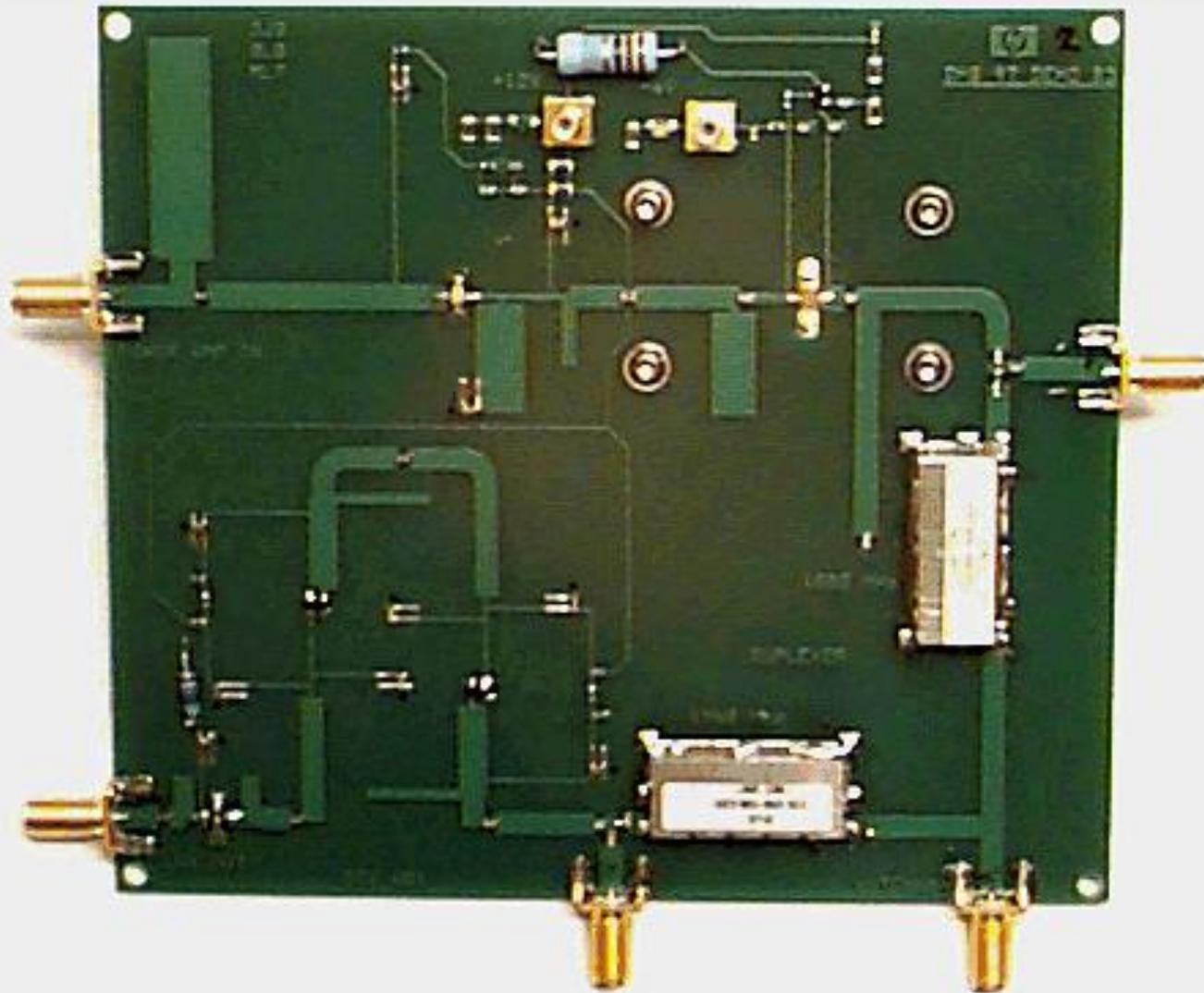

# Examples

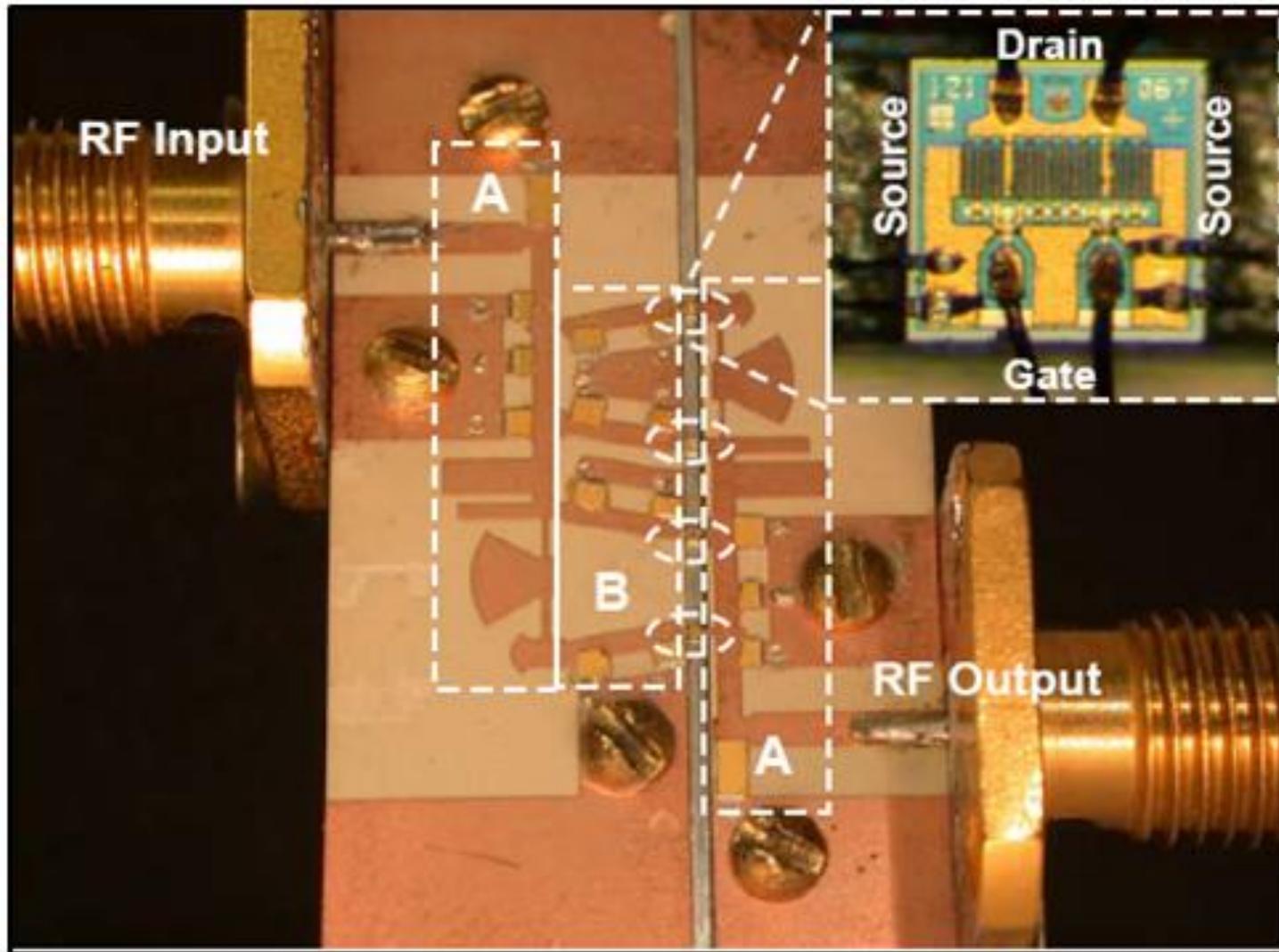


# Examples

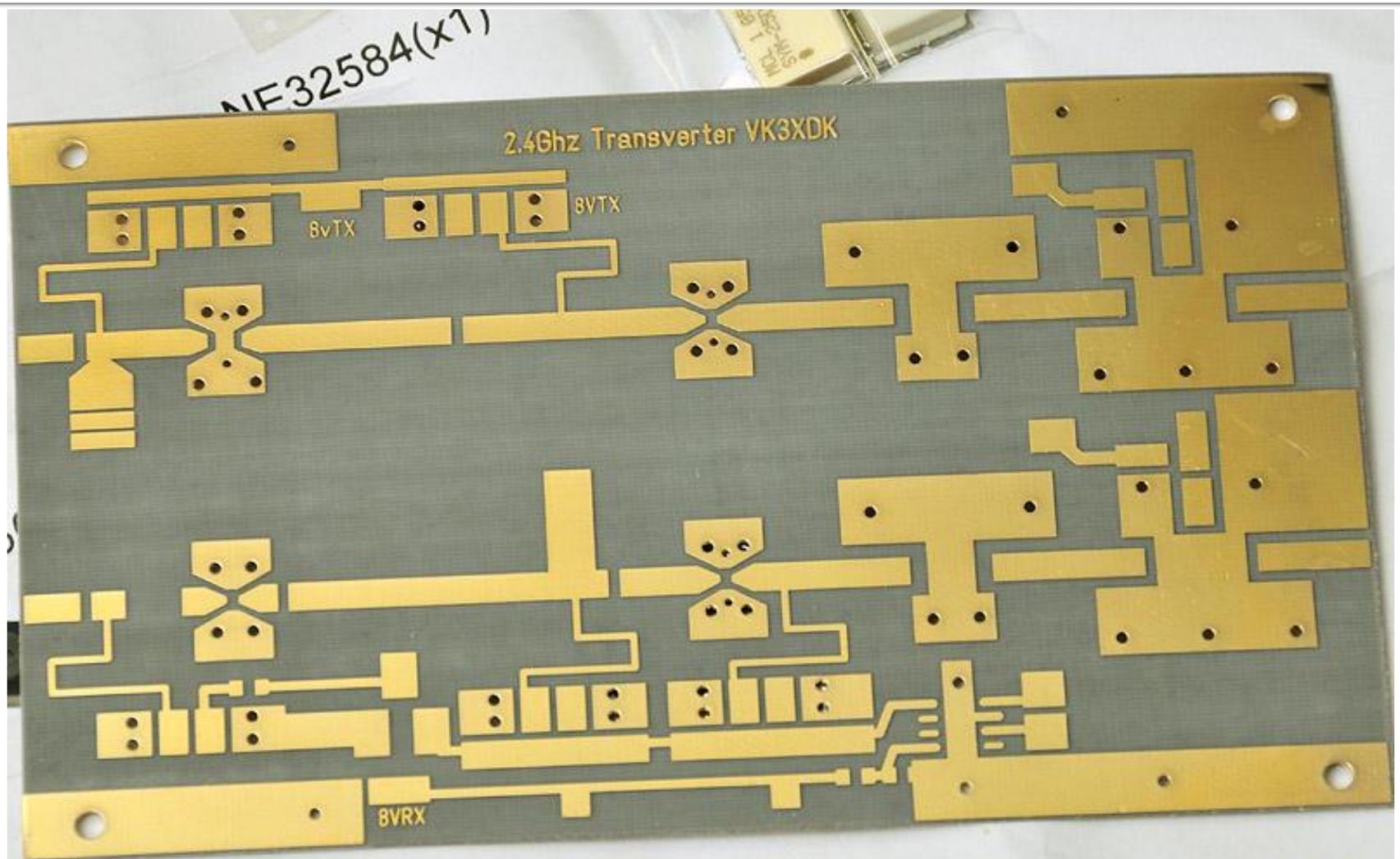


VK4CP

# Examples

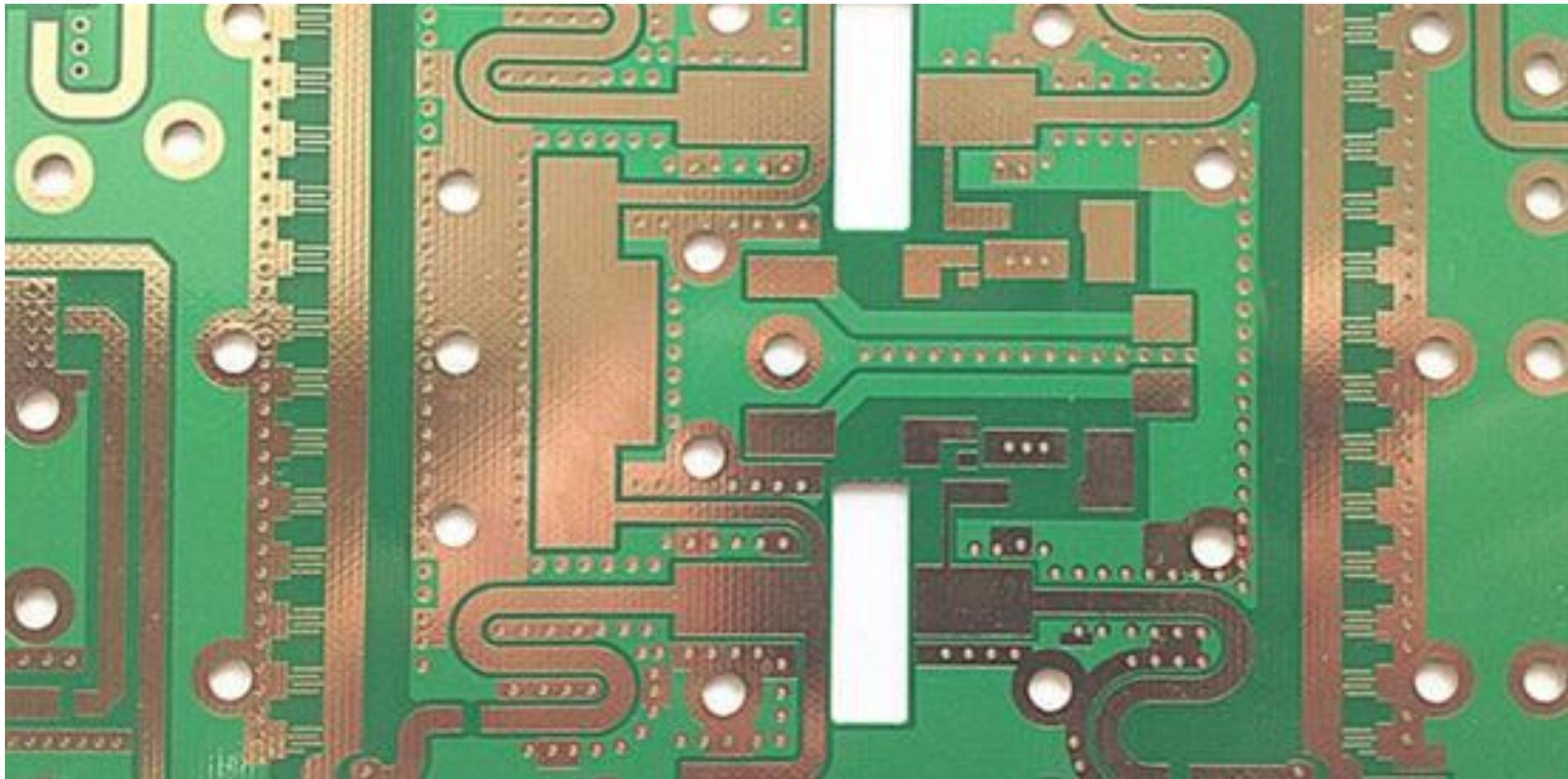

# Examples

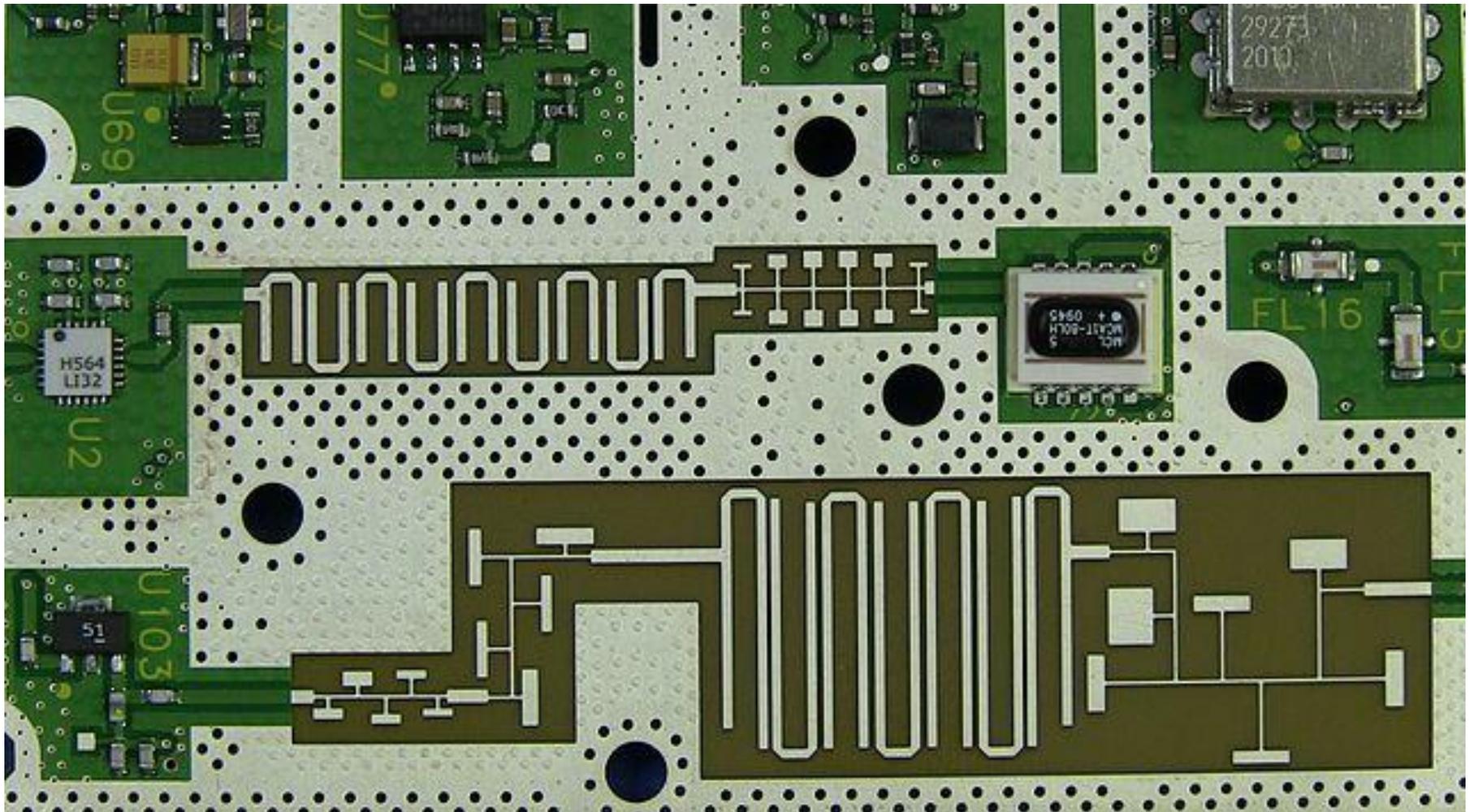

# Voltage standing wave ratio

$$V(z) = V_0^+ \cdot (e^{-j\beta \cdot z} + \Gamma \cdot e^{j\beta \cdot z}) \quad |V(z)| = |V_0^+| \cdot |e^{-j\beta \cdot z}| \cdot |1 + \Gamma \cdot e^{2j\beta \cdot z}| \quad \Gamma = |\Gamma| \cdot e^{j\theta}$$

$$|V(z)| = |V_0^+| \cdot |1 + |\Gamma| \cdot e^{\theta + 2j\beta \cdot z}|$$

maximum magnitude value for  $e^{\theta + 2j\beta \cdot z} = 1$

$$V_{\max} = |V_0^+| \cdot (1 + |\Gamma|)$$

minimum magnitude value for  $e^{\theta + 2j\beta \cdot z} = -1$

$$V_{\min} = |V_0^+| \cdot (1 - |\Gamma|)$$


- SWR is defined as the ratio between maximum and minimum

- (Voltage) Standing Wave Ratio

$$VSWR = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

- real number  $1 \leq VSWR < \infty$
- a measure of the mismatch (SWR = 1 means a matched line)

# The lossless line +/-

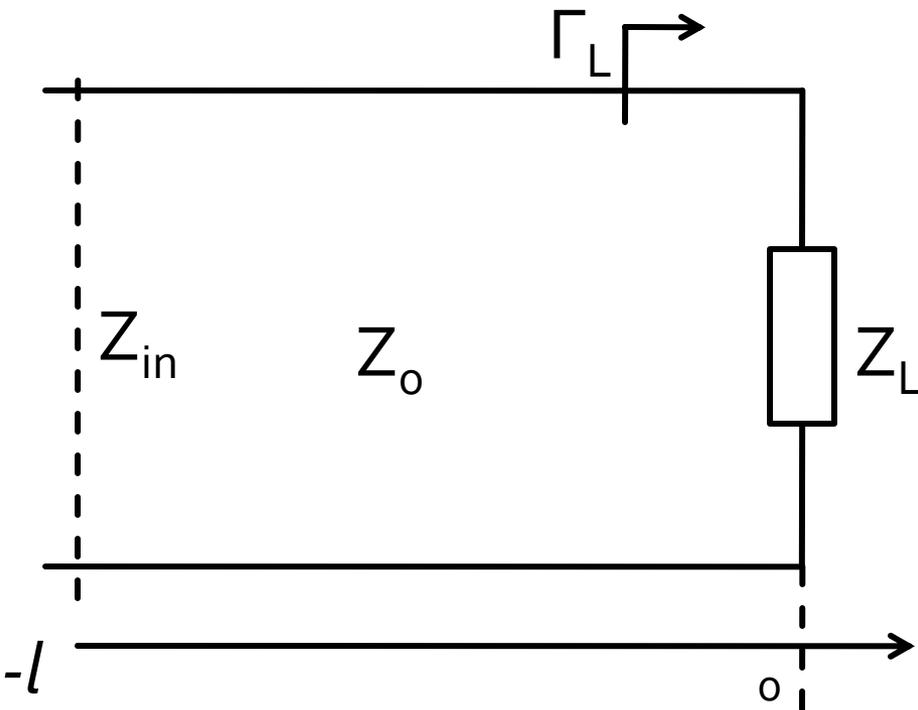

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

$$V(z) = V_0^+ e^{-\gamma \cdot z} + V_0^- e^{\gamma \cdot z}$$

$$I(z) = I_0^+ e^{-\gamma \cdot z} + I_0^- e^{\gamma \cdot z}$$

$$\Gamma(-l) = \Gamma(0) \cdot e^{-2j \cdot \beta \cdot l}$$

$$\Gamma_{in} = \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}$$

Power transfer


# Impedance Matching

# Course Topics

- Transmission lines
- **Impedance matching and tuning**
- Directional couplers
- Power dividers
- Microwave amplifier design
- Microwave filters
- ~~Oscillators and mixers?~~

# Matching


- Source matched to load ?

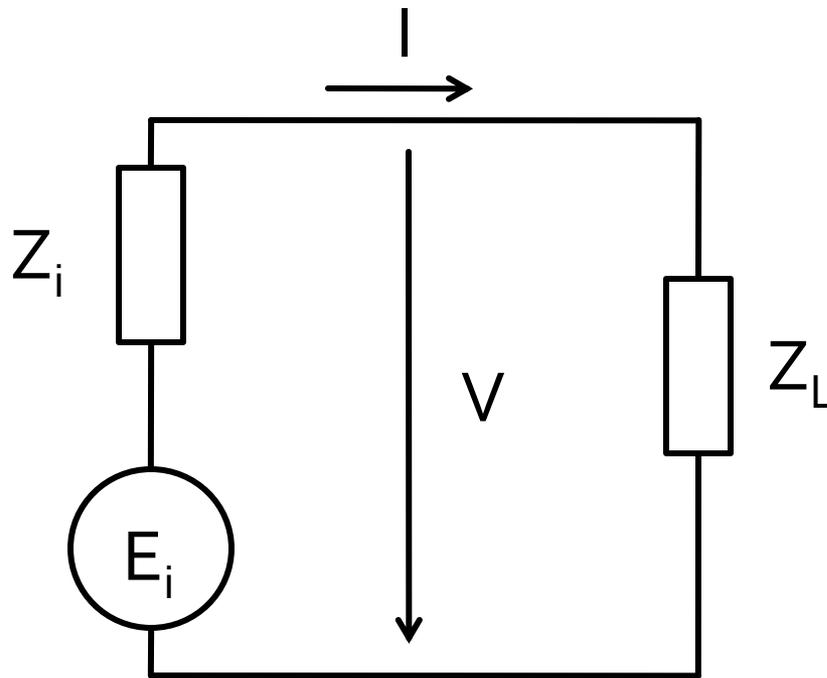

- impedance values ?
- existence of reflections ?

# Matching, real impedances

- Source matched to load

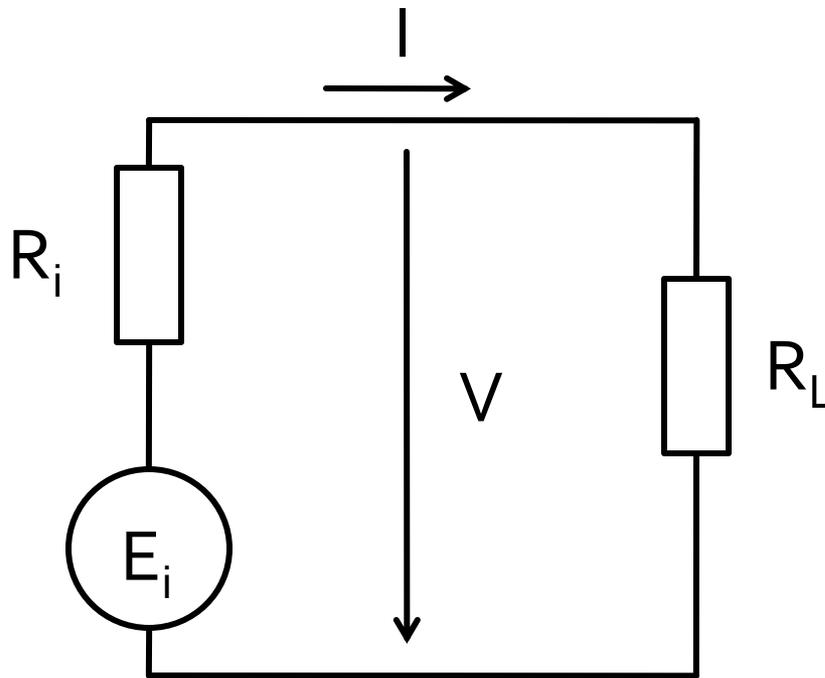

$$I = \frac{E_i}{R_i + R_L}$$

$$V = \frac{E_i \cdot R_L}{R_i + R_L}$$

$$P_L = R_L \cdot I^2$$


$$P_L = \frac{R_L \cdot E_i^2}{(R_i + R_L)^2}$$

# Matching, real impedances

$$P_L = R_L \cdot I^2 \quad P_L = \frac{R_L \cdot E_i^2}{(R_i + R_L)^2}$$


- Power dissipated on load
  - $R_i = 50\Omega$
  - $R_L = 0 \rightarrow P_L = 0$
  - $R_L = \infty \rightarrow P_L = 0$

# Matching, real impedances

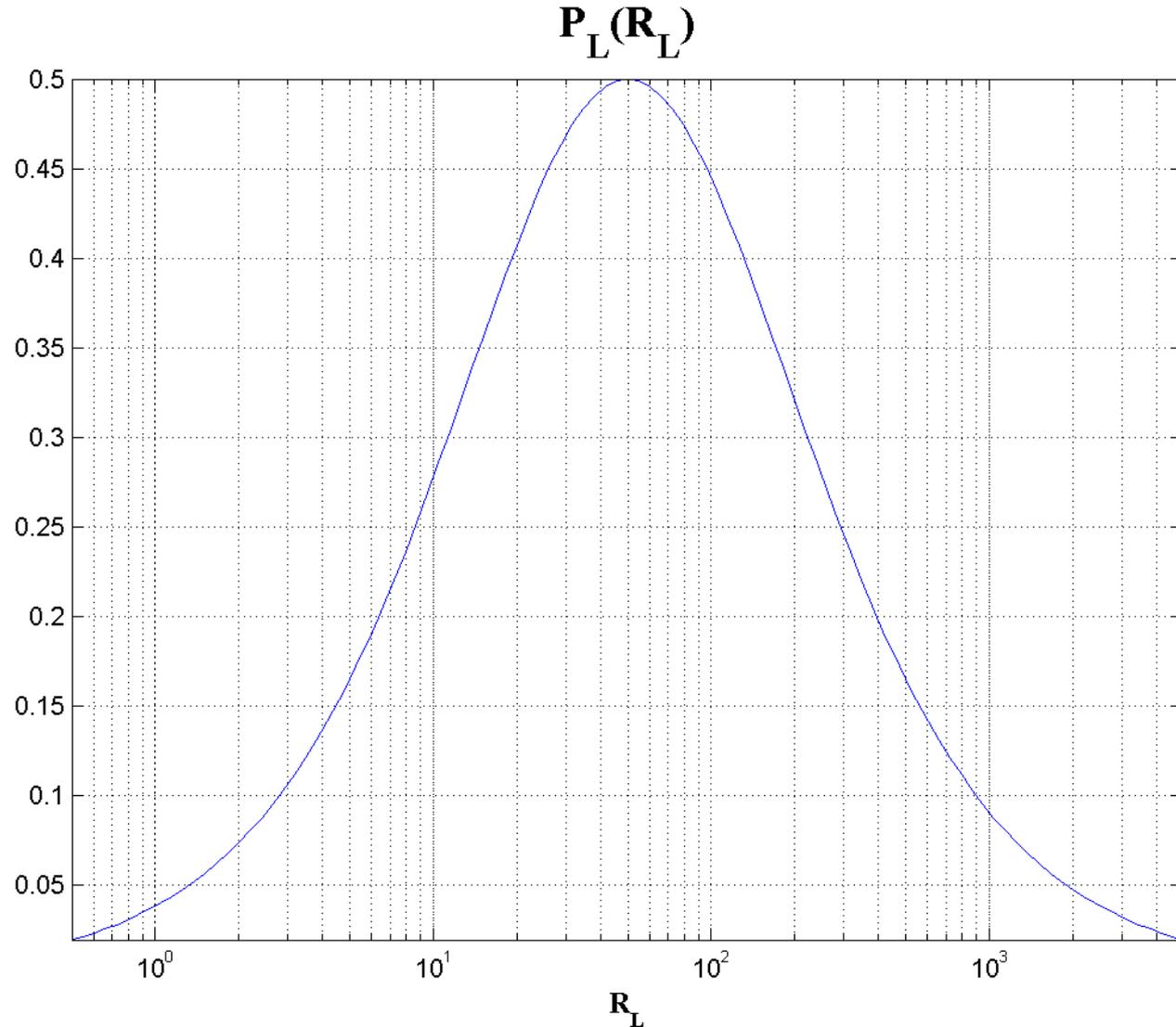

# Matching, complex impedances

- Source matched to load

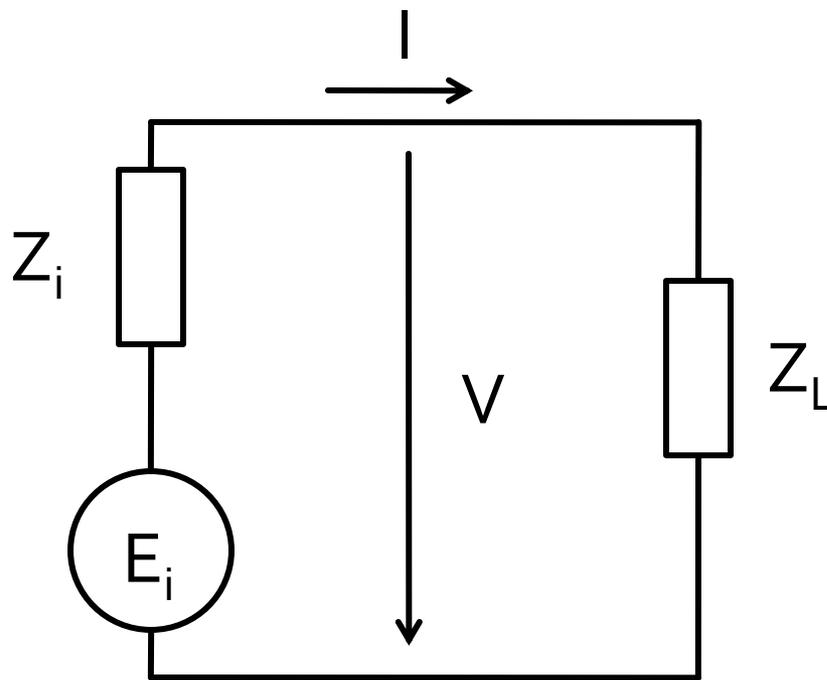

$$I = \frac{E_i}{Z_i + Z_L}$$

$$V = \frac{E_i \cdot Z_L}{Z_i + Z_L}$$

$$P_L = \operatorname{Re}\{Z_L \cdot |I|^2\}$$

$$P_L = \operatorname{Re}\{Z_L\} \cdot \left| \frac{E_i}{Z_i + Z_L} \right|^2$$

# Matching

$$P_L = \frac{R_L \cdot |E_i|^2}{|Z_i + Z_L|^2} = \frac{R_L \cdot |E_i|^2}{|(R_i + R_L) + j \cdot (X_i + X_L)|^2}$$

$$|a + j \cdot b| = \sqrt{a^2 + b^2}$$


$$P_L = \frac{R_L \cdot |E_i|^2}{(R_i + R_L)^2 + (X_i + X_L)^2}$$

- Matching
  - maximum power transmitted to the load
  - condition?


# Matching, example

- $E = 10\text{V}$
- $Z_i = 50\ \Omega + j\cdot 50\ \Omega$
- $P_L(Z_L)$  ?


$$P_L = \frac{R_L \cdot |E_i|^2}{(R_i + R_L)^2 + (X_i + X_L)^2}$$

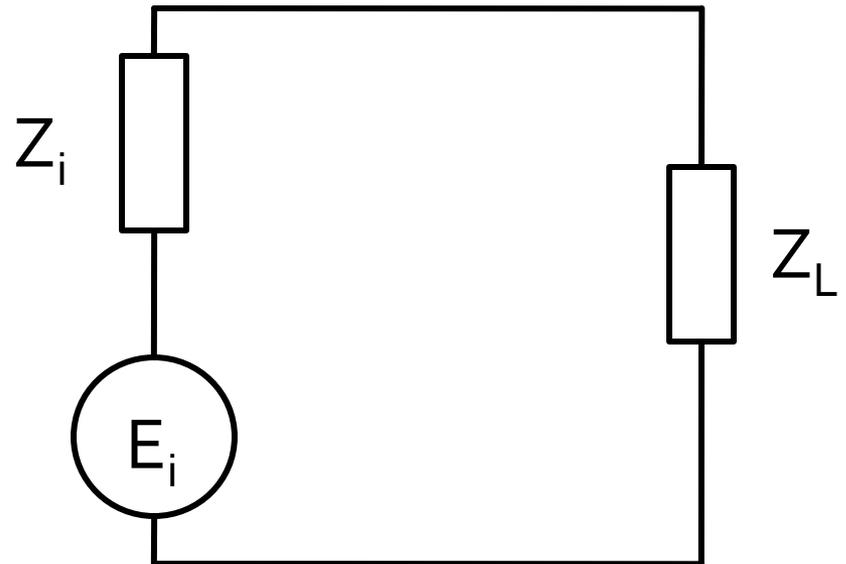

# Matching, example

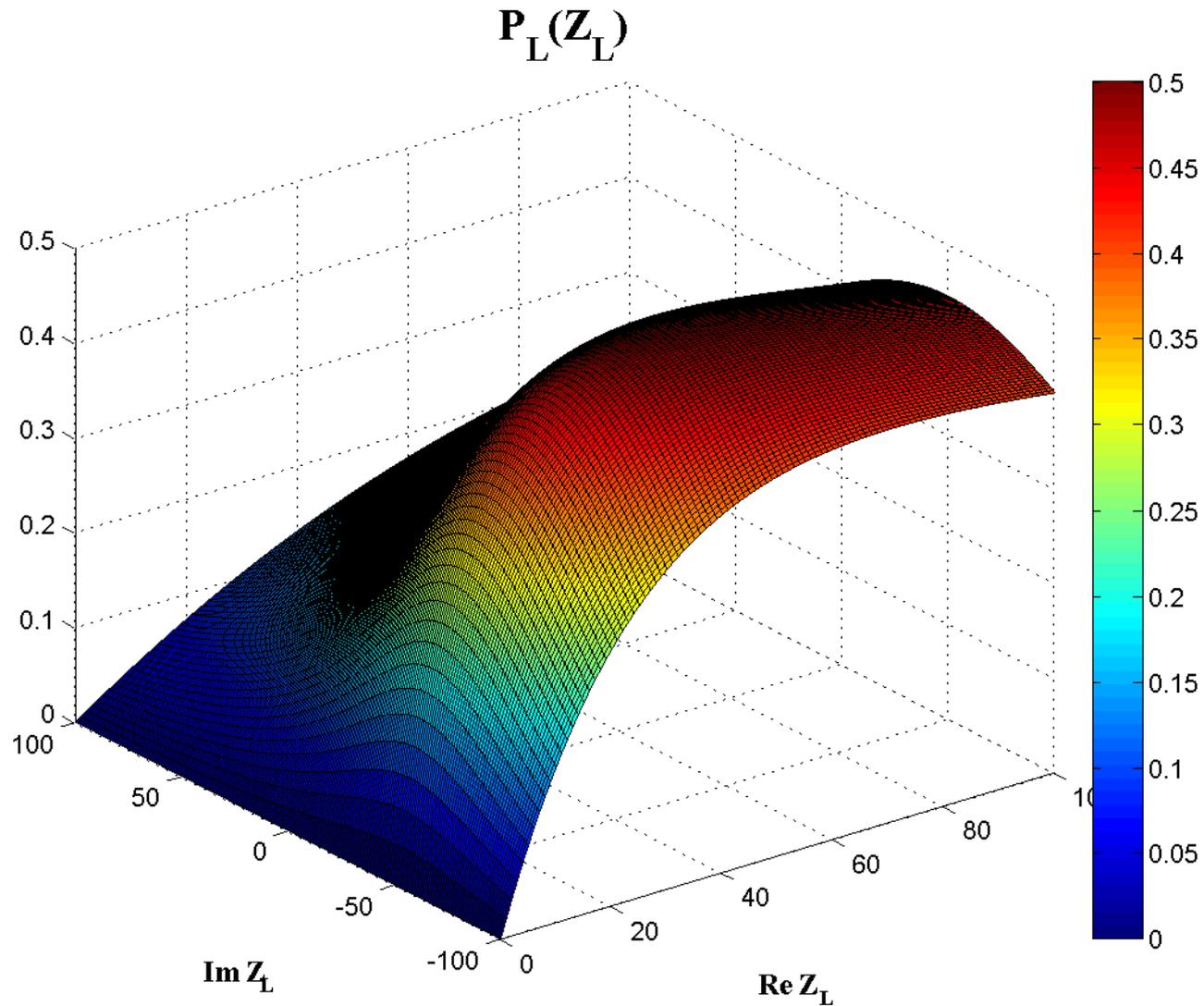

# Matching, example

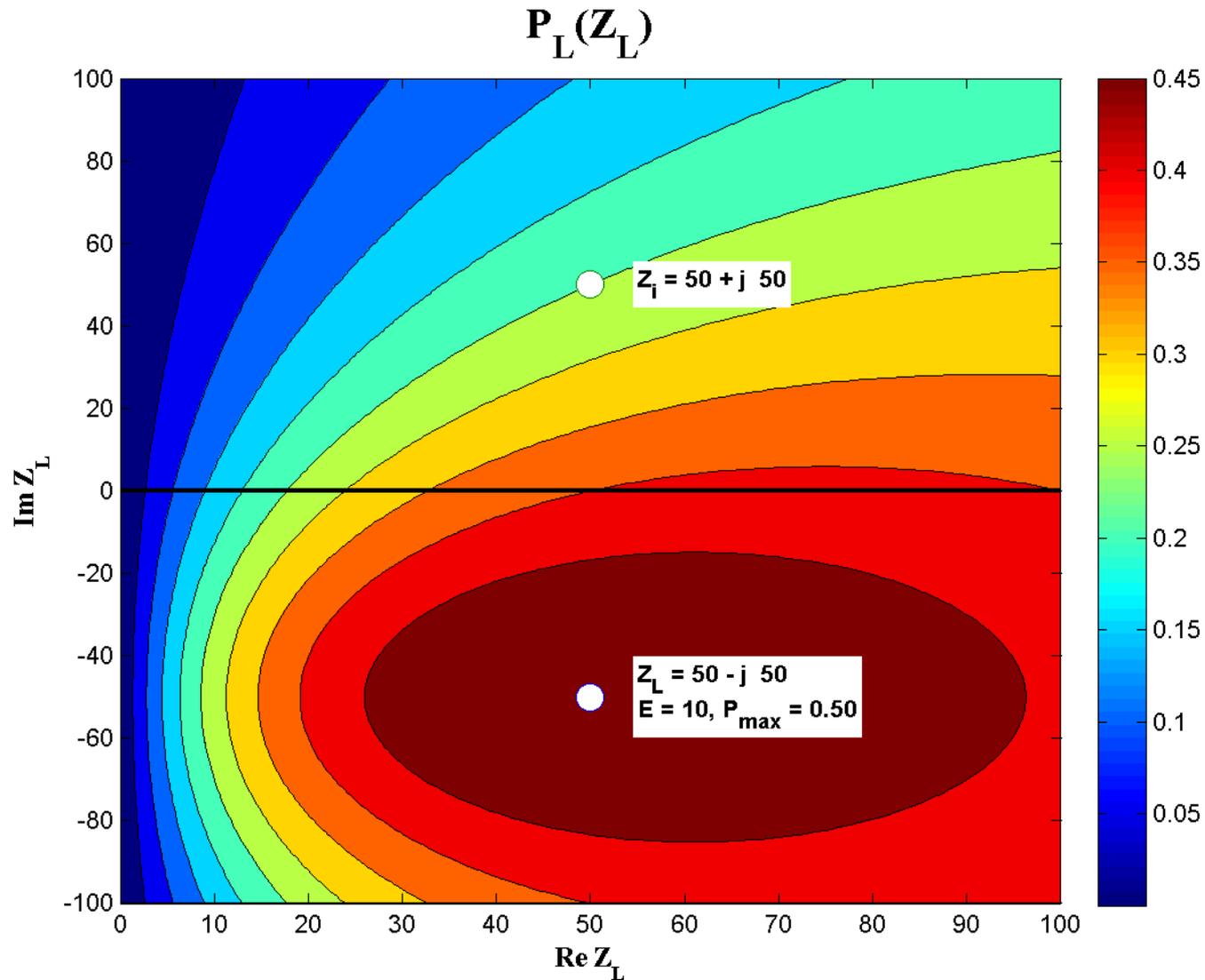

# Matching , from the point of view of power transmission

$$R_i > 0, R_L > 0 \quad P_L = \frac{|E_i|^2}{4R_i + \frac{(R_i - R_L)^2}{R_L} + \frac{(X_i + X_L)^2}{R_L}}$$


$$P_{L\max} = \frac{|E_i|^2}{4R_i} \equiv P_a \quad R_L = R_i, X_L = -X_i$$

- $P_{L\max} = P_a$  : Available Power


$$Z_L = Z_i^*$$
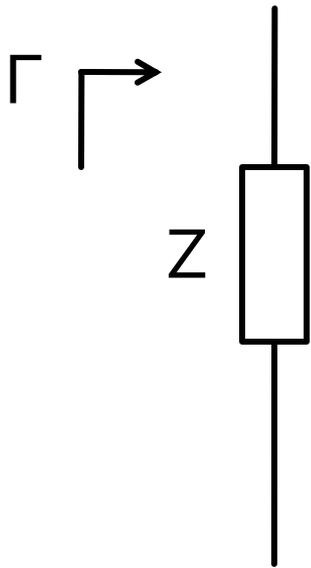
# Reflection coefficient


- Any impedance  $Z_0$  chosen as reference



$$\Gamma = \frac{Z - Z_0^*}{Z + Z_0}$$

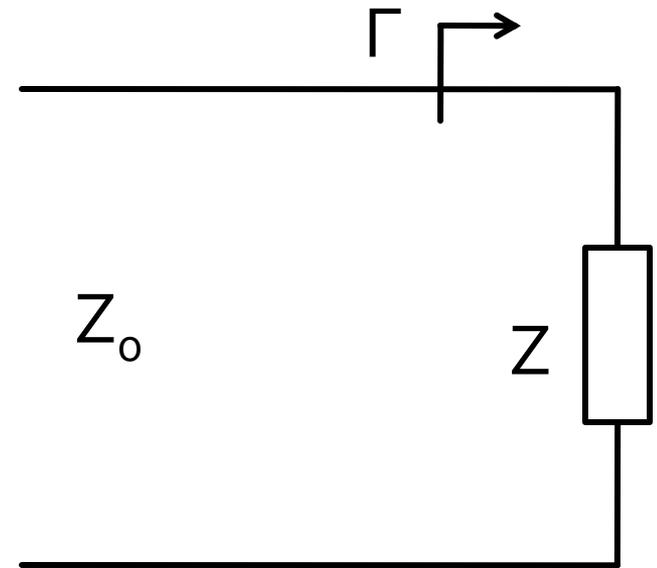
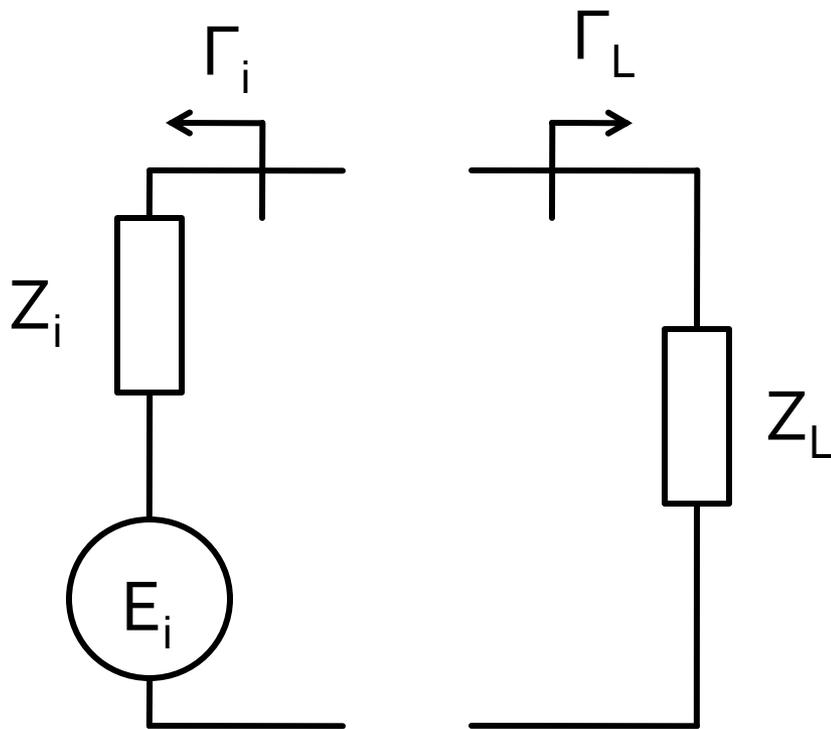
# Matching , from the point of view of power transmission




$$\Gamma_i = \frac{Z_i - Z_0^*}{Z_i + Z_0}$$

$$\Gamma_i = \frac{(R_i - R_0) + j \cdot (X_i + X_0)}{(R_i + R_0) + j \cdot (X_i + X_0)}$$

$$\Gamma_L = \frac{Z_L - Z_0^*}{Z_L + Z_0}$$

$$\Gamma_L = \frac{(R_L - R_0) + j \cdot (X_L + X_0)}{(R_L + R_0) + j \cdot (X_L + X_0)}$$
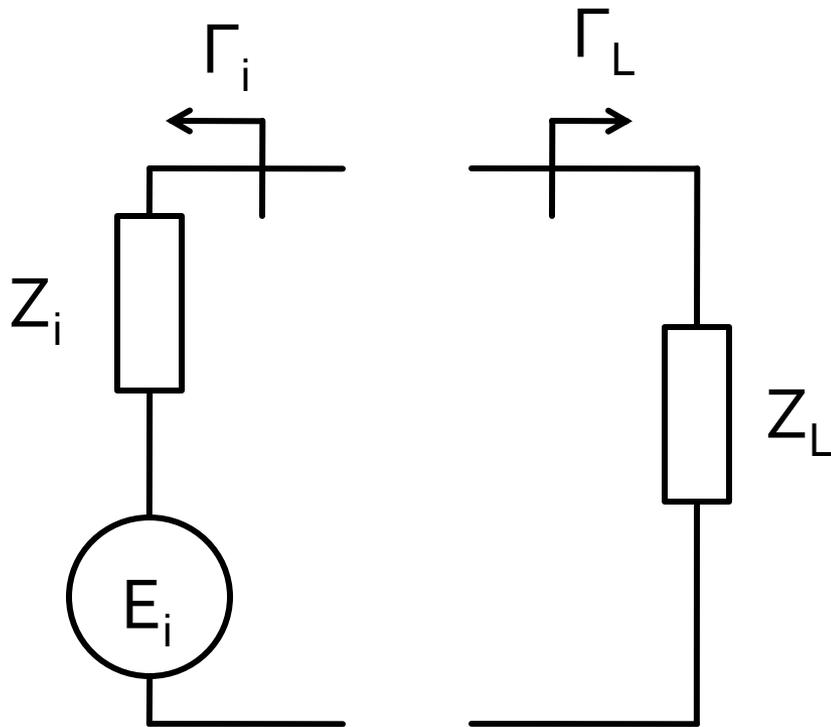
# Matching , from the point of view of power transmission



$$\Gamma_i = \frac{Z_i - Z_0^*}{Z_i + Z_0} = 1 - \frac{Z_0 + Z_0^*}{Z_i + Z_0}$$

$$\Gamma_L = \frac{Z_L - Z_0^*}{Z_L + Z_0} = 1 - \frac{Z_0 + Z_0^*}{Z_L + Z_0}$$

$$\Gamma_i^* = 1 - \frac{Z_0^* + Z_0}{Z_i^* + Z_0^*} = 1 - \frac{Z_0^* + Z_0}{Z_L + Z_0^*}$$

# Matching , from the point of view of power transmission


$$Z_L = Z_i^*$$

If we choose a (any) real  $Z_0$


$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

$$\Gamma_L = \Gamma_i^*$$

- complex numbers
- in the complex plane

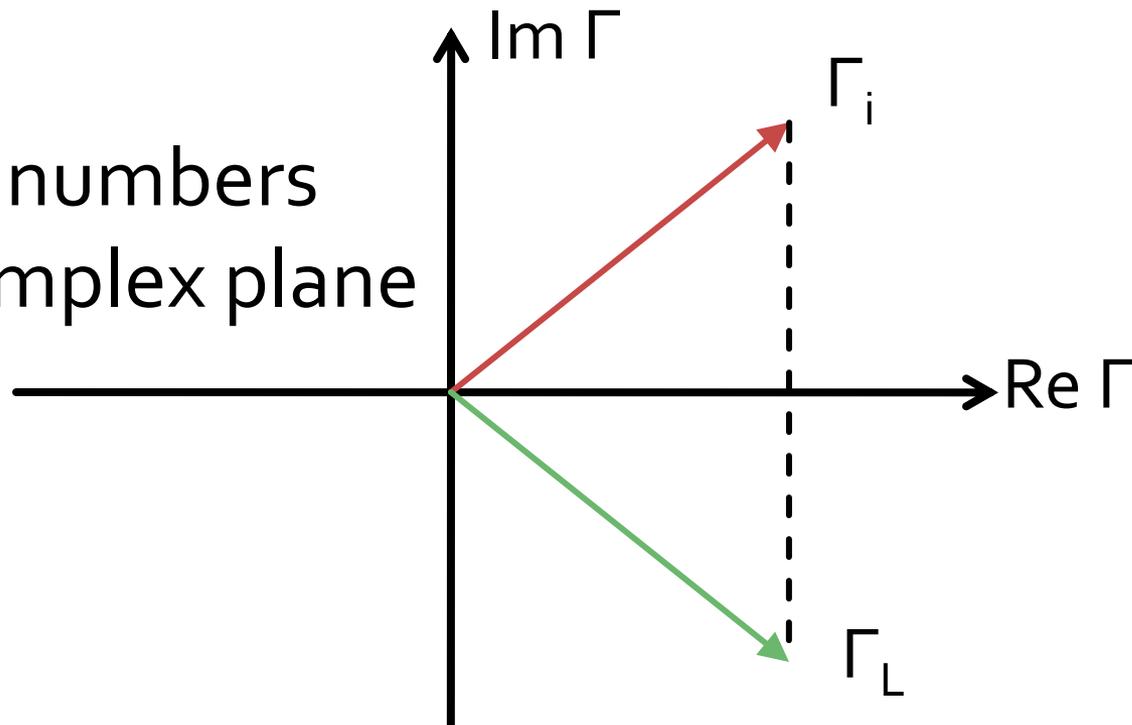


# Reflection and power / Model

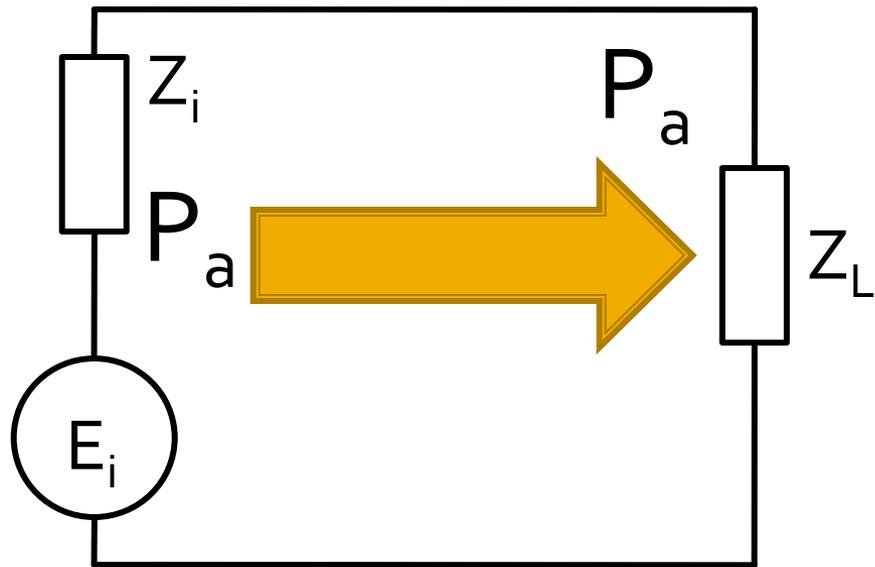

$$Z_L = Z_i^*$$


$$P_L = P_a$$

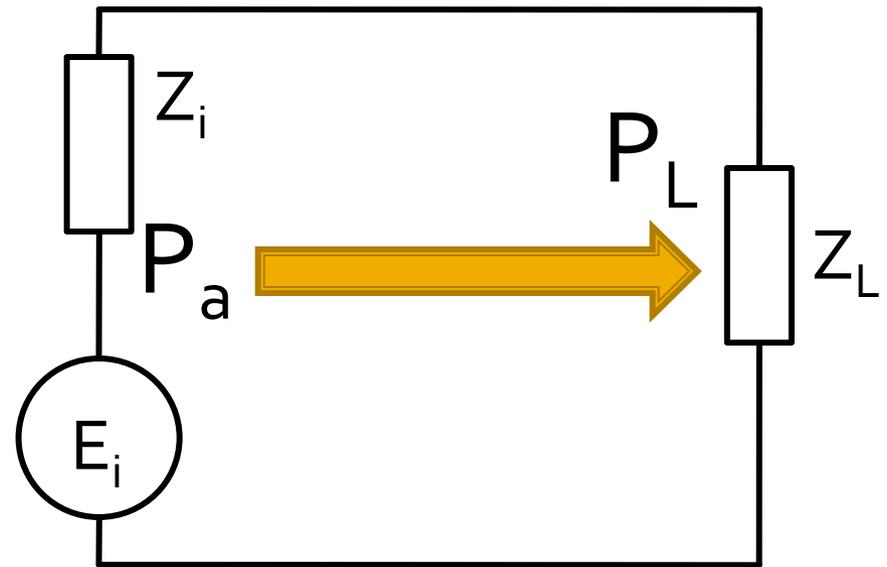

$$Z_L \neq Z_i^*$$


$$P_L < P_a$$

# Reflection and power / Model

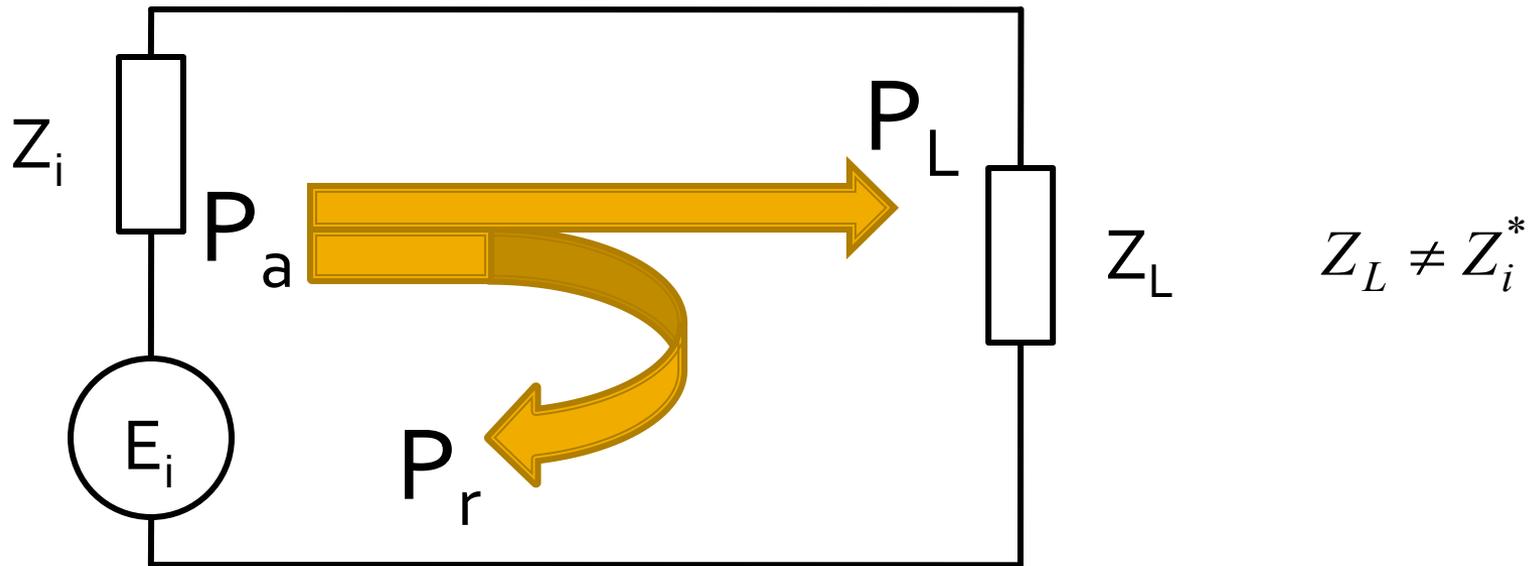

- ~~Power reflection~~
- Power of the reflected wave

# Reflection and power / Model

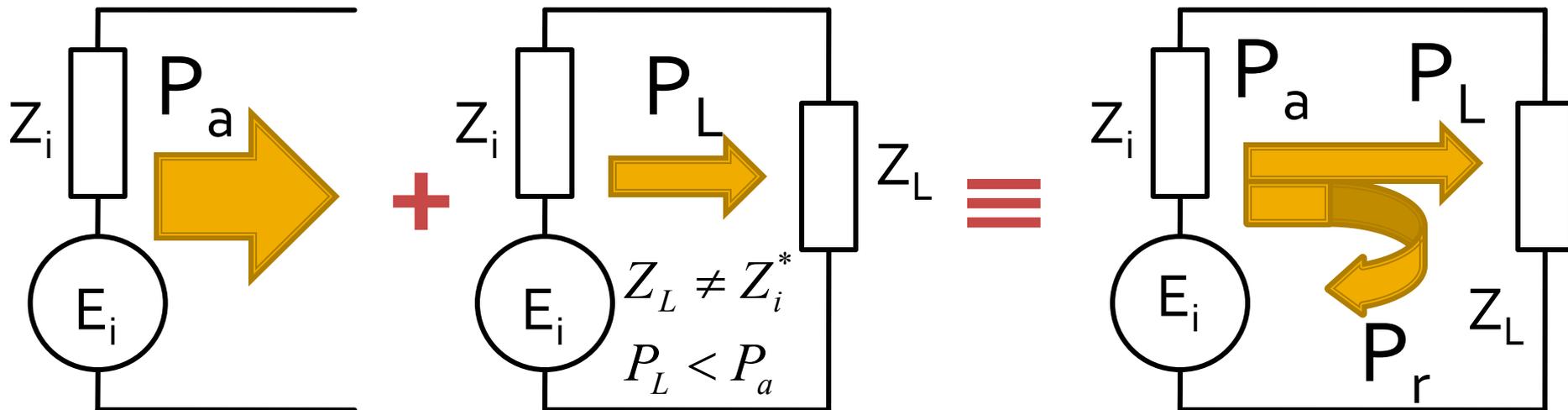


- The source has the ability to send to the load a certain maximum power (available power)  $P_a$
- For a particular load the power sent to the load is less than the maximum (mismatch)  $P_L < P_a$
- The phenomenon is **"as if"** (model) some of the power is reflected  $P_r = P_a - P_L$
- The power is a **scalar** !

# The lossless line


$$P_{avg} = \frac{1}{2} \cdot \frac{|V_0^+|^2}{Z_0} \cdot (1 - |\Gamma|^2)$$

- Average power flow is constant along the line
  - ( **no**  $P_{avg}(\mathbf{z})$  )
  - can be measured
- We can use the power to characterize the amplitude of a signal
  - a very “energetic” (basic physics) point of view
  - more power = “more” signal

# Reflection coefficient

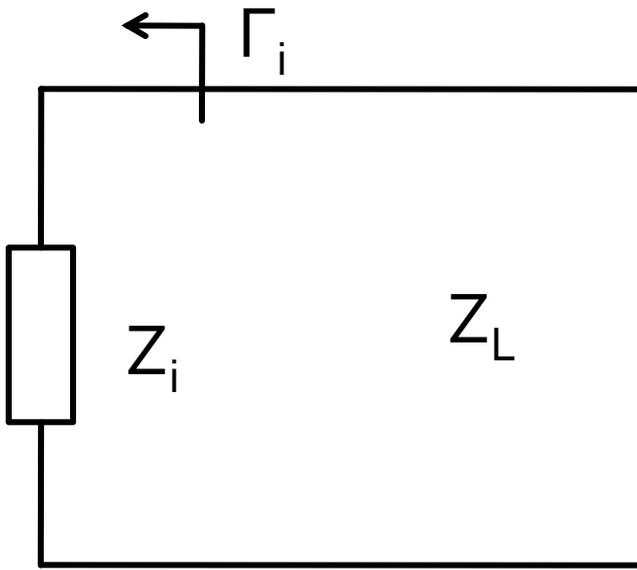
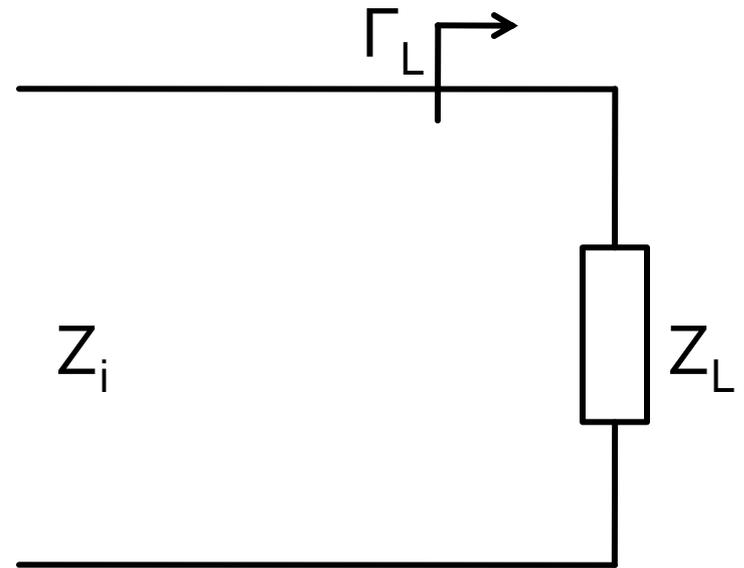
$$\Gamma_i = \frac{Z_i - Z_L^*}{Z_i + Z_L}$$



$$\Gamma_L = \frac{Z_L - Z_i^*}{Z_L + Z_i}$$


# Reflection coefficient

$$\Gamma_i = \frac{(R_i - R_L) + j \cdot (X_i + X_L)}{(R_i + R_L) + j \cdot (X_i + X_L)} \quad \Gamma_L = \frac{(R_L - R_i) + j \cdot (X_L + X_i)}{(R_L + R_i) + j \cdot (X_L + X_i)}$$

$$|\Gamma_i| = \frac{|(R_i - R_L) + j \cdot (X_i + X_L)|}{|(R_i + R_L) + j \cdot (X_i + X_L)|} = \frac{\sqrt{(R_i - R_L)^2 + (X_i + X_L)^2}}{\sqrt{(R_i + R_L)^2 + (X_i + X_L)^2}} = |\Gamma_L|$$

$$|\Gamma_i| = |\Gamma_L| \equiv |\Gamma|$$

# Reflection and power / Model

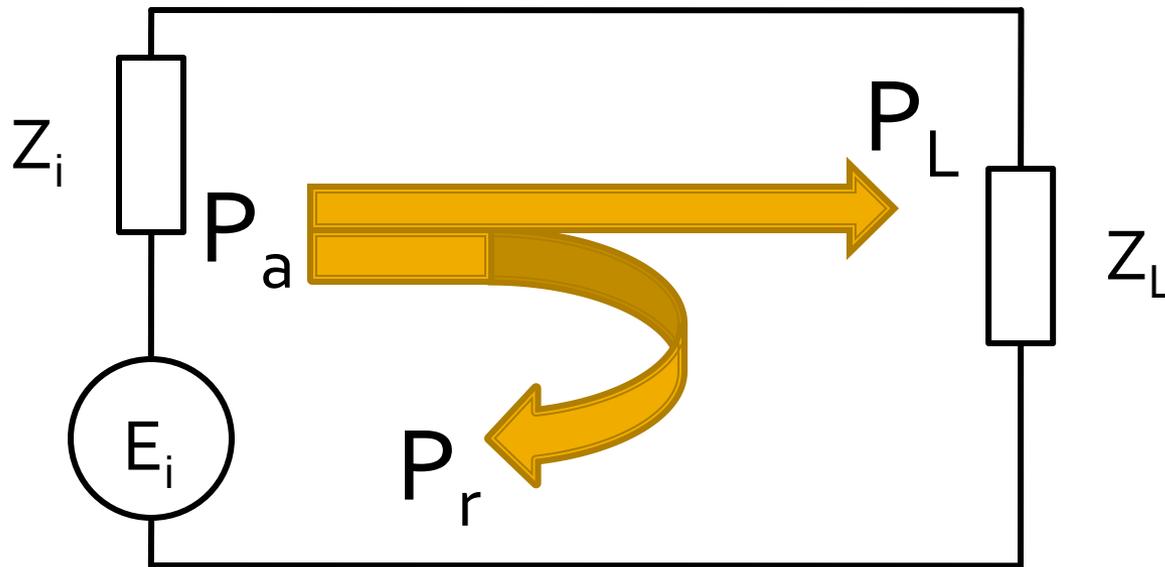

$$P_a = \frac{|E_i|^2}{4R_i}$$

$$P_L = \frac{R_L \cdot |E_i|^2}{(R_i + R_L)^2 + (X_i + X_L)^2}$$

$$P_r = P_a - P_L = \frac{|E_i|^2}{4R_i} - \frac{R_L \cdot |E_i|^2}{(R_i + R_L)^2 + (X_i + X_L)^2} = \frac{|E_i|^2}{4R_i} \cdot \left[ 1 - \frac{4R_L \cdot R_i}{(R_i + R_L)^2 + (X_i + X_L)^2} \right]$$

$$P_r = \frac{|E_i|^2}{4R_i} \cdot \left[ \frac{(R_i - R_L)^2 + (X_i + X_L)^2}{(R_i + R_L)^2 + (X_i + X_L)^2} \right] = P_a \cdot |\Gamma|^2$$

- $|\Gamma|^2$  is a power reflection coefficient

The quarter-wave transformer

# Impedance Matching


# The lossless line, special cases

- $l = k \cdot \lambda/2$      $\beta \cdot l = \frac{2\pi}{\lambda} \cdot l = k \cdot \pi$      $\tan \beta \cdot l = 0$
- $l = \lambda/4 + k \cdot \lambda/2$      $\beta \cdot l = \frac{\pi}{2} + k \cdot \pi$      $\tan \beta \cdot l \rightarrow \infty$

$$Z_{in} = Z_L$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$


- quarter-wave transformer

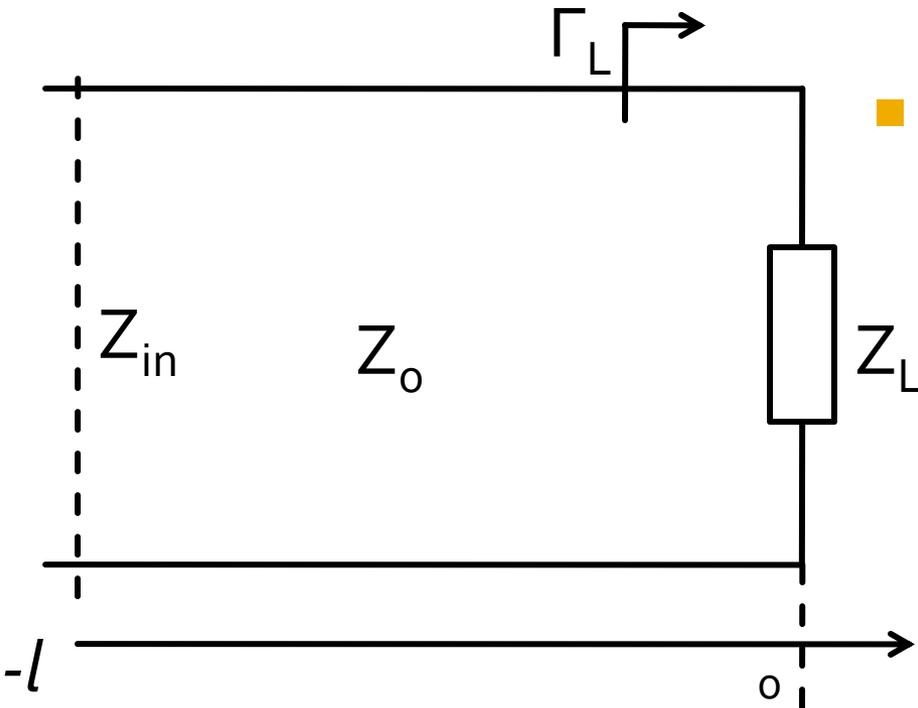

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$
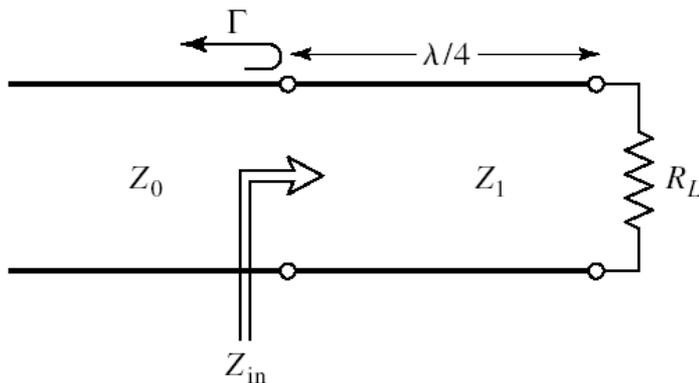
# The quarter-wave transformer

- Feed line – input line with characteristic impedance  $Z_0$
- **Real** load impedance  $R_L$
- We desire matching the load to the feed line with a second line with the length  $\lambda/4$  and characteristic impedance  $Z_1$




$$Z_{in} = Z_1 \frac{1 + \Gamma e^{-2j\beta l}}{1 - \Gamma e^{-2j\beta l}}$$

$$\Gamma_0 = \frac{V_0^-}{V_0^+} = \frac{R_L - Z_1}{R_L + Z_1}$$

$$Z_{in} = Z_1 \frac{R_L + jZ_1 \tan(\beta l)}{Z_1 + jR_L \tan(\beta l)}$$

# The quarter-wave transformer

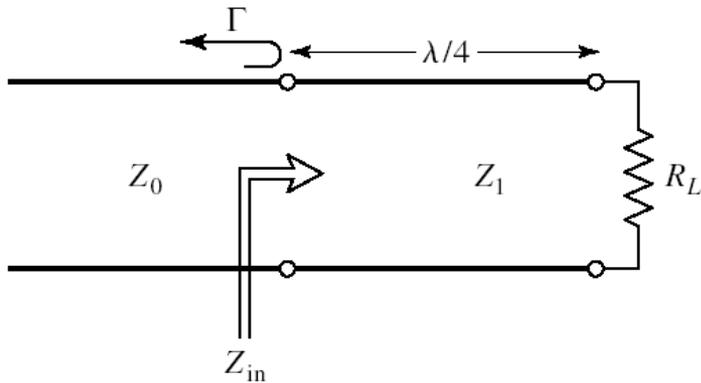

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$\beta \cdot l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}$$

$$Z_{in} = \frac{Z_1^2}{R_L}$$

$$\Gamma_{in} = \frac{Z_1^2 - Z_0 \cdot R_L}{Z_1^2 + Z_0 \cdot R_L} \quad \Gamma_{in} = 0 \quad Z_1 = \sqrt{Z_0 R_L}$$

- In the feed line ( $Z_0$ ) we have only progressive wave
- In the quarter-wave line ( $Z_1$ ) we have standing waves

# The quarter-wave transformer

## ■ The Multiple-Reflection Viewpoint

$$\Gamma = \Gamma_1 - T_1 T_2 \Gamma_3 + T_1 T_2 \Gamma_2 \Gamma_3^2 - T_1 T_2 \Gamma_2^2 \Gamma_3^3 + \dots$$

$$= \Gamma_1 - T_1 T_2 \Gamma_3 \sum_{n=0}^{\infty} (-\Gamma_2 \Gamma_3)^n.$$

$$\Gamma_1 = \frac{Z_1 - Z_0}{Z_1 + Z_0},$$



$$\Gamma_2 = \frac{Z_0 - Z_1}{Z_0 + Z_1} = -\Gamma_1,$$

$$\Gamma_3 = \frac{R_L - Z_1}{R_L + Z_1},$$

$$T_1 = \frac{2Z_1}{Z_1 + Z_0},$$

$$T_2 = \frac{2Z_0}{Z_1 + Z_0}.$$
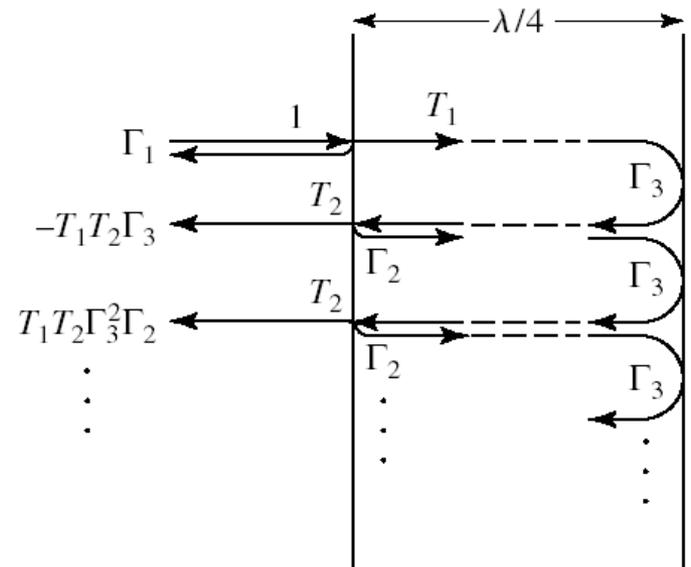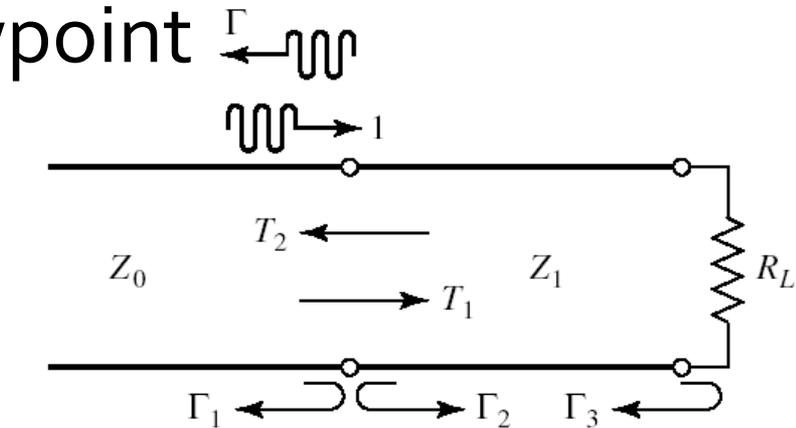
$$\left. \begin{array}{l} T_1 \\ T_2 \end{array} \right\} T = 1 - \Gamma$$



# The quarter-wave transformer

## ■ The Multiple-Reflection Viewpoint


$$\sum_{n=0}^{\infty} x^n = \frac{1}{1-x}, \quad \text{for } |x| < 1,$$

$$\Gamma = \Gamma_1 - \frac{T_1 T_2 \Gamma_3}{1 + \Gamma_2 \Gamma_3} = \frac{\Gamma_1 + \Gamma_1 \Gamma_2 \Gamma_3 - T_1 T_2 \Gamma_3}{1 + \Gamma_2 \Gamma_3}.$$

$$\Gamma_1 - \Gamma_3(\Gamma_1^2 + T_1 T_2) = \frac{2(Z_1^2 - Z_0 R_L)}{(Z_1 + Z_0)(R_L + Z_1)},$$

$$\Gamma_1^2 + T_1 T_2 = \frac{(Z_1 - Z_0)^2}{(Z_1 + Z_0)^2} + \frac{4Z_1 Z_0}{(Z_1 + Z_0)^2} = 1$$
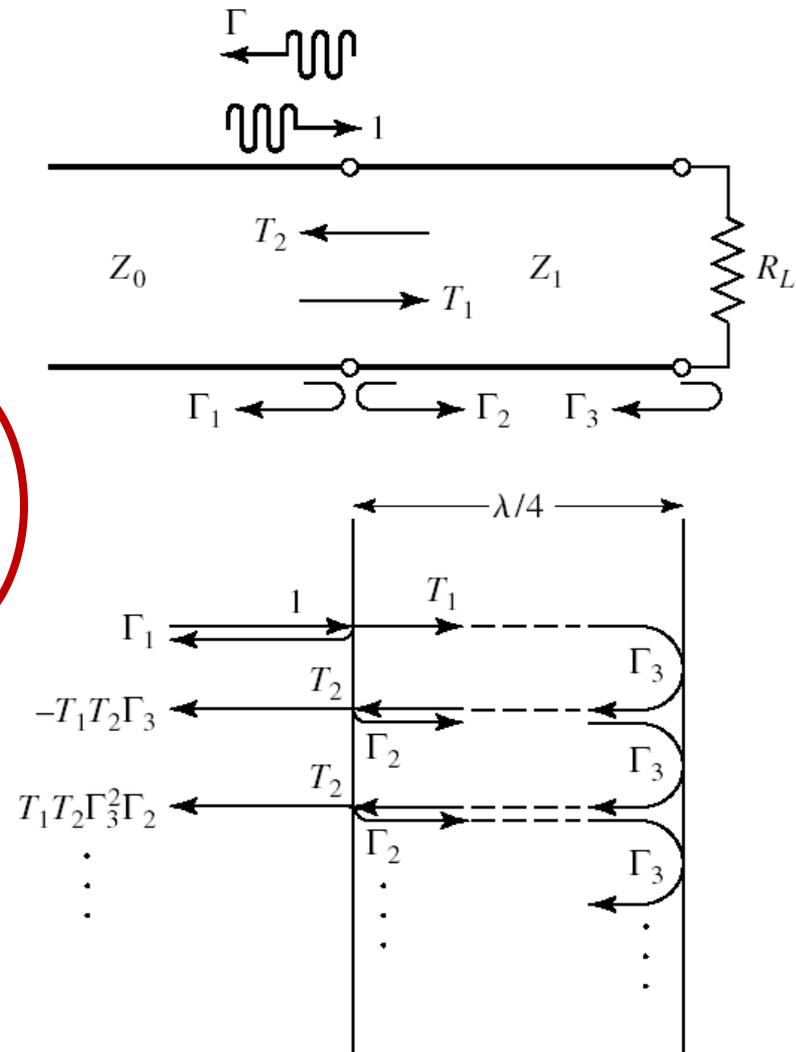
$$\Gamma = 0 \leftrightarrow Z_1^2 - Z_0 \cdot R_L = 0$$



# Frequency response

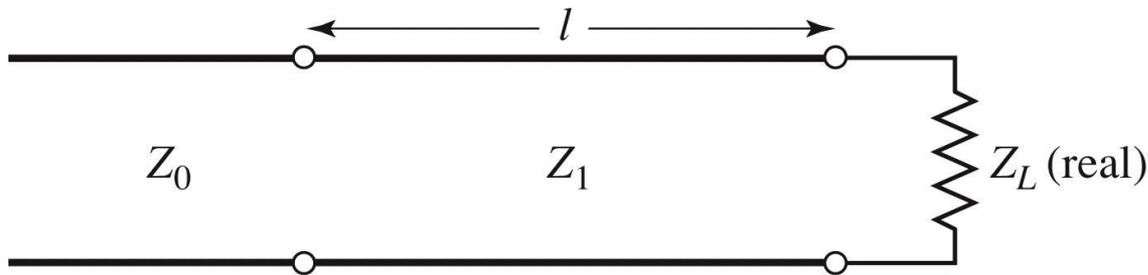


Figure 5.10  
© John Wiley & Sons, Inc. All rights reserved.

$$Z_1 = \sqrt{Z_0 \cdot Z_L}$$

■ **(only)** at  $f_0$

$$l = \frac{\lambda_0}{4} \quad \beta_0 \cdot l = \frac{2\pi}{\lambda_0} \cdot \frac{\lambda_0}{4} = \frac{\pi}{2}$$

$$Z_{in} = Z_1 \cdot \frac{Z_L + j \cdot Z_1 \cdot \tan(\beta \cdot l)}{Z_1 + j \cdot Z_L \cdot \tan(\beta \cdot l)}$$

$$\theta = \beta \cdot l$$

$$t = \tan(\beta \cdot l)$$

$$Z_{in} = Z_1 \cdot \frac{Z_L + j \cdot Z_1 \cdot t}{Z_1 + j \cdot Z_L \cdot t}$$

$$\Gamma = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z_1(Z_L - Z_0) + jt(Z_1^2 - Z_0Z_L)}{Z_1(Z_L + Z_0) + jt(Z_1^2 + Z_0Z_L)}$$

$$Z_1^2 = Z_0 \cdot Z_L$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0 + j2t\sqrt{Z_0Z_L}}$$

# Frequency response

- matching quality  $\equiv$  power reflection coefficient

$$\begin{aligned} |\Gamma| &= \frac{|Z_L - Z_0|}{[(Z_L + Z_0)^2 + 4t^2 Z_0 Z_L]^{1/2}} \\ &= \frac{1}{\left\{ (Z_L + Z_0)^2 / (Z_L - Z_0)^2 + [4t^2 Z_0 Z_L / (Z_L - Z_0)^2] \right\}^{1/2}} \\ &= \frac{1}{\left\{ 1 + [4Z_0 Z_L / (Z_L - Z_0)^2] + [4Z_0 Z_L t^2 / (Z_L - Z_0)^2] \right\}^{1/2}} \\ &= \frac{1}{\left\{ 1 + [4Z_0 Z_L / (Z_L - Z_0)^2] \sec^2 \theta \right\}^{1/2}}, \end{aligned}$$

$$\sec \theta = \frac{1}{\cos \theta} \rightarrow$$


$$\sec^2 \theta = 1 + \tan^2 \theta = 1 + t^2$$

# Frequency response

- we assume that the operating frequency is near the design frequency (narrow bandwidth)

$$f \approx f_0 \quad l \approx \frac{\lambda_0}{4} \quad \theta \approx \frac{\pi}{2} \quad \sec^2 \theta = 1 + \tan^2 \theta \gg 1$$

$$|\Gamma| \cong \frac{|Z_L - Z_0|}{2 \cdot \sqrt{Z_0 \cdot Z_L}} \cdot |\cos \theta|$$

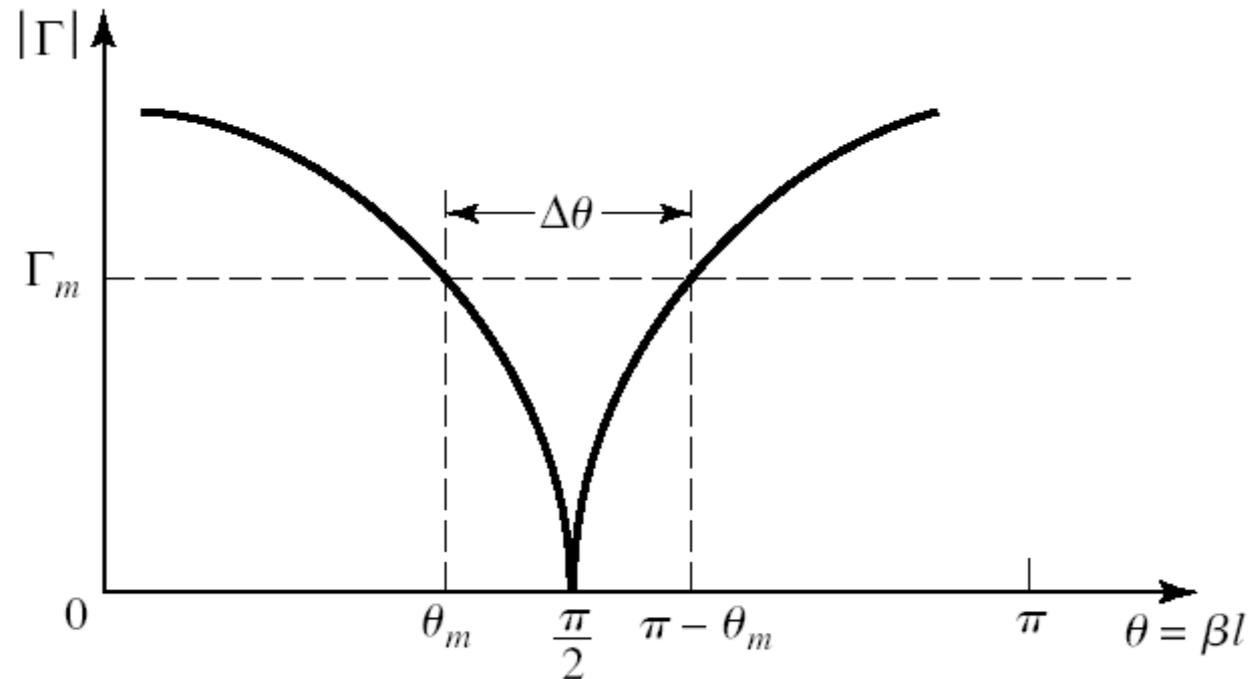


# Frequency response

- we set a maximum value  $\Gamma_m$  for an acceptable reflection coefficient magnitude then the bandwidth of the matching transformer,  $\theta_m$

$$\frac{1}{\Gamma_m^2} = 1 + \left( \frac{2\sqrt{Z_0 Z_L}}{Z_L - Z_0} \sec \theta_m \right)^2,$$

$$\cos \theta_m = \frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_0 Z_L}}{|Z_L - Z_0|}.$$
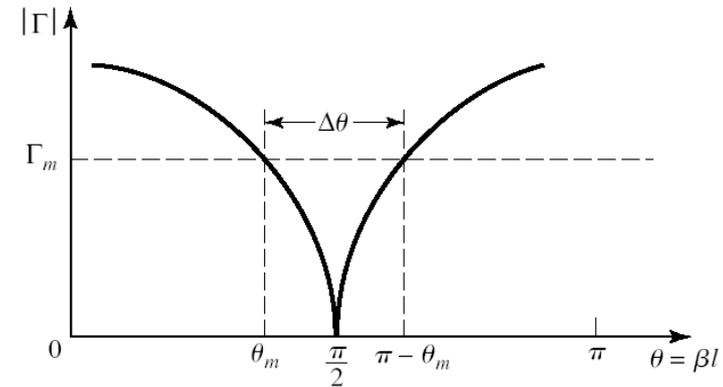
$$\Delta\theta = 2 \left( \frac{\pi}{2} - \theta_m \right)$$



- for TEM lines

$$\theta = \beta \cdot l = \beta \cdot \frac{\lambda_0}{4} = \frac{2\pi \cdot f}{v_f} \cdot \frac{1}{4} \cdot \frac{v_f}{f_0} = \frac{\pi \cdot f}{2f_0}$$

$$f_m = \frac{2 \cdot \theta_m \cdot f_0}{\pi}$$

$$\frac{\Delta f}{f_0} = \frac{2 \cdot (f_0 - f_m)}{f_0} = 2 - \frac{4 \cdot \theta_m}{\pi} = 2 - \frac{4}{\pi} \cdot \cos^{-1} \left[ \frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \cdot \frac{2\sqrt{Z_0 \cdot Z_L}}{|Z_L - Z_0|} \right]$$


# Frequency response

- When non-TEM lines (such as waveguides) are used, the propagation constant is no longer a linear function of frequency, and the wave impedance will be frequency dependent, but in practice the bandwidth of the transformer is often small enough that these complications do not substantially affect the result
- We ignored also the effect of reactances associated with discontinuities when there is a step change in the dimensions of a transmission line ( $Z_0 \rightarrow Z_1$ ). This can often be compensated by making a small adjustment in the length of the matching section
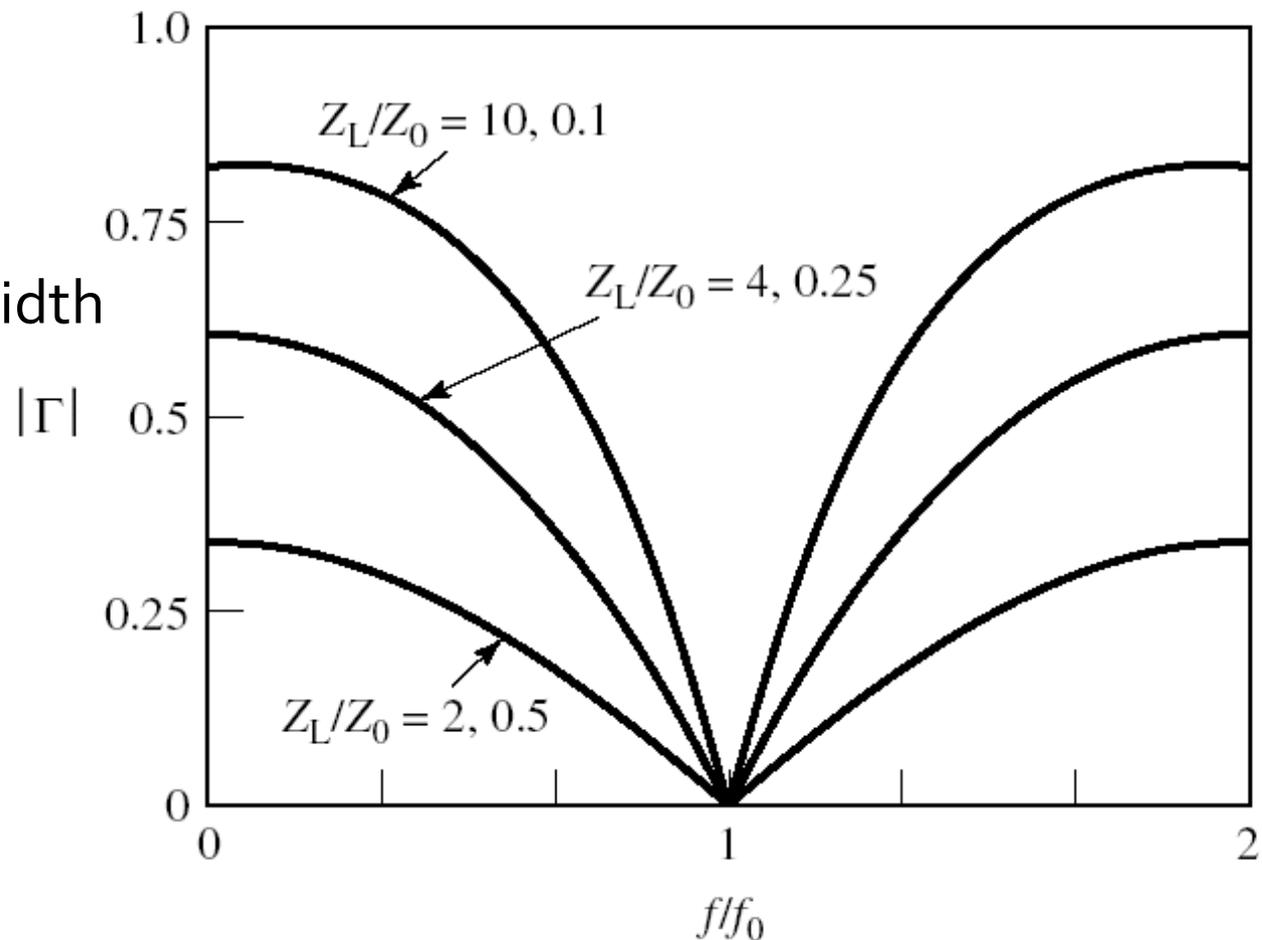
# Frequency response

- Bandwidth depends on the initial mismatch

increased bandwidth  
for smaller load  
mismatches



# Example


- A quarter-wave matching transformer to match a  $10\Omega$  load to a  $50\Omega$  transmission line at  $f_0=3\text{GHz}$ 
  - Determine the percent bandwidth for  $\text{SWR}<1.5$

$$Z_1 = \sqrt{Z_0 Z_L} = \sqrt{(50)(10)} = 22.36 \Omega, \quad \Gamma_m = \frac{\text{SWR} - 1}{\text{SWR} + 1} = \frac{1.5 - 1}{1.5 + 1} = 0.2.$$

$$\begin{aligned} \frac{\Delta f}{f_0} &= 2 - \frac{4}{\pi} \cos^{-1} \left[ \frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_0 Z_L}}{|Z_L - Z_0|} \right] \\ &= 2 - \frac{4}{\pi} \cos^{-1} \left[ \frac{0.2}{\sqrt{1 - (0.2)^2}} \frac{2\sqrt{(50)(10)}}{|10 - 50|} \right] \\ &= 0.29, \text{ or } 29\%. \end{aligned}$$

# Simulation

## ■ ADS Simulation

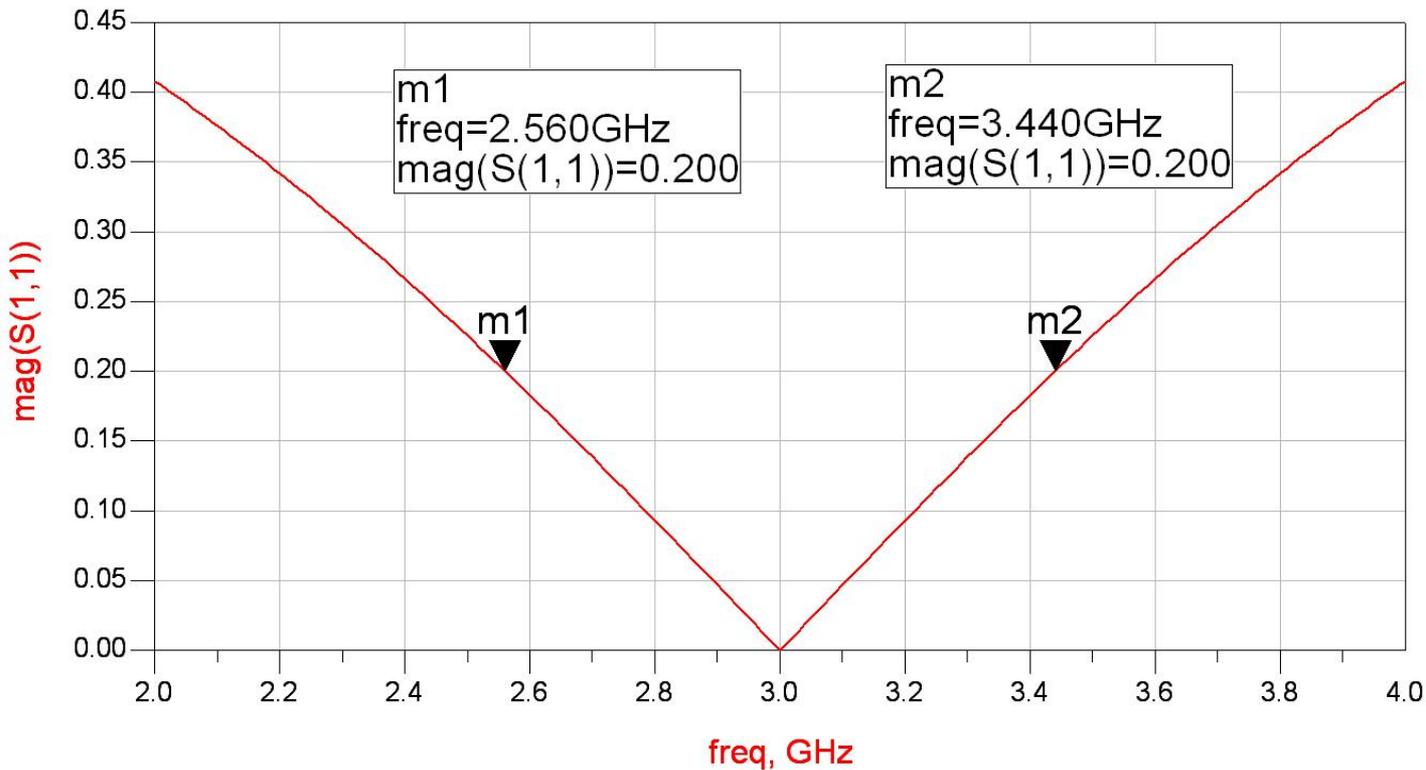


$$\Delta f = 0.88 \text{GHz}$$

$$|\Gamma(3 \text{GHz})| = 3 \cdot 10^{-5}$$

$$\frac{\Delta f}{f_0} = \frac{0.88}{3} = 0.2933$$

# Full bandwidth simulation

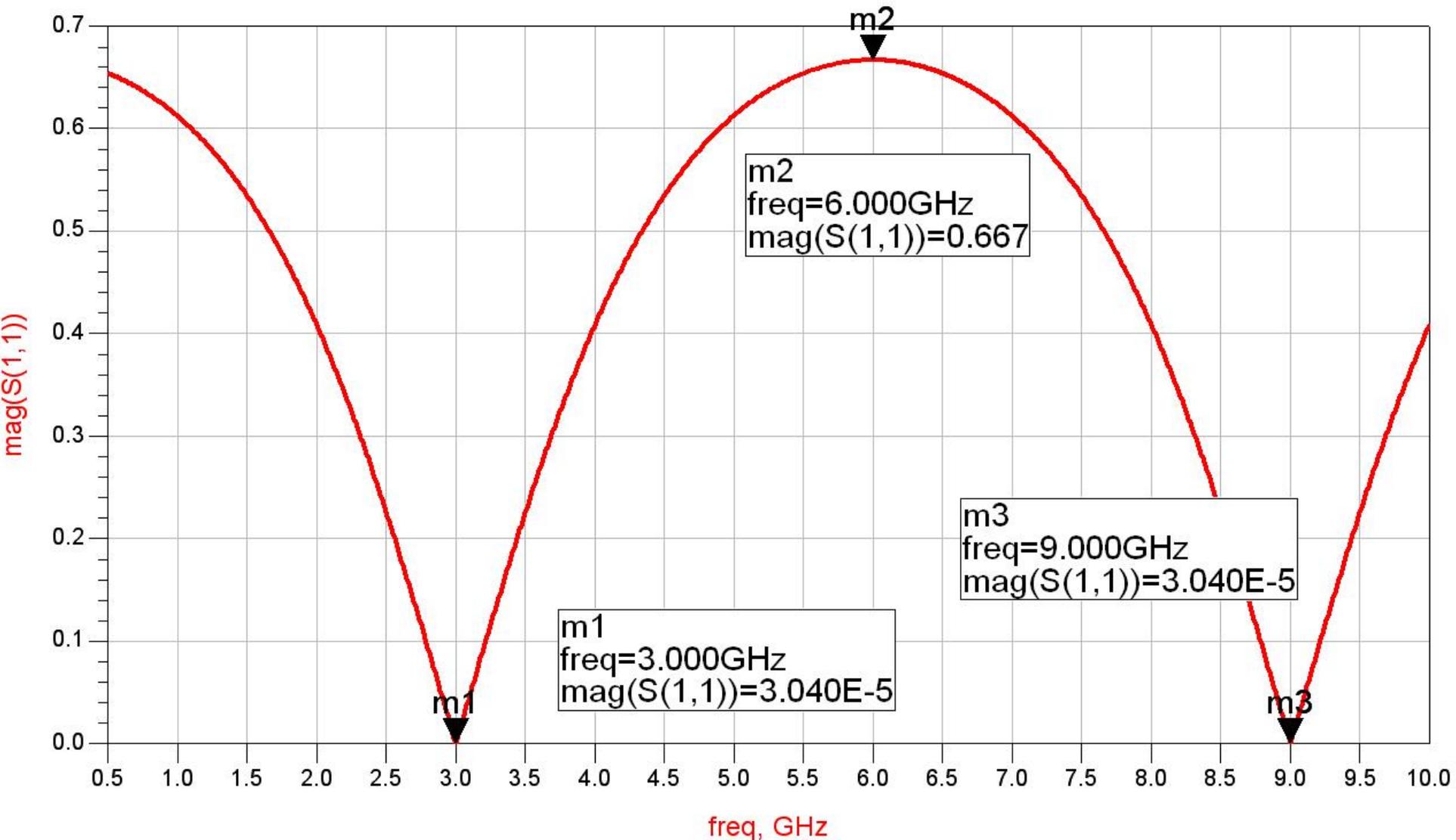

Laboratory 1

# Impedance Matching

# The quarter-wave transformer



S-PARAMETERS


S\_Param

SP1


Start=0.5 GHz

Stop=5.5 GHz

Step=0.001 GHz

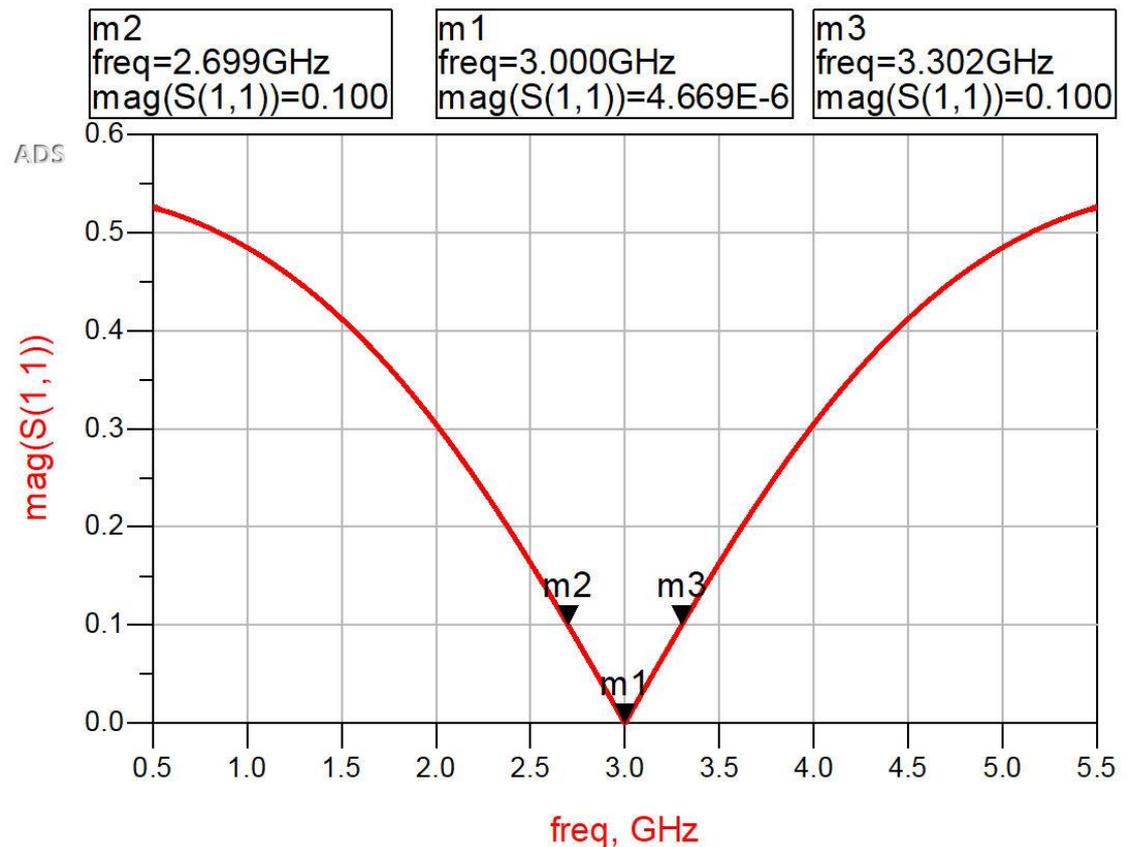


# Binomial multisection transformer

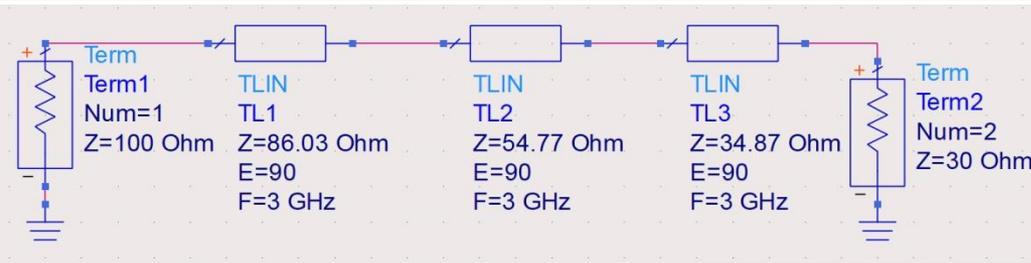


 S-PARAMETERS

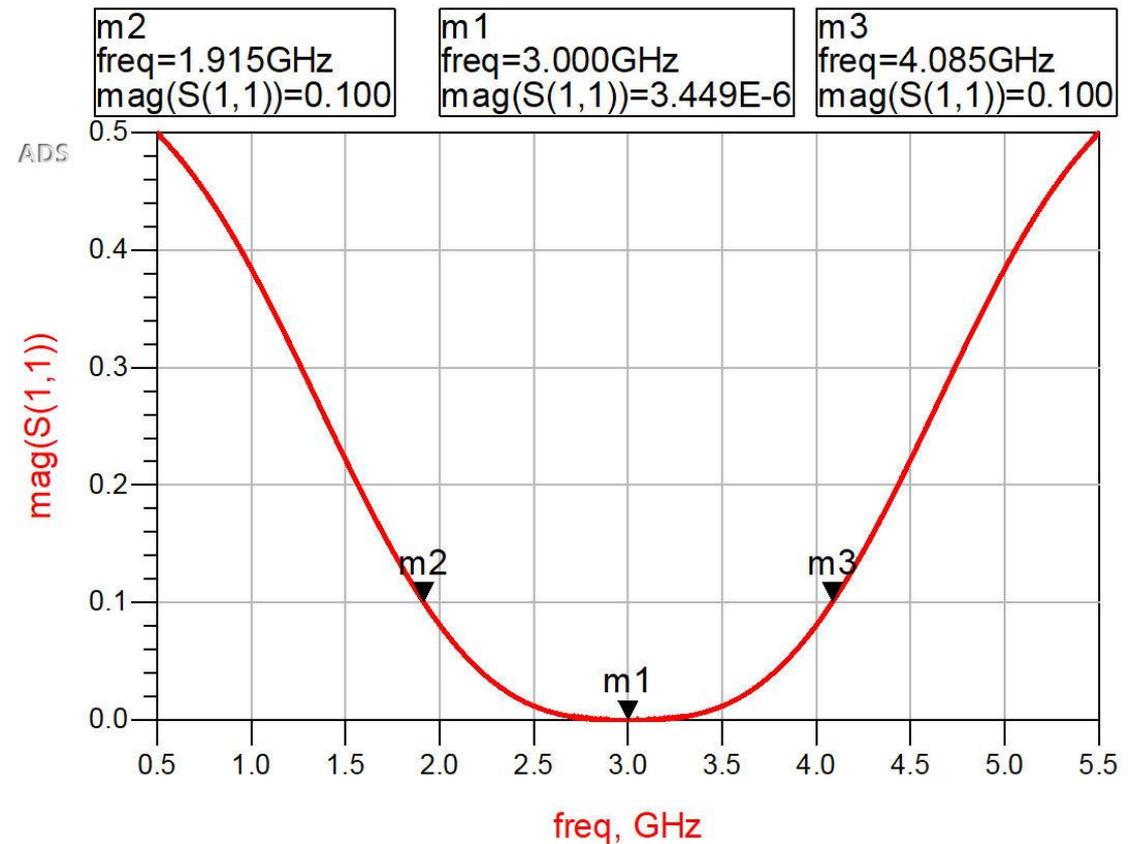S\_Param  
SP1  
Start=0.5 GHz  
Stop=5.5 GHz  
Step=0.001 GHz




# Chebyshev multisection transformer

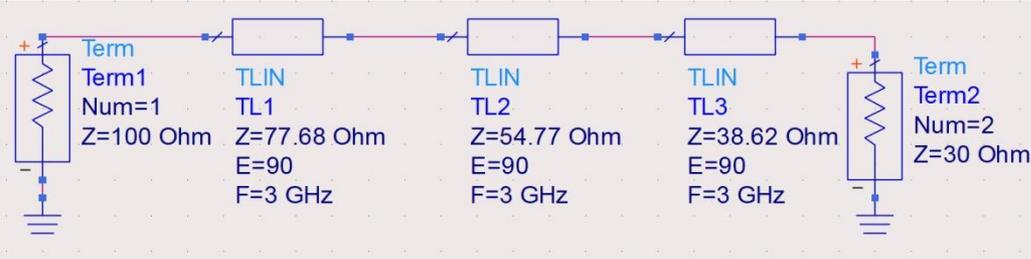
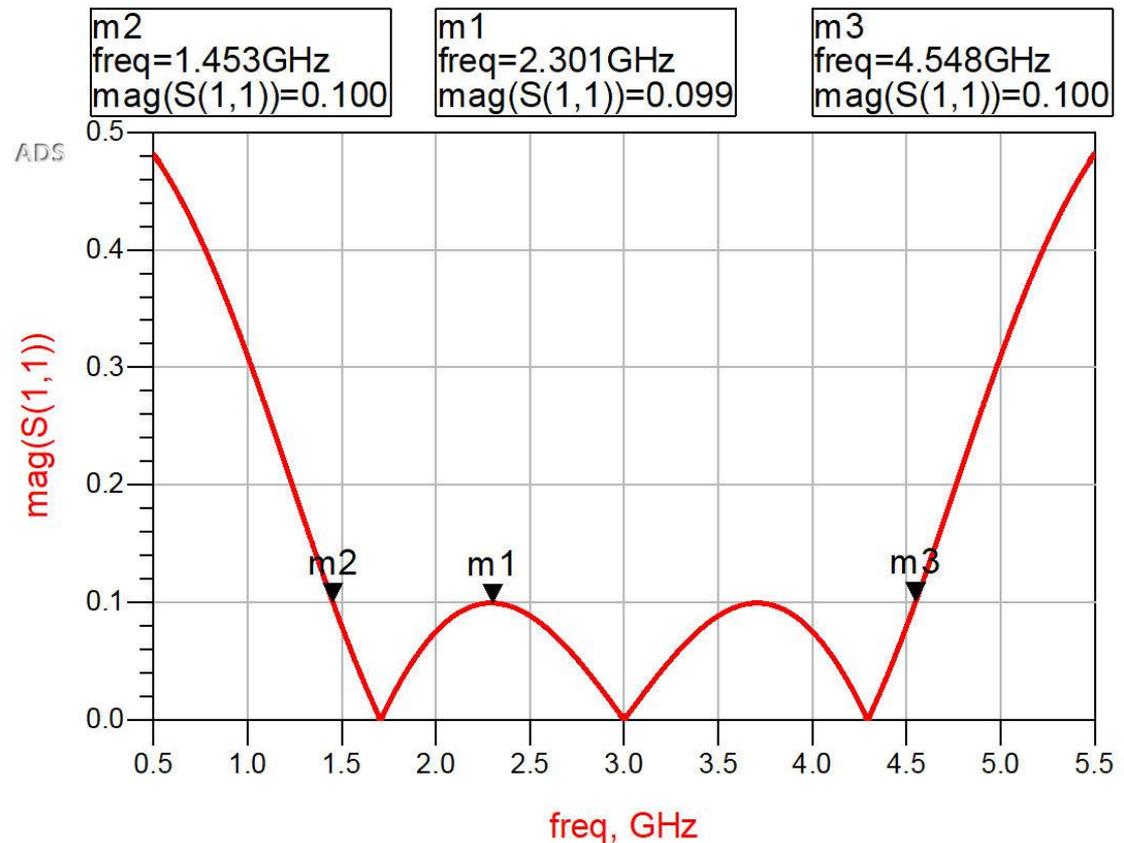
## S-PARAMETERS

S\_Param  
SP1  
Start=0.5 GHz  
Stop=5.5 GHz  
Step=0.001 GHz



# Contact

- Microwave and Optoelectronics Laboratory
- <https://rf-opto.etti.tuiasi.ro>
- [rdamian@etti.tuiasi.ro](mailto:rdamian@etti.tuiasi.ro)