

Lecture 7  
2025/2026

# Microwave Devices and Circuits for Radiocommunications

# 2025/2026

- 2C/1L, **MDCR**
- Attendance at minimum 7 sessions (course or laboratory)
- Lectures- **associate professor Radu Damian**
  - Tuesday **12-14, P2**
  - E – 50% final grade
  - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
    - first test L1: 24.02.2026 (t2 and t3 not announced, lecture)
    - 3att.=+0.5p
  - all materials/equipments authorized


# 2025/2026

- Laboratory – **associate professor Radu Damian**
  - Monday 14-16, II.13 / (even weeks)
  - L – 25% final grade
    - ADS, 4 sessions
    - Attendance + **personal results**
  - P – 25% final grade
    - ADS, 3 sessions (-1? 24.02.2026)
    - personal homework

General theory


# Microwave Network Analysis

# Course Topics

- Transmission lines
  - Impedance matching and tuning
  - Directional couplers
  - Power dividers
  - Microwave amplifier design
  - Microwave filters
  - ~~Oscillators and mixers?~~
- 

# Scattering matrix – S

- Scattering parameters

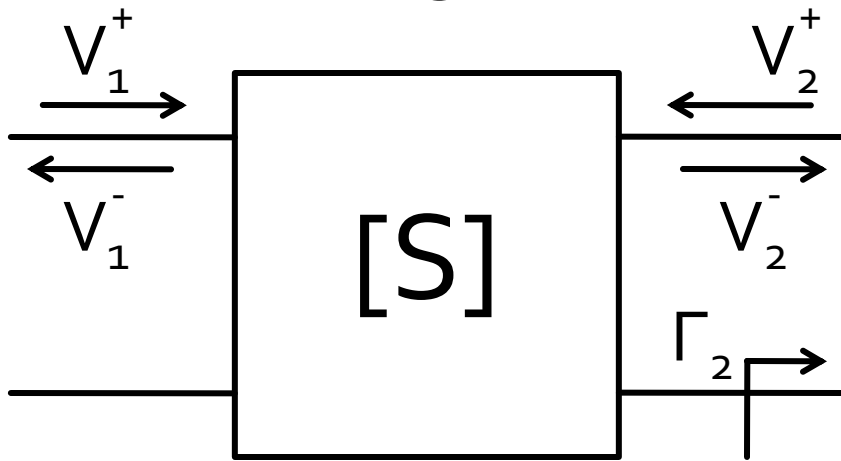

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0}$$

- $V_2^+ = 0$  meaning: port 2 is terminated in matched load to avoid reflections towards the port

$$\Gamma_2 = 0 \rightarrow V_2^+ = 0$$

# Power waves for N ports

$$[b] = [F] \cdot ([Z] - [Z_R]^*) \cdot ([Z] + [Z_R])^{-1} \cdot [F]^{-1} \cdot [a]$$

- The scattering matrix for power waves,  $[S_p]$

$$[b] = [S_p] \cdot [a]$$

$$[S_p] = [F] \cdot ([Z] - [Z_R]^*) \cdot ([Z] + [Z_R])^{-1} \cdot [F]^{-1}$$

- But:  $[S] = ([Z] - [Z_0]) \cdot ([Z] + [Z_0])^{-1}$

- Typically


$$Z_{0i} = Z_{Ri} = R_0, \forall i$$

$$R_0 = 50\Omega$$

$$[S_p] \equiv [S]$$

- they coincide!!!

# Scattering matrix – S

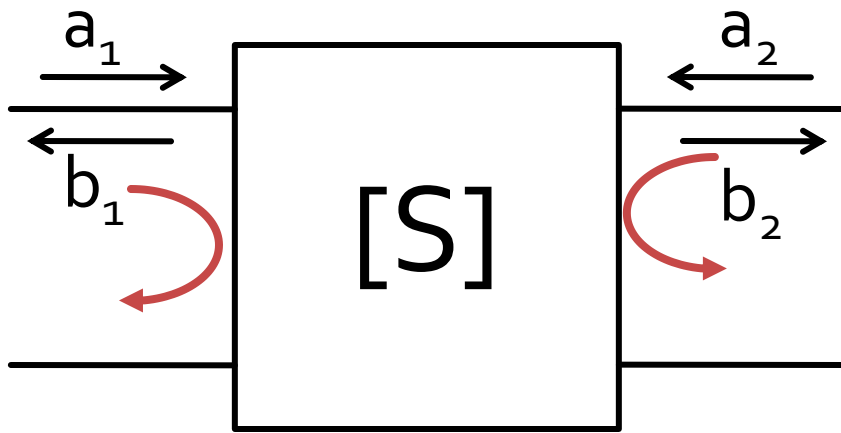


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

- $S_{11}$  and  $S_{22}$  are **reflection coefficients** at ports 1 and 2 when the other port is **matched**

# Scattering matrix – S

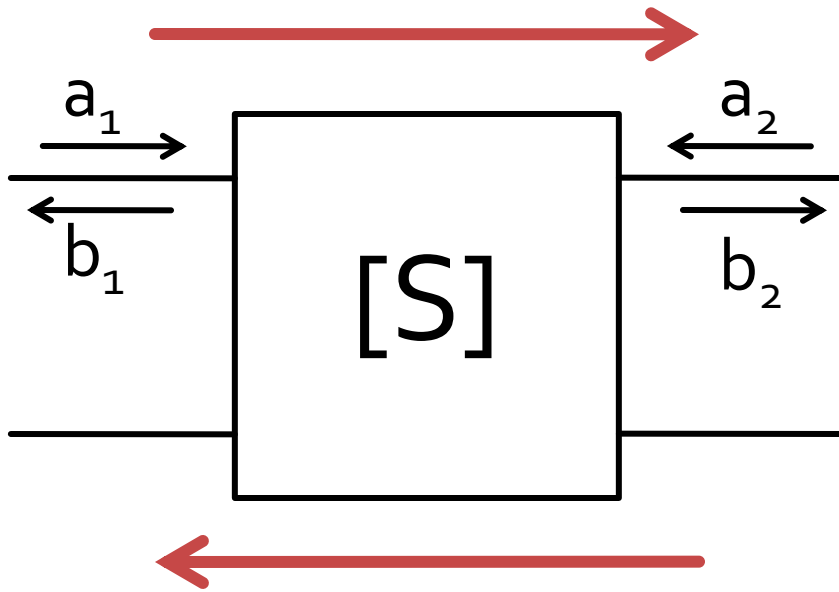


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$$

- $S_{21}$  si  $S_{12}$  are signal amplitude **gain** when the other port is **matched**

# Scattering matrix – S

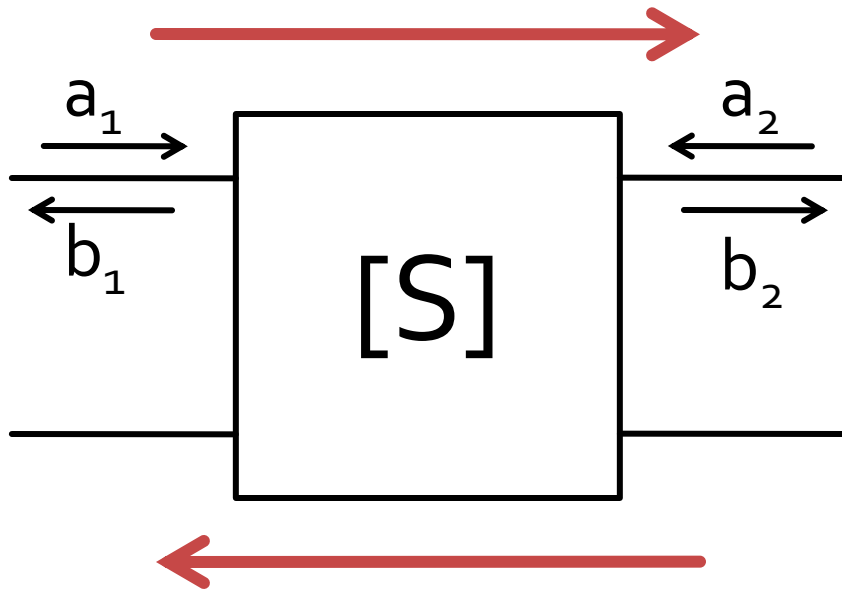

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- $a, b$ 
  - information about signal power **AND** signal phase
- $S_{ij}$ 
  - network effect (gain) over signal power **including** phase information


# Power dividers and directional couplers

# Course Topics


- Transmission lines
- Impedance matching and tuning
- **Directional couplers**
- **Power dividers**
- Microwave amplifier design
- Microwave filters
- ~~Oscillators and mixers~~
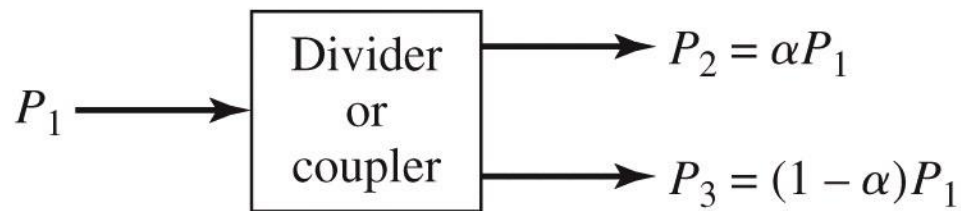
# Power dividers and couplers

- Desired functionality:
  - division
  - combining
- of signal power



(a)

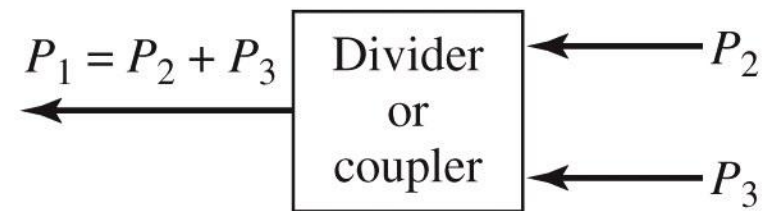


(b)
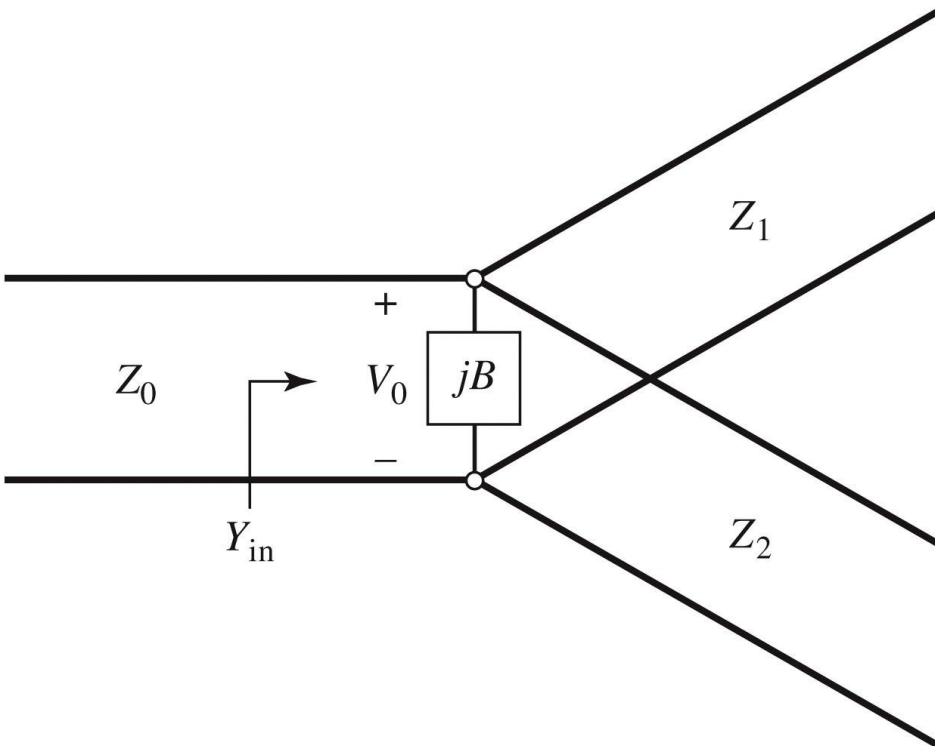
# Power division of the T-junction


- if the lines are lossless, the network is reciprocal, so it cannot be matched at all ports simultaneously

- there may be fringing fields and higher order modes associated with the discontinuity at such a junction
- the stored energy can be accounted for by a lumped susceptance: **B**
- Designing the power divider targets matching to the input line  $Z_0$ 
  - outputs (unmatched,  $Z_1$  and  $Z_2$ ) can be, if needed, matched to  $Z_0$  ( $\lambda/4$ , binomial, Chebyshev)


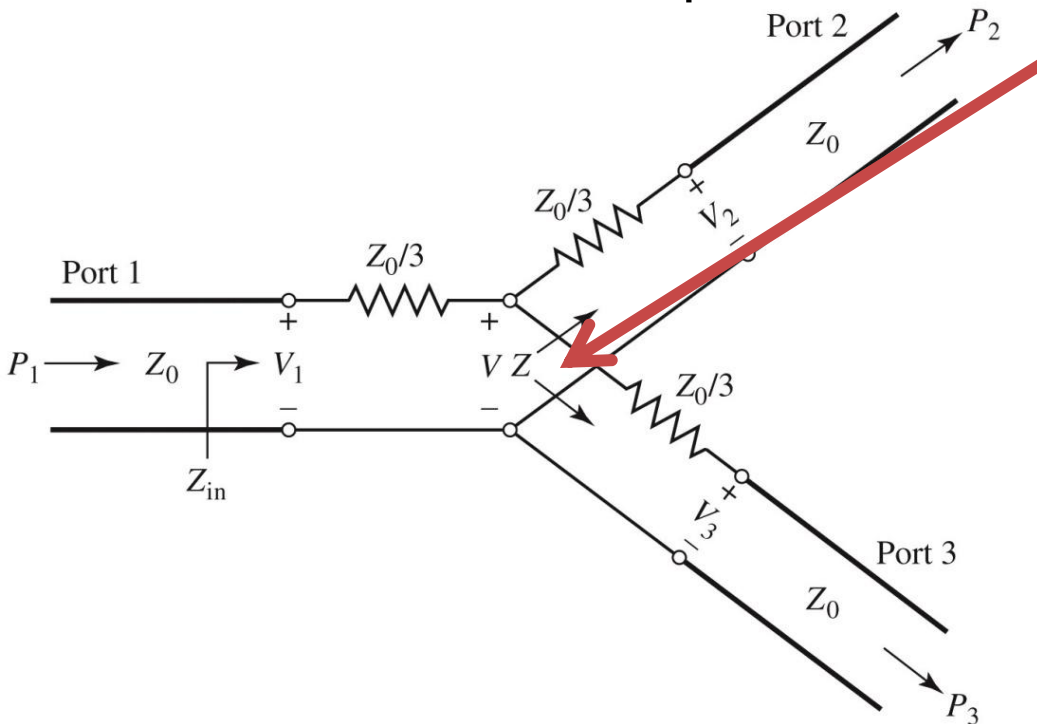
# Resistive Divider

- If a three-port divider contains lossy components, it can be made to be :
  - reciprocal
  - matched at all ports



The impedance  $Z$ , seen looking into the  $Z_0/3$  resistor followed by a terminated output line:

$$Z = \frac{Z_0}{3} + Z_0 = \frac{4Z_0}{3}$$

The input line will be terminated with a  $Z_0/3$  resistor in series with two such lines  $Z$  in parallel


$$Z_{in} = \frac{Z_0}{3} + \frac{1}{2} \cdot \frac{4Z_0}{3} = Z_0$$

so it will be matched:  $S_{11} = 0$


from symmetry:  $S_{11} = S_{22} = S_{33} = 0$
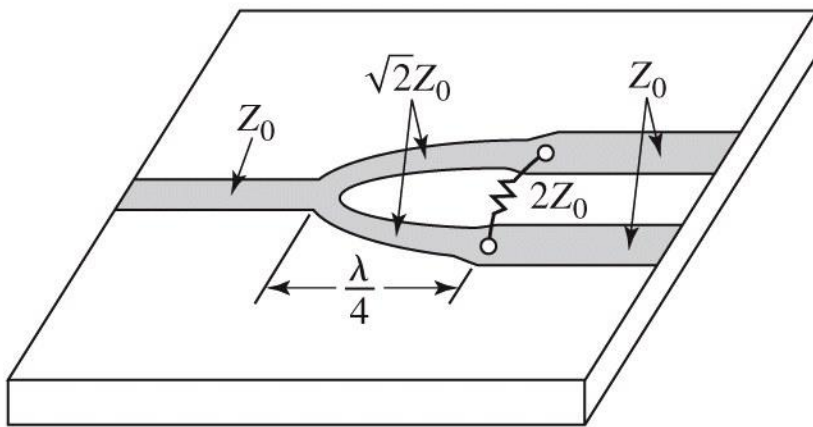
# The Wilkinson power divider

- one input line
- two  $\lambda/4$  transformers
- one resistor between the output lines




(a)

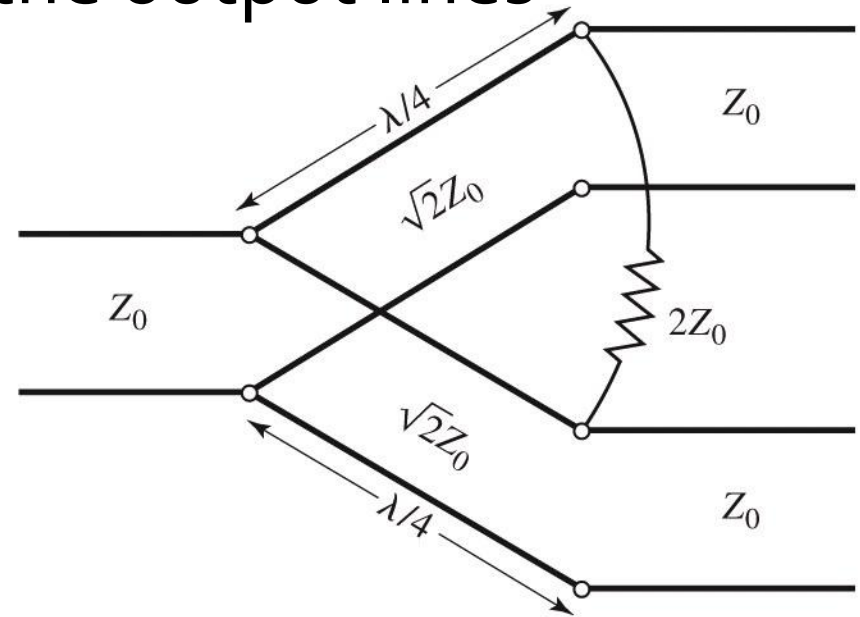


(b)

# The Wilkinson power divider

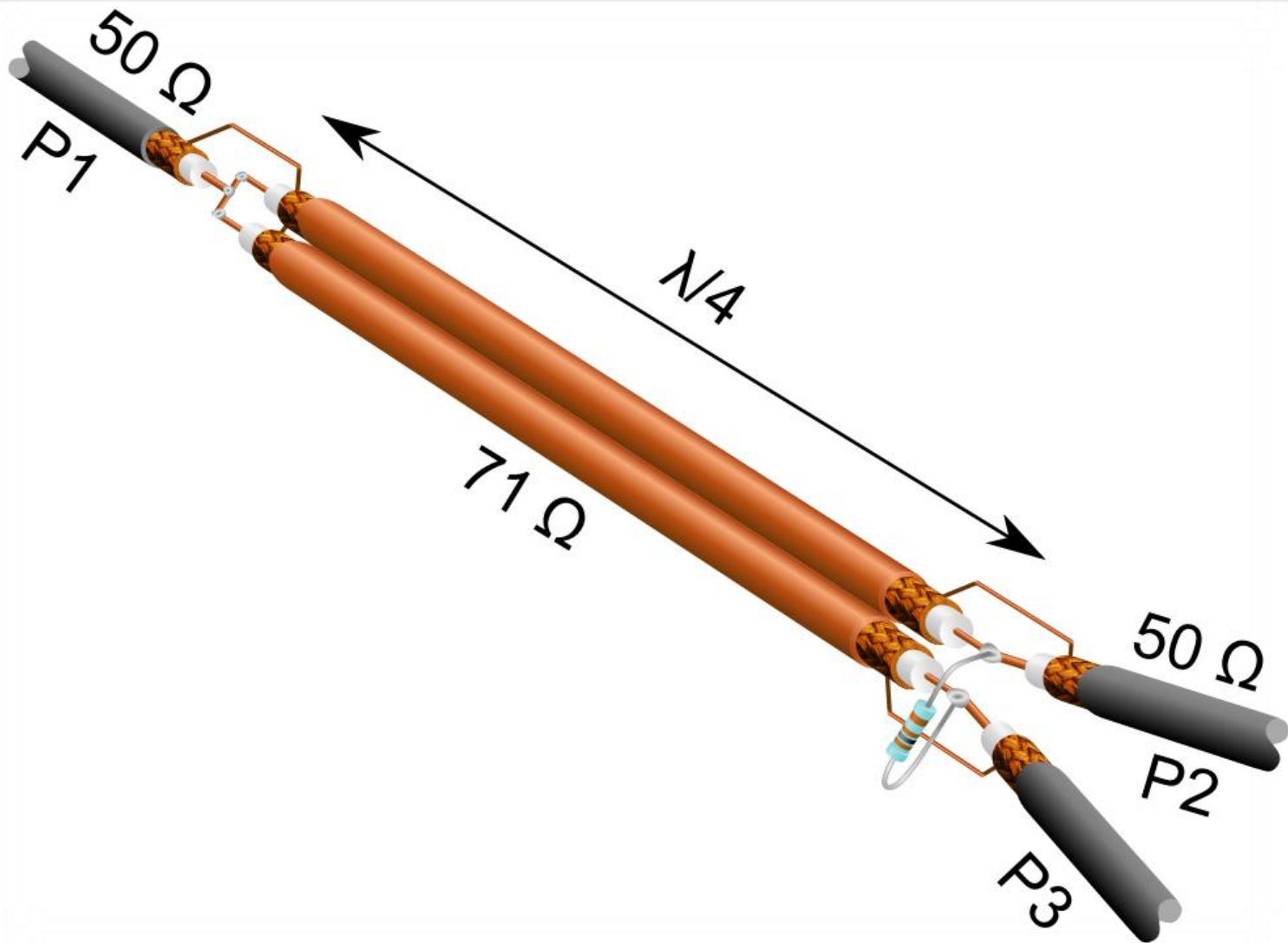

# Directional couplers

# Directional Coupler

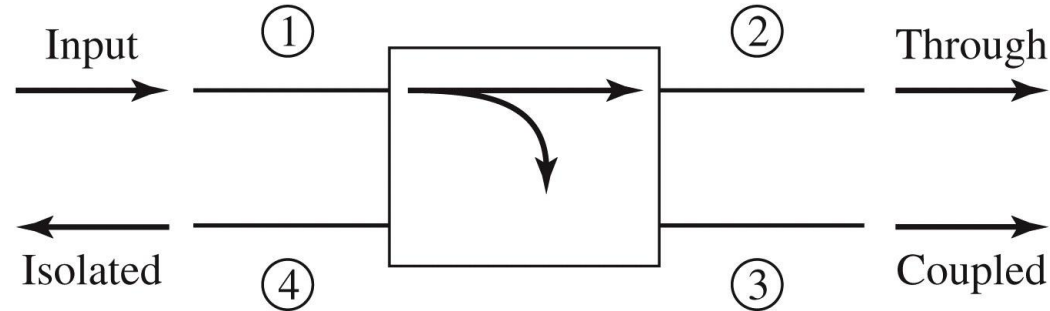

$$|S_{12}|^2 = \alpha^2 = 1 - \beta^2$$

$$|S_{13}|^2 = \beta^2$$

**Coupling**

$$C = 10 \log \frac{P_1}{P_3} = -20 \cdot \log(\beta) [\text{dB}]$$

**Directivity**


$$D = 10 \log \frac{P_3}{P_4} = 20 \cdot \log \left( \frac{\beta}{|S_{14}|} \right) [\text{dB}]$$

**Isolation**

$$I = 10 \log \frac{P_1}{P_4} = -20 \cdot \log |S_{14}| [\text{dB}]$$

$$I = D + C, \quad [\text{dB}]$$

Figure 7.4  
© John Wiley & Sons, Inc. All rights reserved.

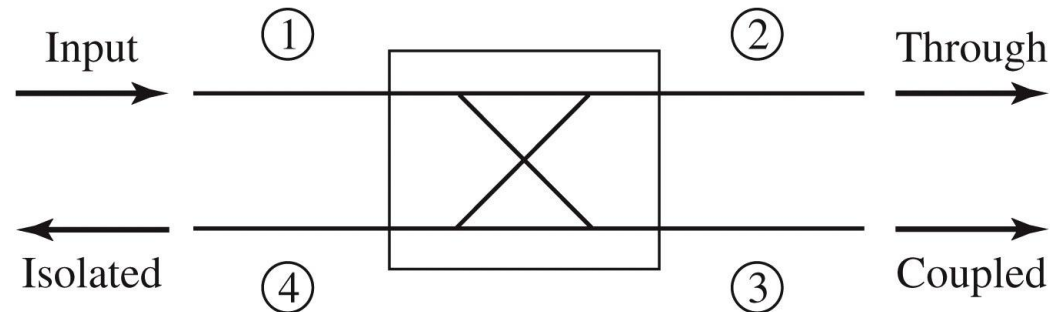

Directional Couplers

# Laboratory no. 2

# The quadrature (90°) hybrid

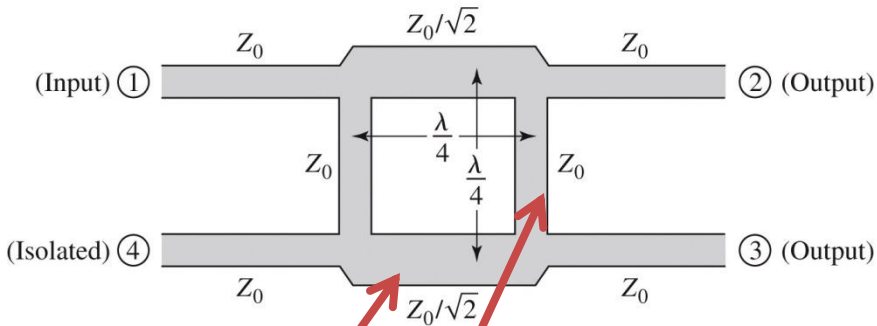


Figure 7.21  
© John Wiley & Sons, Inc. All rights reserved.

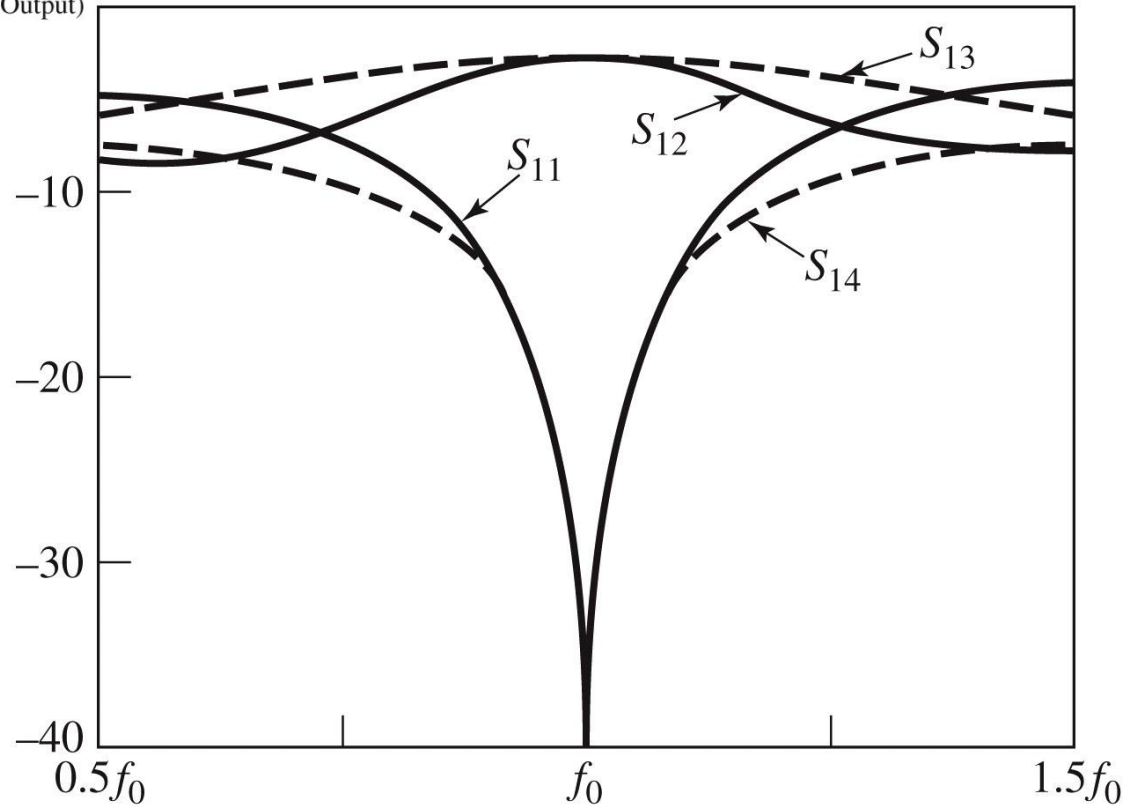



Figure 7.25  
© John Wiley & Sons, Inc. All rights reserved.

$$y_2^2 = 1 + y_1^2$$

$$|\beta| = \frac{\sqrt{y_2^2 - 1}}{y_2}$$

$$C[\text{dB}] = -20 \cdot \log_{10} \frac{\sqrt{y_2^2 - 1}}{y_2}$$

# The 180° ring hybrid

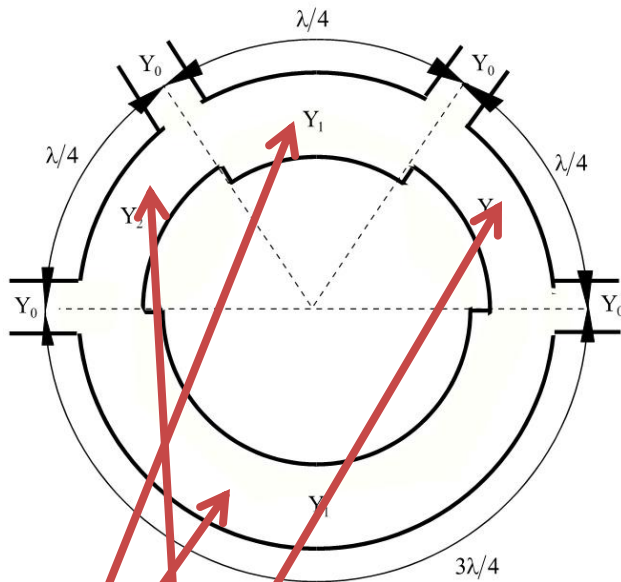

$$y_1^2 + y_2^2 = 1$$

$$|\beta| = y_1$$

$$C \text{ [dB]} = -20 \cdot \log_{10}(y_1)$$


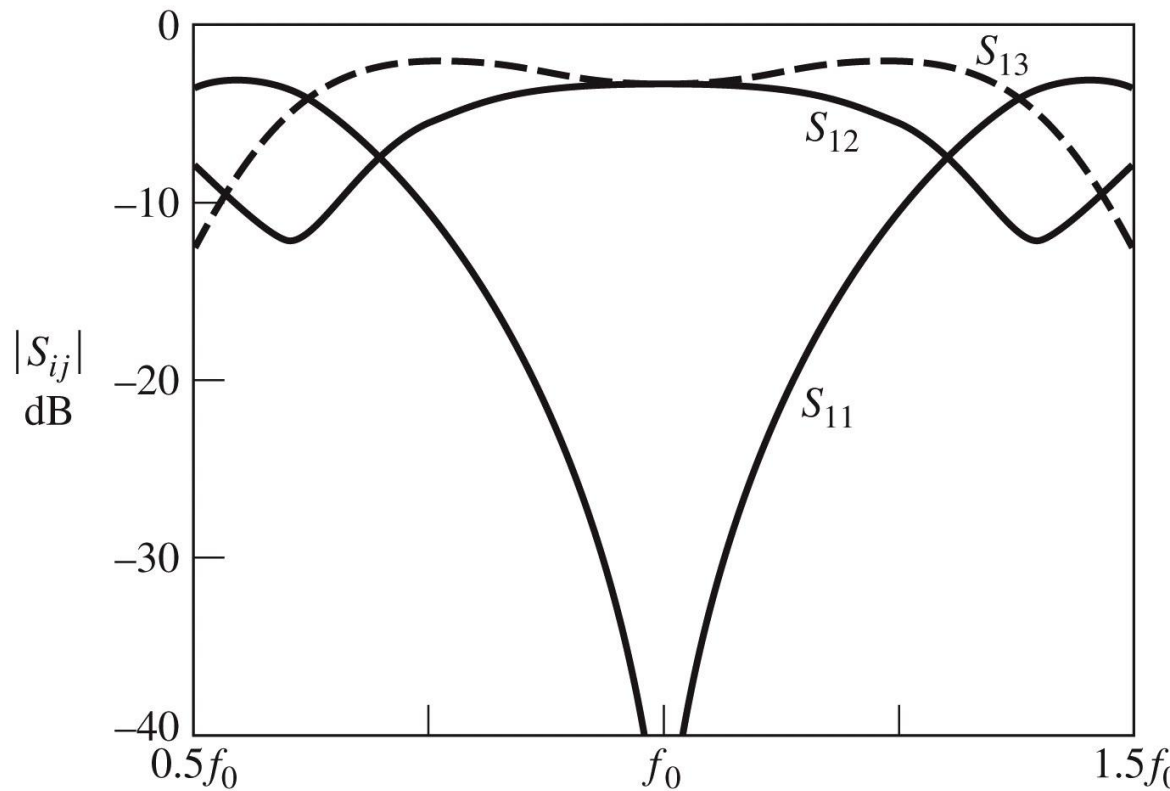


Figure 7.46  
© John Wiley & Sons, Inc. All rights reserved.

# Coupled Line Coupler

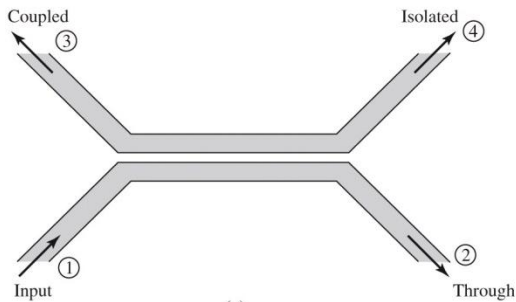

Coupling, Directivity (dB)

$$Z_{ce} Z_{co} = Z_0^2$$

$$|\beta| = \frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}}$$

$$C \text{ [dB]} = -20 \cdot \log_{10} \left( \frac{Z_{ce} - Z_{co}}{Z_{ce} + Z_{co}} \right)$$

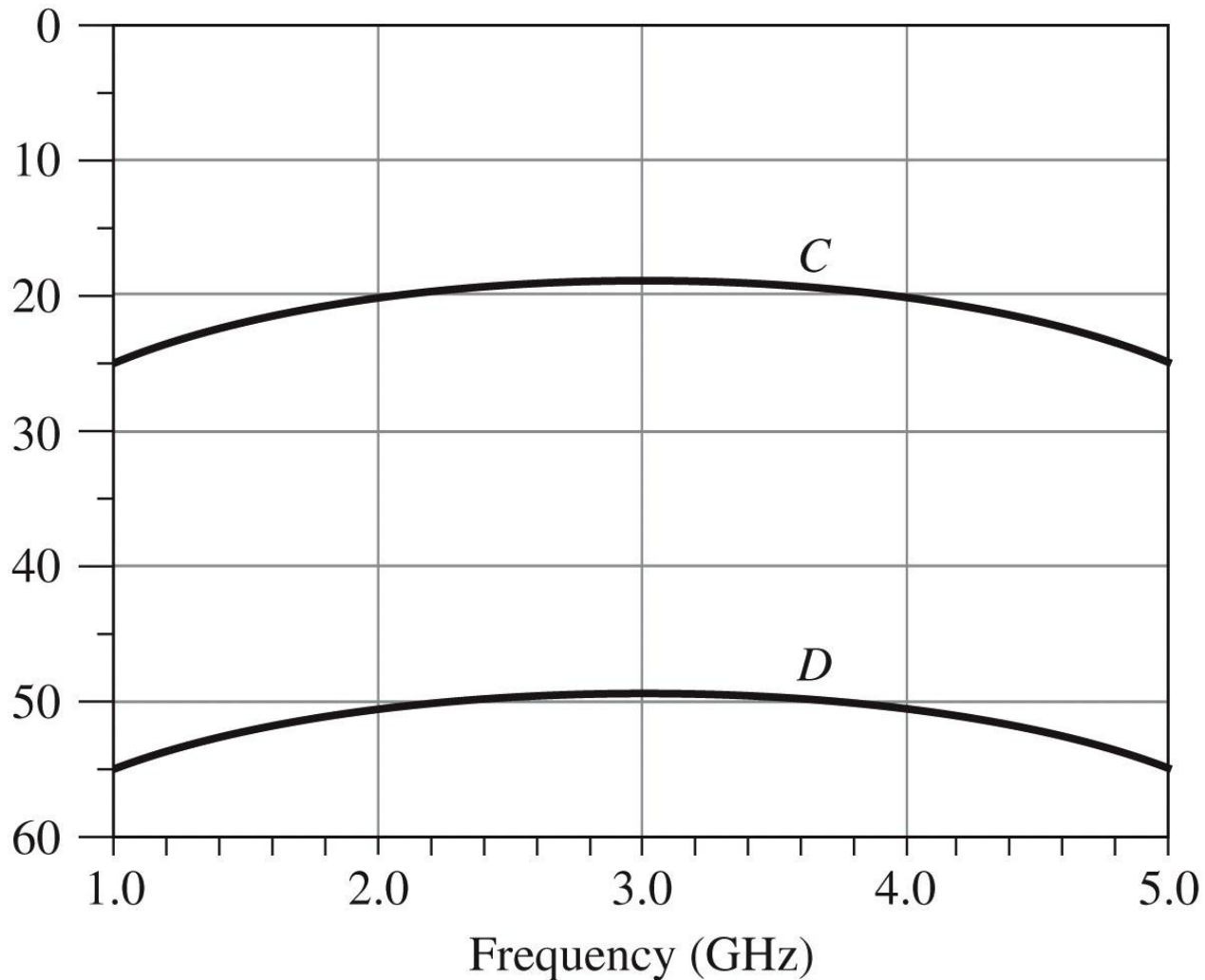



Figure 7.34  
© John Wiley & Sons, Inc. All rights reserved.

Impedance Matching



# The Smith Chart

# Course Topics


- Transmission lines
  - Impedance matching and tuning
  - Directional couplers
  - Power dividers
  - Microwave amplifier design
  - Microwave filters
  - ~~Oscillators and mixers?~~
- 





# The Smith Chart

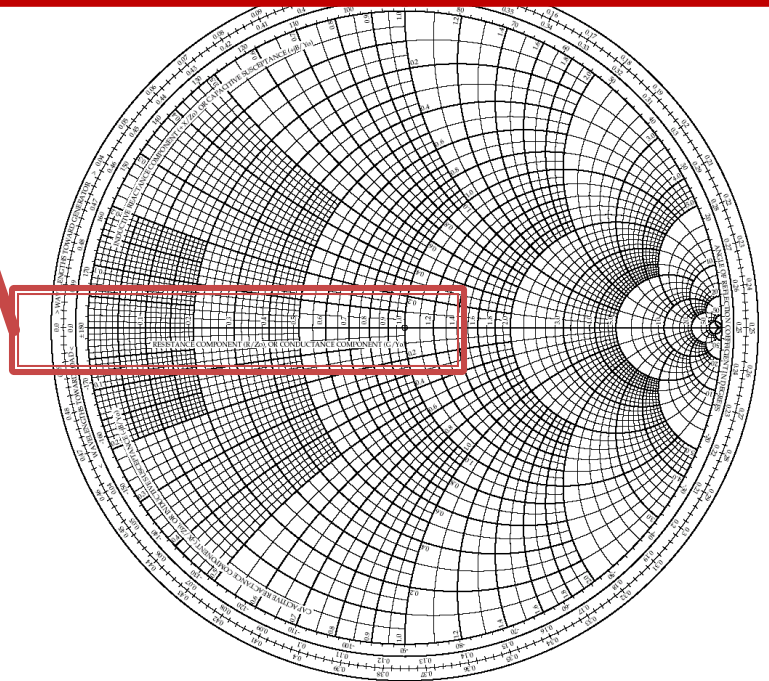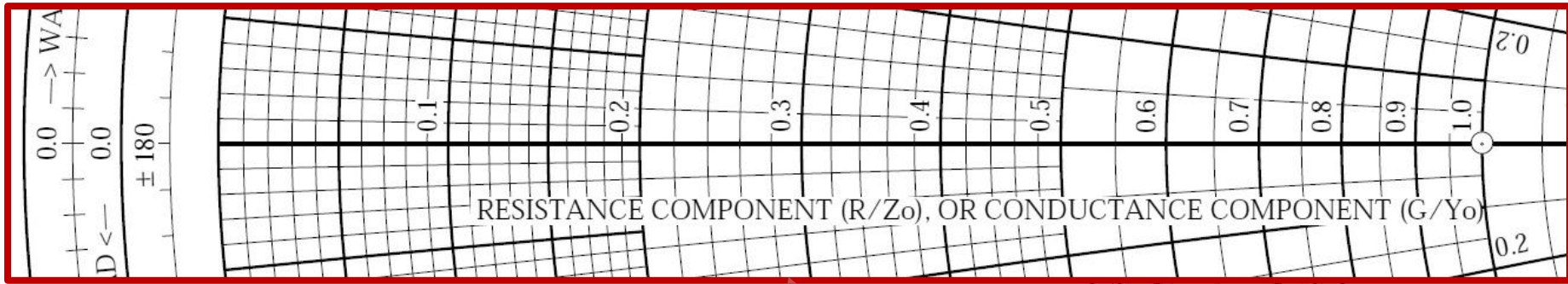

# The Smith Chart

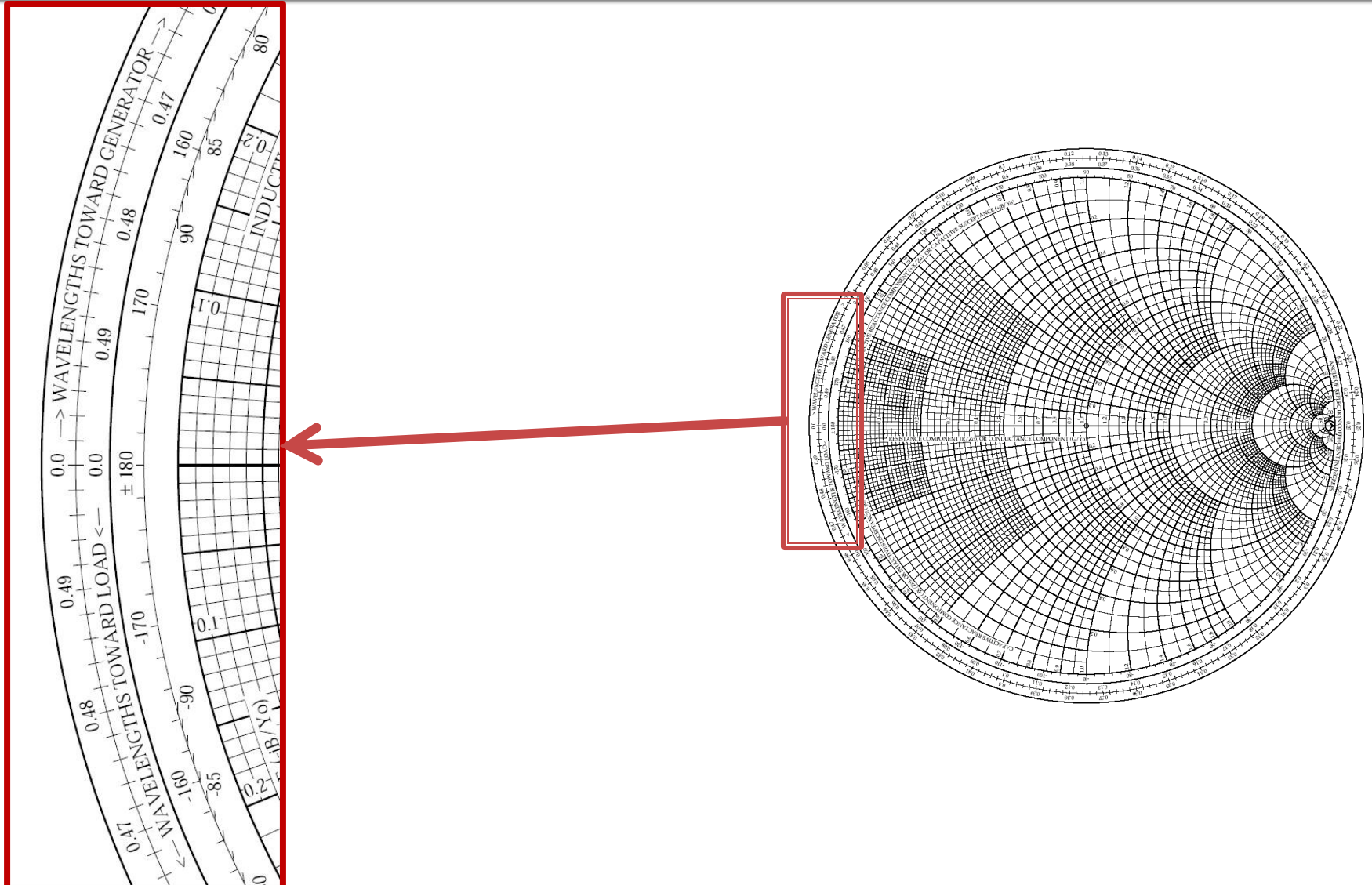


# The Smith Chart

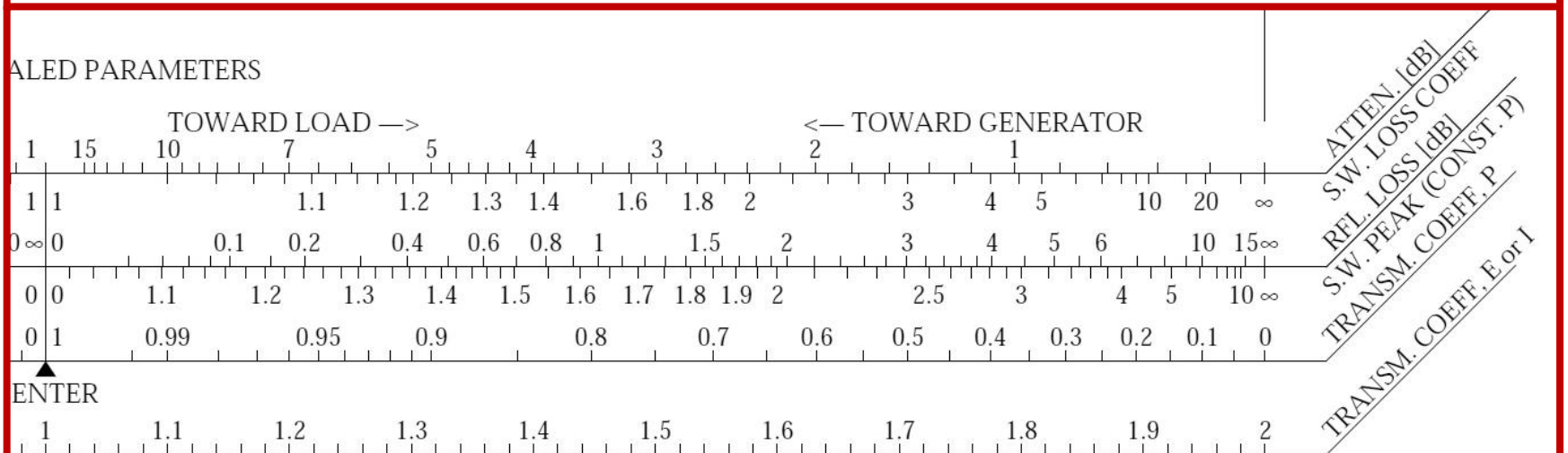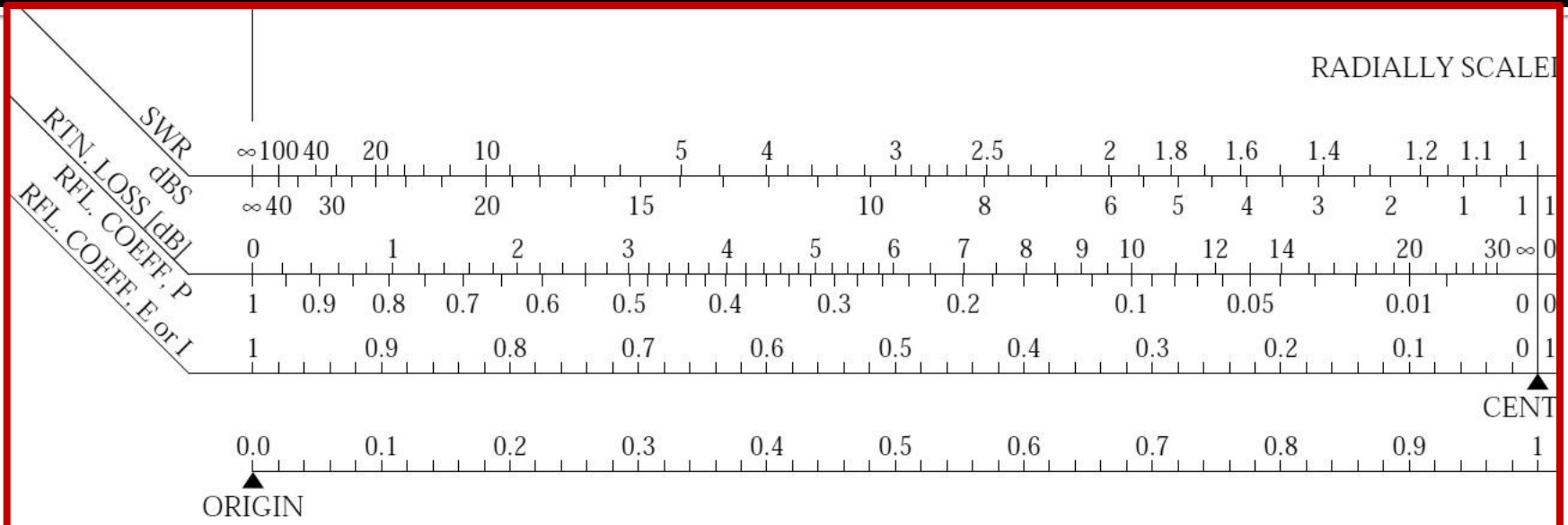





# The Smith Chart

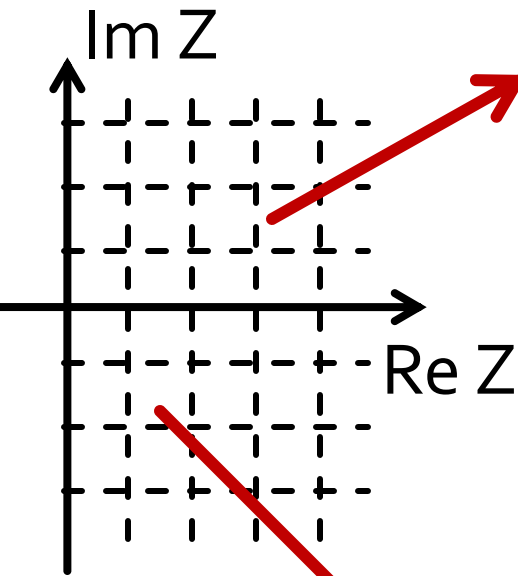
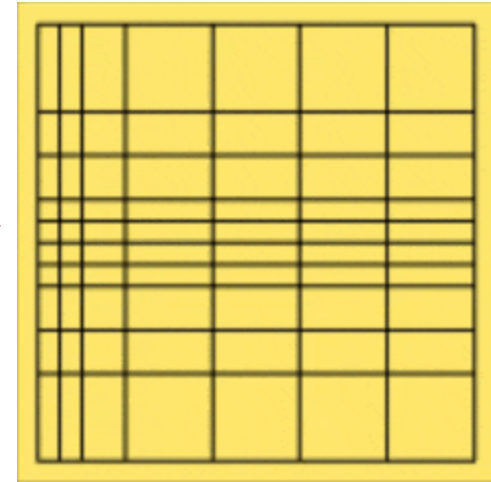
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$



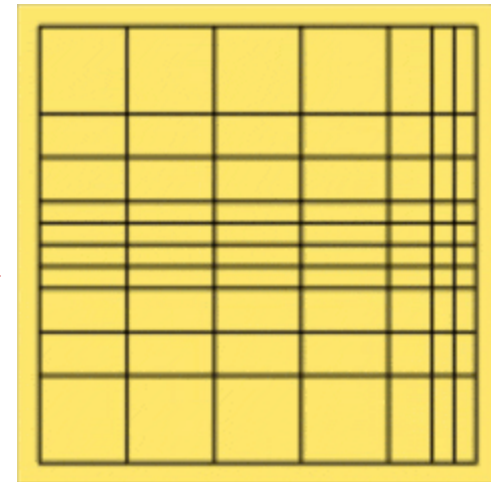
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Y_0 - Y_L}{Y_0 + Y_L} = \frac{1 - y_L}{1 + y_L}$$


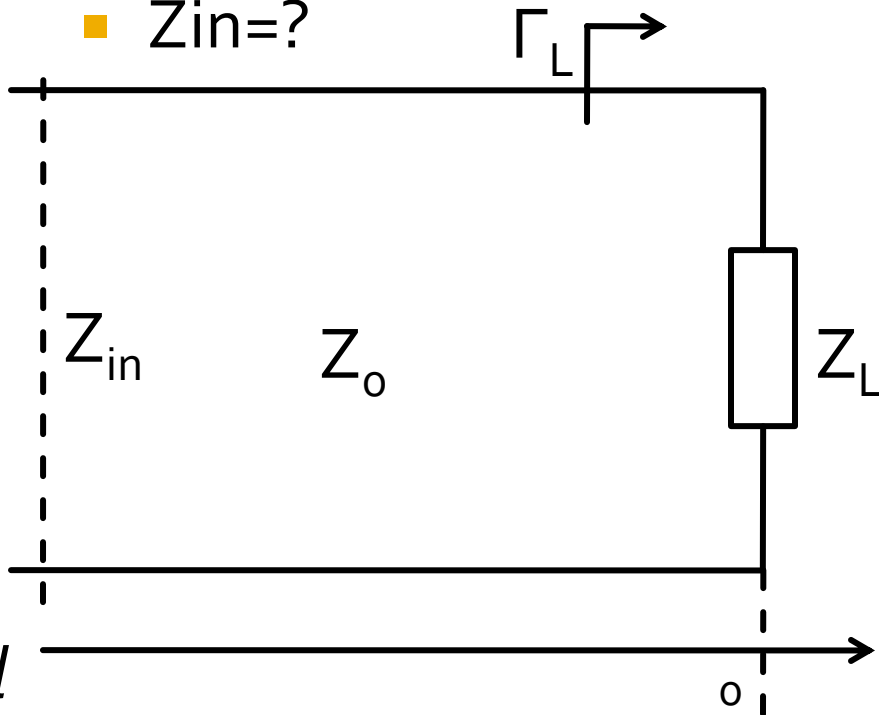
# Traditional usage

- transmission line
  - $100\Omega$  characteristic impedance
  - $0.3\lambda$  length
  - $Z_L = 40\Omega + j \cdot 70\Omega$  load
- $Z_{in} = ?$



$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

$$Z_{in} = 36.5340\Omega - j \cdot 61.1190\Omega$$

# Traditional usage


- transmission line
  - 100Ω impedance
  - 0.3λ length
  - $Z_L = 40\Omega + j \cdot 70\Omega$  load
- normalization with  $Z_0 = 100\Omega$

$$z_L = \frac{Z_L}{Z_0} = 0.4 + j \cdot 0.7$$


- movement with 0.3λ on a line with  $Z_0 = 100\Omega$  (**circle**)

- from  $z_L$  (0.105λ)
- to  $z_{in}$  (0.405λ)

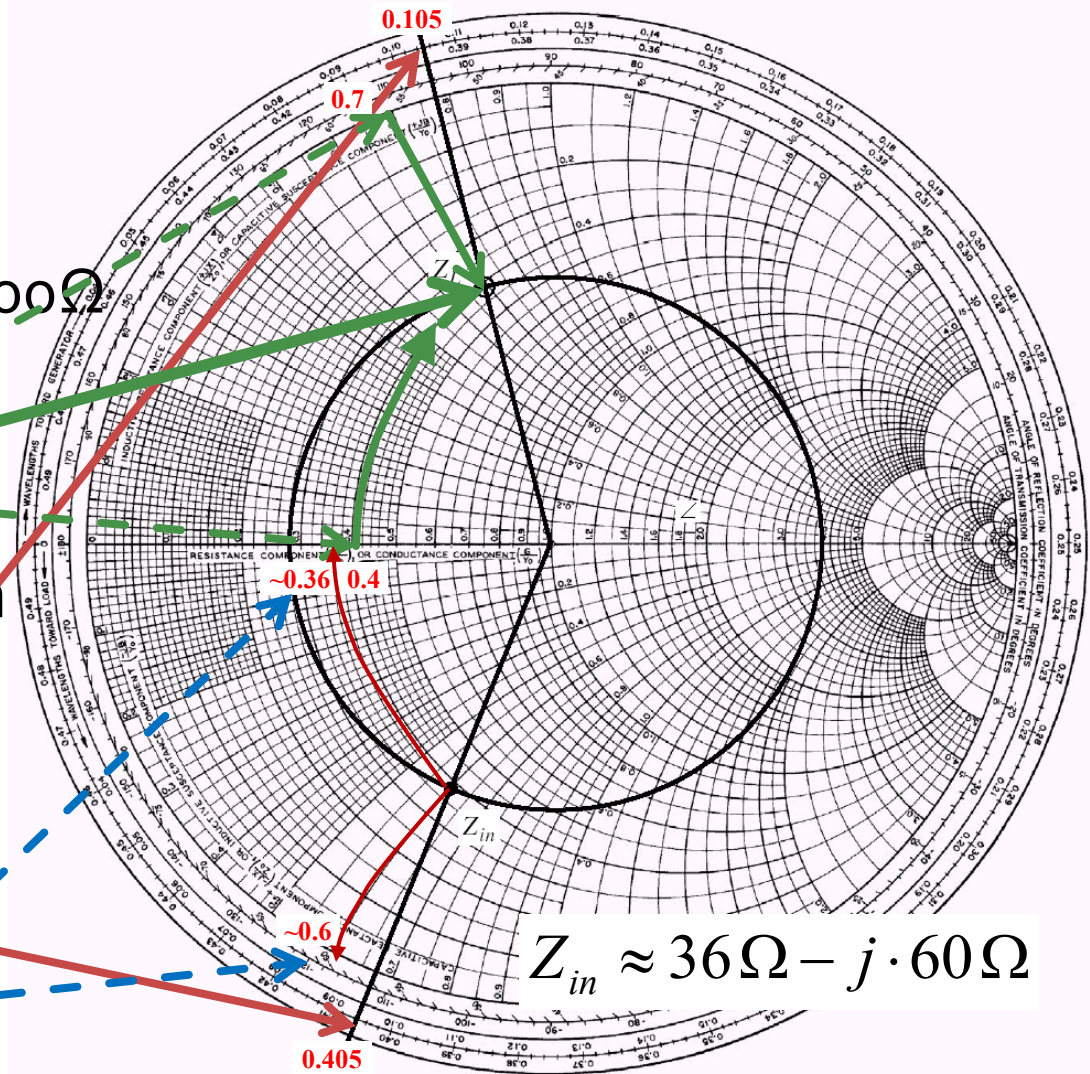
$$z_{in} \approx 0.36 - j \cdot 0.6 = \frac{Z_{in}}{Z_0}$$



# The Smith Chart

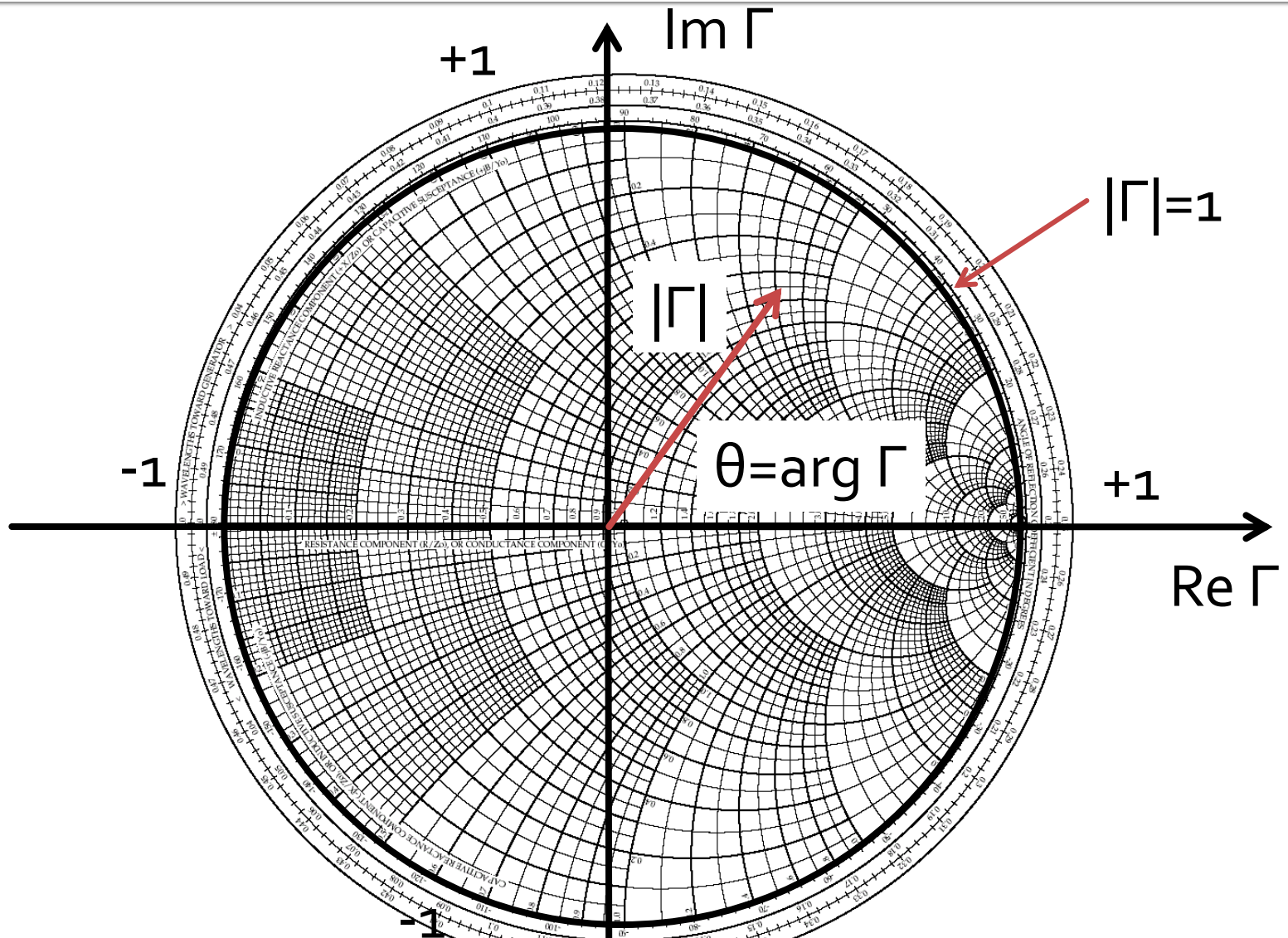

# The Smith Chart

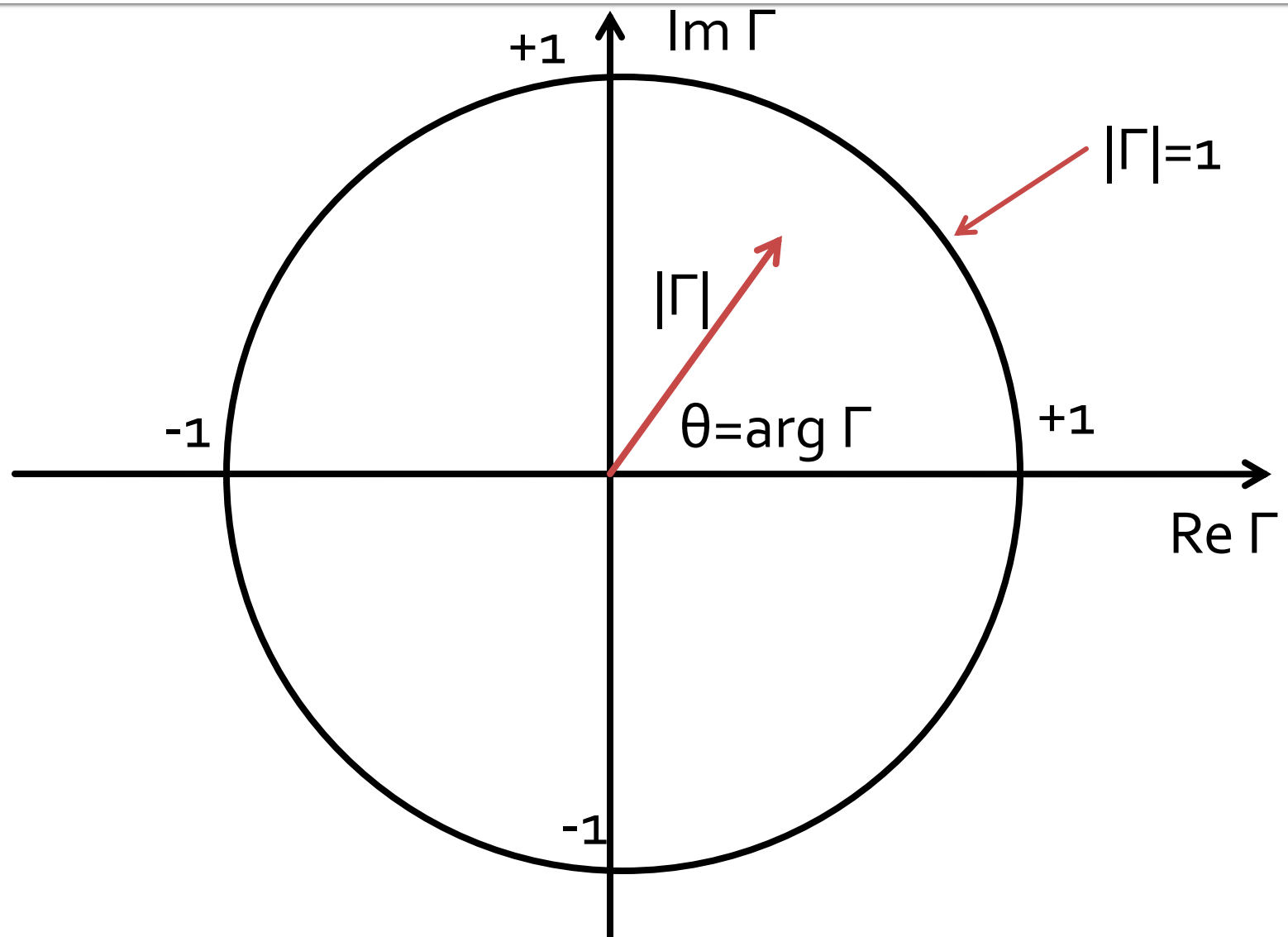




# The Smith Chart

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$


$$z_L = r_L + j \cdot x_L$$

$$r_L = ct.$$


$$x_L = ct.$$

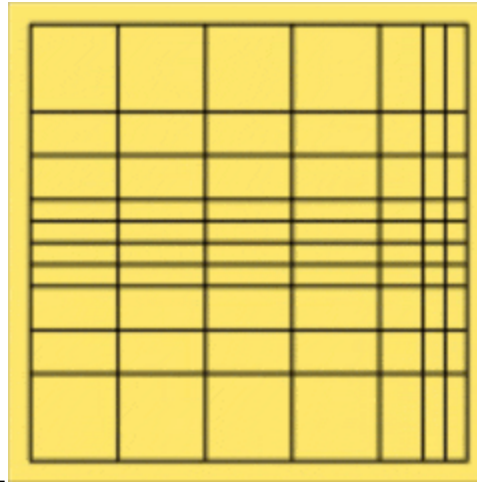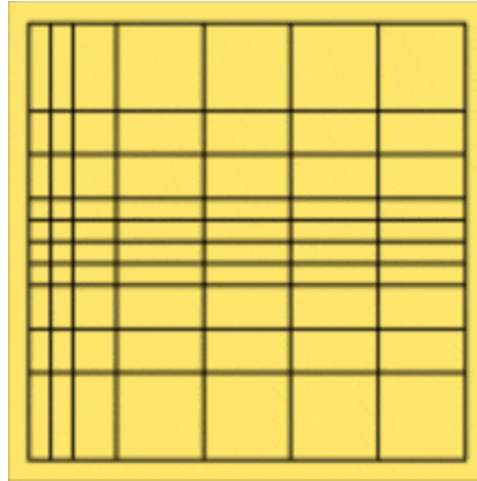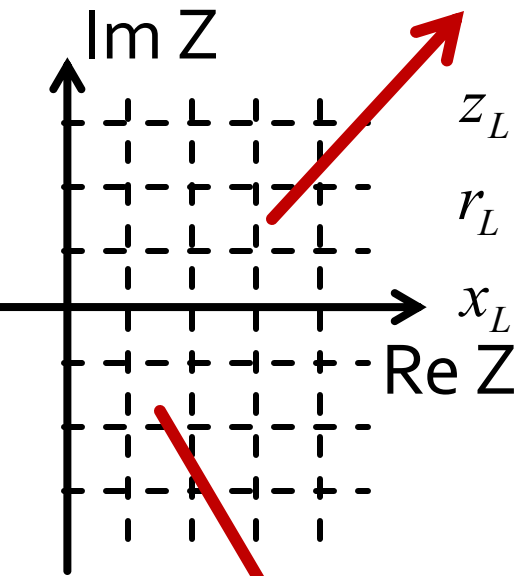
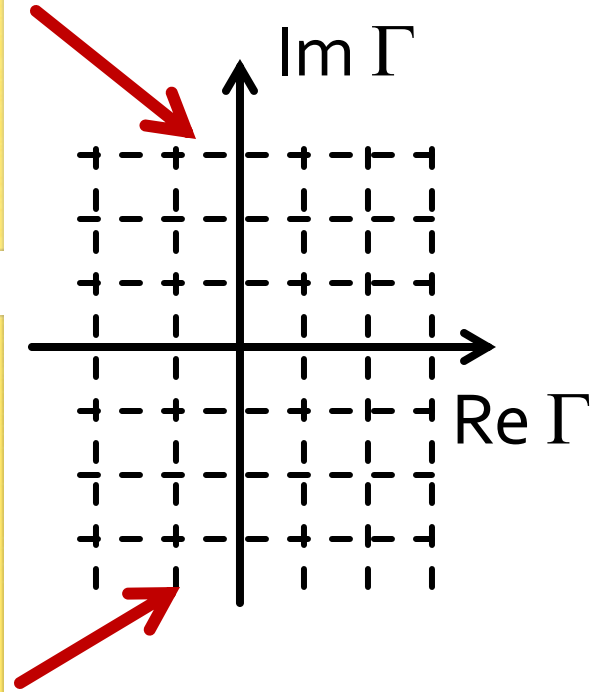
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Y_0 - Y_L}{Y_0 + Y_L} = \frac{1 - y_L}{1 + y_L}$$



# The Smith Chart

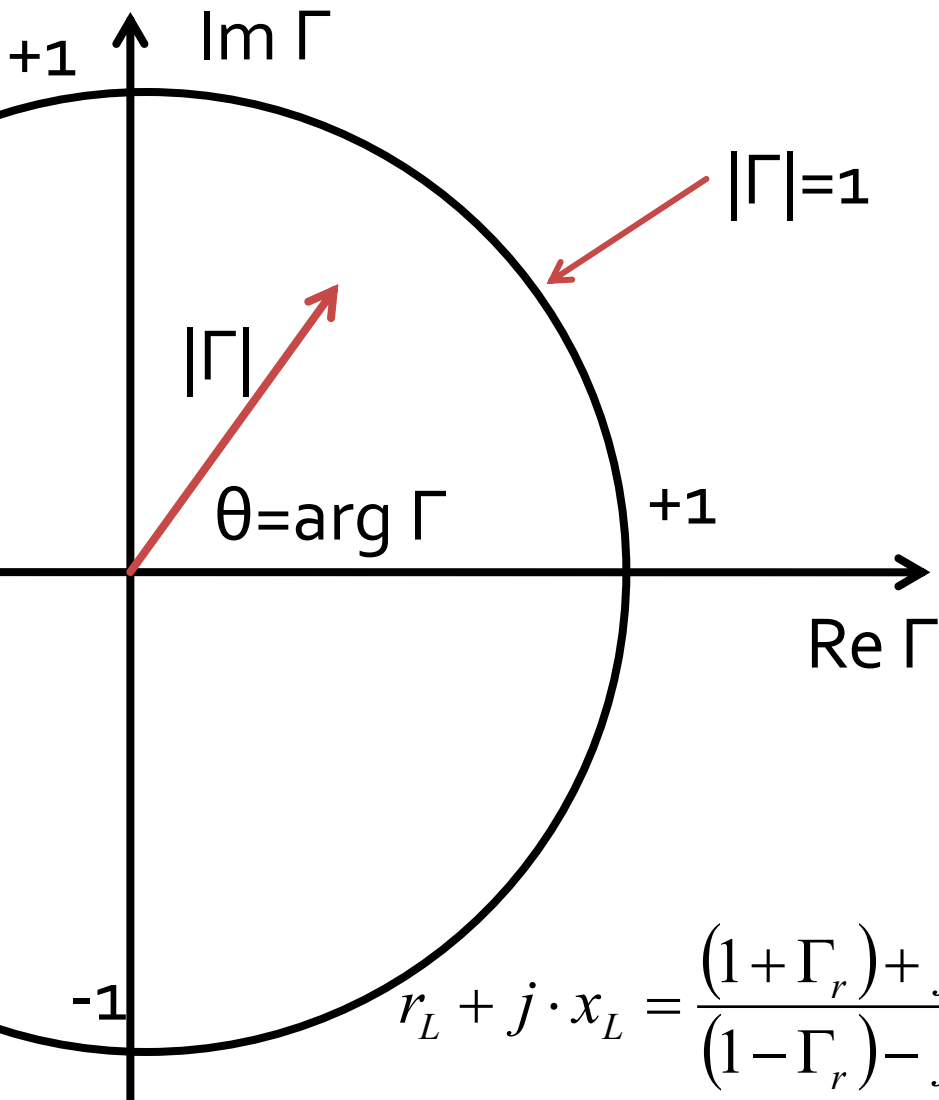

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1} = |\Gamma| \cdot e^{j\theta}$$

$$z_L = \frac{Z_L}{Z_0} \quad y_L = \frac{Y_L}{Y_0} = \frac{Z_0}{Z_L}$$


normalization  $Z_L \rightarrow z_L$  allows using the same chart for any reference impedance  $Z_0$  (the plot becomes independent of the chosen  $Z_0$ )

$$\Gamma = \Gamma_r + j \cdot \Gamma_i$$

$$z_L = \frac{1 + |\Gamma| \cdot e^{j\theta}}{1 - |\Gamma| \cdot e^{j\theta}} = r_L + j \cdot x_L$$

$$r_L + j \cdot x_L = \frac{(1 + \Gamma_r) + j \cdot \Gamma_i}{(1 - \Gamma_r) - j \cdot \Gamma_i} = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} + j \cdot \frac{2 \cdot \Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

# The Smith Chart

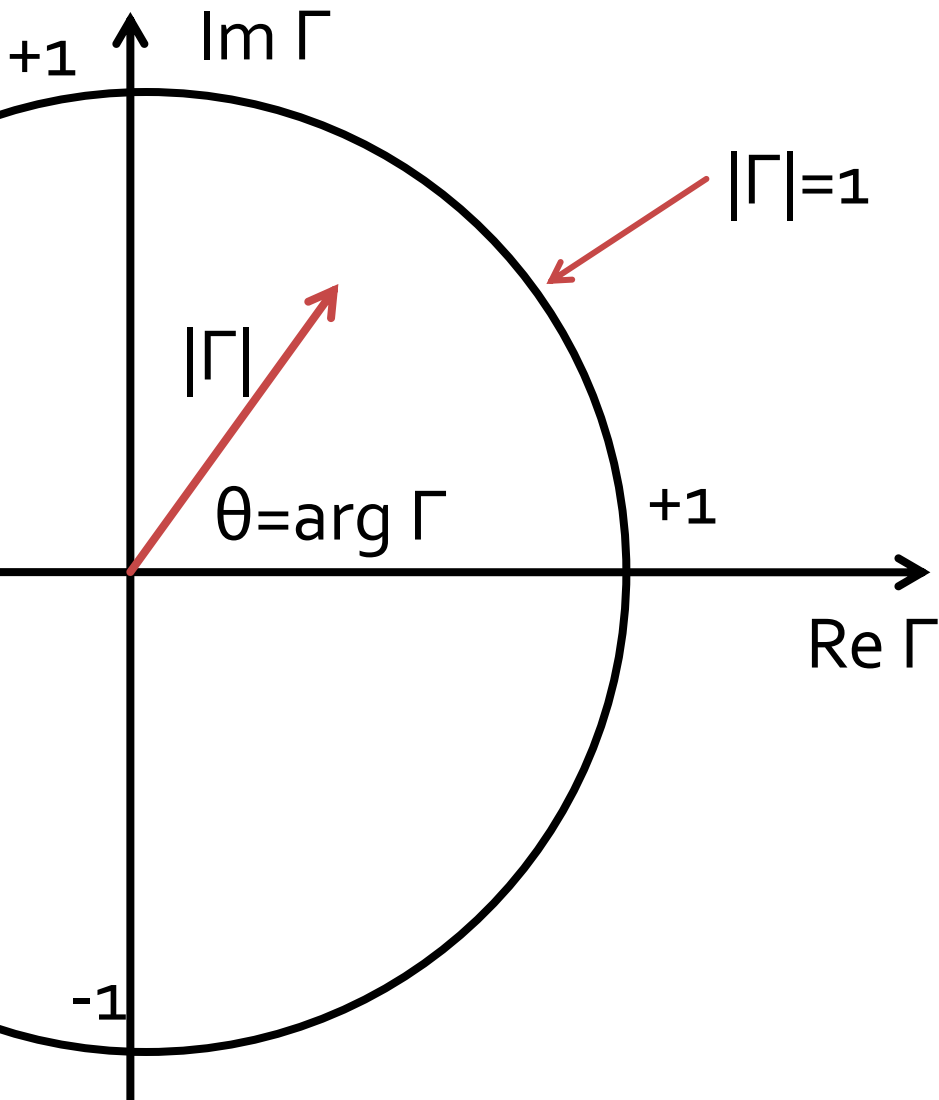

$$r_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$


$$x_L = \frac{2 \cdot \Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

■ Rearranged


$$\left( \Gamma_r - \frac{r_L}{1 + r_L} \right)^2 + \Gamma_i^2 = \left( \frac{1}{1 + r_L} \right)^2$$

$$(\Gamma_r - 1)^2 + \left( \Gamma_i - \frac{1}{x_L} \right)^2 = \left( \frac{1}{x_L} \right)^2$$

# The Smith Chart

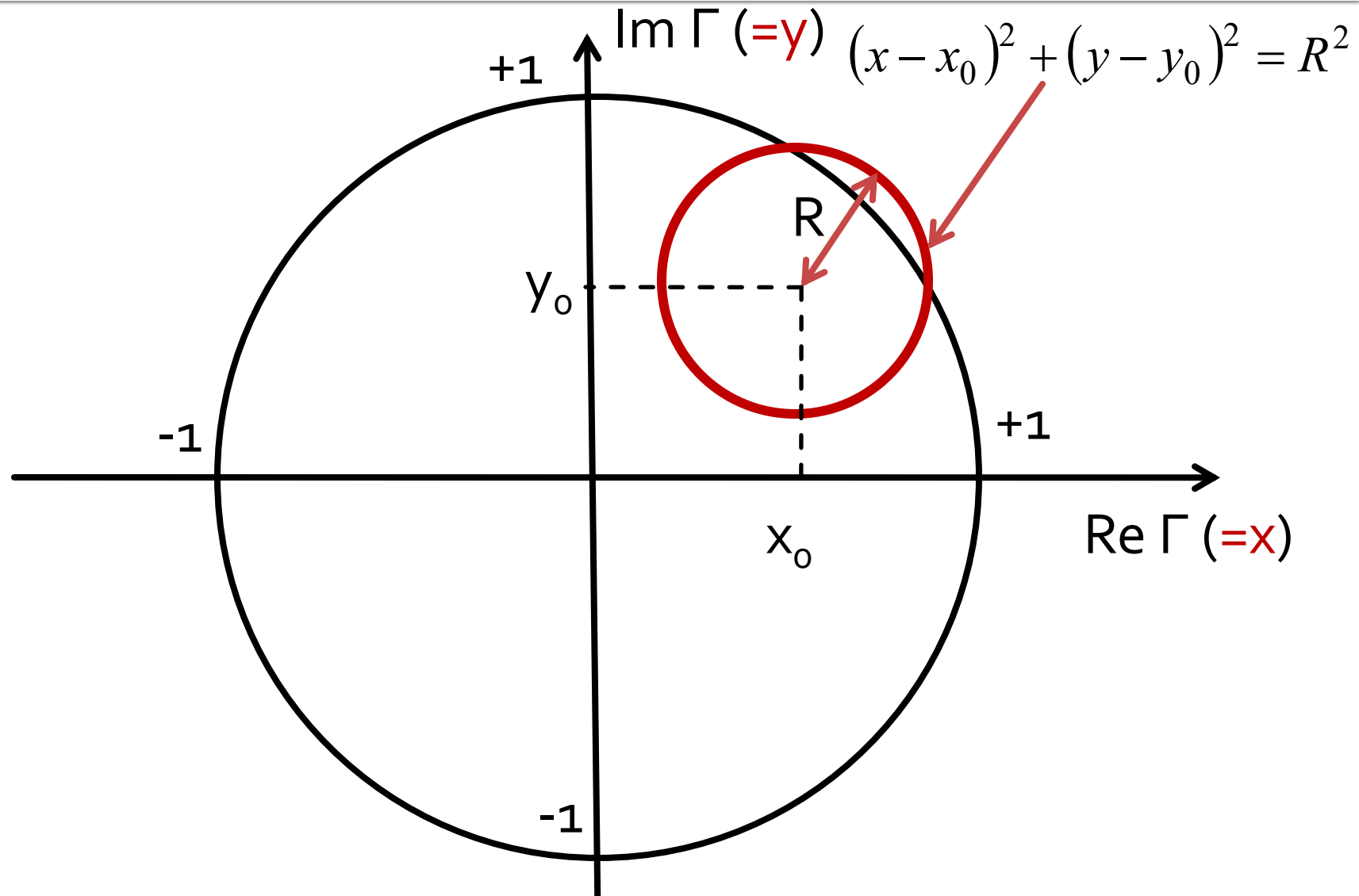

# The Smith Chart

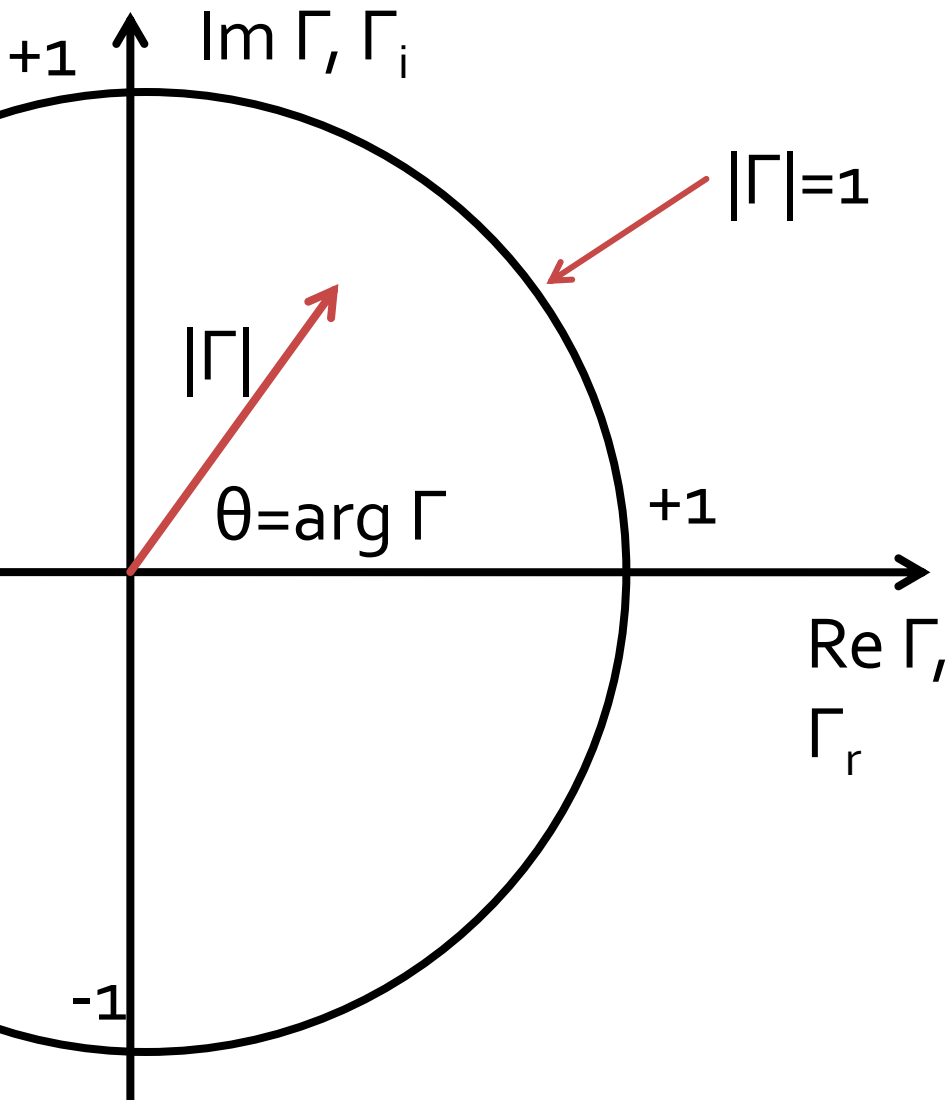

$$\left( \Gamma_r - \frac{r_L}{1+r_L} \right)^2 + \Gamma_i^2 = \left( \frac{1}{1+r_L} \right)^2$$

$$(\Gamma_r - 1)^2 + \left( \Gamma_i - \frac{1}{x_L} \right)^2 = \left( \frac{1}{x_L} \right)^2$$

- **Circles** in the  $(\Gamma_r, \Gamma_i)$  complex plane

$$(x - x_0)^2 + (y - y_0)^2 = R^2$$

# The Smith Chart, resistance

$$\left( \Gamma_r - \frac{r_L}{1+r_L} \right)^2 + \Gamma_i^2 = \left( \frac{1}{1+r_L} \right)^2$$

$$(x - x_0)^2 + (y - y_0)^2 = R^2$$

$$\begin{cases} x_0 = \frac{r_L}{1+r_L} \\ y_0 = 0 \\ R = \frac{1}{1+r_L} \end{cases}$$

- The locus (the set of all points whose location satisfies one or more specified conditions) of the points generated by all impedances having normalized resistance  $r_L$  is a circle which:

- have its **center on the horizontal axis** ( $y_0=0$ )

- passes through the point  **$x=1, y=0$** , whatever  $x_0, r_L$

- have its radius between 0 and 1

- tends to 0 for large  $r_L$

- tends to 1 for small  $r_L$


- when  $r_L$  is **1** passes also through **origin**

- for any **positive**  $r_L$  radius is **<1**

$$\left( 1 - \frac{r_L}{1+r_L} \right)^2 + 0 = \left( \frac{1}{1+r_L} \right)^2$$

$$\left( 0 - \frac{r_L}{1+r_L} \right)^2 = \left( \frac{1}{1+r_L} \right)^2 \leftrightarrow r_L = 1$$

# The Smith Chart, resistance

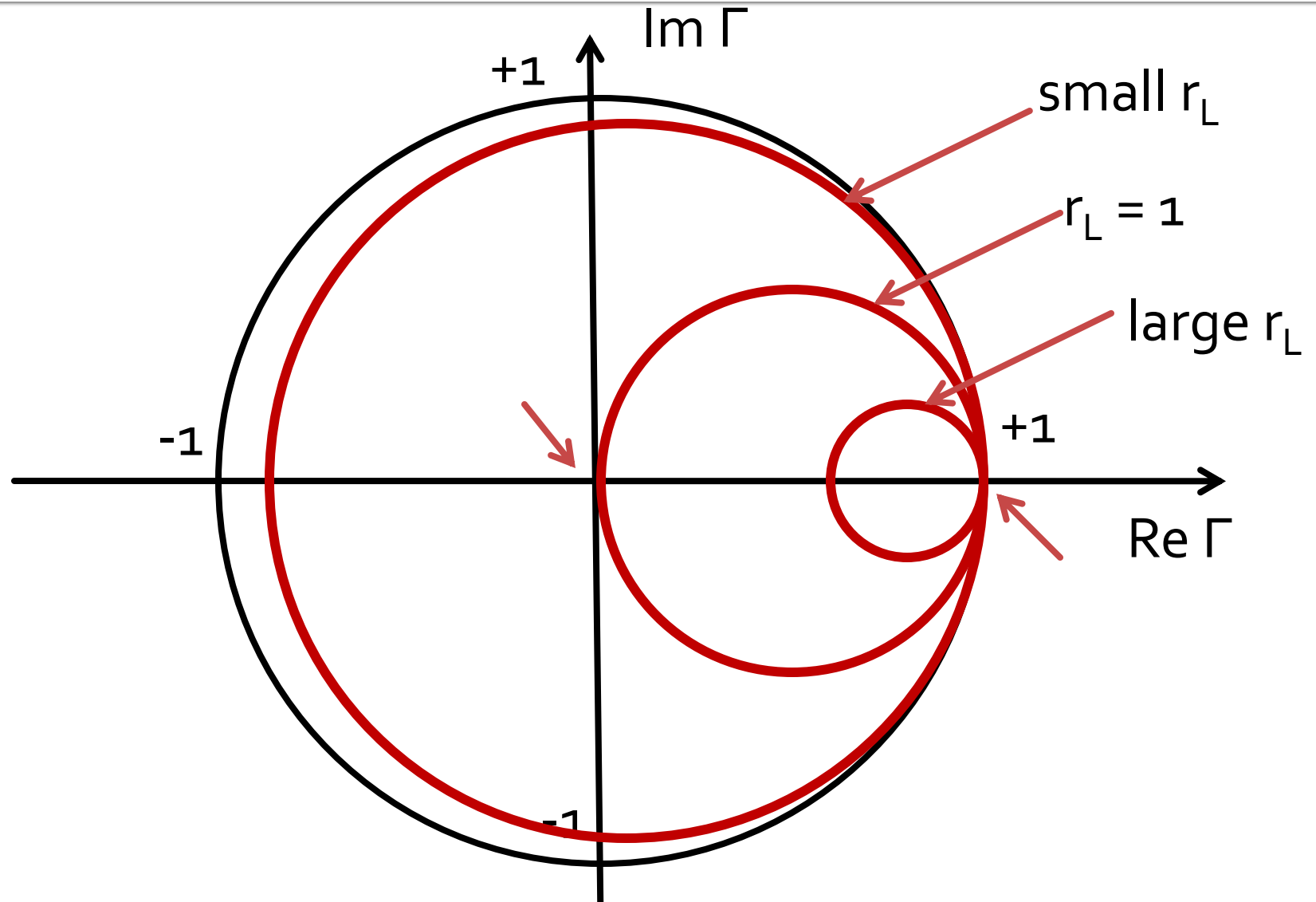

# The Smith Chart, reactance

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L}\right)^2 = \left(\frac{1}{x_L}\right)^2$$

$$(x - x_0)^2 + (y - y_0)^2 = R^2$$

$$\left\{ \begin{array}{l} x_0 = 1 \\ y_0 = \frac{1}{x_L} \\ R = \frac{1}{|x_L|} \end{array} \right.$$

- The locus of the points generated by all impedances having normalized resistance  $x_L$  is a circle which:

- have its **center on a line parallel with the vertical axis** ( $x_0=1$ )

- passes through  **$x=1, y=0$**  point, whatever  $x_0, x_L$

- have its radius between 0 and  $\infty$

- tends to 0 for large  $|x_L|$


- tends to  $\infty$  for small  $|x_L|$

$$(1-1)^2 + \left(0 - \frac{1}{x_L}\right)^2 = \left(\frac{1}{x_L}\right)^2$$


- when  $x_L$  is **o** transforms itself in the **horizontal axis**

- if  $x_L > 0$  the circle is above the horizontal axis, otherwise is below it


# The Smith Chart, reactance

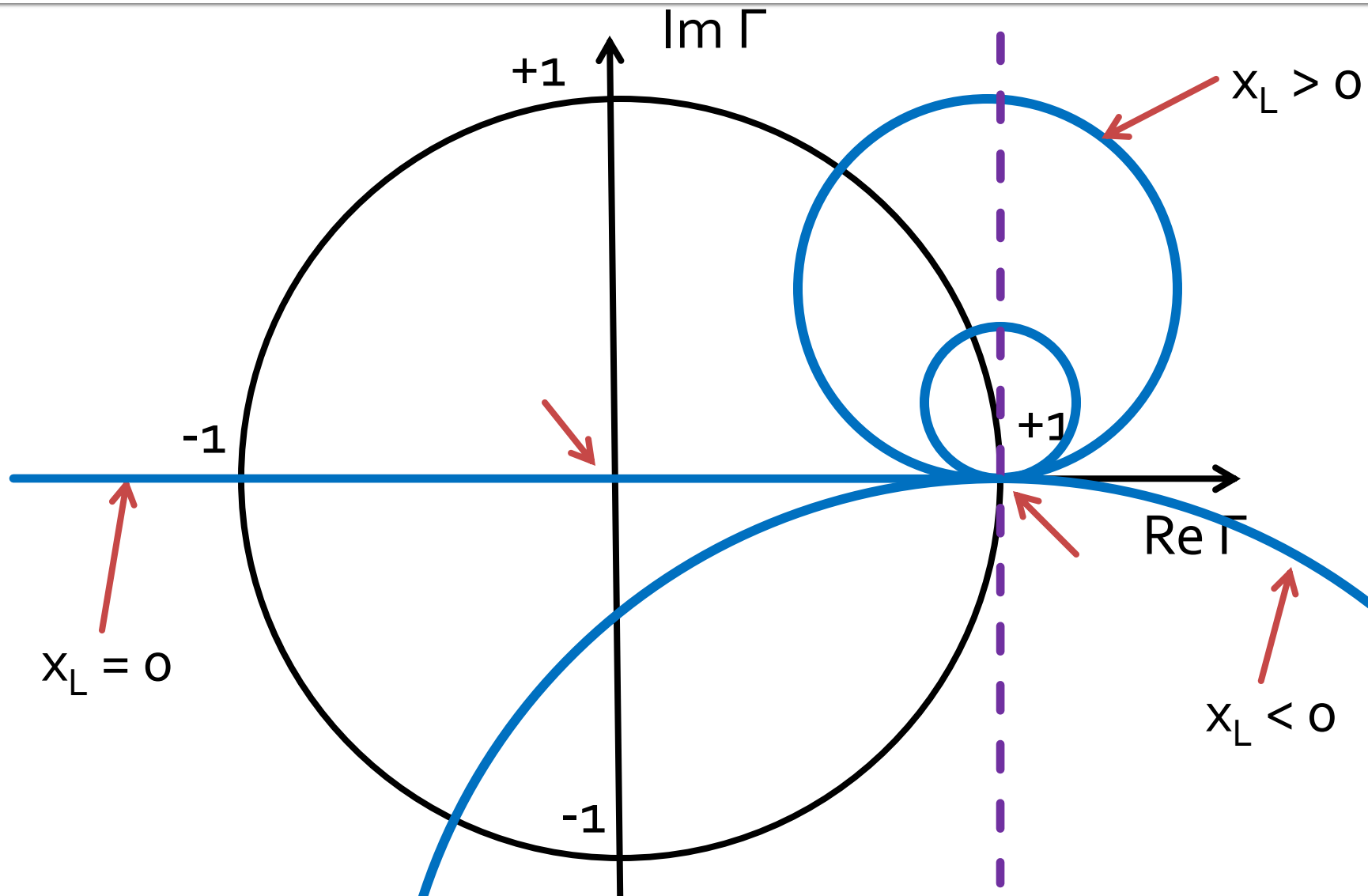


# The Smith Chart, impedance

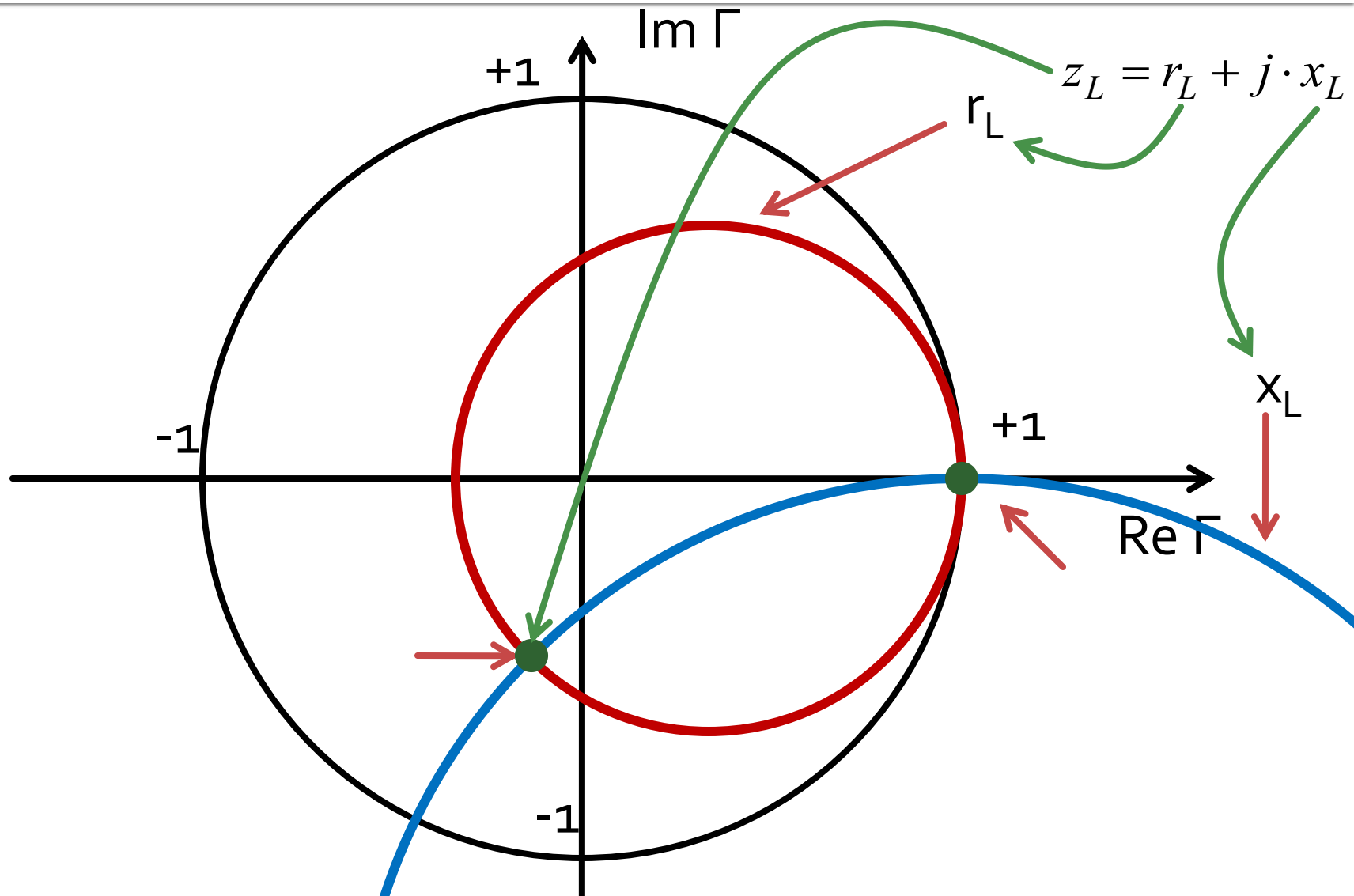
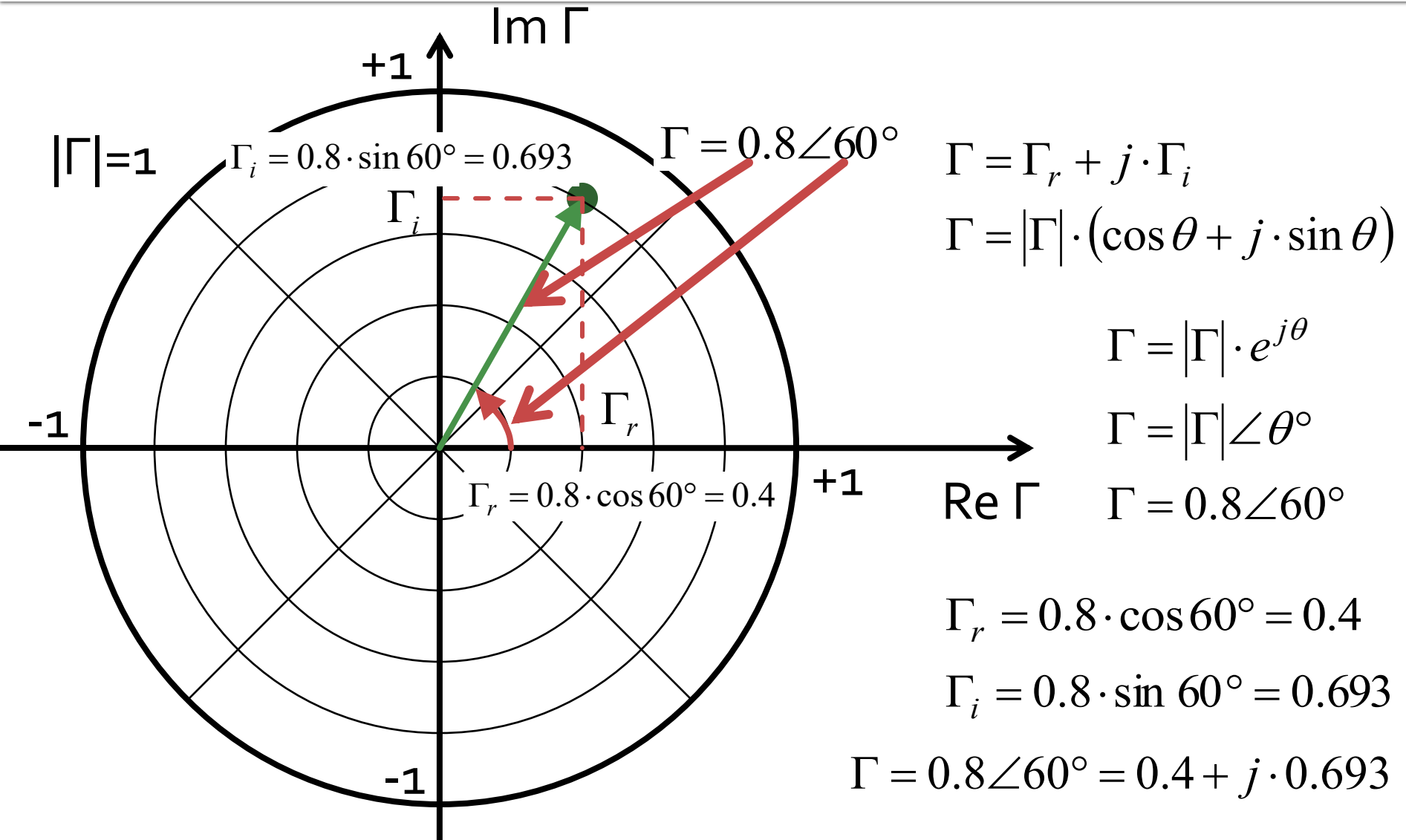
# The Smith Chart, reflection coefficient, Cartesian coordinate system


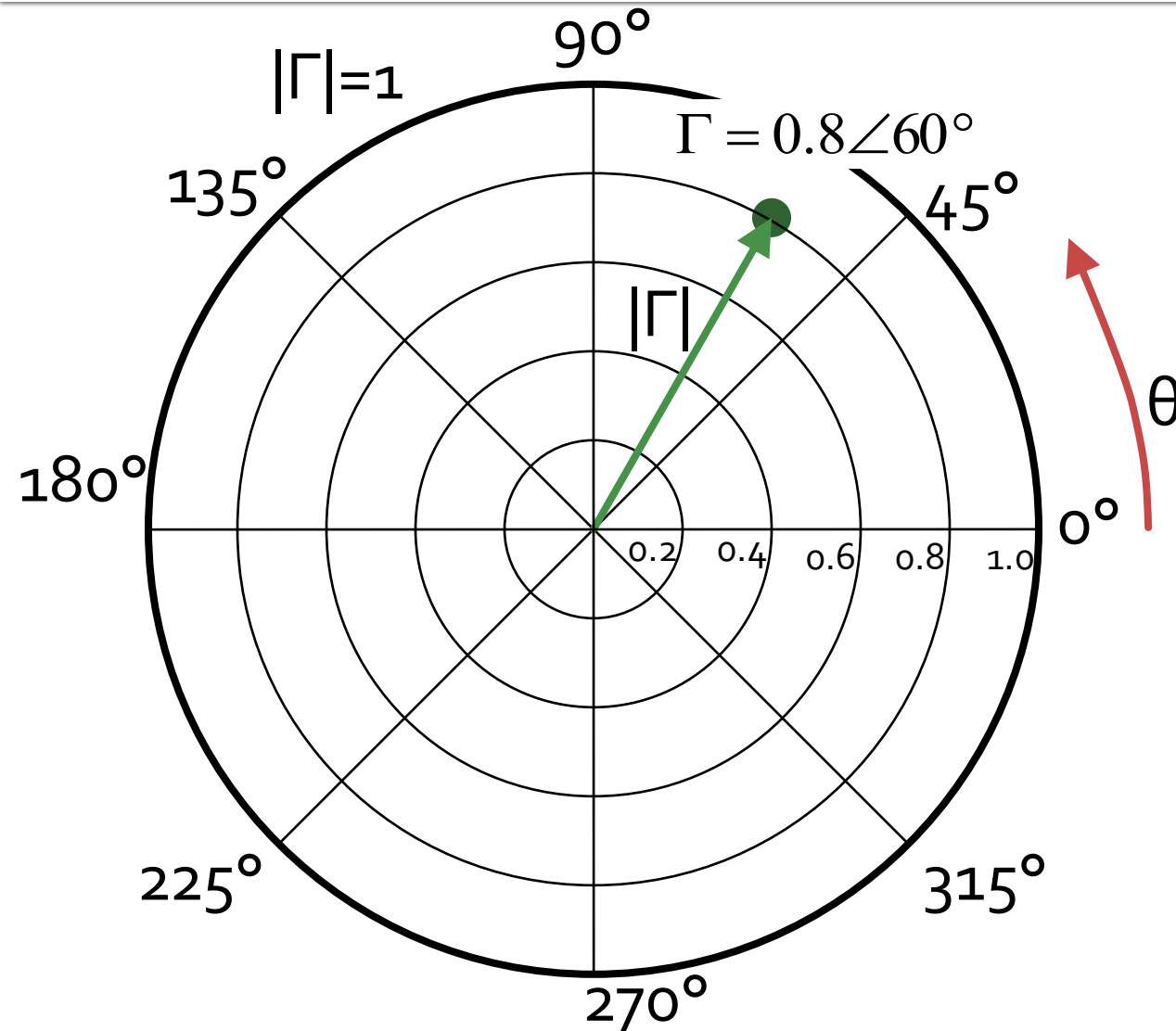
# The Smith Chart, reflection coefficient, Polar coordinate system



$$\Gamma = \Gamma_r + j \cdot \Gamma_i$$

$$\Gamma = |\Gamma| \cdot (\cos \theta + j \cdot \sin \theta)$$

$$\Gamma = |\Gamma| \cdot e^{j\theta}$$


$$\Gamma = |\Gamma| \angle \theta^\circ$$

$$\Gamma = 0.8 \angle 60^\circ$$

$$\Gamma_r = 0.8 \cdot \cos 60^\circ = 0.4$$

$$\Gamma_i = 0.8 \cdot \sin 60^\circ = 0.693$$
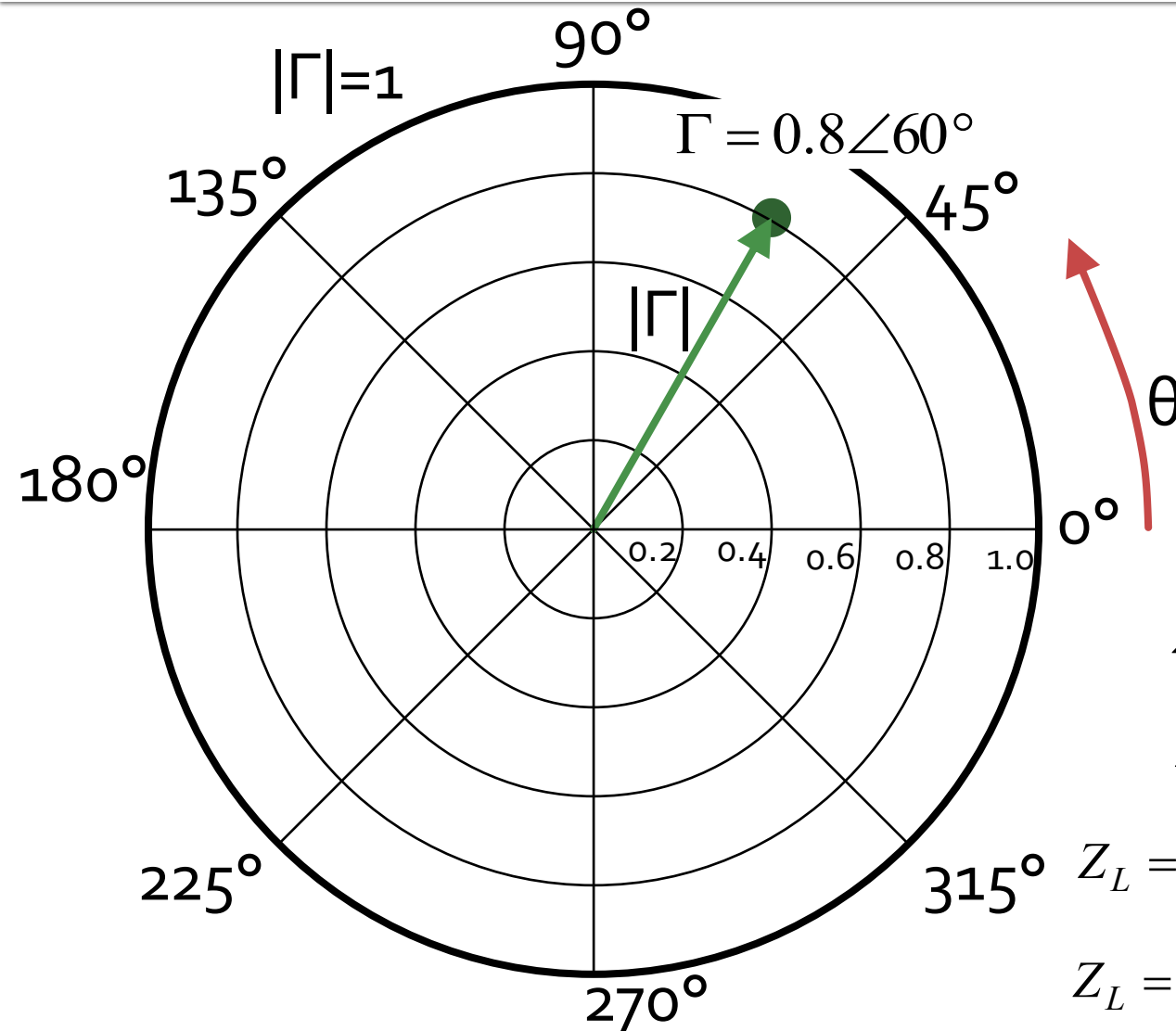
# The Smith Chart, reflection coefficient, impedance



$$\Gamma = |\Gamma| \cdot e^{j\theta}$$

$$\Gamma = |\Gamma| \angle \theta^\circ$$

$$\Gamma = 0.8 \angle 60^\circ$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$

$$z_L = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + 0.8 \angle 60^\circ}{1 - 0.8 \angle 60^\circ}$$


$$z_L = 0.429 + j \cdot 1.65$$

$$Z_L = Z_0 \cdot \frac{1 + \Gamma}{1 - \Gamma} = 50\Omega \cdot \frac{1 + 0.8 \angle 60^\circ}{1 - 0.8 \angle 60^\circ}$$


$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$
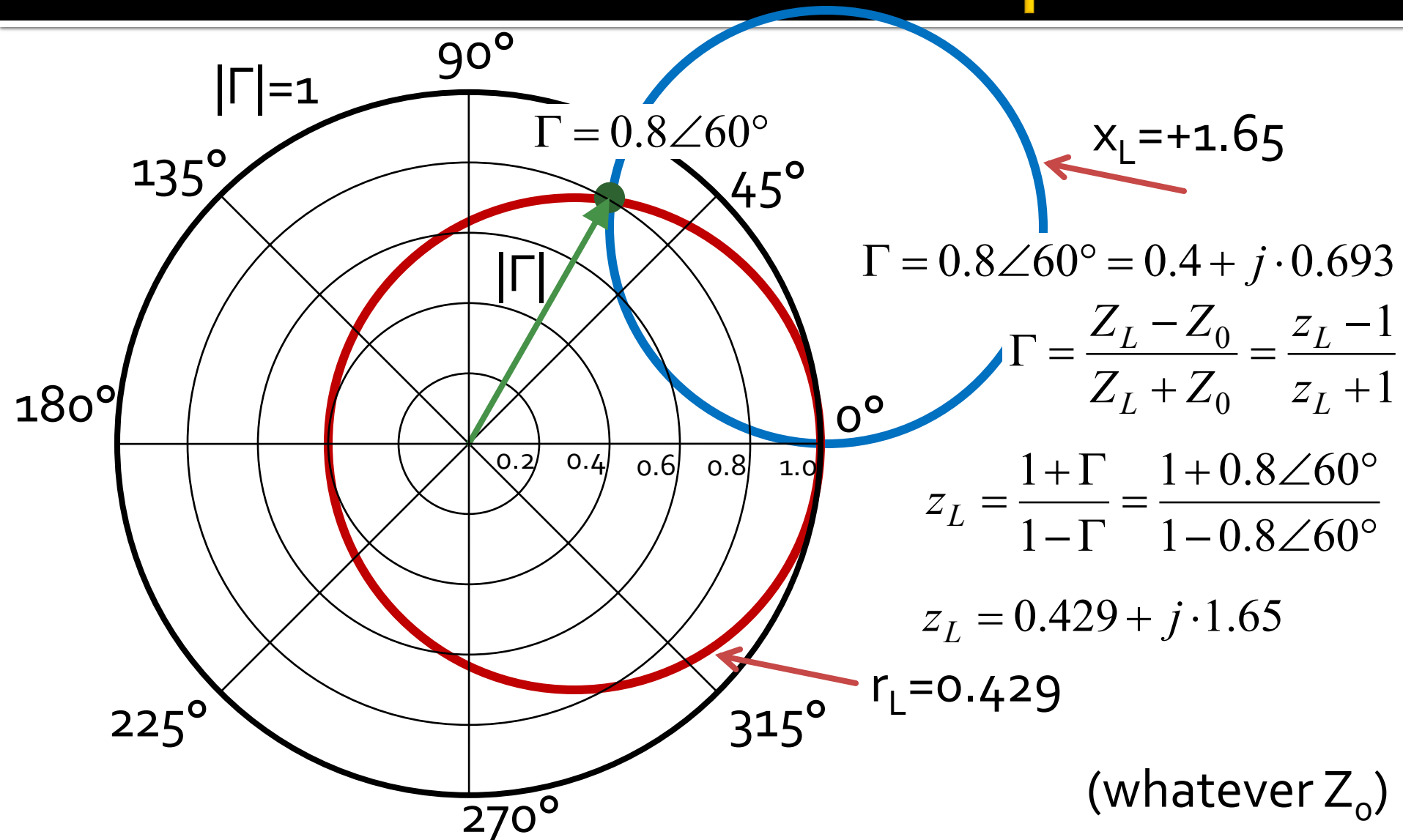
# Equivalence



reflection coefficient  $\Leftrightarrow$  impedance


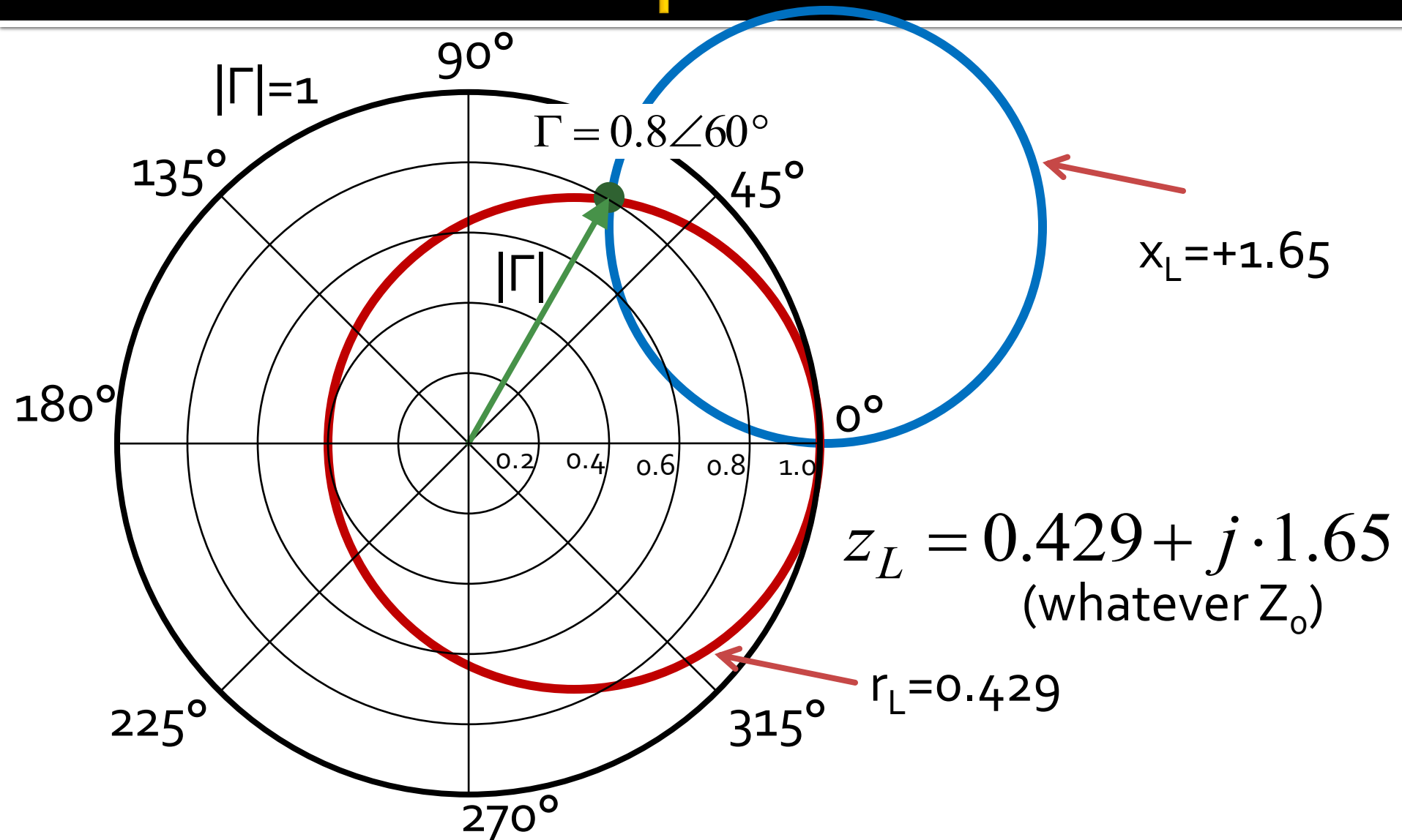
# The Smith Chart, reflection coefficient $\Leftrightarrow$ impedance


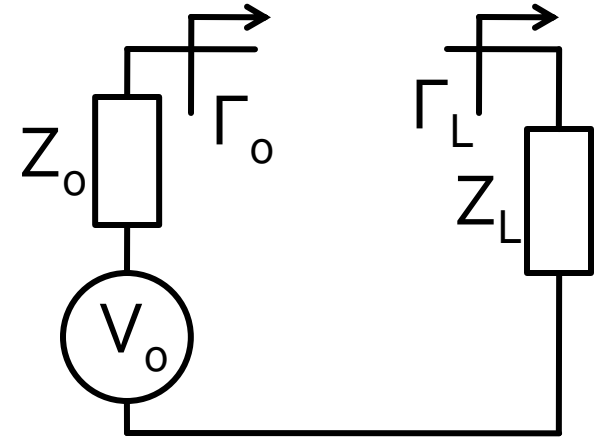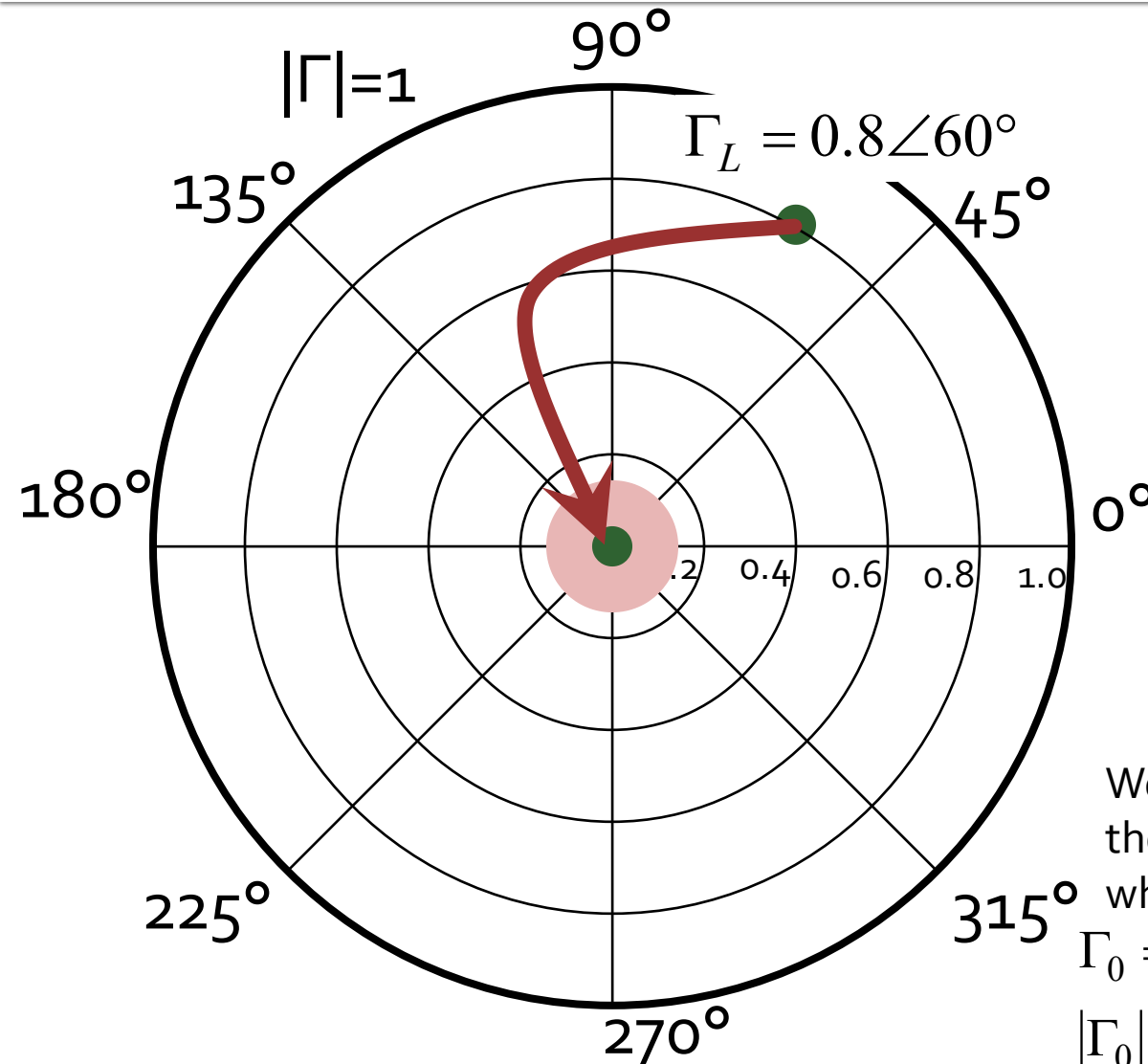
# The Smith Chart, reflection coefficient, matching



Matching  $Z_L$  load to  $Z_o$  source.  
We normalize  $Z_L$  over  $Z_o$

$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

$$z_L = 0.429 + j \cdot 1.65$$

$$\Gamma_L = 0.8 \angle 60^\circ$$


We must move the point denoting the reflection coefficient in the area where with a  $Z_o$  source we have:

$$\Gamma_0 = 0 \quad \text{perfect match} \quad \bullet$$


$$|\Gamma_0| \leq \Gamma_m \quad \text{"good enough" match} \quad \circ$$

# Example

## ■ Laboratory 1

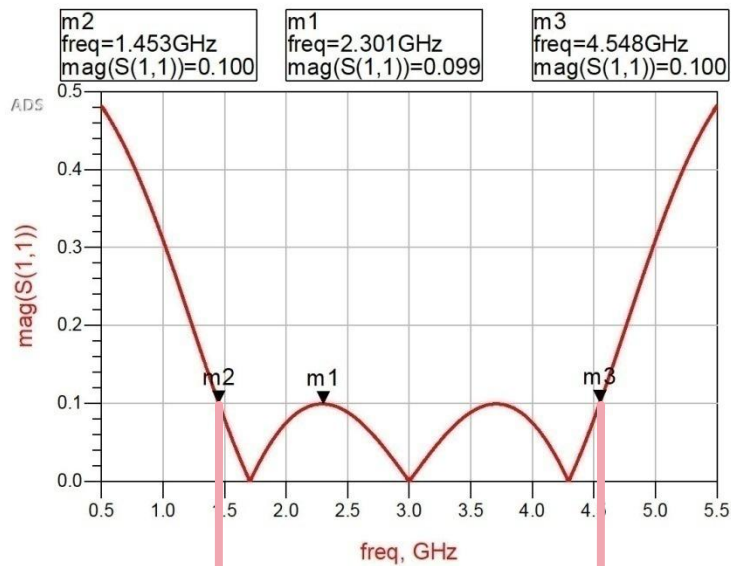


$$|\Gamma_0| \leq \Gamma_m$$

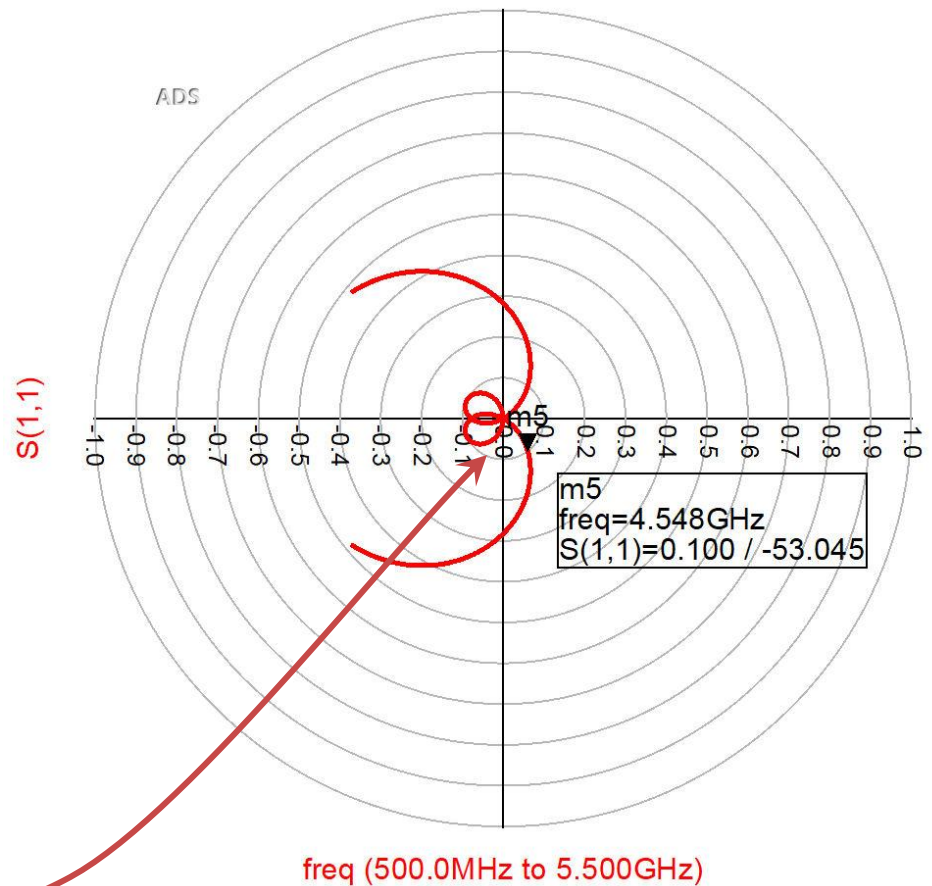


# Example



## ■ Laboratory 1

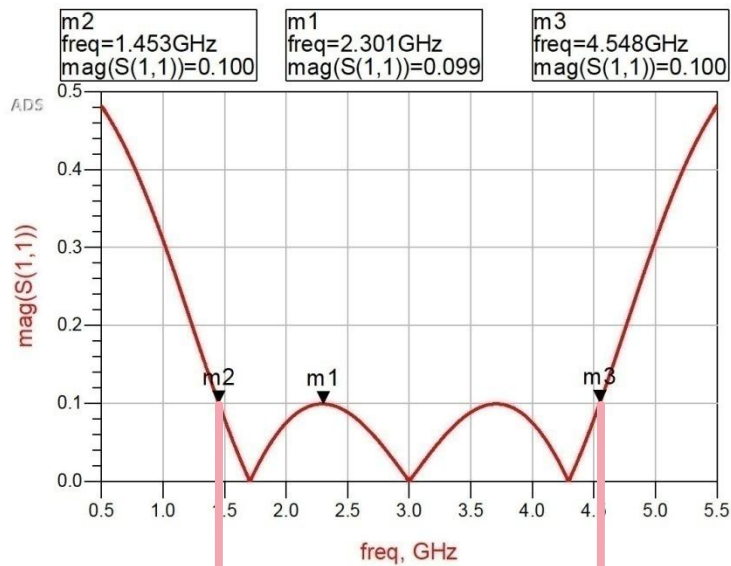

$$|\Gamma_0| \leq \Gamma_m$$

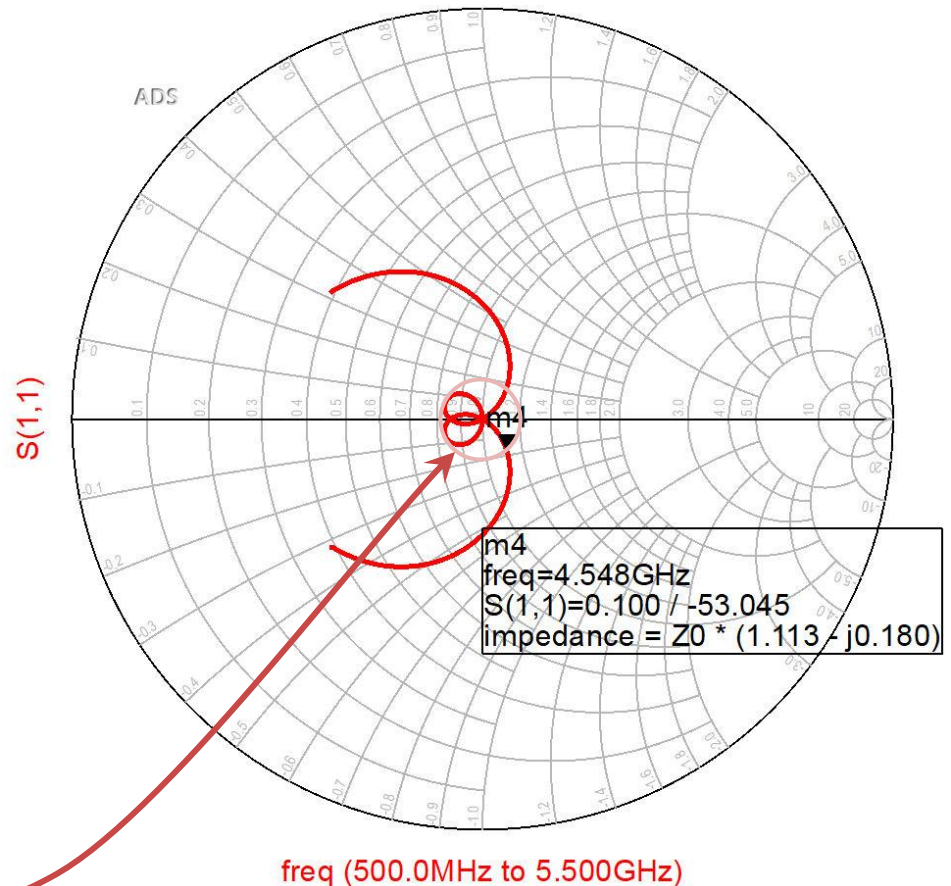
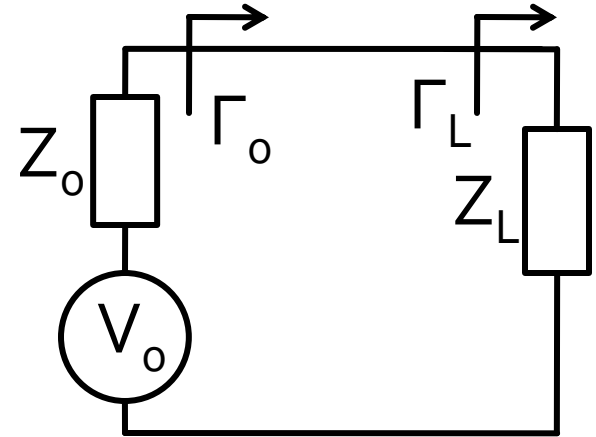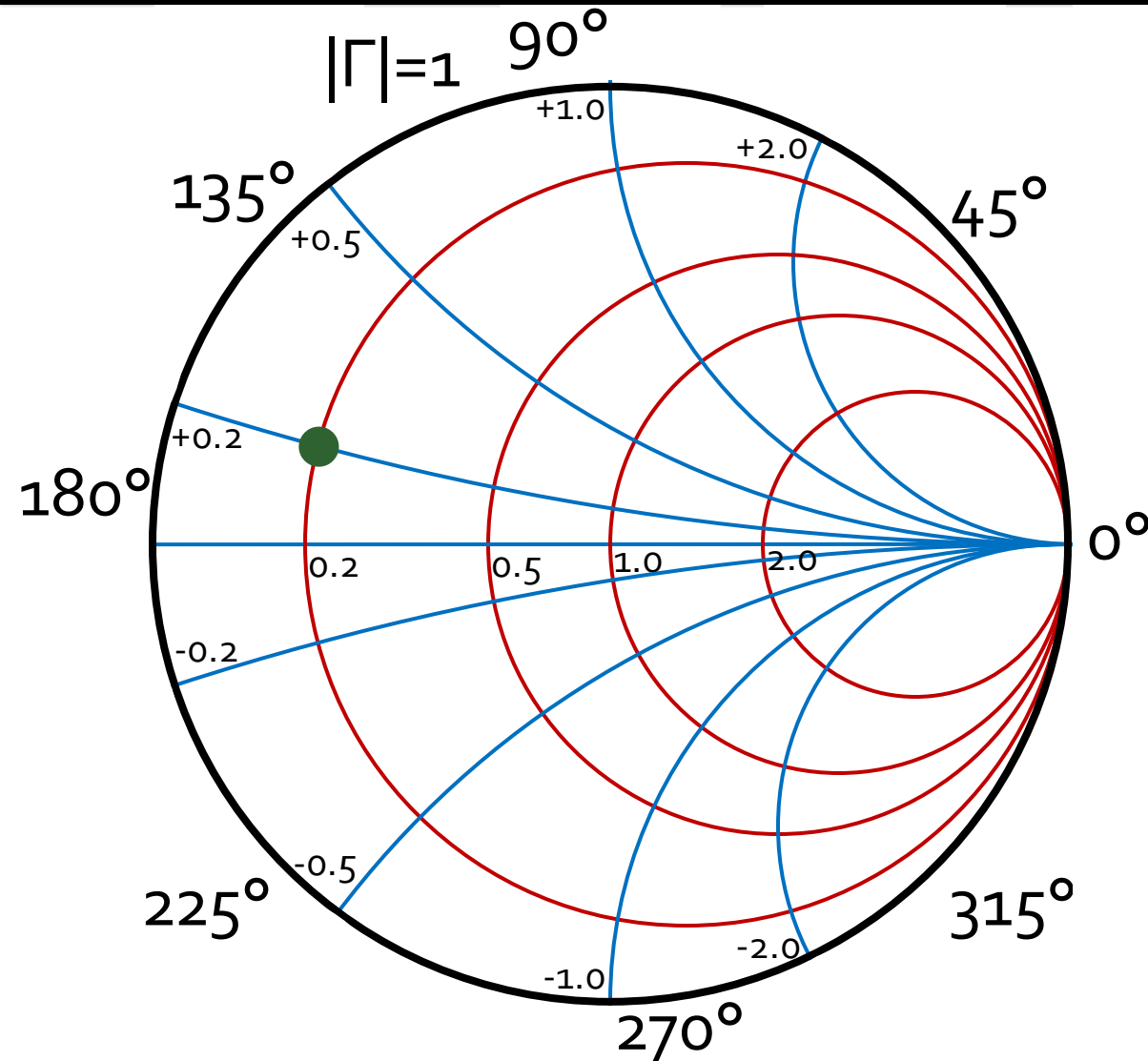
# The Smith Chart, impedance/reflection coefficient





$$Z_0 = 50\Omega$$

$$Z_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = 0.2 + j \cdot 0.2$$

$$\Gamma_L = \Gamma_0 = 0.678 \angle 156.5^\circ$$

# The Smith Chart, series reactance

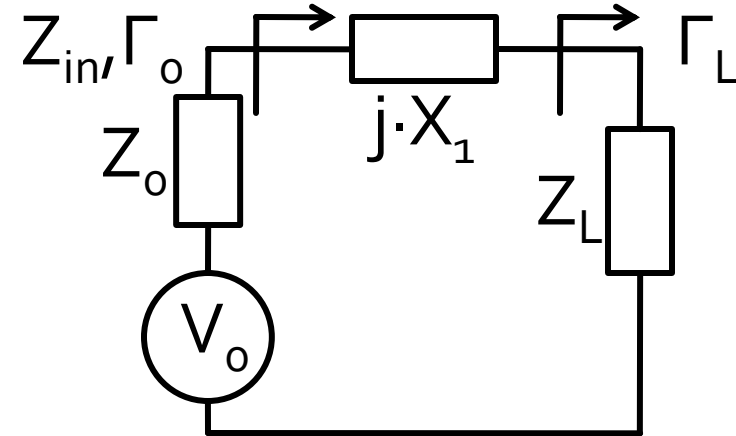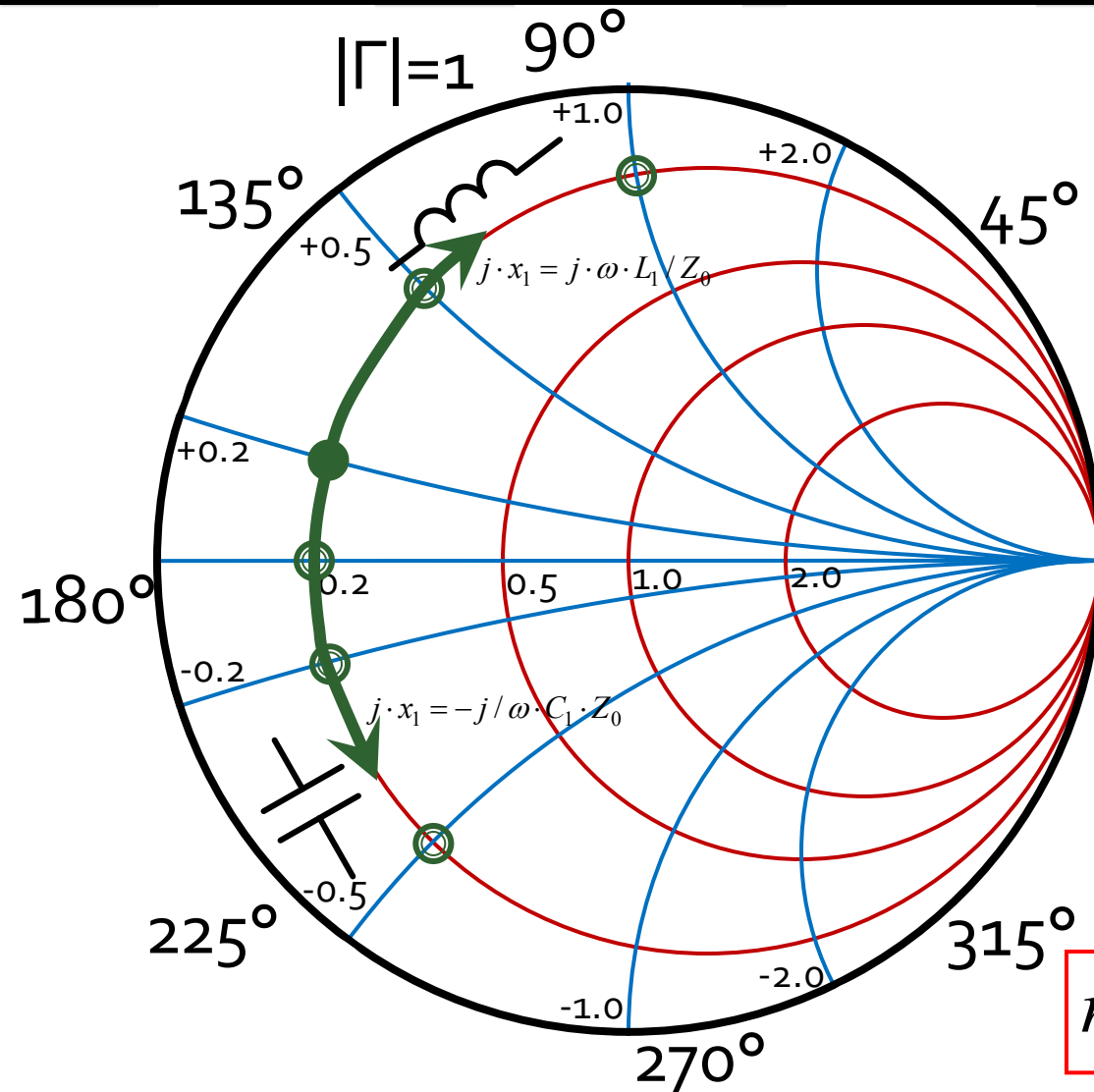

$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$


$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_L + j \cdot X_1 = R_L + j \cdot (X_L + X_1)$$

$$z_{in} = r_L + j \cdot (x_L + x_1)$$

$$r_{in} = r_L \quad \begin{array}{l} j \cdot x_1 = j \cdot \omega \cdot L_1 / Z_0 > 0 \\ j \cdot x_1 = -j / \omega \cdot C_1 \cdot Z_0 < 0 \end{array}$$

# ADS, Smith Chart, series reactance

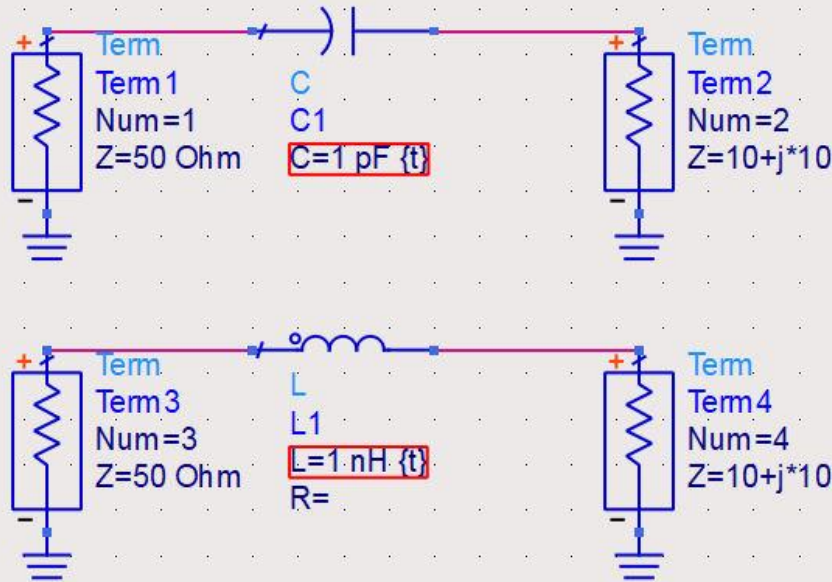

**Tune Parameters**

Simulate: While Slider Moves

Tune

Parameters: Include Opt Params, Enable/Disable..., Display Full Name

Snap Slider to Step

Traces and Values: Store..., Recall..., Trace Visibility..., Reset Values

Close Unassociated Data Displays

Update Schematic

Close Help

adaptare\_LC\_lib:X\_S:schematic


Component	Value	Max	Min	Step	Scale
C1.C (pF)	39.605	50	0.5	0.1	Lin
L1.L (nH)	0.895	40	0.5	0.1	Lin





S-PARAMETERS

S\_Param  
SP1  
Freq=1.0 GHz

# ADS, Smith Chart, series reactance

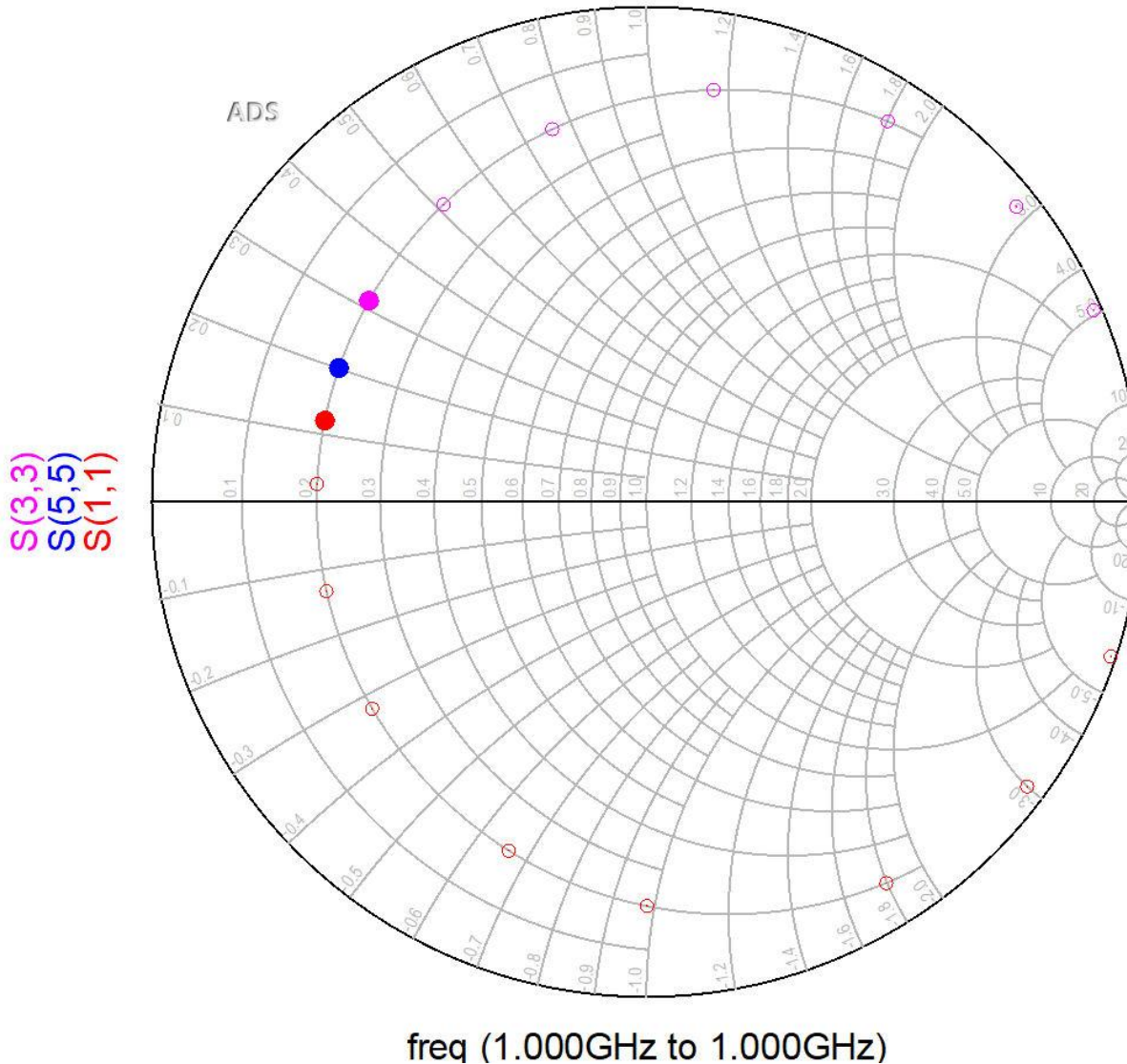

# The Smith Chart, series resistance

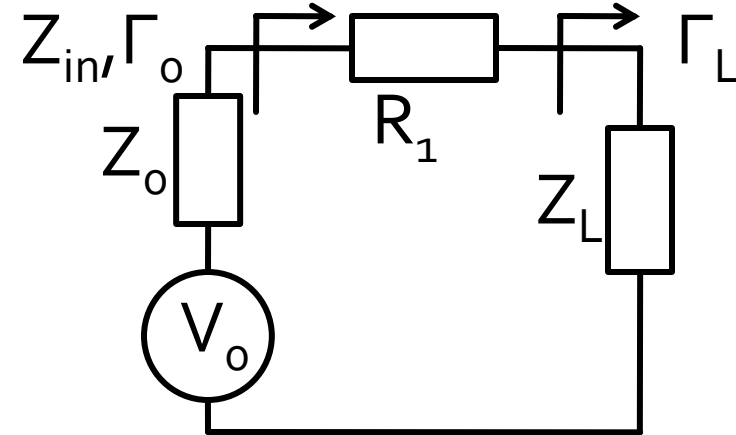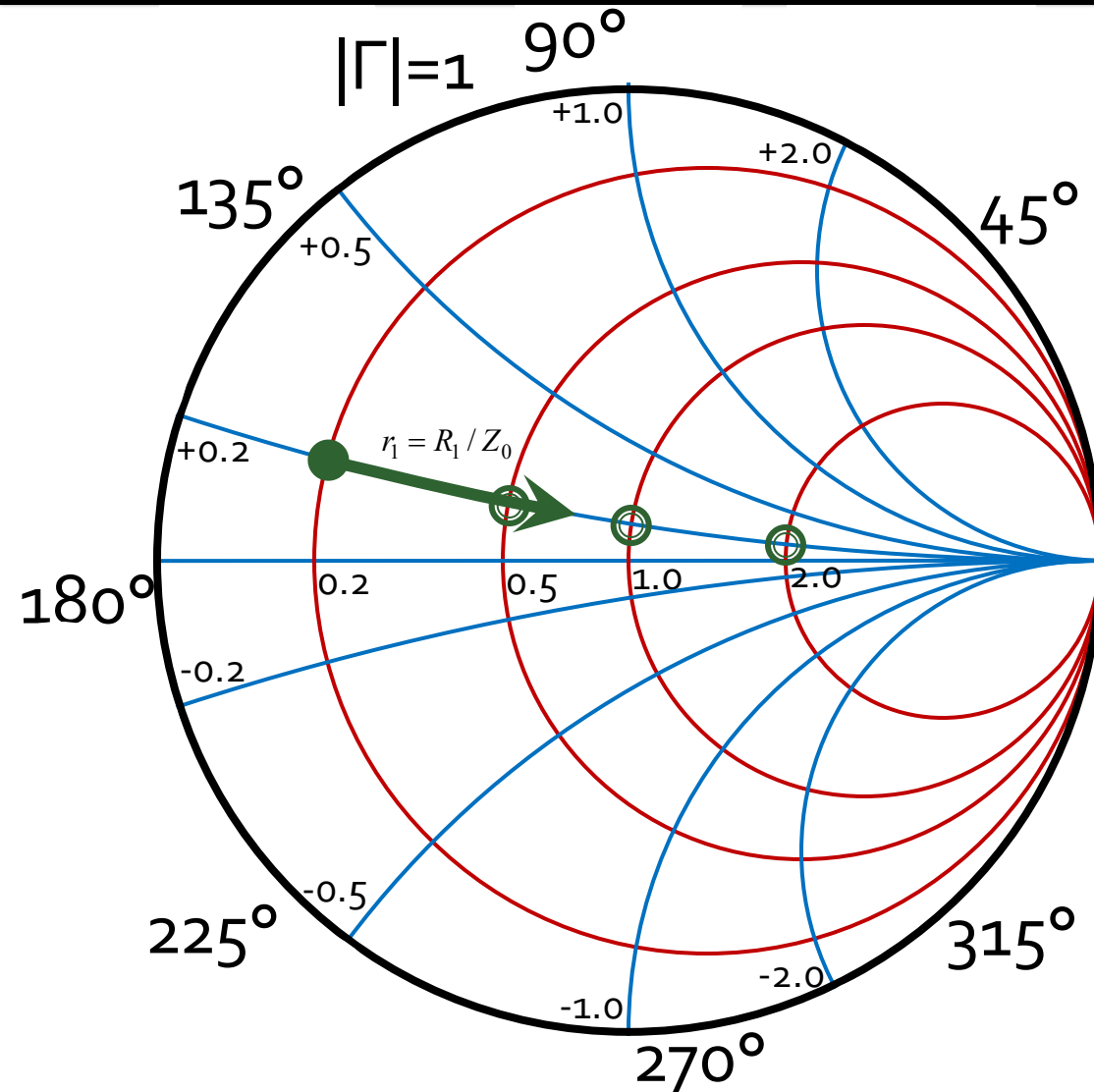

$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$


$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_L + R_1 = (R_L + R_1) + j \cdot X_L$$



$$z_{in} = z_L + r_1 = (r_L + r_1) + j \cdot x_L$$

$$x_{in} = x_L \quad r_{in} = r_L + R_1 / Z_0$$

# ADS, Smith Chart, series resistance

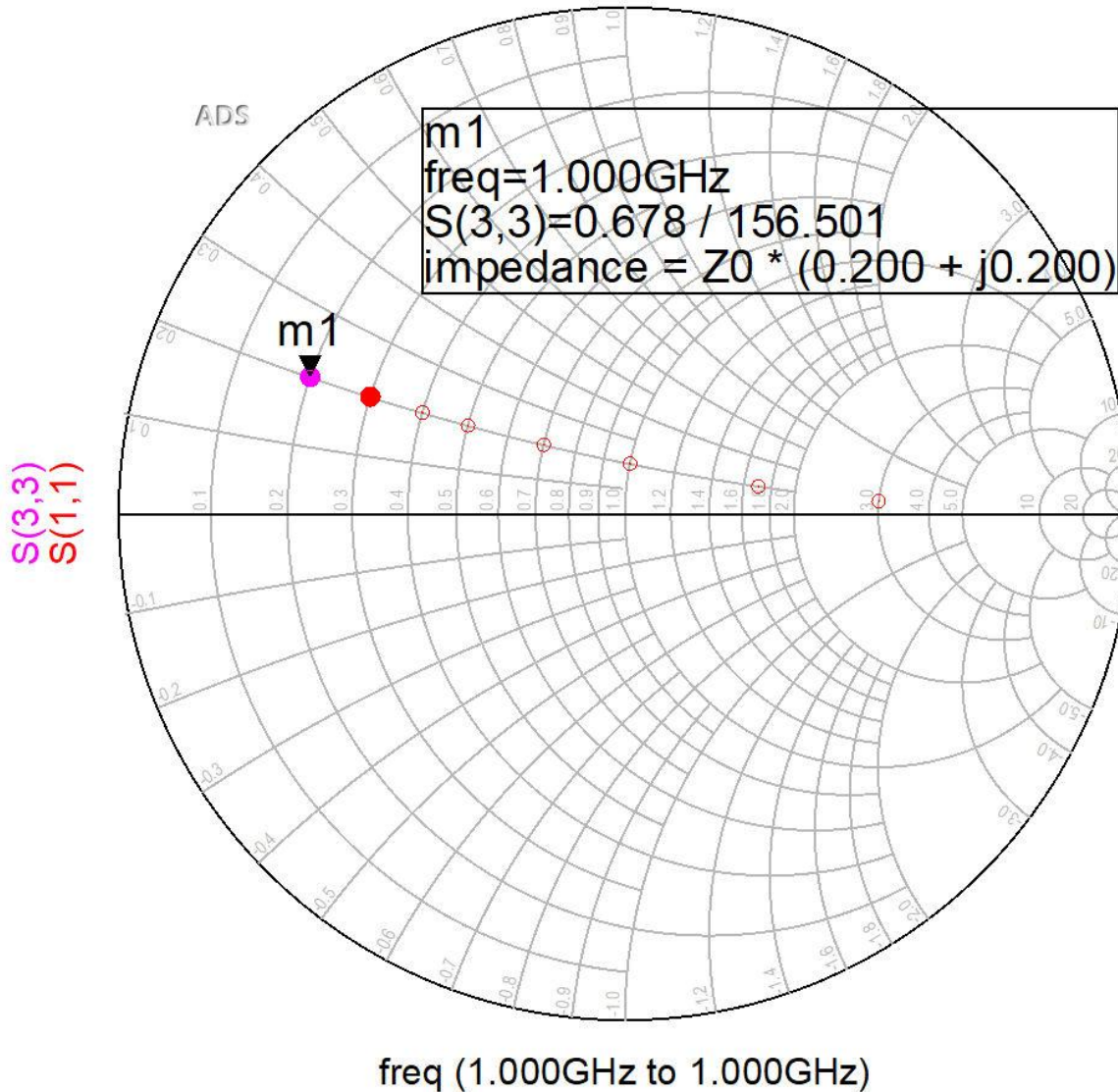
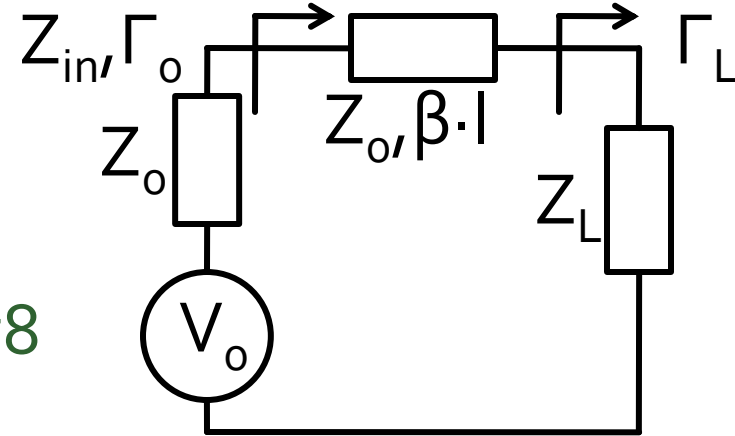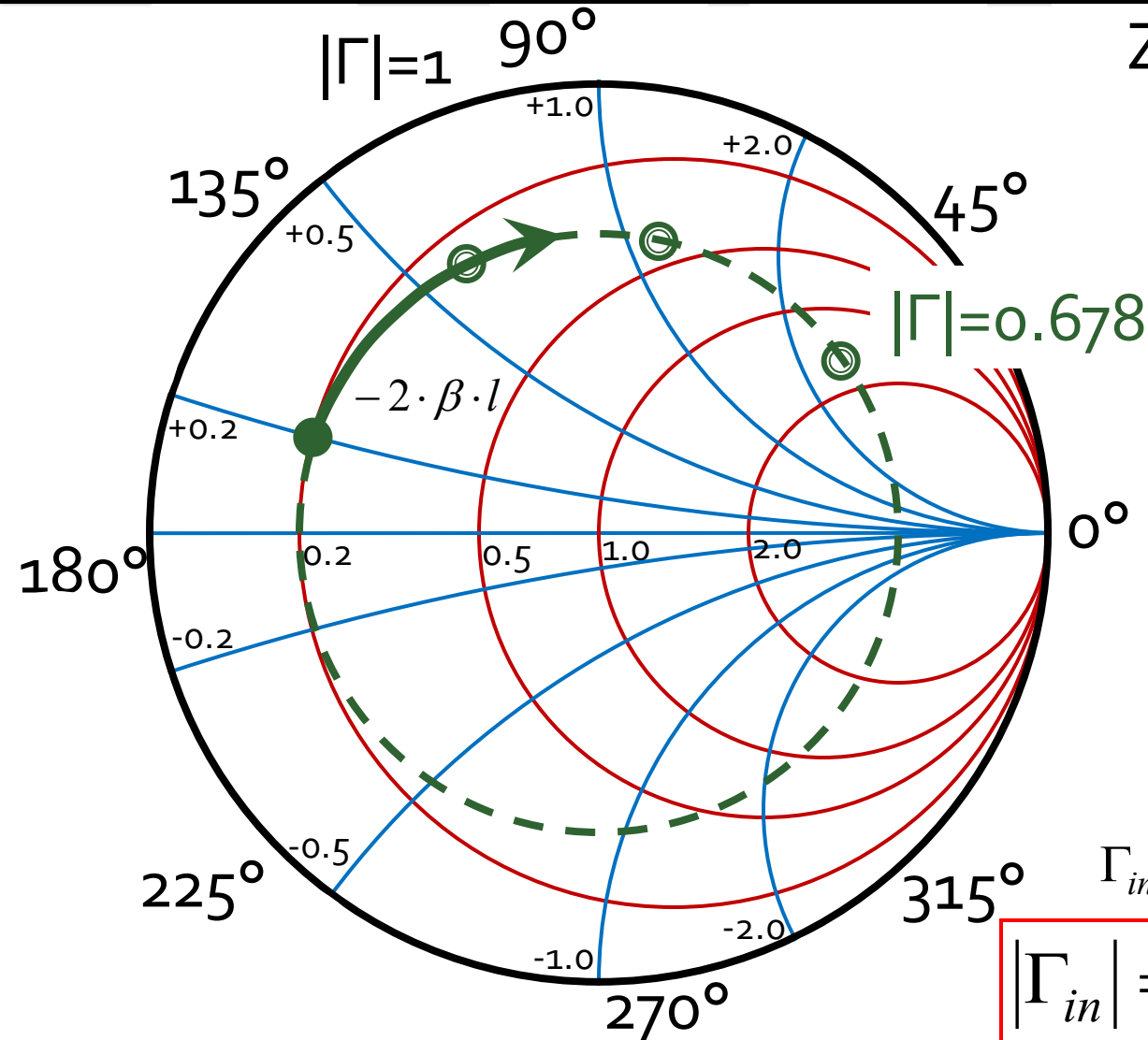
# The Smith Chart, series transmission line, $Z_0$



$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$


$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_0 \cdot \frac{1 + \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}}{1 - \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}}$$


$$\Gamma_{in} = \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}$$

$$|\Gamma_{in}| = |\Gamma_L| \quad \arg(\Gamma_{in}) = \arg(\Gamma_L) - 2 \cdot \beta \cdot l$$

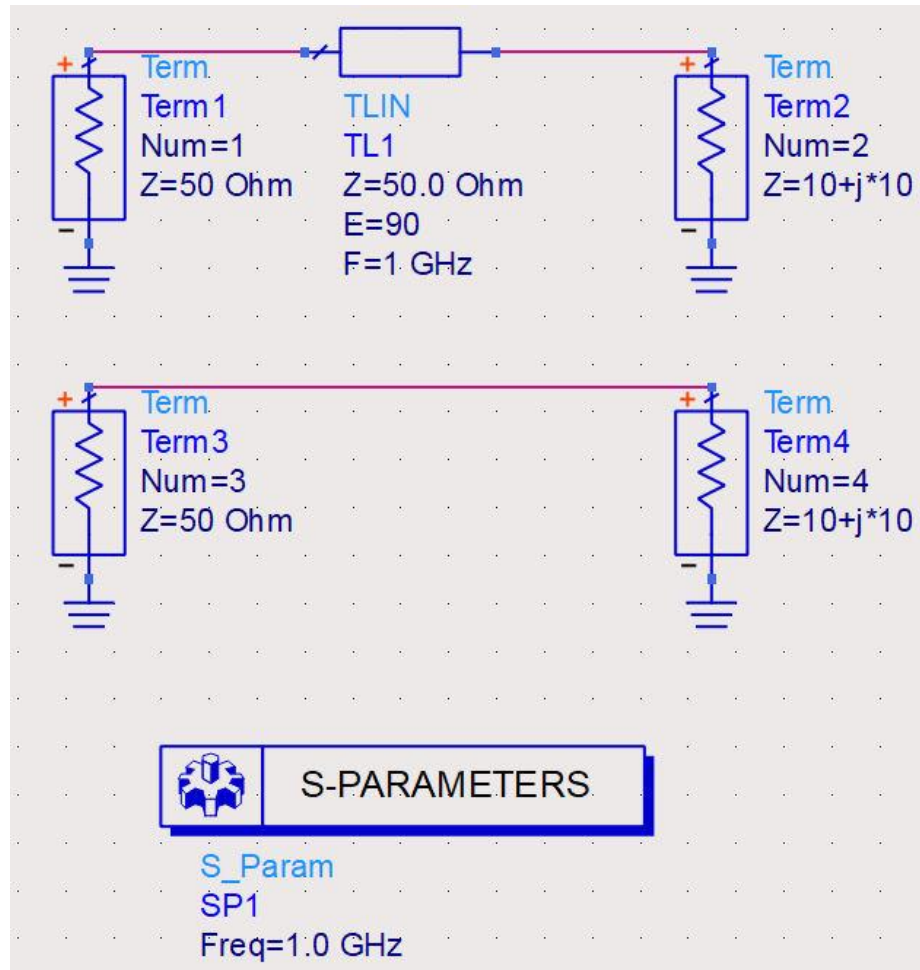
# ADS, Smith Chart, series transmission line



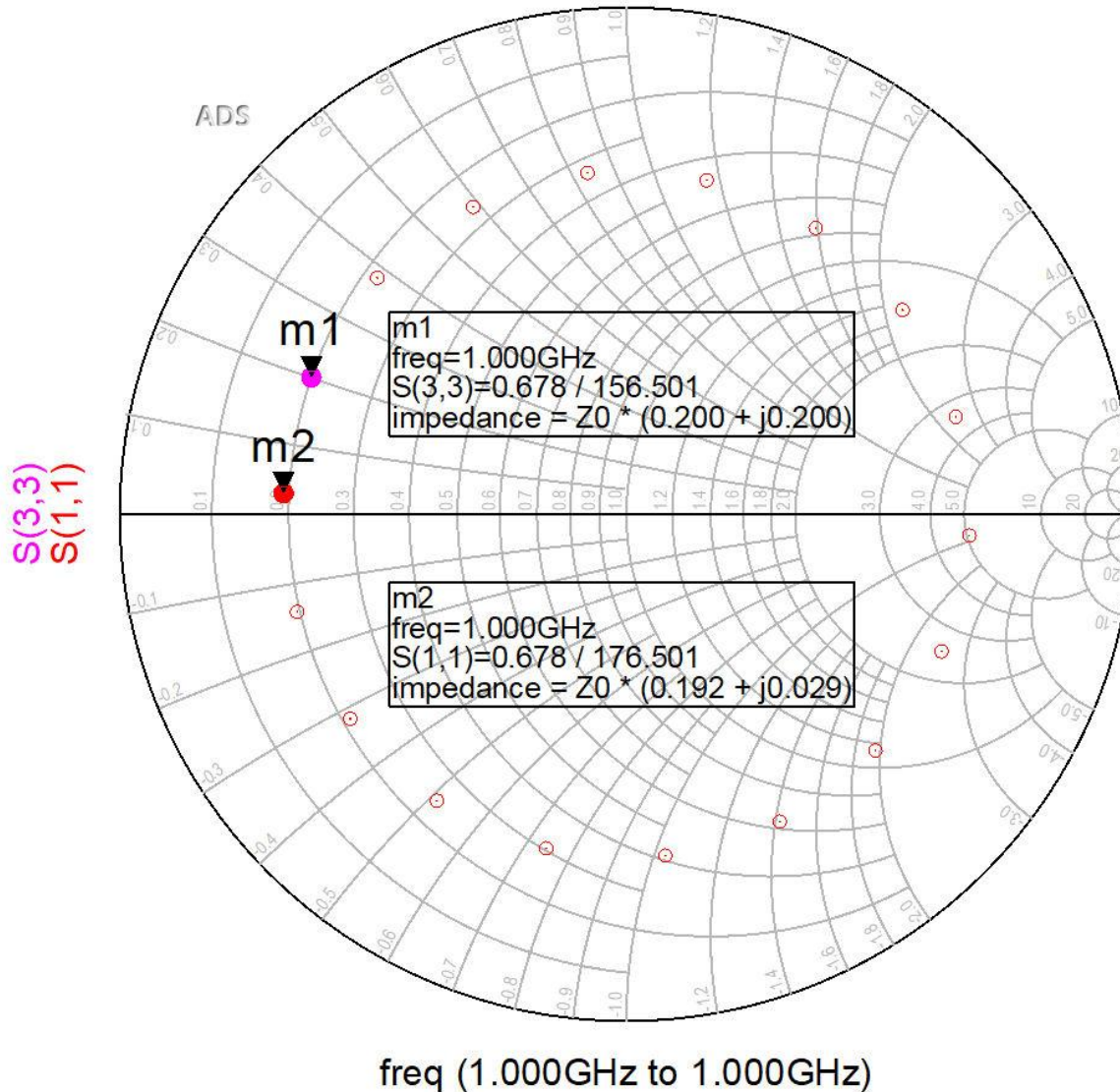
# ADS, Smith Chart, series transmission line



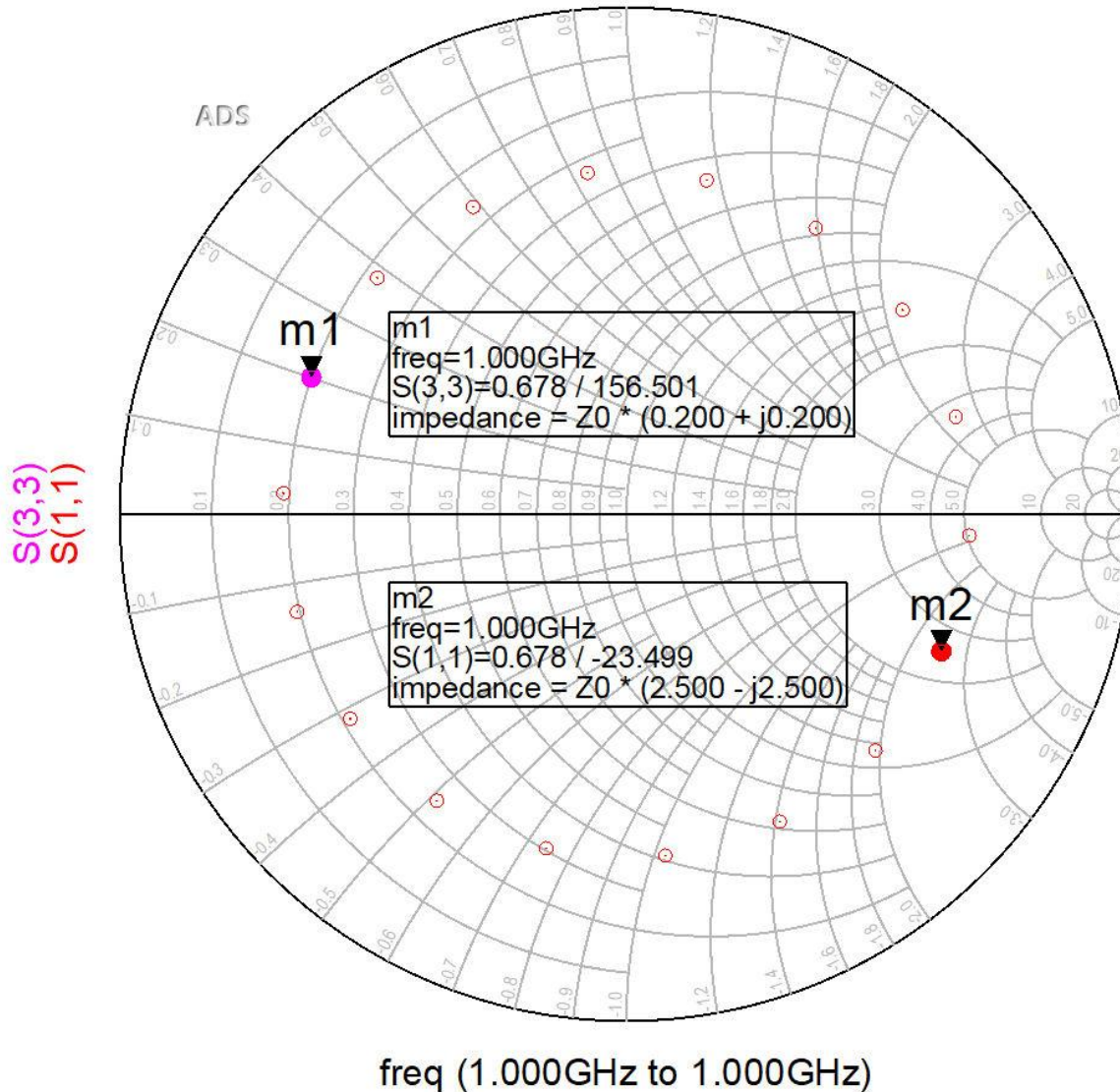
# ADS, Smith Chart, series transmission line, $E=90^\circ$



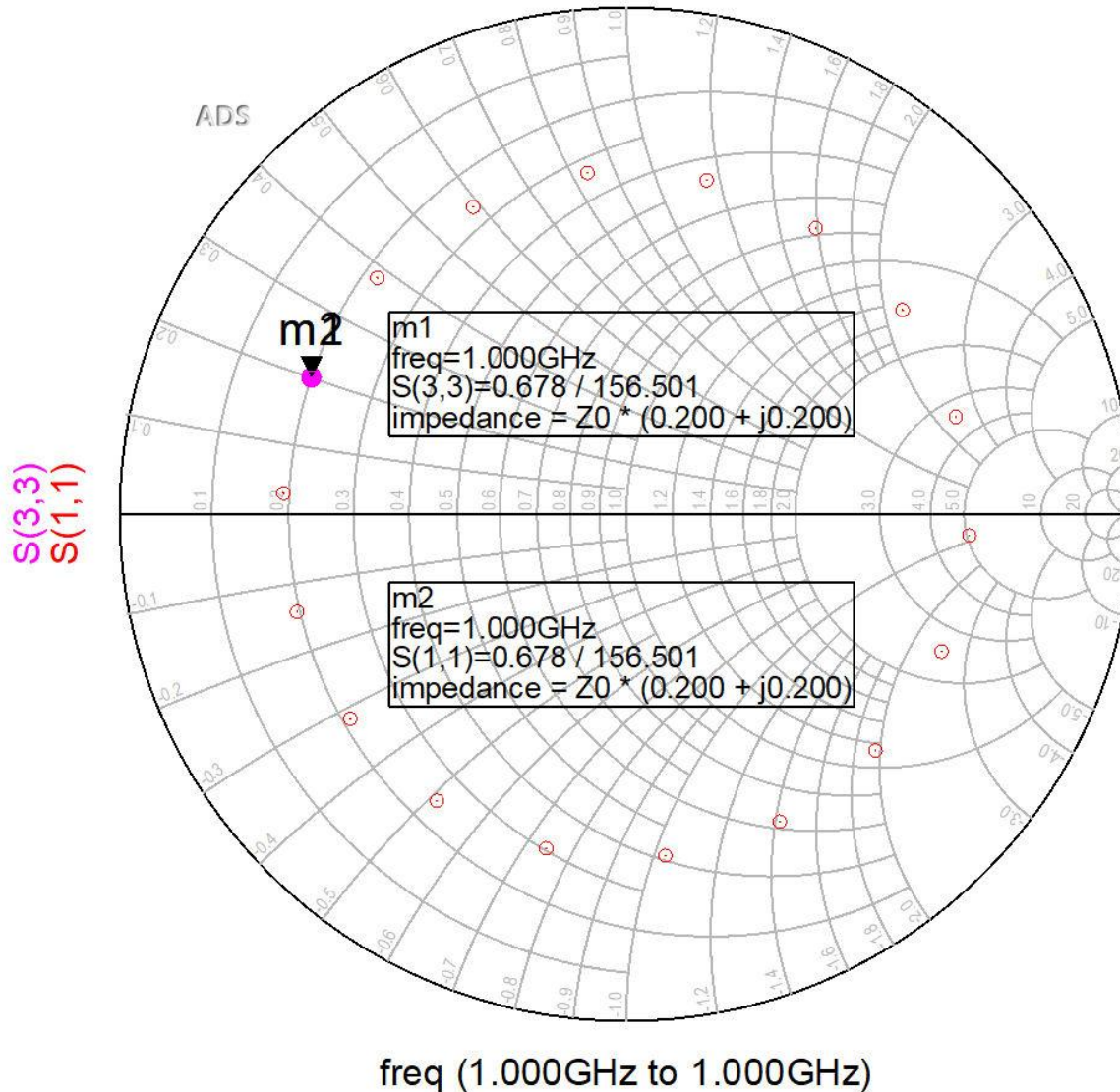
# ADS, Smith Chart, series transmission line, $E=180^\circ$


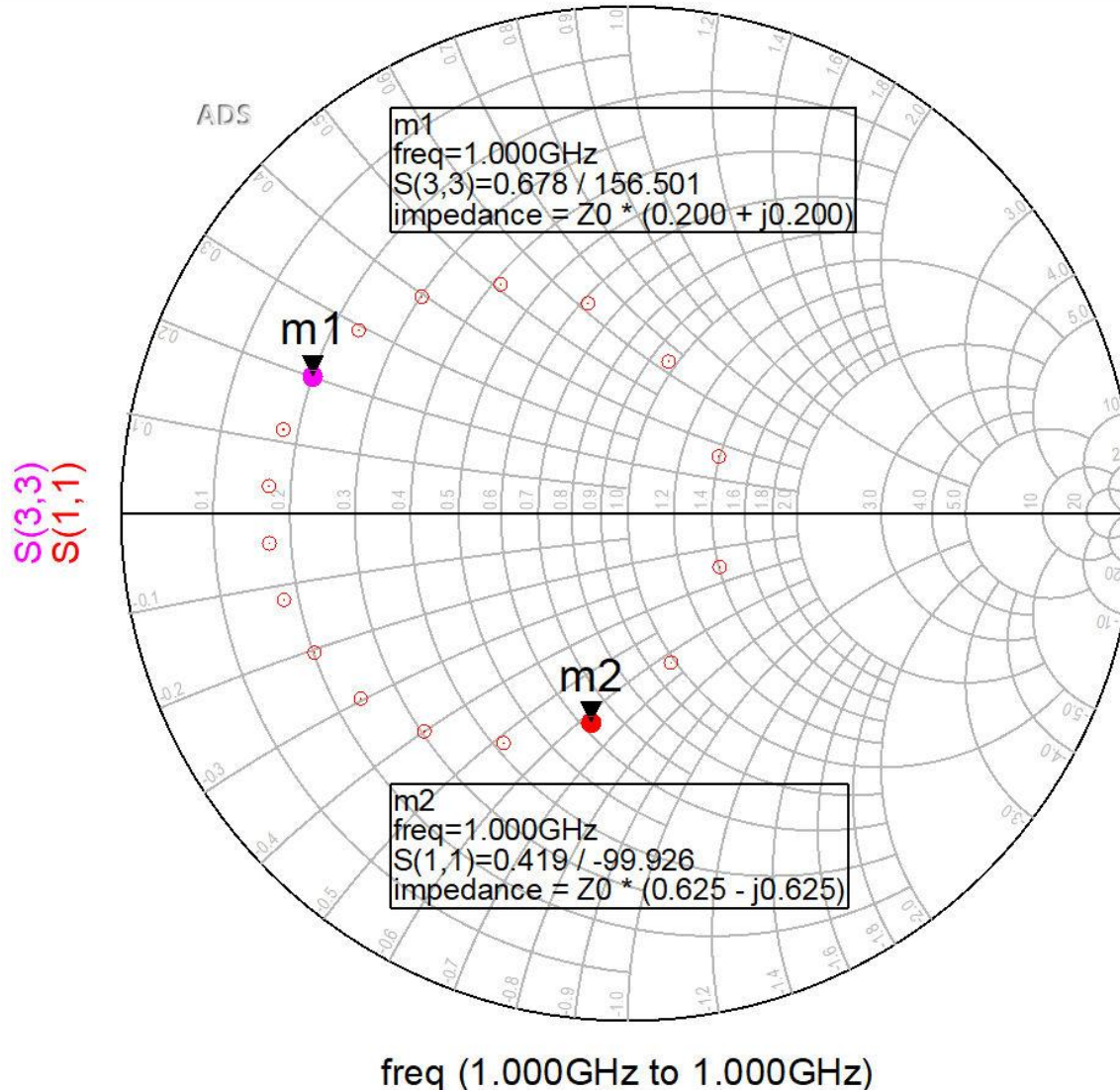
# ADS, Smith Chart, series transmission line, $Z=25\Omega \neq Z_0$



# The Admittance Smith Chart

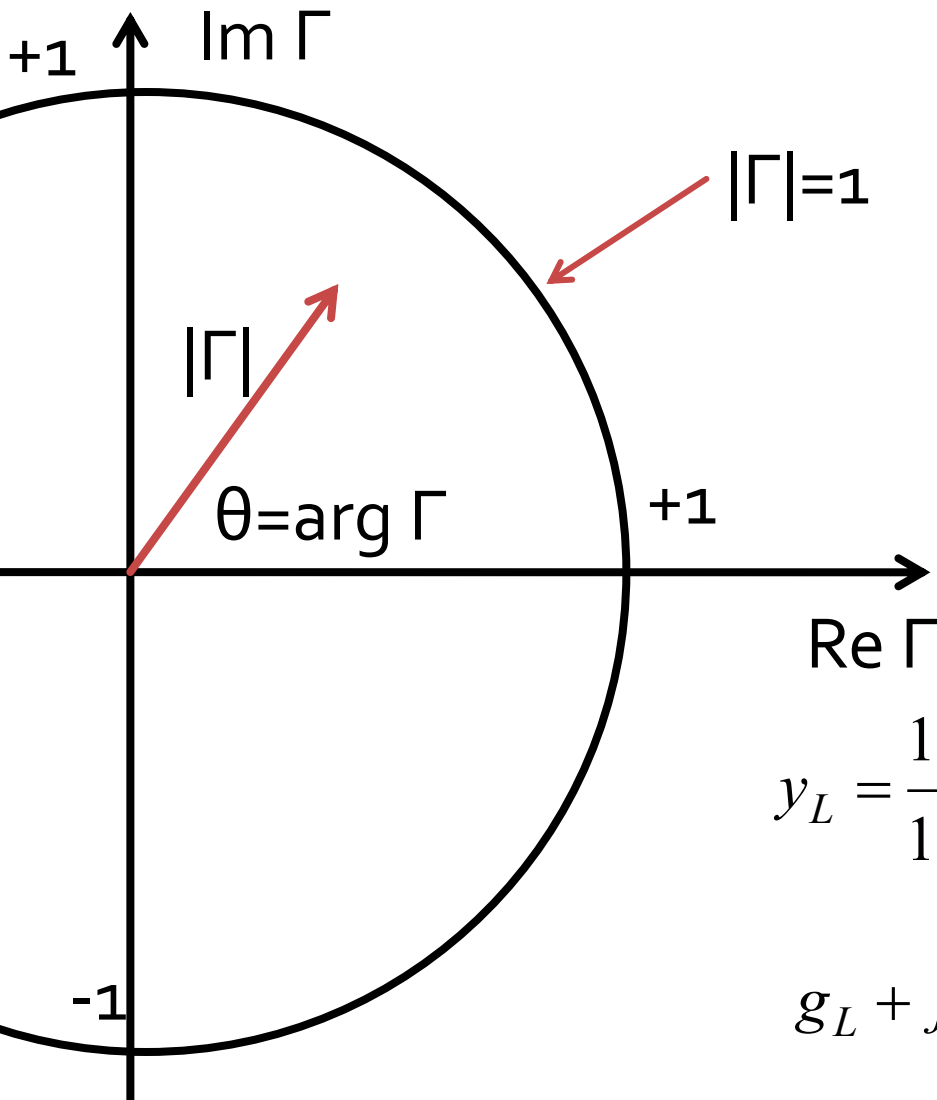

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1} = |\Gamma| \cdot e^{j\theta}$$


$$\Gamma = \Gamma_r + j \cdot \Gamma_i$$

$$z_L = \frac{1 + |\Gamma| \cdot e^{j\theta}}{1 - |\Gamma| \cdot e^{j\theta}} = r_L + j \cdot x_L$$

$$y_L = \frac{1 - |\Gamma| \cdot e^{j\theta}}{1 + |\Gamma| \cdot e^{j\theta}} = \frac{1}{r_L + j \cdot x_L} = g_L + j \cdot b_L$$

$$g_L + j \cdot b_L = \frac{(1 - \Gamma_r) - j \cdot \Gamma_i}{(1 + \Gamma_r) + j \cdot \Gamma_i}$$

# The Admittance Smith Chart

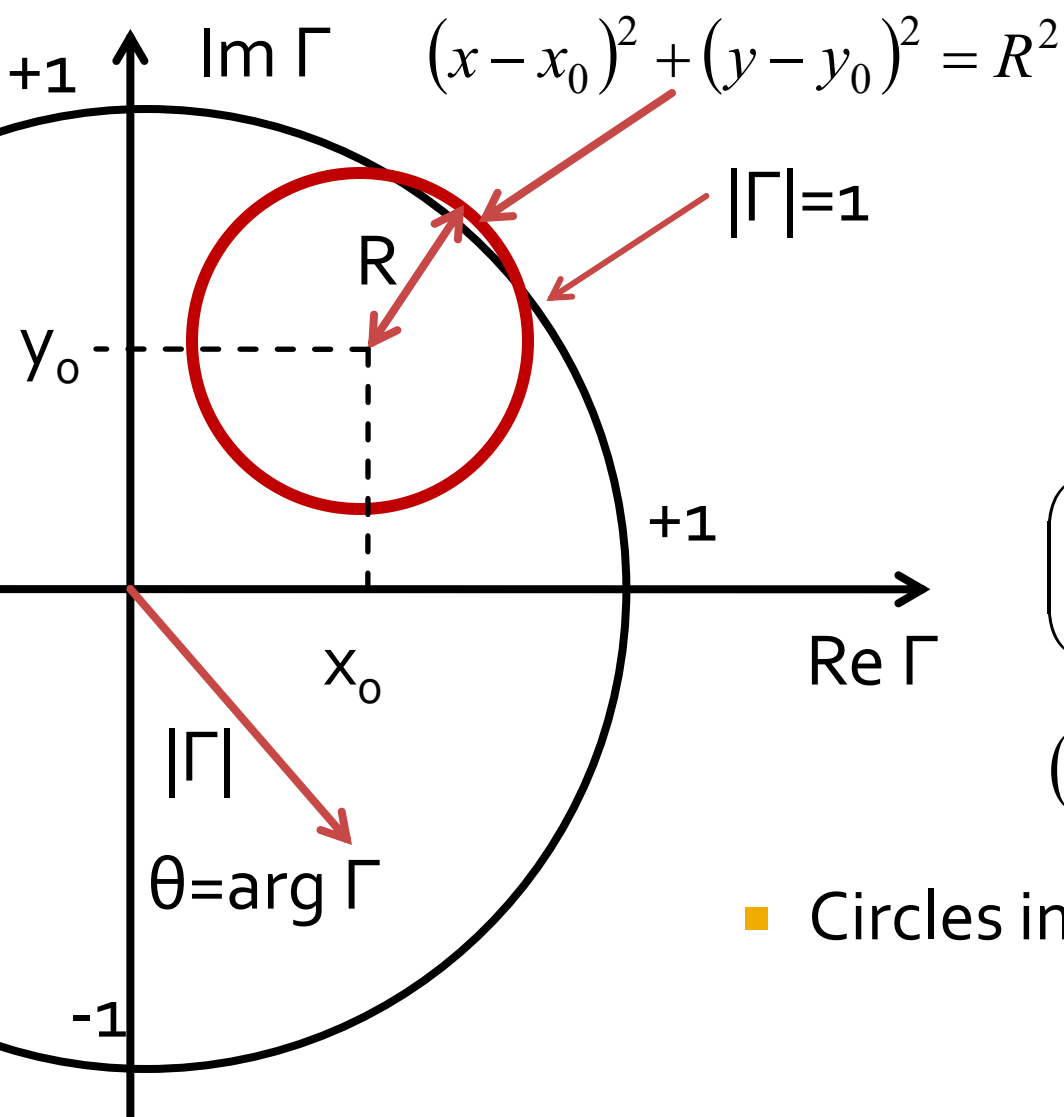

$$g_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 + \Gamma_r)^2 + \Gamma_i^2}$$

$$b_L = \frac{-2 \cdot \Gamma_i}{(1 + \Gamma_r)^2 + \Gamma_i^2}$$

## ■ Rearranged


$$\left( \Gamma_r + \frac{g_L}{1 + g_L} \right)^2 + \Gamma_i^2 = \left( \frac{1}{1 + g_L} \right)^2$$

$$(\Gamma_r + 1)^2 + \left( \Gamma_i + \frac{1}{b_L} \right)^2 = \left( \frac{1}{b_L} \right)^2$$


- Circles in the  $(\Gamma_r, \Gamma_i)$  complex plane

$$(x - x_0)^2 + (y - y_0)^2 = R^2$$


# The Smith Chart, conductance

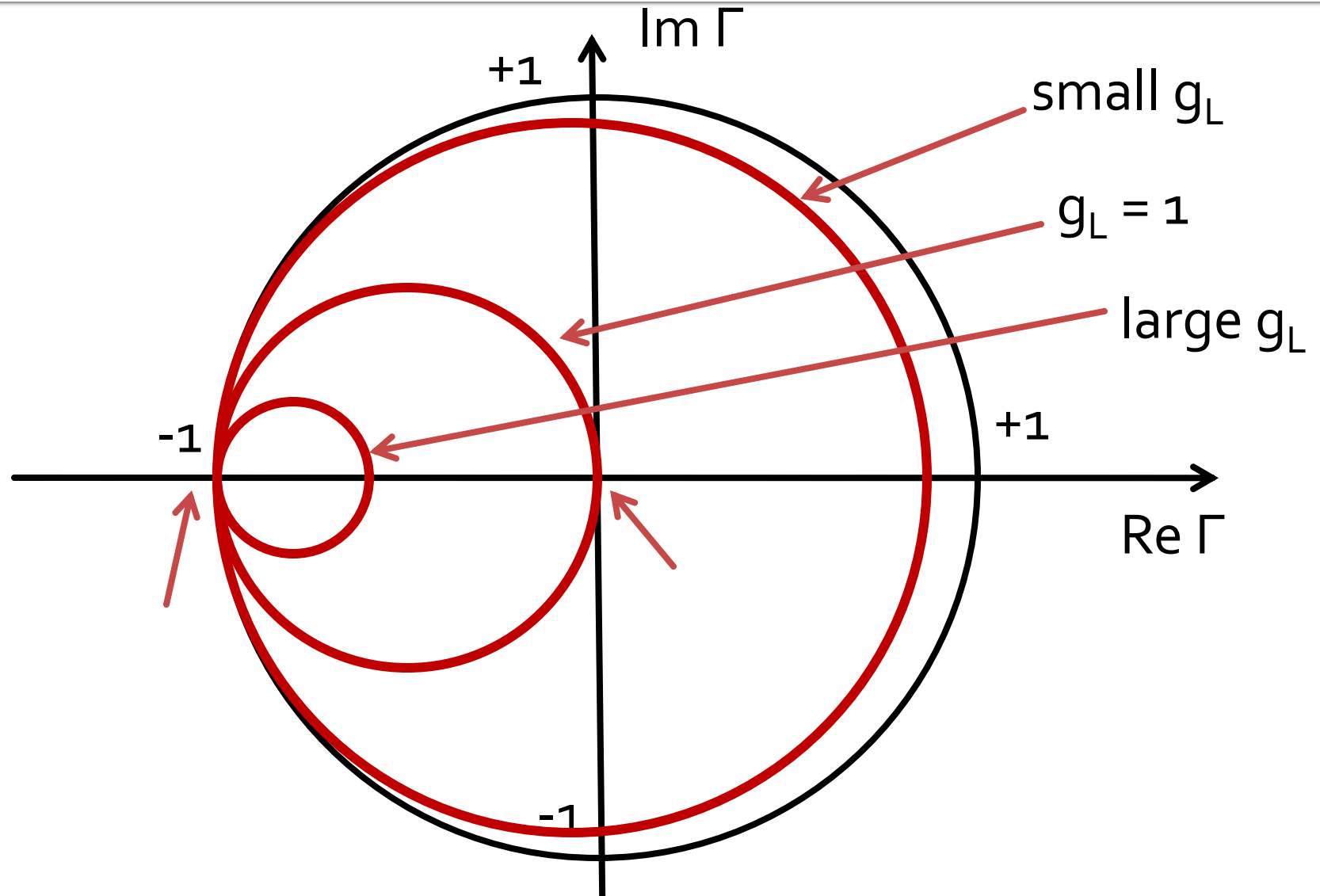



# The Smith Chart, susceptance

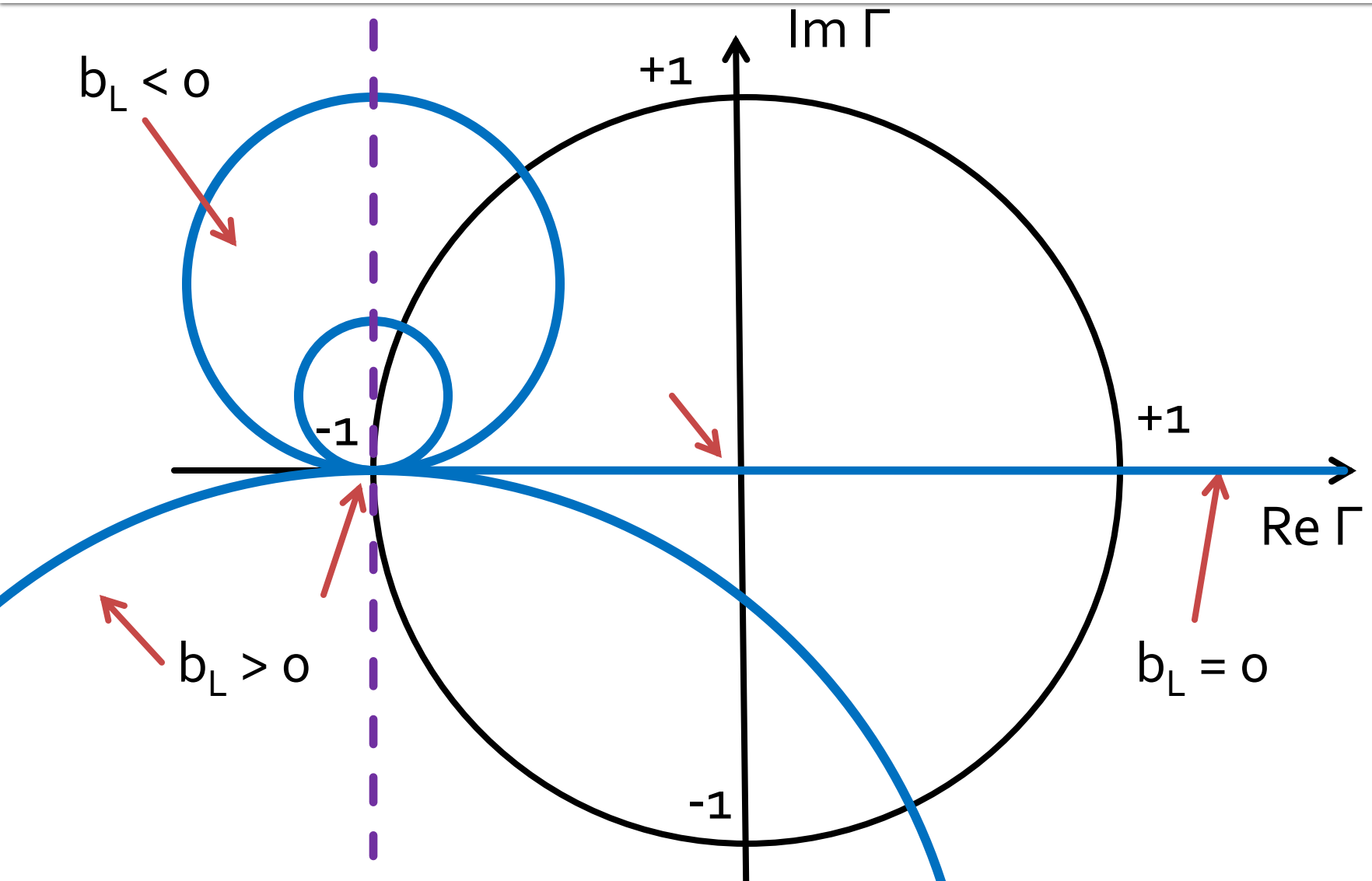
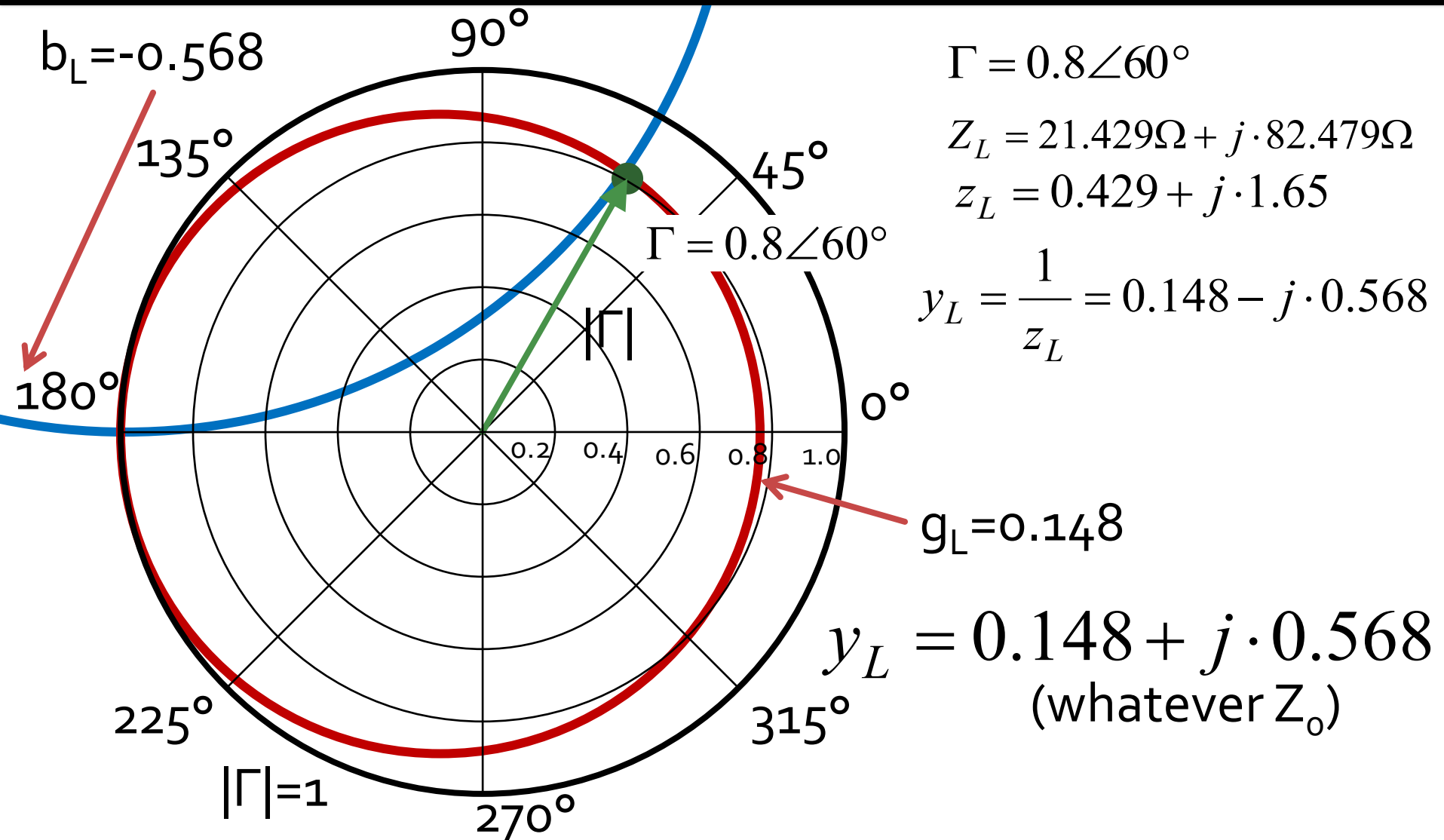
# The Smith Chart, reflection coefficient $\Leftrightarrow$ admittance


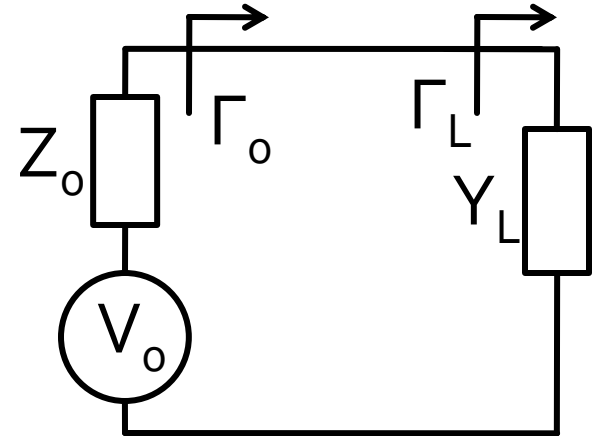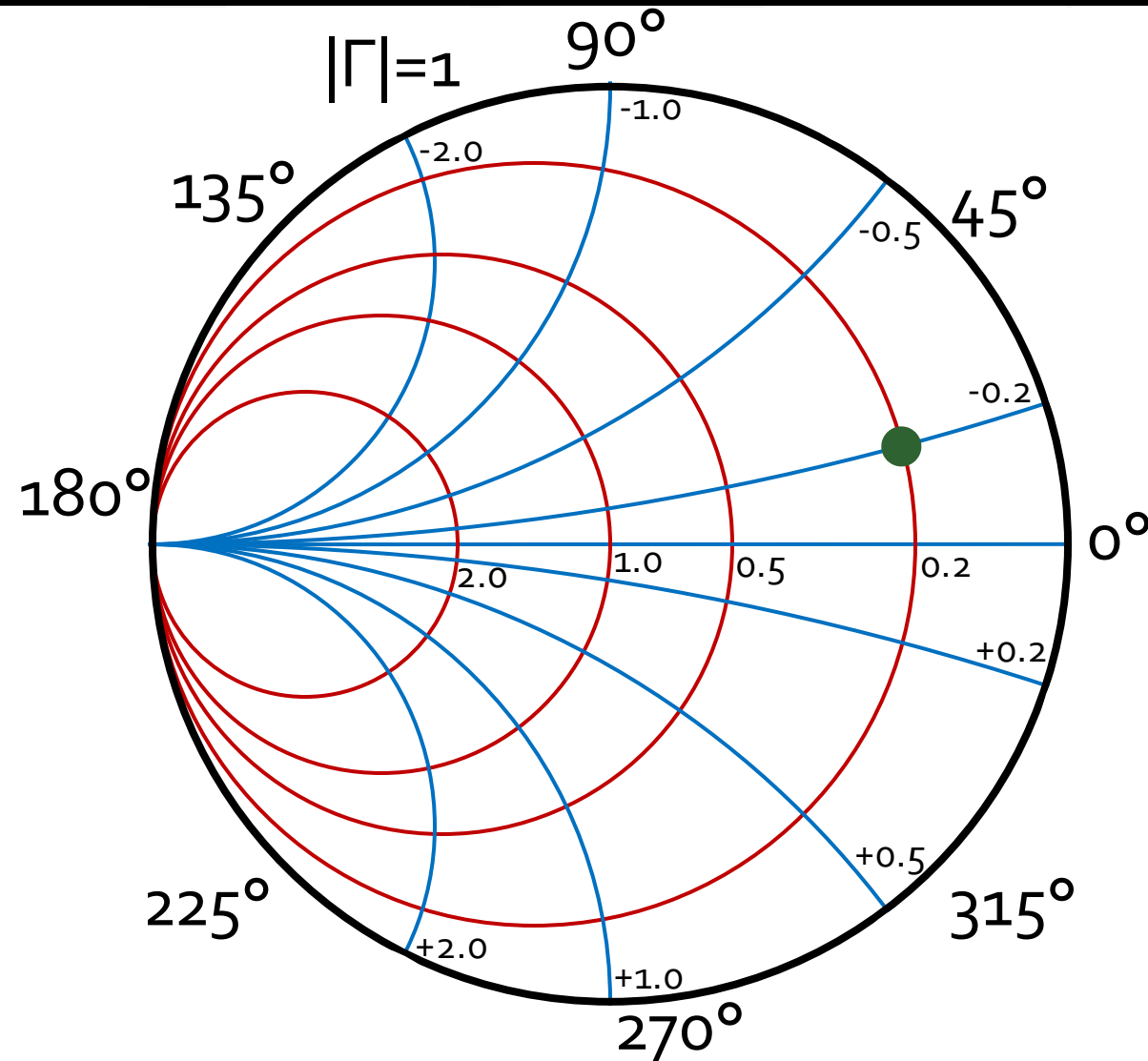
# The Smith Chart, reflection coefficient $\Leftrightarrow$ admittance



$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$Z_L = 125\Omega + j \cdot 125\Omega$$



$$z_L = 2.5 + j \cdot 2.5$$

$$\Gamma_L = \Gamma_0 = 0.678 \angle 23.5^\circ$$

$$Y_L = \frac{1}{Z_L} = 0.004S - j \cdot 0.004S$$

$$y_L = \frac{1}{z_L} = \frac{Y_L}{Y_0} = 0.2 - j \cdot 0.2$$

# The Smith Chart, shunt susceptance

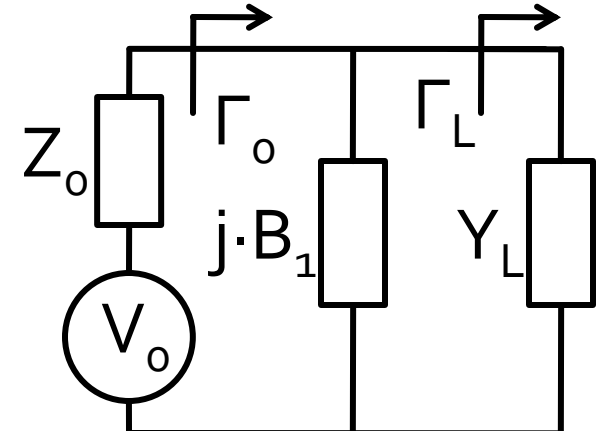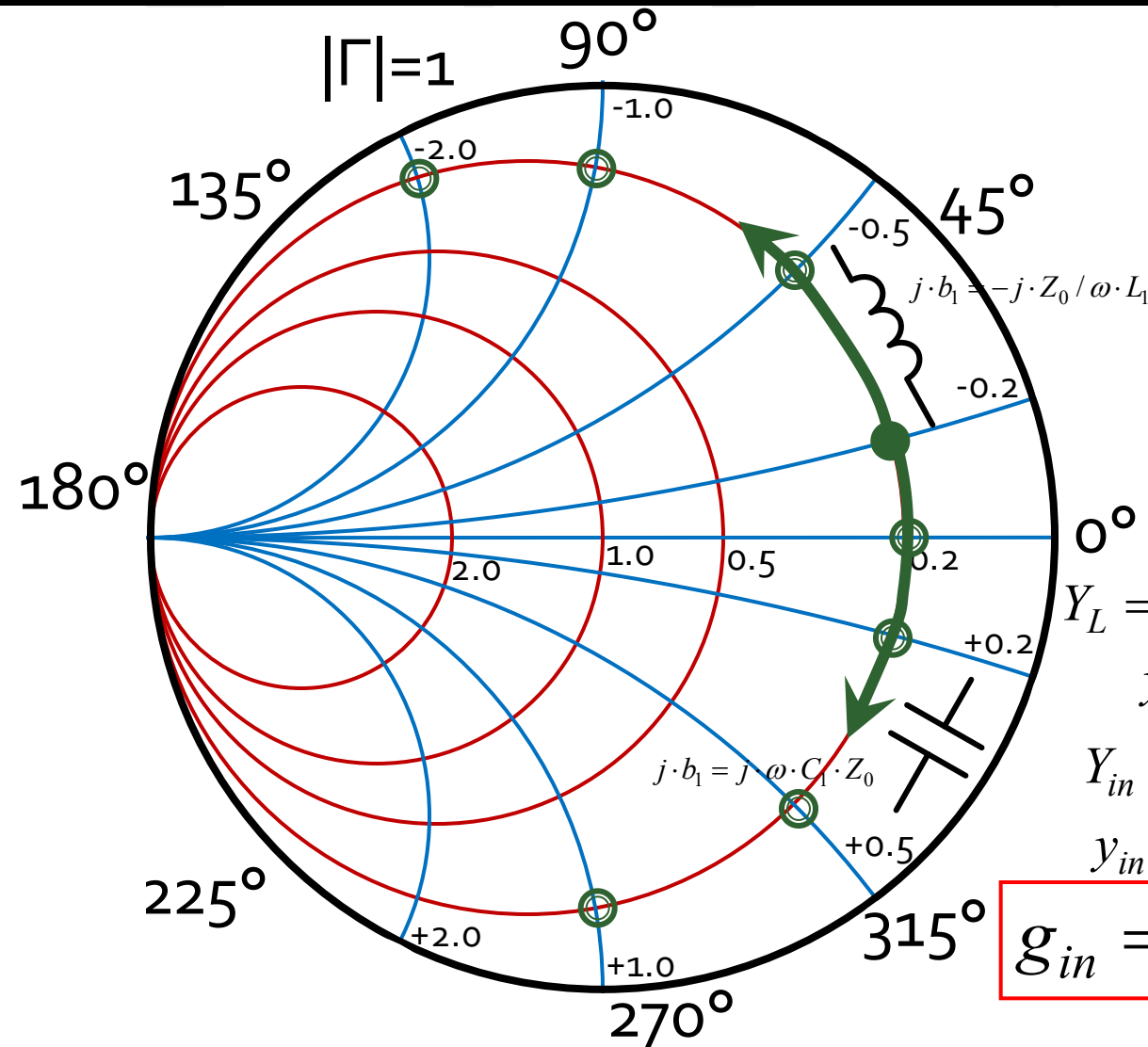

$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$\Gamma_L = 0.678 \angle 23.5^\circ$$

$$Y_L = G_L + j \cdot B_L = 0.004S + j \cdot 0.004$$

$$y_L = g_L + j \cdot b_L = 0.2 - j \cdot 0.2$$

$$Y_{in} = Y_L + j \cdot B_1 = G_L + j \cdot (B_L + B_1)$$




$$y_{in} = g_L + j \cdot (b_L + b_1)$$


$$g_{in} = g_L$$

$$j \cdot b_1 = j \cdot \omega \cdot C_1 \cdot Z_0 > 0$$

$$j \cdot b_1 = -j \cdot Z_0 / \omega \cdot L_1 < 0$$

# ADS, shunt susceptance

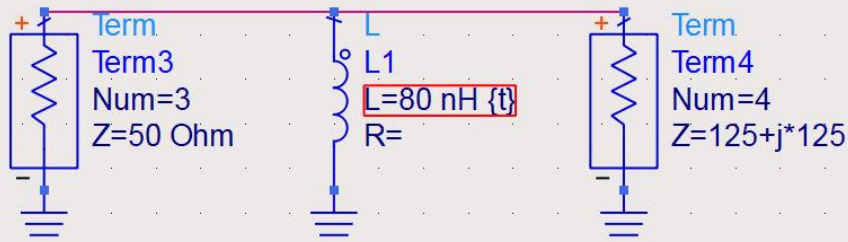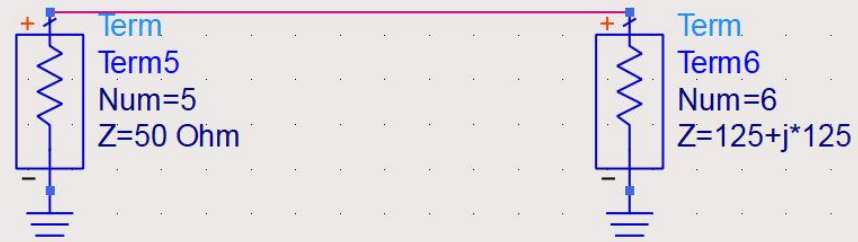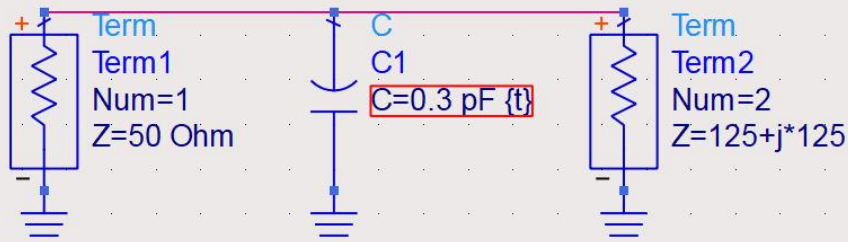

 S-PARAMETERS

S\_Param  
SP1  
Freq=1.0 GHz

Tune Parameters

Simulate  
While Slider Moves  
Tune

Parameters  
Include Opt Params  
Enable/Disable...  
Display Full Name  
Snap Slider to Step

Traces and Values  
Store... Recall...  
Trace Visibility...  
Reset Values  
Close Unassociated Data Displays

Update Schematic  
Close Help


adaptare\_IC\_lib:X:schematic

L1.L (nH)  
Value 80  
Max 100  
Min 0.5  
Step 0.1  
Scale Lin



C1.C (pF)  
Value 0.3  
Max 50  
Min 0.1  
Step 0.1  
Scale Lin

Detailed description: A screenshot of the 'Tune Parameters' dialog box in ADS. The dialog is titled 'Tune Parameters' and has a close button. It is divided into several sections. The 'Simulate' section has a dropdown menu set to 'While Slider Moves' and a 'Tune' button. The 'Parameters' section has buttons for 'Include Opt Params', 'Enable/Disable...', and 'Display Full Name', and a checkbox for 'Snap Slider to Step'. The 'Traces and Values' section has buttons for 'Store...', 'Recall...', 'Trace Visibility...', 'Reset Values', and 'Close Unassociated Data Displays'. At the bottom are 'Update Schematic', 'Close', and 'Help' buttons. The main area shows two parameter sliders for 'L1.L (nH)' and 'C1.C (pF)'. The 'L1.L' slider has a value of 80, a max of 100, a min of 0.5, a step of 0.1, and a linear scale. The 'C1.C' slider has a value of 0.3, a max of 50, a min of 0.1, a step of 0.1, and a linear scale.

# ADS, shunt susceptance

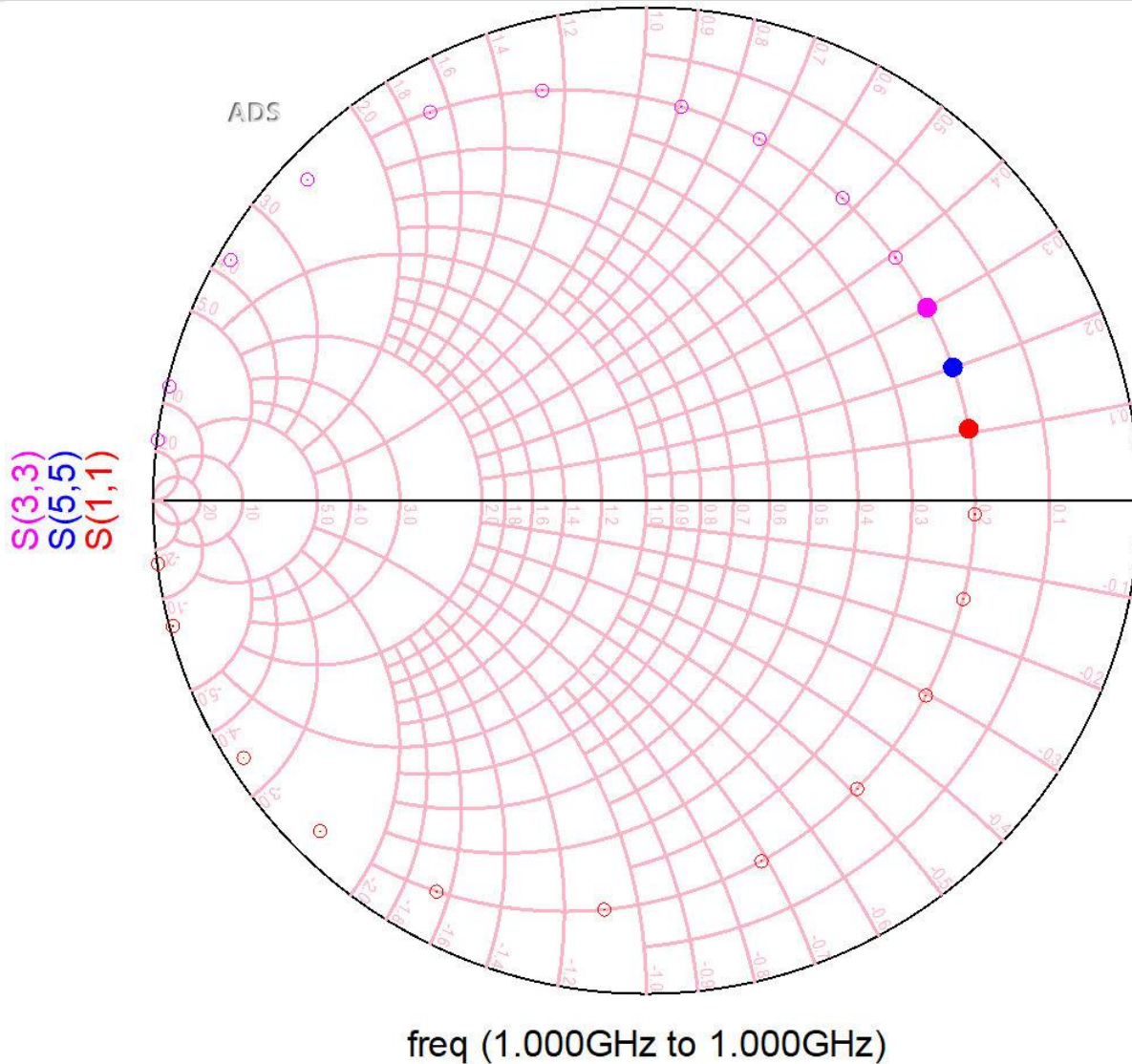

# The Smith Chart, shunt conductance

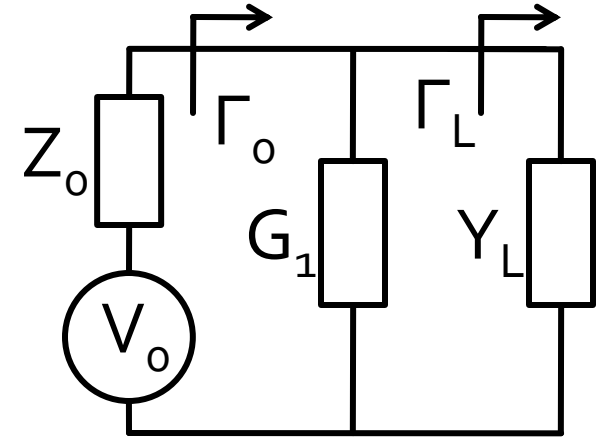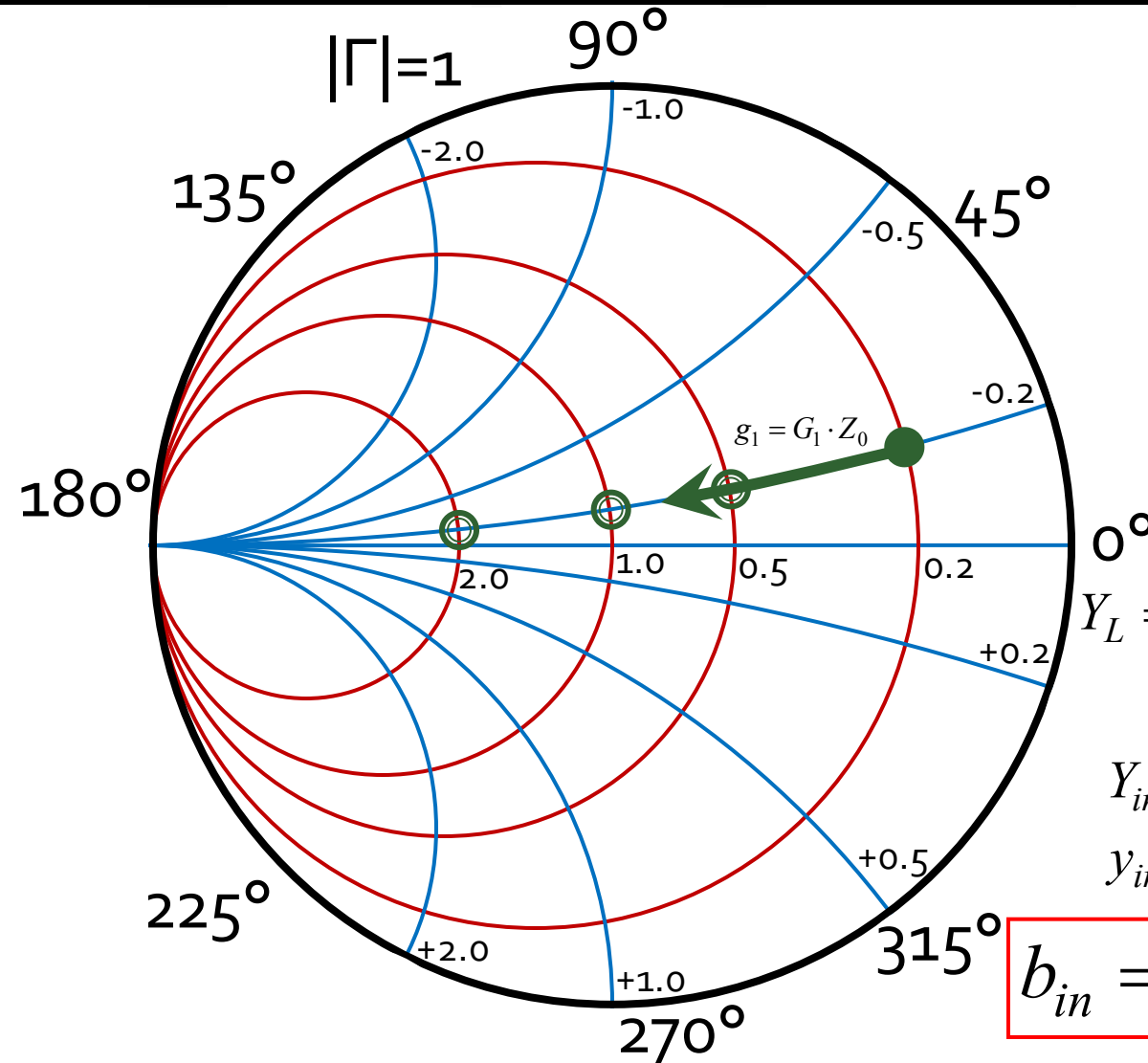

$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$\Gamma_L = 0.678 \angle 23.5^\circ$$

$$Y_L = G_L + j \cdot B_L = 0.004S + j \cdot 0.004$$

$$y_L = g_L + j \cdot b_L = 0.2 - j \cdot 0.2$$


$$Y_{in} = Y_L + G_1 = (G_L + G_1) + j \cdot B_L$$

$$y_{in} = (g_L + g_1) + j \cdot b_L$$

$$b_{in} = b_L$$

$$g_{in} = g_L + G_1 \cdot Z_0$$


# ADS, shunt conductance

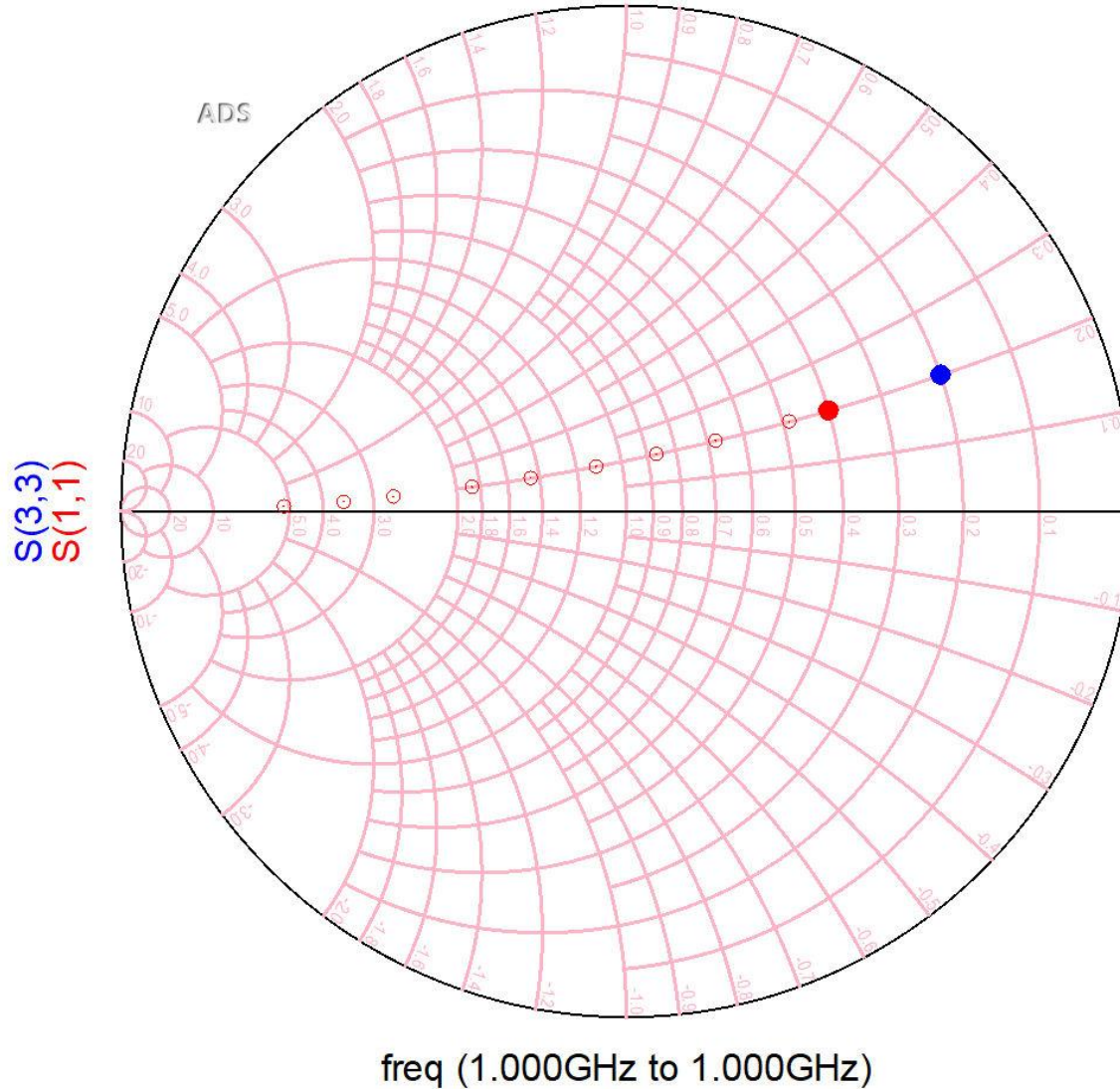

# Constant VSWR circles

- Certain applications may require a certain ratio between maximum / minimum line voltage
- $VSWR = \text{const} \rightarrow |\Gamma| = \text{const}$



$$VSWR = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

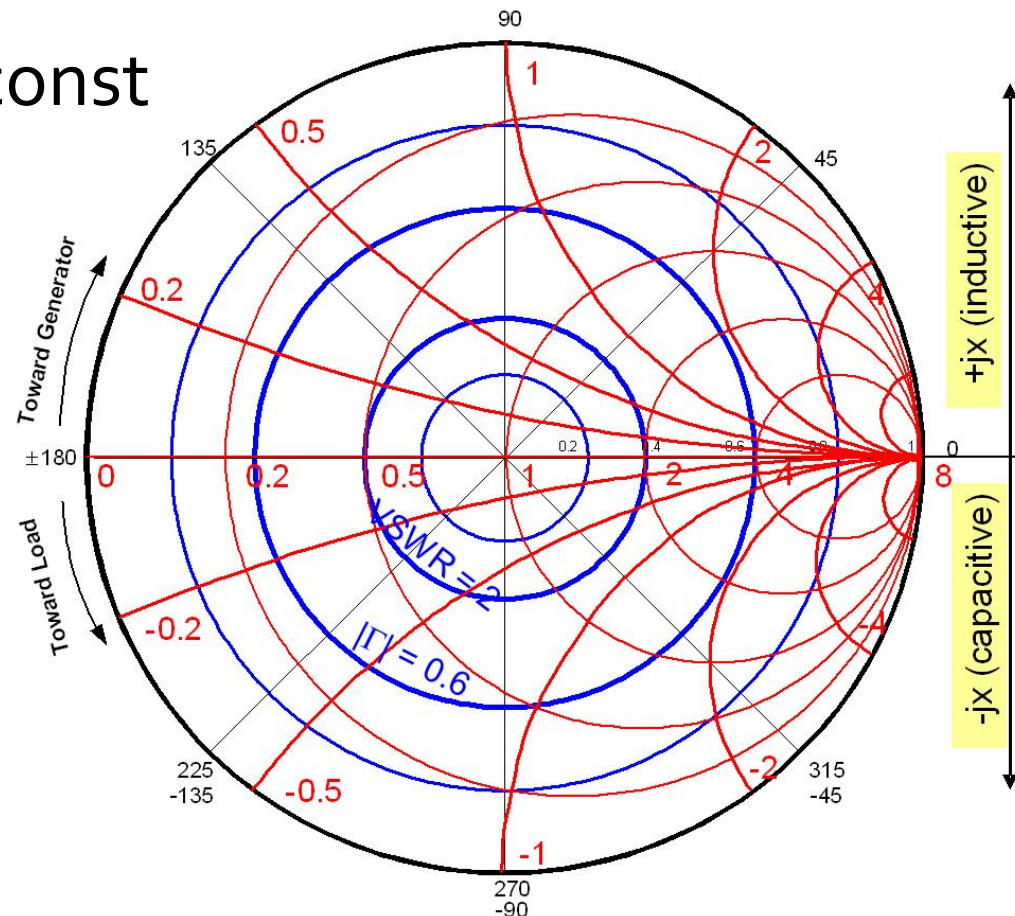
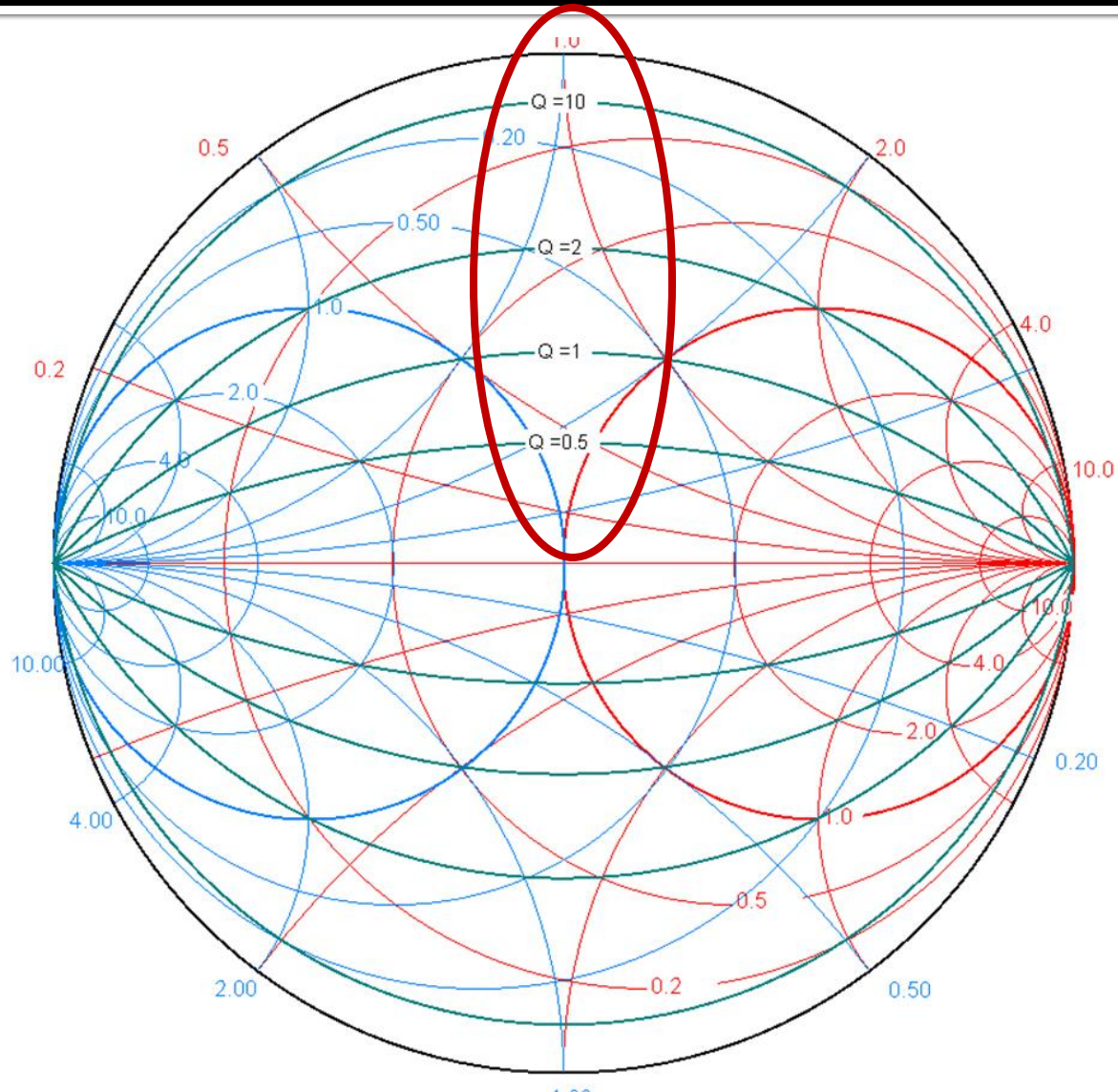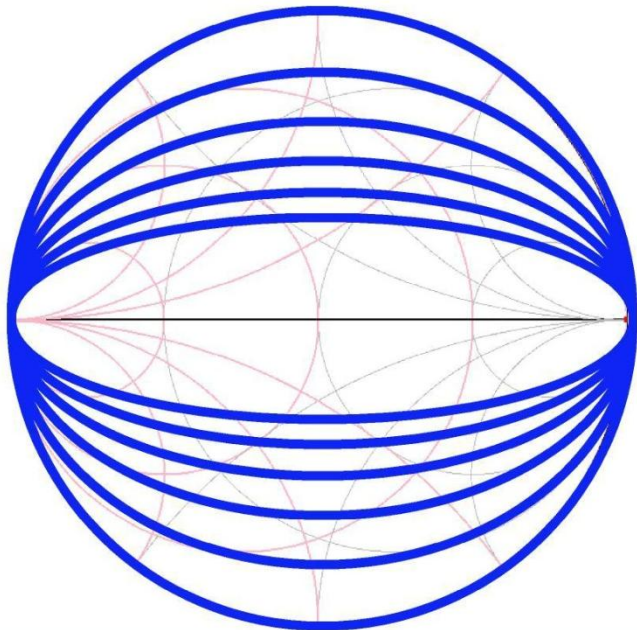
# Constant Q circles

- Quality factor Q

$$Q = \frac{X}{R} = \frac{G}{B} = \text{const}$$





Impedance matching

# Impedance Matching with lumped elements (L Networks)

# Course Topics

- Transmission lines
- Impedance matching and tuning
- Directional couplers
- Power dividers
- Microwave amplifier design
- Microwave filters
- ~~Oscillators and mixers?~~
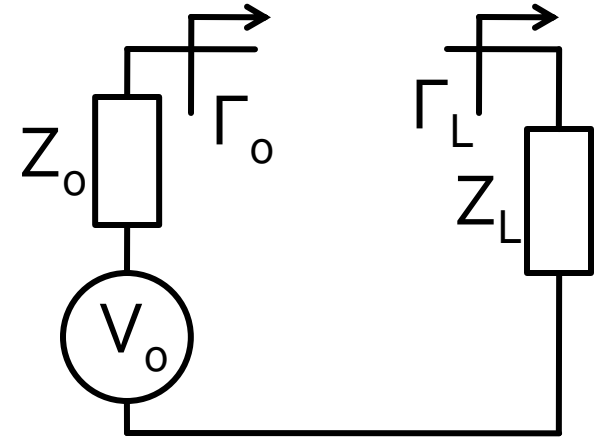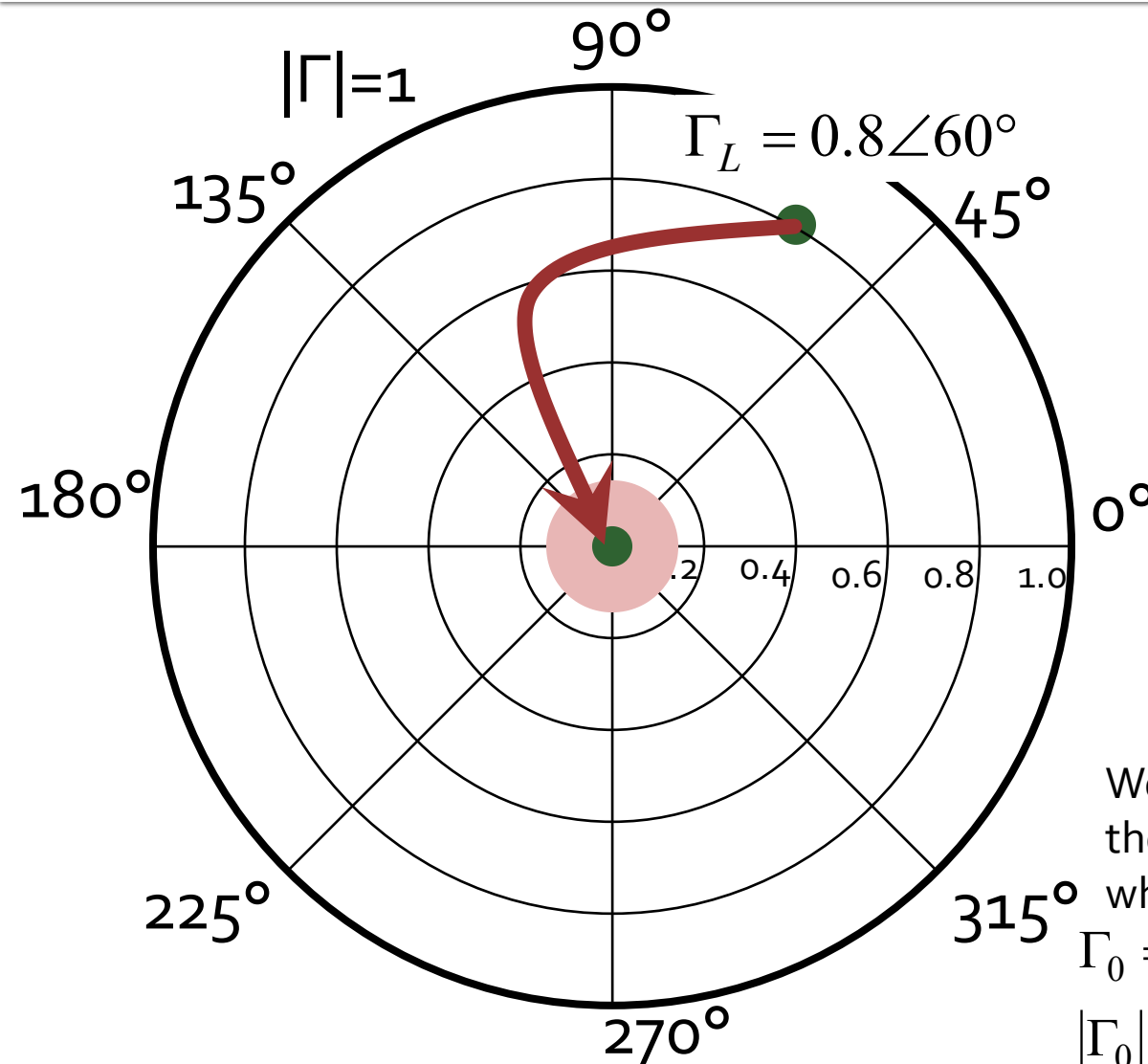
# The Smith Chart, reflection coefficient, impedance matching



Matching  $Z_L$  load to  $Z_o$  source.  
We normalize  $Z_L$  over  $Z_o$

$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

$$z_L = 0.429 + j \cdot 1.65$$



$$\Gamma_L = 0.8 \angle 60^\circ$$

We must move the point denoting the reflection coefficient in the area where with a  $Z_o$  source we have:

$\Gamma_0 = 0$  perfect match ●

$|\Gamma_0| \leq \Gamma_m$  "good enough" match ●

# The Smith Chart, series reactance

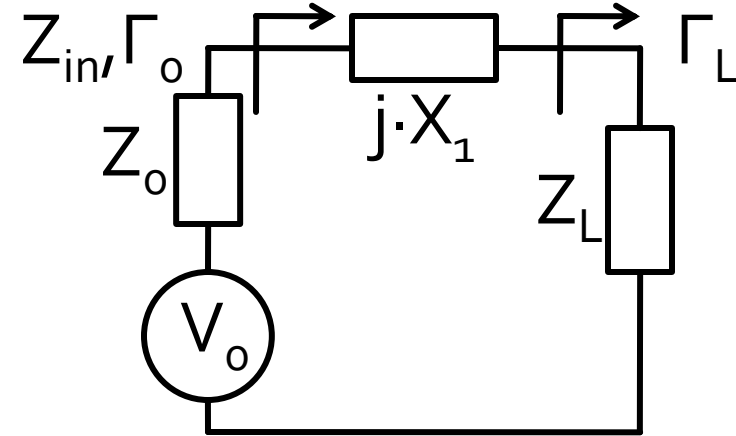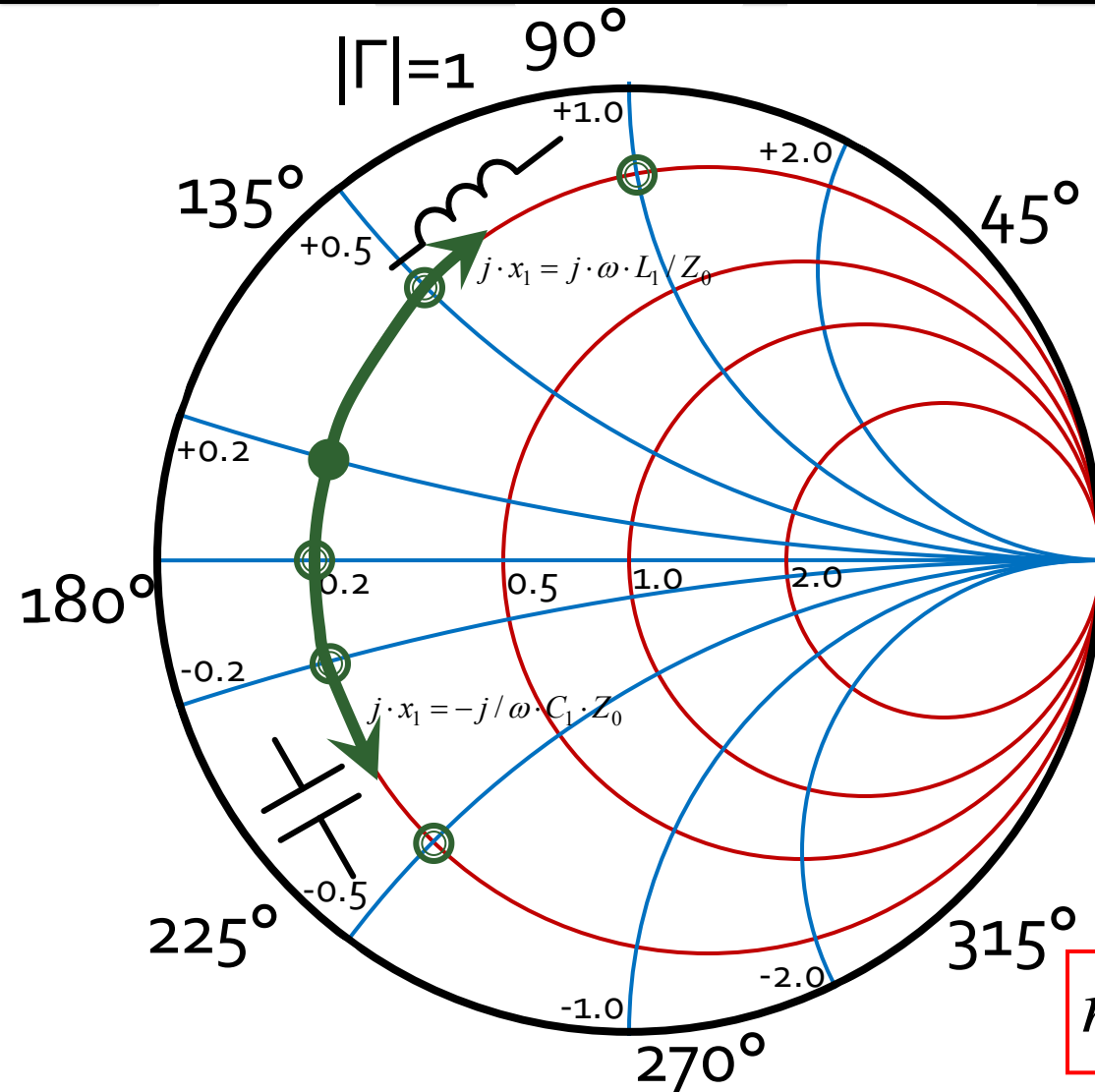

$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$

$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_L + j \cdot X_1 = R_L + j \cdot (X_L + X_1)$$



$$z_{in} = r_L + j \cdot (x_L + x_1)$$

$$r_{in} = r_L$$

$$j \cdot x_1 = j \cdot \omega \cdot L_1 / Z_0 > 0$$

$$j \cdot x_1 = -j / \omega \cdot C_1 \cdot Z_0 < 0$$

# The Smith Chart, series resistance

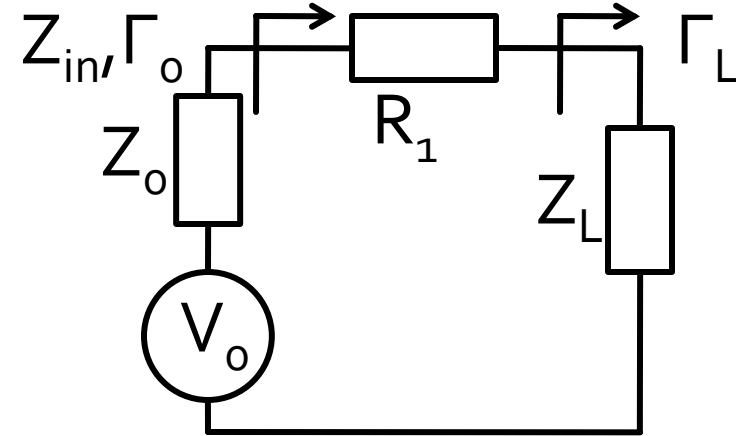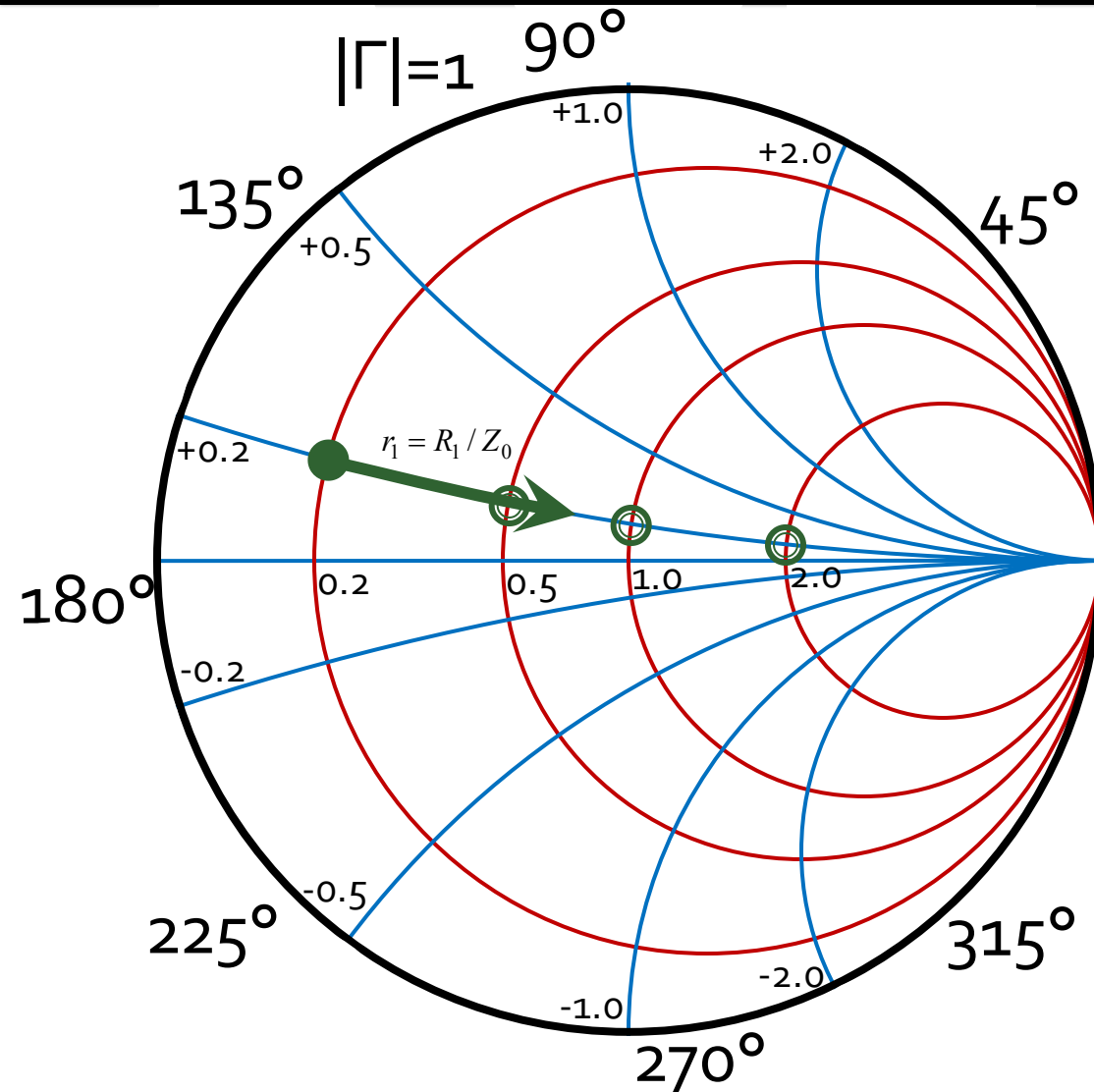

$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$



$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_L + R_1 = (R_L + R_1) + j \cdot X_L$$

$$z_{in} = z_L + r_1 = (r_L + r_1) + j \cdot x_L$$

$$x_{in} = x_L \quad r_{in} = r_L + R_1 / Z_0$$
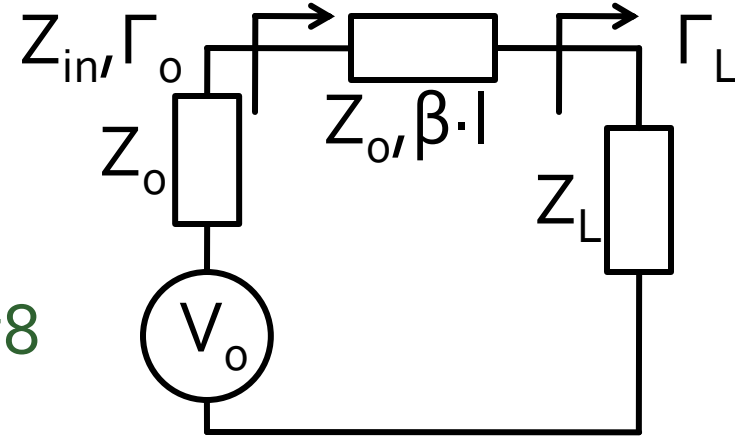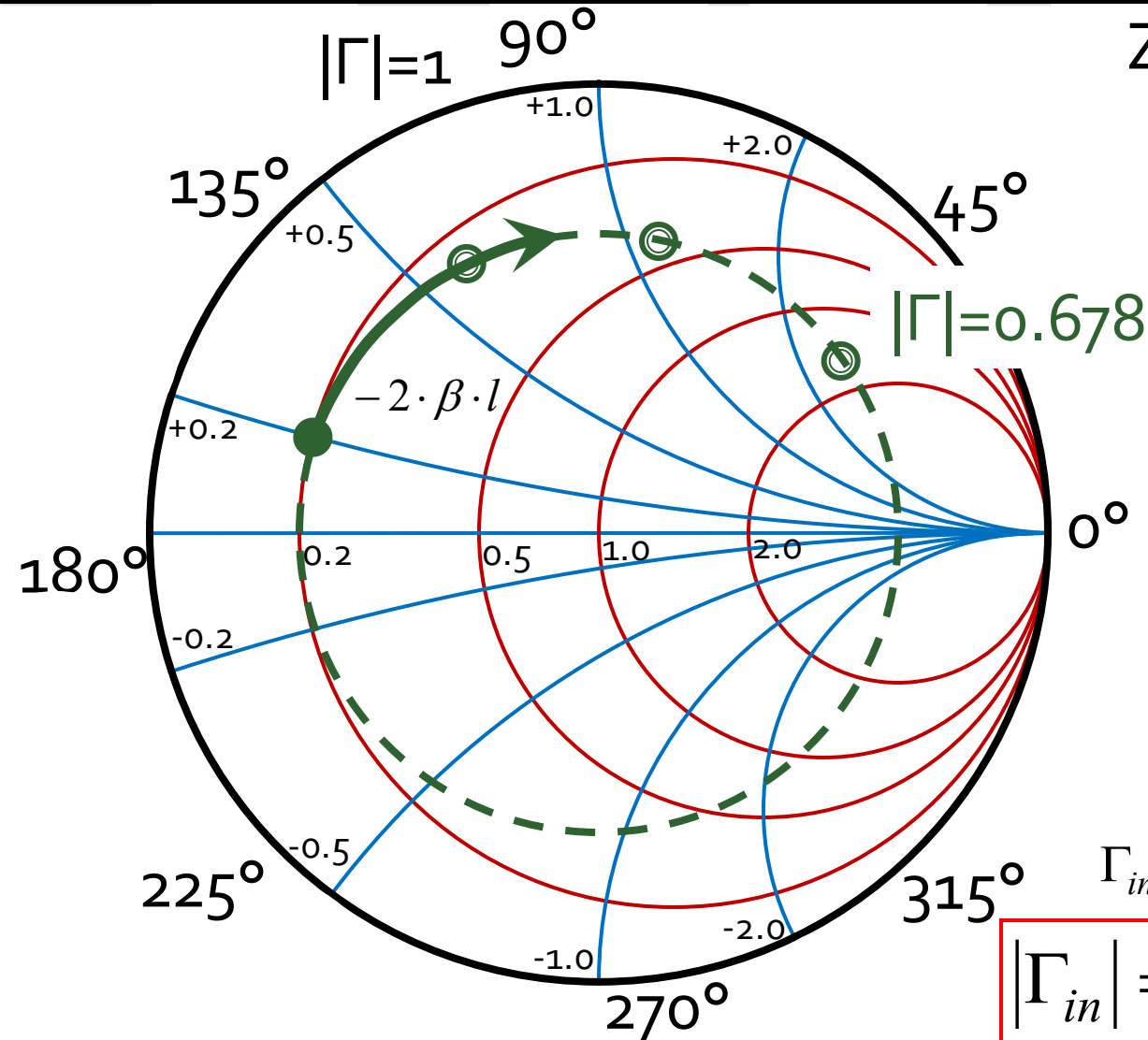
# The Smith Chart, series transmission line, $Z_0$



$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$



$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_0 \cdot \frac{1 + \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}}{1 - \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}}$$

$$\Gamma_{in} = \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}$$

$$|\Gamma_{in}| = |\Gamma_L| \quad \arg(\Gamma_{in}) = \arg(\Gamma_L) - 2 \cdot \beta \cdot l$$

# The Smith Chart, shunt susceptance

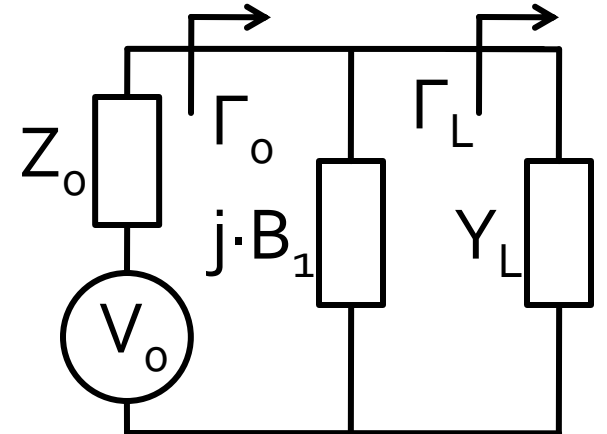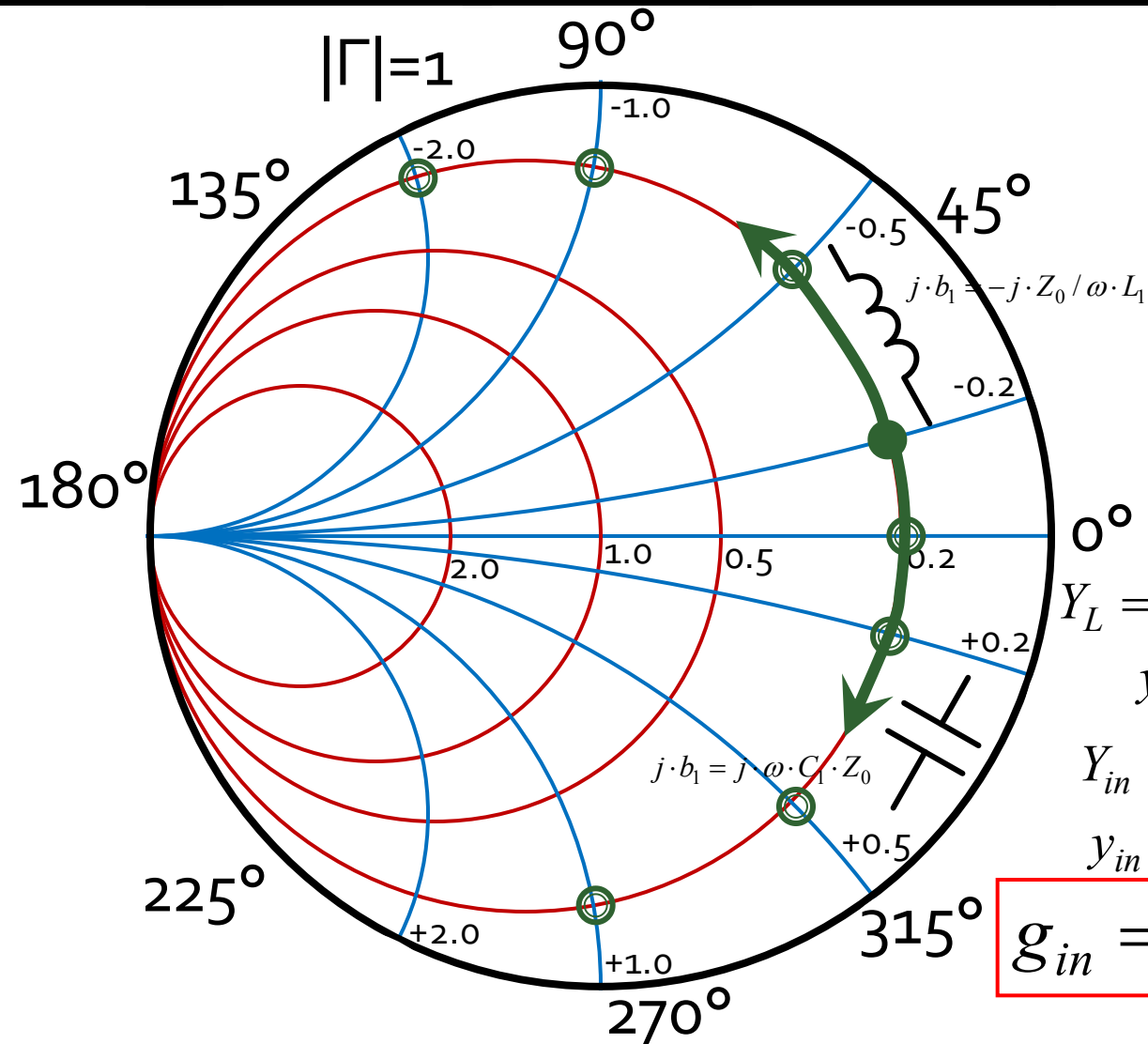

$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$\Gamma_L = 0.678 \angle 23.5^\circ$$

$$Y_L = G_L + j \cdot B_L = 0.004S + j \cdot 0.004$$

$$y_L = g_L + j \cdot b_L = 0.2 - j \cdot 0.2$$

$$Y_{in} = Y_L + j \cdot B_1 = G_L + j \cdot (B_L + B_1)$$



$$y_{in} = g_L + j \cdot (b_L + b_1)$$

$$g_{in} = g_L$$

$$j \cdot b_1 = j \cdot \omega \cdot C_1 \cdot Z_0 > 0$$

$$j \cdot b_1 = -j \cdot Z_0 / \omega \cdot L_1 < 0$$

# The Smith Chart, shunt conductance

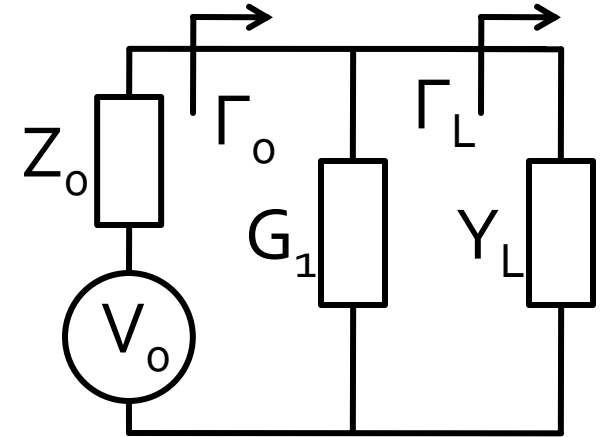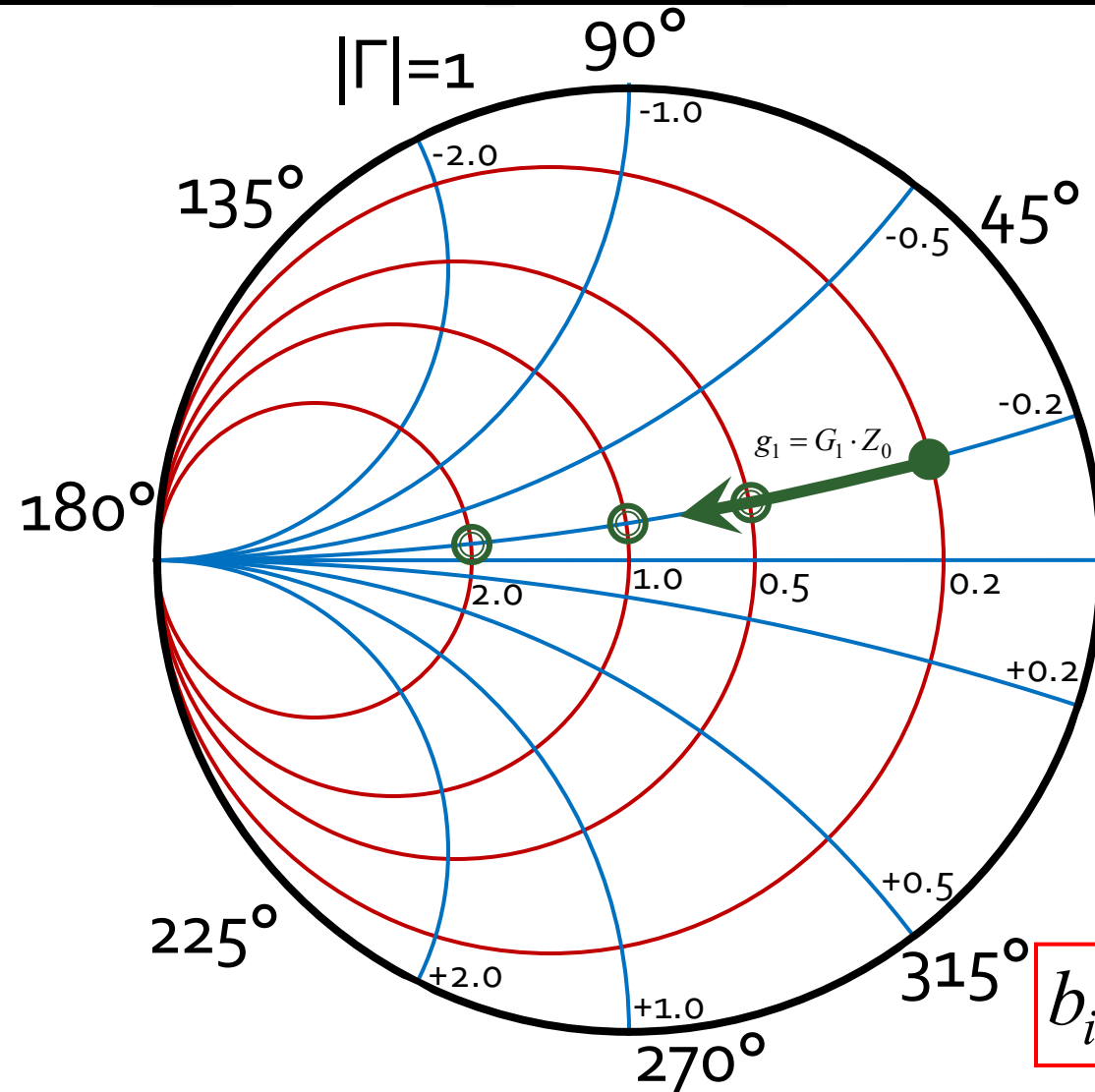

$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$\Gamma_L = 0.678 \angle 23.5^\circ$$

$$Y_L = G_L + j \cdot B_L = 0.004S + j \cdot 0.004$$

$$y_L = g_L + j \cdot b_L = 0.2 - j \cdot 0.2$$



$$Y_{in} = Y_L + G_1 = (G_L + G_1) + j \cdot B_L$$

$$y_{in} = (g_L + g_1) + j \cdot b_L$$

$$b_{in} = b_L$$

$$g_{in} = g_L + G_1 \cdot Z_0$$

# Impedance matching

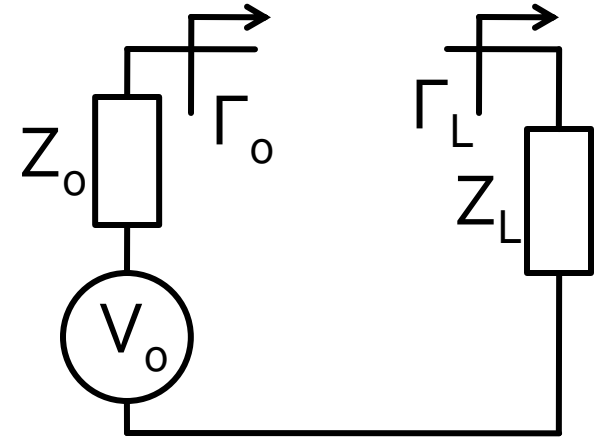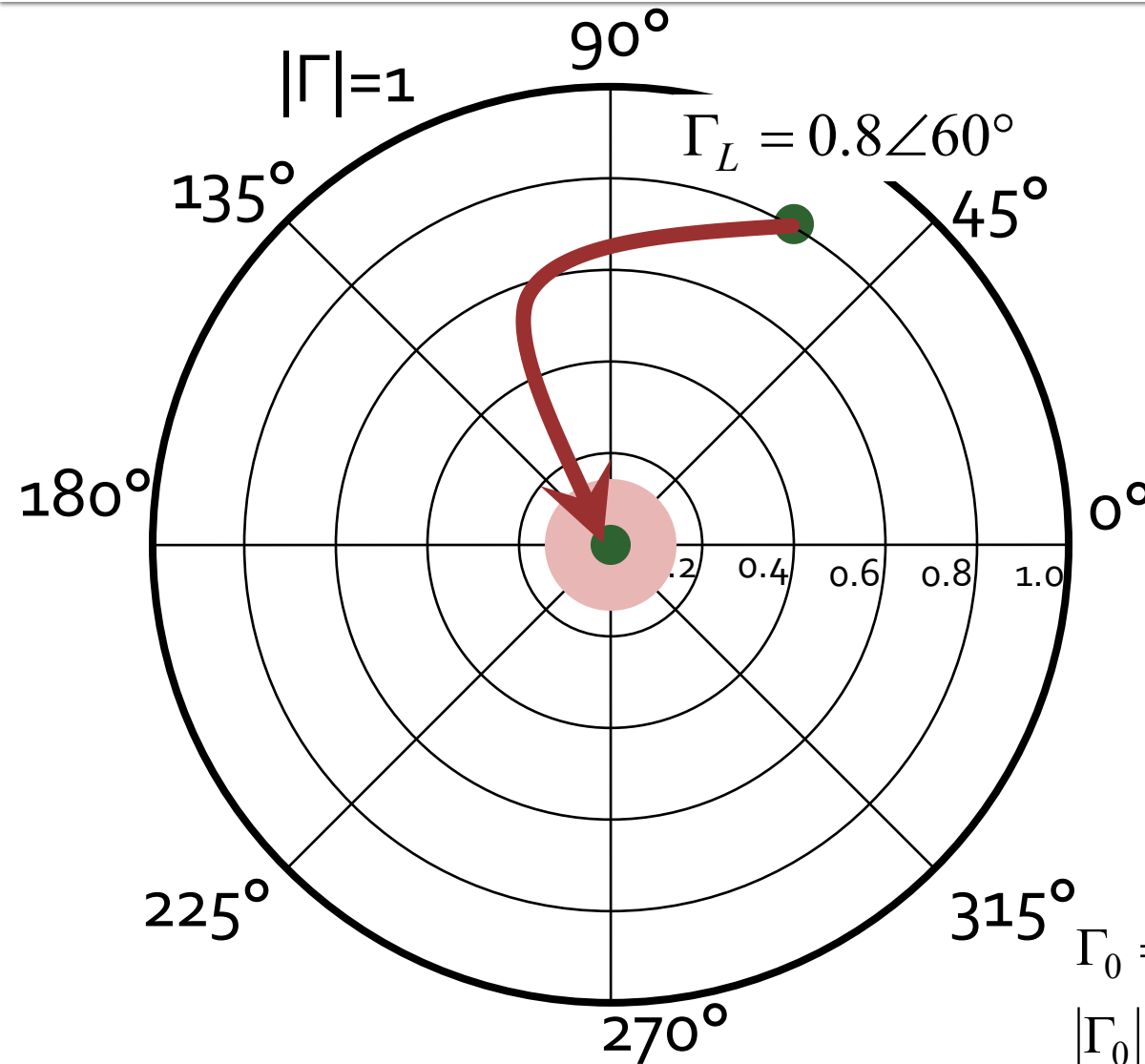



## How?

$\Gamma_0 = 0$  perfect match ●

$|\Gamma_0| \leq \Gamma_m$  "good enough" match ●



# Matching, shunt susceptance

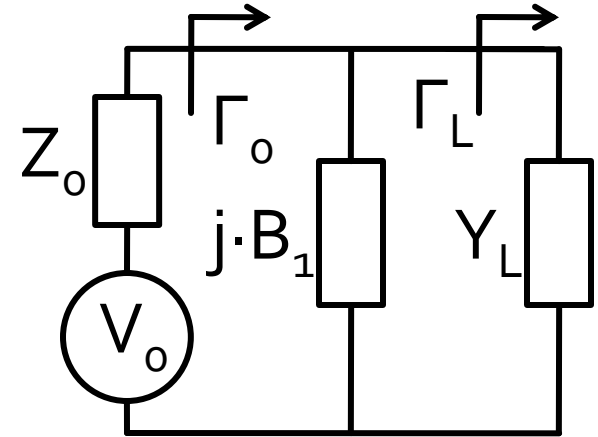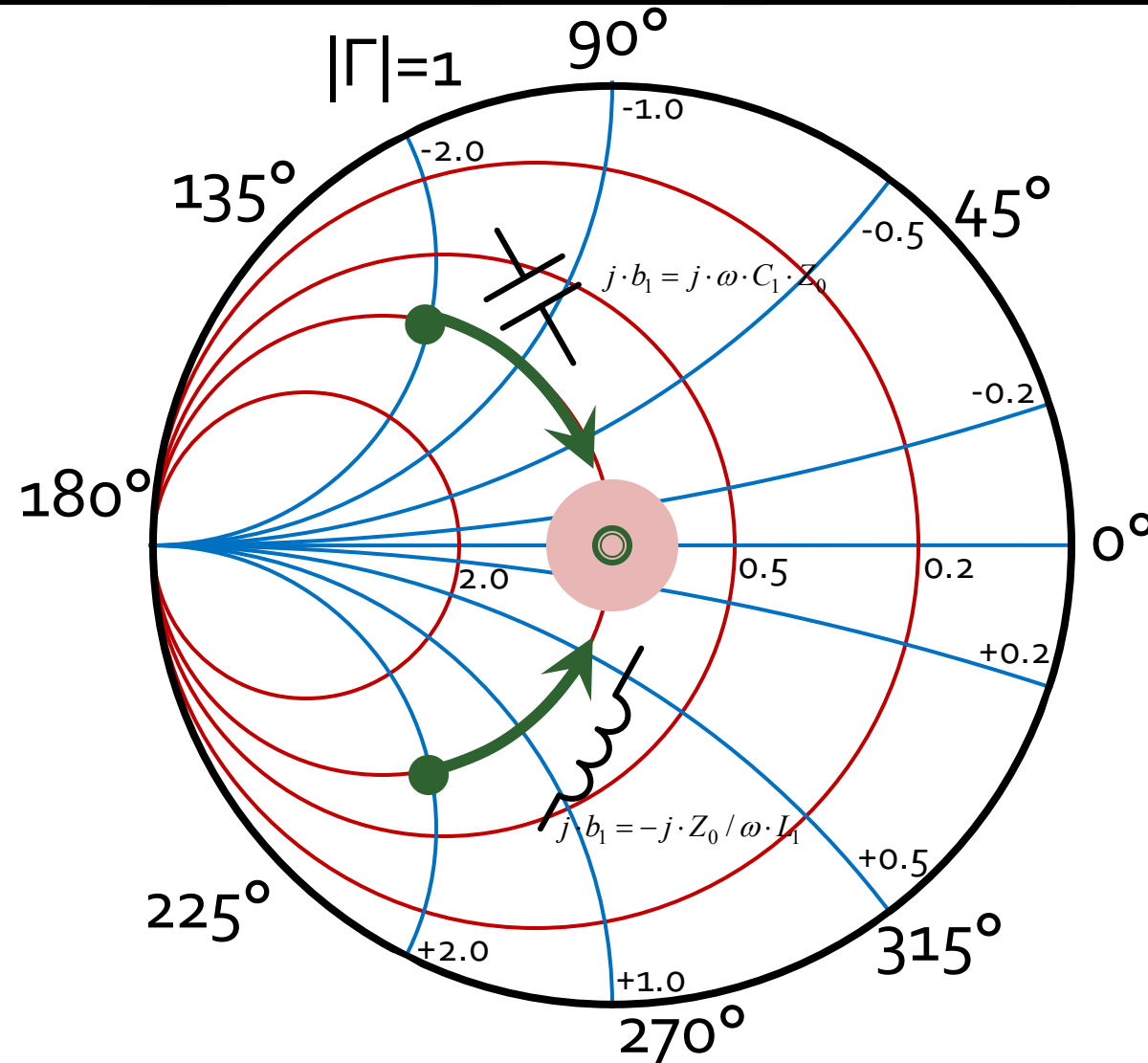

$$y_L = g_L + j \cdot b_L$$


$$y_{in} = g_L + j \cdot (b_L + b_1)$$

$$g_{in} = g_L$$



- Match can be obtained **if and only if**  $g_L = 1$
- we compensate the reactive part of the load  

$$j \cdot b_1 = -j \cdot b_L$$

# Smith chart, $r=1$ and $g=1$


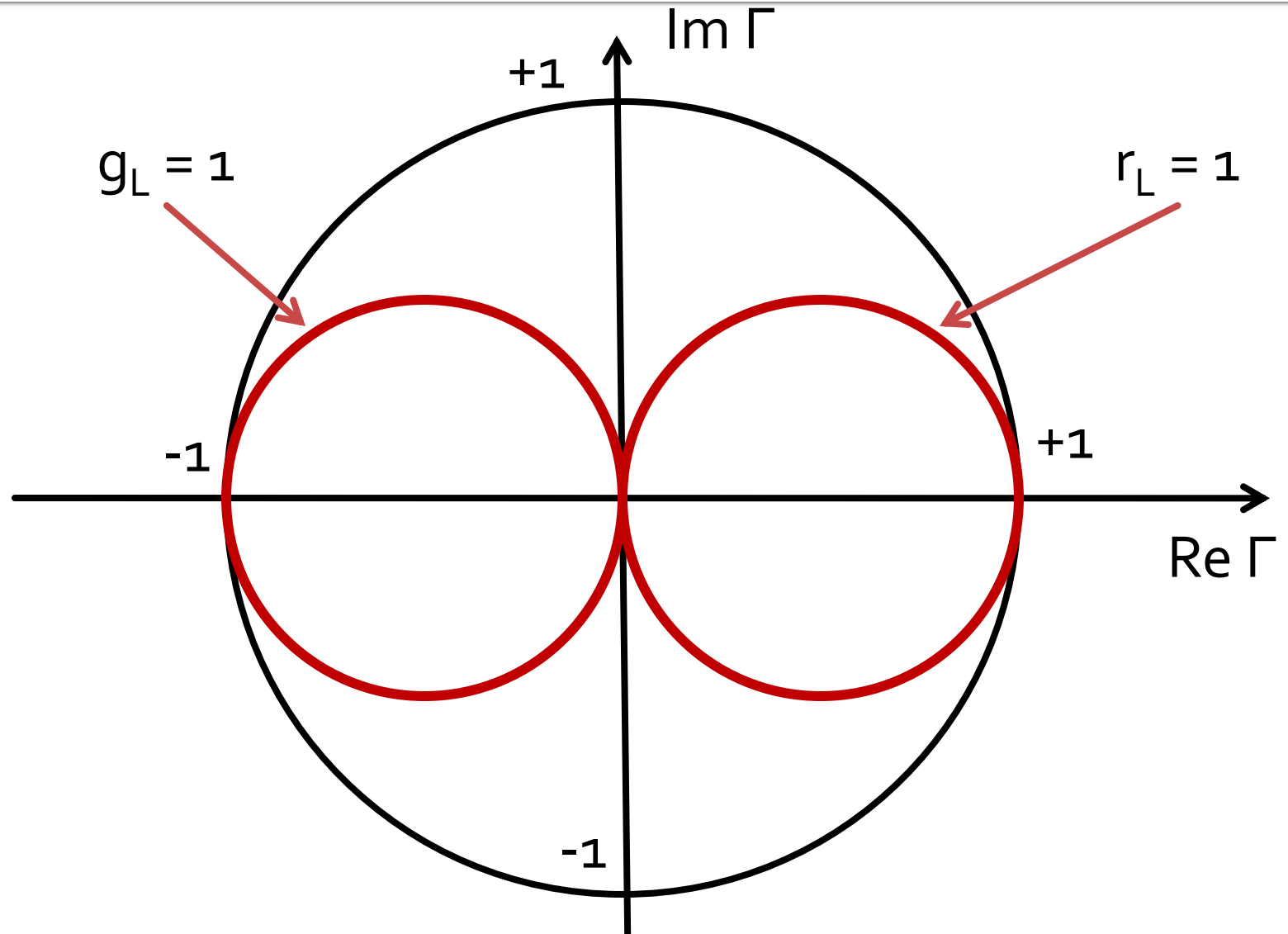

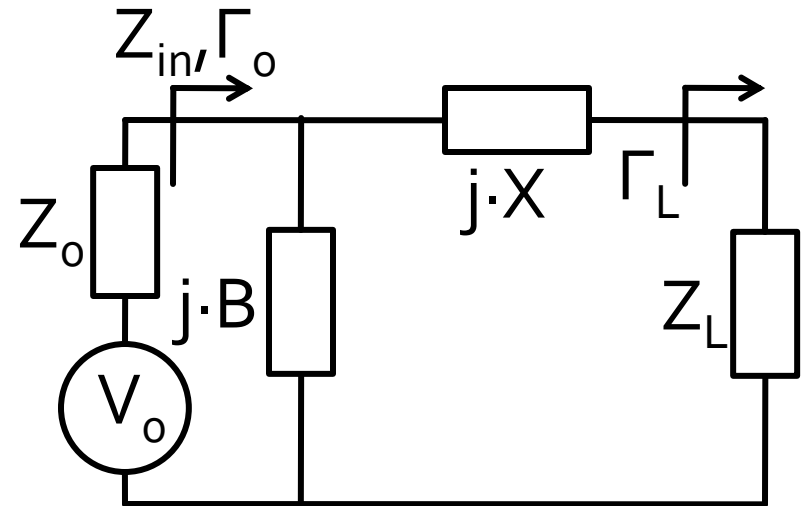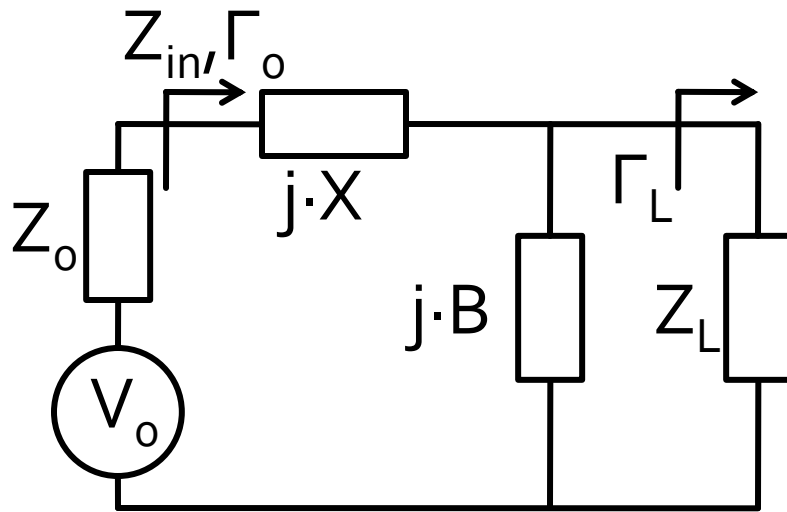
# Matching with 2 reactive elements (L Networks)





- Two steps matching
  - first reactive element moves the reflection coefficient **on the circle**  $r_L = 1/g_L = 1$
  - second element compensates the remaining reactance and achieves the impedance match



# series C, shunt C / shunt C, series C

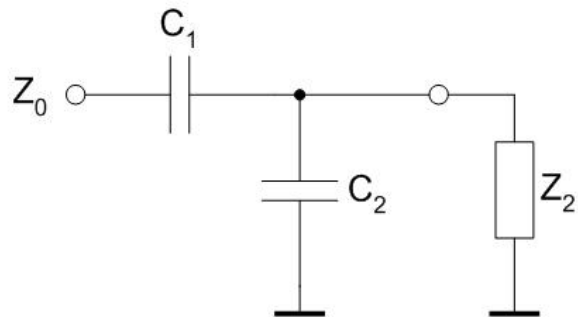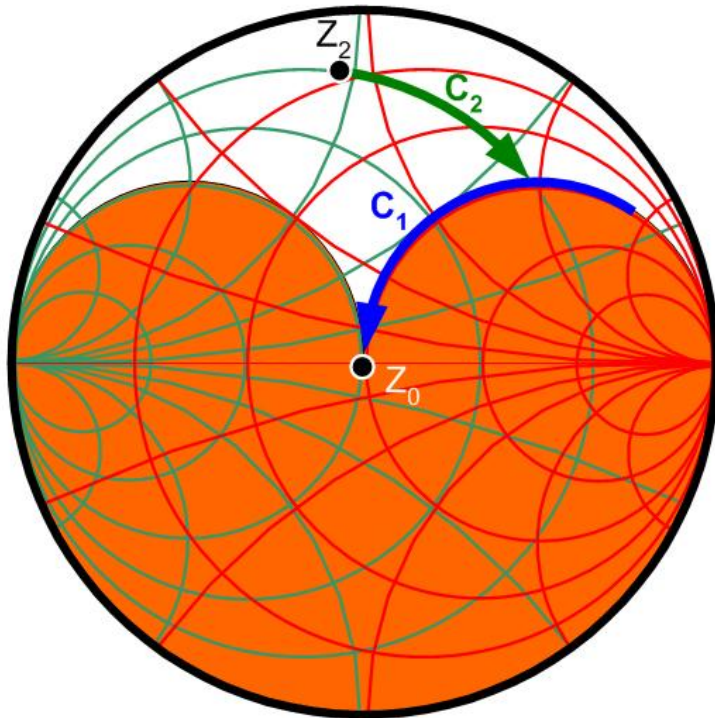



Forbidden area for current network

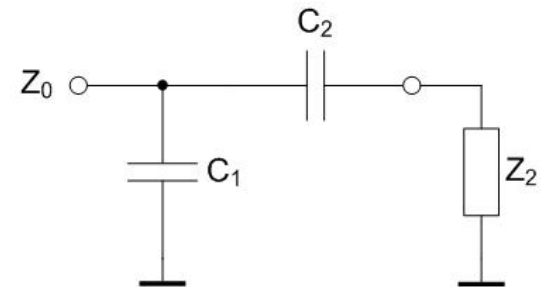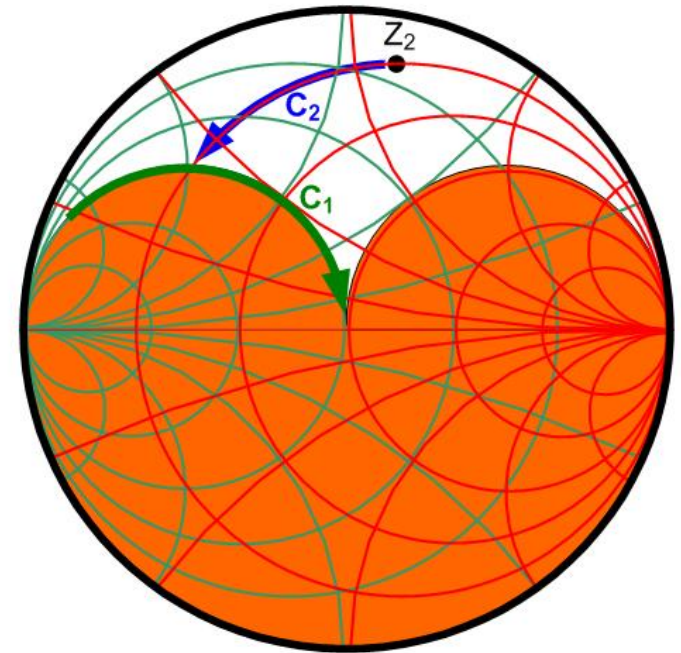



# series L, shunt L / shunt L, series L

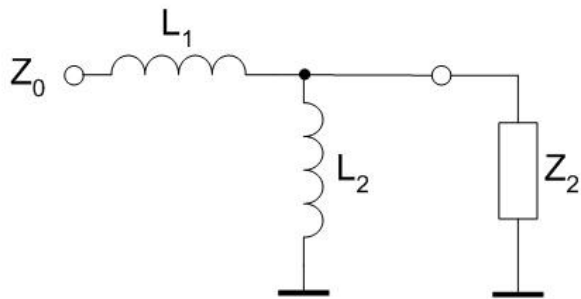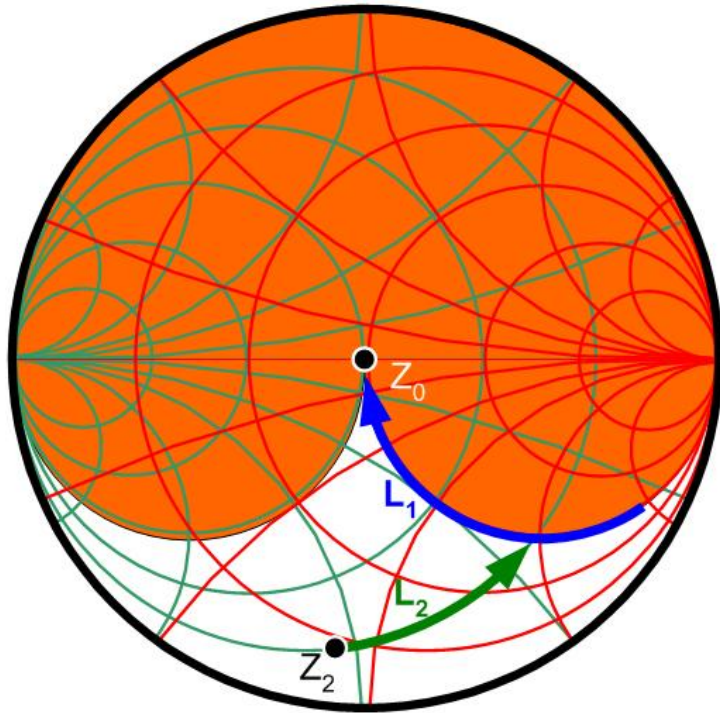



Forbidden area for current network

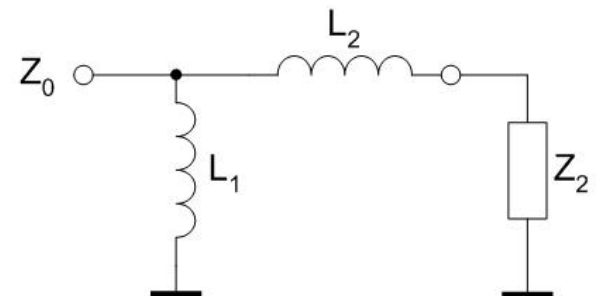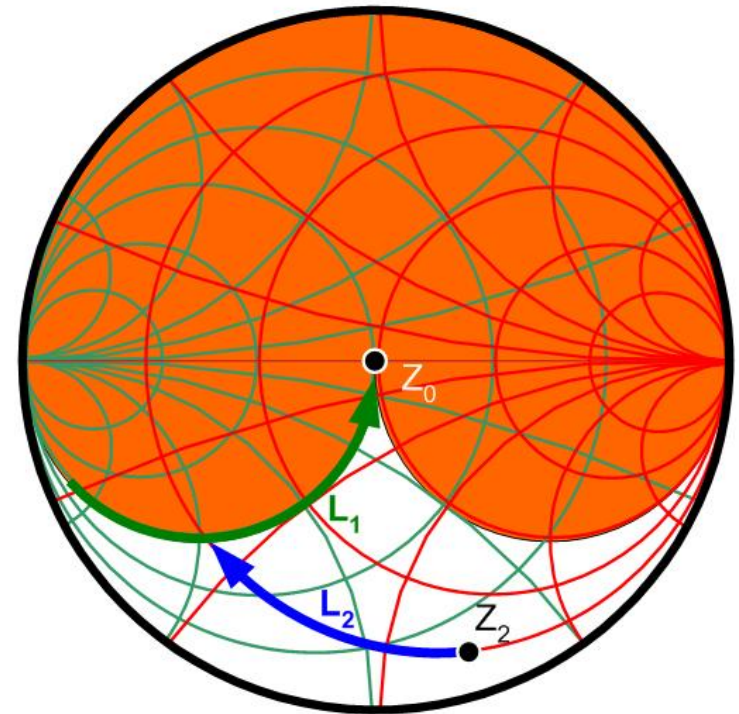



# series L, shunt C / shunt C, series L

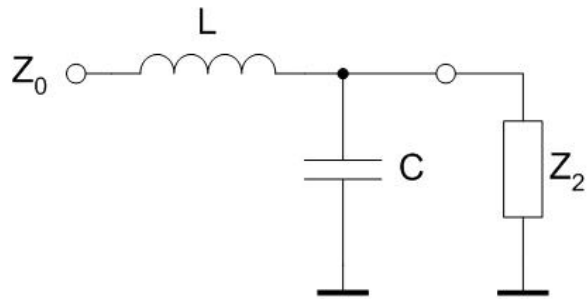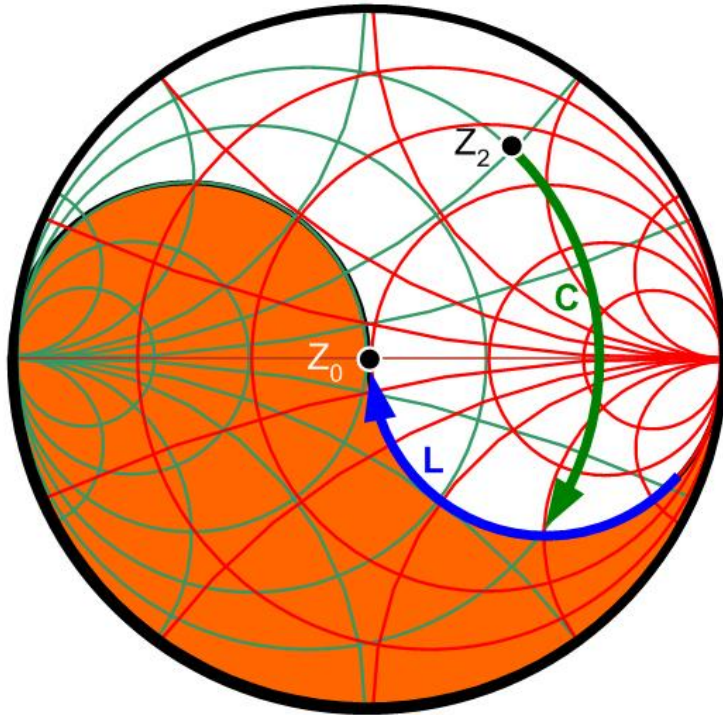



Forbidden area for current network

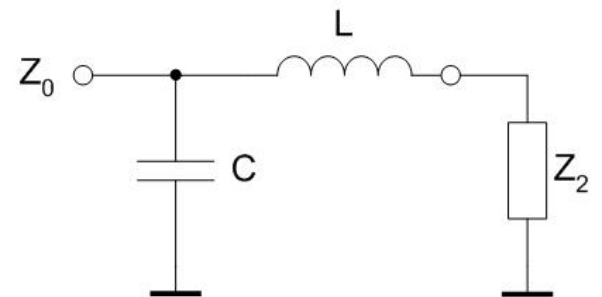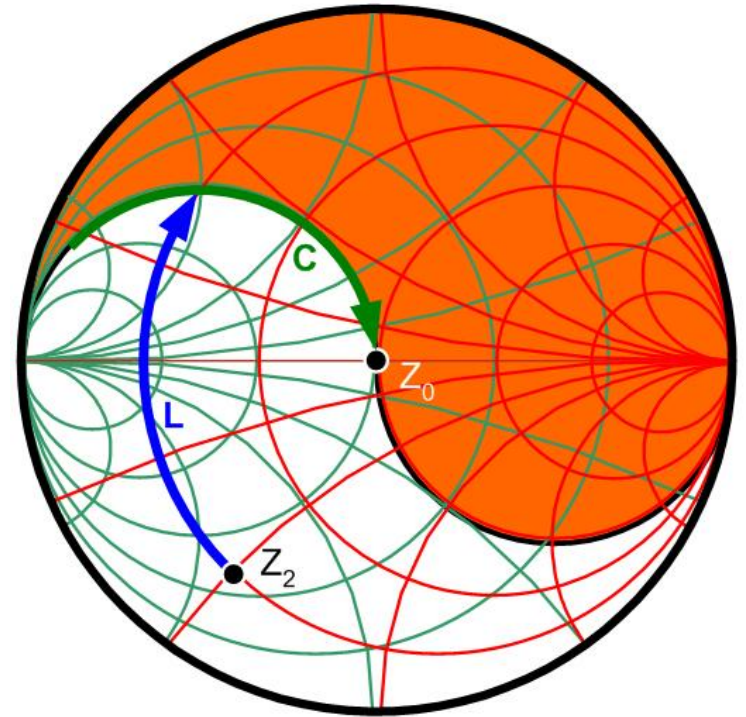


# series C, shunt L / shunt L, series C

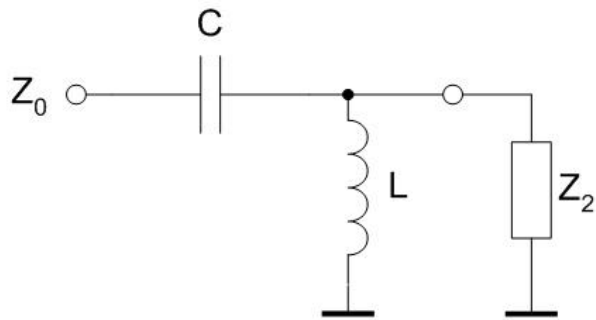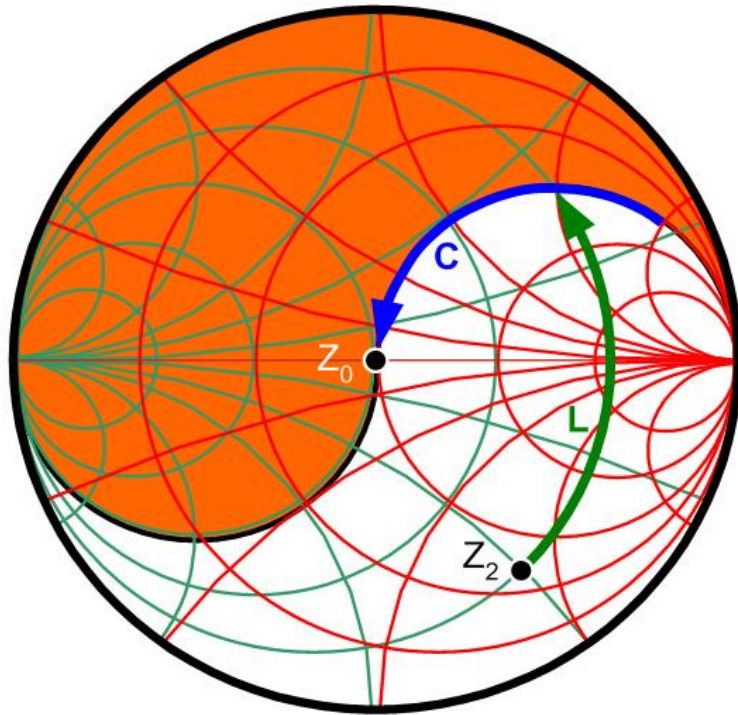

Forbidden area for current network

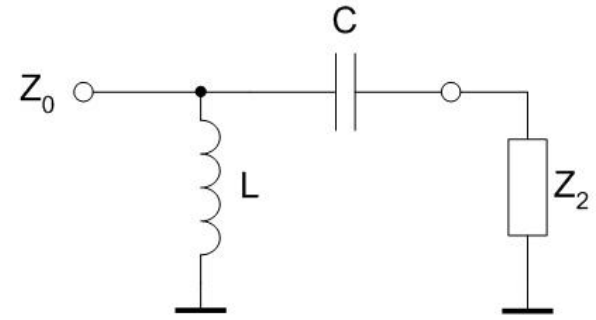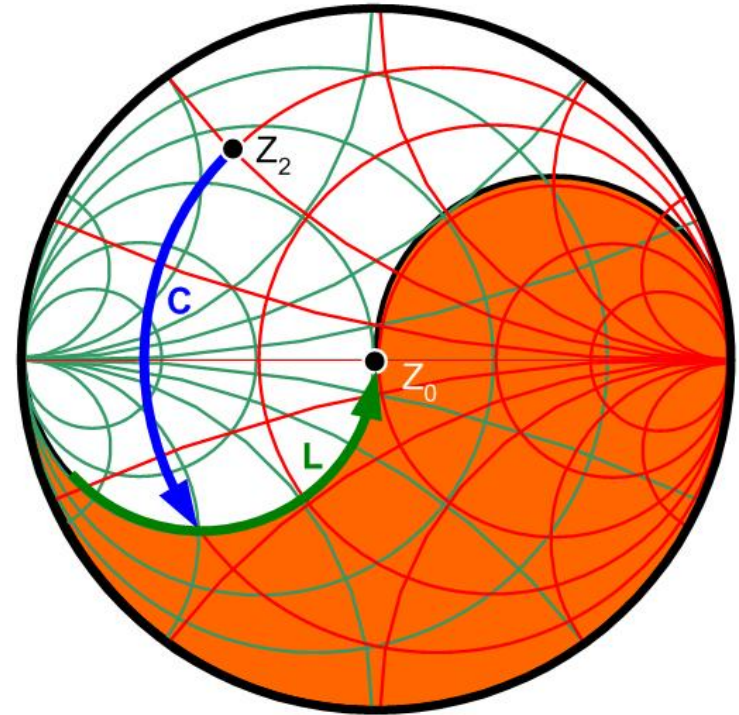
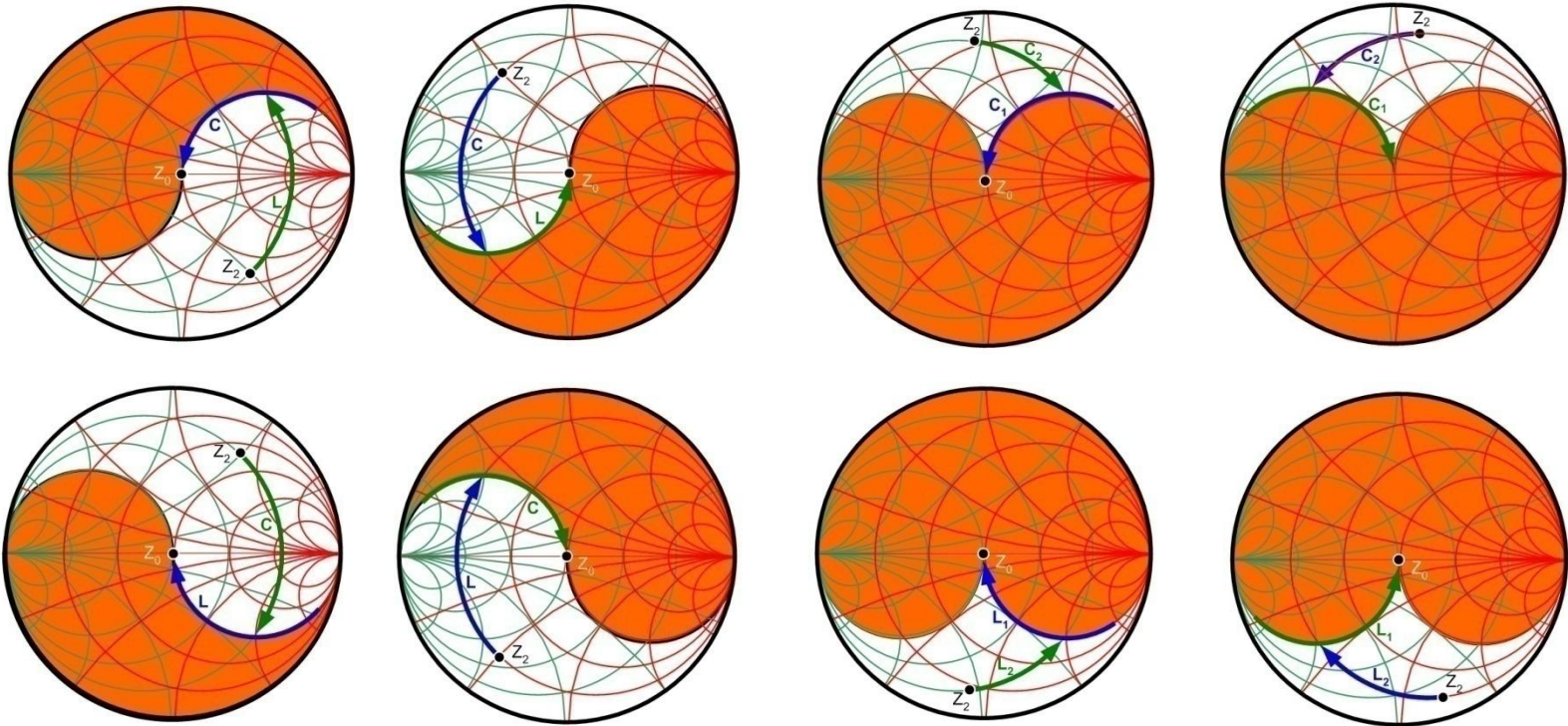
# Matching with 2 reactive elements (L Networks)



Forbidden area for  
current network

# Matching with 2 reactive elements (L Networks)



- For any  $\Gamma_L$  there are at least 2 possible L networks to achieve match (L+C)
- For some starting areas on the Smith Chart there are 4 possibilities (+2 C+C/L+L networks)
- We choose the network that requires components with existent/practically realizable values
- By adding the resistive elements, we can supplement the number of networks but with **loss of signal power (not recommended)**

# Matching with resistive elements

- In microwave frequencies active circuits work very near to the transition frequency  $f_T$
- Any “waste” of signal power **is not recommended**
- Sometimes such an action might be **necessary** to insure device stability



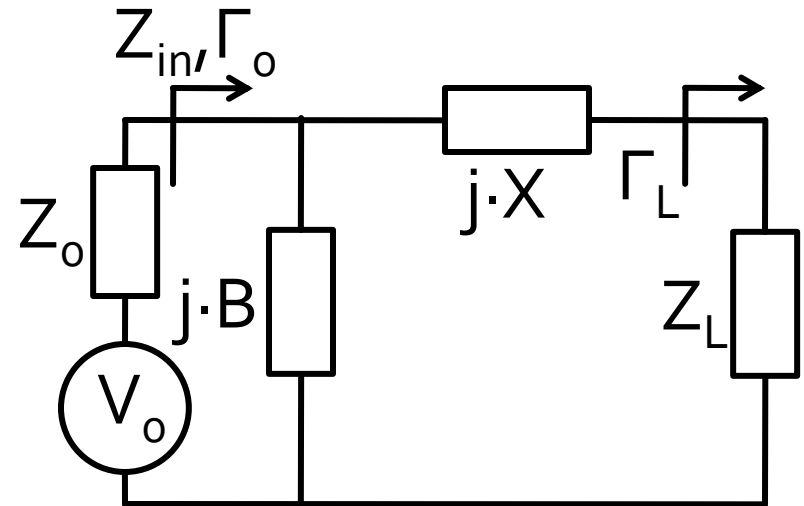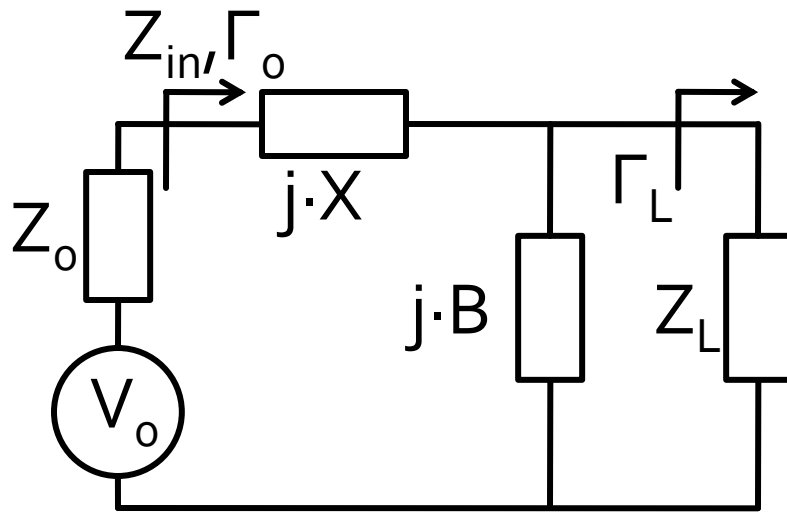
# Matching with 2 reactive elements (L Networks)



- Two step matching
  - for starting reflection coefficient inside the  $r_L = 1$  circle we must use first schematic
  - for starting reflection coefficient outside the  $r_L = 1$  circle we must use second schematic
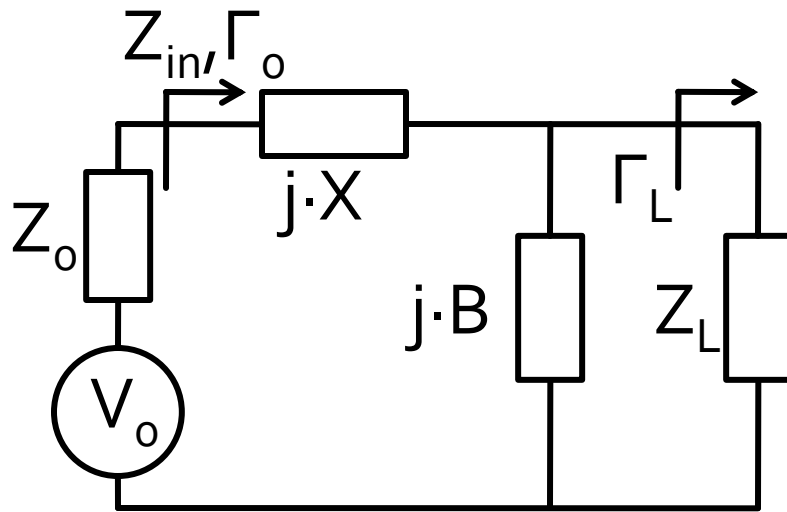
# Matching with 2 reactive elements (L Networks)



$$Z_L = R_L + j \cdot X_L \quad R_L > Z_0 \quad Z_{in} = Z_0$$

$$Z_0 = j \cdot X + \frac{1}{j \cdot B + 1/(R_L + j \cdot X_L)}$$

$$\begin{cases} B \cdot (X \cdot R_L - X_L \cdot Z_0) = R_L - Z_0 \\ X \cdot (1 - B \cdot X_L) = B \cdot Z_0 \cdot R_L - X_L \end{cases}$$

$$B = \frac{X_L \pm \sqrt{R_L/Z_0} \cdot \sqrt{R_L^2 + X_L^2 - Z_0 \cdot R_L}}{R_L^2 + X_L^2}$$


$$X = \frac{1}{B} + \frac{X_L \cdot Z_0}{R_L} - \frac{Z_0}{B \cdot R_L}$$

- the argument of the second square root is always positive for:

$$R_L > Z_0$$

- two physically realizable solutions are possible for B and X
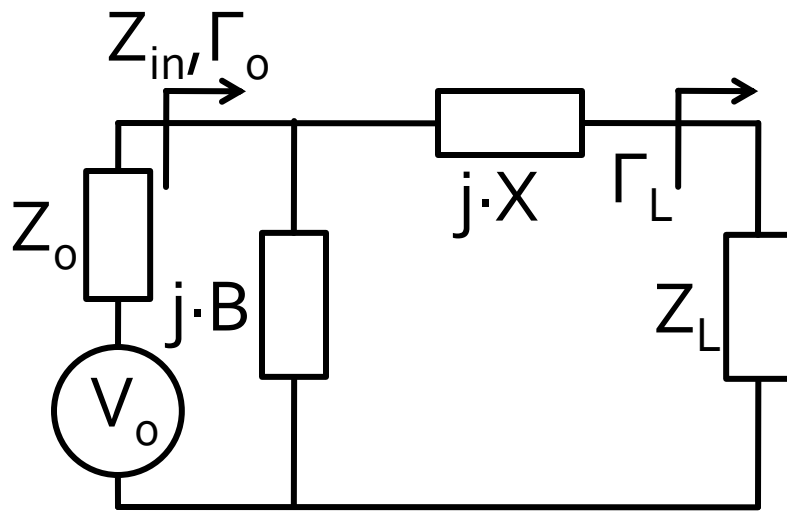
# Matching with 2 reactive elements (L Networks)



$$Z_L = R_L + j \cdot X_L \quad R_L < Z_0 \quad Y_{in} = Y_0 = \frac{1}{Z_0}$$

$$\frac{1}{Z_0} = j \cdot B + \frac{1}{R_L + j \cdot (X + X_L)}$$

$$\begin{cases} B \cdot Z_0 \cdot (X + X_L) = Z_0 - R_L \\ (X + X_L) = B \cdot Z_0 \cdot R_L \end{cases}$$

$$X = \pm \sqrt{R_L \cdot (Z_0 - R_L)} - X_L$$



$$B = \pm \frac{\sqrt{(Z_0 - R_L)/R_L}}{Z_0}$$

- the argument of the square root is always positive for:


$$R_L < Z_0$$

- two physically realizable solutions are possible for B and X


# Example

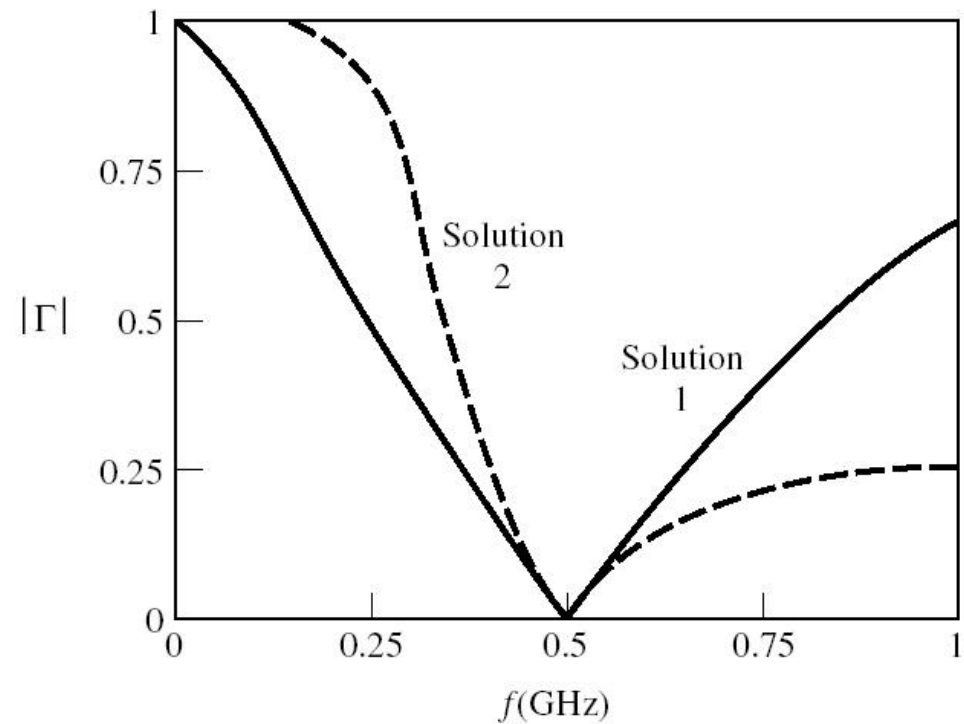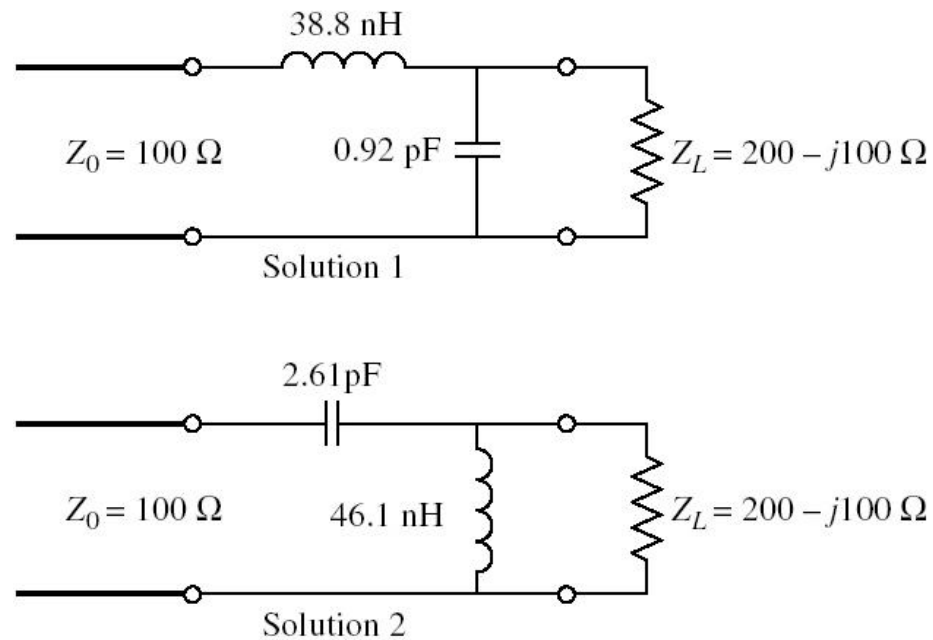

# Example

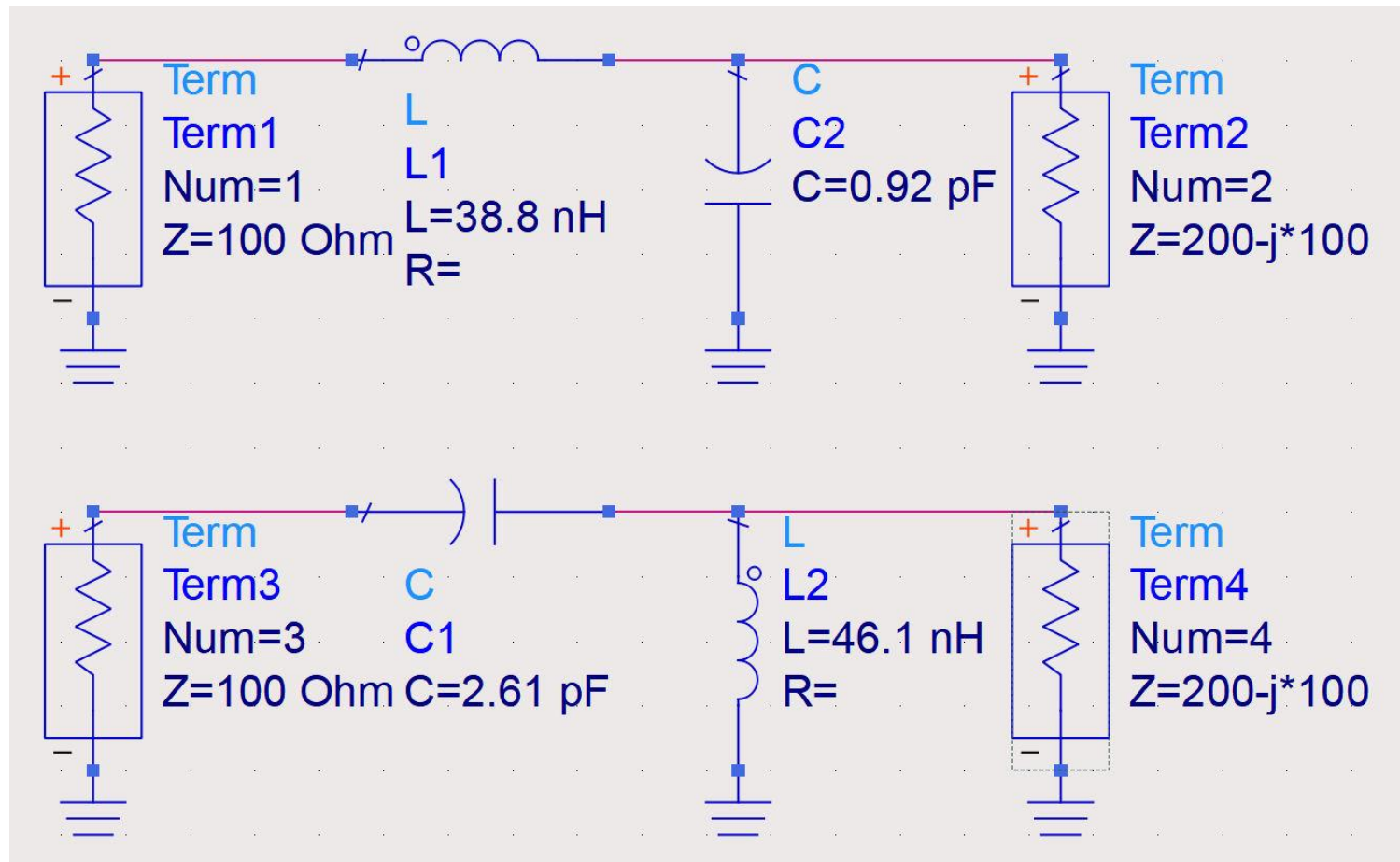



# Example

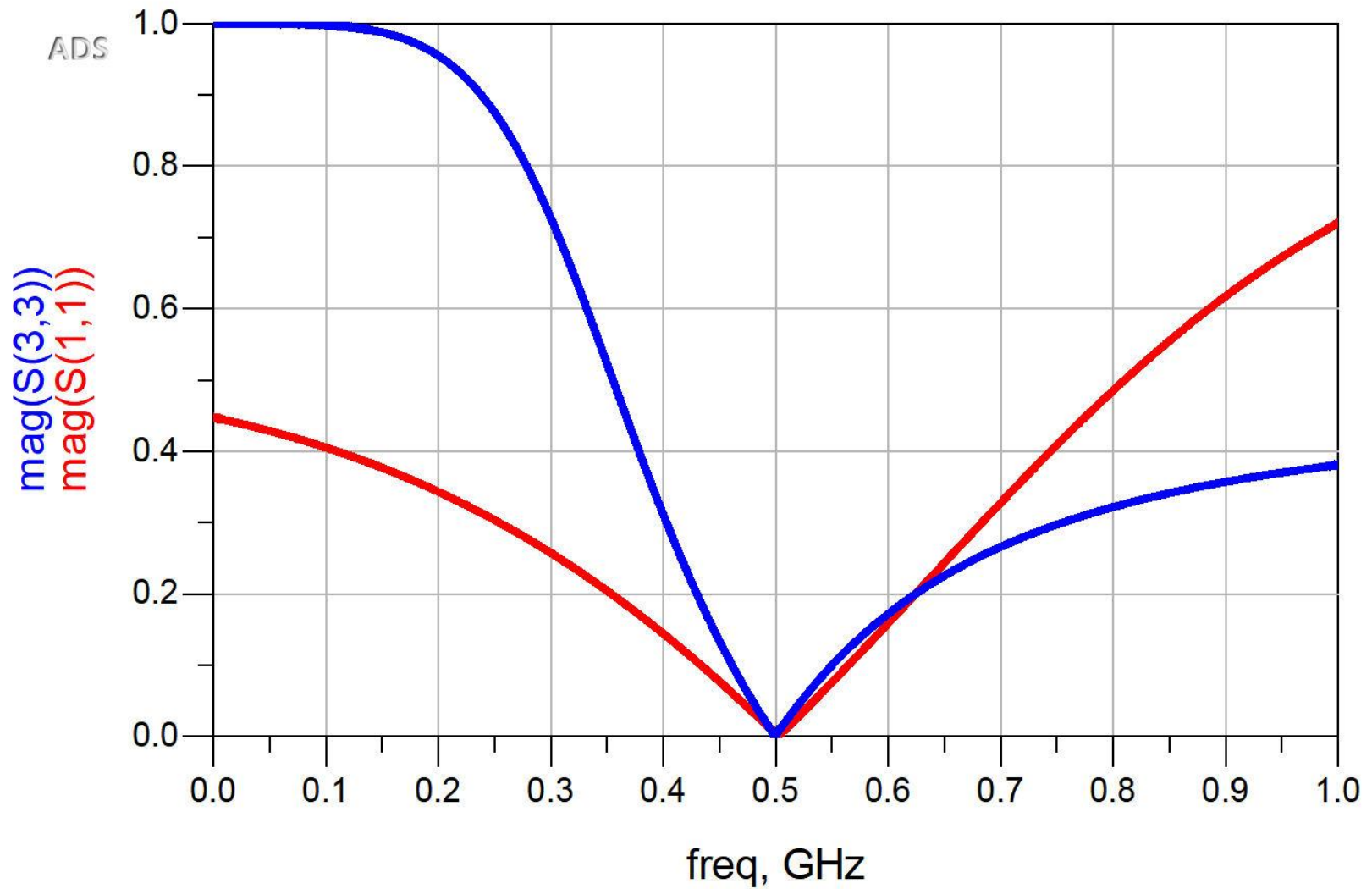
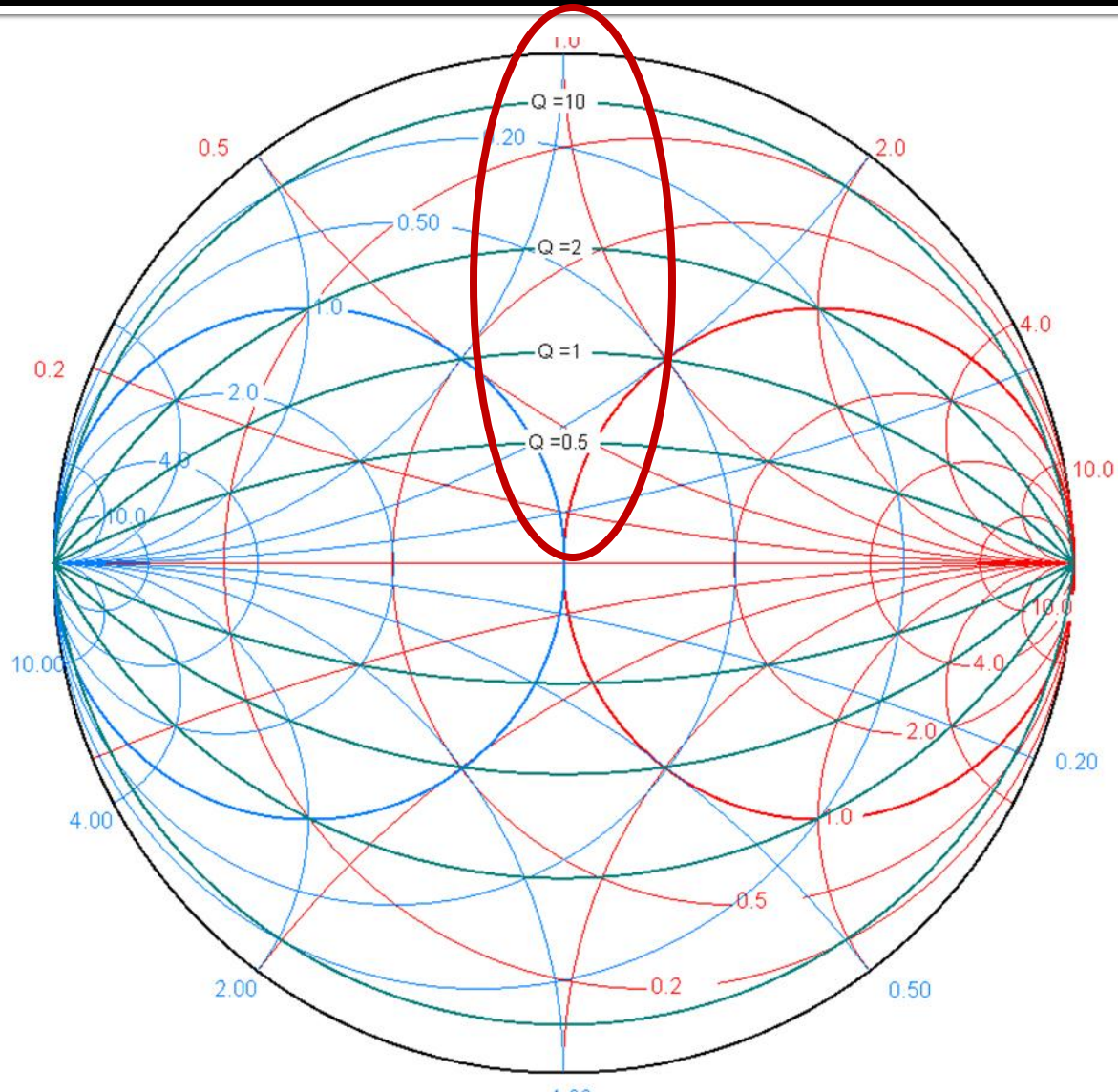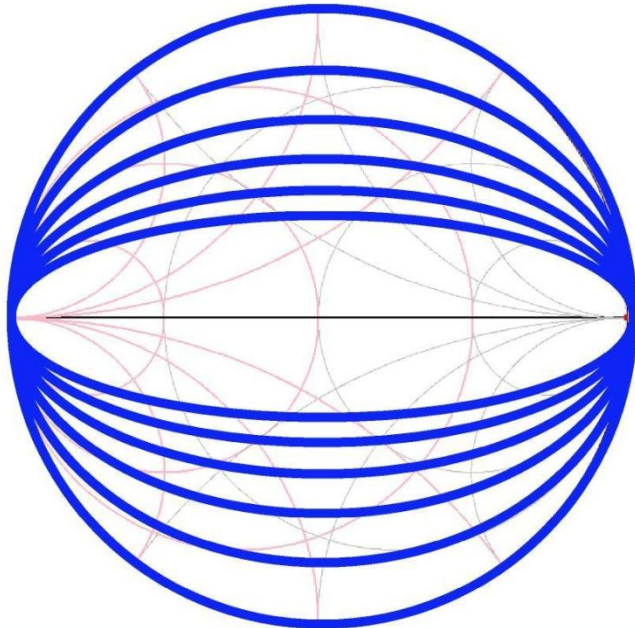
# Constant Q circles


- Quality factor Q

$$Q = \frac{X}{R} = \frac{G}{B} = \text{const}$$



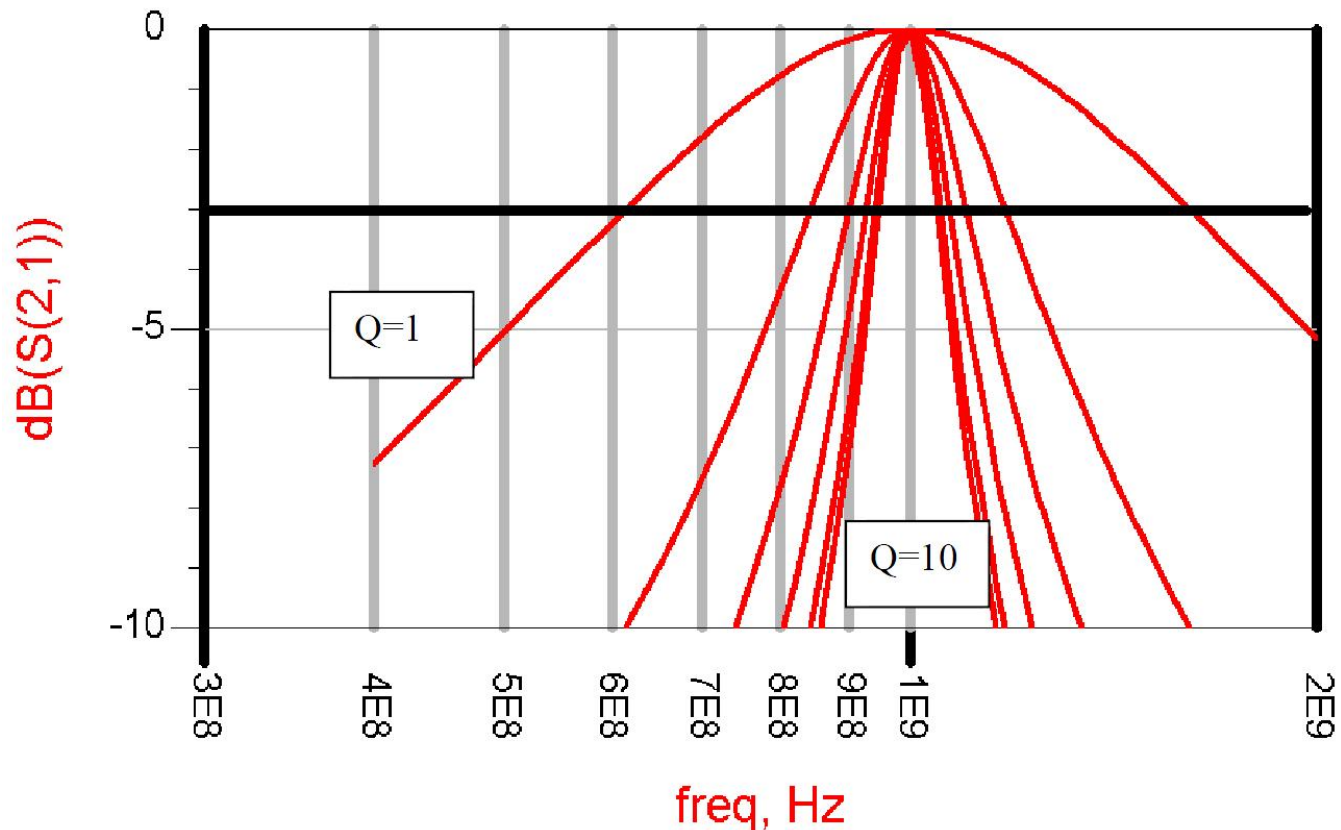
# Quality factor - bandwidth


- High quality factor is equivalent with narrow bandwidth




# Match bandwidth

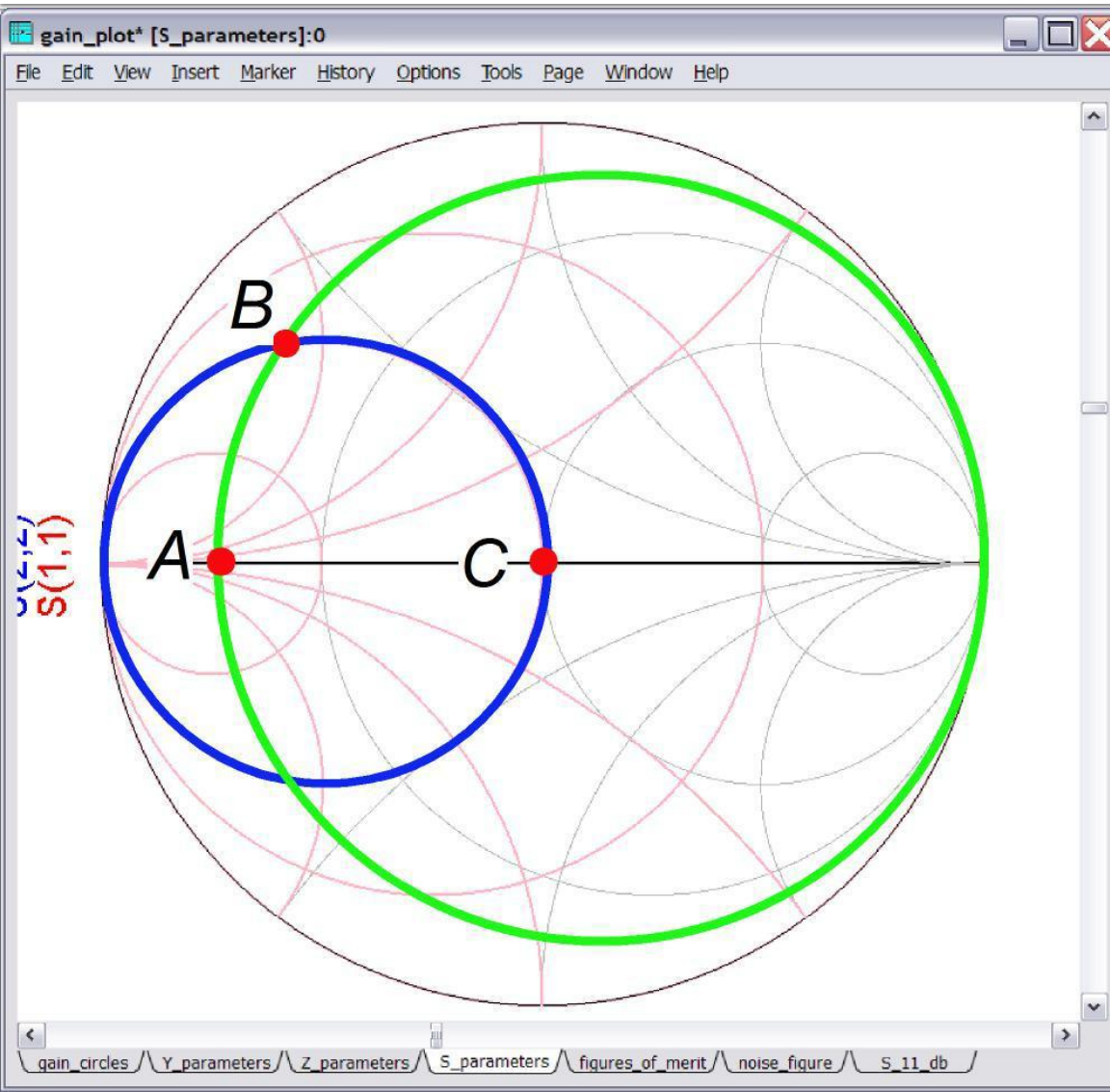

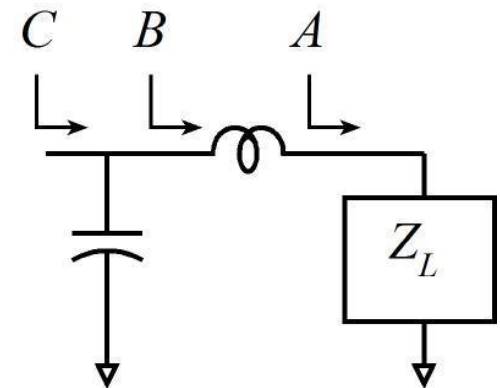
- The position with highest Q for intermediate reflection coefficients (B) imposes the match bandwidth




# Match bandwidth

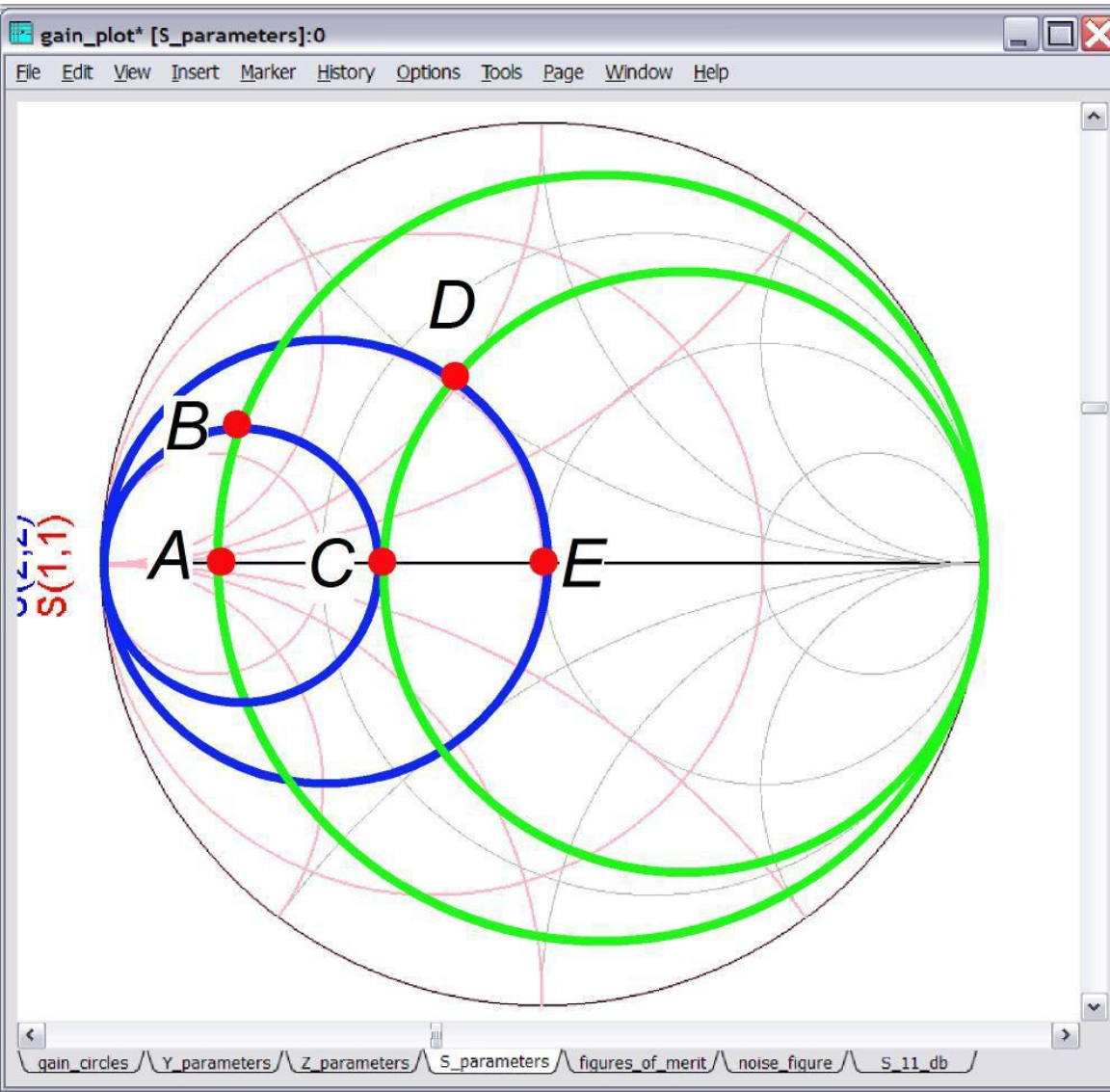

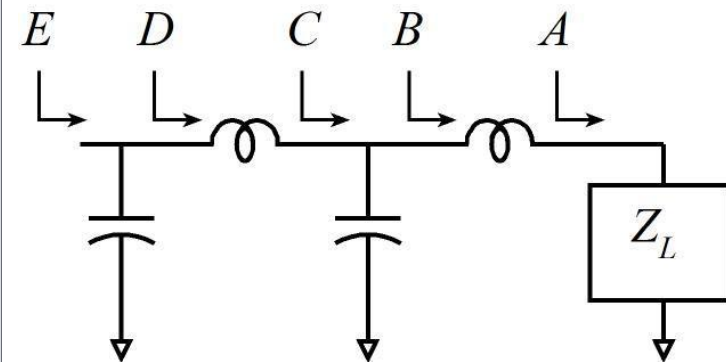
- Wider matching bandwidth can be obtained with multiple, smaller steps, insuring that all intermediate reflection coefficients (B, D) correspond to smaller Q




# Match bandwidth

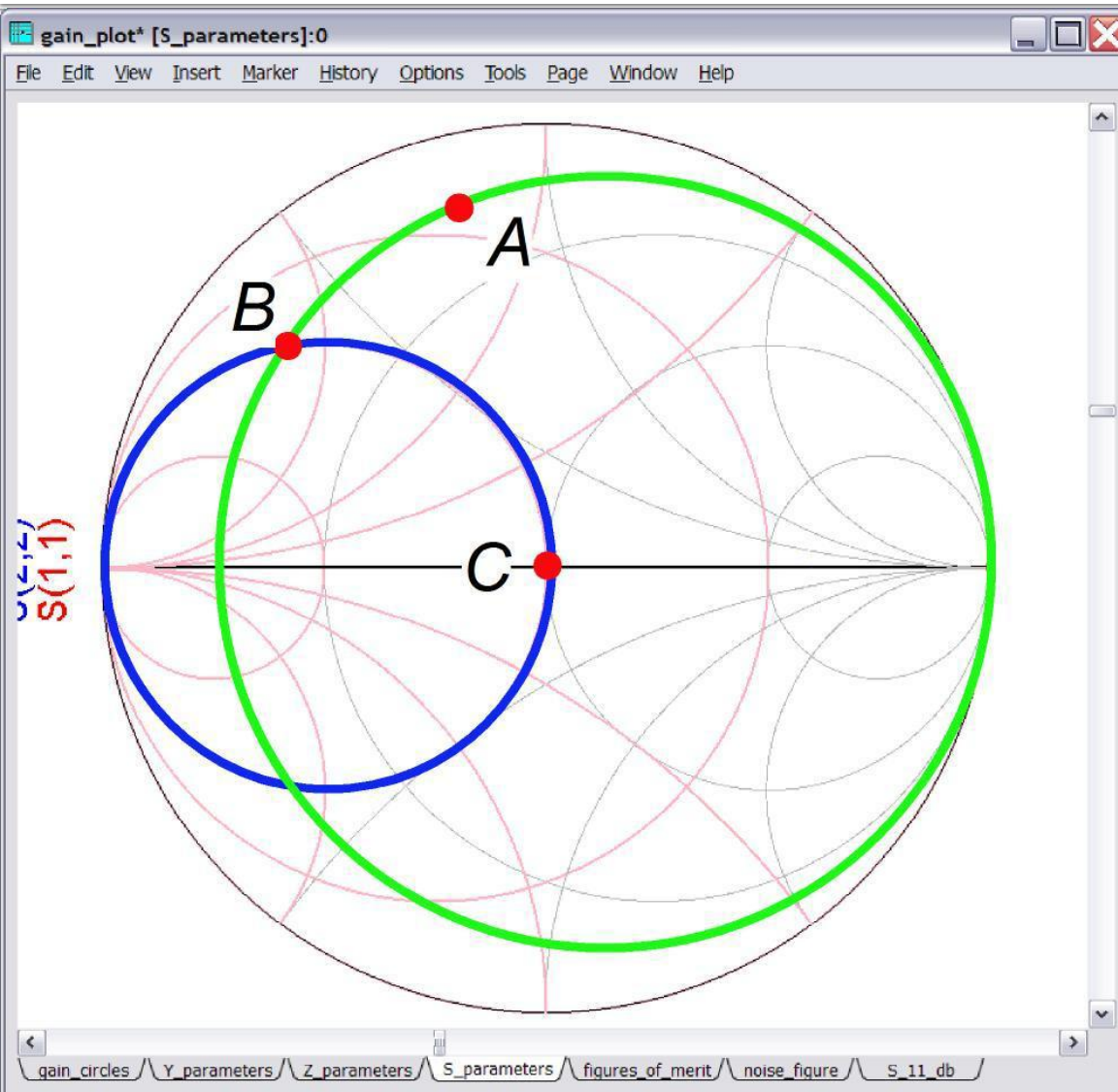

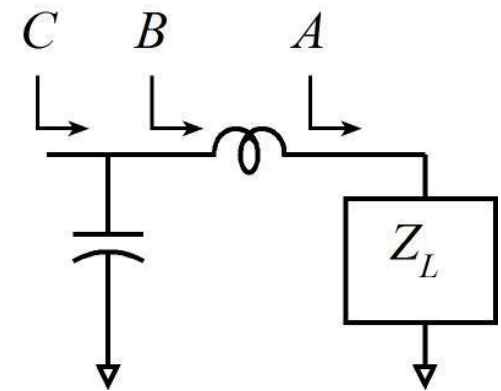- For high Q starting reflection coefficients (A) narrow bandwidth match is unavoidable


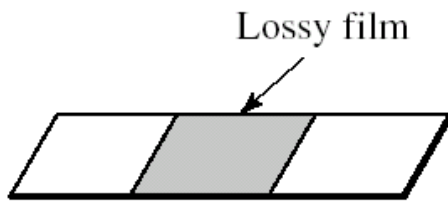
# Practical realization of lumped elements for microwave frequencies




Planar resistor


Lossy film



Chip resistor

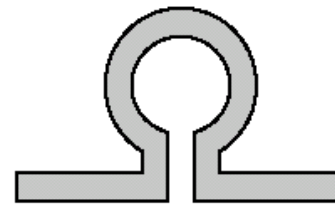


Loop inductor

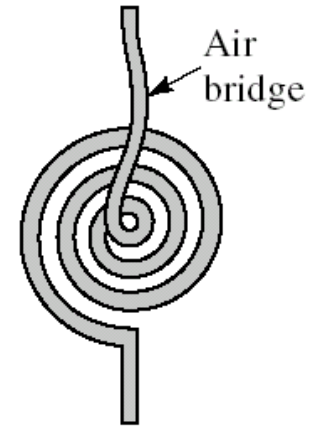


Spiral inductor



Interdigital gap capacitor

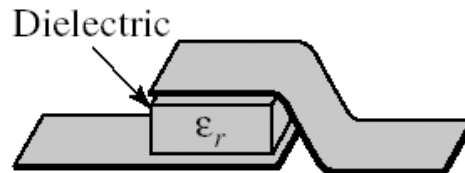

Metal-insulator-metal capacitor

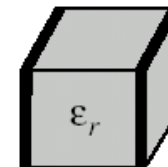

Chip capacitor

# Contact

- Microwave and Optoelectronics Laboratory
- <https://rf-opto.etti.tuiasi.ro>
- [rdamian@etti.tuiasi.ro](mailto:rdamian@etti.tuiasi.ro)