

Lecture 8

2025/2026

# Microwave Devices and Circuits for Radiocommunications

# 2025/2026

- 2C/1L, **MDCR**
- Attendance at minimum 7 sessions (course or laboratory)
- Lectures- **associate professor Radu Damian**
  - Tuesday **12-14, P2**
  - E – 50% final grade
  - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
    - first test L1: 24.02.2026 (t2 and t3 not announced, lecture)
    - 3att.=+0.5p
  - all materials/equipments authorized


# 2025/2026

- Laboratory – **associate professor Radu Damian**
  - Monday 14-16, Il.13 / (even weeks)
  - L – 25% final grade
    - ADS, 4 sessions
    - Attendance + **personal results**
  - P – 25% final grade
    - ADS, 3 sessions (-1? 24.02.2026)
    - personal homework

General theory


# Microwave Network Analysis

# Course Topics

- Transmission lines
  - Impedance matching and tuning
  - Directional couplers
  - Power dividers
  - Microwave amplifier design
  - Microwave filters
  - ~~Oscillators and mixers?~~
- 

# Scattering matrix – S

- Scattering parameters

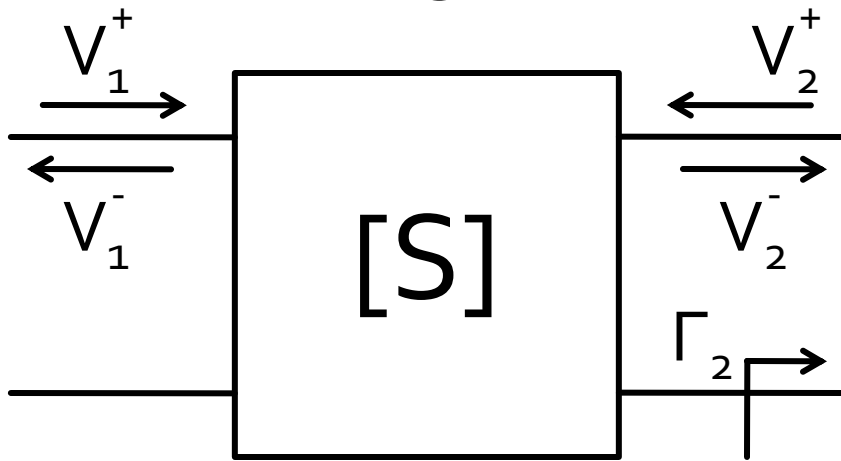

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0}$$

- $V_2^+ = 0$  meaning: port 2 is terminated in matched load to avoid reflections towards the port

$$\Gamma_2 = 0 \rightarrow V_2^+ = 0$$

# Power waves for N ports

$$[b] = [F] \cdot ([Z] - [Z_R]^*) \cdot ([Z] + [Z_R])^{-1} \cdot [F]^{-1} \cdot [a]$$

- The scattering matrix for power waves,  $[S_p]$

$$[b] = [S_p] \cdot [a]$$

$$[S_p] = [F] \cdot ([Z] - [Z_R]^*) \cdot ([Z] + [Z_R])^{-1} \cdot [F]^{-1}$$

- But:  $[S] = ([Z] - [Z_0]) \cdot ([Z] + [Z_0])^{-1}$

- Typically


$$Z_{0i} = Z_{Ri} = R_0, \forall i$$

$$R_0 = 50\Omega$$

$$[S_p] \equiv [S]$$

- they coincide!!!

# Scattering matrix – S

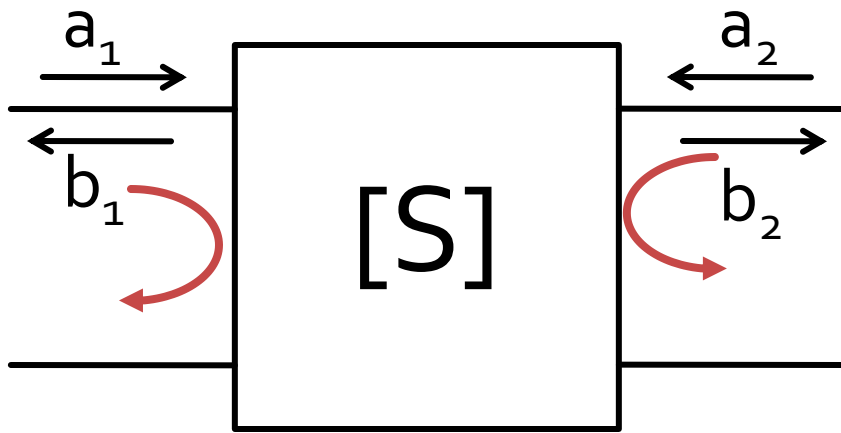


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

- $S_{11}$  and  $S_{22}$  are **reflection coefficients** at ports 1 and 2 when the other port is **matched**

# Scattering matrix – S

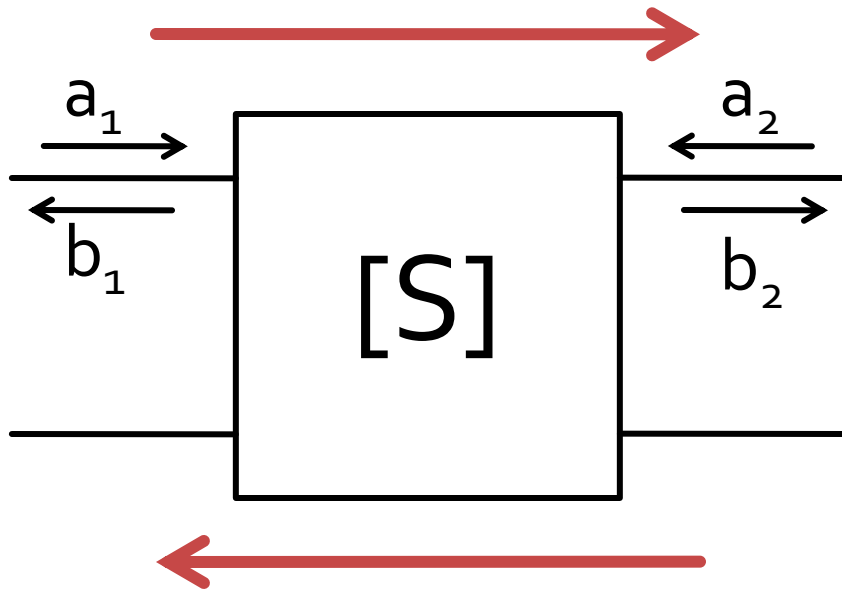


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$$

- $S_{21}$  si  $S_{12}$  are signal amplitude **gain** when the other port is **matched**

# Scattering matrix – S

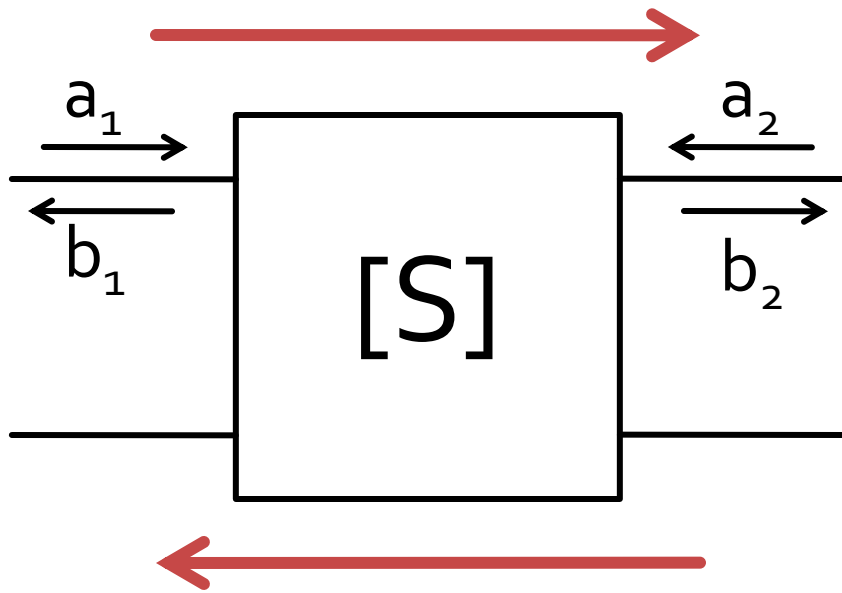

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$


$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- $a, b$ 
  - information about signal power **AND** signal phase
- $S_{ij}$ 
  - network effect (gain) over signal power **including** phase information


Impedance Matching

# The Smith Chart


# Course Topics

- Transmission lines
  - Impedance matching and tuning
  - Directional couplers
  - Power dividers
  - Microwave amplifier design
  - Microwave filters
  - ~~Oscillators and mixers?~~
- 


# The Smith Chart

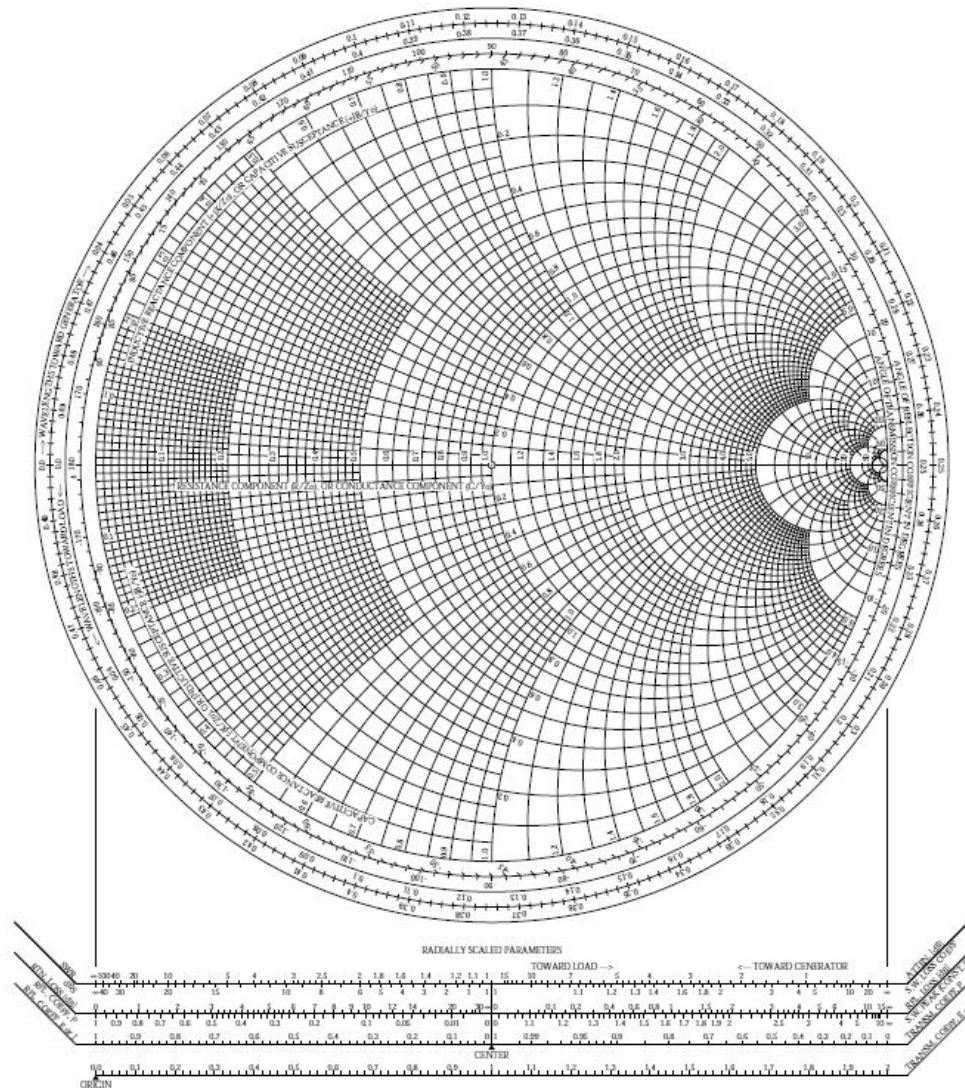

# The Smith Chart

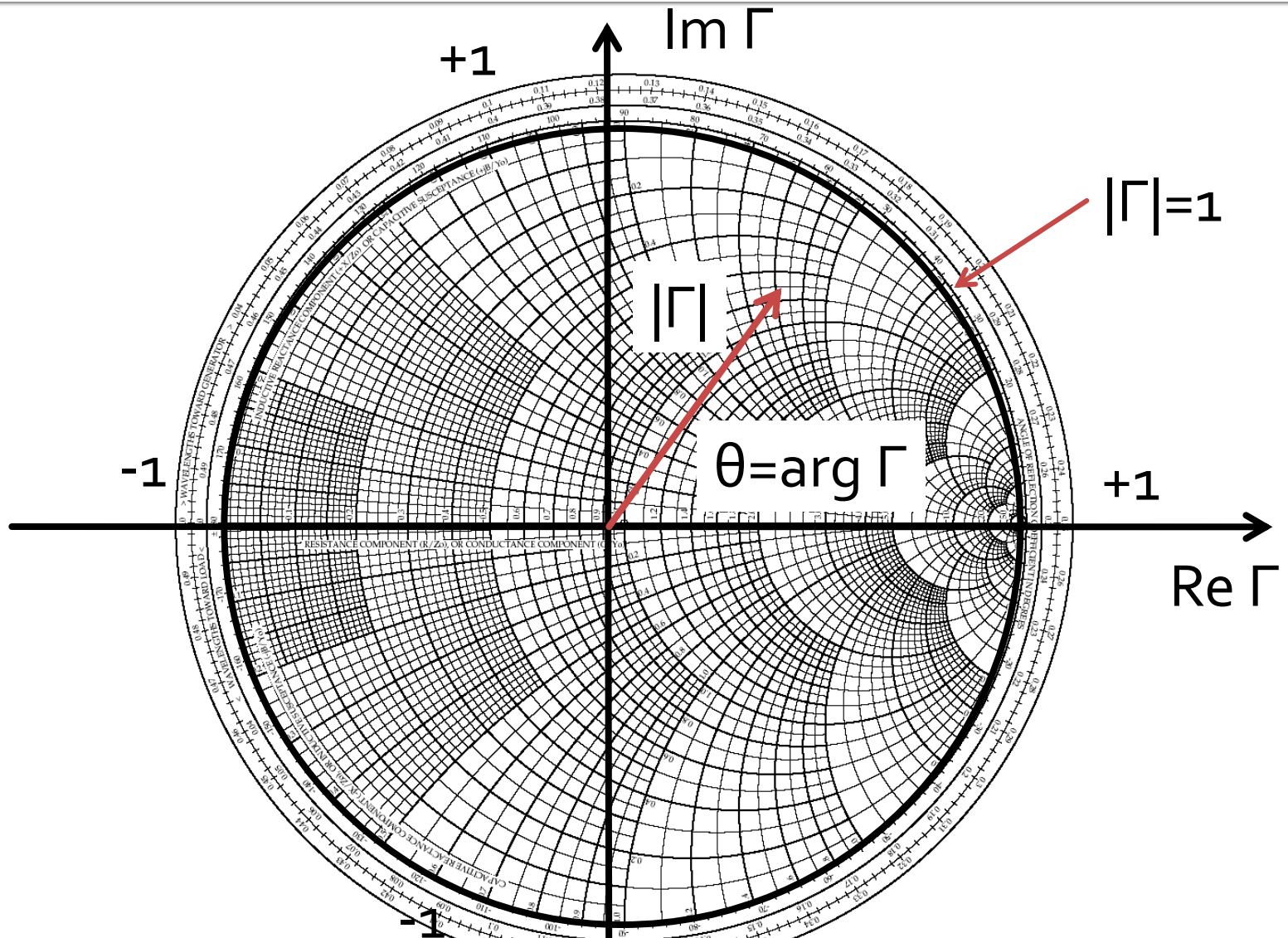

# The Smith Chart

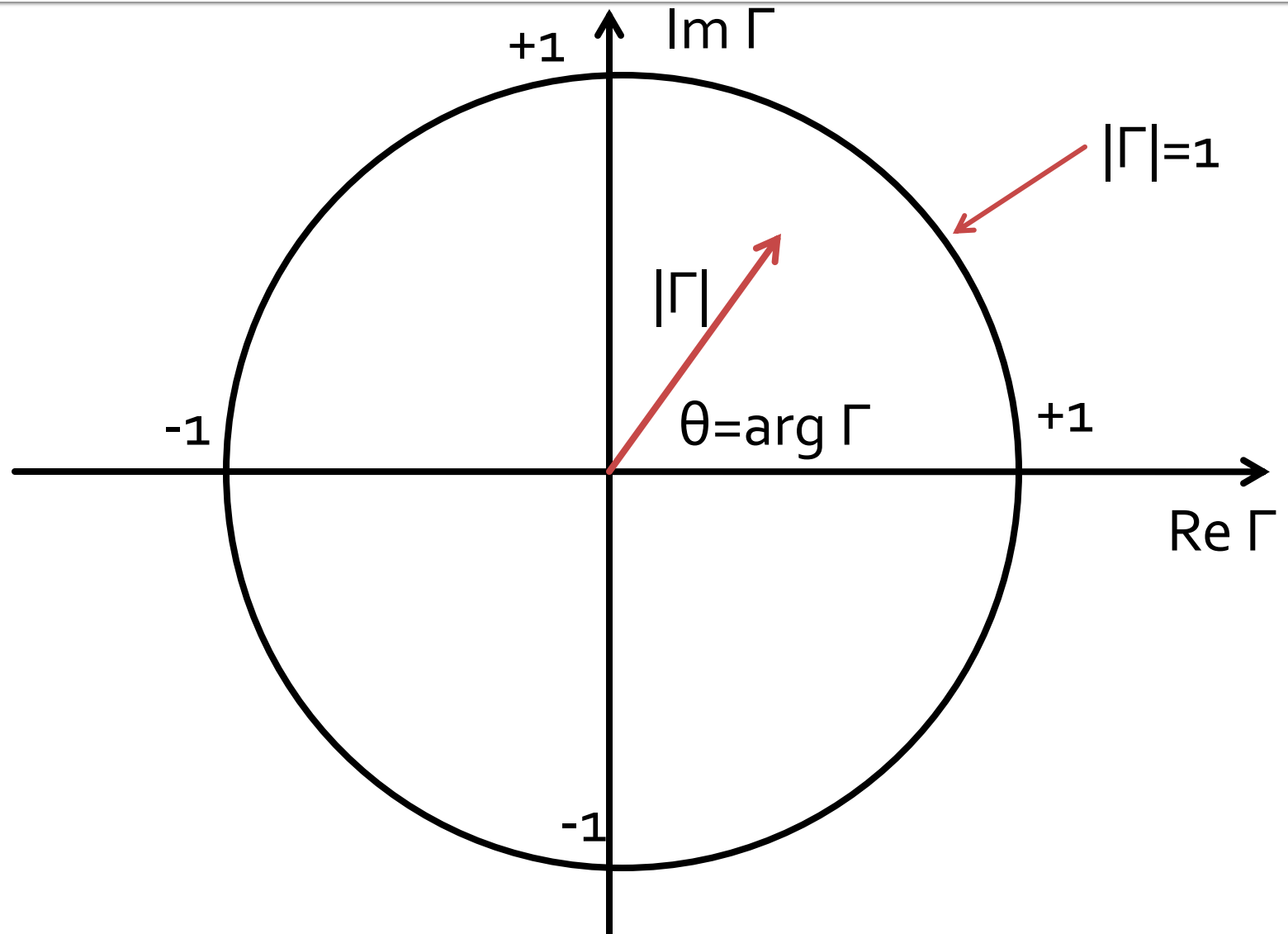




# The Smith Chart

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$


$$z_L = r_L + j \cdot x_L$$

$$r_L = ct.$$


$$x_L = ct.$$

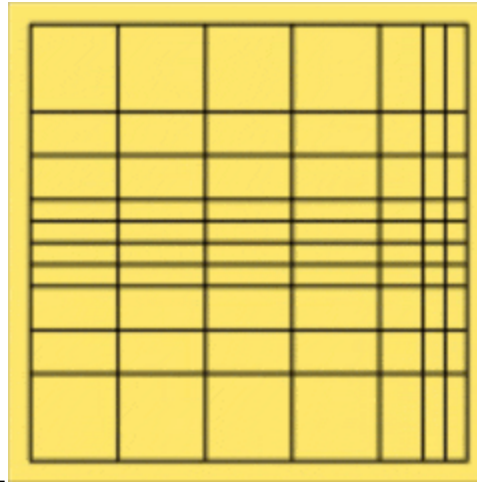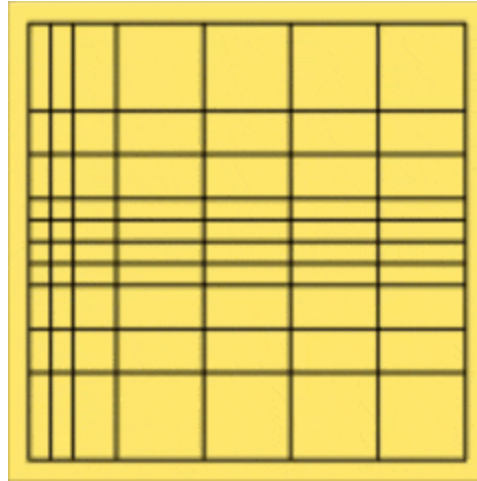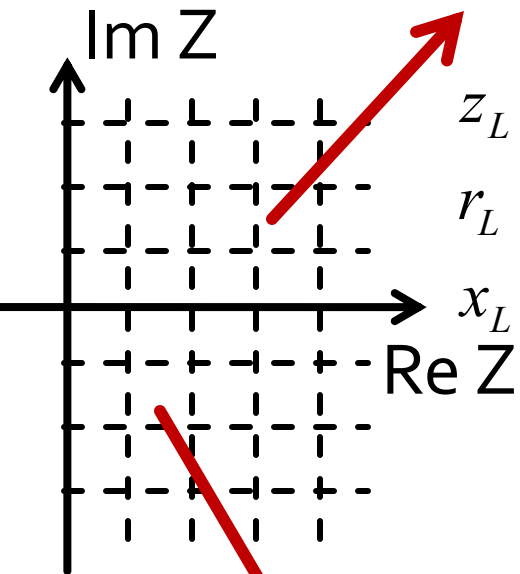

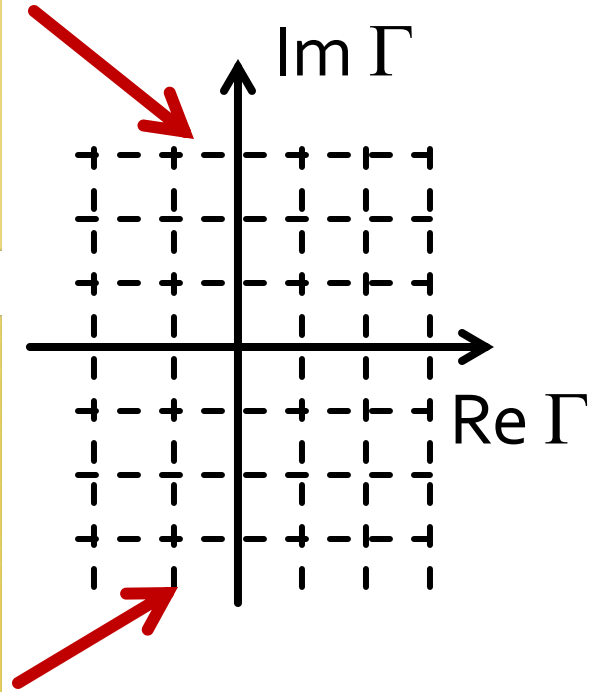
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Y_0 - Y_L}{Y_0 + Y_L} = \frac{1 - y_L}{1 + y_L}$$




# The Smith Chart, resistance

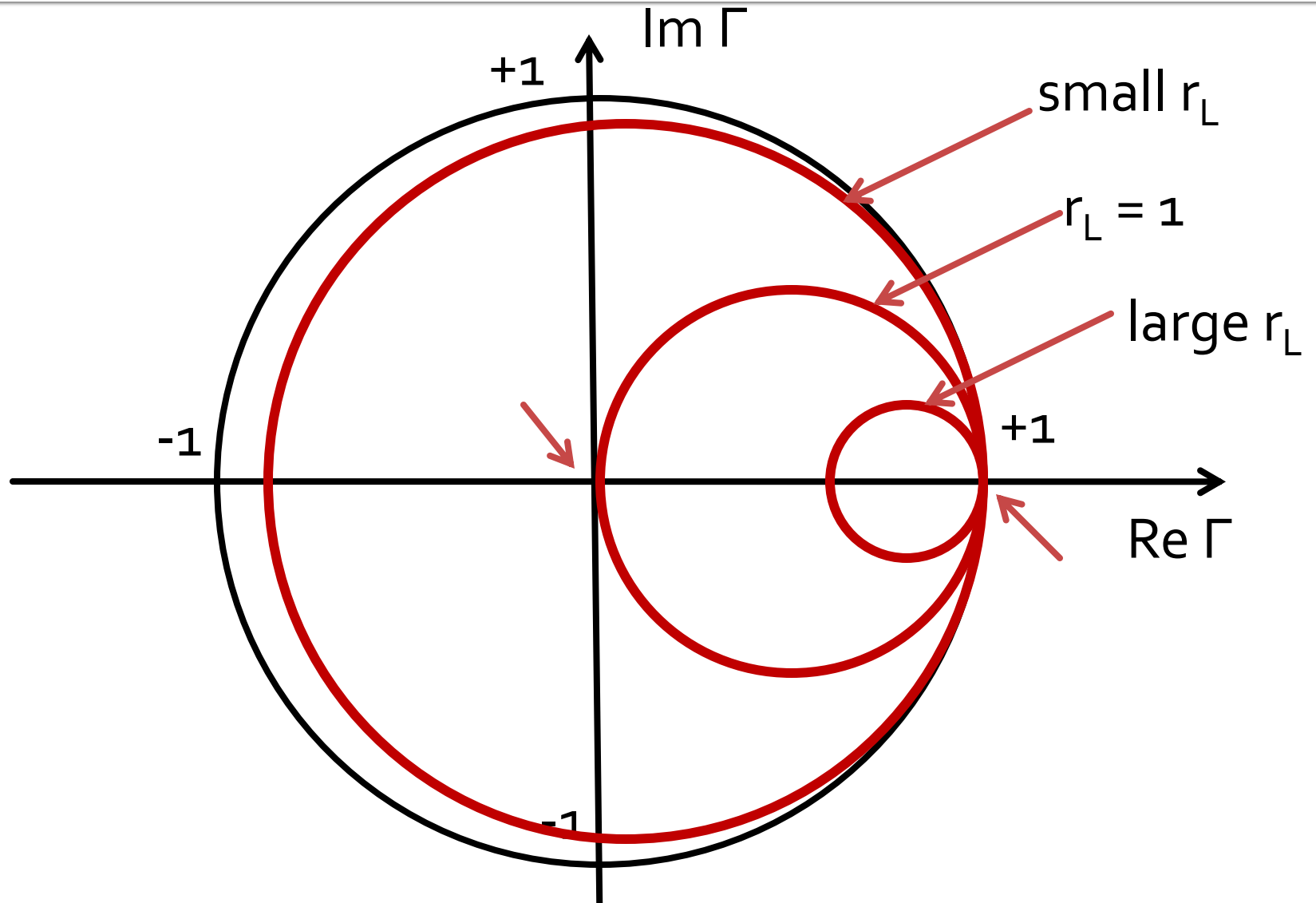


# The Smith Chart, reactance

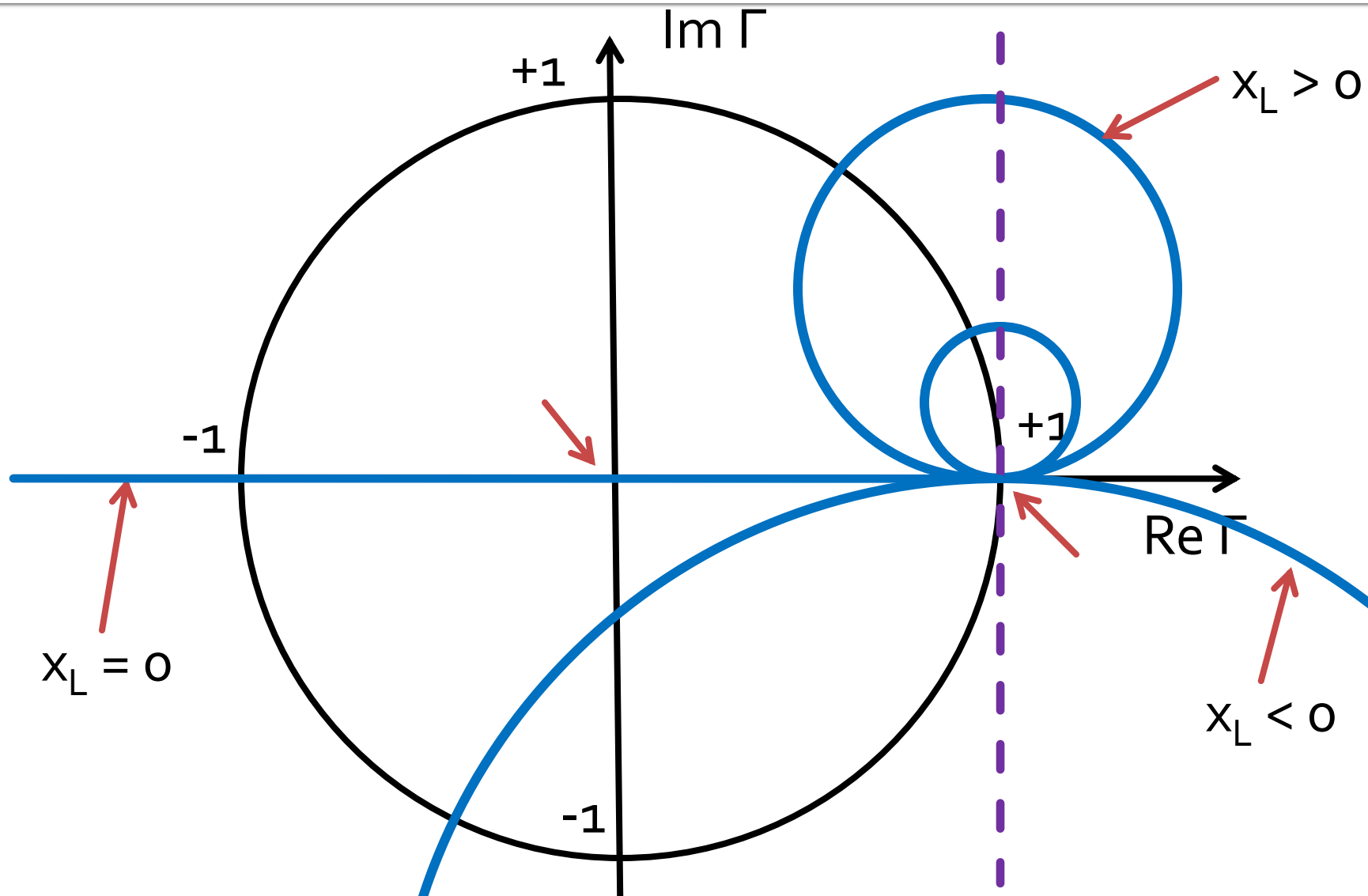

# The Smith Chart, impedance

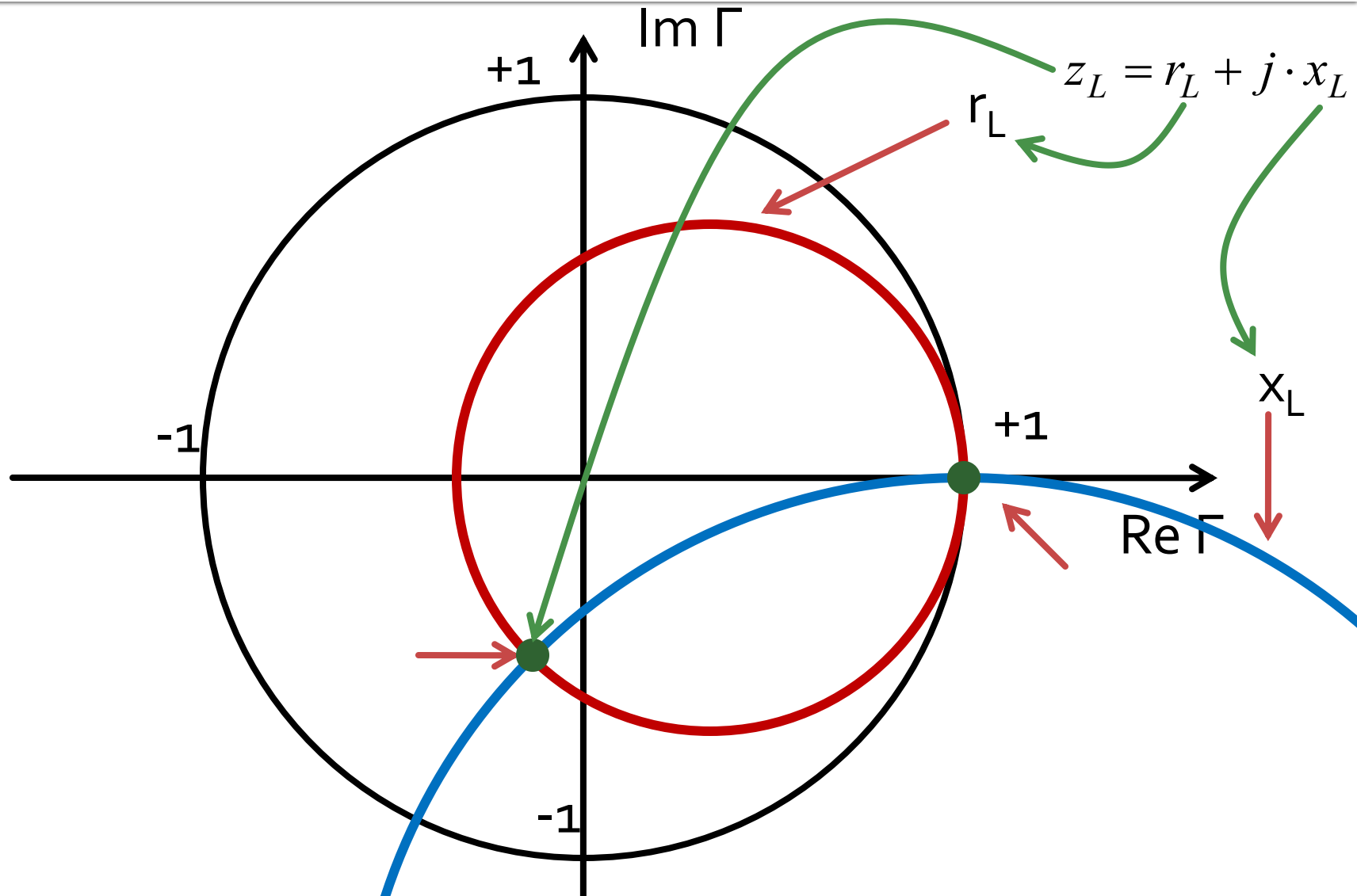

# The Admittance Smith Chart

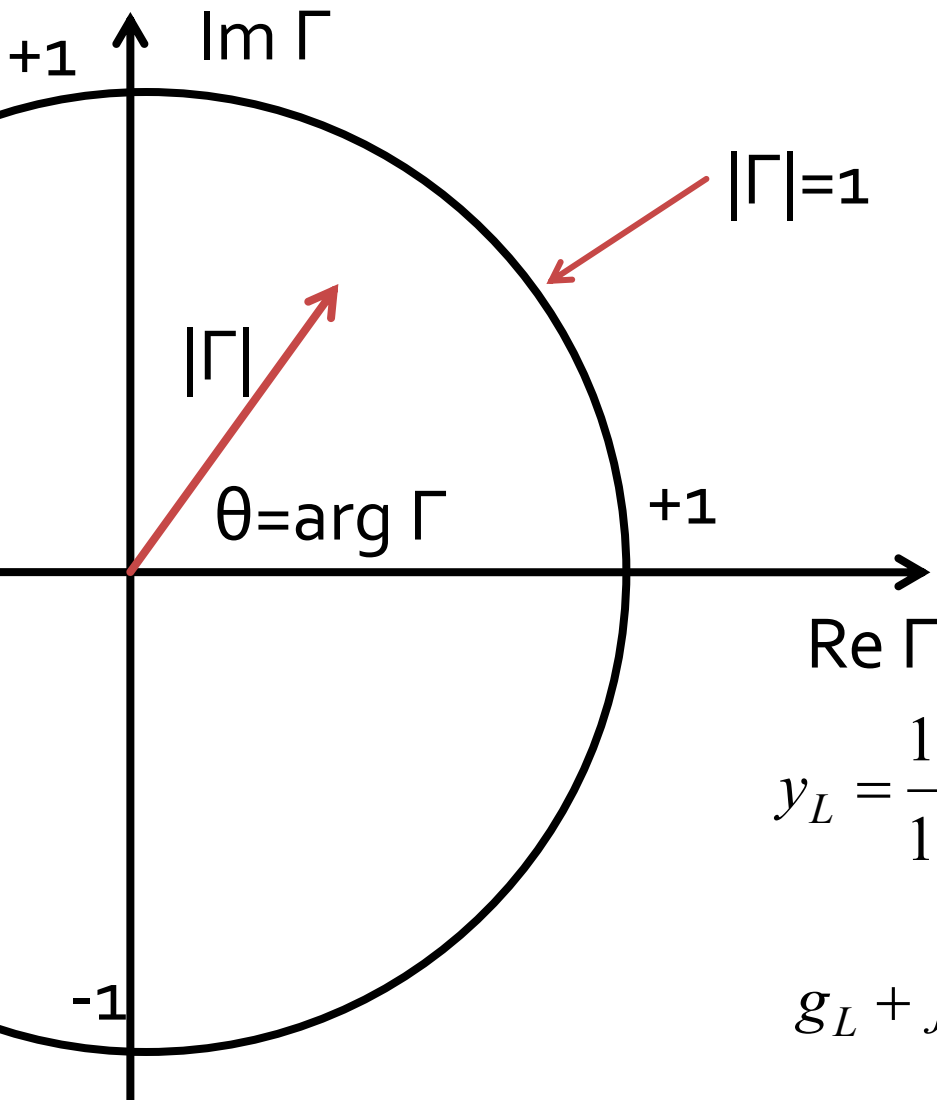

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1} = |\Gamma| \cdot e^{j\theta}$$


$$\Gamma = \Gamma_r + j \cdot \Gamma_i$$

$$z_L = \frac{1 + |\Gamma| \cdot e^{j\theta}}{1 - |\Gamma| \cdot e^{j\theta}} = r_L + j \cdot x_L$$


$$y_L = \frac{1 - |\Gamma| \cdot e^{j\theta}}{1 + |\Gamma| \cdot e^{j\theta}} = \frac{1}{r_L + j \cdot x_L} = g_L + j \cdot b_L$$

$$g_L + j \cdot b_L = \frac{(1 - \Gamma_r) - j \cdot \Gamma_i}{(1 + \Gamma_r) + j \cdot \Gamma_i}$$

# The Smith Chart, conductance

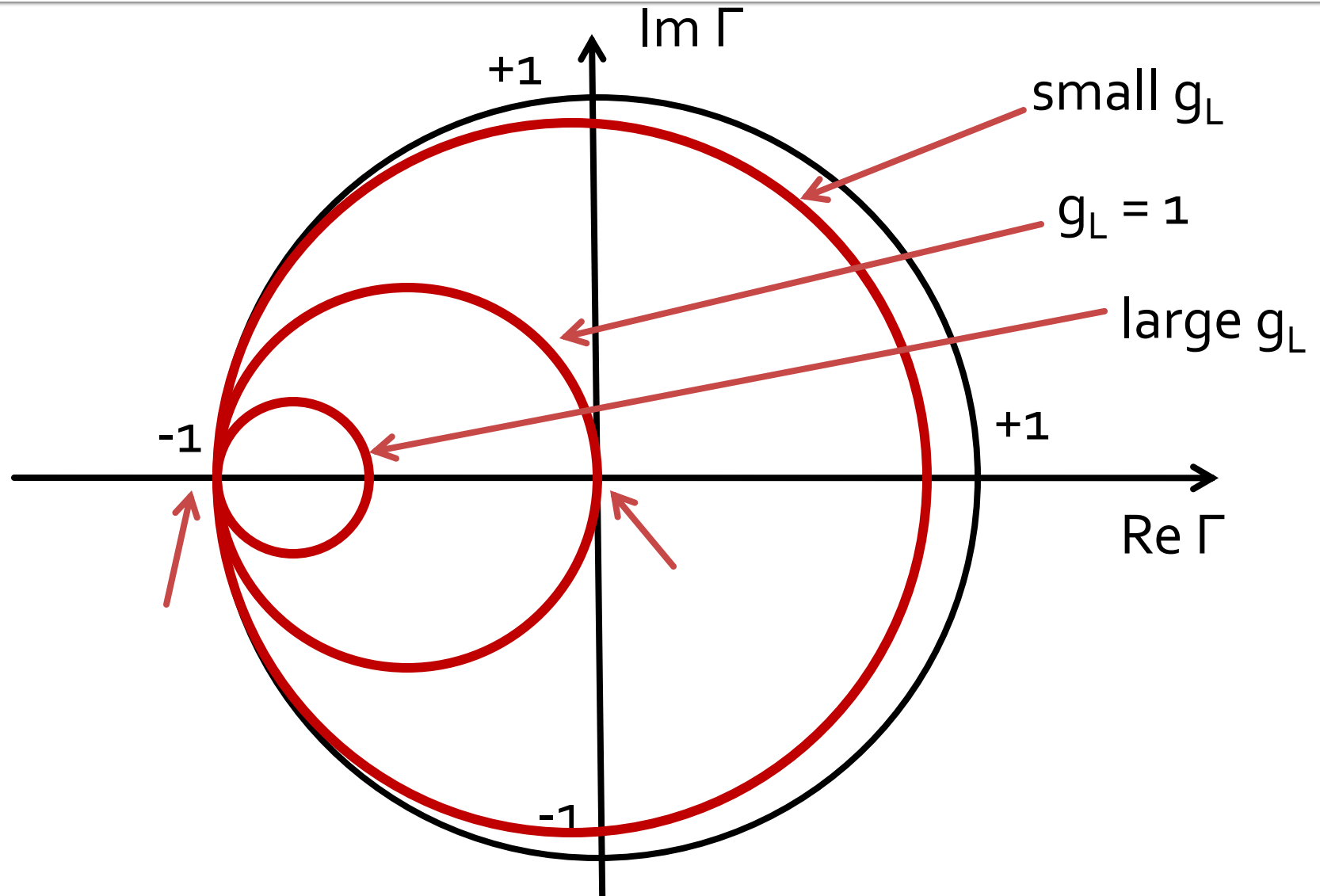

# The Smith Chart, susceptance

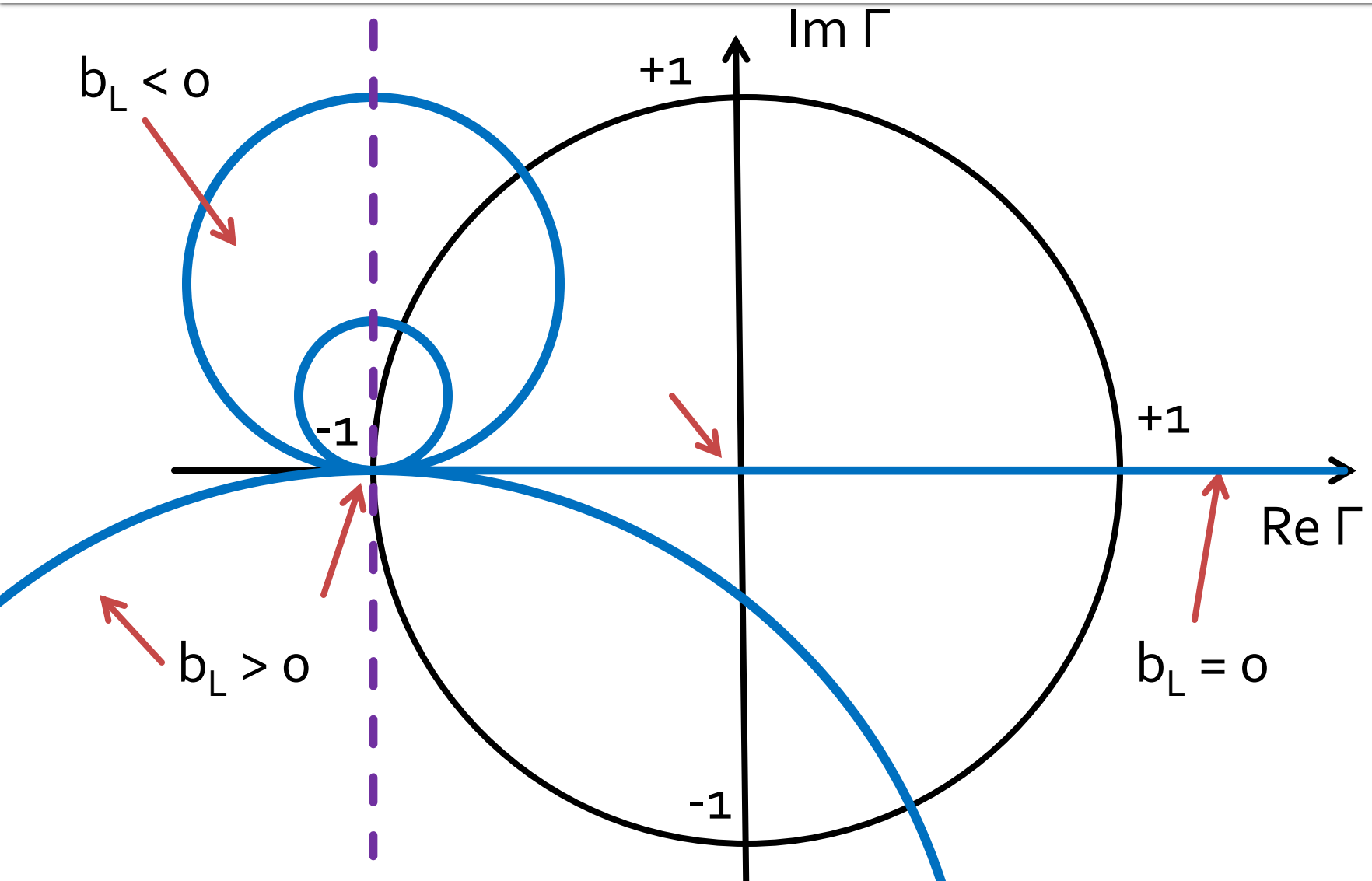



Impedance matching

# **Impedance Matching with lumped elements (L Networks)**

# Course Topics

- Transmission lines
- **Impedance matching and tuning**
- Directional couplers
- Power dividers
- Microwave amplifier design
- Microwave filters
- ~~Oscillators and mixers?~~
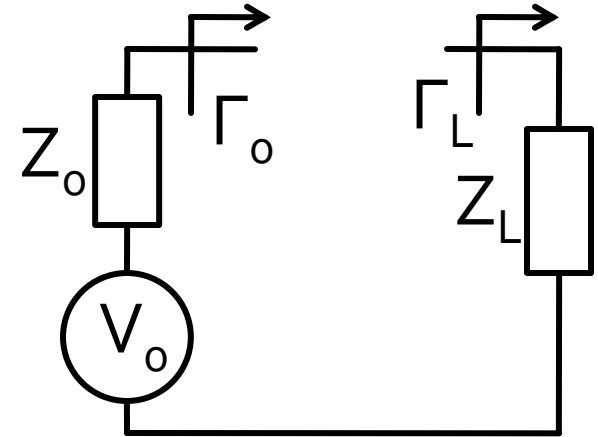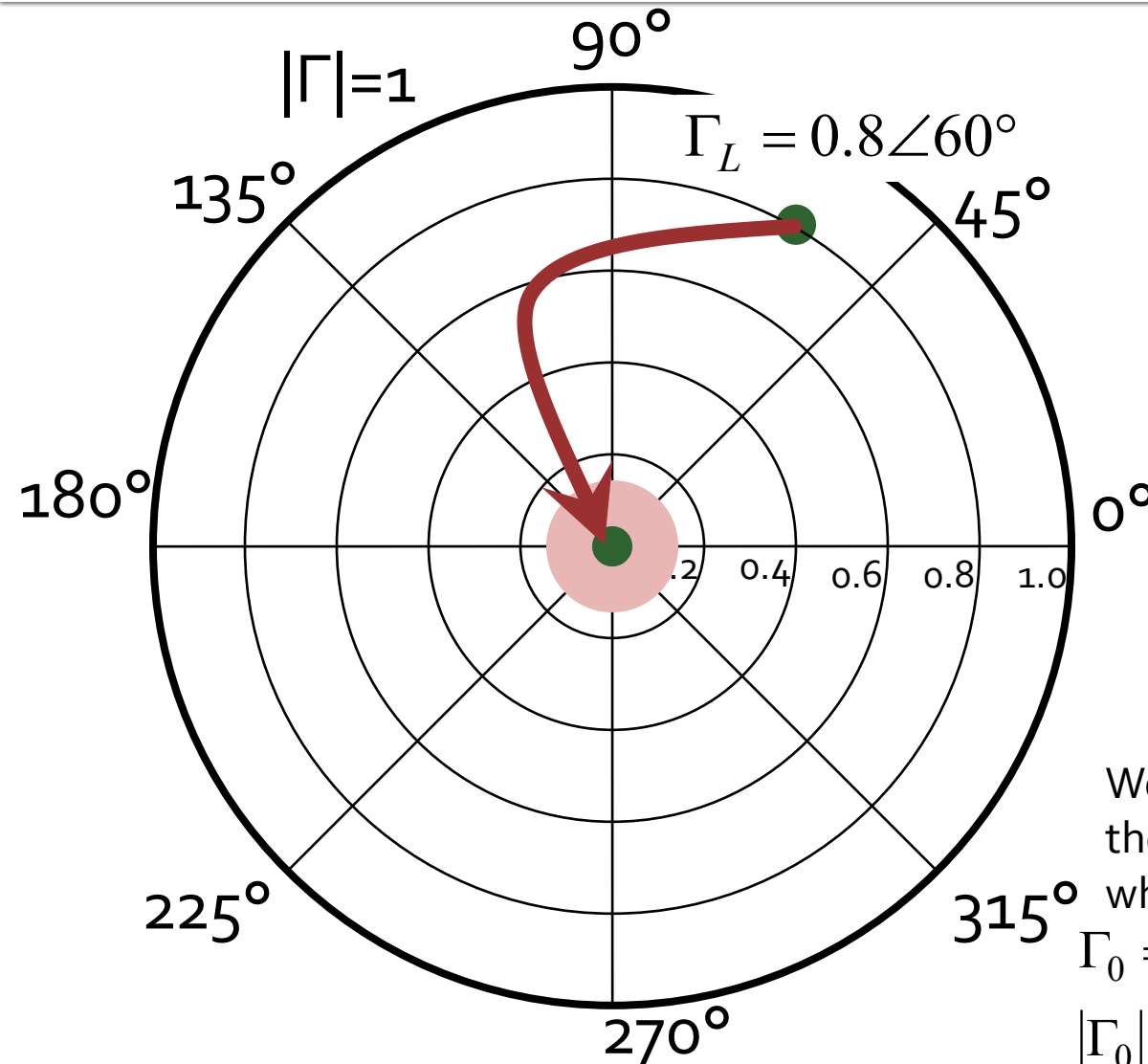
# The Smith Chart, reflection coefficient, impedance matching



Matching  $Z_L$  load to  $Z_o$  source.  
We normalize  $Z_L$  over  $Z_o$

$$Z_L = 21.429\Omega + j \cdot 82.479\Omega$$

$$z_L = 0.429 + j \cdot 1.65$$



$$\Gamma_L = 0.8 \angle 60^\circ$$

We must move the point denoting the reflection coefficient in the area where with a  $Z_o$  source we have:

$$\Gamma_0 = 0 \text{ perfect match } \bullet$$

$$|\Gamma_0| \leq \Gamma_m \text{ "good enough" match } \bullet$$

# The Smith Chart, series reactance

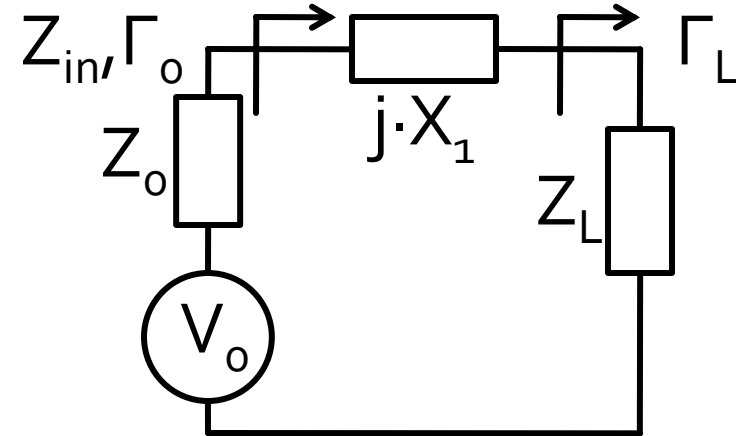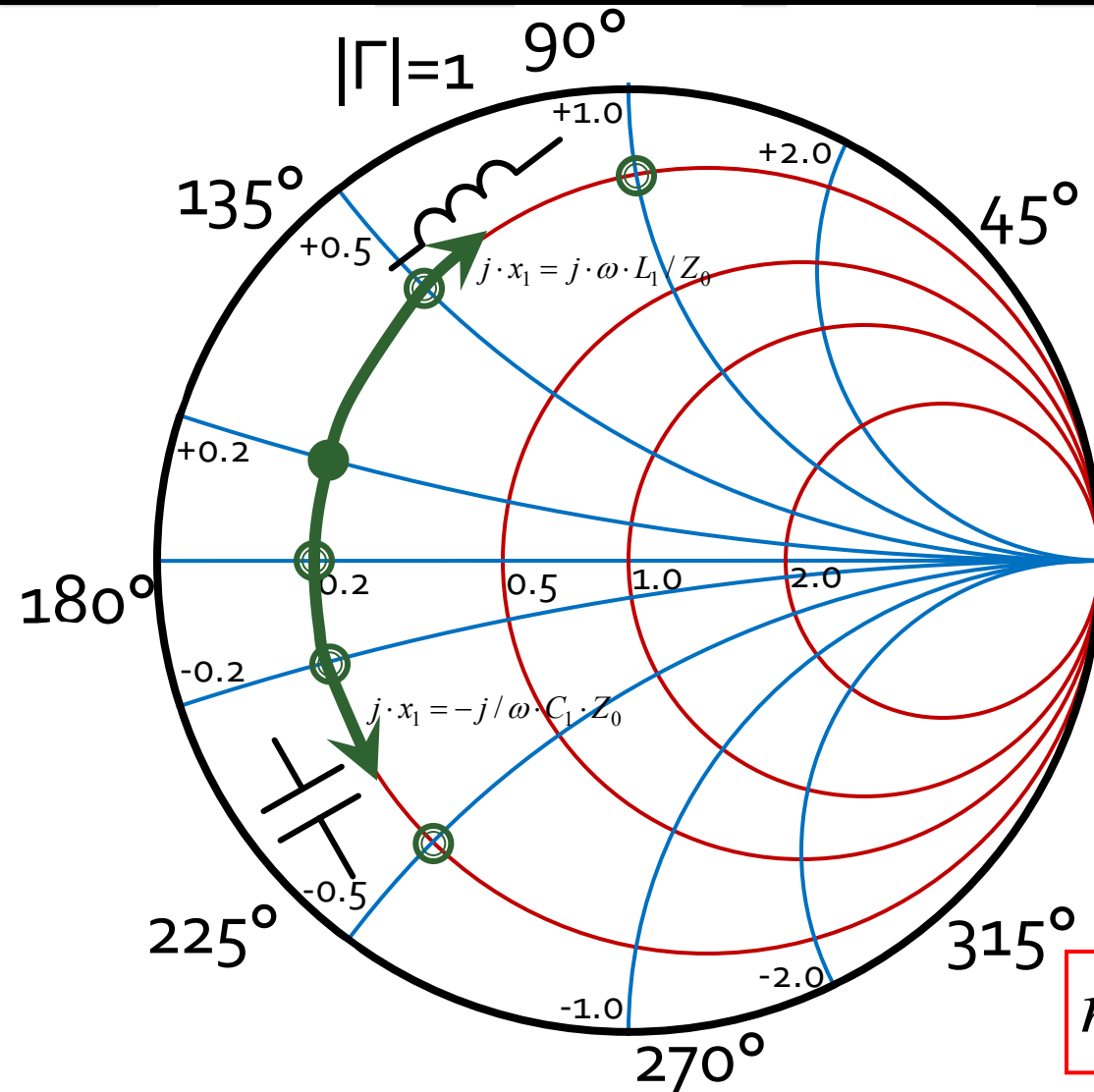

$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$



$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_L + j \cdot X_1 = R_L + j \cdot (X_L + X_1)$$

$$z_{in} = r_L + j \cdot (x_L + x_1)$$

$$r_{in} = r_L \quad \begin{matrix} j \cdot x_1 = j \cdot \omega \cdot L_1 / Z_0 > 0 \\ j \cdot x_1 = -j / \omega \cdot C_1 \cdot Z_0 < 0 \end{matrix}$$

# The Smith Chart, series resistance

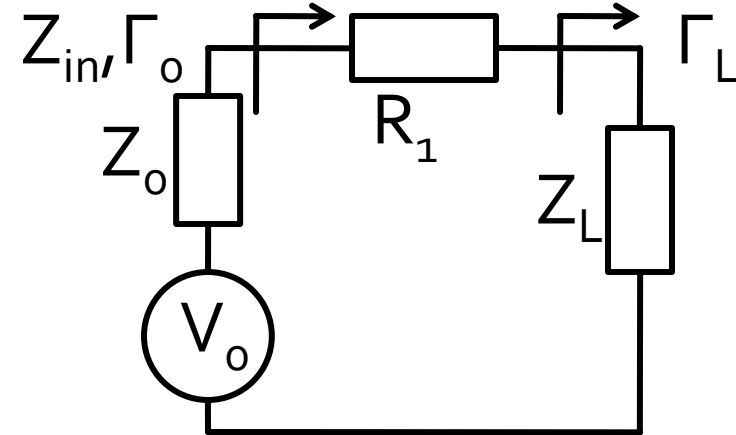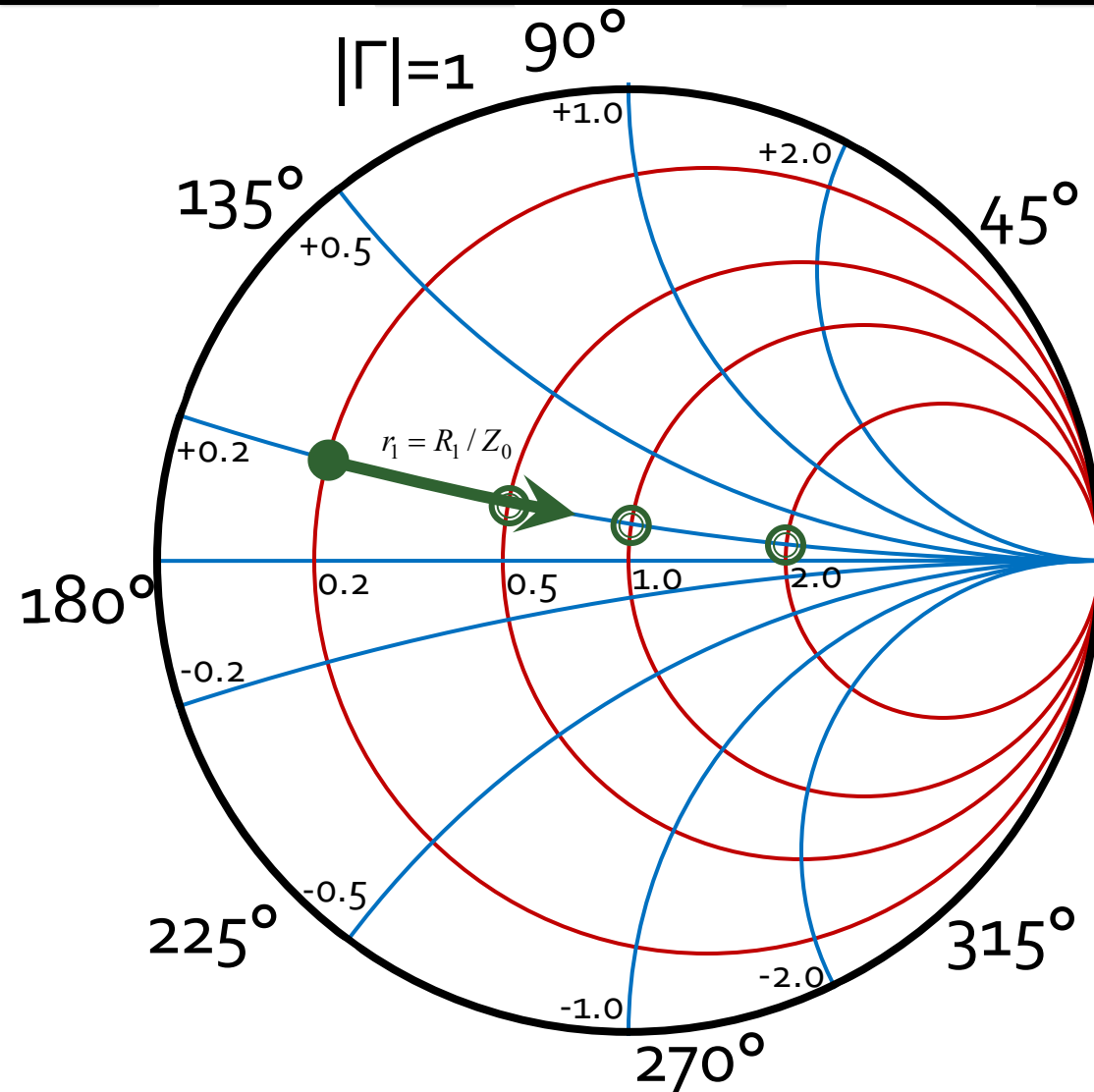

$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$



$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_L + R_1 = (R_L + R_1) + j \cdot X_L$$

$$z_{in} = z_L + r_1 = (r_L + r_1) + j \cdot x_L$$

$$x_{in} = x_L \quad r_{in} = r_L + R_1 / Z_0$$
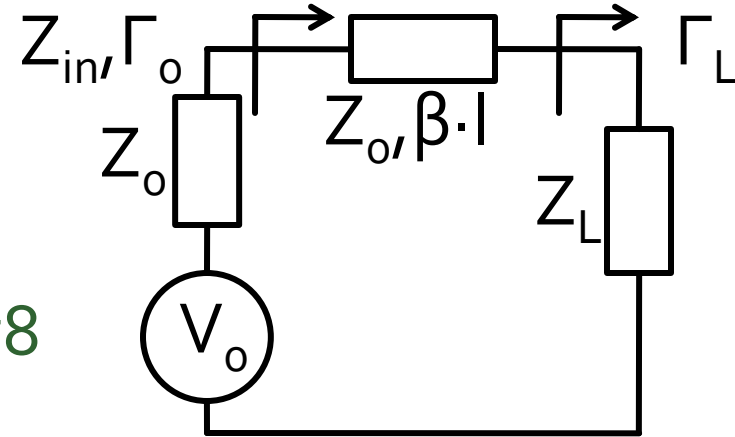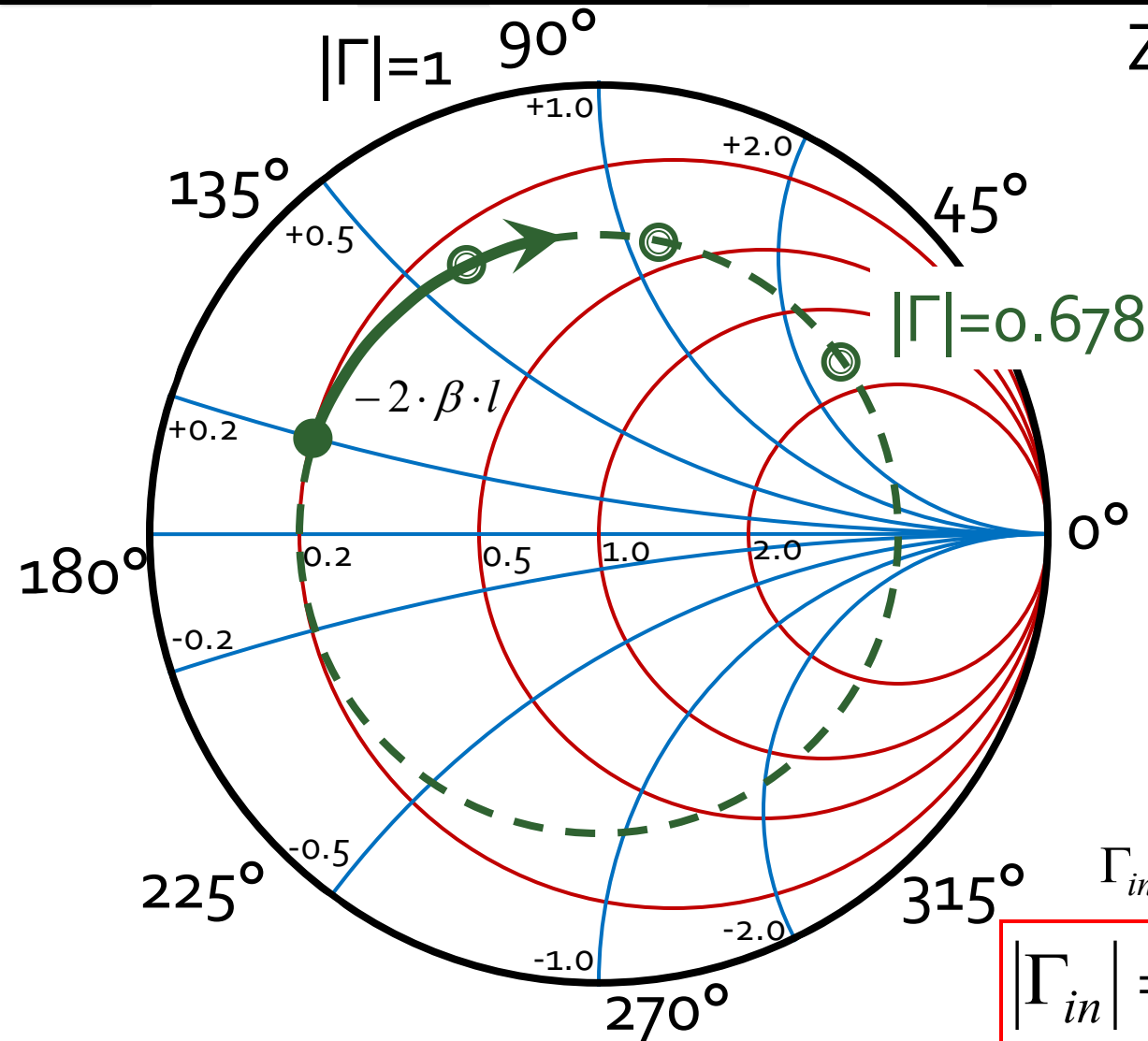
# The Smith Chart, series transmission line, $Z_0$



$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$



$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_0 \cdot \frac{1 + \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}}{1 - \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}}$$

$$\Gamma_{in} = \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}$$

$$|\Gamma_{in}| = |\Gamma_L| \quad \arg(\Gamma_{in}) = \arg(\Gamma_L) - 2 \cdot \beta \cdot l$$

# The Smith Chart, shunt susceptance

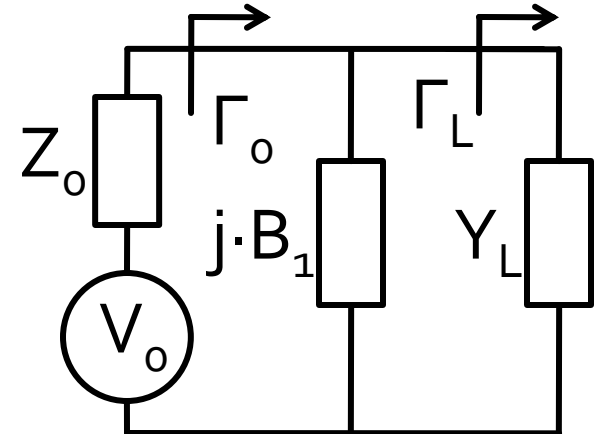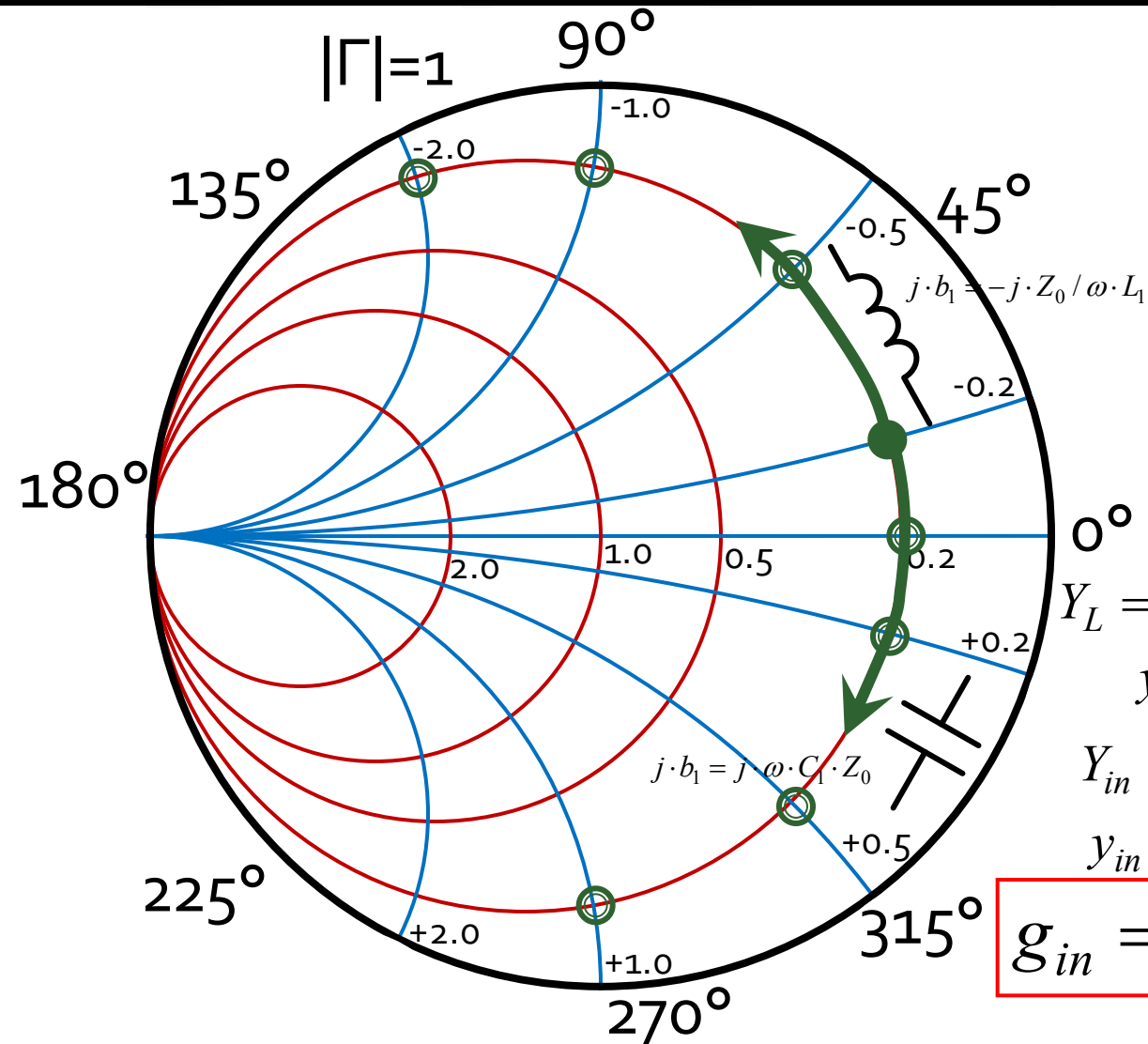

$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$\Gamma_L = 0.678 \angle 23.5^\circ$$

$$Y_L = G_L + j \cdot B_L = 0.004S + j \cdot 0.004$$

$$y_L = g_L + j \cdot b_L = 0.2 - j \cdot 0.2$$

$$Y_{in} = Y_L + j \cdot B_1 = G_L + j \cdot (B_L + B_1)$$



$$y_{in} = g_L + j \cdot (b_L + b_1)$$

$$g_{in} = g_L$$

$$j \cdot b_1 = j \cdot \omega \cdot C_1 \cdot Z_0 > 0$$

$$j \cdot b_1 = -j \cdot Z_0 / \omega \cdot L_1 < 0$$

# The Smith Chart, shunt conductance

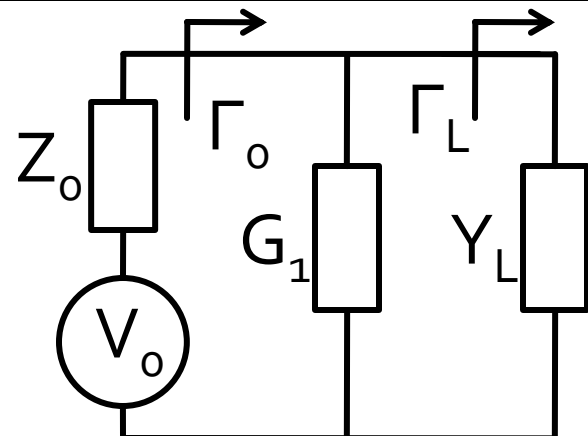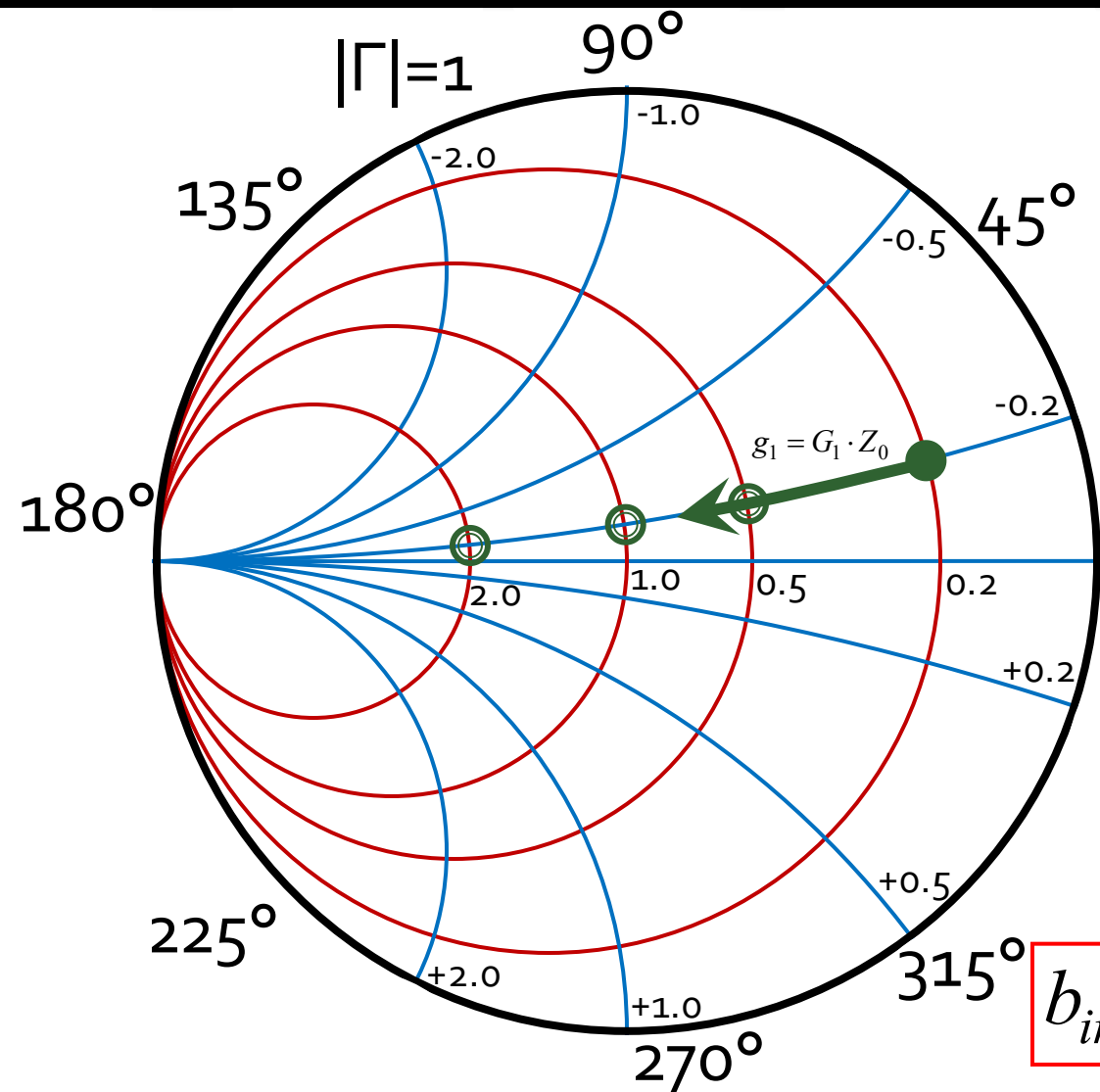

$$Z_0 = 50\Omega, Y_0 = 0.02S$$

$$\Gamma_L = 0.678 \angle 23.5^\circ$$

$$Y_L = G_L + j \cdot B_L = 0.004S + j \cdot 0.004$$

$$y_L = g_L + j \cdot b_L = 0.2 - j \cdot 0.2$$



$$Y_{in} = Y_L + G_1 = (G_L + G_1) + j \cdot B_L$$

$$y_{in} = (g_L + g_1) + j \cdot b_L$$

$$b_{in} = b_L$$

$$g_{in} = g_L + G_1 \cdot Z_0$$

# Impedance matching

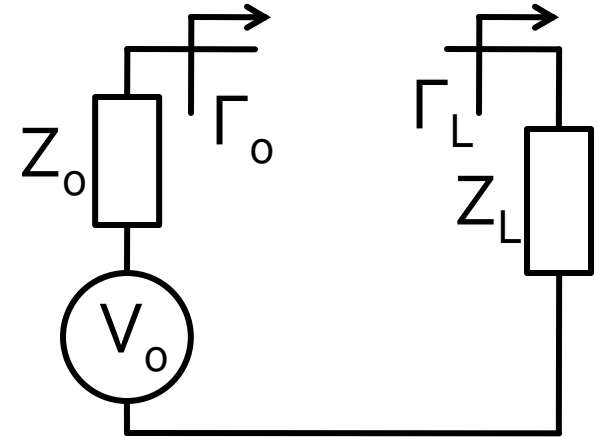
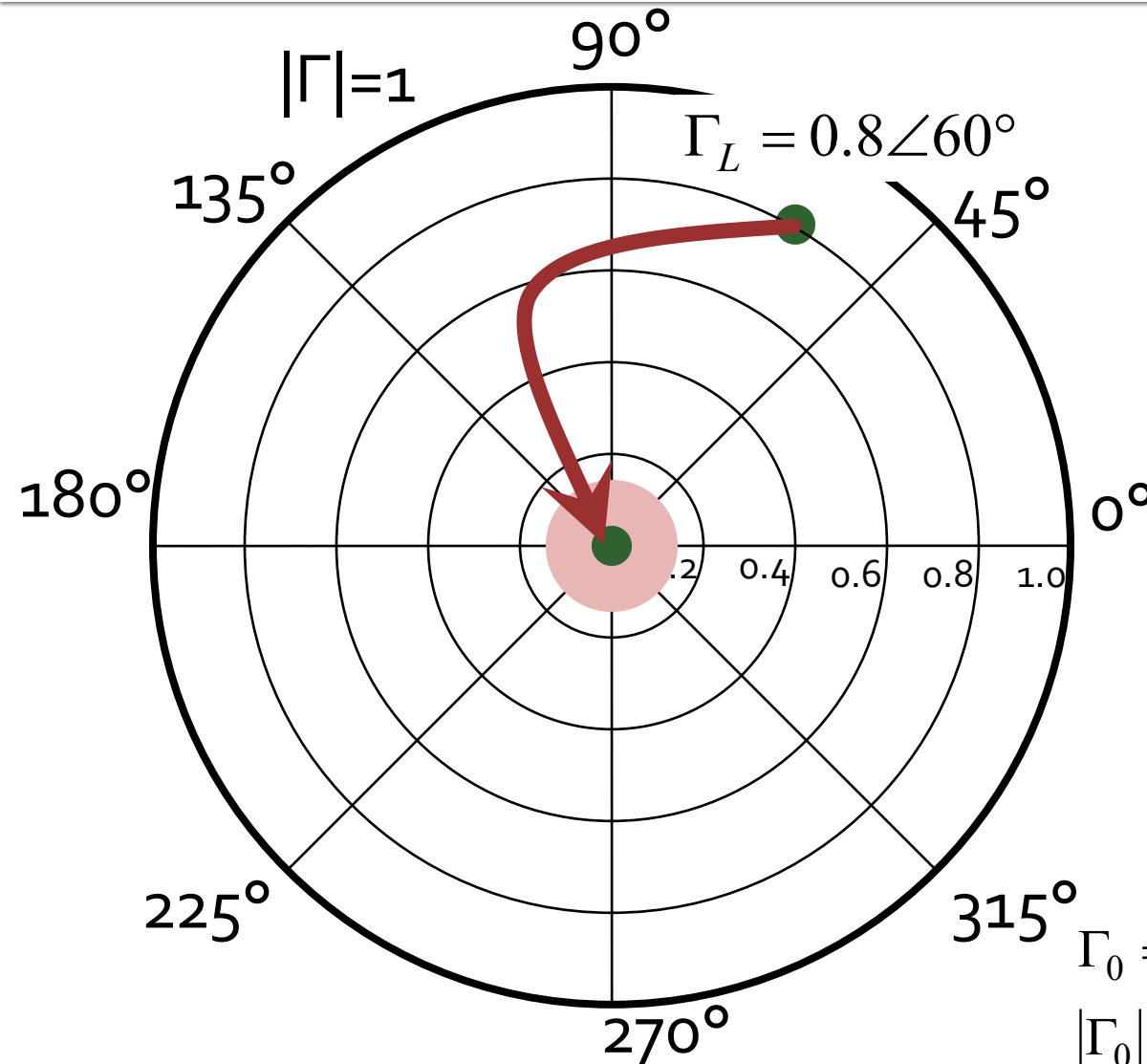


**How?**

$\Gamma_0 = 0$  perfect match ●

$|\Gamma_0| \leq \Gamma_m$  "good enough" match ●

# Matching, series reactance

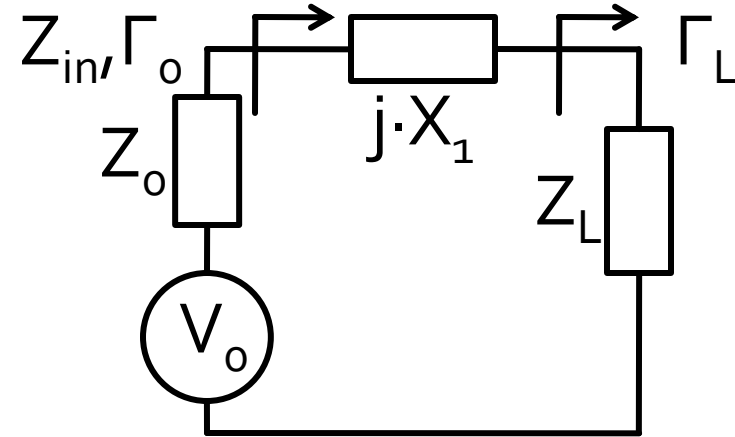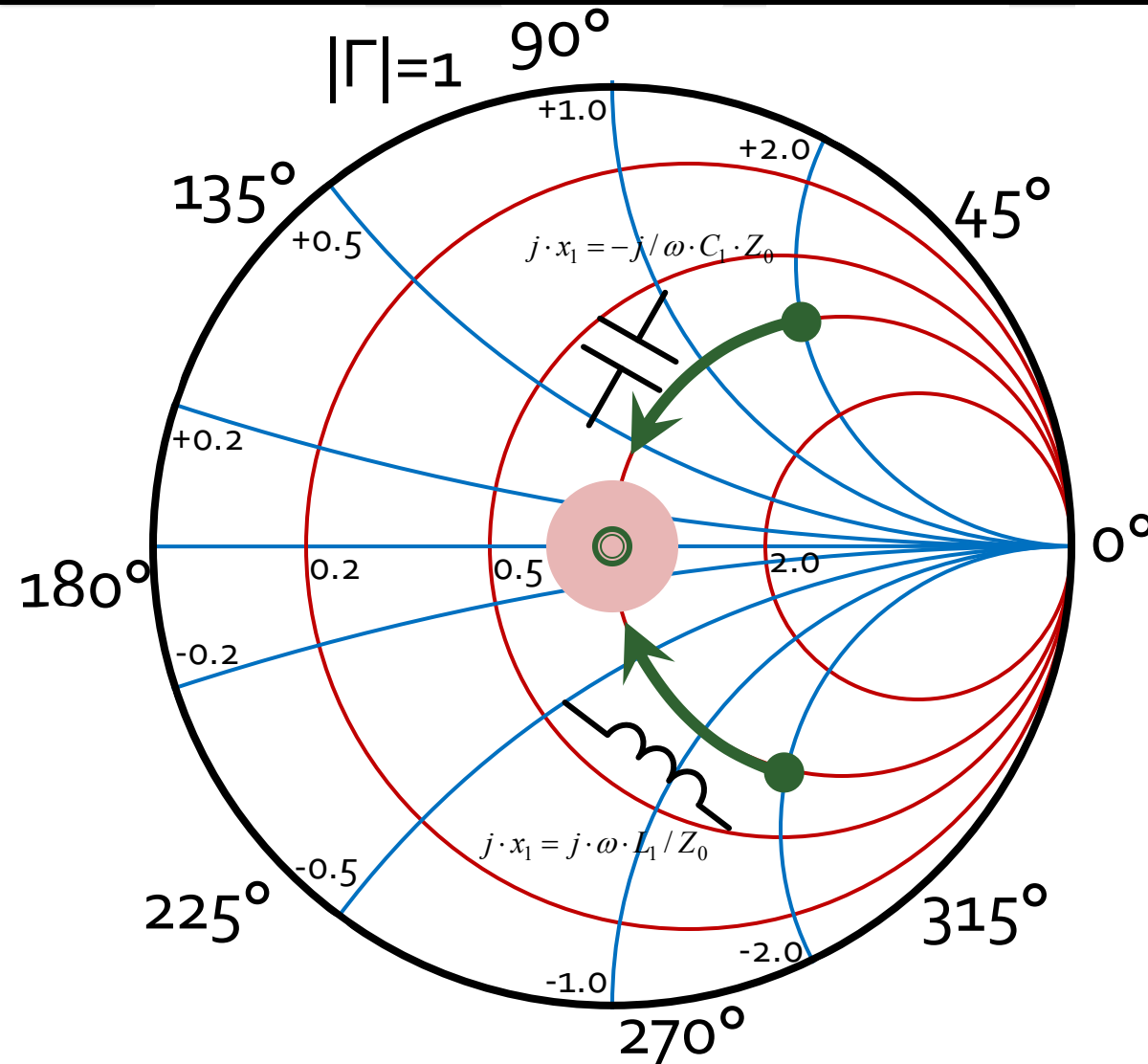

$$z_L = r_L + j \cdot x_L$$



$$z_{in} = r_L + j \cdot (x_L + x_1)$$

$$r_{in} = r_L$$

- Match can be obtained **if and only if**  $r_L = 1$
- we compensate the reactive part of the load

$$j \cdot x_1 = -j \cdot x_L$$

# Matching, shunt susceptance

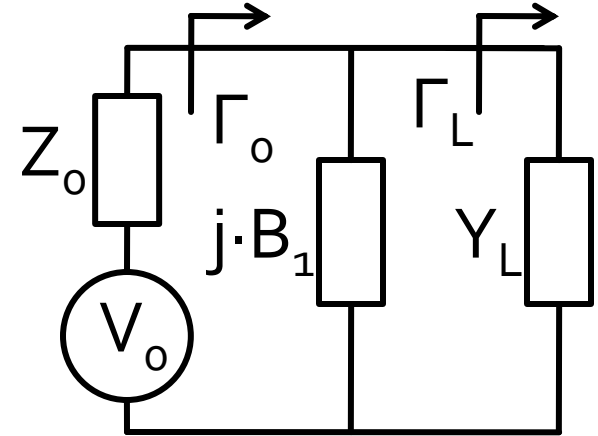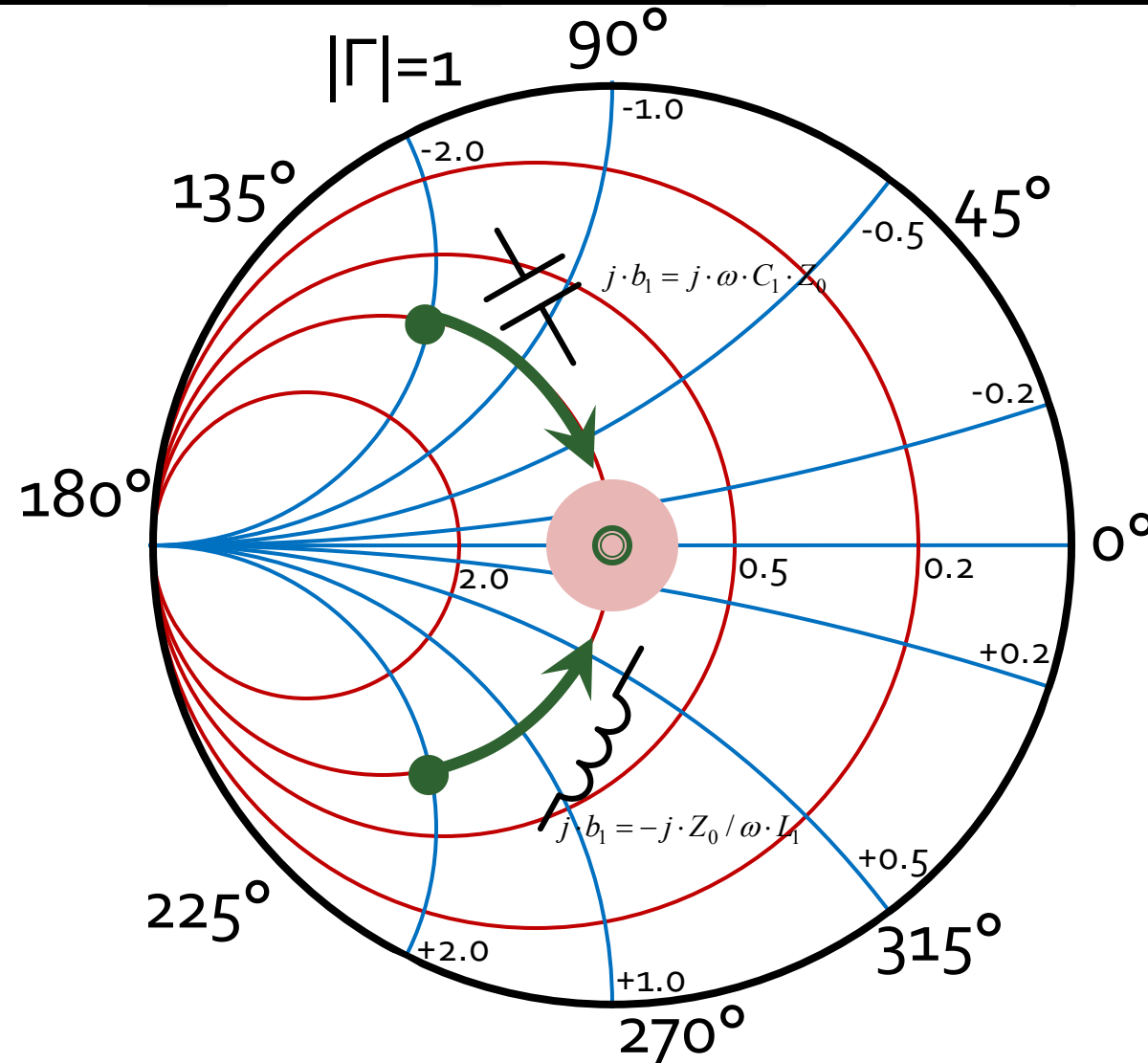


$$y_L = g_L + j \cdot b_L$$

$$y_{in} = g_L + j \cdot (b_L + b_1)$$



$$g_{in} = g_L$$

- Match can be obtained **if and only if**  $g_L = 1$
- we compensate the reactive part of the load
 
$$j \cdot b_1 = -j \cdot b_L$$

# Smith chart, $r=1$ and $g=1$


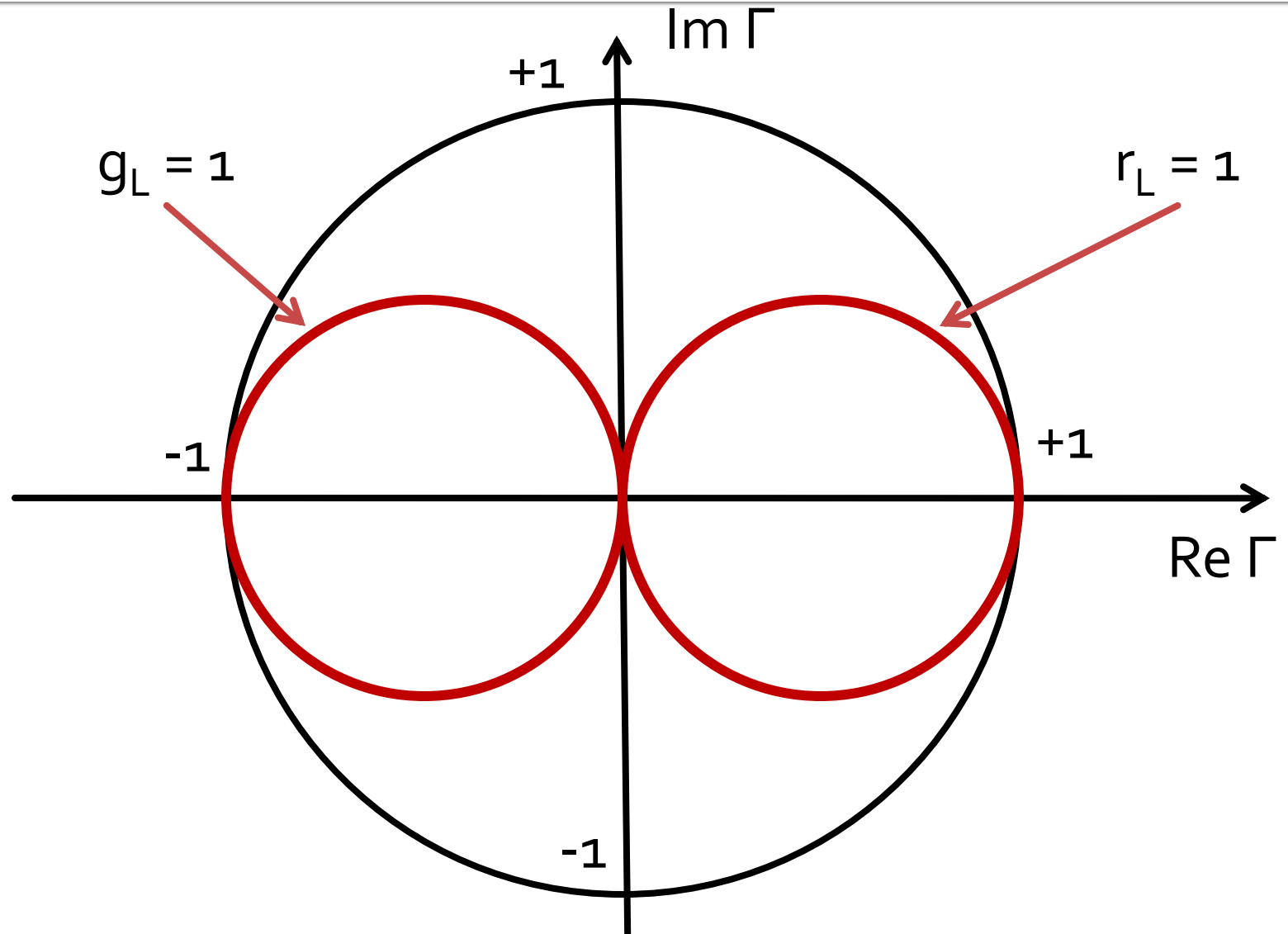

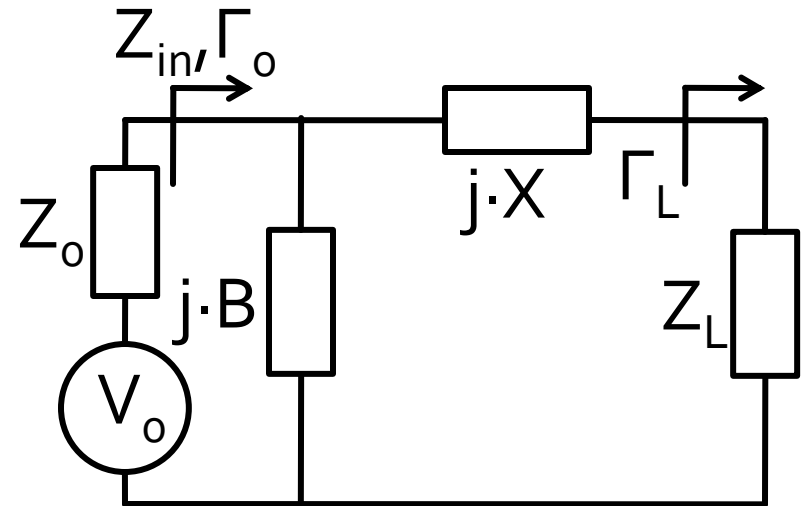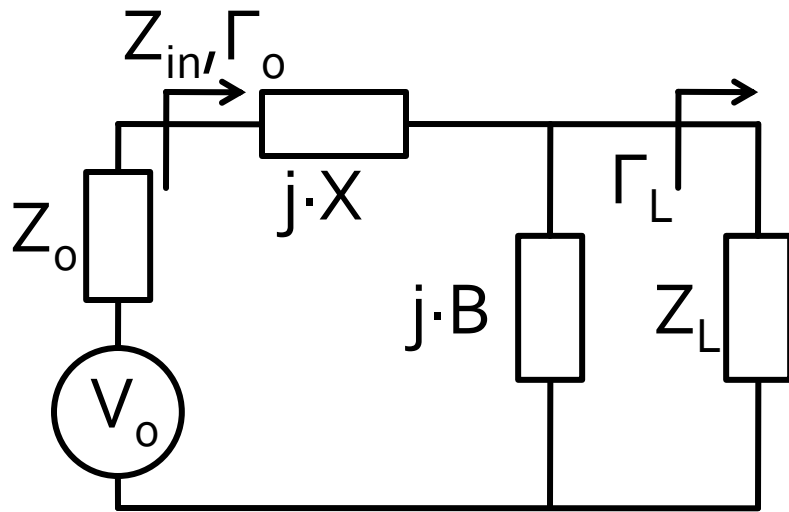
# Matching with 2 reactive elements (L Networks)





- Two steps matching
  - first reactive element moves the reflection coefficient **on the circle**  $r_L = 1/g_L = 1$
  - second element compensates the remaining reactance and achieves the impedance match



# series L, shunt C / shunt C, series L

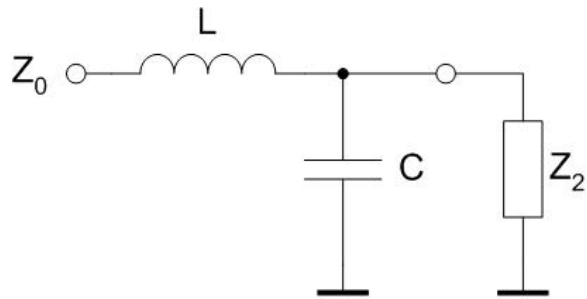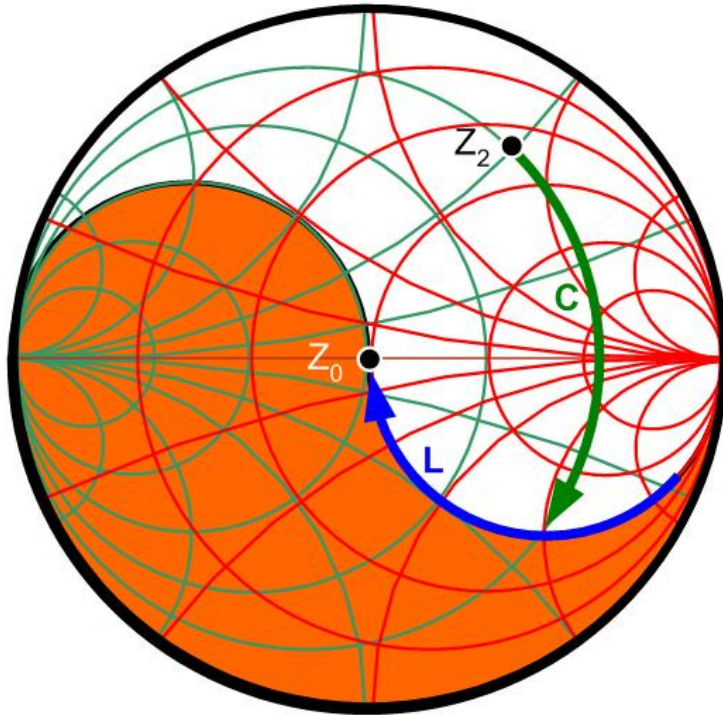

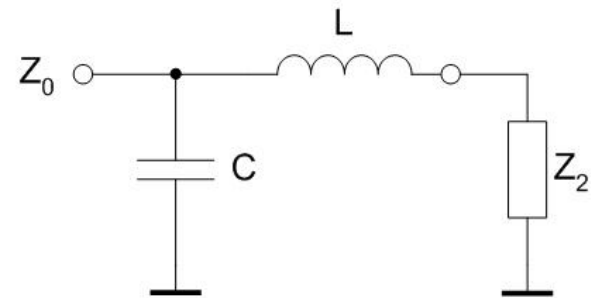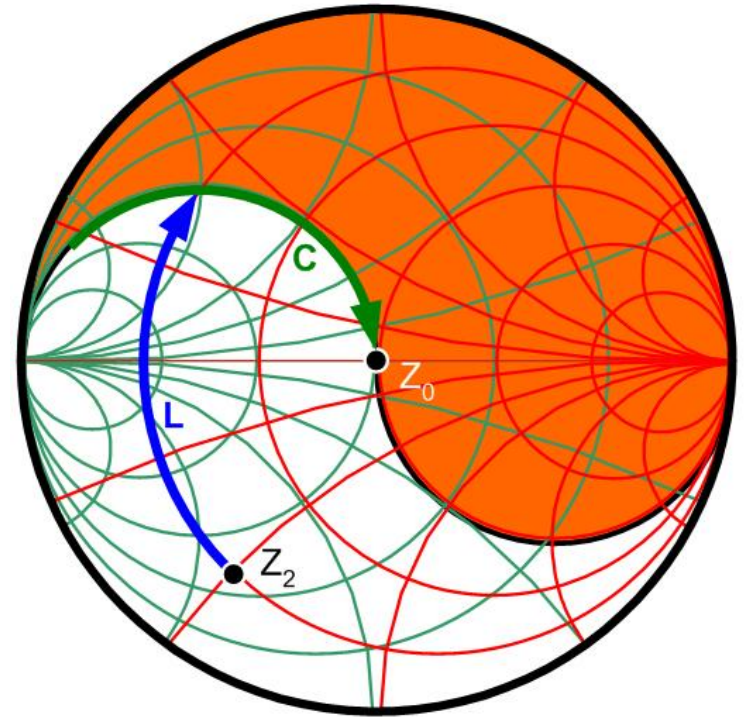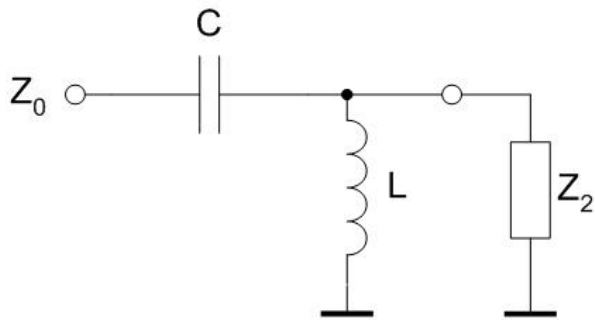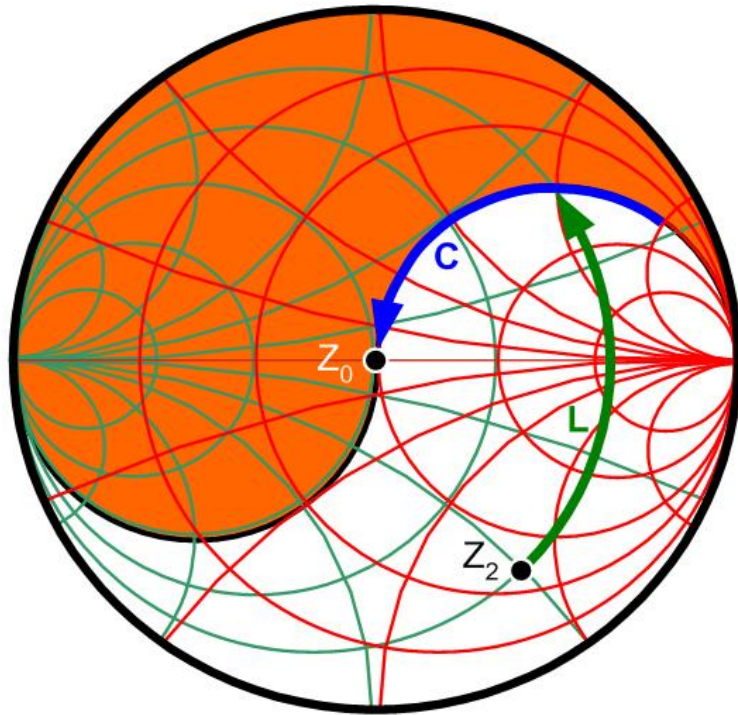
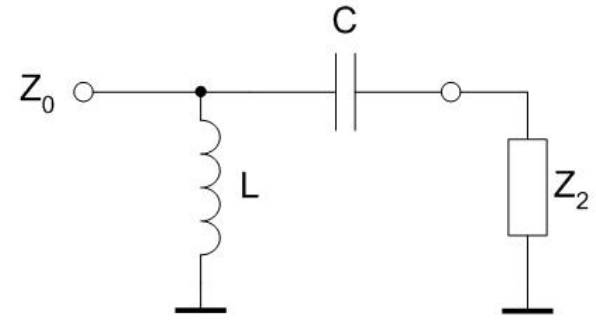
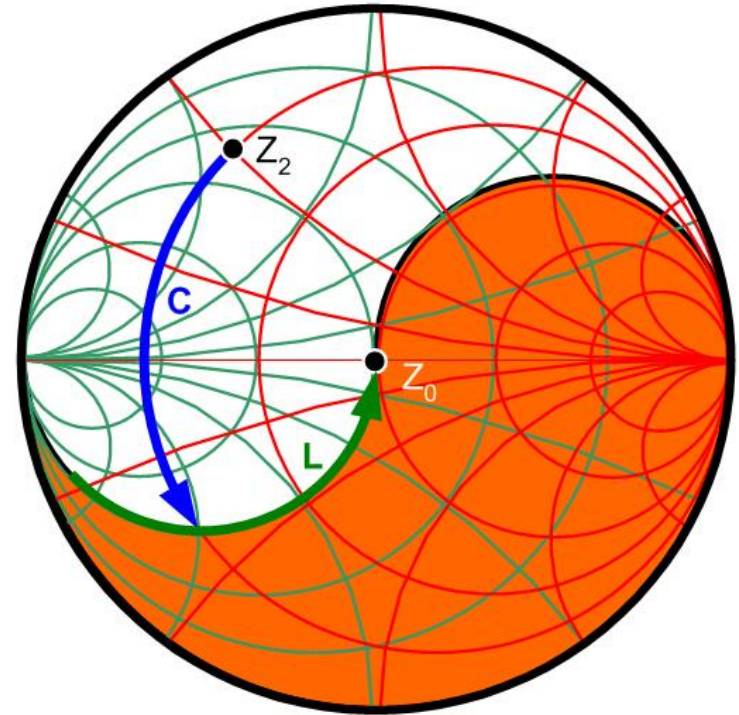
Forbidden area for current network




# series C, shunt L / shunt L, series C



 Forbidden area for current network



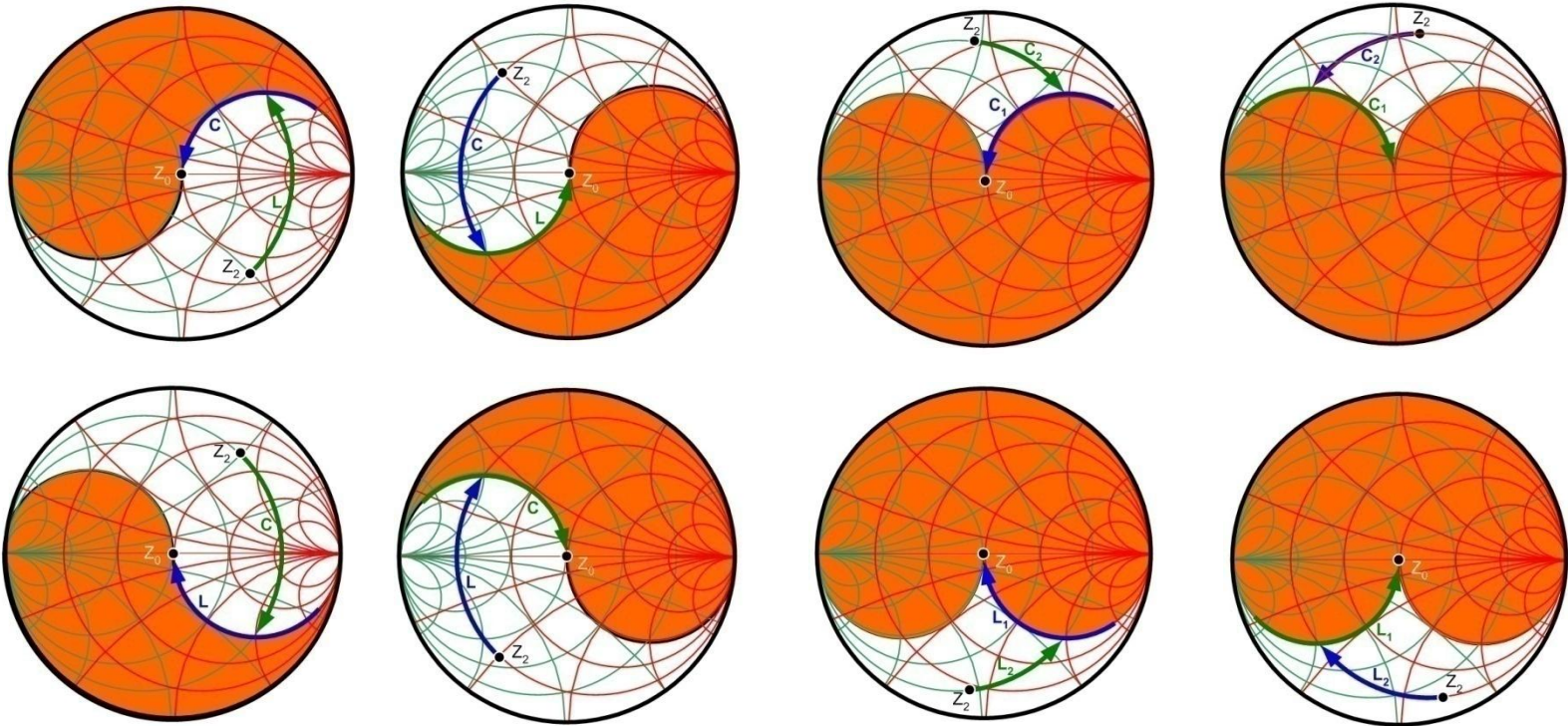
# Matching with 2 reactive elements (L Networks)



Forbidden area for  
current network
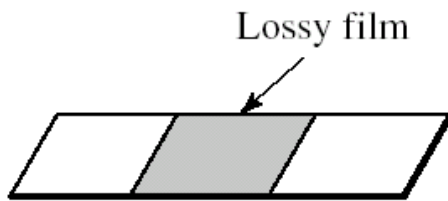
# Practical realization of lumped elements for microwave frequencies




Planar resistor


Lossy film



Chip resistor

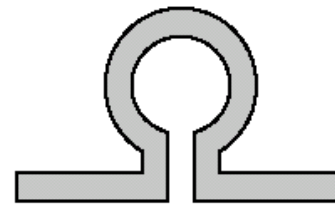


Loop inductor

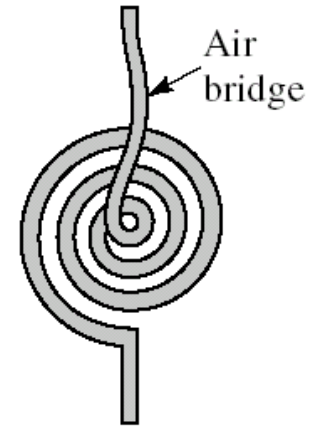


Spiral inductor



Interdigital gap capacitor

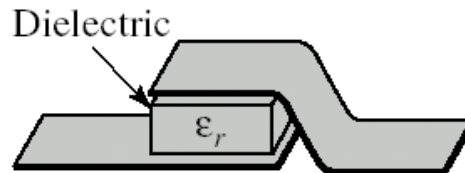

Metal-insulator-metal capacitor

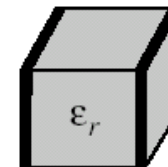

Chip capacitor



Impedance Matching

# Impedance Matching with Stubs

# Stub

- **Stub** (en) = "rest, ciot, cotor, capăt" (ro)
- We avoid the necessity to use lumped elements
- Matching is achieved (with higher accuracy) using usual  $Z_0$  transmission lines of the circuit
- We use one or more lengths of transmission line (stub) connected either in parallel or in series with the transmission feed line :
  - open-circuited
  - short-circuited
- Usually open-circuited transmission lines are easier to implement and are preferred
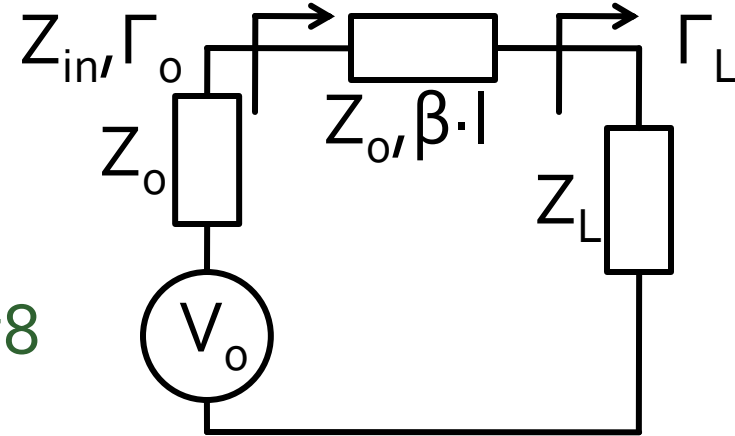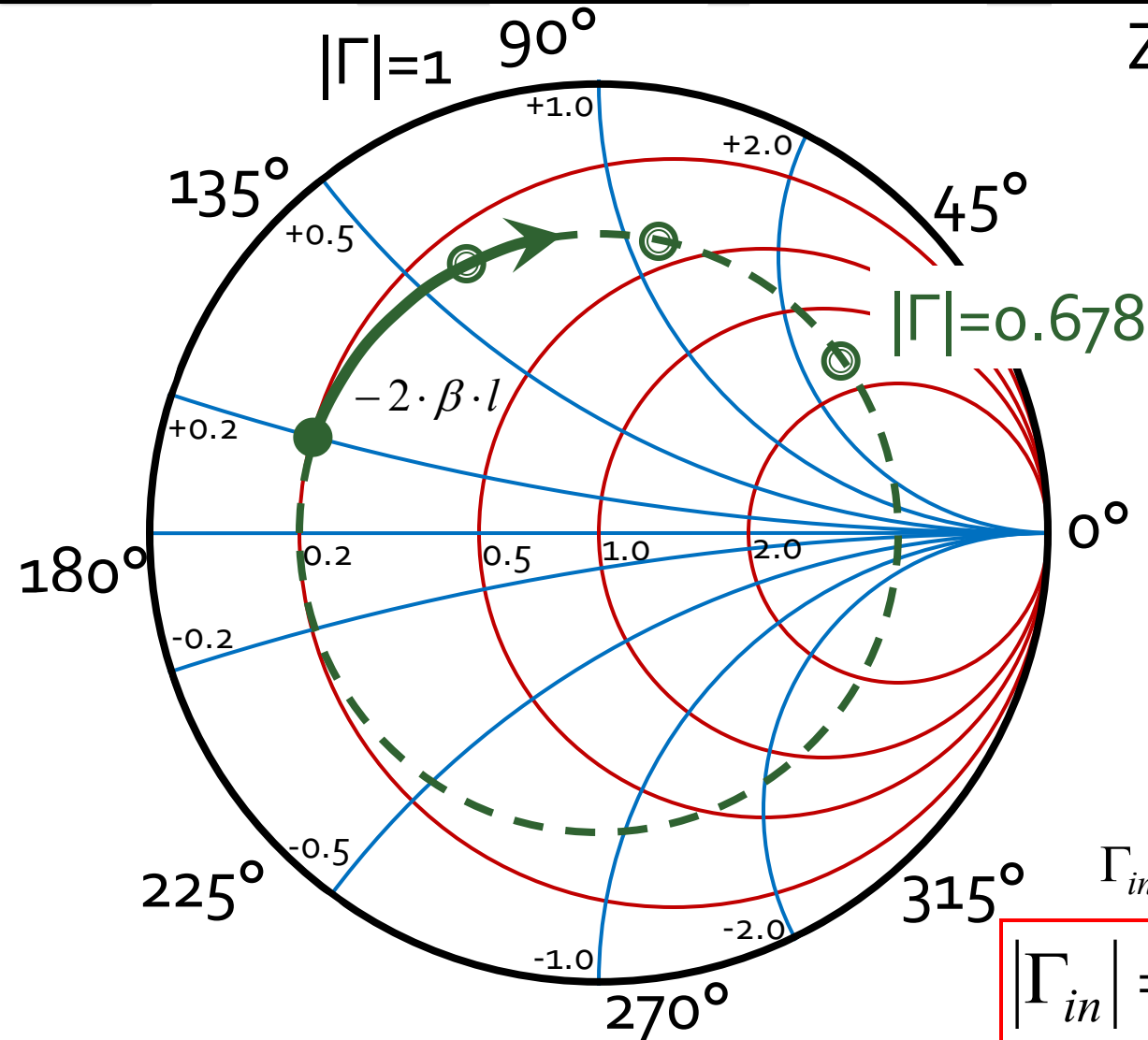
# The Smith Chart, series transmission line, $Z_0$



$$Z_0 = 50\Omega$$

$$Z_L = R_L + j \cdot X_L = 10\Omega + j \cdot 10\Omega$$

$$z_L = r_L + j \cdot x_L = 0.2 + j \cdot 0.2$$



$$\Gamma_L = 0.678 \angle 156.5^\circ$$

$$Z_{in} = Z_0 \cdot \frac{1 + \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}}{1 - \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}}$$

$$\Gamma_{in} = \Gamma_L \cdot e^{-2j \cdot \beta \cdot l}$$

$$|\Gamma_{in}| = |\Gamma_L| \quad \arg(\Gamma_{in}) = \arg(\Gamma_L) - 2 \cdot \beta \cdot l$$

# Matching, series reactance

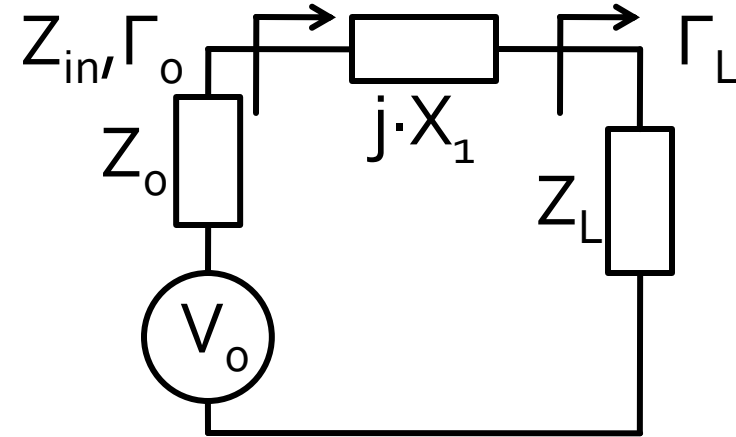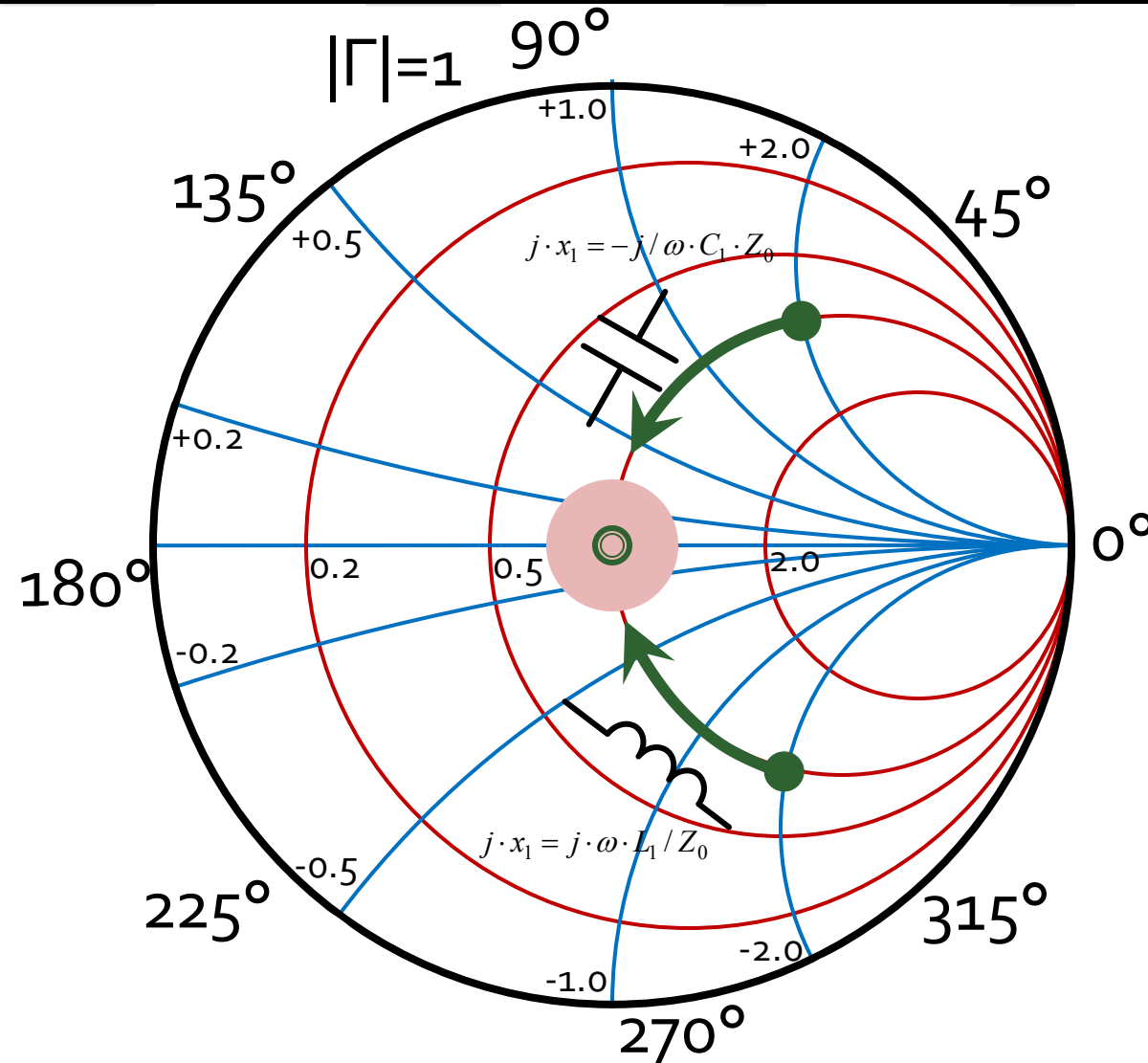

$$Z_L = r_L + j \cdot x_L$$



$$Z_{in} = r_L + j \cdot (x_L + x_1)$$

$$r_{in} = r_L$$

- Match can be obtained **if and only if**  $r_L = 1$
- we compensate the reactive part of the load

$$j \cdot x_1 = -j \cdot x_L$$

# Matching, shunt susceptance

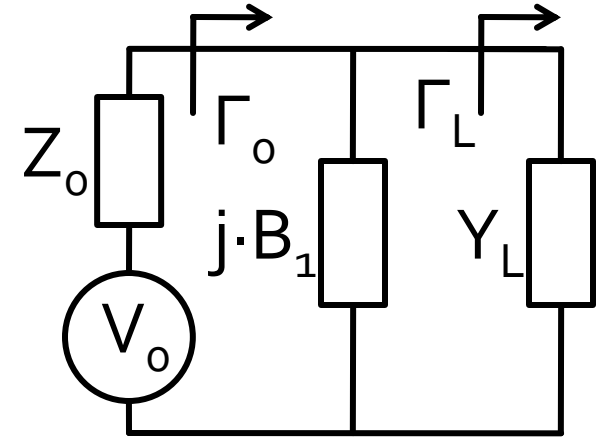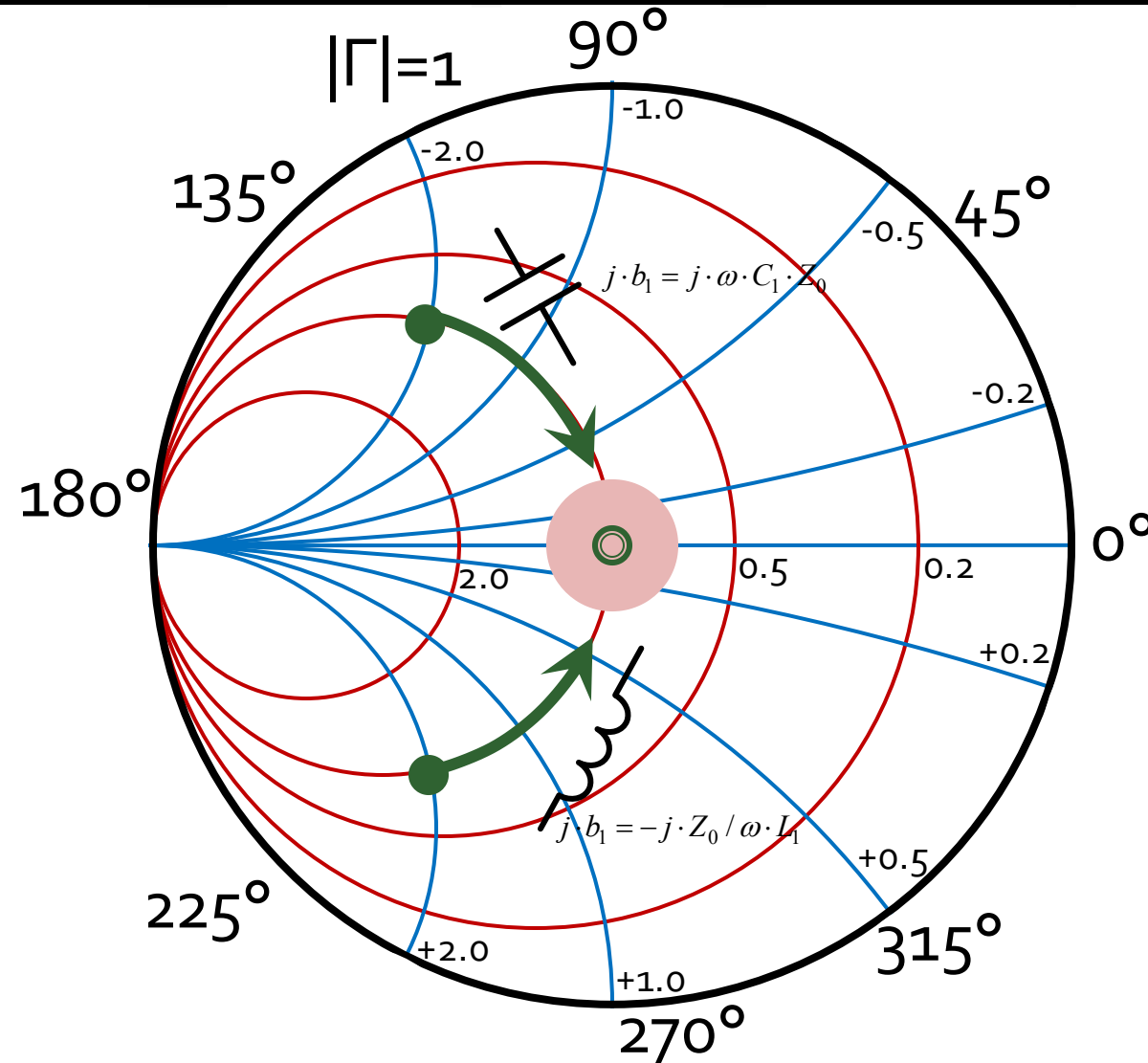


$$y_L = g_L + j \cdot b_L$$

$$y_{in} = g_L + j \cdot (b_L + b_1)$$

$$g_{in} = g_L$$


- Match can be obtained **if and only if**  $g_L = 1$
- we compensate the reactive part of the load  $j \cdot b_1 = -j \cdot b_L$

# Smith chart, $r=1$ and $g=1$

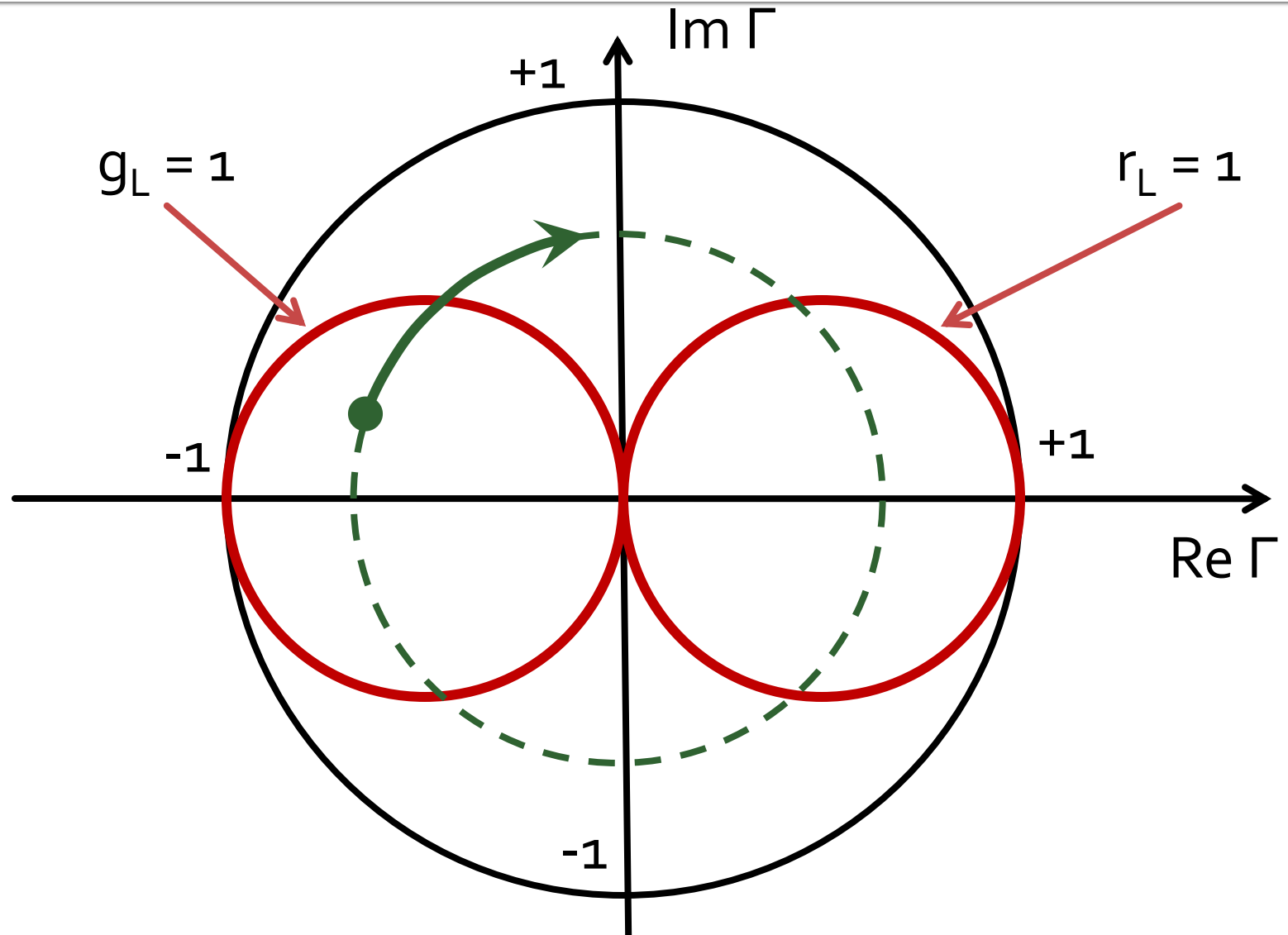


# Single stub tuning

- Shunt Stub

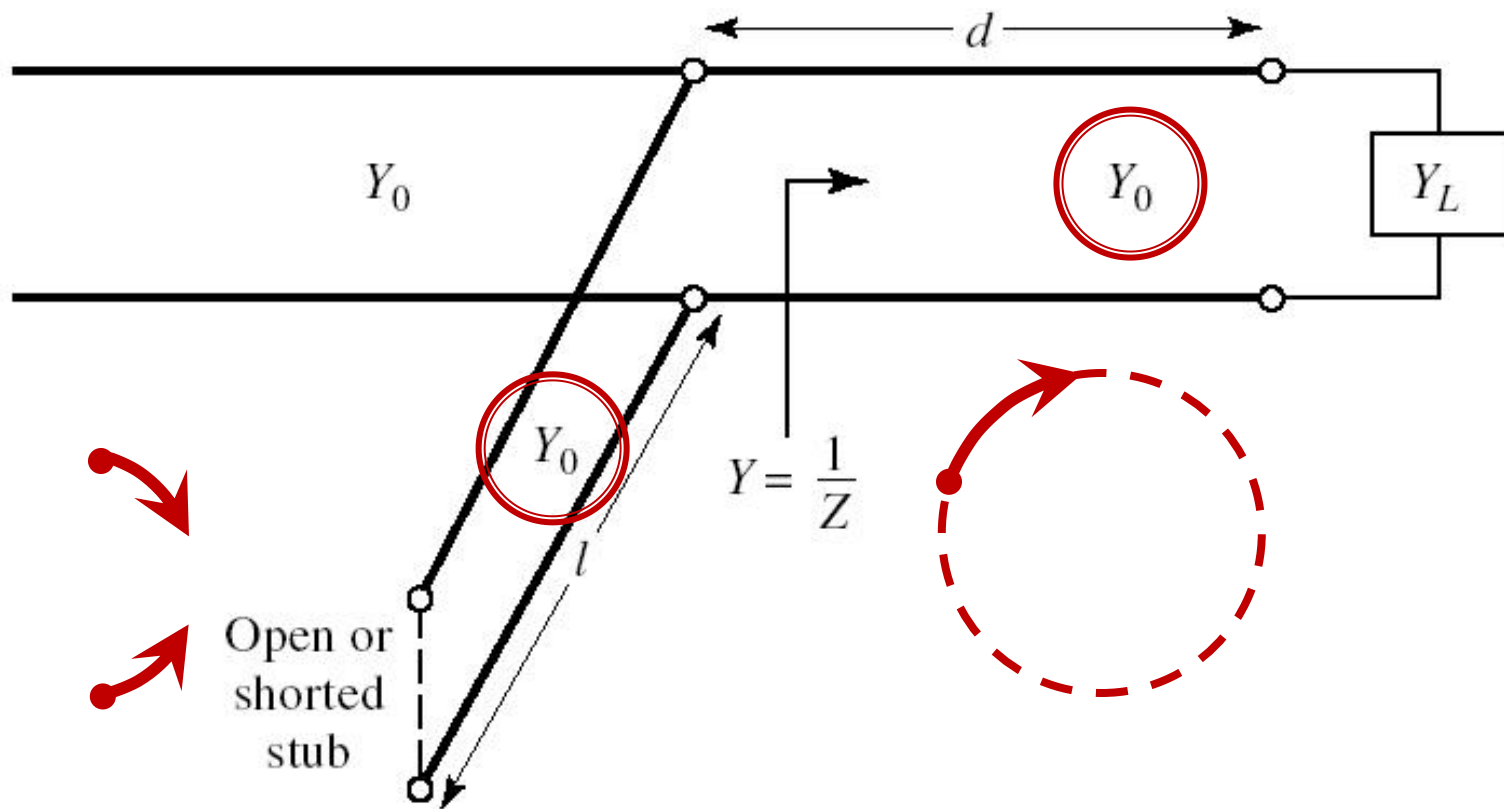
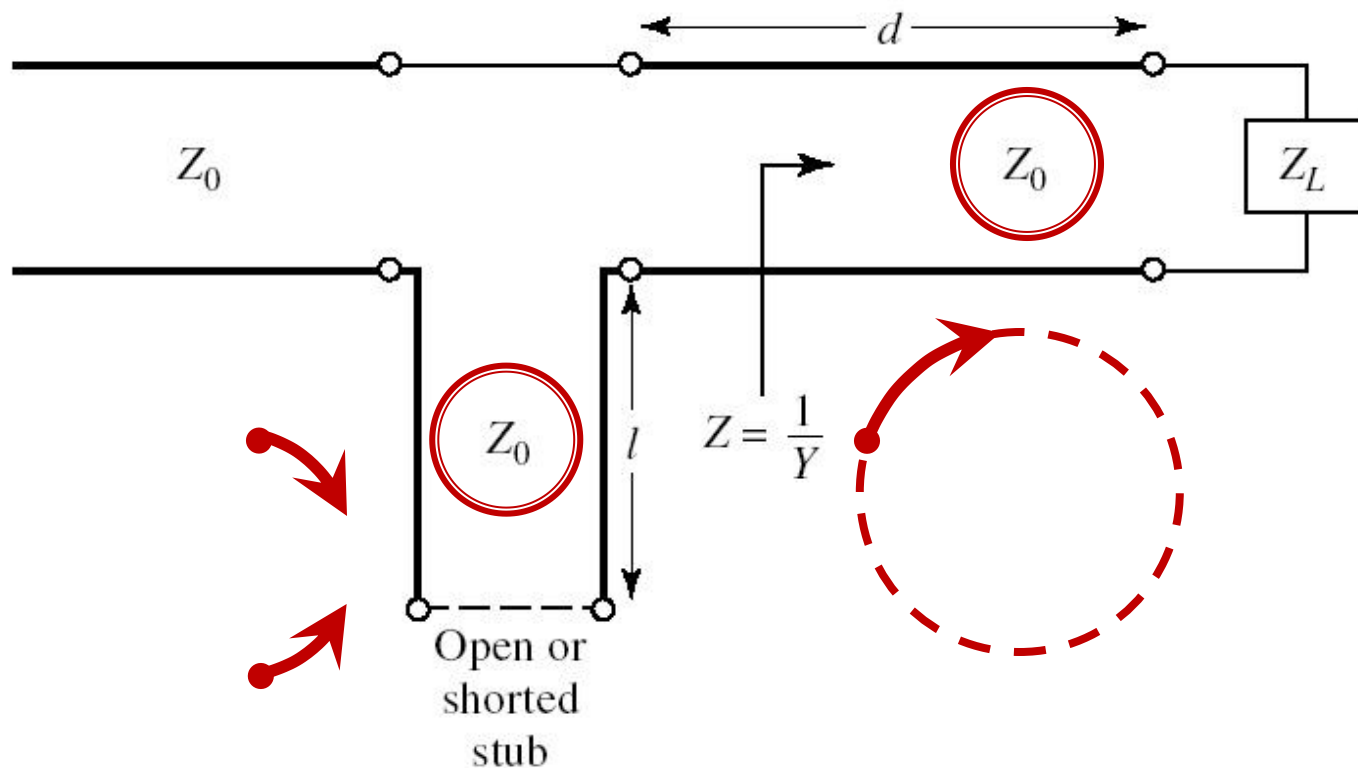
# Single stub tuning

- Series Stub
- difficult to realize in single conductor line technologies (microstrip)




# Shunt Stub

Sectiune de linie paralel

---

# Case 1, Shunt Stub

- Shunt Stub

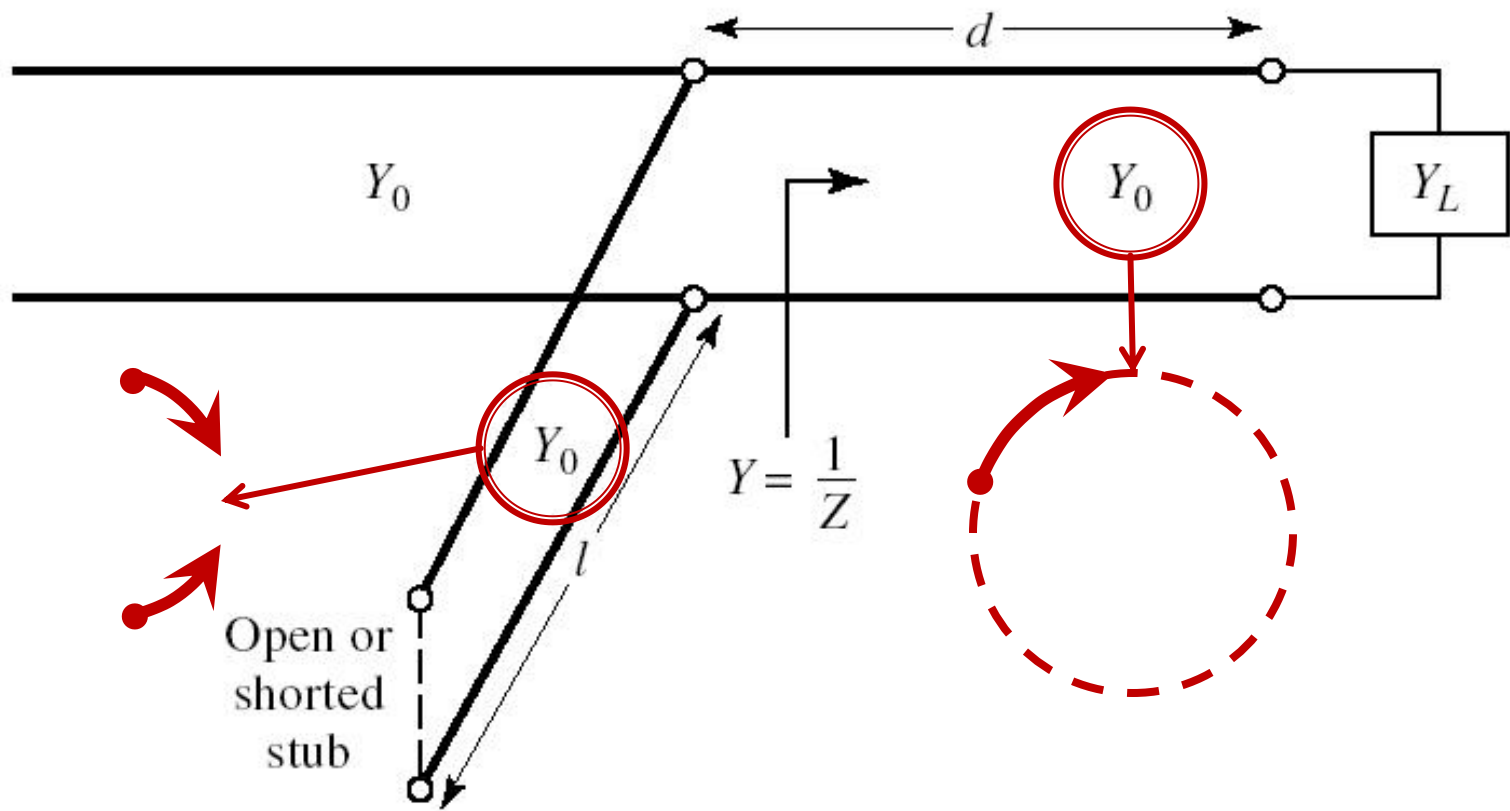

# Case 1, Shunt Stub


- We use a series transmission line to move the reflection coefficient **on the circle**  $g_L = 1$
- We compensate the remaining reactive part of the load with a shunt reactance to achieve match
- The shunt reactance is made with a stub which can be,  
as needed:
  - open-circuited
  - short-circuited

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

$$Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l$$



$$Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$
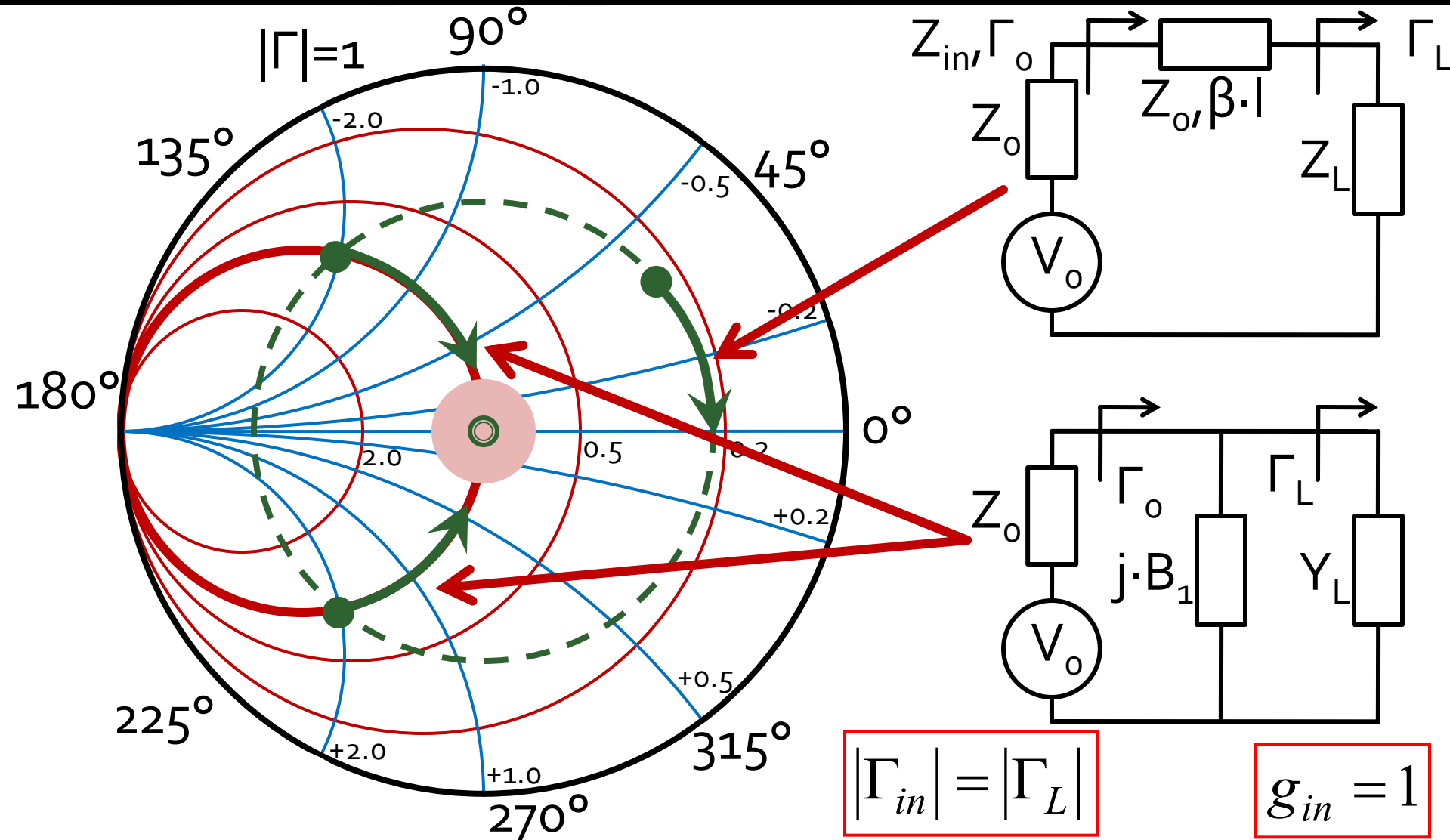
# Matching, series line + shunt susceptance



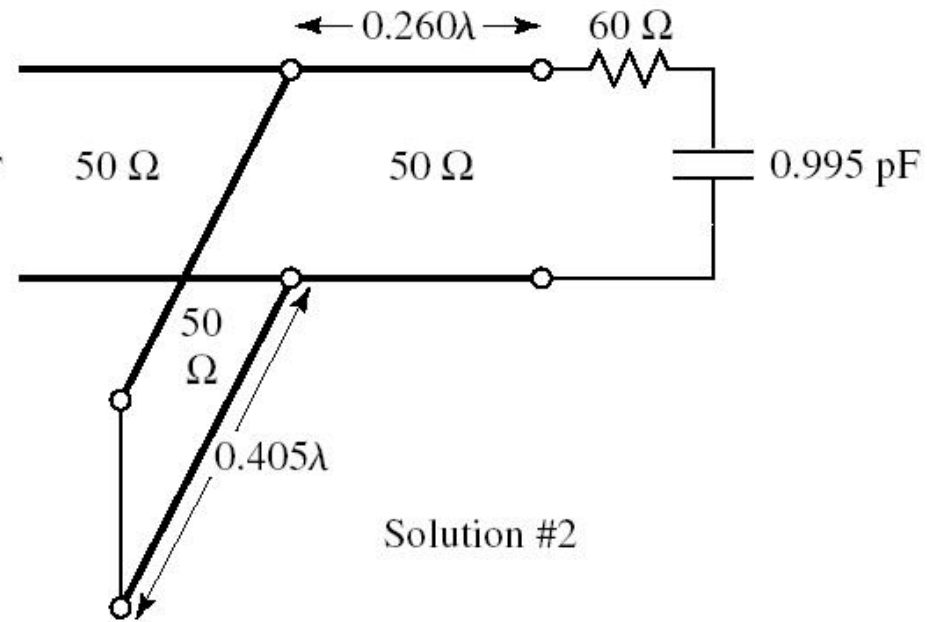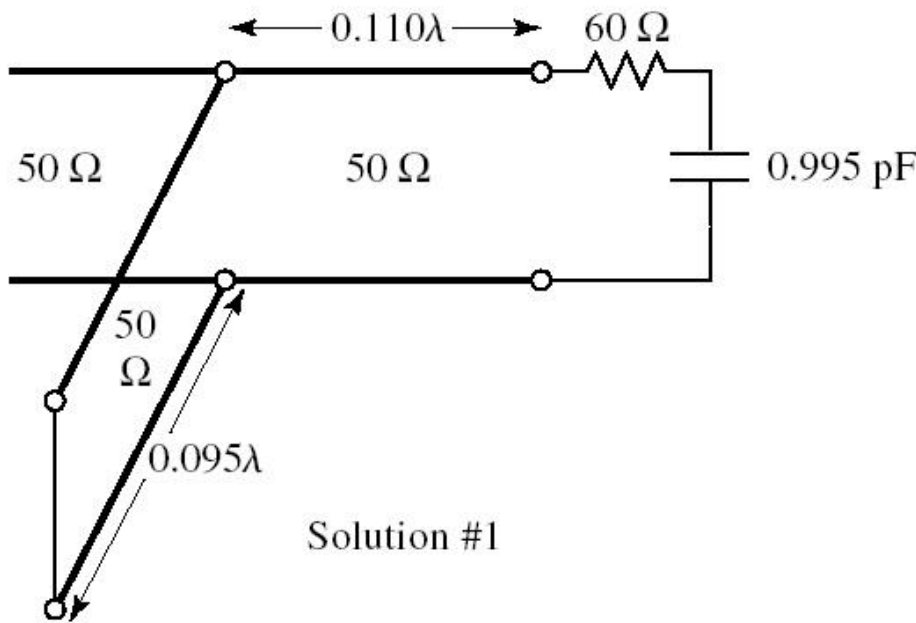
# Example, Shunt Stub, sc.


- load:  $60\ \Omega$  series with  $0.995\ \text{pF}$  at  $2\ \text{GHz}$
- two possible solutions




# Example, Shunt Stub, sc.

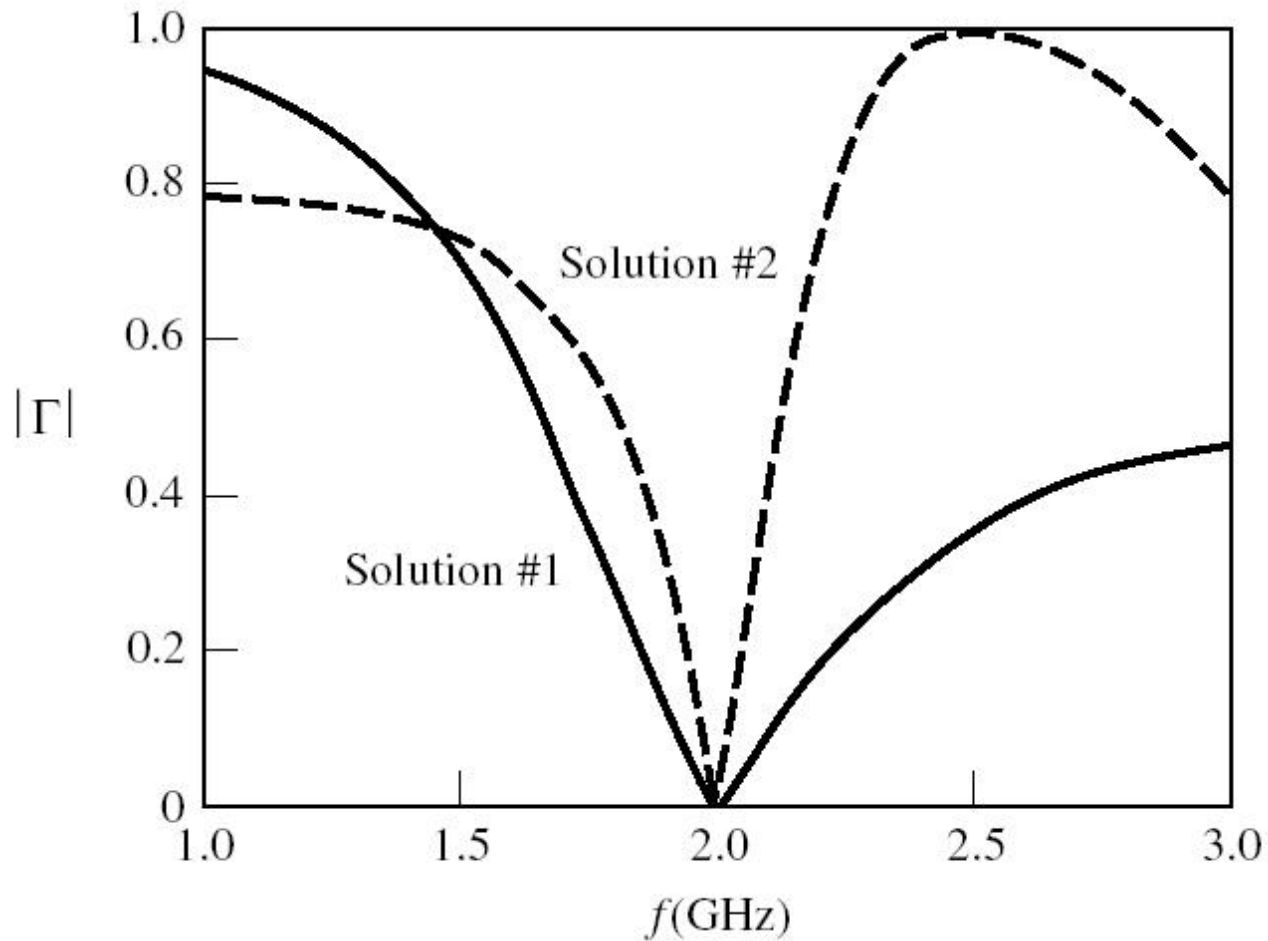


# Example, Shunt Stub, sc.

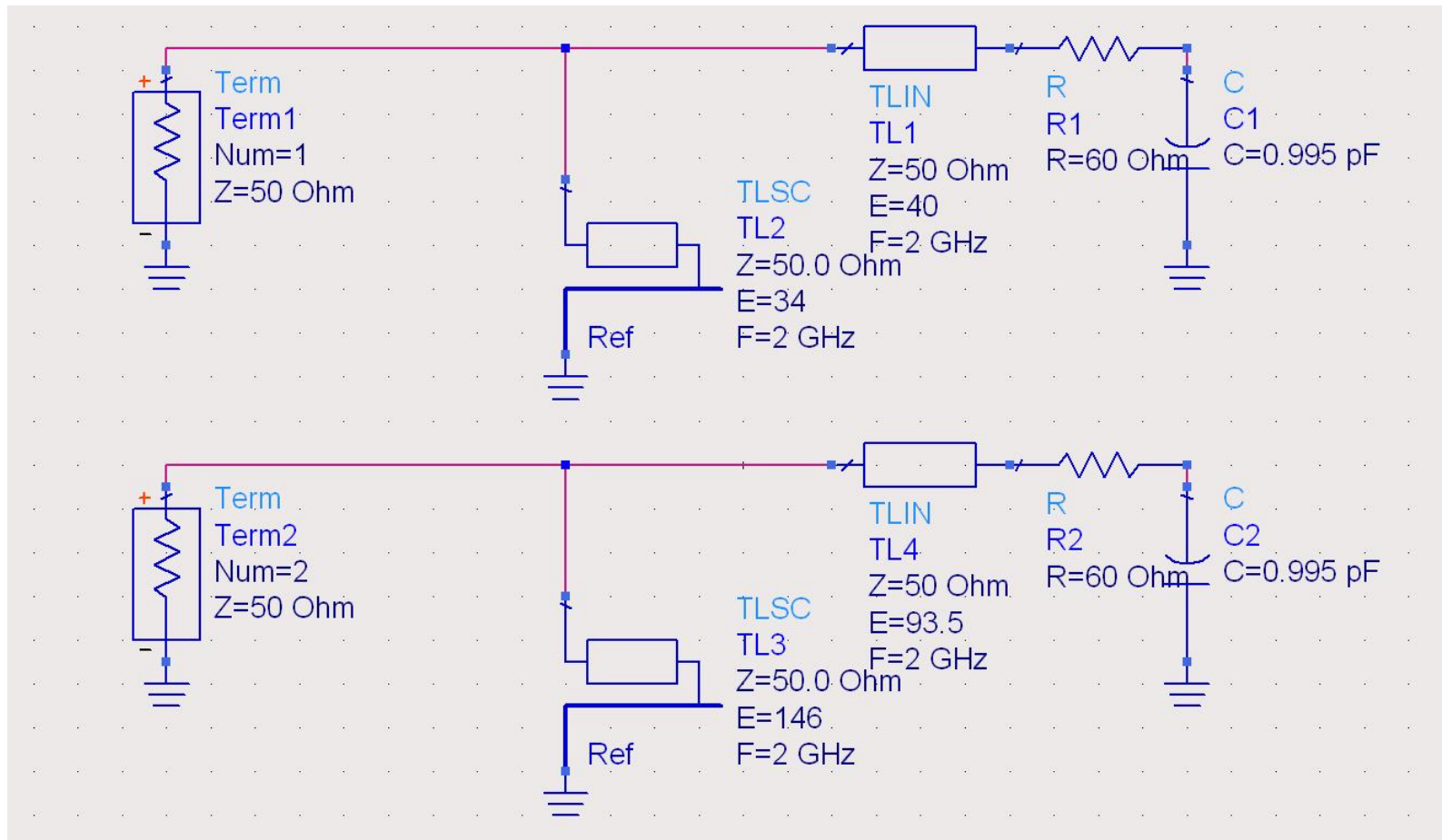


# Example, Shunt Stub, sc.

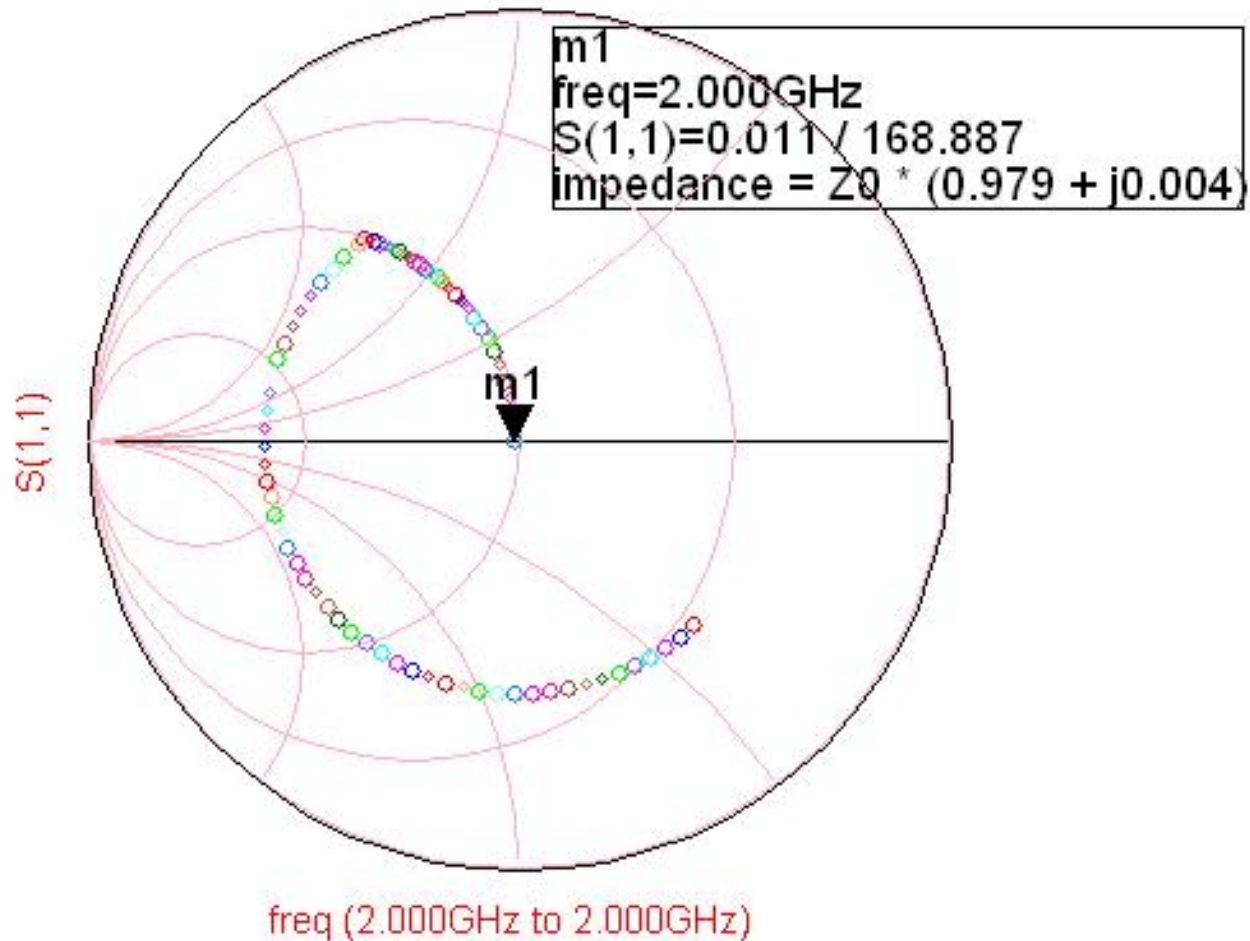


# Example, Shunt Stub, sc.

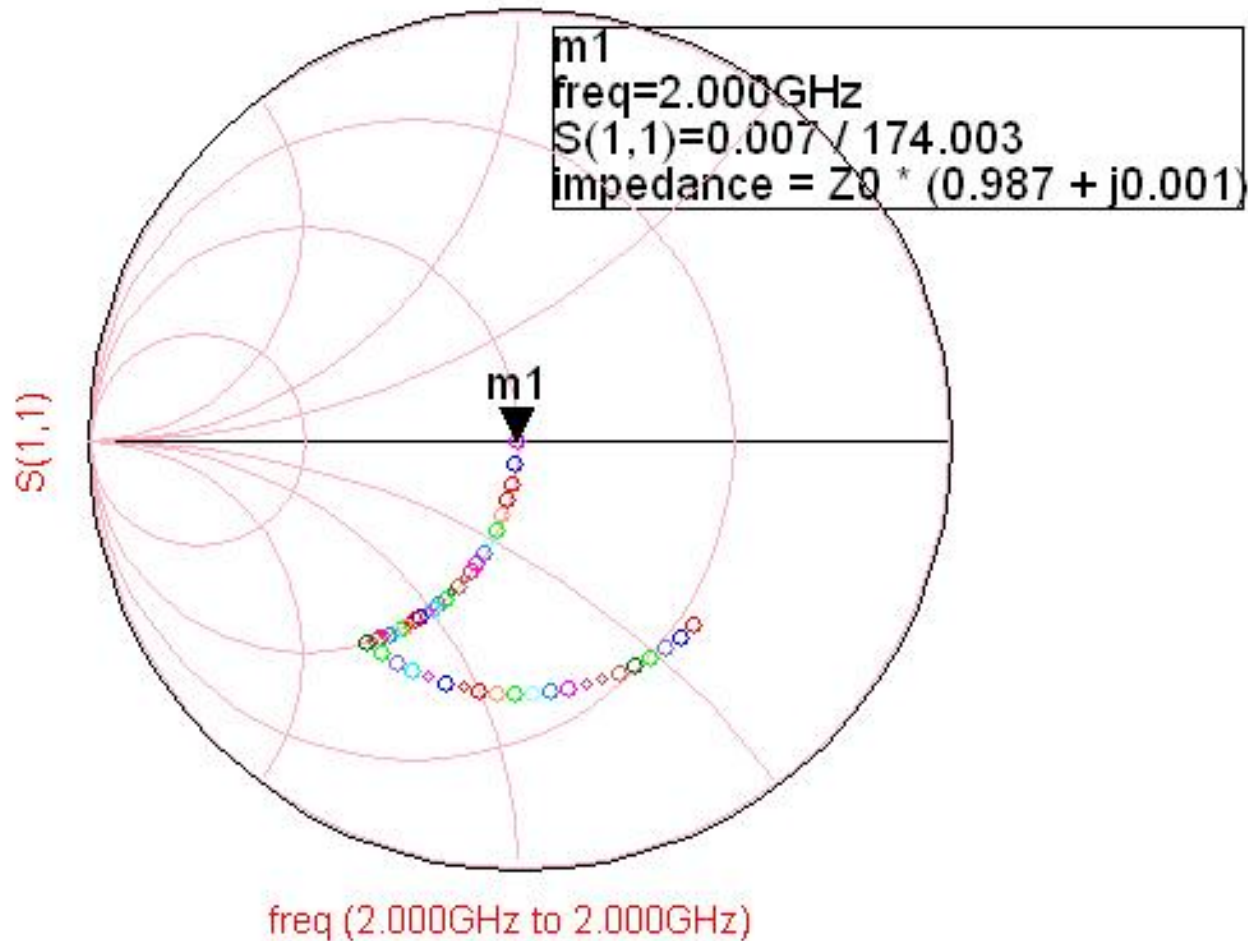

# Example, Shunt Stub, sc.

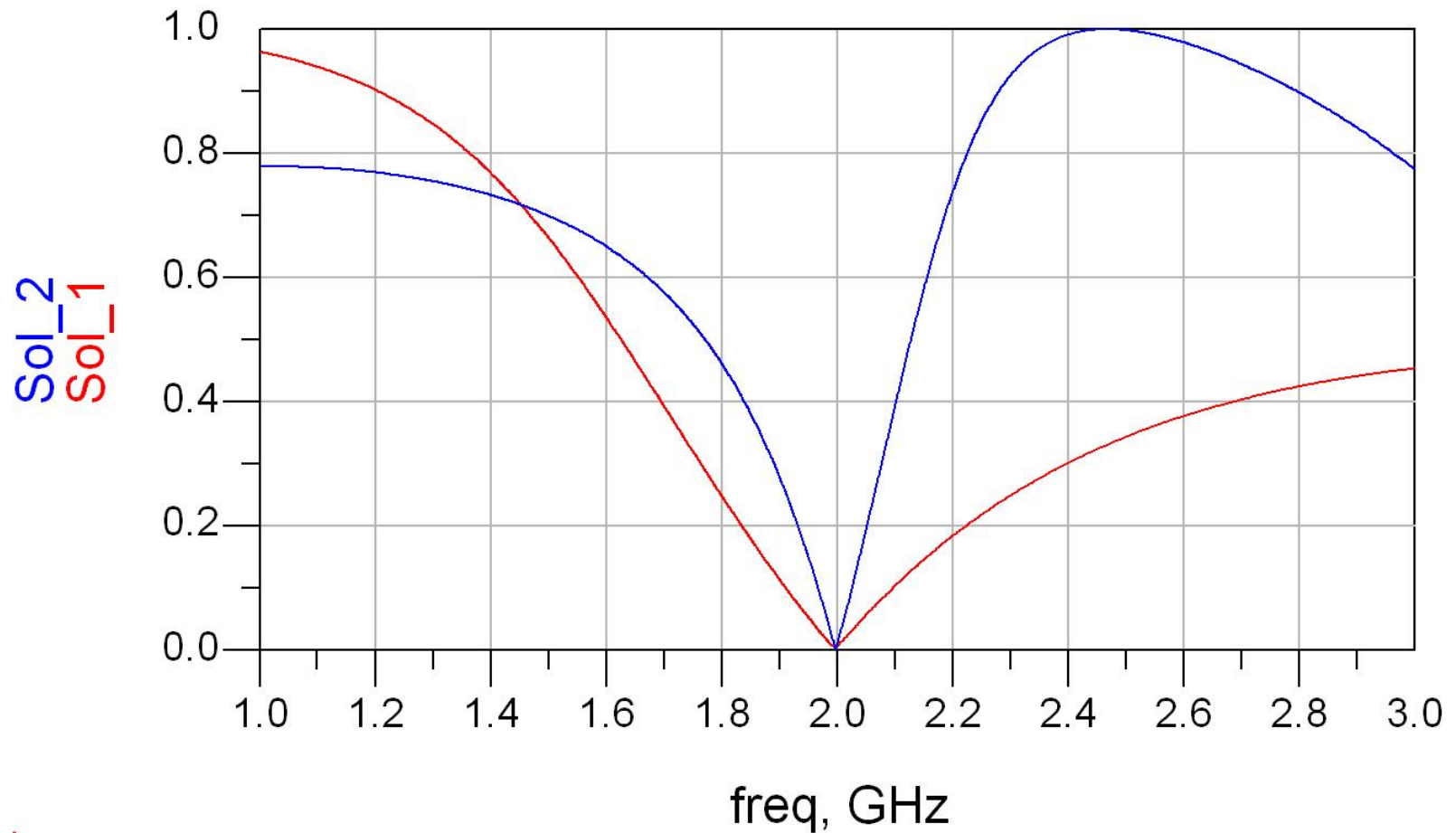

# Example, Shunt Stub, sc.

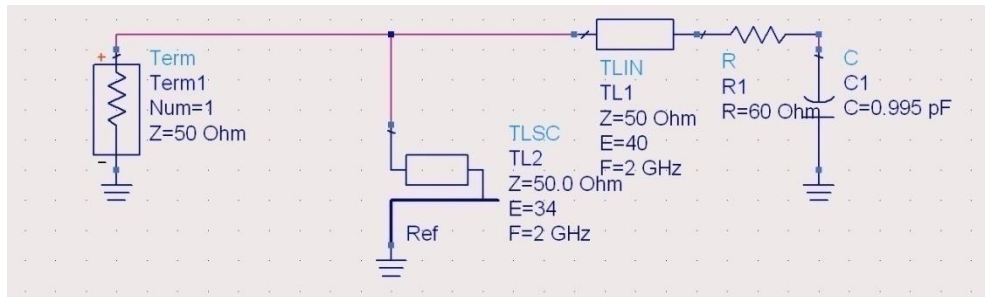


$$l_1 = \frac{40^\circ}{360^\circ} \cdot \lambda = 0.111 \cdot \lambda$$

$$l_2 = \frac{34^\circ}{360^\circ} \cdot \lambda = 0.094 \cdot \lambda$$


$$l_1 = \frac{93.5^\circ}{360^\circ} \cdot \lambda = 0.260 \cdot \lambda$$
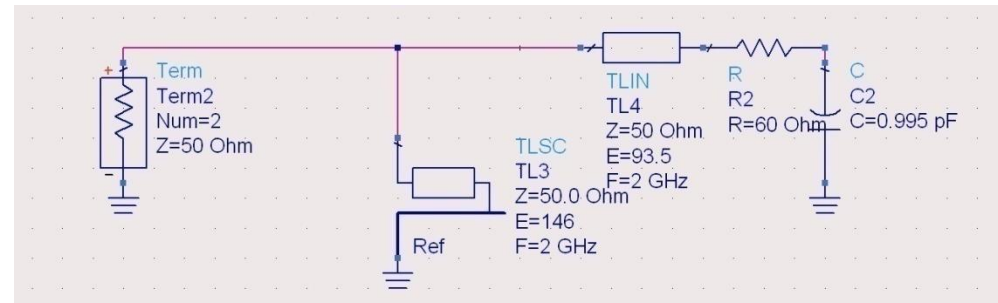
$$l_2 = \frac{146^\circ}{360^\circ} \cdot \lambda = 0.406 \cdot \lambda$$



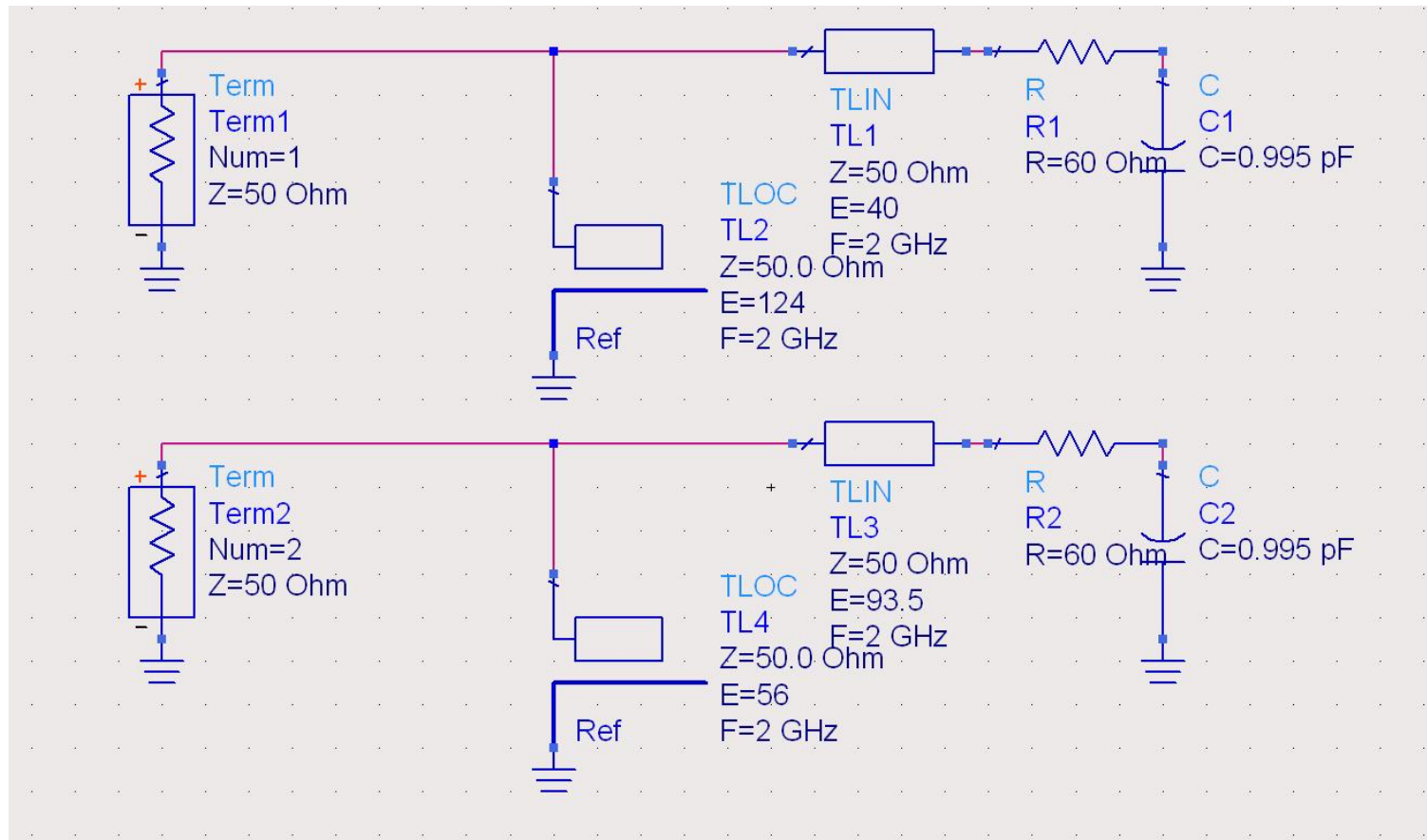
# Example, Shunt Stub, oc.


- load:  $60\ \Omega$  series with  $0.995\ \text{pF}$  at  $2\ \text{GHz}$
- two possible solutions




# Example, Shunt Stub, oc.

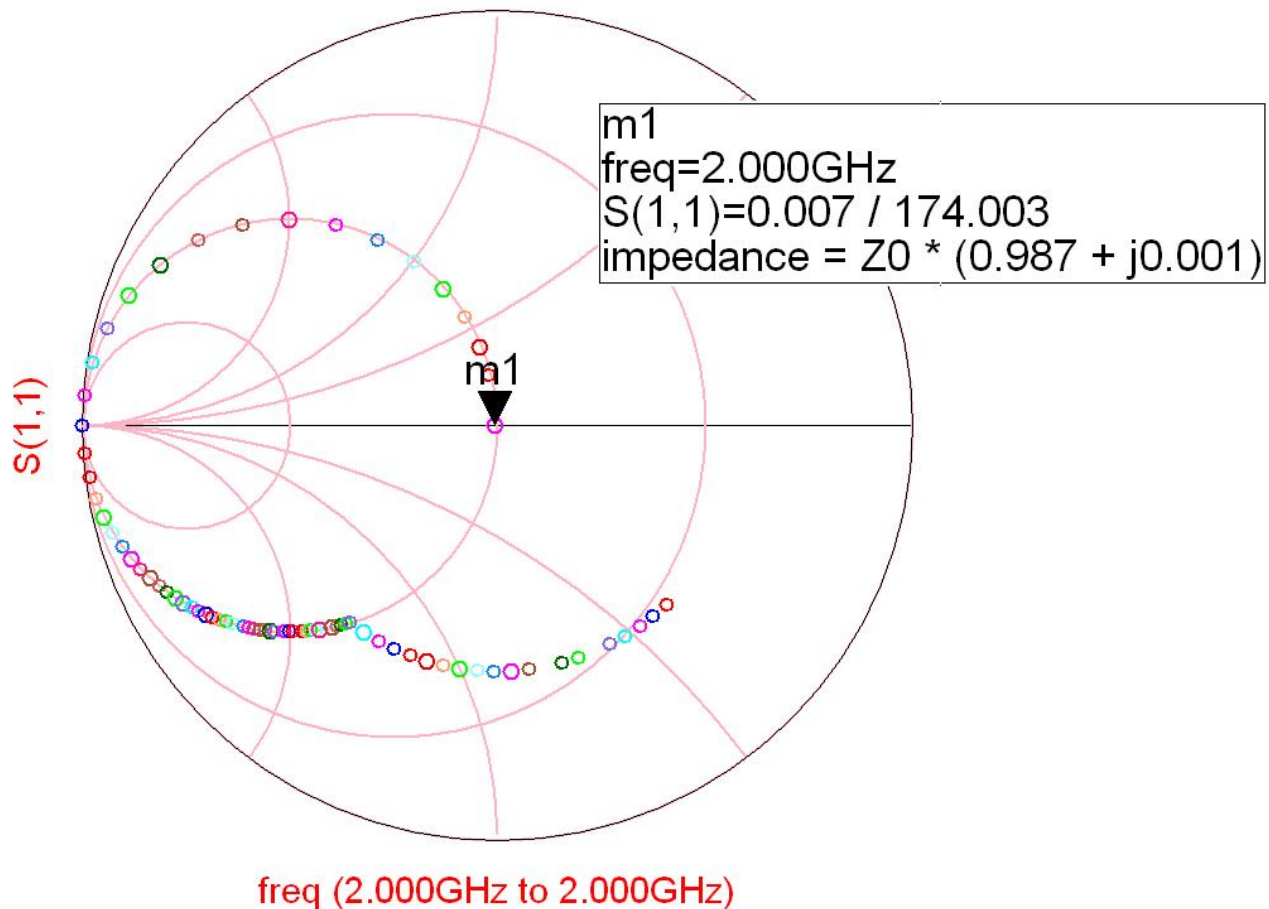


# Example, Shunt Stub, oc.

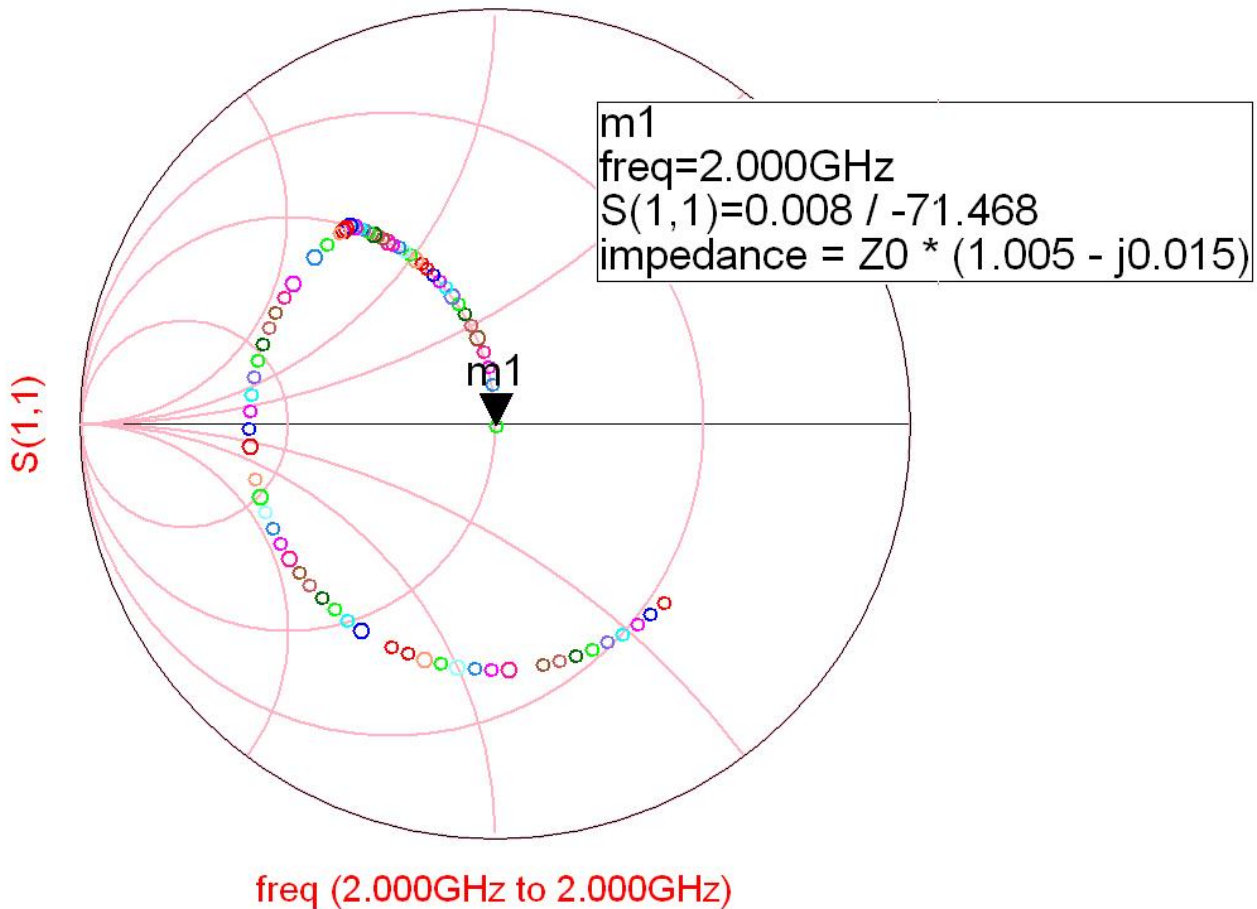

# Example, Shunt Stub, oc.

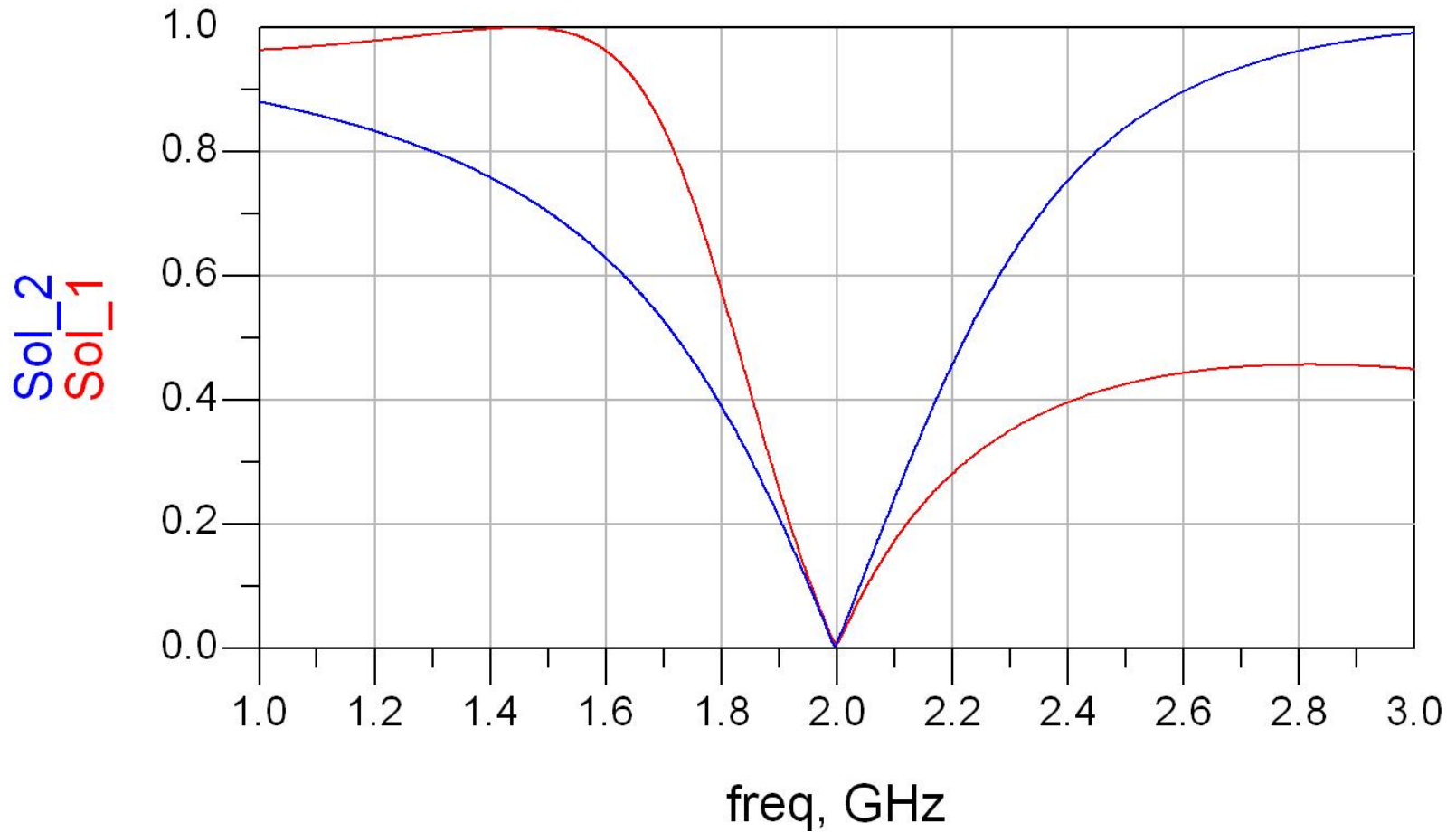

# Example, Shunt Stub, oc.

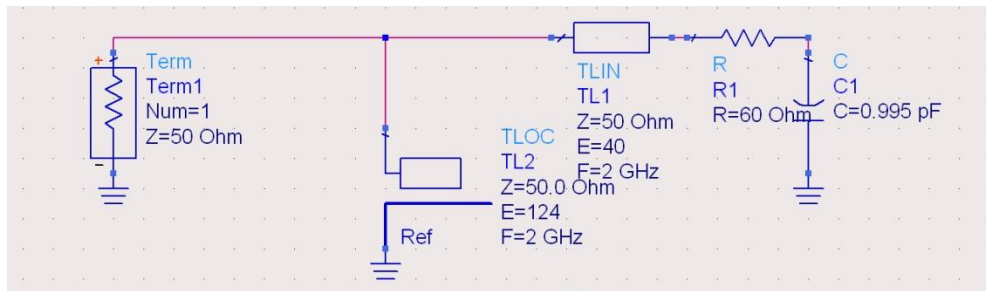


$$l_1 = \frac{40^\circ}{360^\circ} \cdot \lambda = 0.111 \cdot \lambda$$



$$l_2 = \frac{124^\circ}{360^\circ} \cdot \lambda = 0.344 \cdot \lambda = 0.094 \cdot \lambda + \frac{\lambda}{4}$$
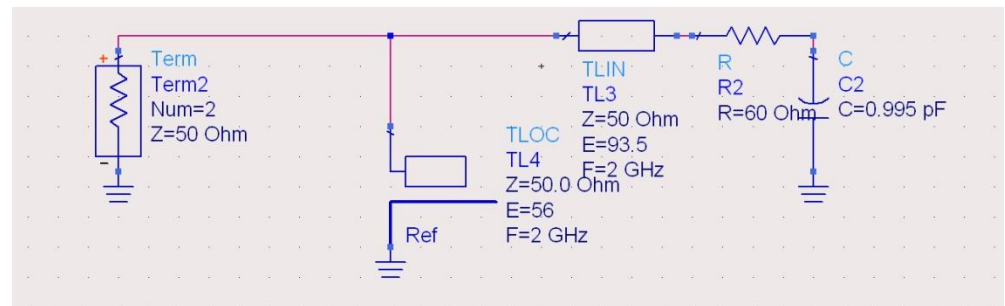
$$l_1 = \frac{93.5^\circ}{360^\circ} \cdot \lambda = 0.260 \cdot \lambda$$



$$l_2 = \frac{56^\circ}{360^\circ} \cdot \lambda = 0.156 \cdot \lambda = 0.406 \cdot \lambda - \frac{\lambda}{4}$$



# Shunt Stub, some notes

- mathematical functions which offer the input impedance in a stub are periodic functions of  $l$ , tan/cot based functions

$$Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l$$

$$Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$

- adding or subtracting

$$E = \beta \cdot l = \pi = 180^\circ \quad l = k \cdot \frac{\lambda}{2}, \forall k \in \mathbf{N}$$

doesn't change the result (full rotation around the Smith Chart – hence the  $0.5\lambda$  gradation of the circumference of the diagram)

# Shunt Stub, some notes

- adding or subtracting  $\lambda/4$  transforms the impedance:

$$Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l$$

$$Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$

$$\tan \beta \cdot \left( l + \frac{\lambda}{4} \right) = \tan \left( \beta \cdot l + \frac{\pi}{2} \right) = \frac{\sin(\beta \cdot l + \pi/2)}{\cos(\beta \cdot l + \pi/2)} = \frac{\cos \beta \cdot l}{-\sin \beta \cdot l} = -\cot \beta \cdot l$$

from the open-circuited value to the short-circuited one and vice versa


- For tuning in ADS it's better to start from the neutral point (value of the electrical length of the line which doesn't influence the circuit)
  - series line:  $E = \beta \cdot l = 0$
  - shunt stub:  $Z_{in} \rightarrow \infty, \tan \beta \cdot l / \cot \beta \cdot l \rightarrow \infty, E = 90^\circ / 0^\circ$

# Analytical solution

Shunt Stub

---

# Analytical solution, impedances

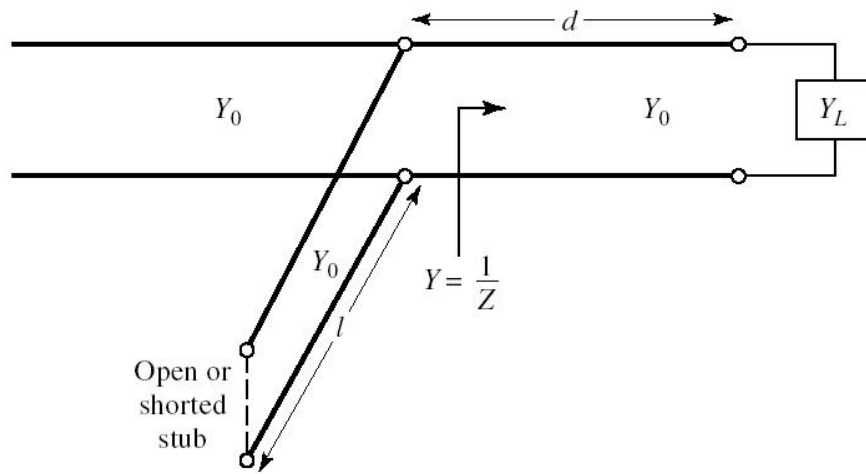

$$Z_L = \frac{1}{Y_L} = R_L + j \cdot X_L$$

$$Z = Z_0 \cdot \frac{(R_L + j \cdot X_L) + j \cdot Z_0 \cdot t}{Z_0 + j \cdot (R_L + j \cdot X_L) \cdot t}$$

$$\overset{\text{not}}{t} = \tan \beta \cdot d \quad Y = G + j \cdot B = \frac{1}{Z}$$


$$G = \frac{R_L \cdot (1 + t^2)}{R_L^2 + (X_L + Z_0 \cdot t)^2}$$

$$B = \frac{R_L^2 \cdot t - (Z_0 - X_L \cdot t) \cdot (X_L + Z_0 \cdot t)}{Z_0 \cdot [R_L^2 + (X_L + Z_0 \cdot t)^2]}$$

- $d$  (which implies  $t$ ) is chosen so that:  $G = Y_0 = \frac{1}{Z_0}$

$$Z_0 \cdot (R_L - Z_0) \cdot t^2 - 2 \cdot X_L \cdot Z_0 \cdot t + (R_L \cdot Z_0 - R_L^2 - X_L^2) = 0$$

# Analytical solution

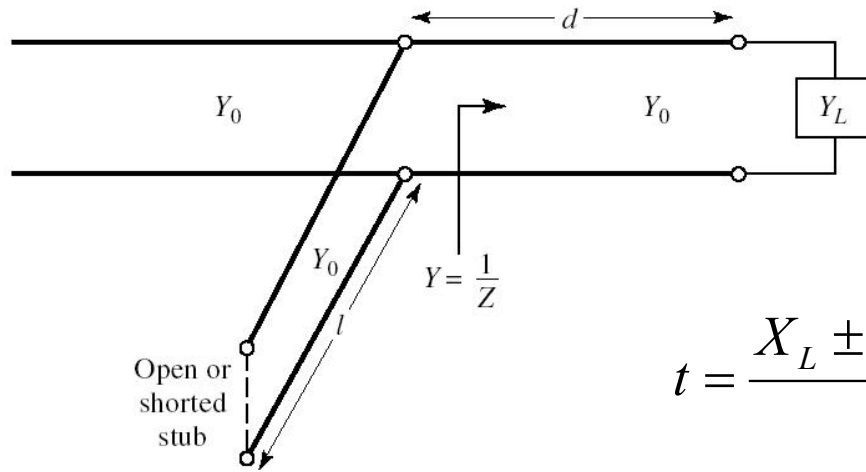


$$t = -\frac{X_L}{2 \cdot Z_0}, \quad R_L = Z_0$$

$$t = \frac{X_L \pm \sqrt{R_L \cdot [(Z_0 - R_L)^2 + X_L^2]} / Z_0}{R_L - Z_0} \quad R_L \neq Z_0$$

- second grade equation, 2 solutions possible
- $d$  computed from  $t$

$$\frac{d}{\lambda} = \begin{cases} \frac{1}{2\pi} \cdot \arctan t & t \geq 0 \\ \frac{1}{2\pi} \cdot (\pi + \arctan t) & t < 0 \end{cases}$$

# Analytical solution

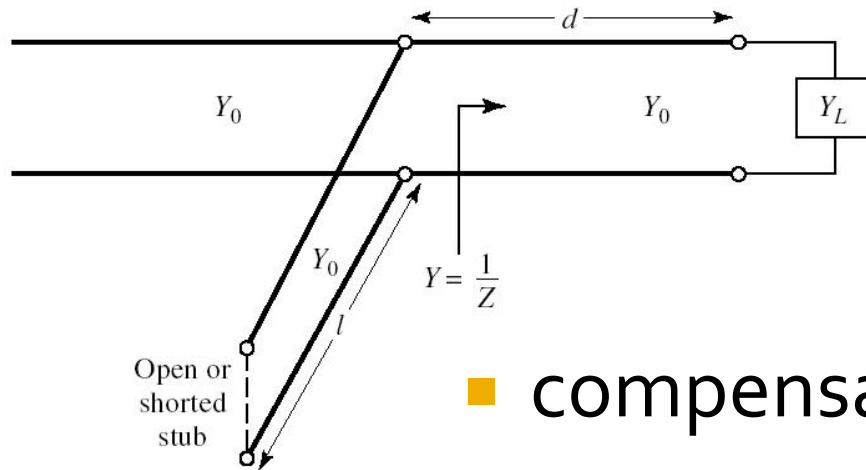

$$B_S = -B$$

$$B = \frac{R_L^2 \cdot t - (Z_0 - X_L \cdot t) \cdot (X_L + Z_0 \cdot t)}{Z_0 \cdot [R_L^2 + (X_L + Z_0 \cdot t)^2]}$$

- compensating susceptance is:


$$\frac{l_{oc}}{\lambda} = \frac{1}{2\pi} \cdot \arctan\left(\frac{B_S}{Y_0}\right) = \frac{-1}{2\pi} \cdot \arctan\left(\frac{B}{Y_0}\right)$$

$$\frac{l_{sc}}{\lambda} = \frac{-1}{2\pi} \cdot \arctan\left(\frac{Y_0}{B_S}\right) = \frac{1}{2\pi} \cdot \arctan\left(\frac{Y_0}{B}\right)$$

- for **negative lengths** we add  $\lambda/2$
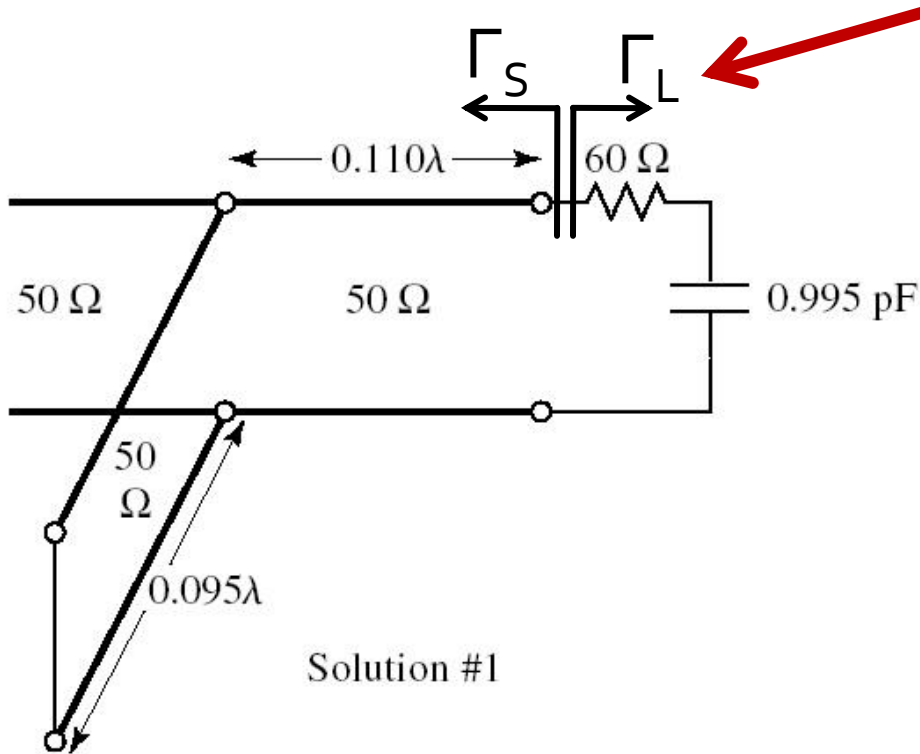
# Analytical solution, reflection coefficient

- load:  $60\ \Omega$  series with  $0.995\ \text{pF}$  at  $2\ \text{GHz}$



$$Z_L = R_L + \frac{1}{j \cdot \omega \cdot C_L} = 60\ \Omega - j \cdot 79.977\ \Omega$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 0.405 - j \cdot 0.432$$

$$Y_L = \frac{1}{Z_L} = 0.006\ \text{S} + j \cdot 0.008\ \text{S}$$

$$y_L = \frac{Y_L}{Y_0} = 0.3 + j \cdot 0.4$$

- matching requires obtaining conjugate value for  $\Gamma$


$$\Gamma_S = \Gamma_L^* = 0.405 + j \cdot 0.432$$

$$\Gamma_S = 0.593 \angle 46.85^\circ$$

$$|\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ$$
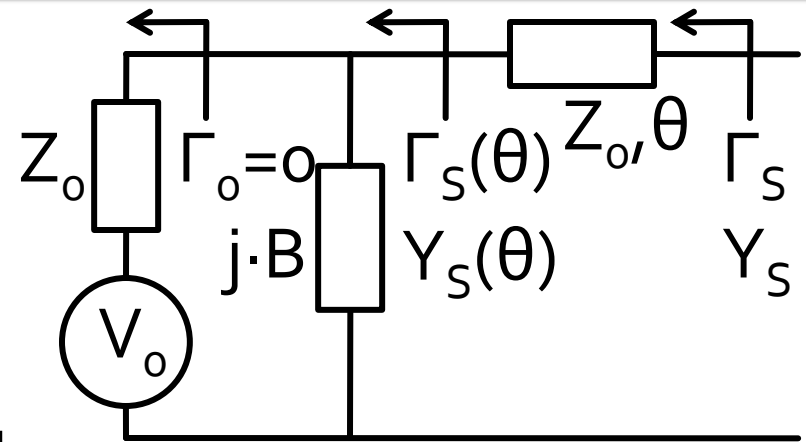
# Analytical solution, $\Gamma$

- series line
  - electrical length  $E = \beta \cdot l = \theta$
  - moves the reflection coefficient on the circle  $g=1$
- shunt stub
  - electrical length  $E = \beta \cdot l_{sp} = \theta_{sp}$
  - moves the reflection coefficient to the center of the Smith Chart ( $\Gamma_o = 0$ )



$$y_s = \frac{Y_s}{Y_0} = Y_s \cdot Z_0 = Y_s \cdot 50\Omega$$

$$y_s = \frac{1 - \Gamma_s}{1 + \Gamma_s} = 0.3 - j \cdot 0.4$$

$$\Gamma_s(\theta) = [\Gamma_L(\theta)]^* = [\Gamma_L \cdot e^{-2j\theta}]^*$$

$$\Gamma_s(\theta) = \Gamma_L^* \cdot e^{2j\theta} = \Gamma_s \cdot e^{2j\theta}$$

$$y_s(\theta) = \frac{1 - \Gamma_s(\theta)}{1 + \Gamma_s(\theta)} = \frac{1 - \Gamma_s \cdot e^{2j\theta}}{1 + \Gamma_s \cdot e^{2j\theta}}$$

# A.S., $\Gamma$ , series line, proof

- After the series line with electrical length  $\theta$ :

$$\operatorname{Re}[y_S(\theta)] = 1 \qquad \operatorname{Im}[y_S(\theta)] = B$$

$$\operatorname{Re}[y_S(\theta)] = \frac{1}{2} \cdot [y_S(\theta) + y_S^*(\theta)] \qquad \operatorname{Im}[y_S(\theta)] = \frac{1}{2j} \cdot [y_S(\theta) - y_S^*(\theta)]$$

$$\operatorname{Re}[y_S(\theta)] = \frac{1}{2} \cdot \left[ \frac{1 - \Gamma_S \cdot e^{2j\theta}}{1 + \Gamma_S \cdot e^{2j\theta}} + \frac{1 - \Gamma_S^* \cdot e^{-2j\theta}}{1 + \Gamma_S^* \cdot e^{-2j\theta}} \right] \qquad \Gamma_S = |\Gamma_S| \cdot e^{j\varphi}$$

$$\operatorname{Re}[y_S(\theta)] = \frac{1}{2} \cdot \left[ \frac{(1 - |\Gamma_S| \cdot e^{j(\varphi+2\theta)}) \cdot (1 + |\Gamma_S| \cdot e^{-j(\varphi+2\theta)}) + (1 - |\Gamma_S| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 + |\Gamma_S| \cdot e^{j(\varphi+2\theta)})}{(1 + |\Gamma_S| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 + |\Gamma_S| \cdot e^{j(\varphi+2\theta)})} \right]$$

$$\operatorname{Re}[y_S(\theta)] = \frac{1}{2} \cdot \left[ \frac{2 - 2 \cdot |\Gamma_S|^2}{1 + |\Gamma_S|^2 + 2 \cdot |\Gamma_S| \cdot \cos(\varphi + 2\theta)} \right] = 1 \quad \Rightarrow \quad \boxed{\cos(\varphi + 2\theta) = -|\Gamma_S|}$$

# A.S., $\Gamma$ , series line, usage

- Equations for computing the series line  $\theta$ :

$$\operatorname{Re}[y_S(\theta)] = 1 \Rightarrow \boxed{\cos(\varphi + 2\theta) = -|\Gamma_S|}$$

$$\Gamma_S = |\Gamma_S| \cdot e^{j\varphi} \quad \Gamma_S = 0.593 \angle 46.85^\circ \quad |\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ$$

- two solutions possible, in the  $0 \div 180^\circ$  range
  - add  $\lambda/2 \Leftrightarrow 180^\circ$  as needed

$$\theta = \frac{1}{2} \cdot [\pm \cos^{-1}(-|\Gamma_S|) - \varphi + k \cdot 360^\circ] = \frac{1}{2} \cdot [\pm \cos^{-1}(-|\Gamma_S|) - \varphi] + k \cdot 180^\circ$$

$$\cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^\circ \quad \forall k \in \mathbb{N}$$

$$(46.85^\circ + 2\theta) = \begin{cases} +126.35^\circ \\ -126.35^\circ \end{cases} \quad \theta = \begin{cases} +39.7^\circ \\ -86.6^\circ + 180^\circ = +93.4^\circ \end{cases}$$

# A.S., $\Gamma$ , shunt stub, proof

- Equations for computing the shunt stub  $\theta_{sp}$ :

$$\operatorname{Re}[y_S(\theta)] = 1 \qquad \cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\operatorname{Im}[y_S(\theta)] = \frac{1}{2j} \cdot \left[ \frac{1 - \Gamma_S \cdot e^{2j\theta}}{1 + \Gamma_S \cdot e^{2j\theta}} - \frac{1 - \Gamma_S^* \cdot e^{-2j\theta}}{1 + \Gamma_S^* \cdot e^{-2j\theta}} \right] \qquad \Gamma_S = |\Gamma_S| \cdot e^{j\varphi}$$

$$\operatorname{Im}[y_S(\theta)] = \frac{1}{2j} \cdot \left[ \frac{(1 - |\Gamma_S| \cdot e^{j(\varphi+2\theta)}) \cdot (1 + |\Gamma_S| \cdot e^{-j(\varphi+2\theta)}) - (1 - |\Gamma_S| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 + |\Gamma_S| \cdot e^{j(\varphi+2\theta)})}{(1 + |\Gamma_S| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 + |\Gamma_S| \cdot e^{j(\varphi+2\theta)})} \right]$$

$$\operatorname{Im}[y_S(\theta)] = \frac{1}{2j} \cdot \left[ \frac{2 \cdot |\Gamma_S| \cdot e^{-j(\varphi+2\theta)} - 2 \cdot |\Gamma_S| \cdot e^{+j(\varphi+2\theta)}}{1 + |\Gamma_S|^2 + 2 \cdot |\Gamma_S| \cdot \cos(\varphi + 2\theta)} \right] = \frac{-2 \cdot |\Gamma_S| \cdot \sin(\varphi + 2\theta)}{1 + |\Gamma_S|^2 + 2 \cdot |\Gamma_S| \cdot \cos(\varphi + 2\theta)}$$

$$\cos(\varphi + 2\theta) = -|\Gamma_S| \Rightarrow \qquad \operatorname{Im}[y_S(\theta)] = \frac{-2 \cdot |\Gamma_S| \cdot \sin(\varphi + 2\theta)}{1 - |\Gamma_S|^2}$$

# A.S., $\Gamma$ , shunt stub, proof

- Equations for computing the shunt stub

$$\cos(\varphi + 2\theta) = -|\Gamma_S| \Rightarrow \sin(\varphi + 2\theta) = \pm \sqrt{1 - |\Gamma_S|^2}$$

$$\text{Im}[y_S(\theta)] = \frac{-2 \cdot |\Gamma_S| \cdot \sin(\varphi + 2\theta)}{1 - |\Gamma_S|^2} \Rightarrow \text{Im}[y_S(\theta)] = \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

- two cases

$$\varphi + 2\theta \in [0^\circ, 180^\circ] \Rightarrow \sin(\varphi + 2\theta) \geq 0 \quad \left\{ \begin{array}{l} \sin(\varphi + 2\theta) = \sqrt{1 - |\Gamma_S|^2} \\ \text{Im}[y_S(\theta)] = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} \end{array} \right.$$

$$\varphi + 2\theta \in (-180^\circ, 0^\circ) \Rightarrow \sin(\varphi + 2\theta) < 0 \quad \left\{ \begin{array}{l} \sin(\varphi + 2\theta) = -\sqrt{1 - |\Gamma_S|^2} \\ \text{Im}[y_S(\theta)] = \frac{2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} \end{array} \right.$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

# A.S., $\Gamma$ , shunt stub, proof

- We prefer (for microstrip) open circuited stub

$$Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$

- The normalized susceptance to be introduced to achieve the match
  - $Y(\theta)$  is the admittance seen **towards** the source,  $Z_0$  parallel with  $j \cdot B$

$$b = \text{Im} \left[ \frac{Y_{in,oc}}{Y_0} \right] = \text{Im} \left[ \frac{Z_0}{Z_{in,oc}} \right] = \tan \beta \cdot l = \text{Im}[y_S(\theta)]$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

# Analytical solution, $\Gamma$ , usage

$$(\varphi + 2\theta) = \begin{cases} +126.35^\circ \\ -126.35^\circ \end{cases} \quad \theta = \begin{cases} 39.7^\circ \\ 93.4^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -1.472 \\ +1.472 \end{cases} \quad \theta_{sp} = \begin{cases} -55.8^\circ + 180^\circ = 124.2^\circ \\ +55.8^\circ \end{cases}$$



- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

$$l_1 = \frac{39.7^\circ}{360^\circ} \cdot \lambda = 0.110 \cdot \lambda$$

$$l_2 = \frac{124.2^\circ}{360^\circ} \cdot \lambda = 0.345 \cdot \lambda$$

$$l_1 = \frac{93.4^\circ}{360^\circ} \cdot \lambda = 0.259 \cdot \lambda$$
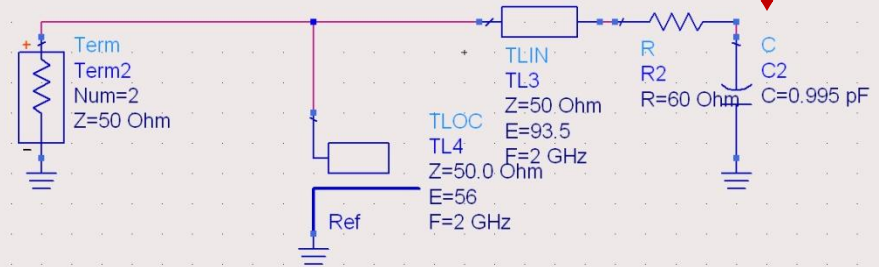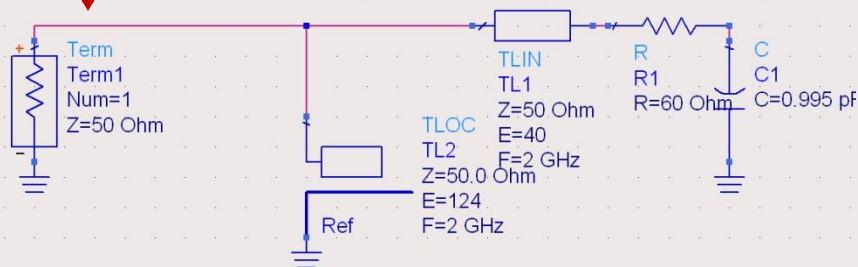
$$l_2 = \frac{55.8^\circ}{360^\circ} \cdot \lambda = 0.155 \cdot \lambda$$




# Series Stub

Sectiune de linie serie

---
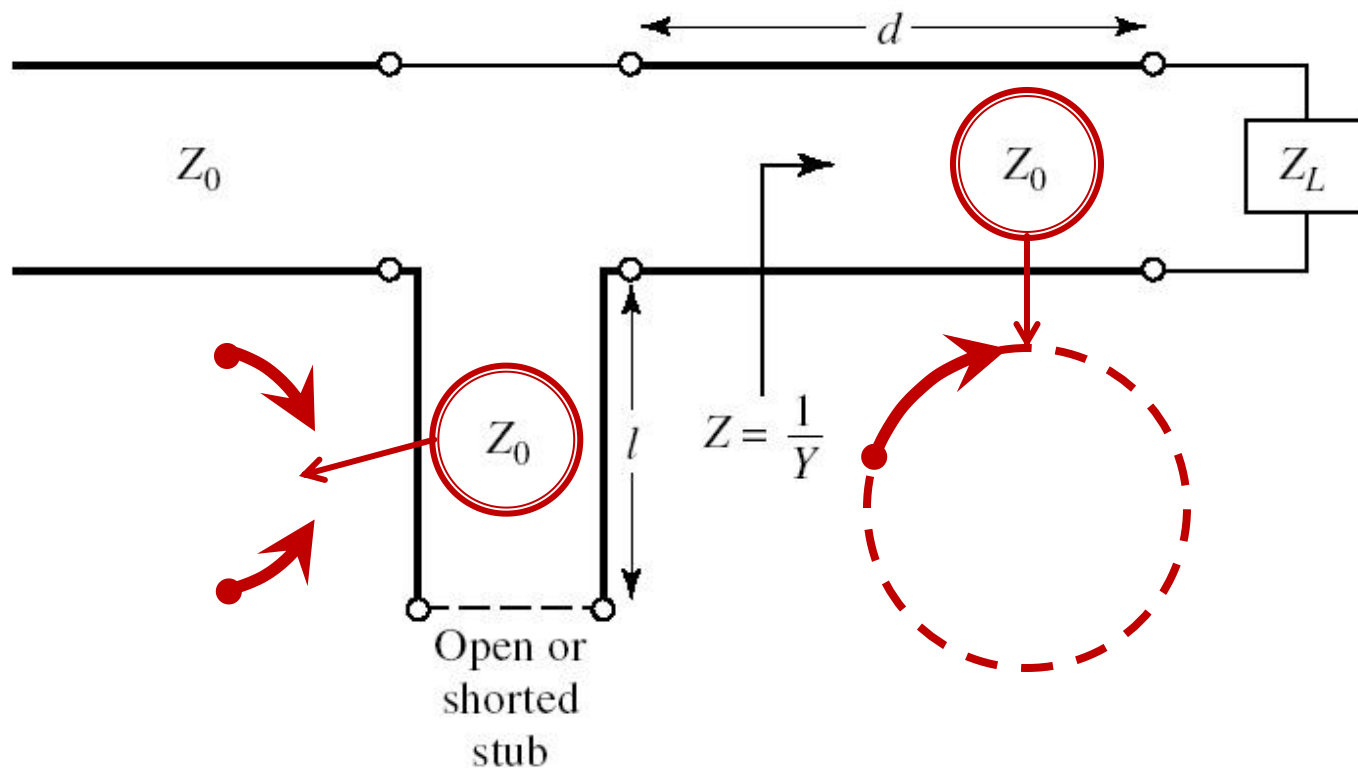
# Case 2, Series Stub

- Series Stub
- difficult to realize in single conductor line technologies (microstrip)



# Case 2, Series Stub




- We use a series transmission line to move the reflection coefficient **on the circle**  $r_L = 1$
- We compensate the remaining reactive part of the load with a series reactance to achieve match
- The series reactance is made with a stub which can be, as needed:
  - open-circuited
  - short-circuited

$$Z_{in} = Z_0 \cdot \frac{Z_L + j \cdot Z_0 \cdot \tan \beta \cdot l}{Z_0 + j \cdot Z_L \cdot \tan \beta \cdot l}$$

$$Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l$$

$$Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$
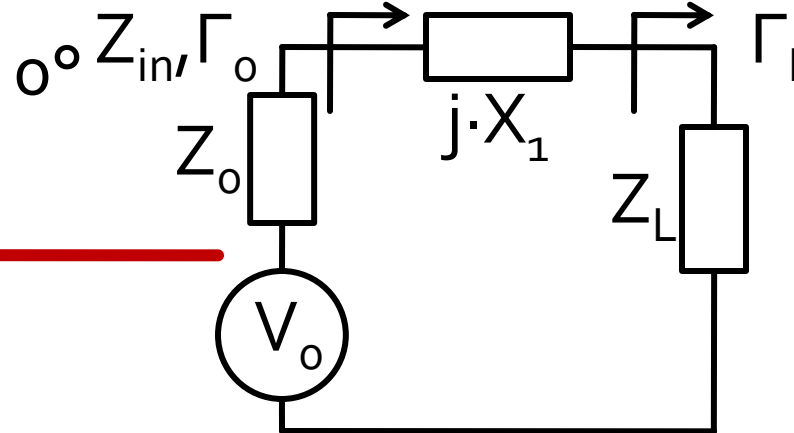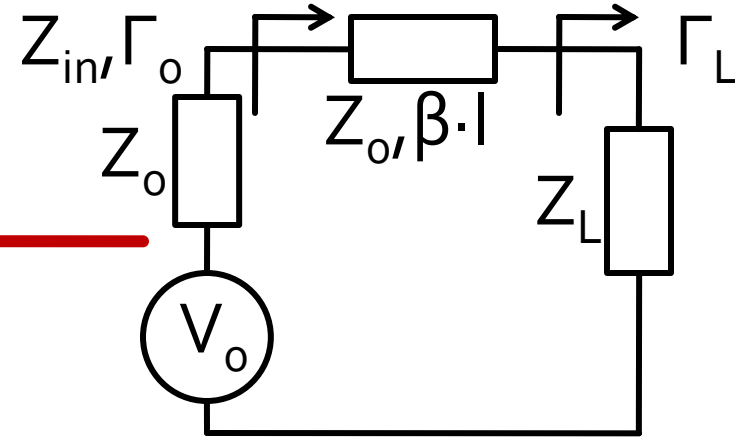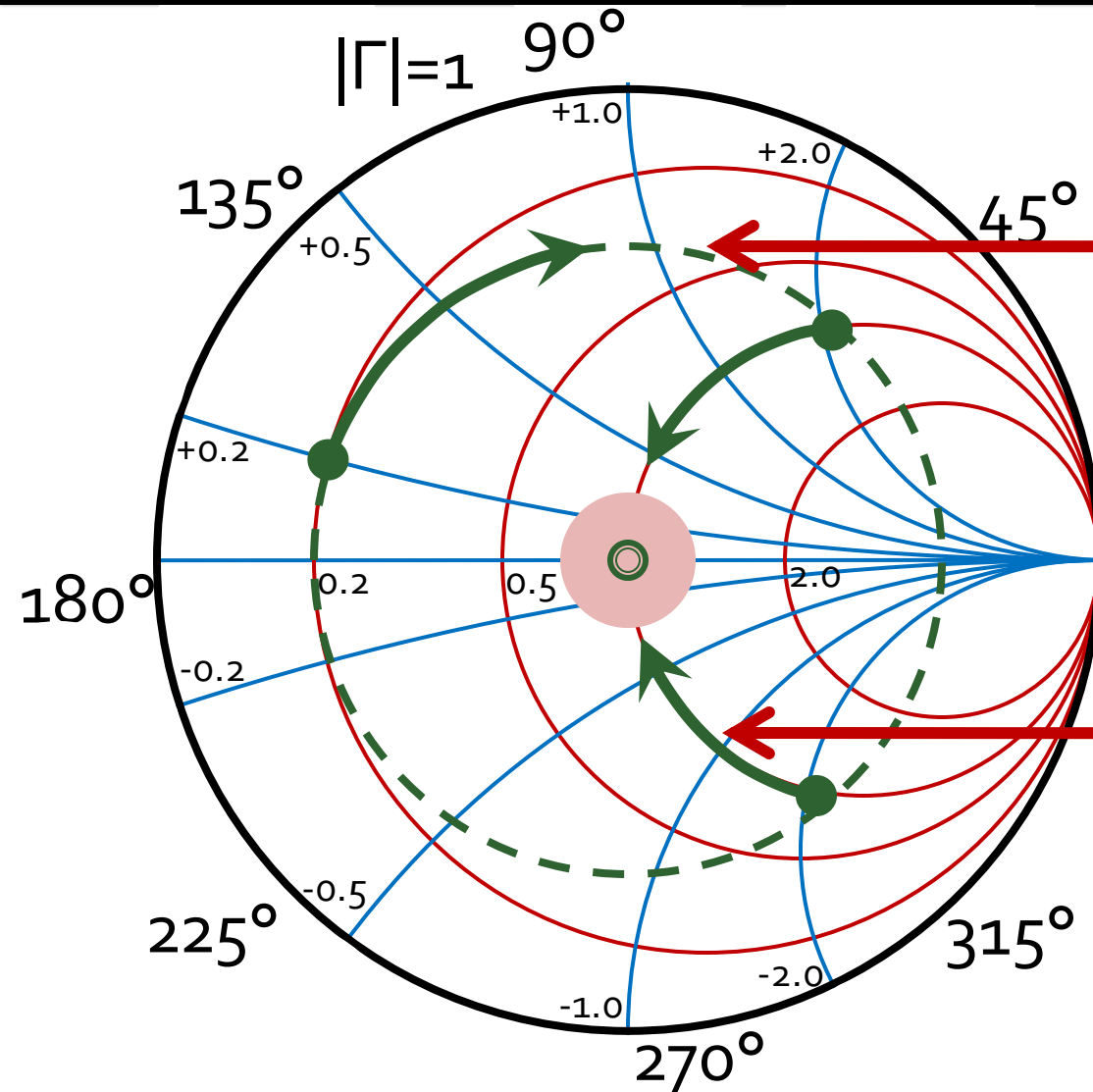
# Matching, series line + series reactance




$$|\Gamma_{in}| = |\Gamma_L|$$


$$r_{in} = 1$$

# Example, Series Stub, oc.

- load:  $100\ \Omega$  series with  $6.37\ \text{nH}$  at  $2\ \text{GHz}$
- two solutions possible

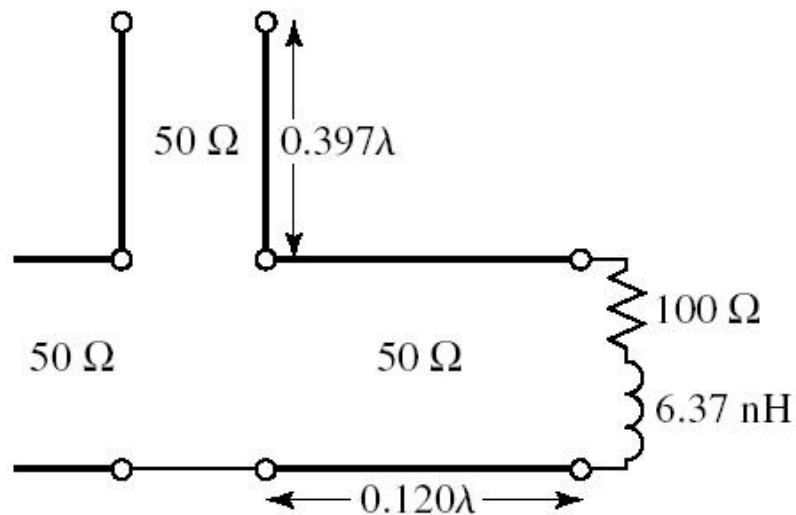


Solution 1

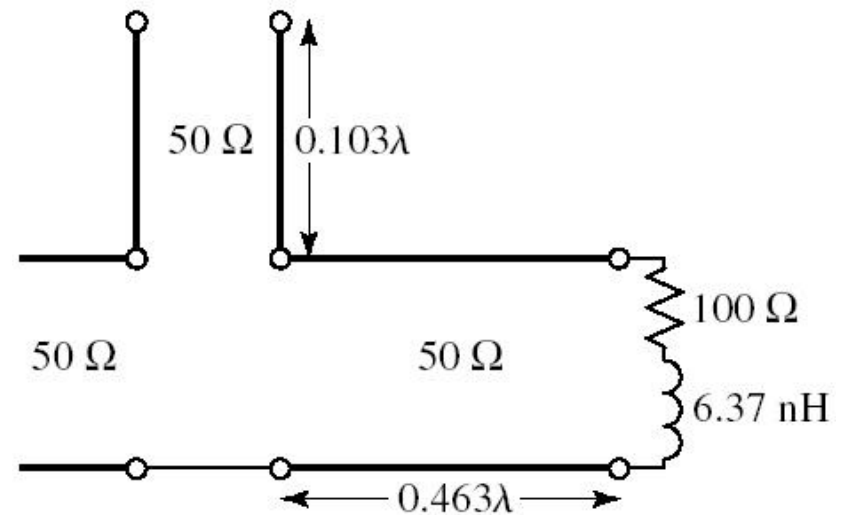


Solution 2


# Example, Series Stub, oc.

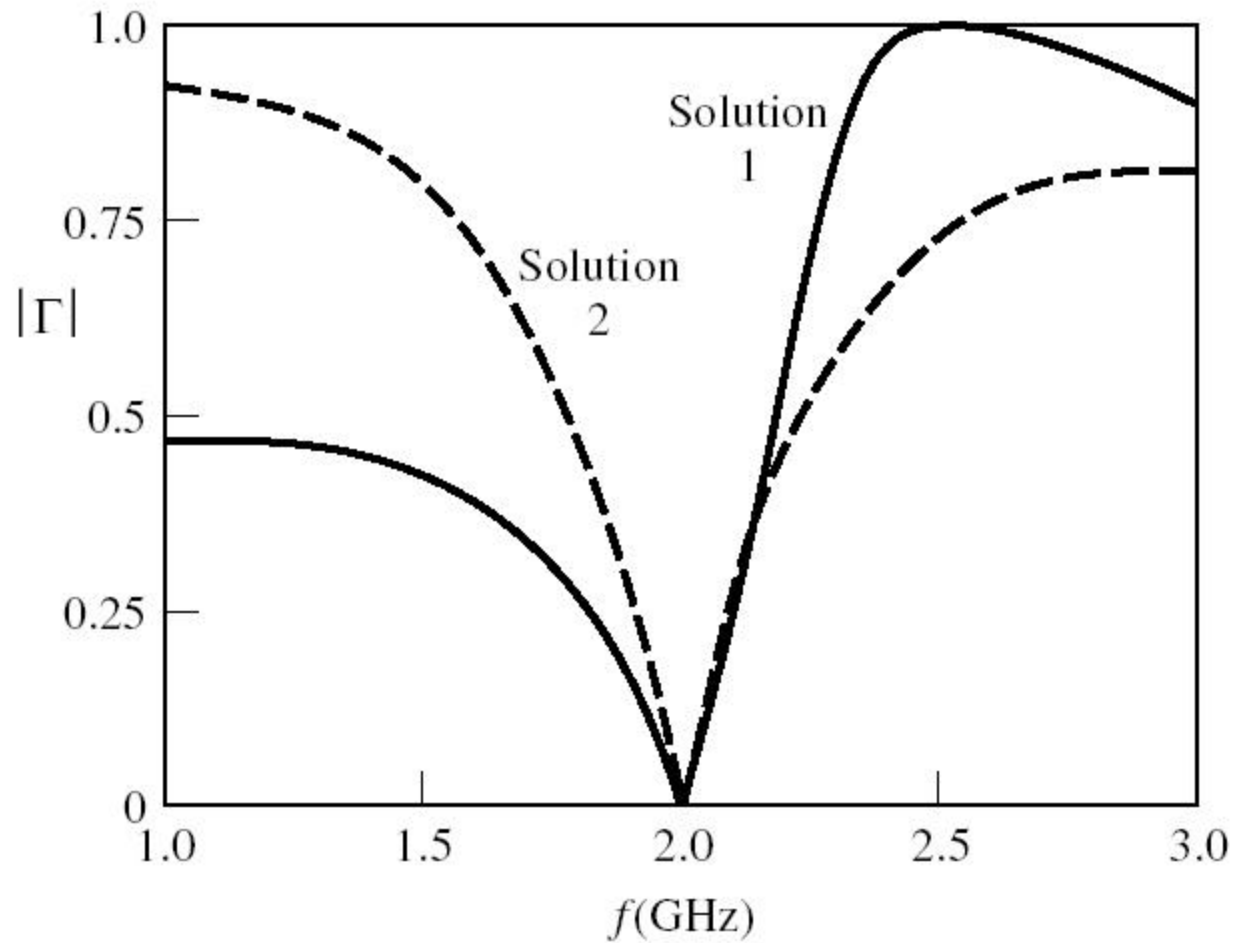

# Example, Series Stub, oc.

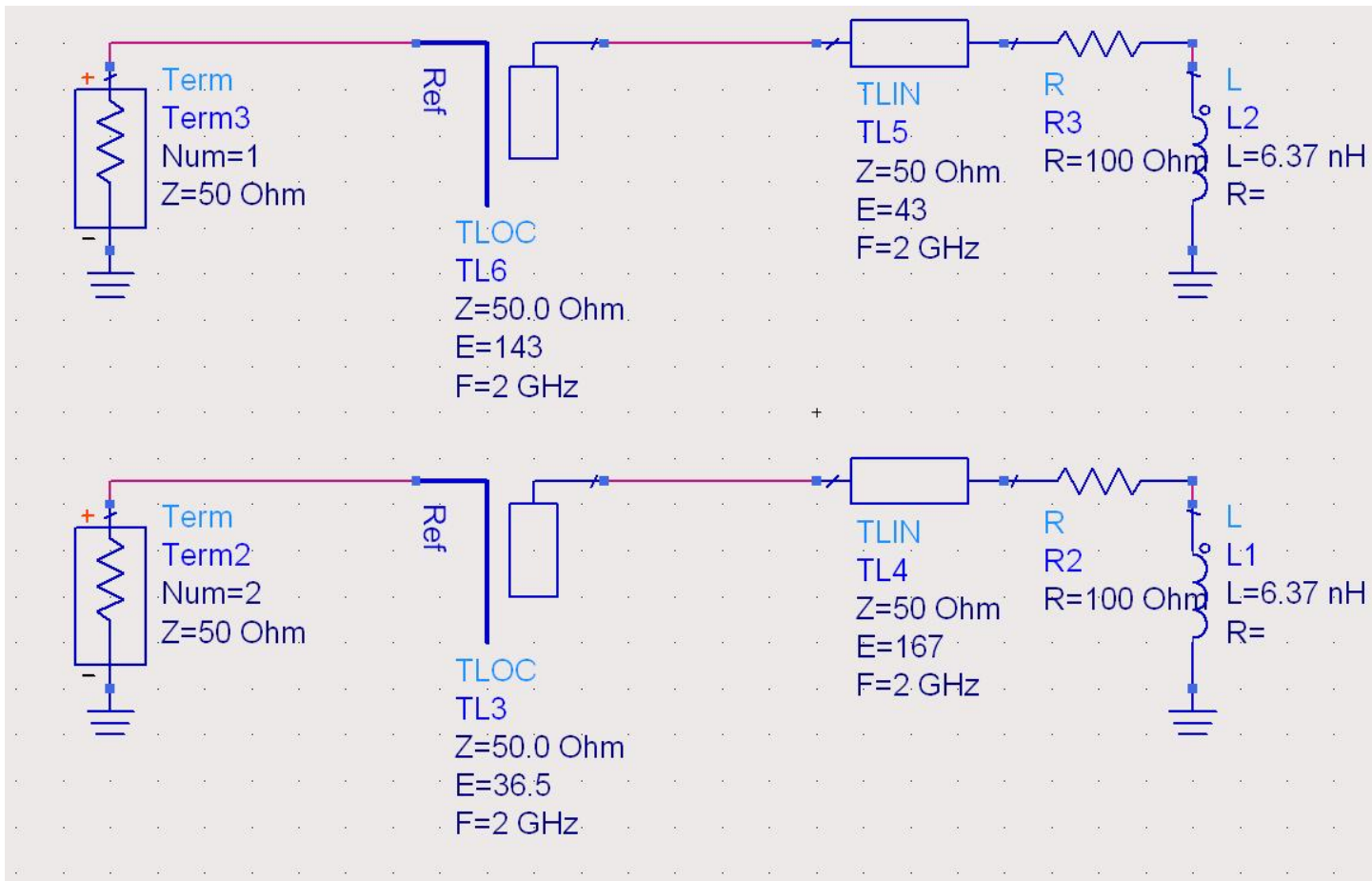


# Example, Series Stub, oc.

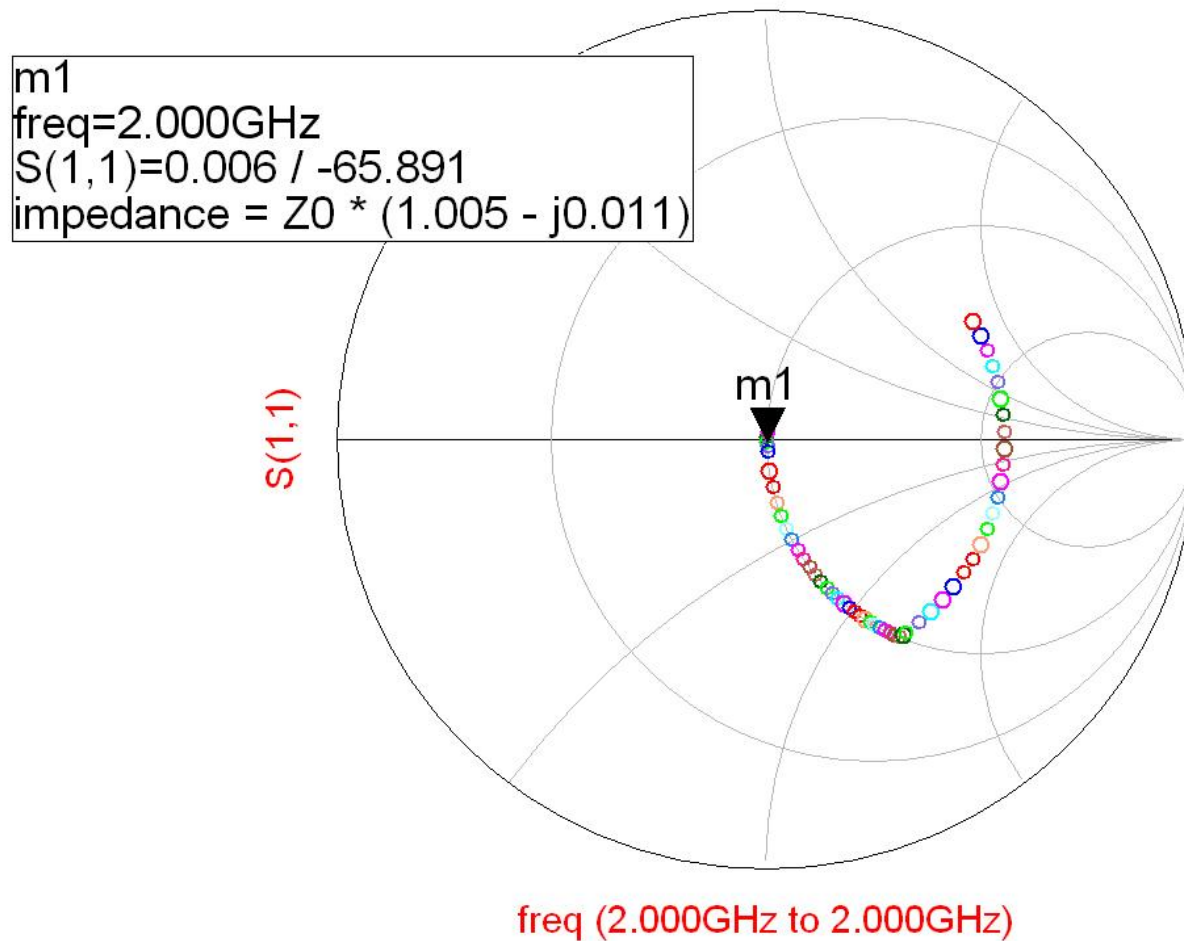

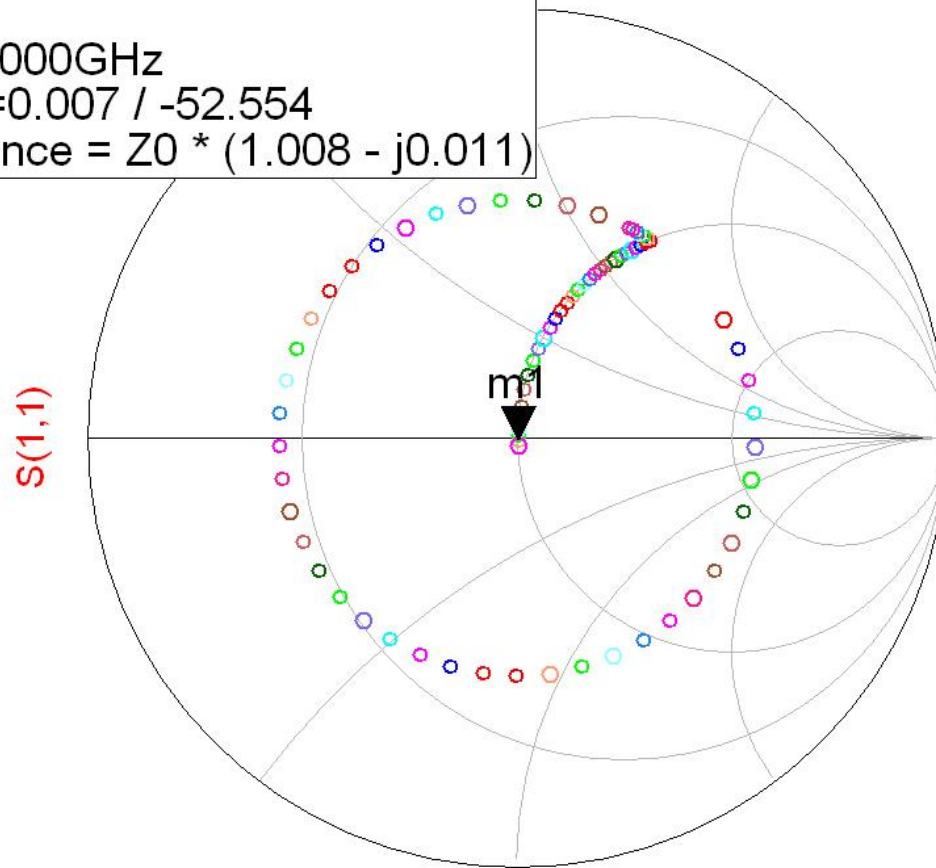
# Example, Series Stub, oc.

m1  
freq=2.000GHz  
 $S(1,1)=0.007 / -52.554$   
impedance =  $Z_0 * (1.008 - j0.011)$




freq (2.000GHz to 2.000GHz)

# Example, Series Stub, oc.

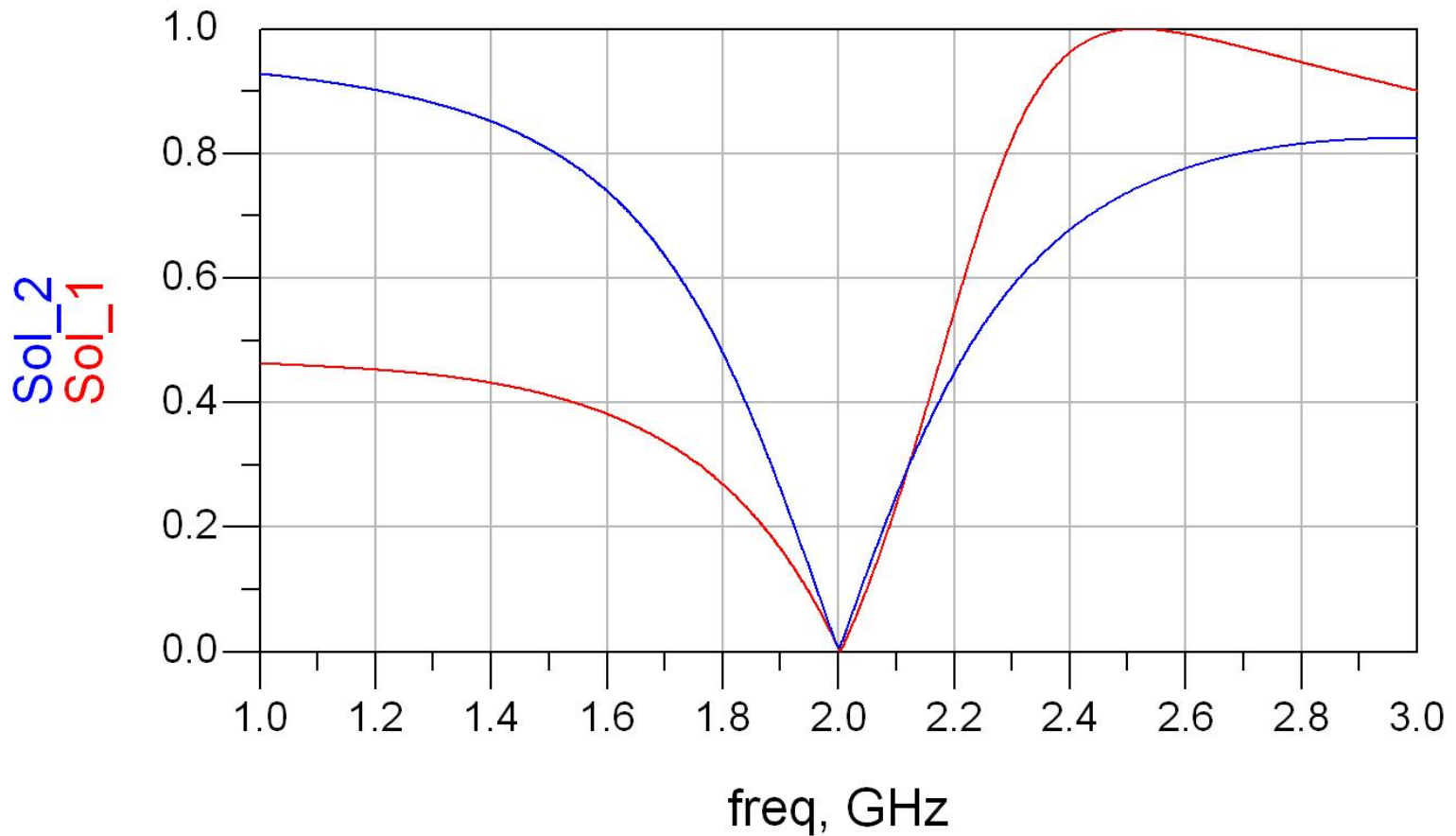

# Example, Series Stub, oc.

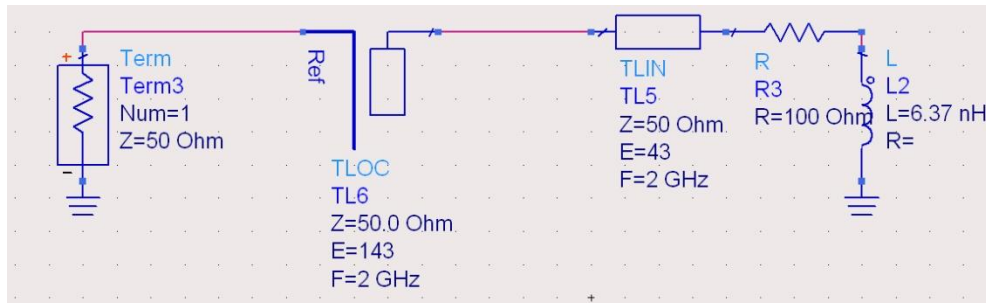


$$l_1 = \frac{43^\circ}{360^\circ} \cdot \lambda = 0.119 \cdot \lambda$$

$$l_2 = \frac{143^\circ}{360^\circ} \cdot \lambda = 0.397 \cdot \lambda$$

$$l_1 = \frac{167^\circ}{360^\circ} \cdot \lambda = 0.464 \cdot \lambda$$
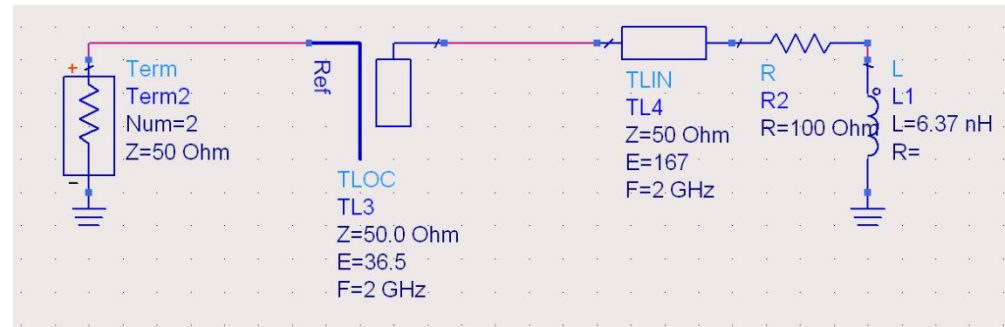
$$l_2 = \frac{36.5^\circ}{360^\circ} \cdot \lambda = 0.101 \cdot \lambda$$




# Analytical solution

Series Stub

---

# Analytical solution, impedances

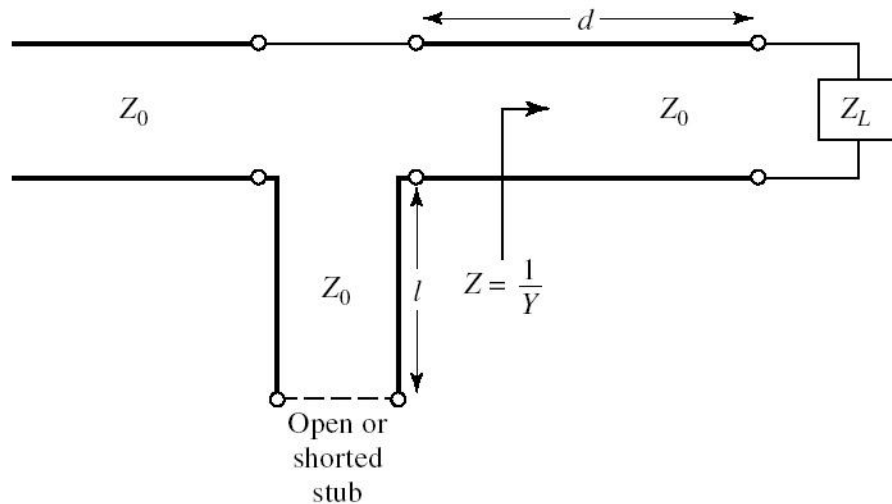

$$Y_L = \frac{1}{Z_L} = G_L + j \cdot B_L$$

$$Y = Y_0 \cdot \frac{(G_L + j \cdot B_L) + j \cdot Y_0 \cdot t}{Y_0 + j \cdot (G_L + j \cdot B_L) \cdot t}$$

$$\text{not } t = \tan \beta \cdot d \quad Z = R + j \cdot X = \frac{1}{Y}$$


$$R = \frac{G_L \cdot (1 + t^2)}{G_L^2 + (G_L + Y_0 \cdot t)^2}$$

$$X = \frac{G_L^2 \cdot t - (Y_0 - B_L \cdot t) \cdot (B_L + Y_0 \cdot t)}{Y_0 \cdot [G_L^2 + (B_L + Y_0 \cdot t)^2]}$$

- $d$  (which implies  $t$ ) is chosen so that:  $R = Z_0 = \frac{1}{Y_0}$

$$Y_0 \cdot (G_L - Y_0) \cdot t^2 - 2 \cdot B_L \cdot Y_0 \cdot t + (G_L \cdot Y_0 - G_L^2 - B_L^2) = 0$$

# Analytical solution

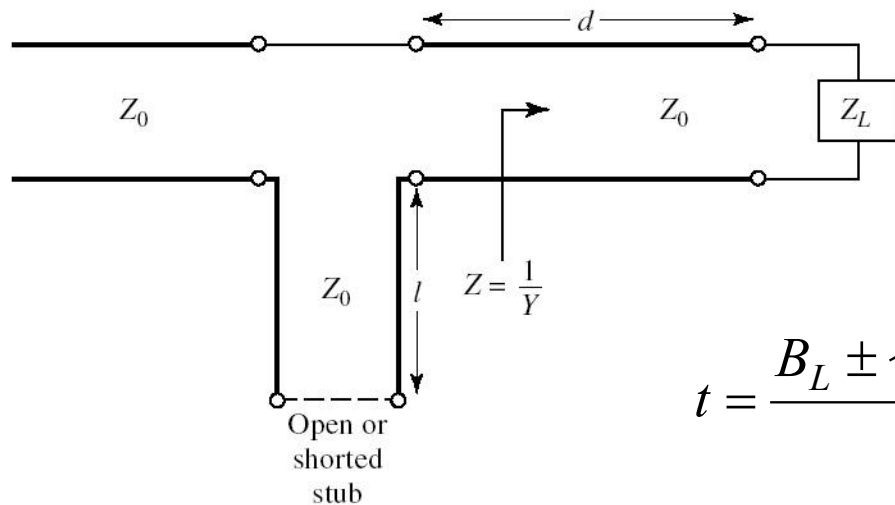


$$t = \frac{-B_L}{2 \cdot Y_0}, \quad G_L = Y_0$$

$$t = \frac{B_L \pm \sqrt{G_L \cdot [(Y_0 - G_L)^2 + B_L^2]} / Y_0}{G_L - Y_0} \quad G_L \neq Y_0$$

- second grade equation, 2 solutions possible
- $d$  computed from  $t$

$$\frac{d}{\lambda} = \begin{cases} \frac{1}{2\pi} \cdot \arctan t & t \geq 0 \\ \frac{1}{2\pi} \cdot (\pi + \arctan t) & t < 0 \end{cases}$$

# Analytical solution

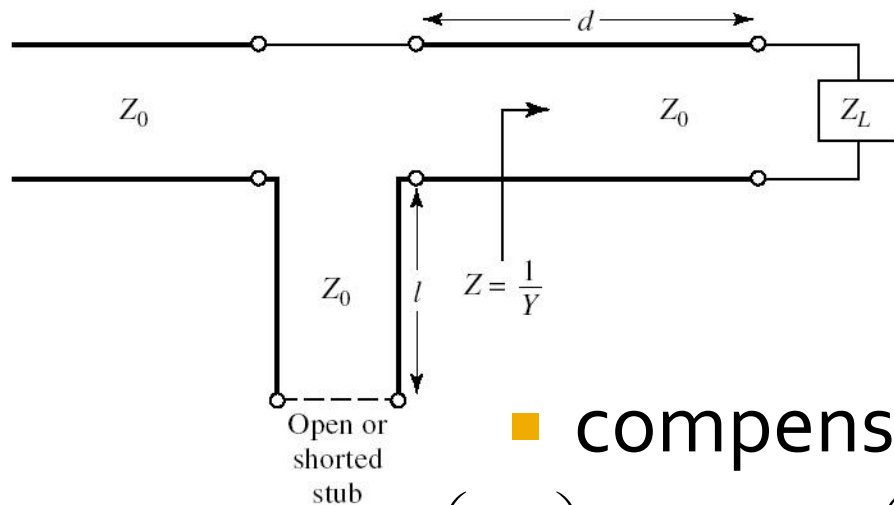

$$X_S = -X$$

$$X = \frac{G_L^2 \cdot t - (Y_0 - B_L \cdot t) \cdot (B_L + Y_0 \cdot t)}{Y_0 \cdot [G_L^2 + (B_L + Y_0 \cdot t)^2]}$$

- compensating reactance is:


$$\frac{l_{sc}}{\lambda} = \frac{1}{2\pi} \cdot \arctan\left(\frac{X_S}{Z_0}\right) = \frac{-1}{2\pi} \cdot \arctan\left(\frac{X}{Z_0}\right)$$

$$\frac{l_{oc}}{\lambda} = \frac{-1}{2\pi} \cdot \arctan\left(\frac{Z_0}{X_S}\right) = \frac{1}{2\pi} \cdot \arctan\left(\frac{Z_0}{X}\right)$$

- for **negative lengths** we add  $\lambda/2$

# Analytical solution, reflection coefficient

- load:  $100\ \Omega$  series with  $6.37\ \text{nH}$  at  $2\ \text{GHz}$

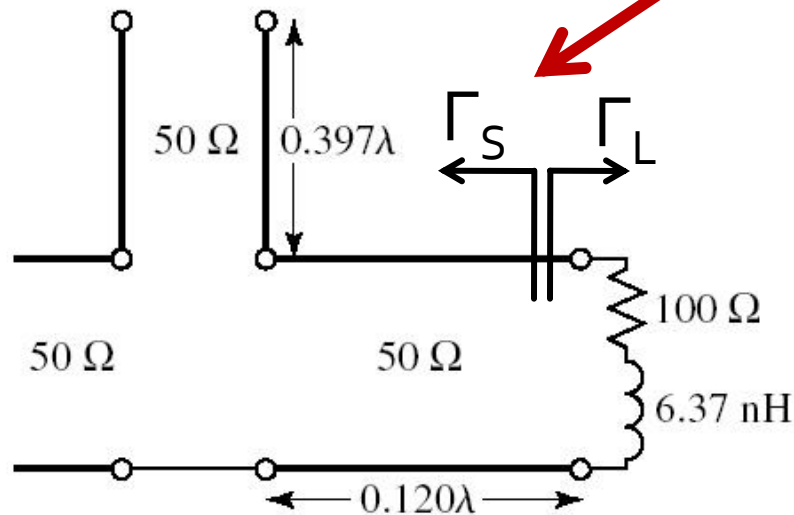

Solution 1

$$Z_L = R_L + \frac{1}{j \cdot \omega \cdot C_L} = 100\ \Omega + j \cdot 80.05\ \Omega$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 0.481 + j \cdot 0.277$$

$$z_L = \frac{Z_L}{Z_0} = 2 + j \cdot 1.6$$

- matching requires obtaining conjugate value for  $\Gamma$

$$\Gamma_S = \Gamma_L^* = 0.481 - j \cdot 0.277$$


$$\Gamma_S = 0.555 \angle -29.92^\circ$$

$$|\Gamma_S| = 0.555; \quad \varphi = -29.92^\circ$$
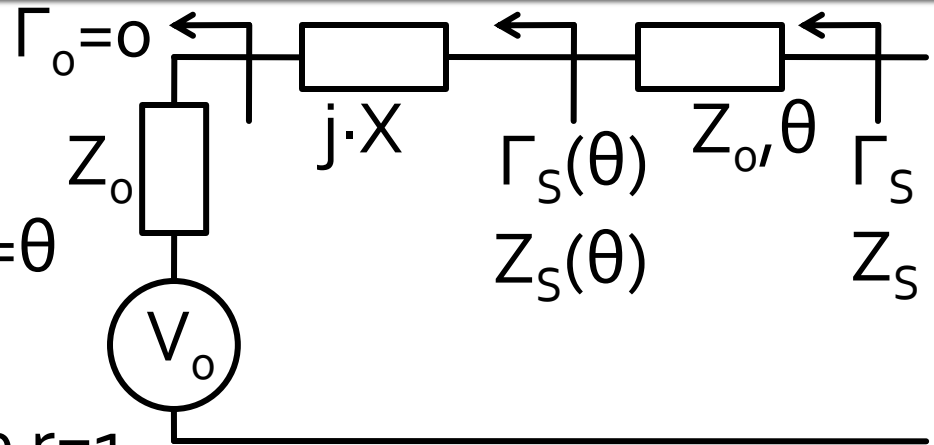
# Analytical solution, $\Gamma$

- series line

- electrical length  $E = \beta \cdot l = \theta$
- moves the reflection coefficient on the circle  $r=1$



- series stub

- electrical length  $E = \beta \cdot l_{ss} = \theta_{ss}$
- moves the reflection coefficient to the center of the Smith Chart ( $\Gamma_0 = 0$ )

$$z_S = \frac{Z_S}{Z_0} = \frac{Z_S}{50\Omega}$$

$$z_S = \frac{1 + \Gamma_S}{1 - \Gamma_S} = 2 - j \cdot 1.6$$

$$\Gamma_S(\theta) = \Gamma_S \cdot e^{2j\theta}$$

$$z_S(\theta) = \frac{1 + \Gamma_S(\theta)}{1 - \Gamma_S(\theta)} = \frac{1 + \Gamma_S \cdot e^{2j\theta}}{1 - \Gamma_S \cdot e^{2j\theta}}$$

# A.S., $\Gamma$ , series line, proof

- After the series line with electrical length  $\theta$ :

$$\operatorname{Re}[z_S(\theta)] = 1 \qquad \operatorname{Im}[z_S(\theta)] = X$$

$$\operatorname{Re}[z_S(\theta)] = \frac{1}{2} \cdot [z_S(\theta) + z_S^*(\theta)] \qquad \operatorname{Im}[z_S(\theta)] = \frac{1}{2j} \cdot [z_S(\theta) - z_S^*(\theta)]$$

$$\operatorname{Re}[z_S(\theta)] = \frac{1}{2} \cdot \left[ \frac{1 + \Gamma_S \cdot e^{2j\theta}}{1 - \Gamma_S \cdot e^{2j\theta}} + \frac{1 + \Gamma_S^* \cdot e^{-2j\theta}}{1 - \Gamma_S^* \cdot e^{-2j\theta}} \right] \qquad \Gamma_S = |\Gamma_S| \cdot e^{j\varphi}$$

$$\operatorname{Re}[z_S(\theta)] = \frac{1}{2} \cdot \left[ \frac{(1 + |\Gamma_S| \cdot e^{j(\varphi+2\theta)}) \cdot (1 - |\Gamma_S| \cdot e^{-j(\varphi+2\theta)}) + (1 + |\Gamma_S| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 - |\Gamma_S| \cdot e^{j(\varphi+2\theta)})}{(1 - |\Gamma_S| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 - |\Gamma_S| \cdot e^{j(\varphi+2\theta)})} \right]$$

$$\operatorname{Re}[z_S(\theta)] = \frac{1}{2} \cdot \left[ \frac{2 - 2 \cdot |\Gamma_S|^2}{1 + |\Gamma_S|^2 - 2 \cdot |\Gamma_S| \cdot \cos(\varphi + 2\theta)} \right] = 1 \quad \Rightarrow \quad \boxed{\cos(\varphi + 2\theta) = |\Gamma_S|}$$

# A.S., $\Gamma$ , series line. usage

- Equations for computing the series line  $\theta$ :

$$\operatorname{Re}[z_S(\theta)] = 1 \Rightarrow \boxed{\cos(\varphi + 2\theta) = |\Gamma_S|}$$

$$\Gamma_S = |\Gamma_S| \cdot e^{j\varphi} \quad \Gamma_S = 0.555 \angle -29.92^\circ \quad |\Gamma_S| = 0.555; \quad \varphi = -29.92^\circ$$

- two solutions possible, in the  $0 \div 180^\circ$  range (add  $\lambda/2 \Leftrightarrow 180^\circ$  as needed)

$$\theta = \frac{1}{2} \cdot [\pm \cos^{-1}(|\Gamma_S|) - \varphi + k \cdot 360^\circ] = \frac{1}{2} \cdot [\pm \cos^{-1}(|\Gamma_S|) - \varphi] + k \cdot 180^\circ$$

$$\forall k \in \mathbb{N}$$

$$\cos(\varphi + 2\theta) = 0.555 \Rightarrow (\varphi + 2\theta) = \pm 56.28^\circ$$

$$(-29.92^\circ + 2\theta) = \begin{cases} +56.28^\circ \\ -56.28^\circ \end{cases}$$

$$\theta = \begin{cases} +43.1^\circ \\ -13.2^\circ + 180^\circ = +166.8^\circ \end{cases}$$

# A.S., $\Gamma$ , series stub, proof

- Equations for computing the series stub  $\theta_{ss}$ :

$$\operatorname{Re}[z_s(\theta)] = 1 \qquad \cos(\varphi + 2\theta) = |\Gamma_s|$$

$$\operatorname{Im}[z_s(\theta)] = \frac{1}{2j} \cdot \left[ \frac{1 + \Gamma_s \cdot e^{2j\theta}}{1 - \Gamma_s \cdot e^{2j\theta}} - \frac{1 + \Gamma_s^* \cdot e^{-2j\theta}}{1 - \Gamma_s^* \cdot e^{-2j\theta}} \right] \qquad \Gamma_s = |\Gamma_s| \cdot e^{j\varphi}$$

$$\operatorname{Im}[z_s(\theta)] = \frac{1}{2j} \cdot \left[ \frac{(1 + |\Gamma_s| \cdot e^{j(\varphi+2\theta)}) \cdot (1 - |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) - (1 + |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 - |\Gamma_s| \cdot e^{j(\varphi+2\theta)})}{(1 - |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}) \cdot (1 - |\Gamma_s| \cdot e^{j(\varphi+2\theta)})} \right]$$

$$\operatorname{Im}[z_s(\theta)] = \frac{1}{2j} \cdot \left[ \frac{2 \cdot |\Gamma_s| \cdot e^{+j(\varphi+2\theta)} - 2 \cdot |\Gamma_s| \cdot e^{-j(\varphi+2\theta)}}{1 + |\Gamma_s|^2 - 2 \cdot |\Gamma_s| \cdot \cos(\varphi + 2\theta)} \right] = \frac{2 \cdot |\Gamma_s| \cdot \sin(\varphi + 2\theta)}{1 + |\Gamma_s|^2 - 2 \cdot |\Gamma_s| \cdot \cos(\varphi + 2\theta)}$$

$$\cos(\varphi + 2\theta) = |\Gamma_s| \Rightarrow \operatorname{Im}[z_s(\theta)] = \frac{2 \cdot |\Gamma_s| \cdot \sin(\varphi + 2\theta)}{1 - |\Gamma_s|^2}$$

# A.S., $\Gamma$ , series stub, proof

- Equations for computing the series stub  $\theta_{ss}$ :

$$\cos(\varphi + 2\theta) = |\Gamma_s| \Rightarrow \sin(\varphi + 2\theta) = \pm \sqrt{1 - |\Gamma_s|^2}$$

$$\text{Im}[z_s(\theta)] = \frac{2 \cdot |\Gamma_s| \cdot \sin(\varphi + 2\theta)}{1 - |\Gamma_s|^2} \Rightarrow \text{Im}[z_s(\theta)] = \frac{\pm 2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}}$$

- two cases:

$$\varphi + 2\theta \in [0^\circ, 180^\circ] \Rightarrow \sin(\varphi + 2\theta) \geq 0 \quad \left\{ \begin{array}{l} \sin(\varphi + 2\theta) = \sqrt{1 - |\Gamma_s|^2} \\ \text{Im}[z_s(\theta)] = \frac{2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} \end{array} \right.$$

$$\varphi + 2\theta \in (-180^\circ, 0^\circ) \Rightarrow \sin(\varphi + 2\theta) < 0 \quad \left\{ \begin{array}{l} \sin(\varphi + 2\theta) = -\sqrt{1 - |\Gamma_s|^2} \\ \text{Im}[z_s(\theta)] = \frac{-2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}} \end{array} \right.$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

# A.S., $\Gamma$ , series stub, proof

- We prefer (for microstrip) open circuited stub

$$Z_{in,oc} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$

- The normalized reactance to be introduced to achieve the match
  - $Z(\theta)$  is the impedance seen **towards** the source,  $Z_0$  series with  $j \cdot X$

$$x = \text{Im} \left[ \frac{Z_{in,oc}}{Z_0} \right] = -\cot \beta \cdot l = \text{Im}[z_s(\theta)]$$

$$\theta_{ss} = \beta \cdot l = \cot^{-1} \frac{\mp 2 \cdot |\Gamma_s|}{\sqrt{1 - |\Gamma_s|^2}}$$

# Analytical solution, $\Gamma$ , usage

$$(\varphi + 2\theta) = \begin{cases} +56.28^\circ \\ -56.28^\circ \end{cases} \quad \theta = \begin{cases} 43.1^\circ \\ 166.8^\circ \end{cases} \quad \text{Im}[z_s(\theta)] = \begin{cases} +1.335 \\ -1.335 \end{cases} \quad \theta_{ss} = \begin{cases} -36.8^\circ + 180^\circ = 143.2^\circ \\ +36.8^\circ \end{cases}$$

- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

$$l_1 = \frac{43.1^\circ}{360^\circ} \cdot \lambda = 0.120 \cdot \lambda$$

$$l_2 = \frac{143.2^\circ}{360^\circ} \cdot \lambda = 0.398 \cdot \lambda$$

$$l_1 = \frac{166.8^\circ}{360^\circ} \cdot \lambda = 0.463 \cdot \lambda$$

$$l_2 = \frac{36.8^\circ}{360^\circ} \cdot \lambda = 0.102 \cdot \lambda$$






# Single stub tuning

- We choose one of the 8 possible solutions (series/shunt, oc./sc.), taking into account:
  - physical dimensions (area occupied on chip/board)
  - sensitivity of the match on length error ( $\Delta\Gamma/\Delta E$ ,  $\Delta\Gamma/\Delta l$ )
  - convenient frequency behavior (bandwidth)
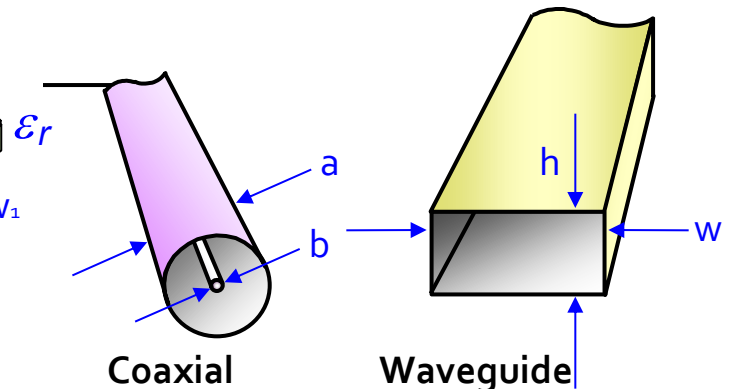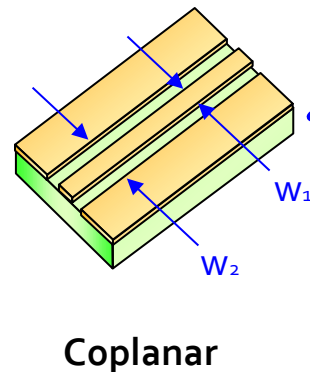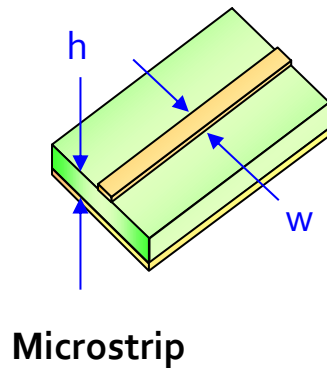
# Single stub tuning

- We choose one of the 8 possible solutions (series/shunt, oc./sc.), taking into account :
  - physical realizability (in the line technology we use)



- Main disadvantage:
  - requires a **variable length of line** between the load and the stub


# Analytical solutions

Exam / Project


---

# Case 1, Shunt Stub

- Shunt Stub

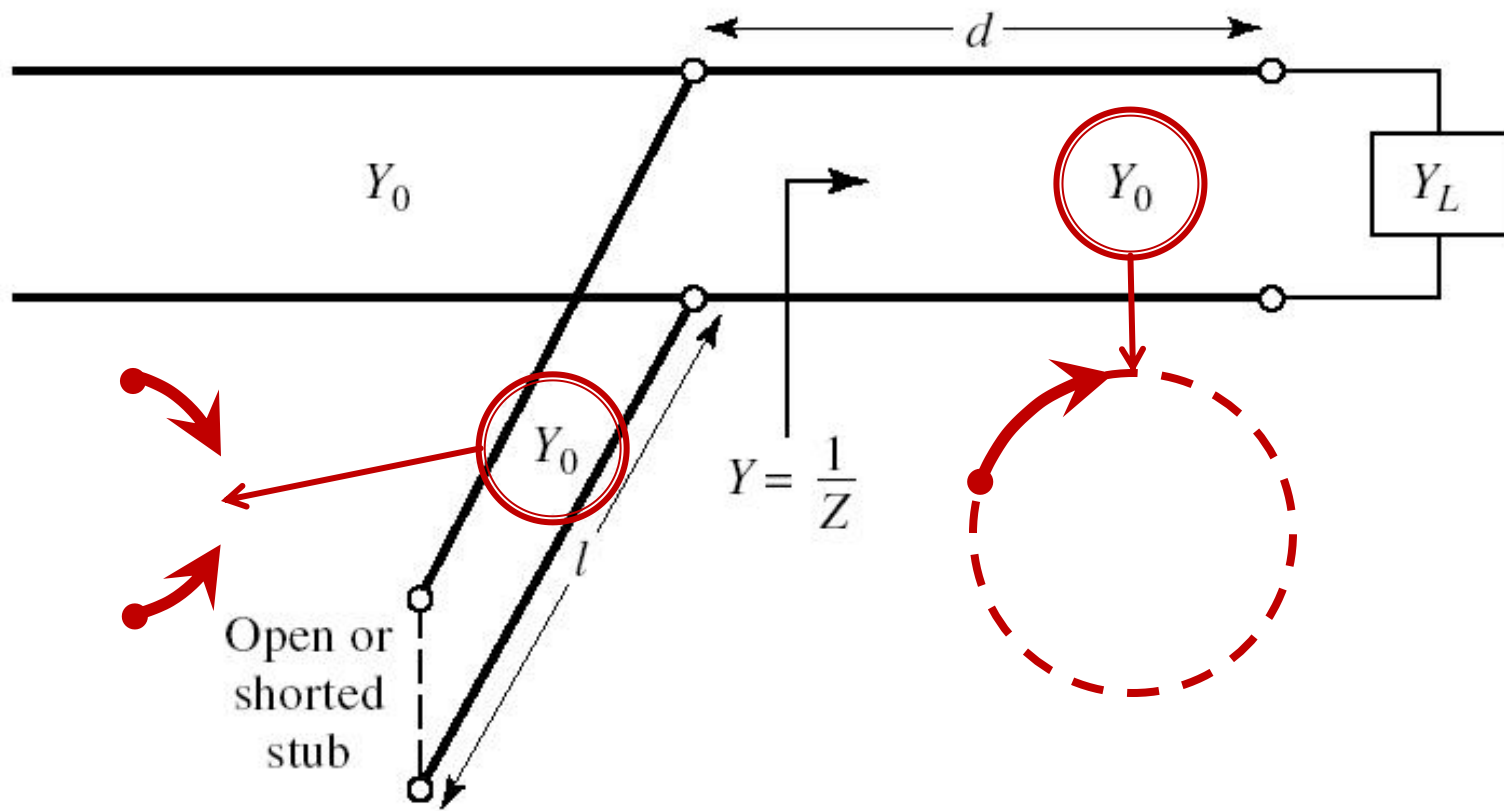
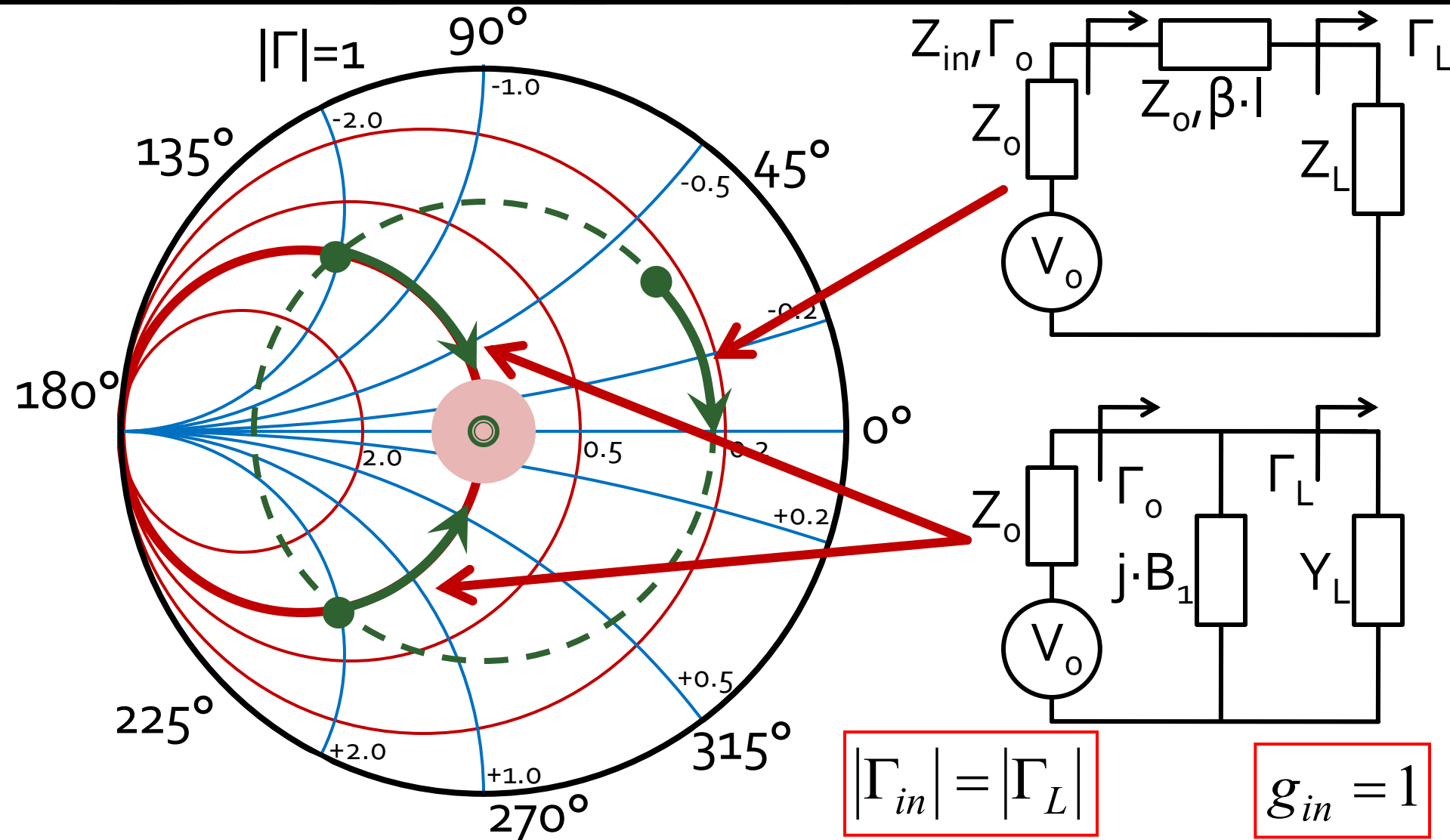
# Matching, series line + shunt susceptance



# Analytical solution, usage

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = 0.593 \angle 46.85^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ \quad \cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **“+” solution** ↓

$$(46.85^\circ + 2\theta) = +126.35^\circ \quad \theta = +39.7^\circ \quad \text{Im } y_S = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.472$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_S) = -55.8^\circ (+180^\circ) \rightarrow \theta_{sp} = 124.2^\circ$$

- **“-” solution** ↓

$$(46.85^\circ + 2\theta) = -126.35^\circ \quad \theta = -86.6^\circ (+180^\circ) \rightarrow \theta = 93.4^\circ$$

$$\text{Im } y_S = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +1.472 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_S) = 55.8^\circ$$

# Analytical solution, usage

$$(\varphi + 2\theta) = \begin{cases} +126.35^\circ \\ -126.35^\circ \end{cases} \quad \theta = \begin{cases} 39.7^\circ \\ 93.4^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -1.472 \\ +1.472 \end{cases} \quad \theta_{sp} = \begin{cases} -55.8^\circ + 180^\circ = 124.2^\circ \\ +55.8^\circ \end{cases}$$



- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

$$l_1 = \frac{39.7^\circ}{360^\circ} \cdot \lambda = 0.110 \cdot \lambda$$

$$l_2 = \frac{124.2^\circ}{360^\circ} \cdot \lambda = 0.345 \cdot \lambda$$


$$l_1 = \frac{93.4^\circ}{360^\circ} \cdot \lambda = 0.259 \cdot \lambda$$
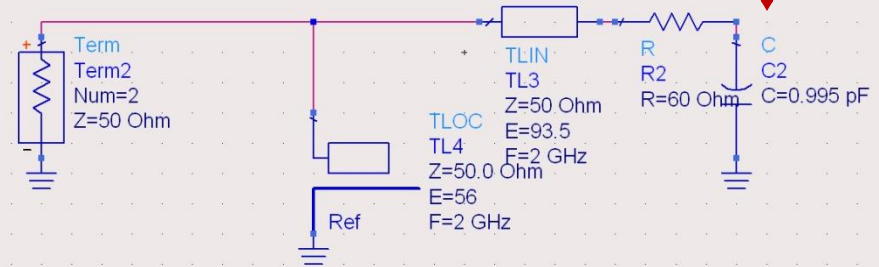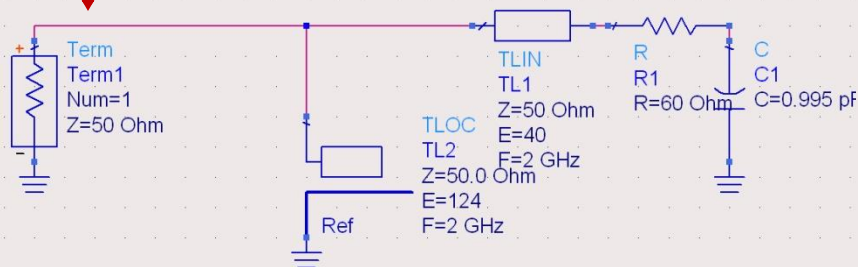
$$l_2 = \frac{55.8^\circ}{360^\circ} \cdot \lambda = 0.155 \cdot \lambda$$





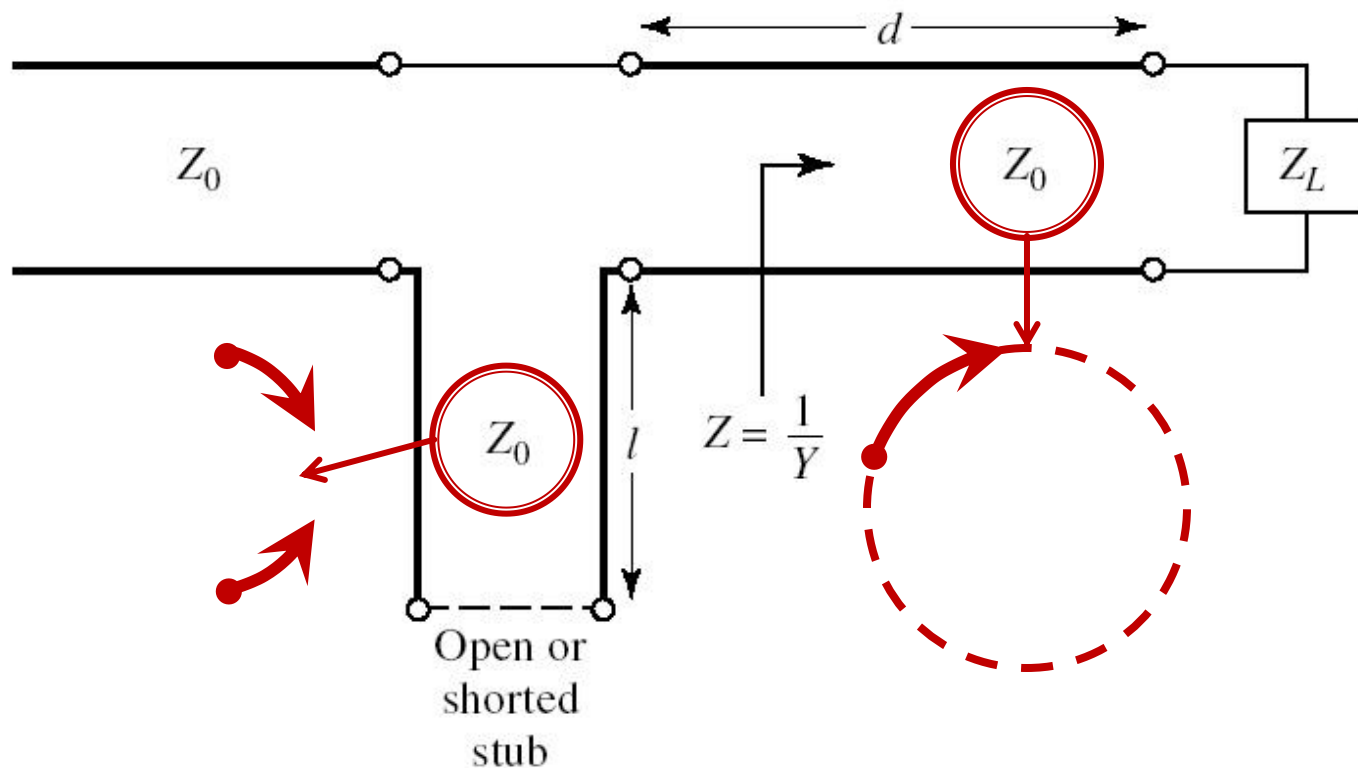
# Case 2, Series Stub

- Series Stub
- difficult to realize in single conductor line technologies (microstrip)


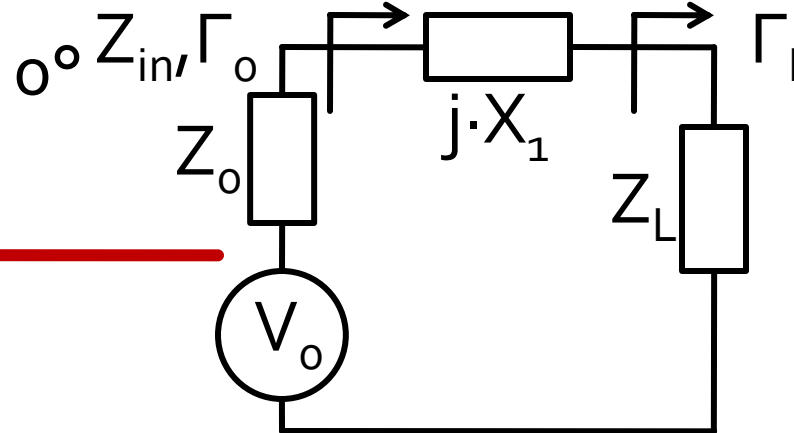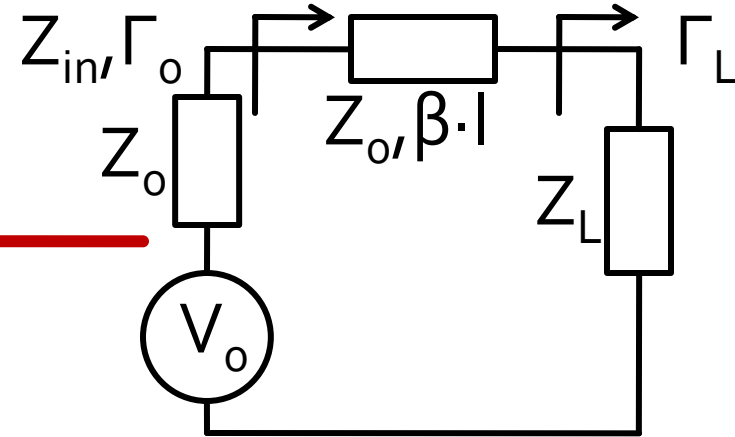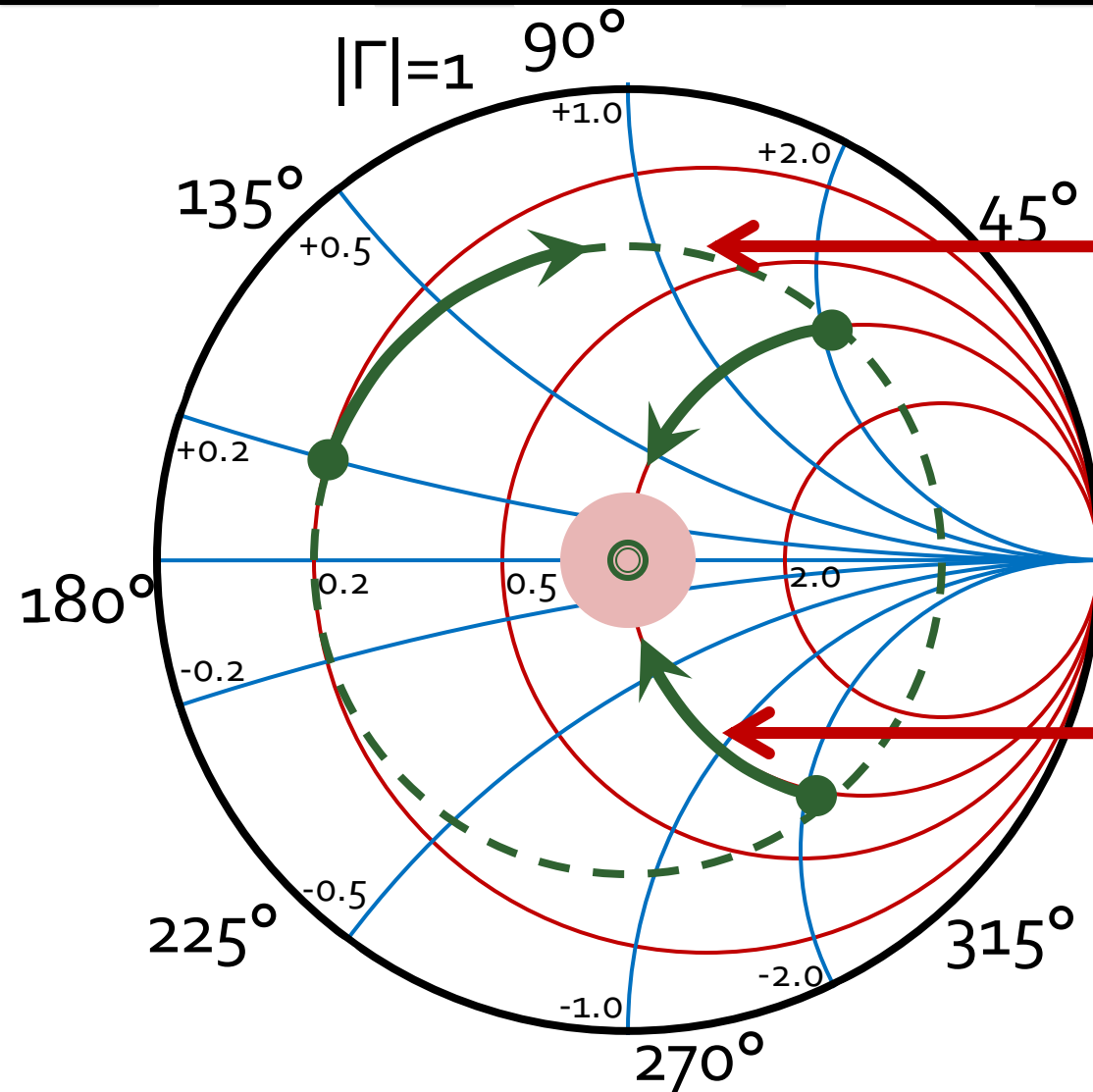
# Matching, series line + series reactance



$$|\Gamma_{in}| = |\Gamma_L|$$

$$r_{in} = 1$$

# Analytical solution, usage

$$\cos(\varphi + 2\theta) = |\Gamma_S|$$

$$\theta_{ss} = \beta \cdot l = \cot^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$\Gamma_S = 0.555 \angle -29.92^\circ$$

$$|\Gamma_S| = 0.555; \quad \varphi = -29.92^\circ \quad \cos(\varphi + 2\theta) = 0.555 \Rightarrow (\varphi + 2\theta) = \pm 56.28^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

- **“+” solution** ↓

$$(-29.92^\circ + 2\theta) = +56.28^\circ \quad \theta = 43.1^\circ \quad \text{Im } z_S = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +1.335$$

$$\theta_{ss} = -\cot^{-1}(\text{Im } z_S) = -36.8^\circ (+180^\circ) \rightarrow \theta_{ss} = 143.2^\circ$$

- **“-” solution** ↓

$$(-29.92^\circ + 2\theta) = -56.28^\circ \quad \theta = -13.2^\circ (+180^\circ) \rightarrow \theta = 166.8^\circ$$

$$\text{Im } z_S = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.335 \quad \theta_{ss} = -\cot^{-1}(\text{Im } z_S) = 36.8^\circ$$

# Analytical solution, usage

$$(\varphi + 2\theta) = \begin{cases} +56.28^\circ \\ -56.28^\circ \end{cases} \quad \theta = \begin{cases} 43.1^\circ \\ 166.8^\circ \end{cases} \quad \text{Im}[z_s(\theta)] = \begin{cases} +1.335 \\ -1.335 \end{cases} \quad \theta_{ss} = \begin{cases} -36.8^\circ + 180^\circ = 143.2^\circ \\ +36.8^\circ \end{cases}$$


- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

$$l_1 = \frac{43.1^\circ}{360^\circ} \cdot \lambda = 0.120 \cdot \lambda$$

$$l_2 = \frac{143.2^\circ}{360^\circ} \cdot \lambda = 0.398 \cdot \lambda$$

$$l_1 = \frac{166.8^\circ}{360^\circ} \cdot \lambda = 0.463 \cdot \lambda$$
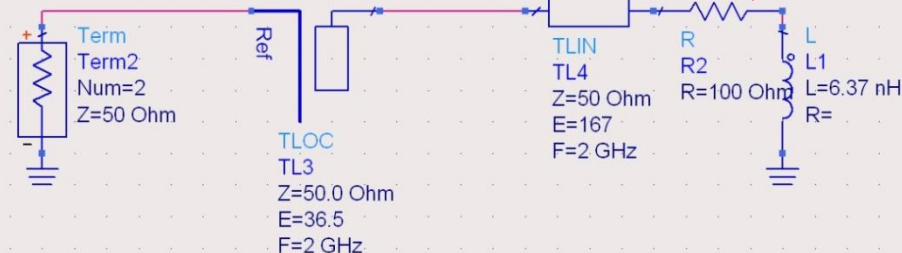
$$l_2 = \frac{36.8^\circ}{360^\circ} \cdot \lambda = 0.102 \cdot \lambda$$



# Stub, observations

- adding or subtracting **180°** ( $\lambda/2$ ) doesn't change the result (full rotation around the Smith Chart)

$$E = \beta \cdot l = \pi = 180^\circ \quad l = k \cdot \frac{\lambda}{2}, \forall k \in \mathbf{N}$$

- if the lines/stubs result with **negative** "length"/ "electrical length" we add  $\lambda/2$  /  $180^\circ$  to obtain physically realizable lines
- adding or subtracting **90°** ( $\lambda/4$ ) change the stub impedance:

$$Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l \quad \Leftrightarrow \quad Z_{in,g} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$

- for the stub we can add or subtract  $90^\circ$  ( $\lambda/4$ ) while in the same time changing **open-circuit**  $\Leftrightarrow$  **short-circuit**


# Double stub tuning

Adaptarea cu doua sectiuni de linie

---
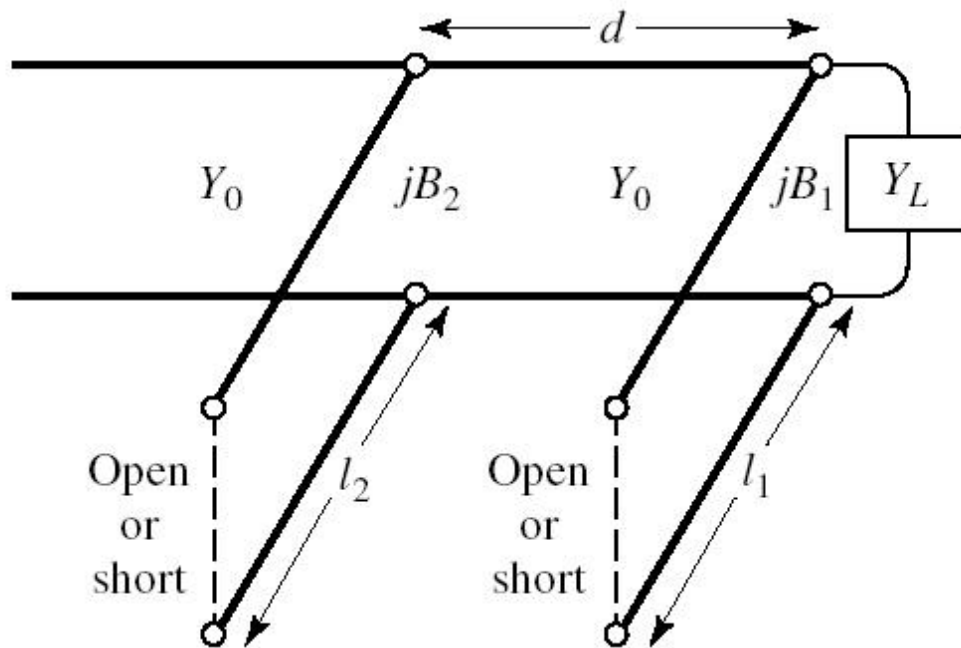
# Double stub tuning

- Double stub tuning
- uses two tuning stubs in fixed positions (a fixed length of line between the stubs)



# Double stub tuning


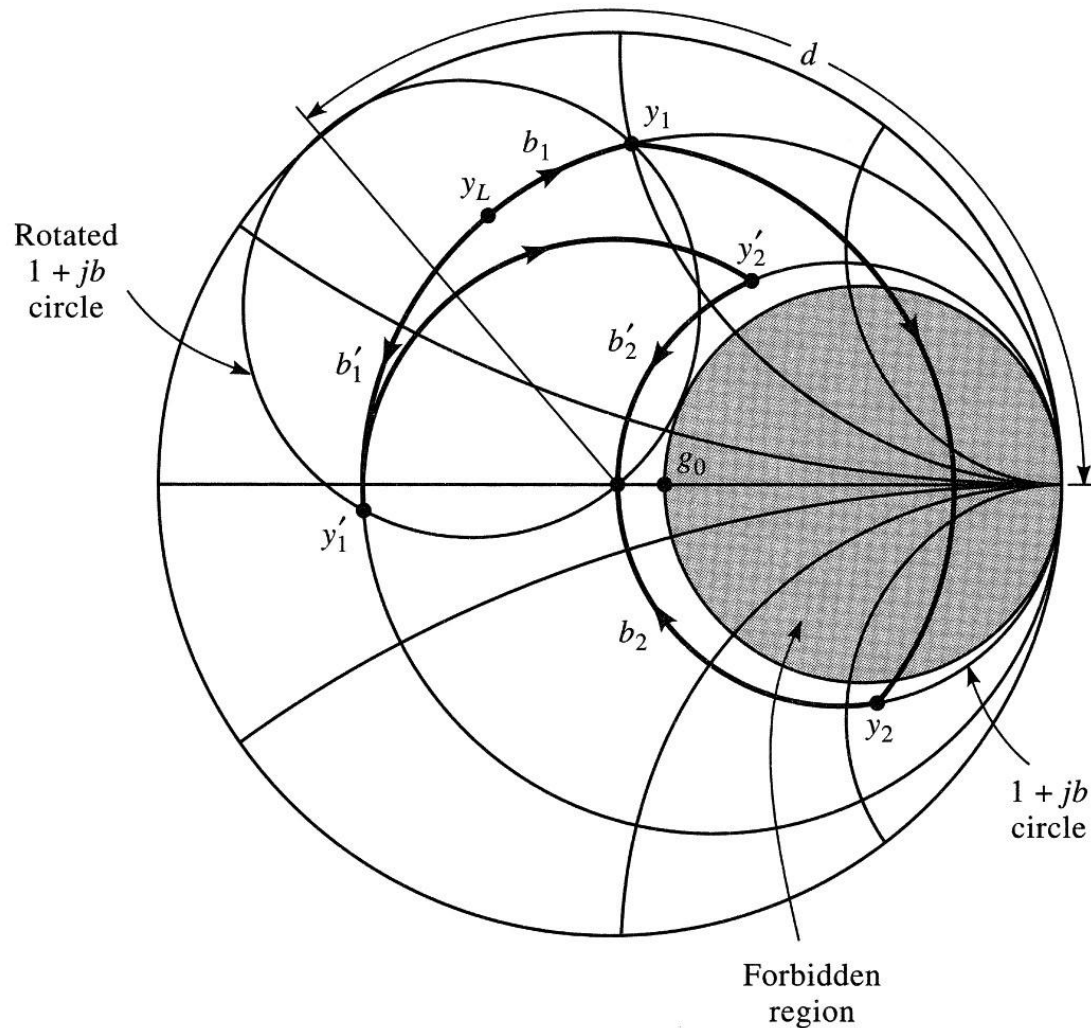
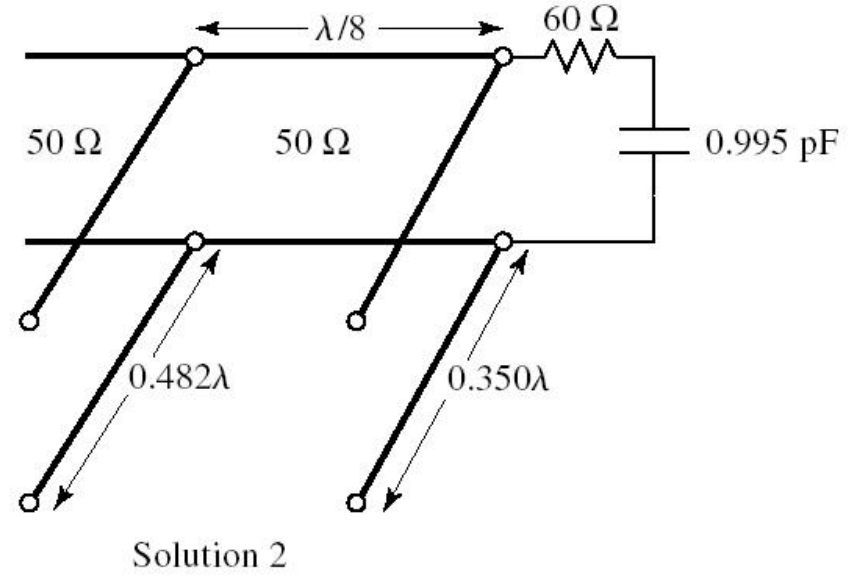


Figure 5.8  
© John Wiley & Sons, Inc. All rights reserved.

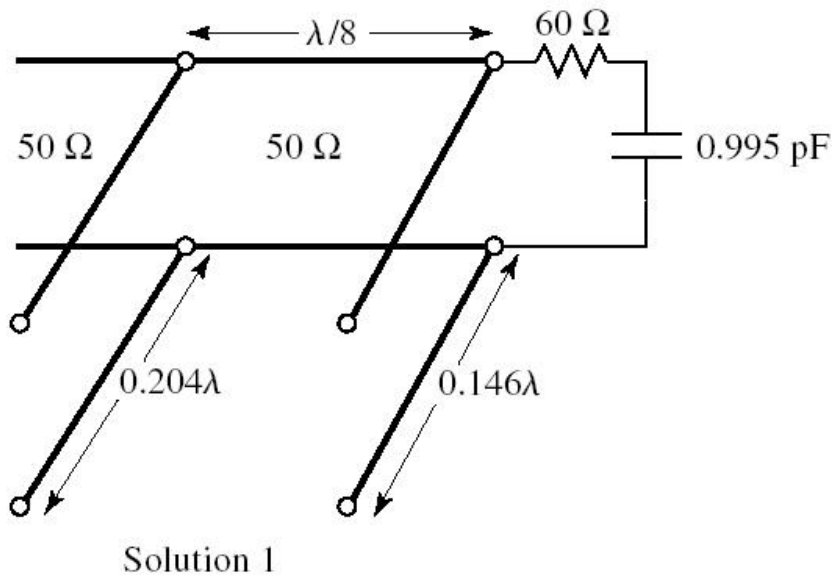
# Double stub tuning

- same load:  $60\ \Omega$  series with  $0.995\ \text{pF}$  at  $2\ \text{GHz}$
- two possible solutions




# Double stub tuning

- two possible solutions





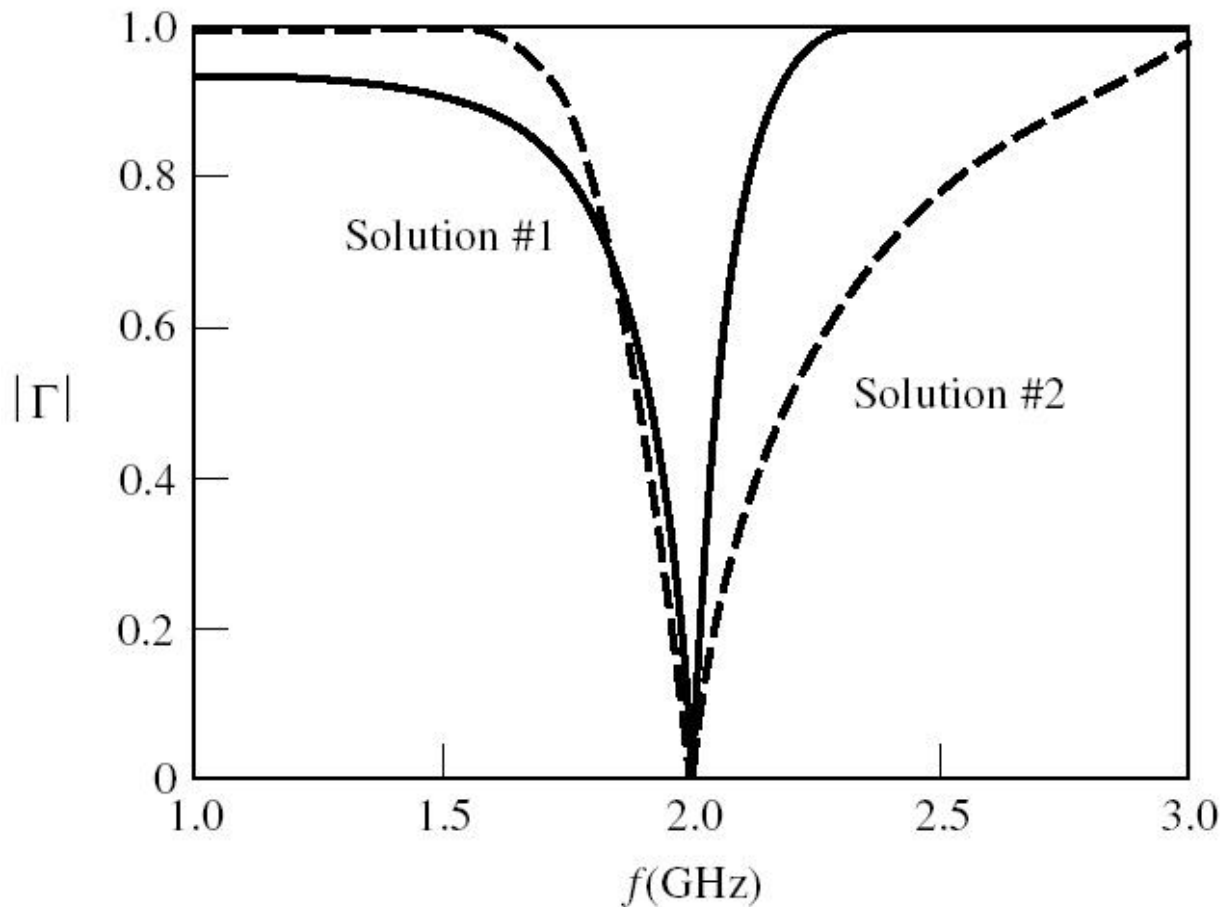

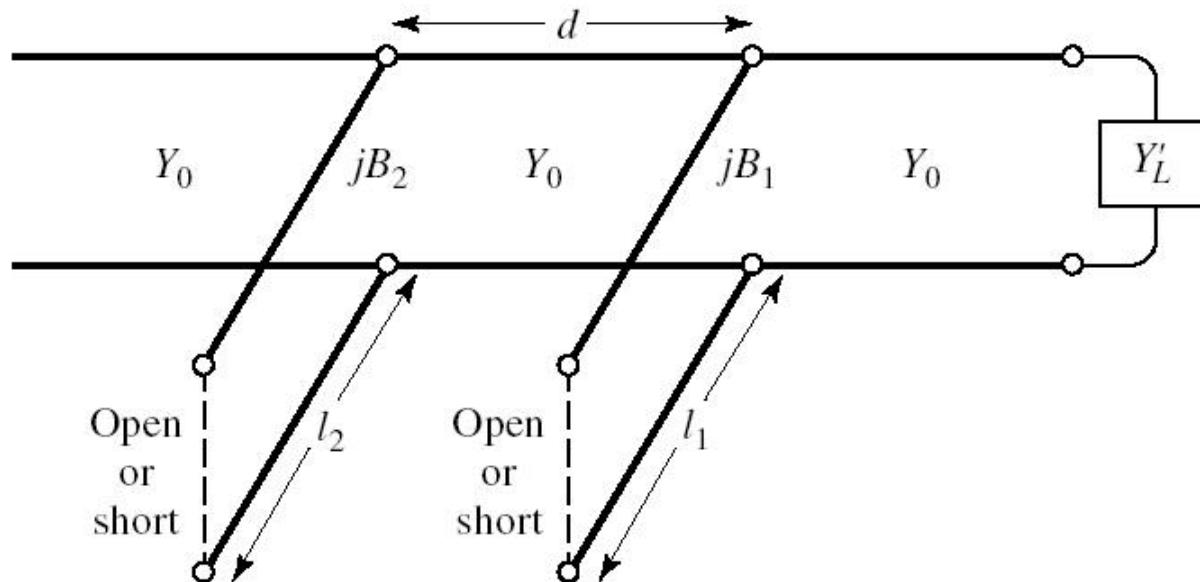
# Double stub tuning

- Typically  $d = \lambda/8$  or  $d = 3\lambda/8$ 
  - $d \rightarrow 0$  and  $d \rightarrow \lambda/2$  offer frequency sensitive solutions
- **Not possible** for every load
  - unless we can add a specific length of line between the load and the first stub



# Impedance Matching with Stubs

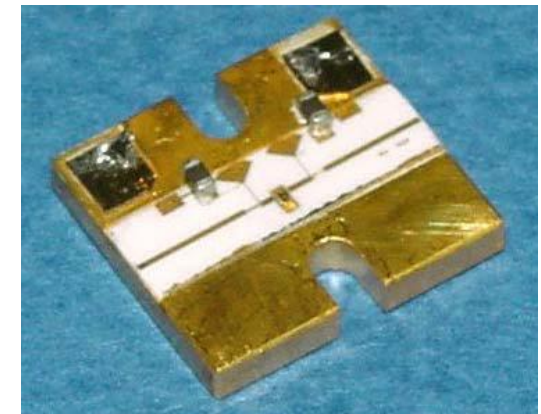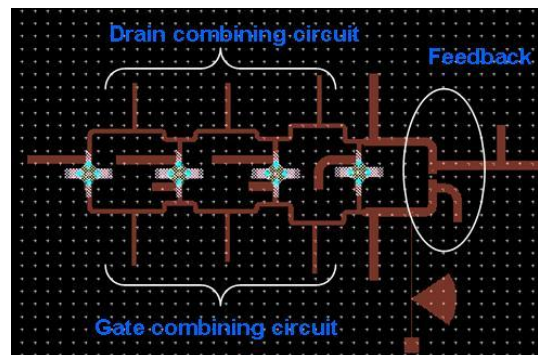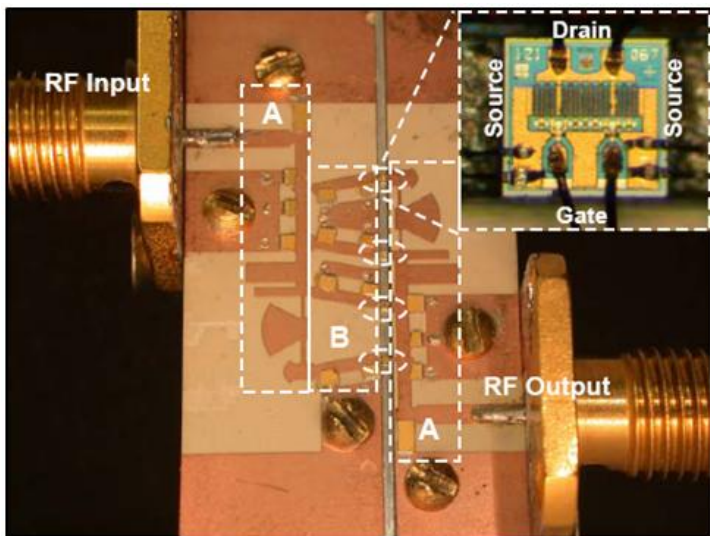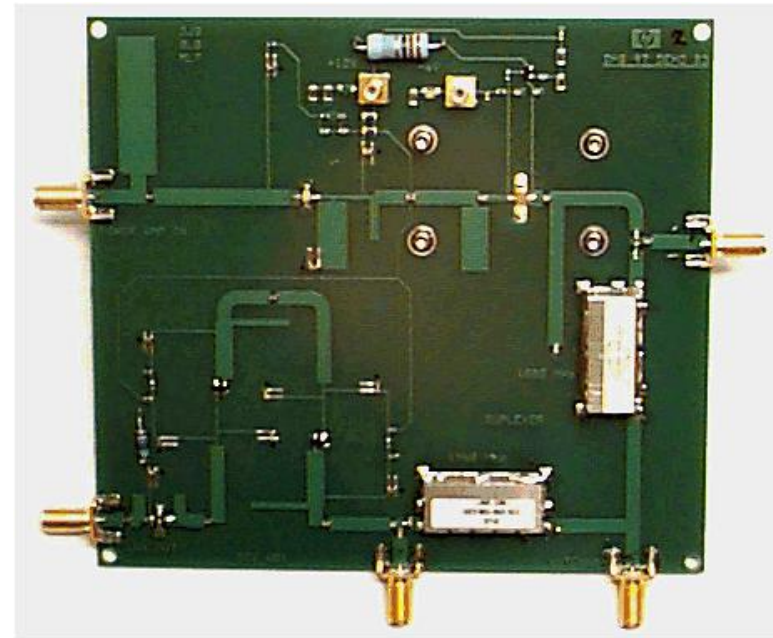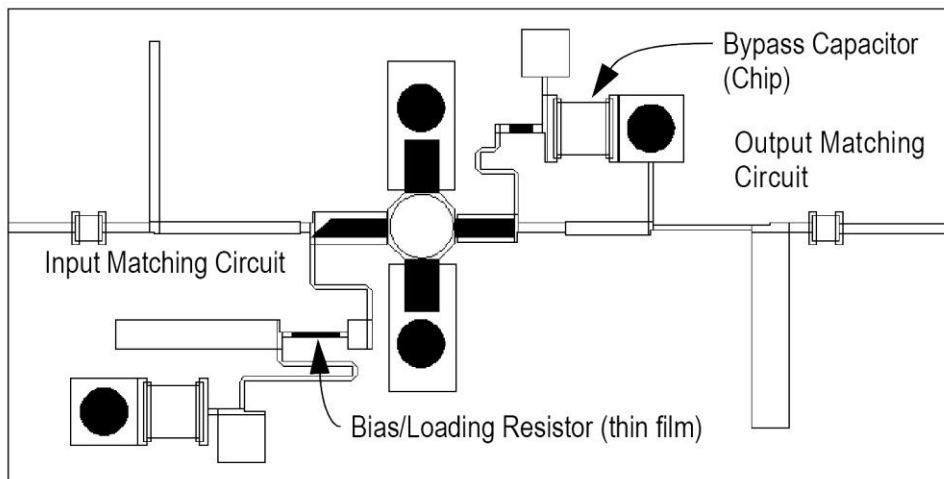


# Microwave Amplifiers


# Course Topics

- Transmission lines
- Impedance matching and tuning
- Directional couplers
- Power dividers
- **Microwave amplifier design**
- Microwave filters
- ~~Oscillators and mixers?~~





# Microwave Amplifiers

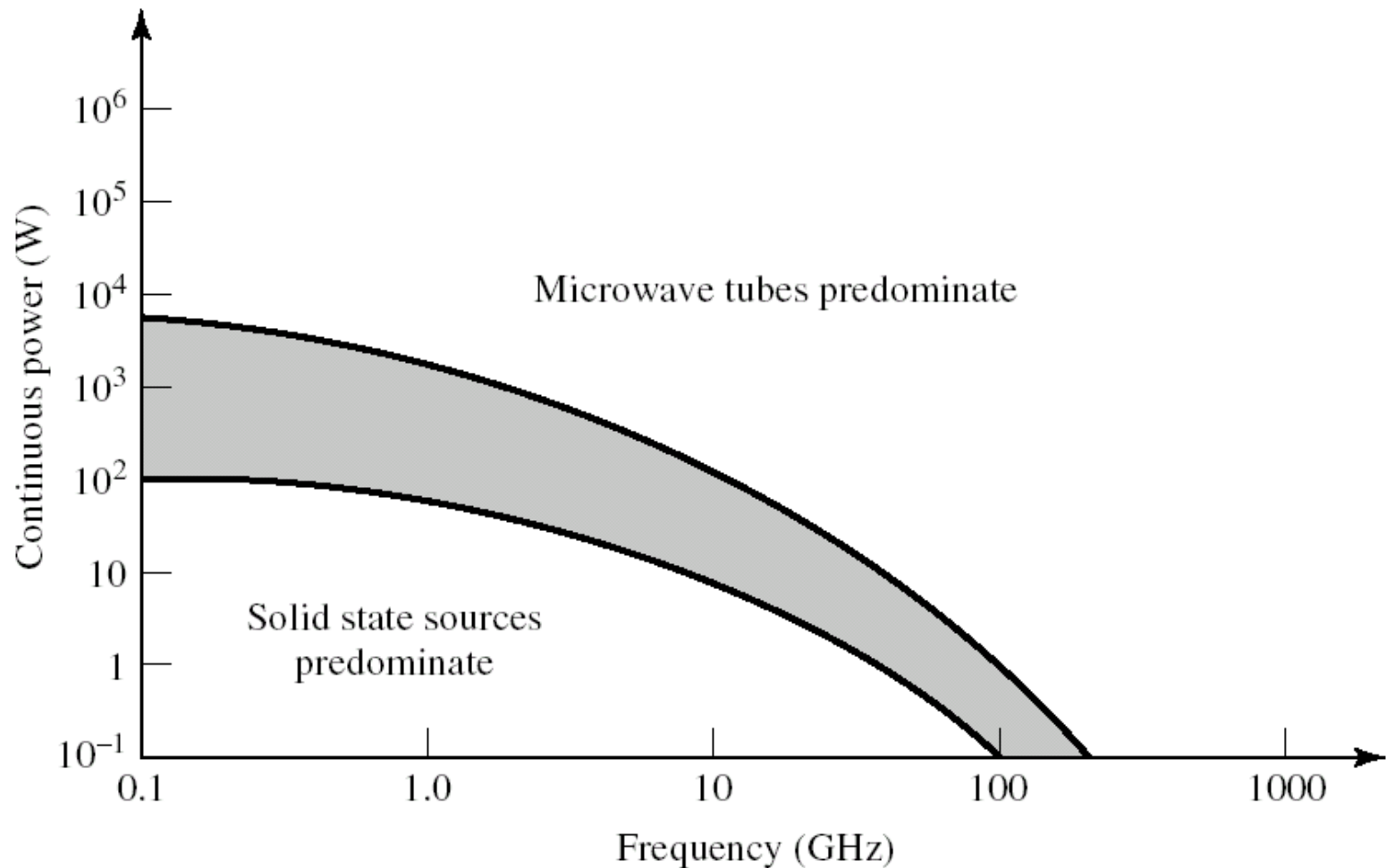

# Balanced amplifiers

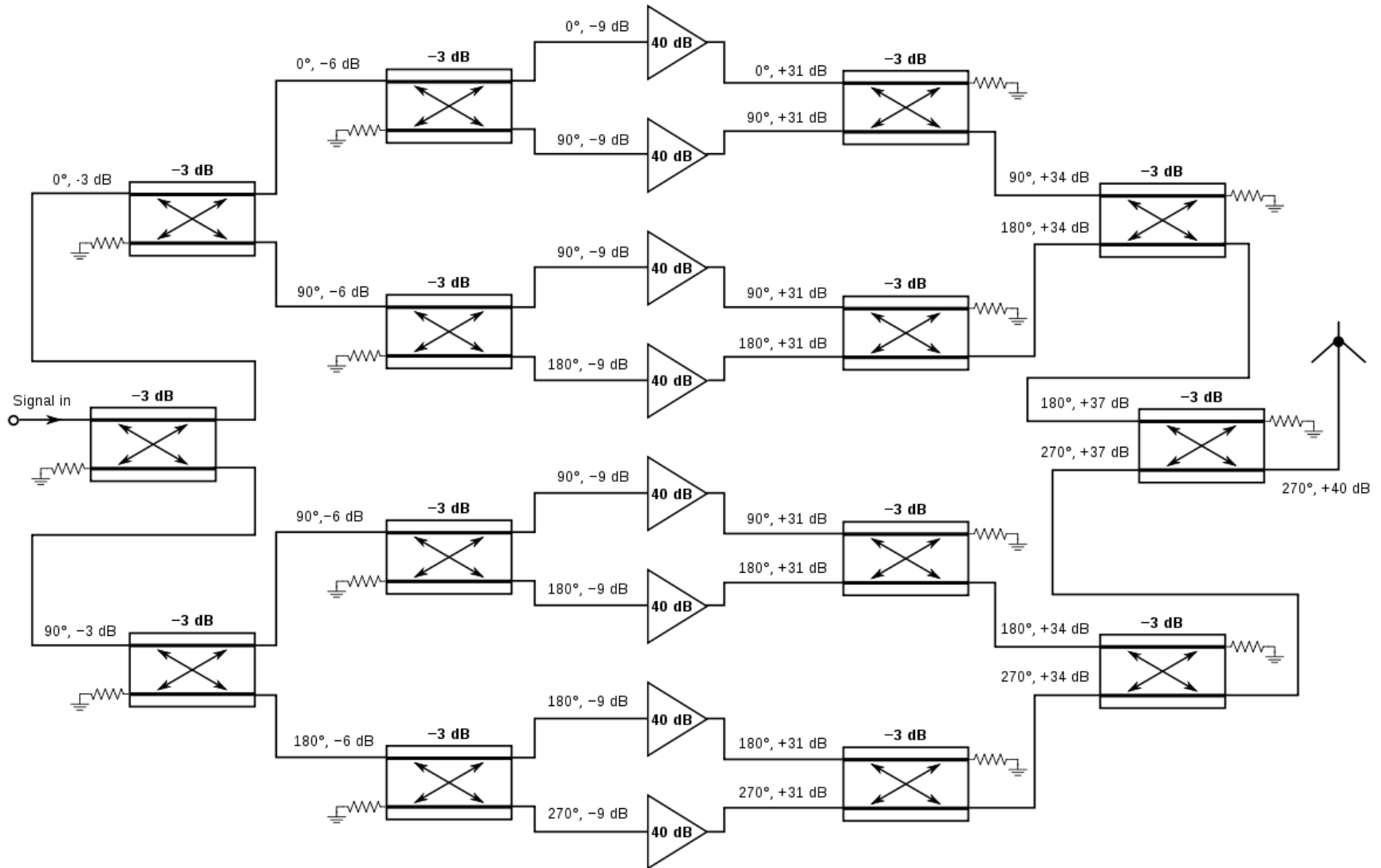

# Microwave Integrated Circuits

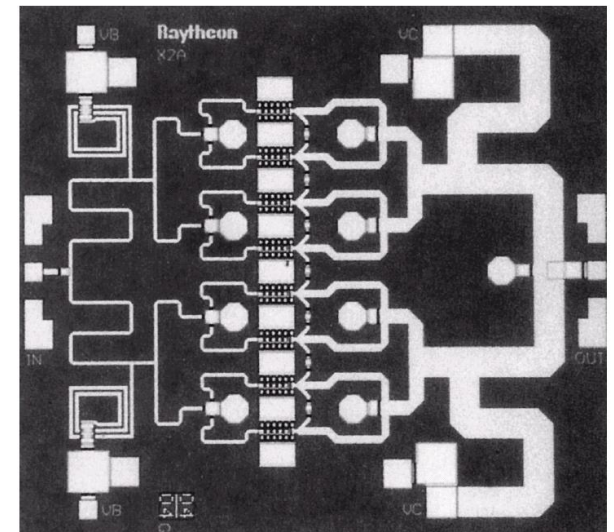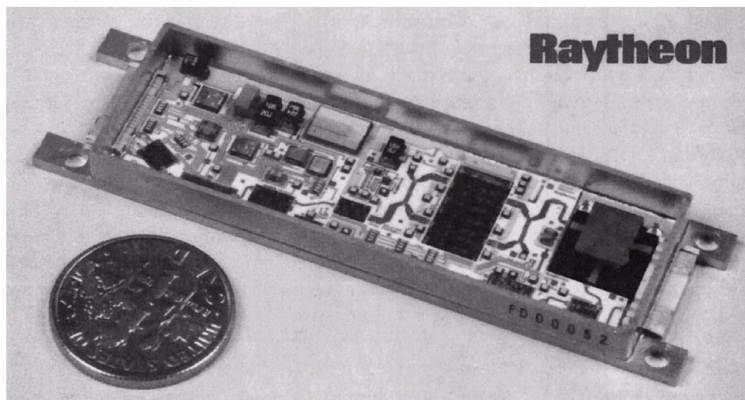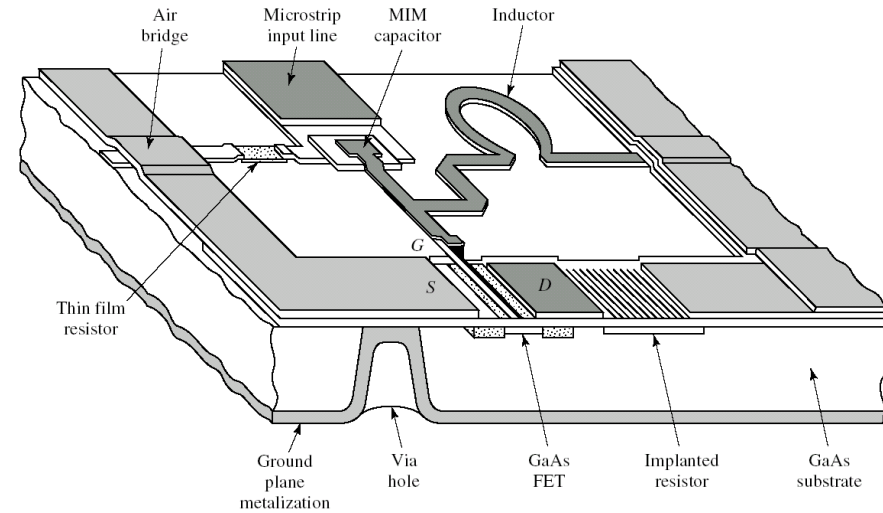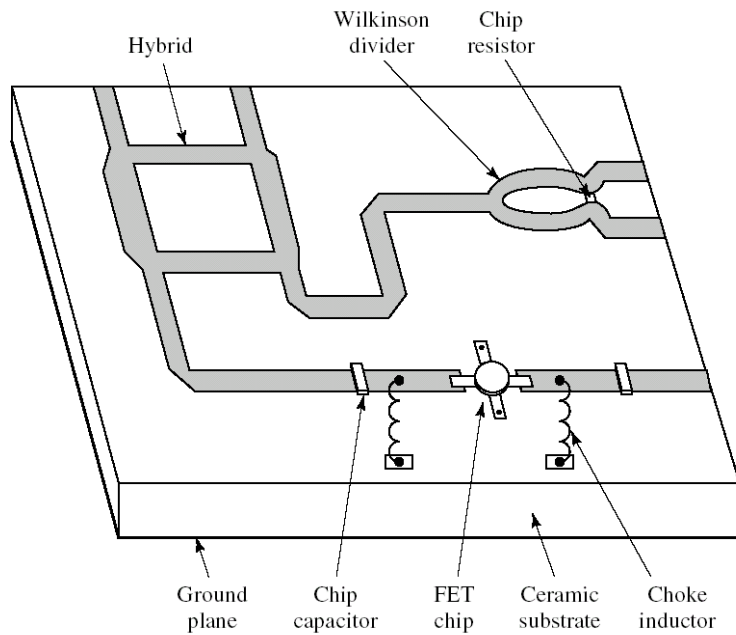

# Contact

- Microwave and Optoelectronics Laboratory
- <https://rf-opto.etti.tuiasi.ro>
- [rdamian@etti.tuiasi.ro](mailto:rdamian@etti.tuiasi.ro)