

Lecture 9
2025/2026

Microwave Devices and Circuits for Radiocommunications

2025/2026

- 2C/1L, **MDCR**
- Attendance at minimum 7 sessions (course or laboratory)
- Lectures- **associate professor Radu Damian**
 - Tuesday **12-14, P2**
 - E – 50% final grade
 - problems + (2p atten. lect.) + (3 tests) + (bonus activity)
 - first test L1: 24.02.2026 (t2 and t3 not announced, lecture)
 - 3att.=+0.5p
 - all materials/equipments authorized


2025/2026

- Laboratory – **associate professor Radu Damian**
 - Monday 14-16, Il.13 / (even weeks)
 - L – 25% final grade
 - ADS, 4 sessions
 - Attendance + **personal results**
 - P – 25% final grade
 - ADS, 3 sessions (-1? 24.02.2026)
 - personal homework

General theory


Microwave Network Analysis

Course Topics

- Transmission lines
 - Impedance matching and tuning
 - Directional couplers
 - Power dividers
 - Microwave amplifier design
 - Microwave filters
 - ~~Oscillators and mixers?~~
- 

Scattering matrix – S

- Scattering parameters

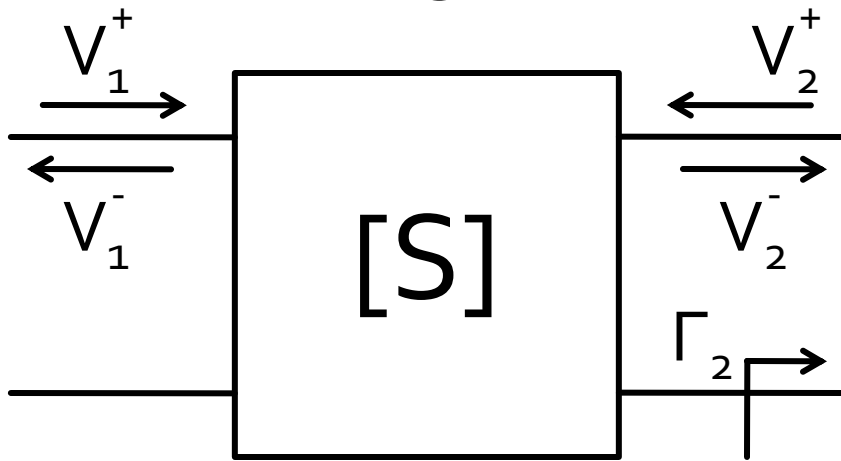

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+ = 0} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+ = 0}$$

- $V_2^+ = 0$ meaning: port 2 is terminated in matched load to avoid reflections towards the port

$$\Gamma_2 = 0 \rightarrow V_2^+ = 0$$

Power waves for N ports

$$[b] = [F] \cdot ([Z] - [Z_R]^*) \cdot ([Z] + [Z_R])^{-1} \cdot [F]^{-1} \cdot [a]$$

- The scattering matrix for power waves, $[S_p]$

$$[b] = [S_p] \cdot [a]$$

$$[S_p] = [F] \cdot ([Z] - [Z_R]^*) \cdot ([Z] + [Z_R])^{-1} \cdot [F]^{-1}$$

- But: $[S] = ([Z] - [Z_0]) \cdot ([Z] + [Z_0])^{-1}$

- Typically


$$Z_{0i} = Z_{Ri} = R_0, \forall i$$

$$R_0 = 50\Omega$$

$$[S_p] \equiv [S]$$

- they coincide!!!

Scattering matrix – S

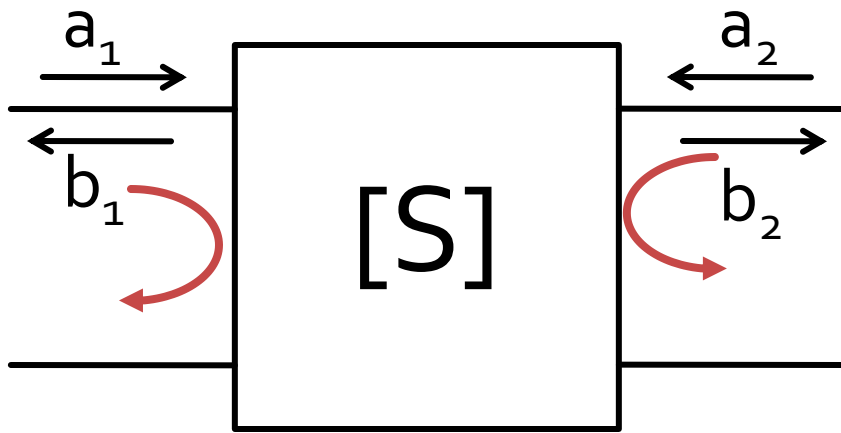


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

- S_{11} and S_{22} are **reflection coefficients** at ports 1 and 2 when the other port is **matched**

Scattering matrix – S

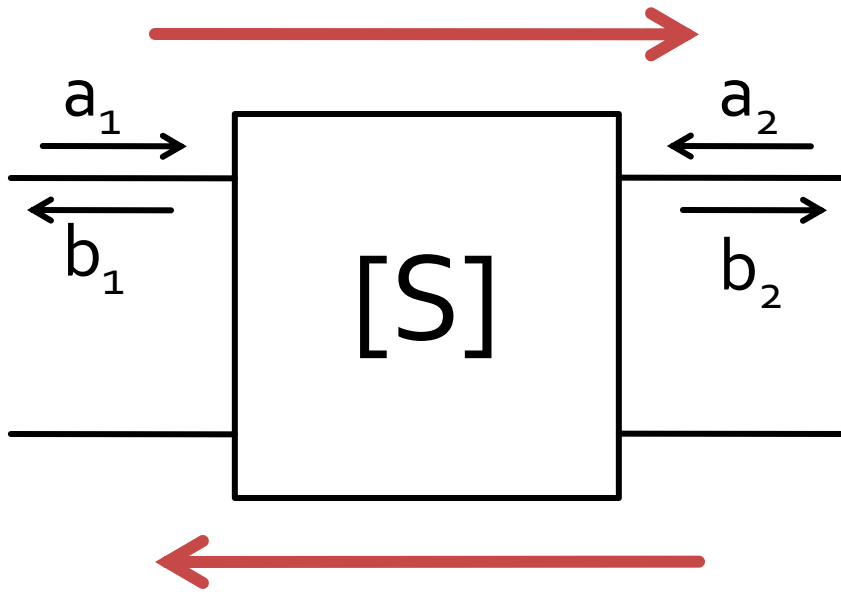


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$$

- S_{21} si S_{12} are signal amplitude **gain** when the other port is **matched**

Scattering matrix – S

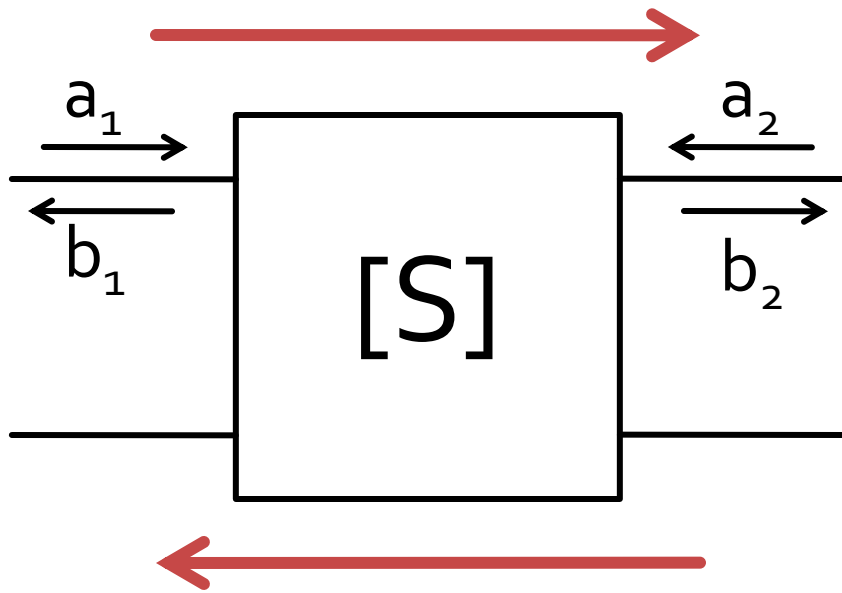

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$


$$|S_{21}|^2 = \frac{\text{Power in } Z_0 \text{ load}}{\text{Power from } Z_0 \text{ source}}$$

- a, b
 - information about signal power **AND** signal phase
- S_{ij}
 - network effect (gain) over signal power **including** phase information


Impedance Matching

The Smith Chart


Course Topics

- Transmission lines
 - Impedance matching and tuning
 - Directional couplers
 - Power dividers
 - Microwave amplifier design
 - Microwave filters
 - ~~Oscillators and mixers?~~
- 

The Smith Chart

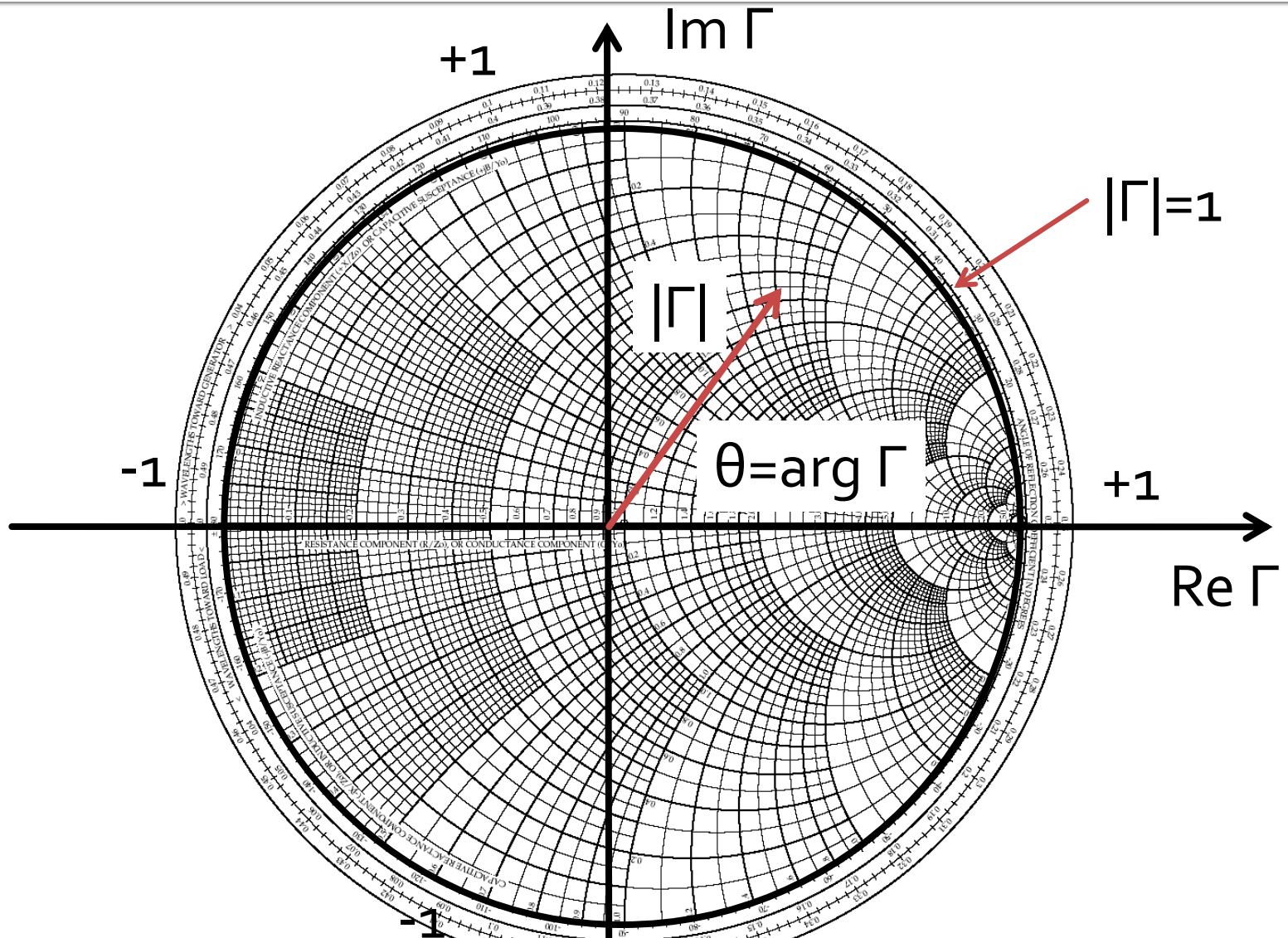

The Smith Chart

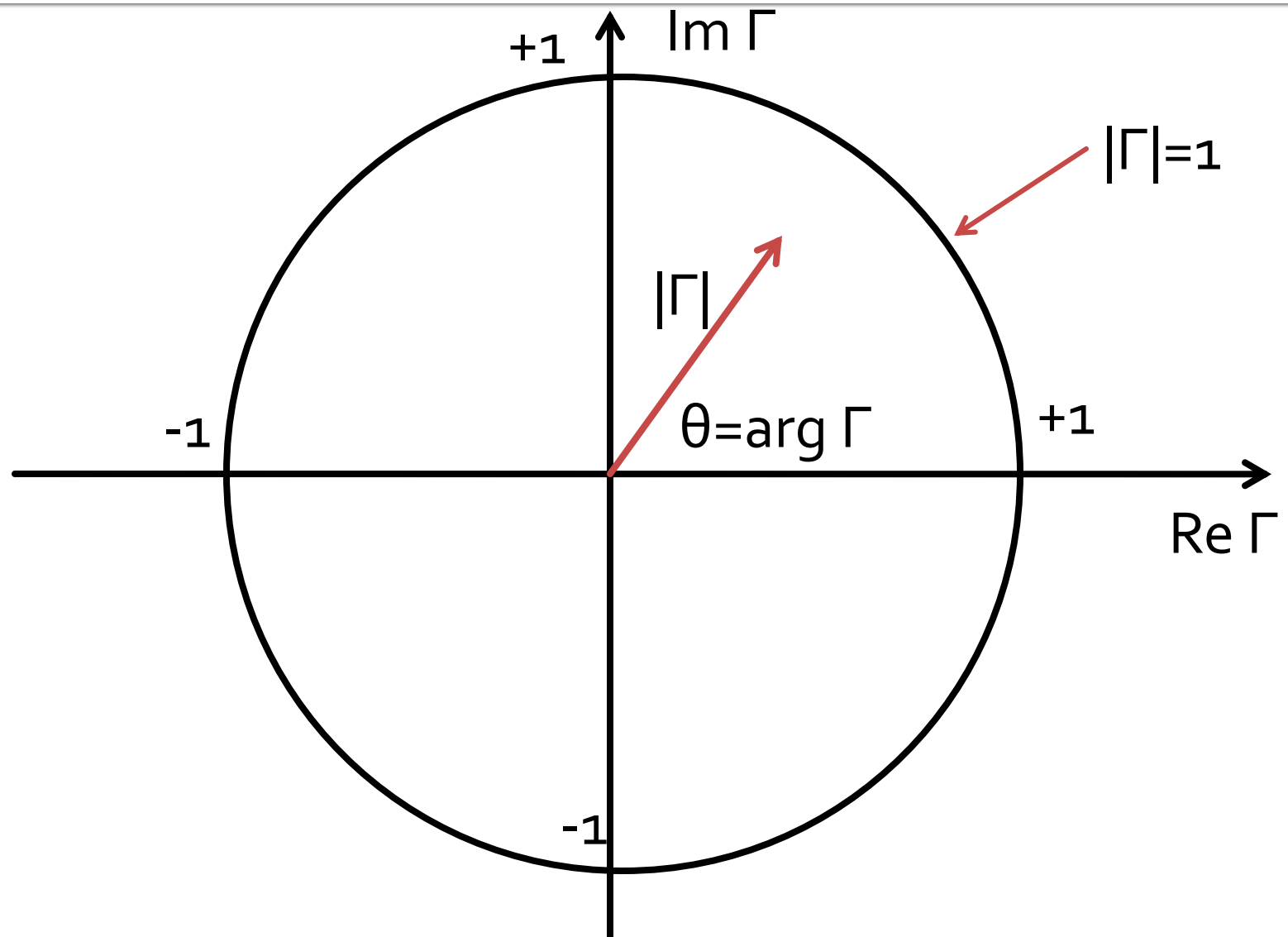




The Smith Chart

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{z_L - 1}{z_L + 1}$$


$$z_L = r_L + j \cdot x_L$$

$$r_L = ct.$$


$$x_L = ct.$$

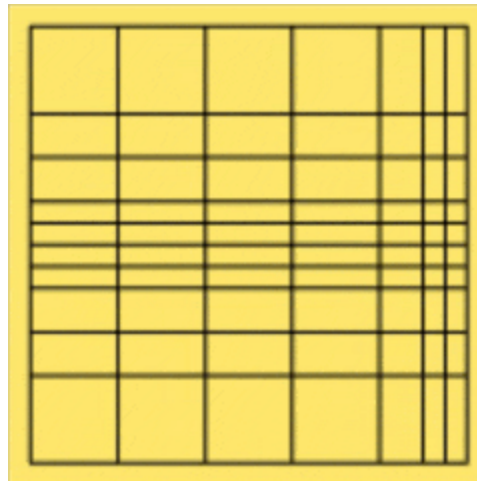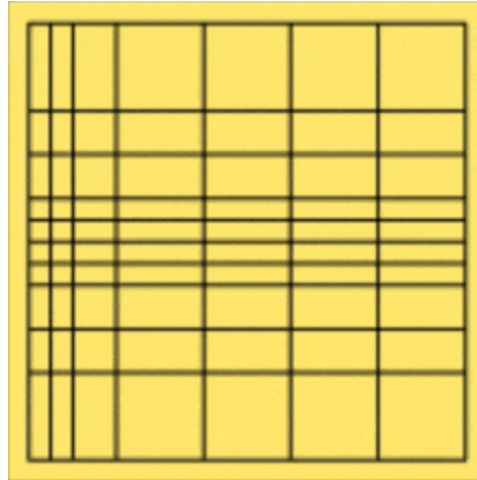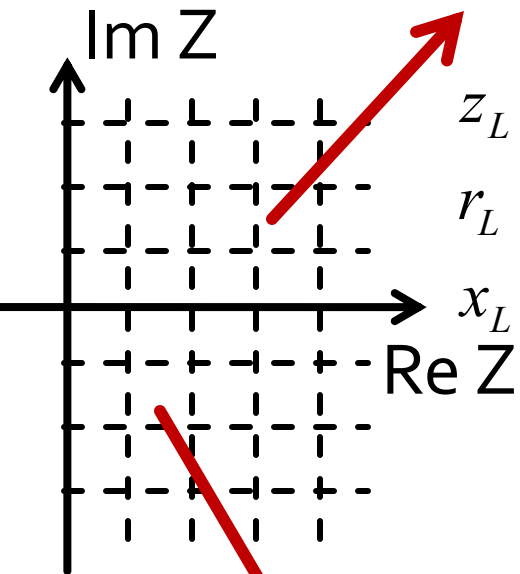

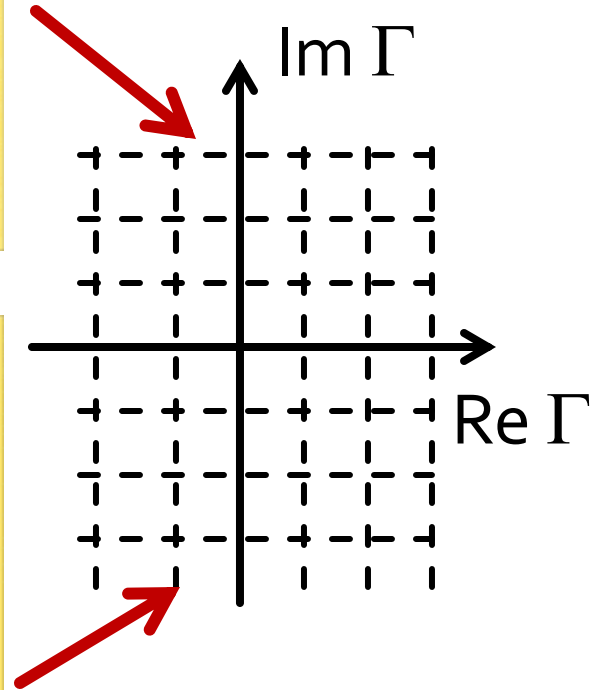
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Y_0 - Y_L}{Y_0 + Y_L} = \frac{1 - y_L}{1 + y_L}$$




The Smith Chart, resistance

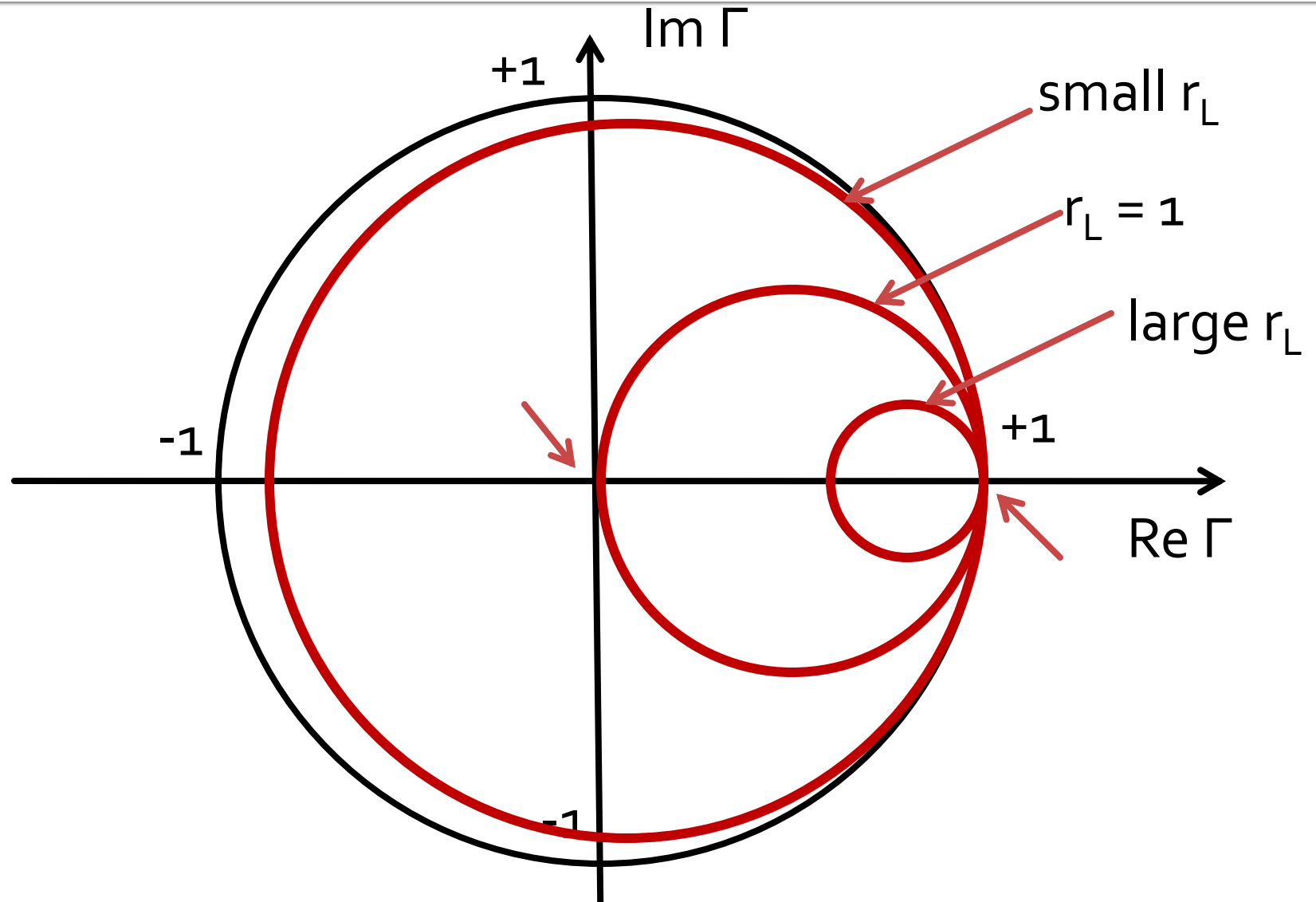

The Smith Chart, reactance

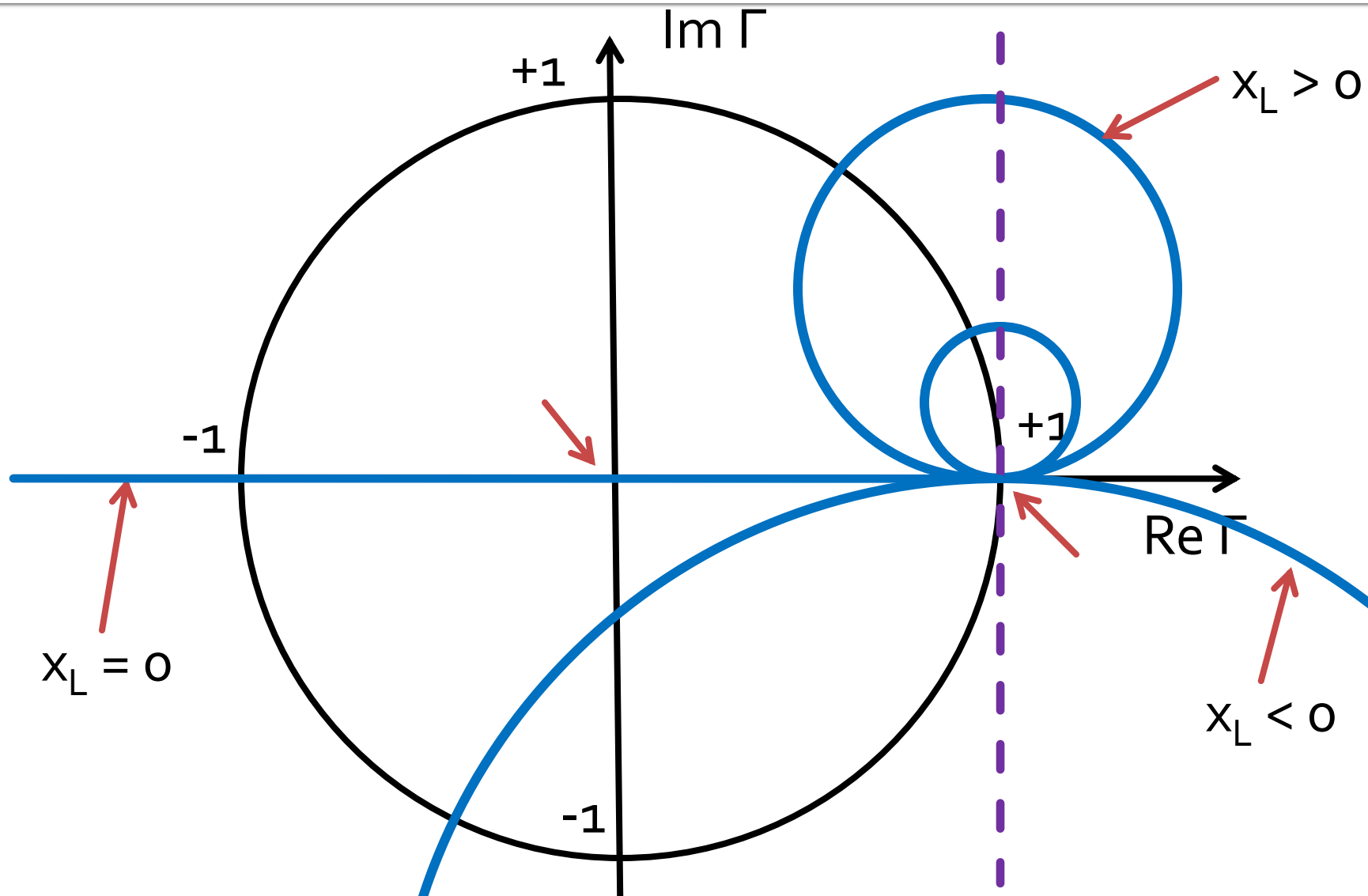

The Smith Chart, impedance

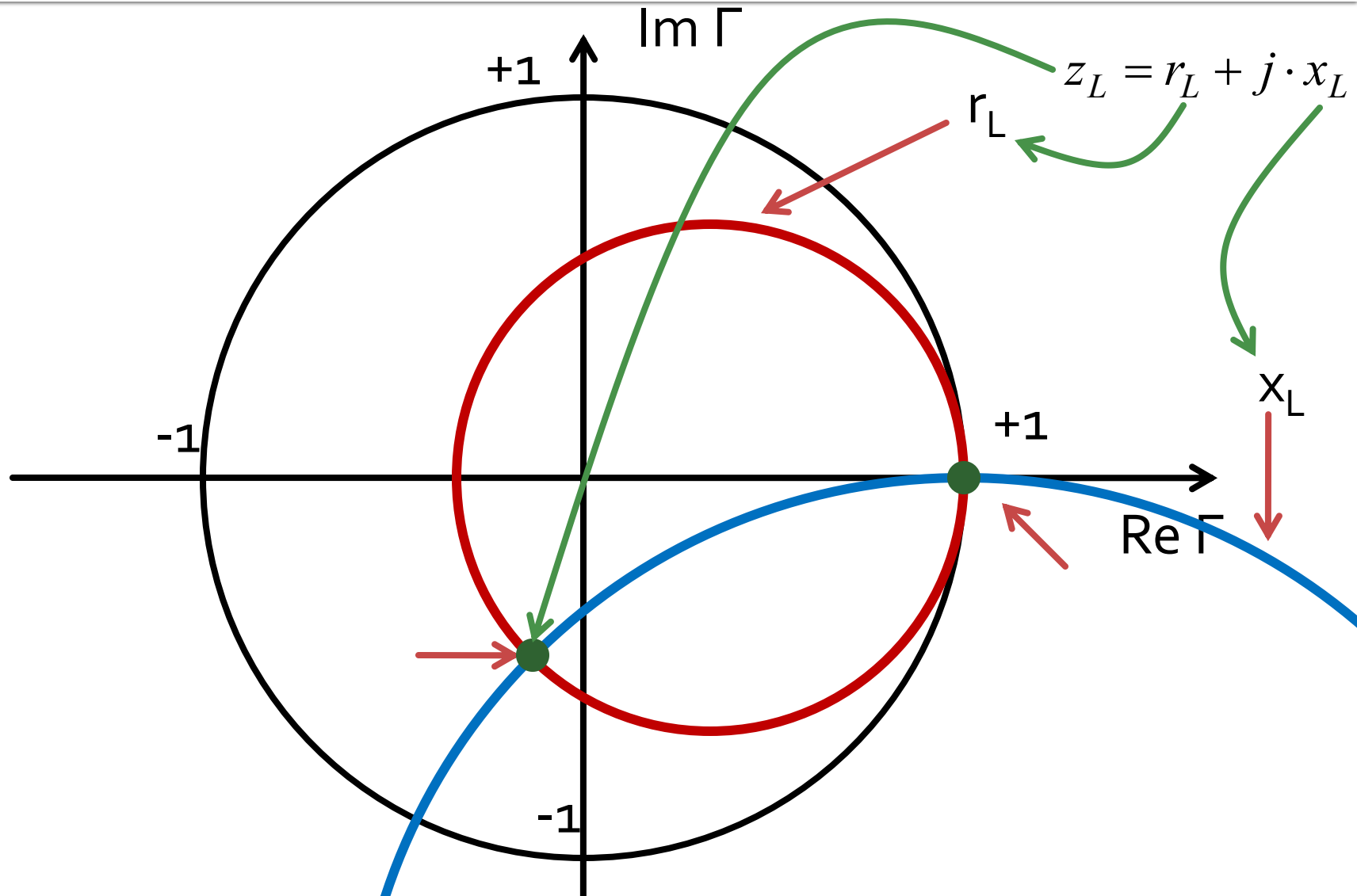



Impedance matching

Impedance Matching with lumped elements (L Networks)

Course Topics

- Transmission lines
- **Impedance matching and tuning**
- Directional couplers
- Power dividers
- Microwave amplifier design
- Microwave filters
- ~~Oscillators and mixers?~~

Impedance matching

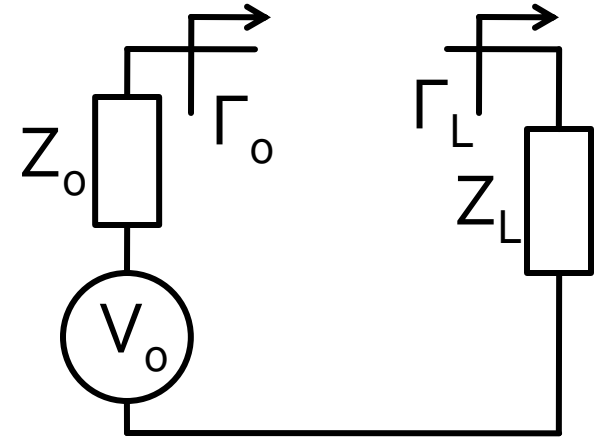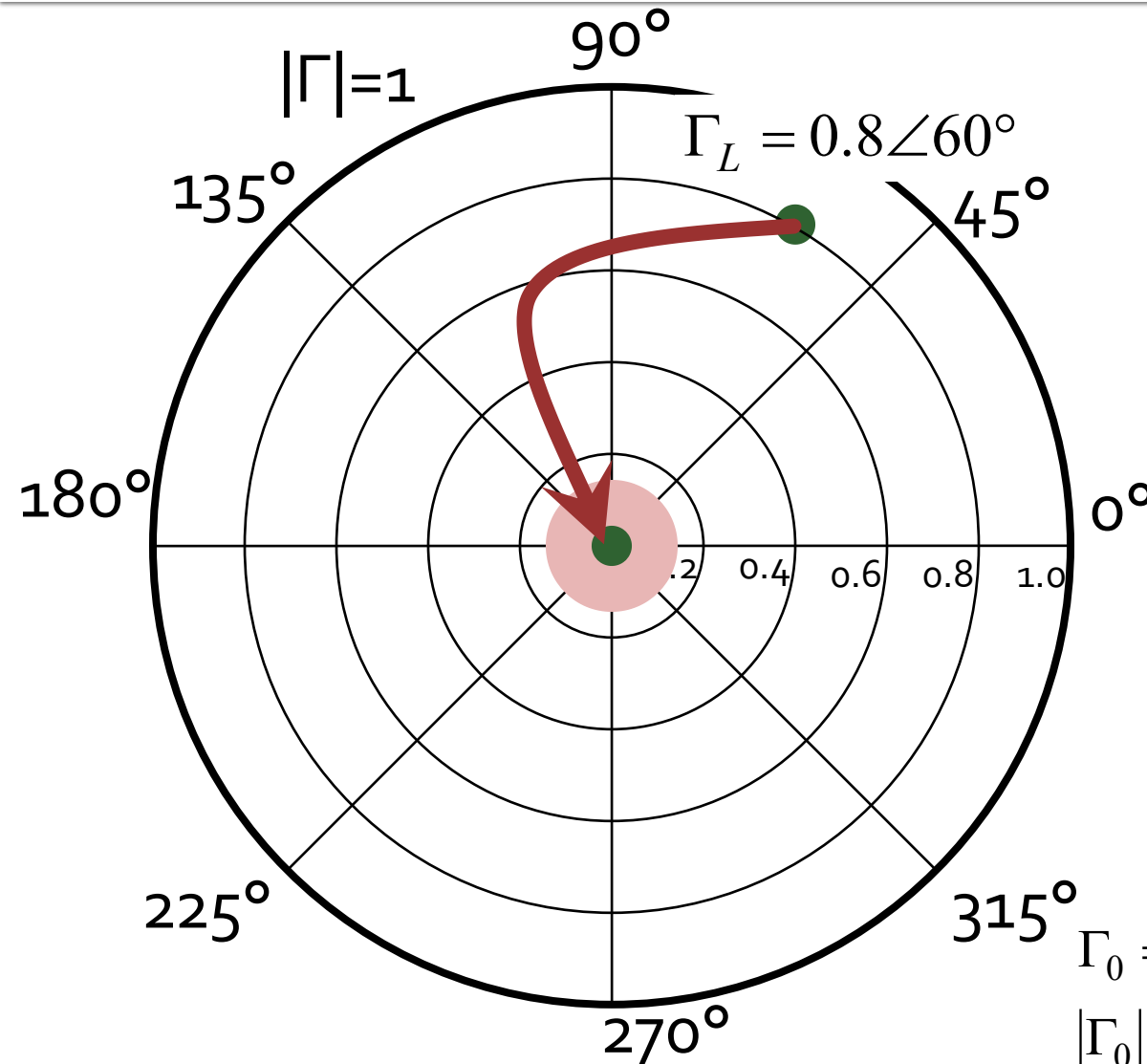


How?



$\Gamma_0 = 0$ perfect match ●

$|\Gamma_0| \leq \Gamma_m$ "good enough" match ●

Smith chart, $r=1$ and $g=1$

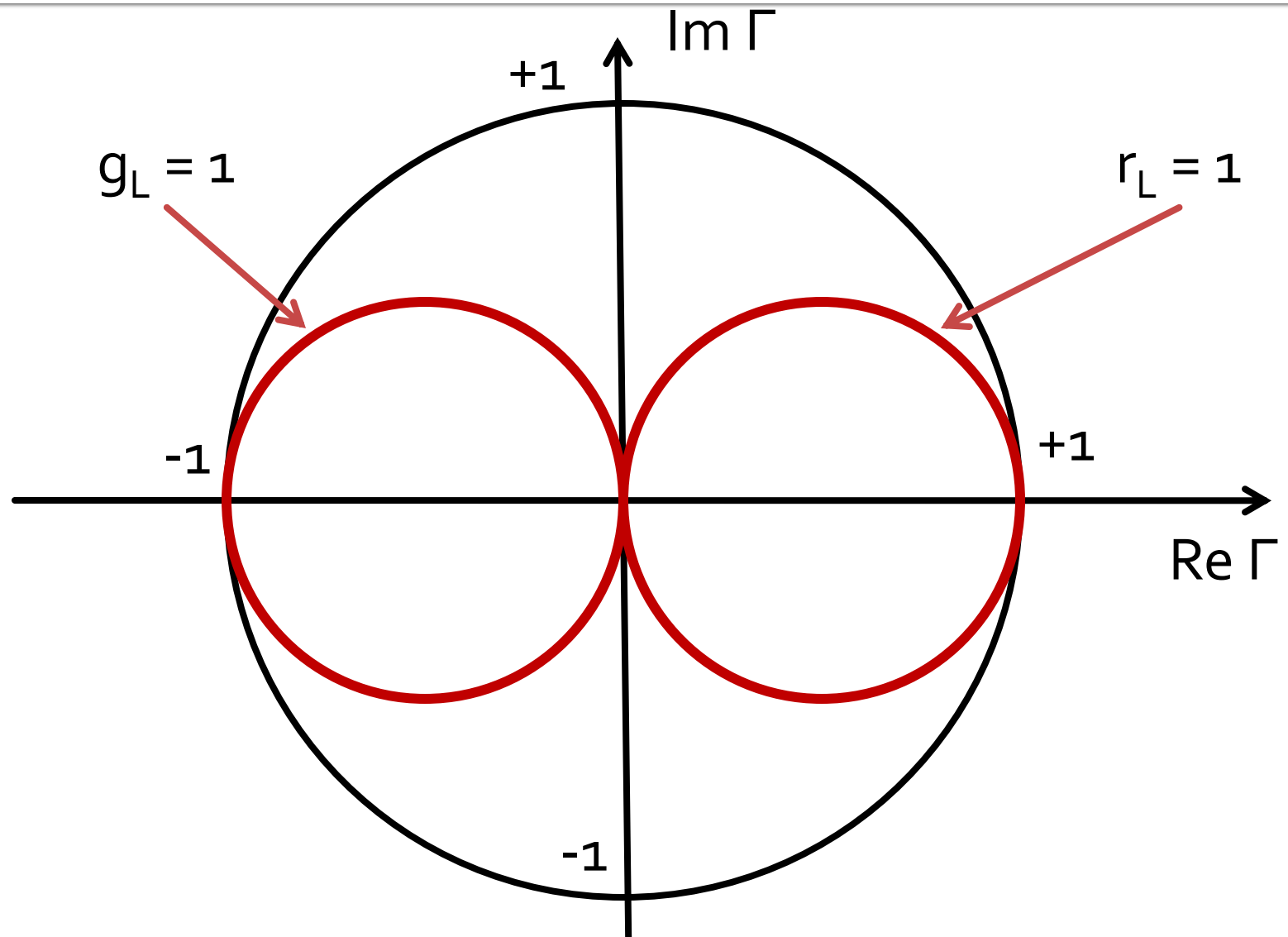


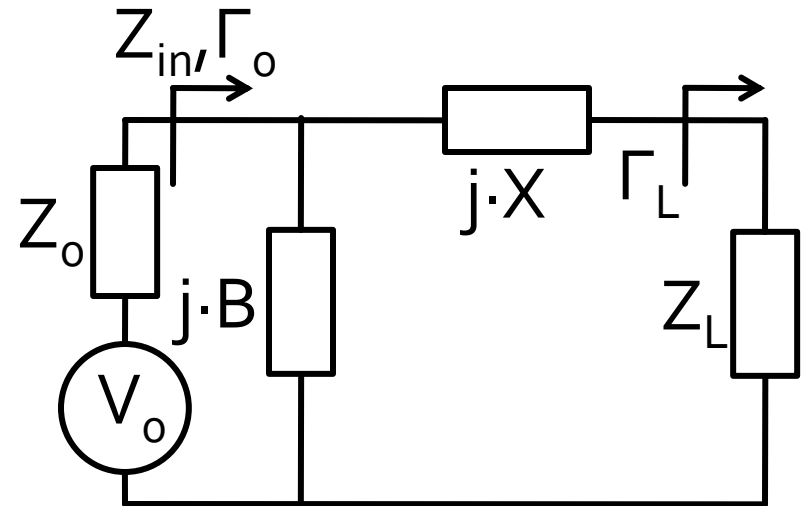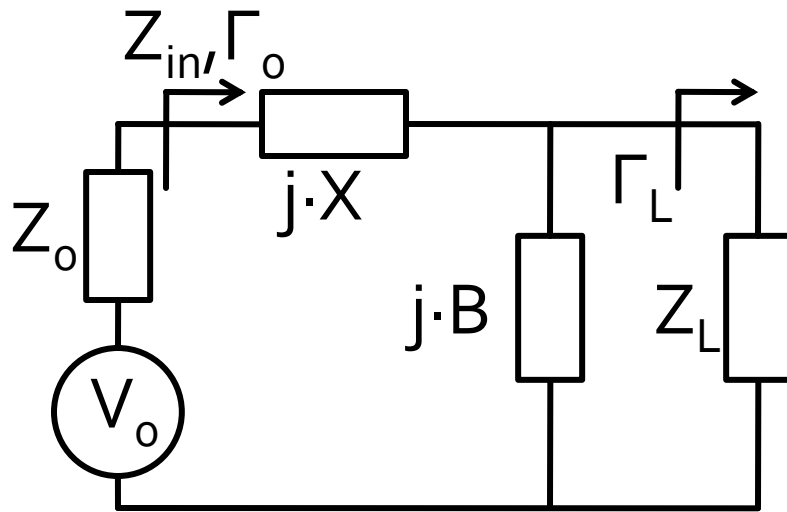Matching with 2 reactive elements (L Networks)



- Two steps matching
 - first reactive element moves the reflection coefficient **on the circle** $r_L = 1/g_L = 1$
 - second element compensates the remaining reactance and achieves the impedance match

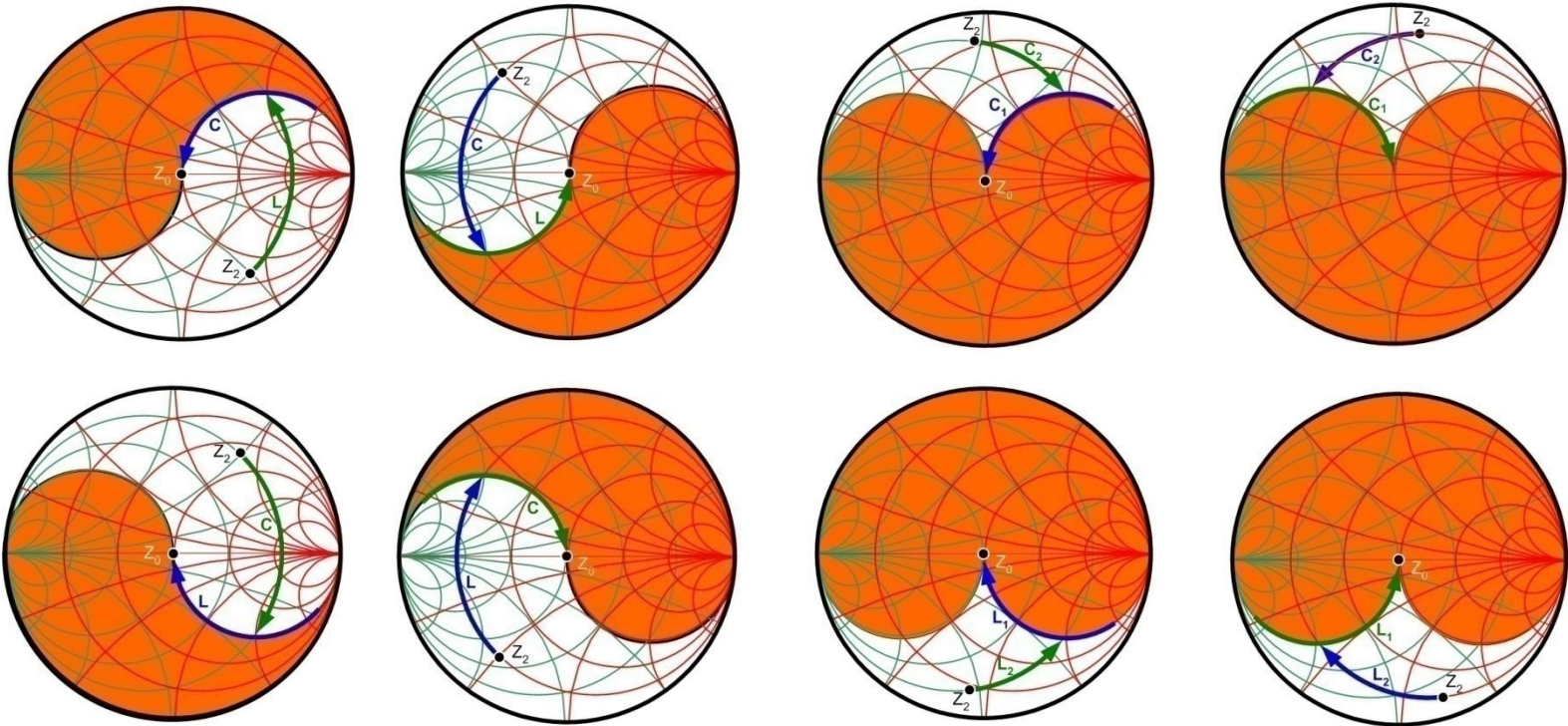Matching with 2 reactive elements (L Networks)




Forbidden area for
current network

Impedance Matching


Impedance Matching with Stubs

Smith chart, $r=1$ and $g=1$

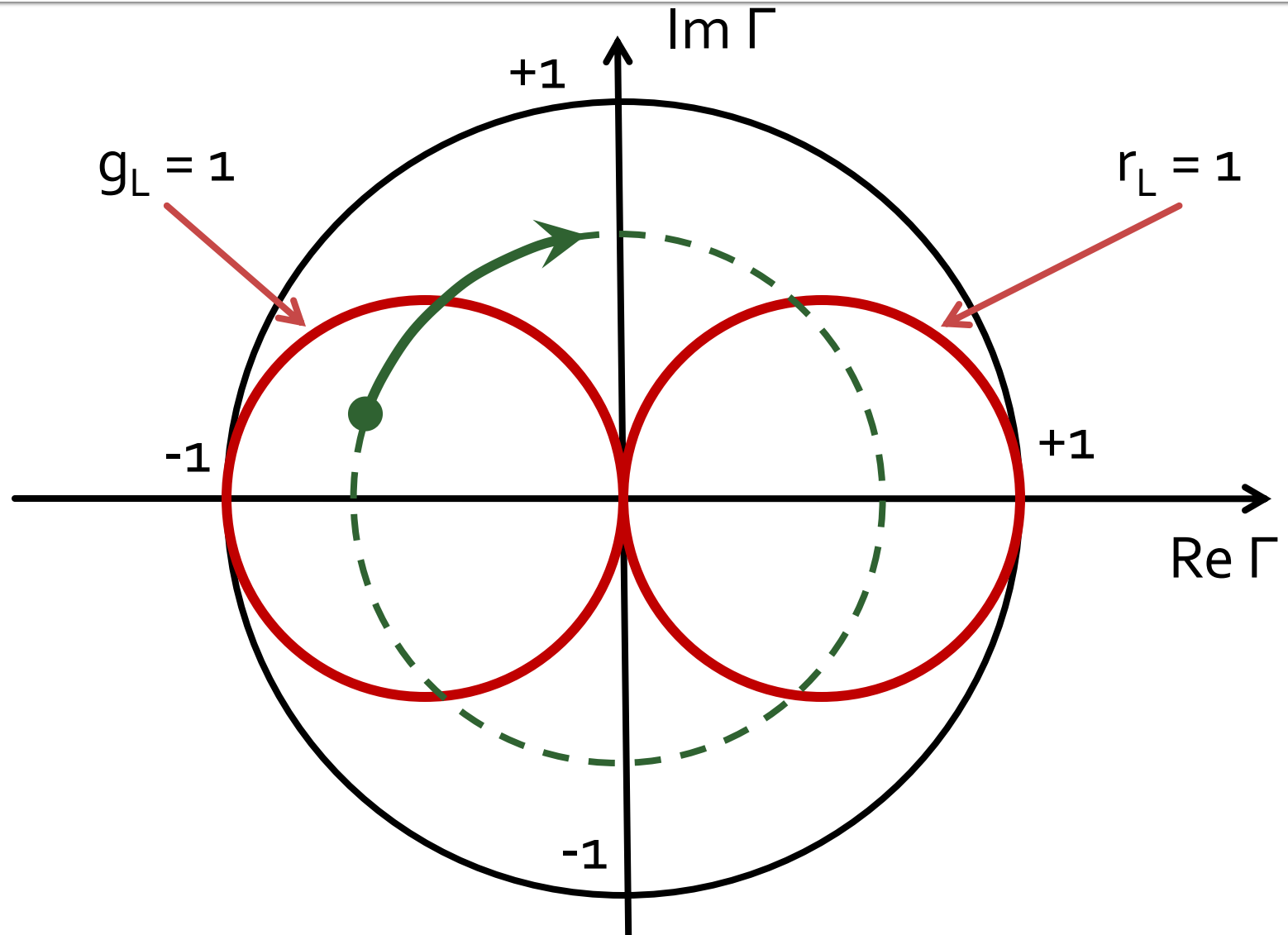


Single stub tuning

- Shunt Stub

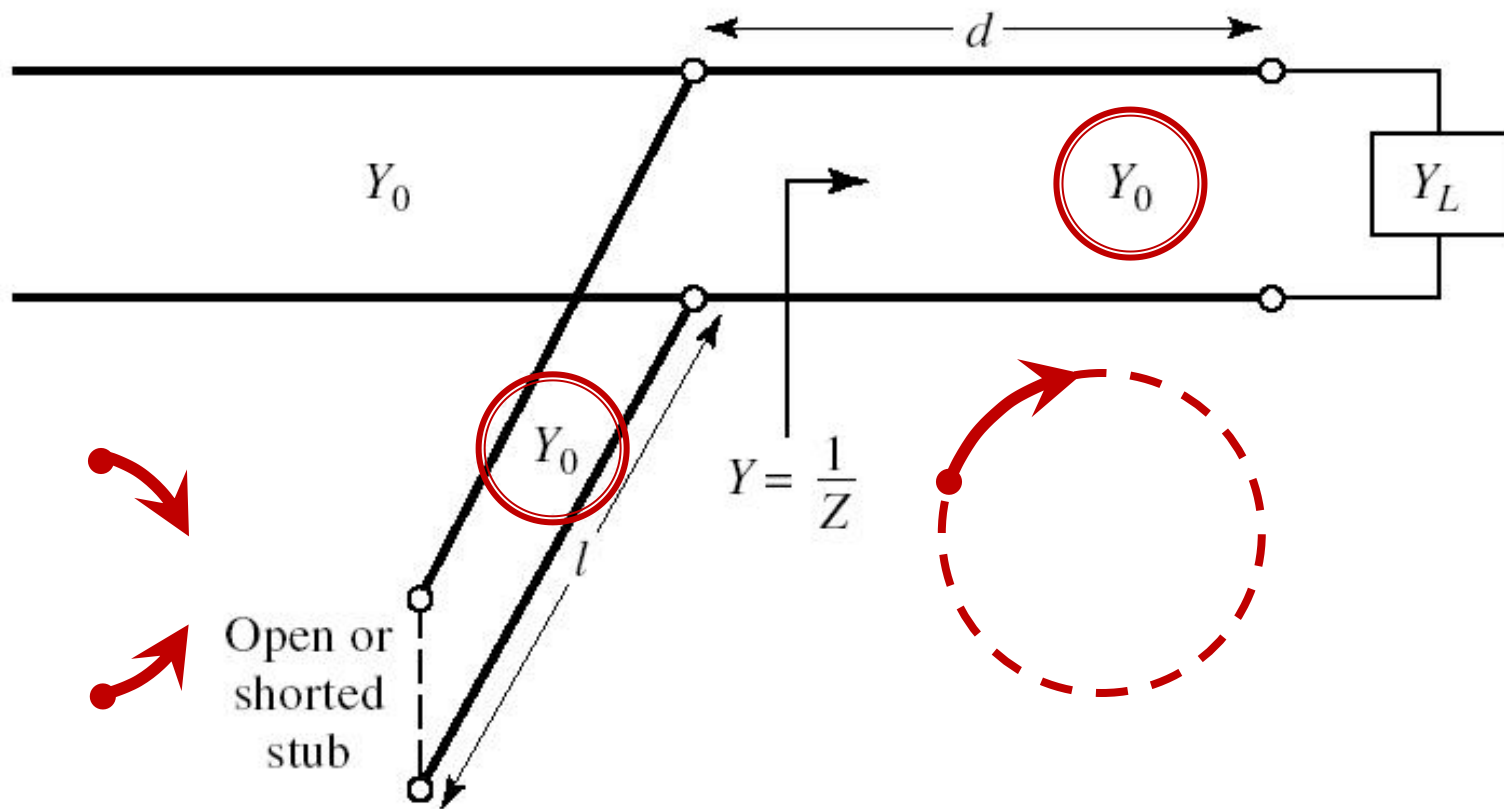

Single stub tuning

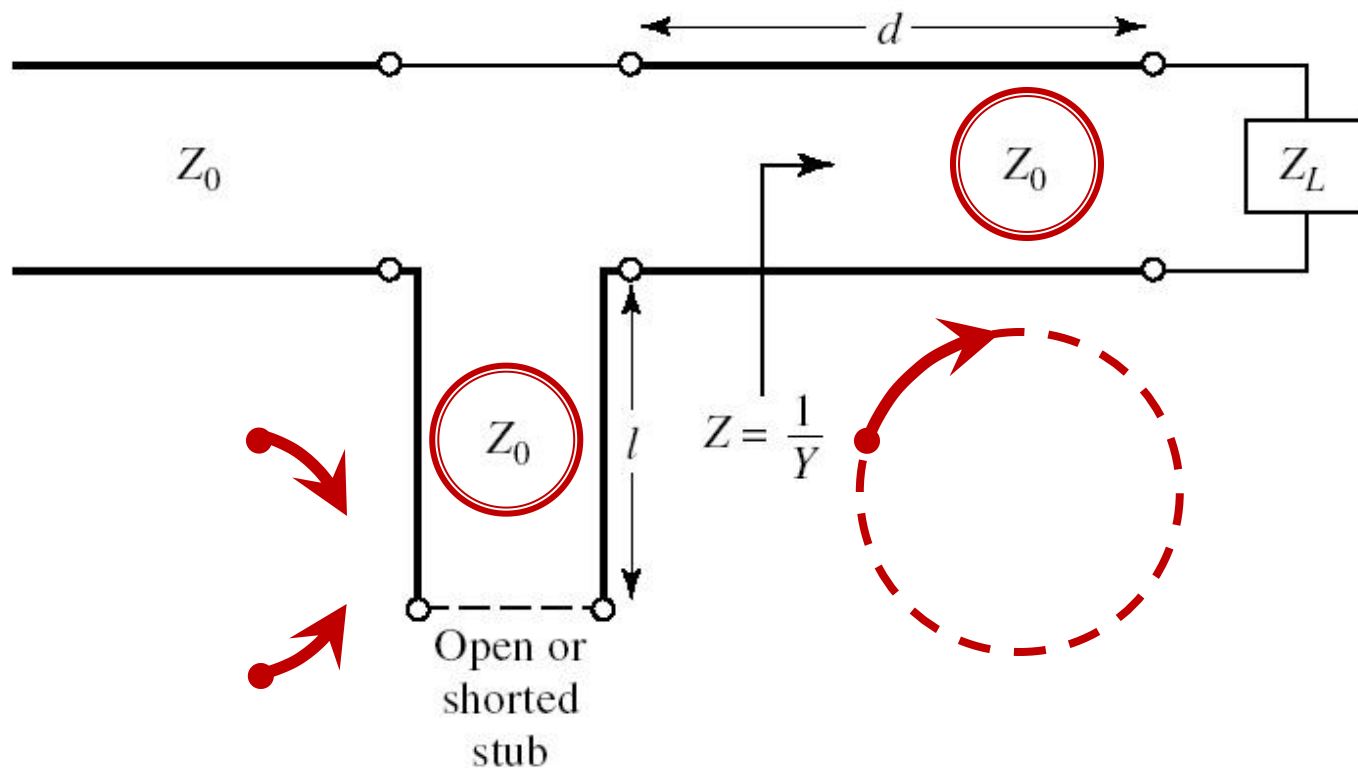- Series Stub
- difficult to realize in single conductor line technologies (microstrip)




Analytical solutions


Exam / Project

Case 1, Shunt Stub

- Shunt Stub

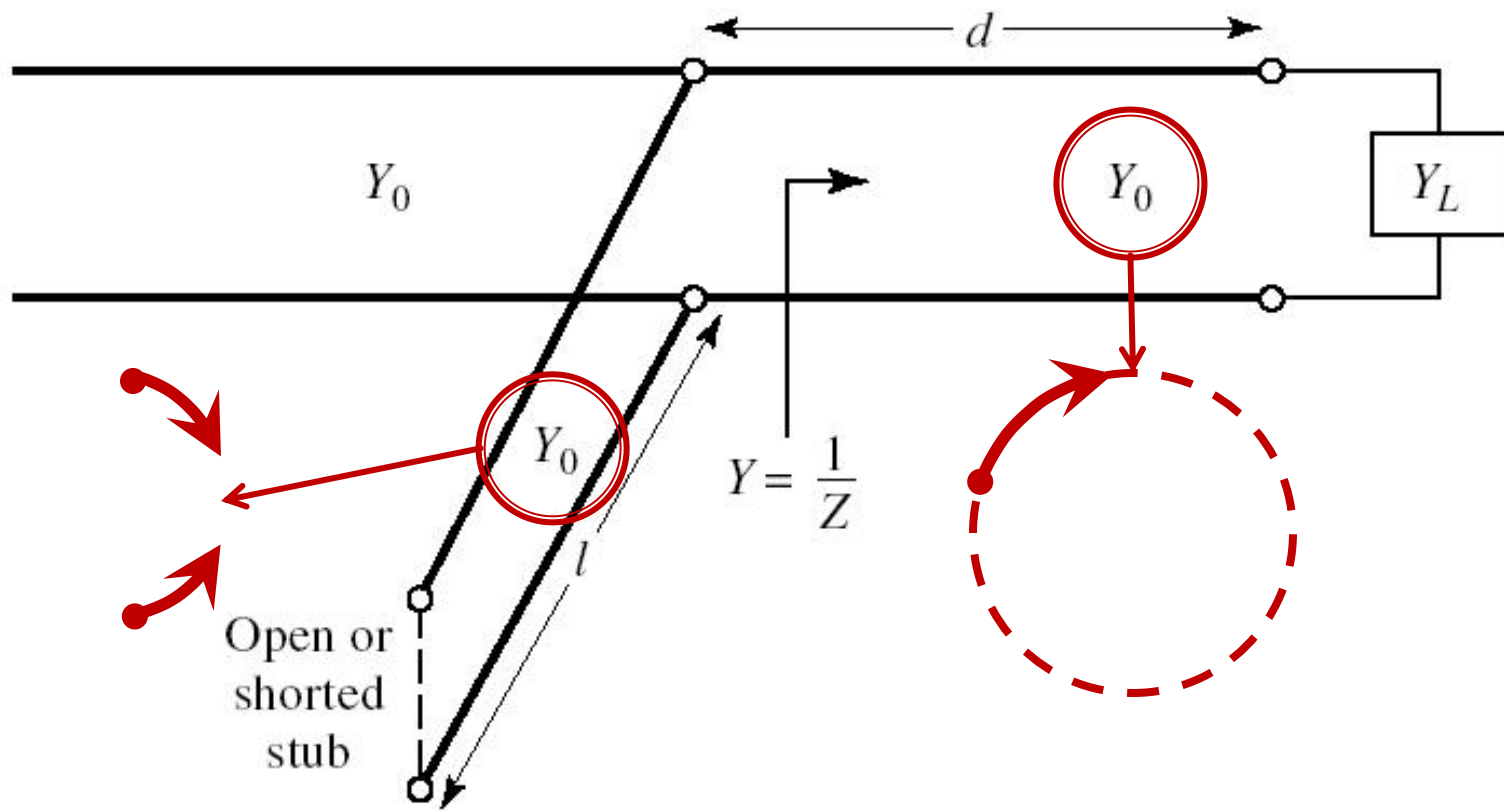

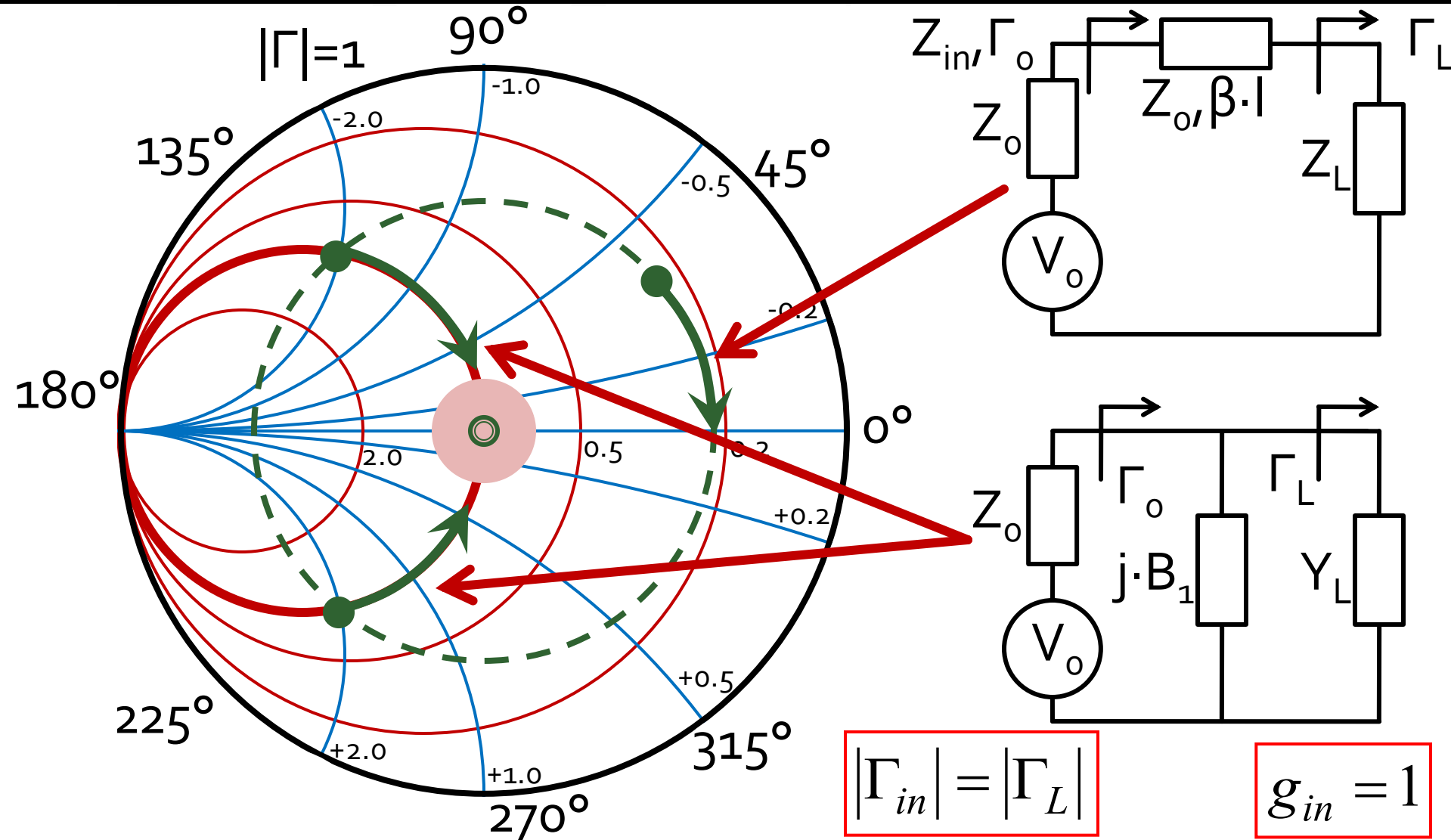Matching, series line + shunt susceptance



Analytical solution, usage

$$\cos(\varphi + 2\theta) = -|\Gamma_S|$$

$$\Gamma_S = 0.593 \angle 46.85^\circ$$

$$\theta_{sp} = \beta \cdot l = \tan^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$|\Gamma_S| = 0.593; \quad \varphi = 46.85^\circ \quad \cos(\varphi + 2\theta) = -0.593 \Rightarrow (\varphi + 2\theta) = \pm 126.35^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

- **“+” solution** ↓

$$(46.85^\circ + 2\theta) = +126.35^\circ \quad \theta = +39.7^\circ \quad \text{Im } y_S = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.472$$

$$\theta_{sp} = \tan^{-1}(\text{Im } y_S) = -55.8^\circ (+180^\circ) \rightarrow \theta_{sp} = 124.2^\circ$$

- **“-” solution** ↓

$$(46.85^\circ + 2\theta) = -126.35^\circ \quad \theta = -86.6^\circ (+180^\circ) \rightarrow \theta = 93.4^\circ$$

$$\text{Im } y_S = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +1.472 \quad \theta_{sp} = \tan^{-1}(\text{Im } y_S) = 55.8^\circ$$

Analytical solution, usage

$$(\varphi + 2\theta) = \begin{cases} +126.35^\circ \\ -126.35^\circ \end{cases} \quad \theta = \begin{cases} 39.7^\circ \\ 93.4^\circ \end{cases} \quad \text{Im}[y_s(\theta)] = \begin{cases} -1.472 \\ +1.472 \end{cases} \quad \theta_{sp} = \begin{cases} -55.8^\circ + 180^\circ = 124.2^\circ \\ +55.8^\circ \end{cases}$$



- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **shunt stub** equation

$$l_1 = \frac{39.7^\circ}{360^\circ} \cdot \lambda = 0.110 \cdot \lambda$$

$$l_2 = \frac{124.2^\circ}{360^\circ} \cdot \lambda = 0.345 \cdot \lambda$$


$$l_1 = \frac{93.4^\circ}{360^\circ} \cdot \lambda = 0.259 \cdot \lambda$$
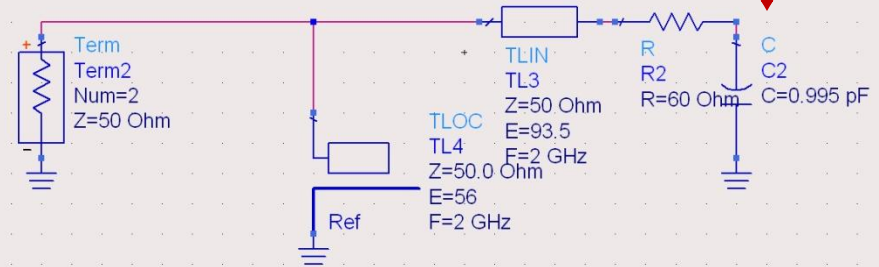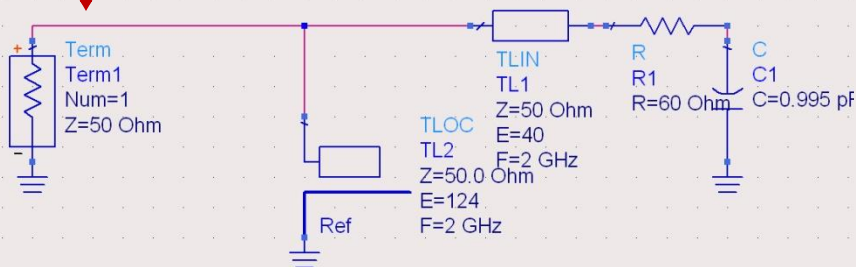
$$l_2 = \frac{55.8^\circ}{360^\circ} \cdot \lambda = 0.155 \cdot \lambda$$






Case 2, Series Stub

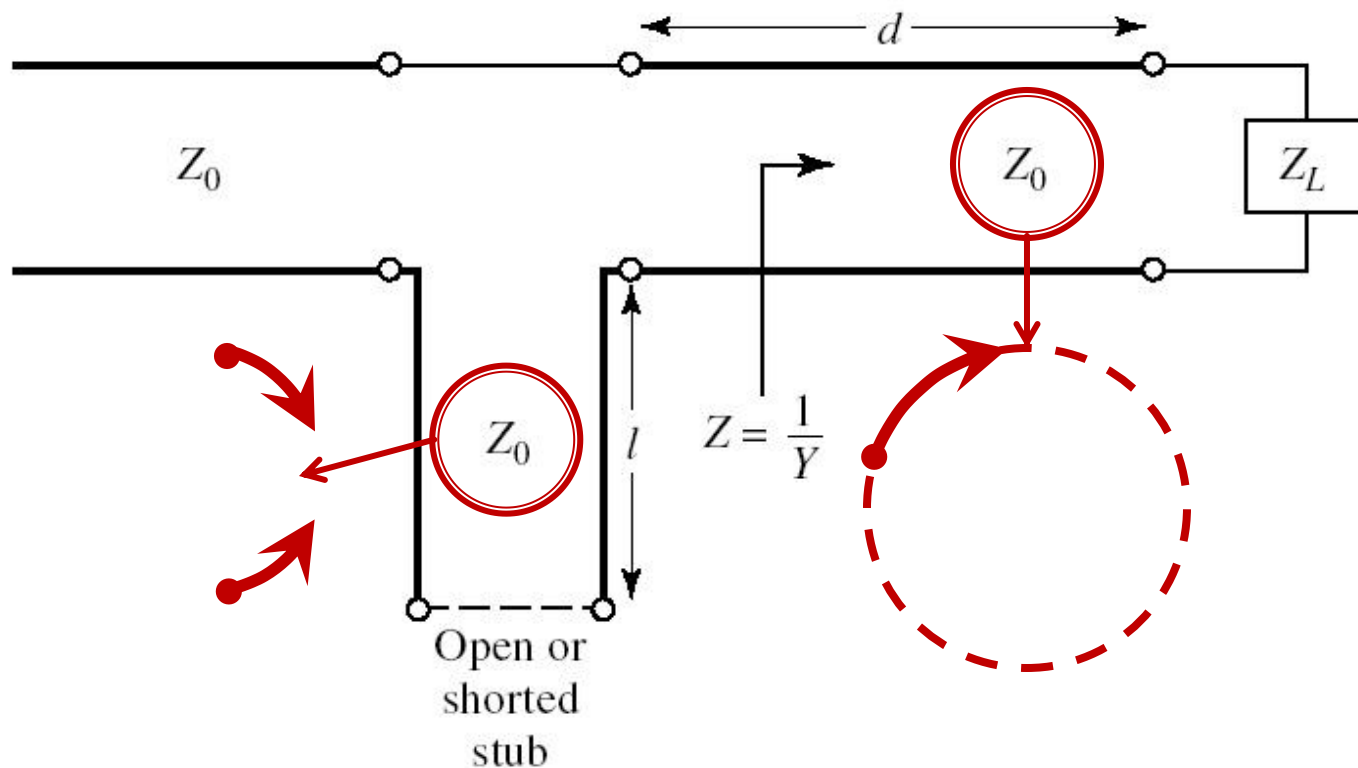- Series Stub
- difficult to realize in single conductor line technologies (microstrip)



Matching, series line + series reactance

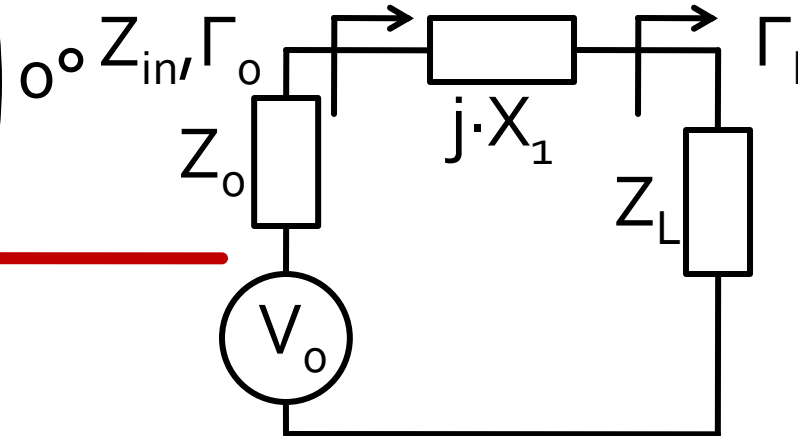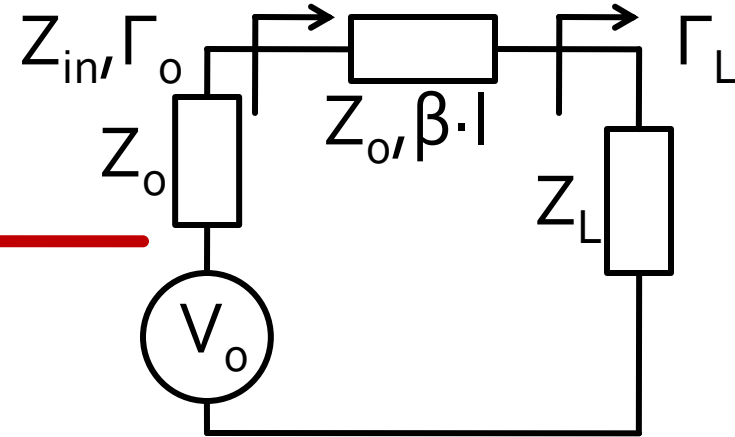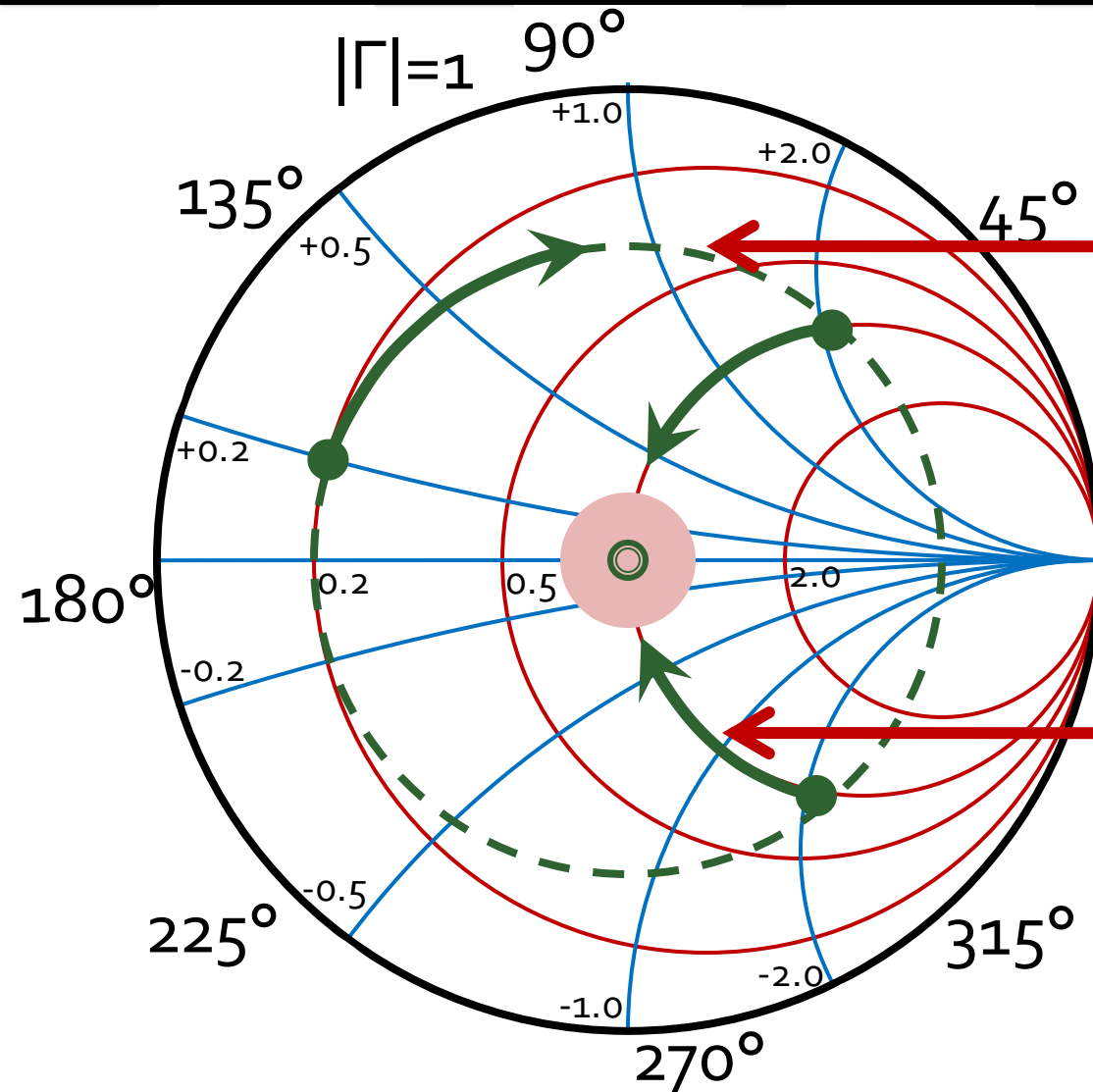

$$|\Gamma_{in}| = |\Gamma_L|$$

$$r_{in} = 1$$

Analytical solution, usage

$$\cos(\varphi + 2\theta) = |\Gamma_S|$$

$$\theta_{ss} = \beta \cdot l = \cot^{-1} \frac{\mp 2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}}$$

$$\Gamma_S = 0.555 \angle -29.92^\circ$$

$$|\Gamma_S| = 0.555; \quad \varphi = -29.92^\circ \quad \cos(\varphi + 2\theta) = 0.555 \Rightarrow (\varphi + 2\theta) = \pm 56.28^\circ$$

- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

- **"+" solution** ↓

$$(-29.92^\circ + 2\theta) = +56.28^\circ \quad \theta = 43.1^\circ \quad \text{Im } z_S = \frac{+2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = +1.335$$

$$\theta_{ss} = -\cot^{-1}(\text{Im } z_S) = -36.8^\circ (+180^\circ) \rightarrow \theta_{ss} = 143.2^\circ$$

- **"-" solution** ↓

$$(-29.92^\circ + 2\theta) = -56.28^\circ \quad \theta = -13.2^\circ (+180^\circ) \rightarrow \theta = 166.8^\circ$$

$$\text{Im } z_S = \frac{-2 \cdot |\Gamma_S|}{\sqrt{1 - |\Gamma_S|^2}} = -1.335 \quad \theta_{ss} = -\cot^{-1}(\text{Im } z_S) = 36.8^\circ$$

Analytical solution, usage

$$(\varphi + 2\theta) = \begin{cases} +56.28^\circ \\ -56.28^\circ \end{cases} \quad \theta = \begin{cases} 43.1^\circ \\ 166.8^\circ \end{cases} \quad \text{Im}[z_s(\theta)] = \begin{cases} +1.335 \\ -1.335 \end{cases} \quad \theta_{ss} = \begin{cases} -36.8^\circ + 180^\circ = 143.2^\circ \\ +36.8^\circ \end{cases}$$

- We choose **one** of the two possible solutions
- The **sign** (+/-) chosen for the **series line** equation imposes the **sign** used for the **series stub** equation

$$l_1 = \frac{43.1^\circ}{360^\circ} \cdot \lambda = 0.120 \cdot \lambda$$

$$l_2 = \frac{143.2^\circ}{360^\circ} \cdot \lambda = 0.398 \cdot \lambda$$

$$l_1 = \frac{166.8^\circ}{360^\circ} \cdot \lambda = 0.463 \cdot \lambda$$

$$l_2 = \frac{36.8^\circ}{360^\circ} \cdot \lambda = 0.102 \cdot \lambda$$



Stub, observations

- adding or subtracting **180°** ($\lambda/2$) doesn't change the result (full rotation around the Smith Chart)

$$E = \beta \cdot l = \pi = 180^\circ \quad l = k \cdot \frac{\lambda}{2}, \forall k \in \mathbf{N}$$

- if the lines/stubs result with **negative** "length"/ "electrical length" we add $\lambda/2$ / 180° to obtain physically realizable lines
- adding or subtracting **90°** ($\lambda/4$) change the stub impedance:

$$Z_{in,sc} = j \cdot Z_0 \cdot \tan \beta \cdot l \quad \Leftrightarrow \quad Z_{in,g} = -j \cdot Z_0 \cdot \cot \beta \cdot l$$


- for the stub we can add or subtract 90° ($\lambda/4$) while in the same time changing **open-circuit** \Leftrightarrow **short-circuit**

Microwave Amplifiers

Course Topics

- Transmission lines
- Impedance matching and tuning
- Directional couplers
- Power dividers
- **Microwave amplifier design**
- Microwave filters
- ~~Oscillators and mixers?~~

Amplifier as two-port

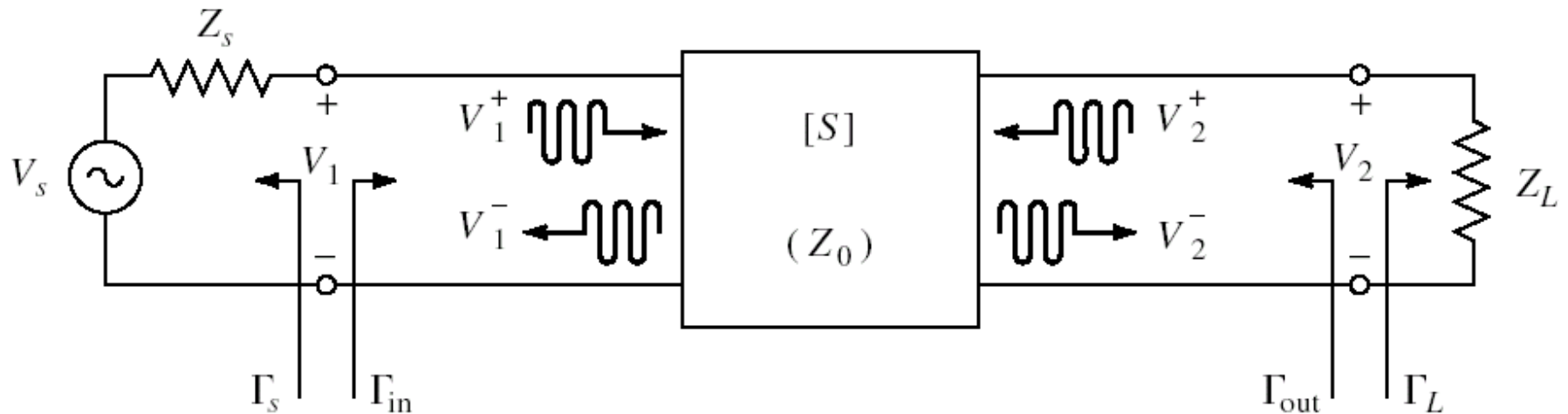

- Characterized with S parameters
- normalized at Z_0 (implicit 50Ω)
- Datasheets: S parameters for specific bias conditions

Datasheets



NE46100 / NE46134

NPN MEDIUM POWER MICROWAVE TRANSISTOR


FEATURES

- HIGH DYNAMIC RANGE
- LOW IM DISTORTION: -40 dBc
- HIGH OUTPUT POWER : 27.5 dBm at TYP
- LOW NOISE: 1.5 dB TYP at 500 MHz
- LOW COST

DESCRIPTION

The NE461 series of NPN silicon epitaxial bipolar transistors is designed for medium power applications requiring high dynamic range. This device exhibits an outstanding combination of high gain and low intermodulation distortion, as well as low noise figure. The NE461 series offers excellent performance and reliability at low cost through titanium, platinum, gold metallization system and direct nitride passivation of the surface of the chip. Devices are available in a low cost surface mount package (SOT-89) as well as in chip form.

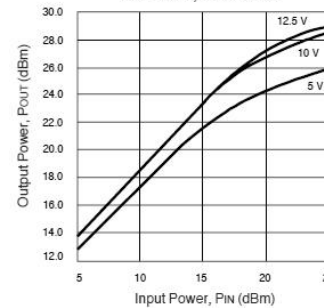NE46134
TYPICAL OUTPUT POWER
vs. INPUT POWER
f = 1.0 GHz, I_c = 100 mA



ELECTRICAL CHARACTERISTICS (T_A = 25°C)

SYMBOLS	PARAMETERS AND CONDITIONS	UNITS	NE46100			NE46134 2SC4536 34		
			MIN	TYP	MAX	MIN	TYP	MAX
f _T	Gain Bandwidth Product at V _{CE} = 10 V, I _c = 100 mA	GHz		5.5			5.5	
N _{FMN}	Minimum Noise Figure ³ at V _{CE} = 10 V, I _c = 50 mA, 500 MHz V _{CE} = 10 V, I _c = 50 mA, 1 GHz	dB		1.5			1.5	
GL	Linear Gain, V _{CE} = 12.5 V, I _c = 100 mA, 2.0 GHz V _{CE} = 12.5 V, I _c = 100 mA, 1.0 GHz	dB		9.0			8.0	
IS _{21E1} ²	Insertion Power Gain at 10 V, 50 mA, f = 1.0 GHz	dB		10.0		5.5	7.0	
h _{FE}	DC Current Gain ² at V _{CE} = 10 V, I _c = 50 mA			40		200	40	200
I _{CBO}	Collector Cutoff Current at V _{CB} = 20 V, I _E = 0 mA	μA				5.0		5.0
I _{EB0}	Emitter Cutoff Current at V _{EB} = 2 V, I _C = 0 mA	μA				5.0		5.0
P _{1dB}	Output Power at 1 dB Compression, V _{CE} = 12.5 V, I _c = 100 mA, 2.0 GHz V _{CE} = 12.5 V, I _c = 100 mA, 1.0 GHz	dBm	27.0					27.5
IM ₃	Intermodulation Distortion, 10 V, 100 mA, F ₁ = 1.0 GHz, F ₂ = 0.99 GHz	dBm						

Datasheets

NE46100




VCE = 5 V, Ic = 50 mA

FREQUENCY (MHz)	S11		S21		S12		S22		K	MAG ² (dB)
	MAG	ANG	MAG	ANG	MAG	ANG	MAG	ANG		
100	0.778	-137	26.776	114	0.028	30	0.555	-102	0.16	29.8
200	0.815	-159	14.407	100	0.035	29	0.434	-135	0.36	26.2
500	0.826	-177	5.855	84	0.040	38	0.400	-162	0.75	21.7
800	0.827	176	3.682	76	0.052	43	0.402	-169	0.91	18.5
1000	0.826	173	2.963	71	0.058	47	0.405	-172	1.02	16.3
1200	0.825	170	2.441	66	0.064	47	0.412	-174	1.08	14.0
1400	0.820	167	2.111	61	0.069	47	0.413	-176	1.17	12.4
1600	0.828	165	1.863	57	0.078	54	0.426	-177	1.15	11.4
1800	0.827	162	1.671	53	0.087	50	0.432	-178	1.14	10.6
2000	0.828	159	1.484	49	0.093	50	0.431	-180	1.17	9.5
2500	0.822	153	1.218	39	0.11	48	0.462	177	1.18	7.8
3000	0.818	148	1.010	30	0.135	46	0.490	174	1.16	6.3
3500	0.824	142	0.876	21	0.147	44	0.507	170	1.16	5.3
4000	0.812	137	0.762	13	0.168	38	0.535	167	1.14	4.3

VCE = 5 V, Ic = 100 mA

100	0.778	-144	27.669	111	0.027	35	0.523	-114	0.27	30.2
200	0.820	-164	14.559	97	0.029	29	0.445	-144	0.42	27.0
500	0.832	-179	5.885	84	0.035	38	0.435	-166	0.81	22.2
800	0.833	175	3.691	76	0.048	45	0.435	-173	0.95	18.8
1000	0.831	172	2.980	71	0.056	51	0.437	-176	1.05	16.0
1200	0.836	169	2.464	67	0.061	52	0.432	-178	1.11	14.0
1400	0.829	166	2.121	61	0.072	53	0.447	-180	1.12	12.6
1600	0.831	164	1.867	58	0.080	54	0.445	179	1.14	11.4



S parameters for transistors

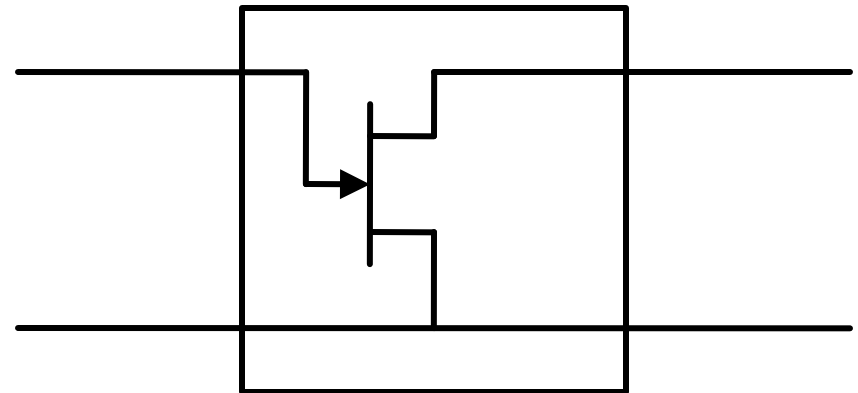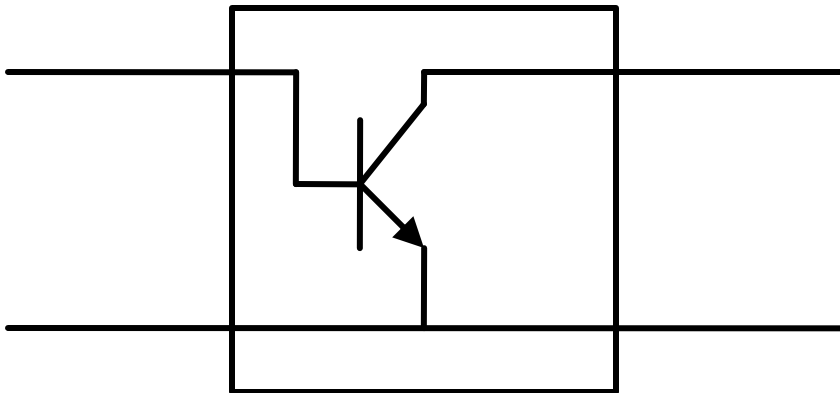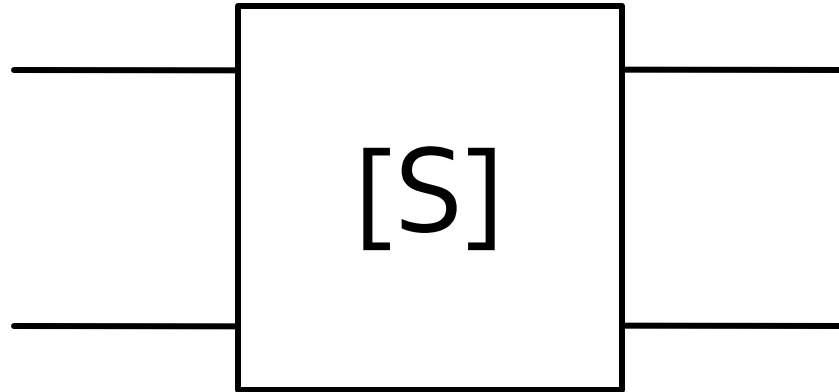

Datasheets

NE46100, NE46134

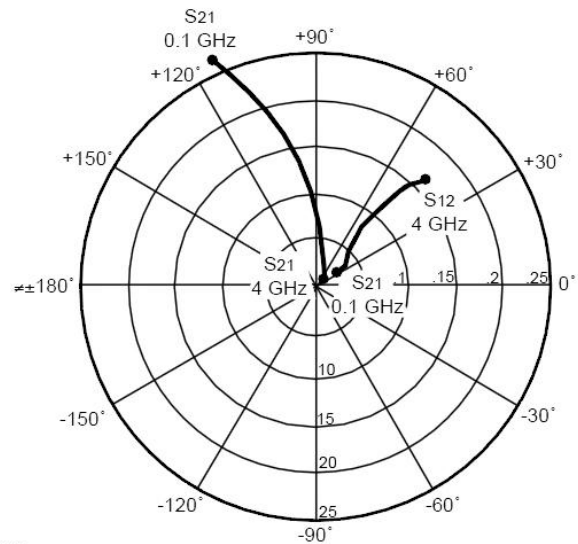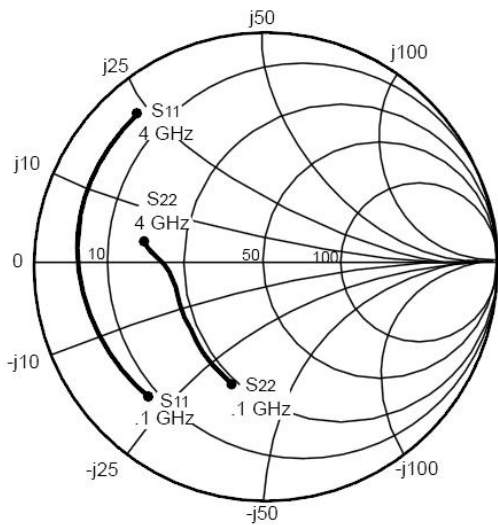TYPICAL COMMON EMITTER SCATTERING PARAMETERS¹ ($T_A = 25^\circ\text{C}$)




Coordinates in Ohms
Frequency in GHz
 $V_{CE} = 5\text{ V}$, $I_c = 50\text{ mA}$

S2P - Touchstone

- Touchstone file format (*.s2p)

```
! SIEMENS Small Signal Semiconductors
! VDS = 3.5 V   ID = 15 mA
# GHz S MA R 50
! f      S11      S21      S12      S22
! GHz   MAG ANG   MAG ANG   MAG ANG   MAG ANG
1.000 0.9800 -18.0 2.230 157.0 0.0240 74.0 0.6900 -15.0
2.000 0.9500 -39.0 2.220 136.0 0.0450 57.0 0.6600 -30.0
3.000 0.8900 -64.0 2.210 110.0 0.0680 40.0 0.6100 -45.0
4.000 0.8200 -89.0 2.230 86.0 0.0850 23.0 0.5600 -62.0
5.000 0.7400 -115.0 2.190 61.0 0.0990 7.0 0.4900 -80.0
6.000 0.6500 -142.0 2.110 36.0 0.1070 -10.0 0.4100 -98.0
!
! f      Fmin  Gammaopt  rn/50
! GHz   dB   MAG ANG   -
2.000   1.00 0.72 27 0.84
4.000   1.40 0.64 61 0.58
```

Amplifier as two-port

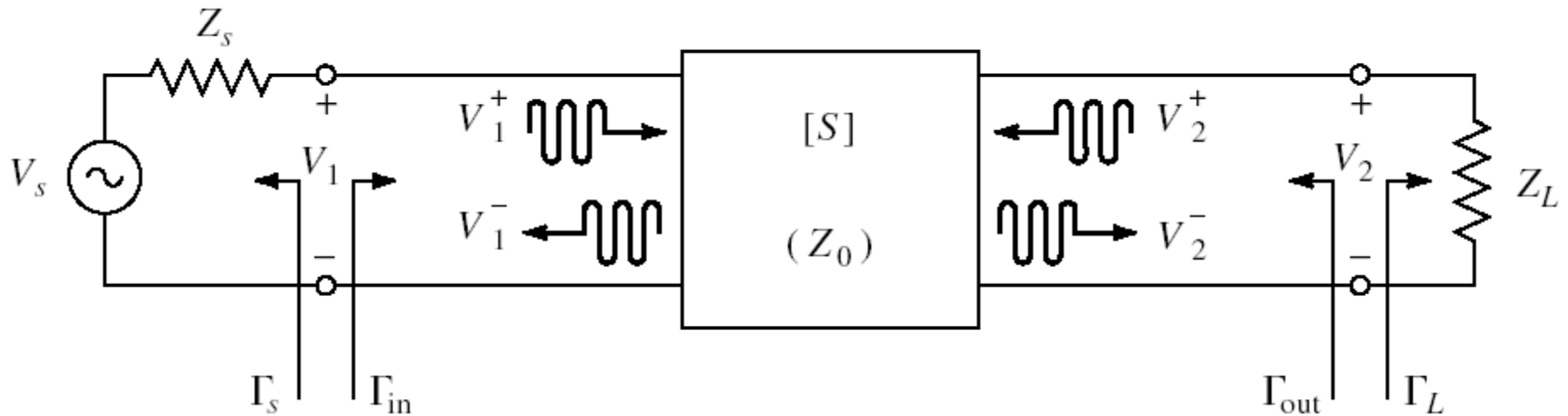


$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \Gamma_S = \frac{Z_S - Z_0}{Z_S + Z_0} \quad \begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$\Gamma_L = \frac{V_2^+}{V_2^-} \quad V_1^- = S_{11} \cdot V_1^+ + S_{12} \cdot V_2^+ = S_{11} \cdot V_1^+ + S_{12} \cdot \Gamma_L \cdot V_2^-$$

$$V_2^- = S_{21} \cdot V_1^+ + S_{22} \cdot V_2^+ = S_{21} \cdot V_1^+ + S_{22} \cdot \Gamma_L \cdot V_2^-$$

Amplifier as two-port

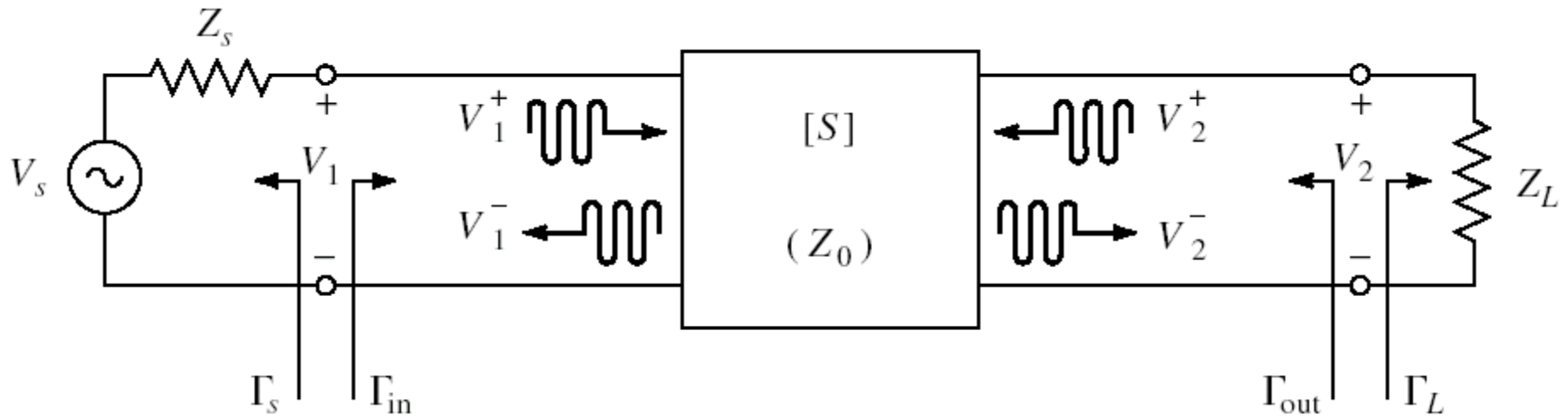

$$V_1^- = S_{11} \cdot V_1^+ + S_{12} \cdot V_2^+ = S_{11} \cdot V_1^+ + S_{12} \cdot \Gamma_L \cdot V_2^-$$


$$V_2^- = S_{21} \cdot V_1^+ + S_{22} \cdot V_2^+ = S_{21} \cdot V_1^+ + S_{22} \cdot \Gamma_L \cdot V_2^-$$

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

■ similarly

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

Amplifier as two-port

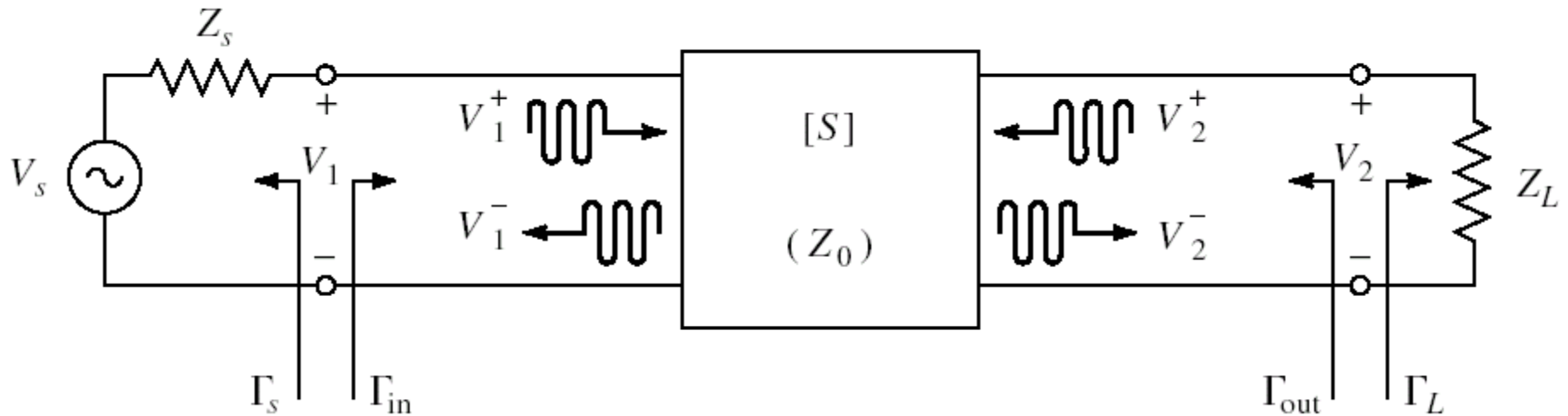


$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$$

Power / Matching

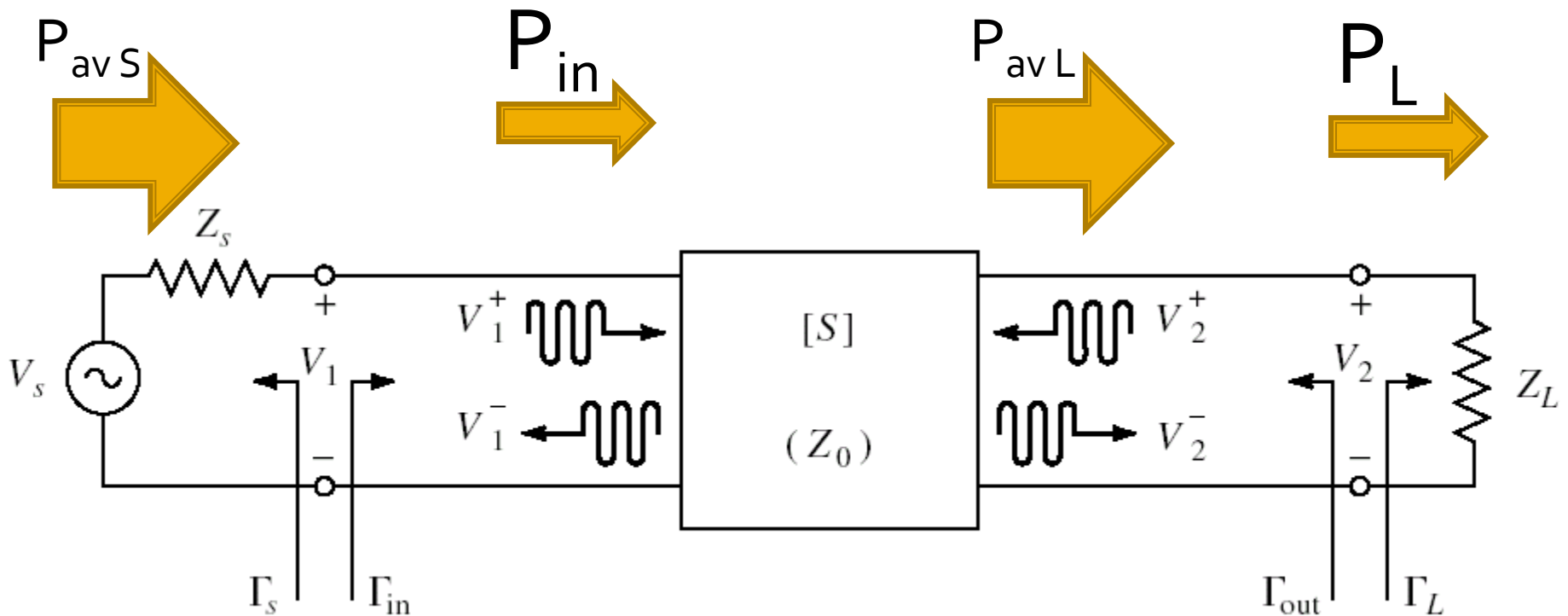- Two ports in which matching influences the power transfer



Signal power

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$$

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$V_1 = \frac{V_S \cdot Z_{in}}{Z_S + Z_{in}} = V_1^+ + V_1^- = V_1^+ \cdot (1 + \Gamma_{in})$$

$$V_1^+ = \frac{V_S}{2} \frac{(1 - \Gamma_S)}{(1 - \Gamma_S \cdot \Gamma_{in})}$$

■ **L3** $P_{in} = \frac{1}{2 \cdot Z_0} \cdot |V_1^+|^2 \cdot (1 - |\Gamma_{in}|^2)$

$$P_L = \frac{1}{2 \cdot Z_0} \cdot |V_2^-|^2 \cdot (1 - |\Gamma_L|^2)$$

$$P_{in} = \frac{|V_S|^2}{8 \cdot Z_0} \cdot \frac{|1 - \Gamma_S|^2}{|1 - \Gamma_S \cdot \Gamma_{in}|^2} (1 - |\Gamma_{in}|^2)$$

$$V_2^- = S_{21} \cdot V_1^+ + S_{22} \cdot V_2^+ = S_{21} \cdot V_1^+ + S_{22} \cdot \Gamma_L \cdot V_2^-$$

$$V_2^- = \frac{S_{21} \cdot V_1^+}{1 - S_{22} \cdot \Gamma_L}$$

$$P_L = \frac{|V_1^+|^2}{2 \cdot Z_0} \cdot \frac{|S_{21}|^2}{|1 - S_{22} \cdot \Gamma_L|^2} (1 - |\Gamma_L|^2)$$

$$P_L = \frac{|V_S|^2}{8 \cdot Z_0} \cdot \frac{|S_{21}|^2 \cdot (1 - |\Gamma_L|^2)}{|1 - S_{22} \cdot \Gamma_L|^2} \cdot \frac{|1 - \Gamma_S|^2}{|1 - \Gamma_S \cdot \Gamma_{in}|^2}$$

Signal power

- Signal power

$$P_{in} = \frac{|V_S|^2}{8 \cdot Z_0} \cdot \frac{|1 - \Gamma_S|^2}{|1 - \Gamma_S \cdot \Gamma_{in}|^2} \left(1 - |\Gamma_{in}|^2\right)$$

$$P_L = \frac{|V_S|^2}{8 \cdot Z_0} \cdot \frac{|S_{21}|^2 \cdot (1 - |\Gamma_L|^2)}{|1 - S_{22} \cdot \Gamma_L|^2} \cdot \frac{|1 - \Gamma_S|^2}{|1 - \Gamma_S \cdot \Gamma_{in}|^2}$$

- Power available from the source

$$P_{avS} = P_{in}|_{\Gamma_{in}=\Gamma_S^*} = \frac{|V_S|^2}{8 \cdot Z_0} \cdot \frac{|1 - \Gamma_S|^2}{(1 - |\Gamma_S|^2)}$$

- Power available on the load (from the network)

$$P_{avL} = P_L|_{\Gamma_L=\Gamma_{out}^*} = \frac{|V_S|^2}{8 \cdot Z_0} \cdot \frac{|S_{21}|^2 \cdot |1 - \Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2 \cdot (1 - |\Gamma_{out}|^2)}$$

Two-Port Power Gains

- Power Gain

$$G = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) \cdot |1 - S_{22} \cdot \Gamma_L|^2}$$

$$P_{in} = P_{in}(\Gamma_S, \Gamma_{in}(\Gamma_L), S)$$

$$P_L = P_L(\Gamma_S, \Gamma_{in}(\Gamma_L), S)$$

- The **actual** power gain **introduced** by the amplifier is less important because a higher gain may be accompanied by a **decrease** in input power (power actually drained from the source)
- We prefer to characterize the amplifier effect looking to the **power actually delivered to the load** in relation to the power **available from the source** (which is a constant)

Two-Port Power Gains

- **Available** power gain

$$G_A = \frac{P_{av L}}{P_{av S}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2)}{|1 - S_{22} \cdot \Gamma_L|^2 \cdot (1 - |\Gamma_{out}|^2)}$$

- **Transducer** power gain

$$G_T = \frac{P_L}{P_{av S}} = \frac{|S_{21}|^2 \cdot (1 - |\Gamma_S|^2) \cdot (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \cdot \Gamma_{in}|^2 \cdot |1 - S_{22} \cdot \Gamma_L|^2}$$

$$\Gamma_{in} = \Gamma_{in}(\Gamma_L)$$


- **Unilateral transducer** power gain

$$G_{TU} = |S_{21}|^2 \cdot \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \cdot \Gamma_S|^2} \cdot \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \cdot \Gamma_L|^2}$$

$$S_{12} \cong 0 \quad \Gamma_{in} = S_{11}$$

Input and output can be treated independently

Amplifier as two-port

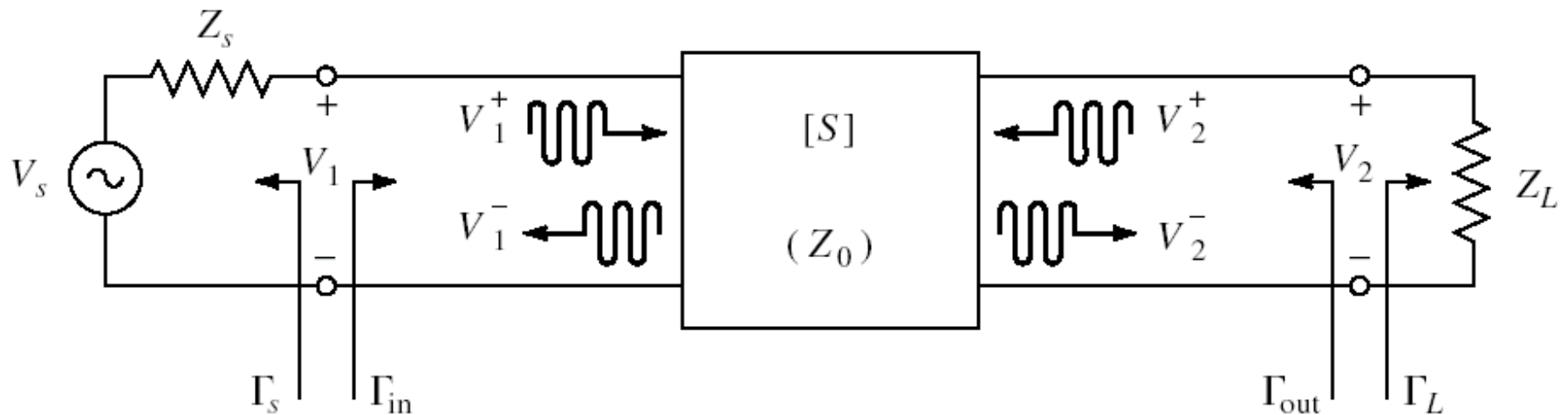


- For an amplifier two-port we are interested in:
 - stability
 - power gain
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)

Microwave Amplifiers

Stability

Amplifier as two-port

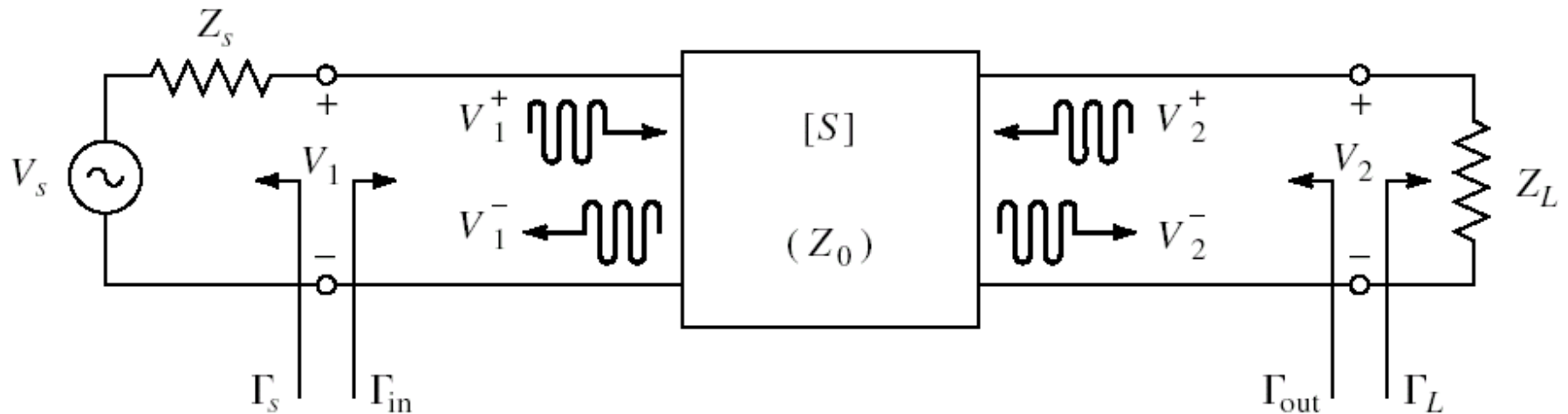

- For an amplifier two-port we are interested in:
 - **stability**
 - power gain
 - noise (sometimes – small signals)
 - linearity (sometimes – large signals)

Stability

- L7 $\Gamma = \Gamma_r + j \cdot \Gamma_i$ $r_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$
 Z_{in} $\Gamma_{in} = \Gamma_r + j \cdot \Gamma_i$
- instability
 $\text{Re}\{Z_{in}\} < 0 \iff 1 - \Gamma_r^2 - \Gamma_i^2 < 0 \quad \Gamma_r^2 + \Gamma_i^2 > 1 \quad |\Gamma_{in}| > 1$
- stability, Z_{in}
 - conditions to be met by Γ_L to achieve (input) stability
 $|\Gamma_{in}| < 1 \quad \left| S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \right| < 1$
- similarly Z_{out}
 - conditions to be met by Γ_S to achieve (output) stability

Stability

$$|\Gamma_{in}| < 1 \quad \left| S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \right| < 1$$

- We can calculate conditions to be met by Γ_L to achieve stability

$$|\Gamma_{out}| < 1 \quad \left| S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S} \right| < 1$$

- We can calculate conditions to be met by Γ_S to achieve stability

Stability

$$|\Gamma_{in}| < 1 \quad \left| S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \right| < 1$$

- The limit between stability/instability

$$|\Gamma_{in}| = 1 \quad \left| S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \right| = 1$$

$$|S_{11} \cdot (1 - S_{22} \cdot \Gamma_L) + S_{12} \cdot S_{21} \cdot \Gamma_L| = |1 - S_{22} \cdot \Gamma_L|$$

- determinant of the S matrix $\Delta = S_{11} \cdot S_{22} - S_{12} \cdot S_{21}$

$$|S_{11} - \Delta \cdot \Gamma_L| = |1 - S_{22} \cdot \Gamma_L|$$

$$|S_{11} - \Delta \cdot \Gamma_L|^2 = |1 - S_{22} \cdot \Gamma_L|^2$$

Stability

$$|S_{11} - \Delta \cdot \Gamma_L|^2 = |1 - S_{22} \cdot \Gamma_L|^2$$

$$a \cdot a^* = |a| \cdot e^{j\theta} \cdot |a| \cdot e^{-j\theta} = |a|^2$$

$$|a + b|^2 = (a + b) \cdot (a + b)^* = (a + b) \cdot (a^* + b^*) = \underbrace{|a|^2} + \underbrace{|b|^2} + \underbrace{a^* \cdot b + a \cdot b^*}$$

$$|S_{11}|^2 + |\Delta|^2 \cdot |\Gamma_L|^2 - (\Delta \cdot \Gamma_L \cdot S_{11}^* + \Delta^* \cdot \Gamma_L^* \cdot S_{11}) = 1 + |S_{22}|^2 \cdot |\Gamma_L|^2 - (S_{22}^* \cdot \Gamma_L^* + S_{22} \cdot \Gamma_L)$$

$$(|S_{22}|^2 - |\Delta|^2) \cdot \Gamma_L \cdot \Gamma_L^* - (S_{22} - \Delta \cdot S_{11}^*) \cdot \Gamma_L - (S_{22}^* - \Delta^* \cdot S_{11}) \cdot \Gamma_L^* = |S_{11}|^2 - 1$$

$$\Gamma_L \cdot \Gamma_L^* - \frac{(S_{22} - \Delta \cdot S_{11}^*) \cdot \Gamma_L + (S_{22}^* - \Delta^* \cdot S_{11}) \cdot \Gamma_L^*}{|S_{22}|^2 - |\Delta|^2} = \frac{|S_{11}|^2 - 1}{|S_{22}|^2 - |\Delta|^2} \quad / \quad + \frac{|S_{22} - \Delta \cdot S_{11}^*|^2}{(|S_{22}|^2 - |\Delta|^2)^2}$$

$$\left| \Gamma_L - \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \right|^2 = \frac{|S_{11}|^2 - 1}{|S_{22}|^2 - |\Delta|^2} + \frac{|S_{22} - \Delta \cdot S_{11}^*|^2}{(|S_{22}|^2 - |\Delta|^2)^2}$$

Plan complex – geometrie analitica

■ solutii

$$(x - x_0)^2 + (y - y_0)^2 = R^2$$

$$a = x + j \cdot y$$

$$C = x_0 + j \cdot y_0$$


$$D(a, C) = |a - C| = R$$

$$a = x_1 + j \cdot y_1$$


$$b = x_2 + j \cdot y_2$$

$$D(a, b) = |a - b| = |b - a|$$
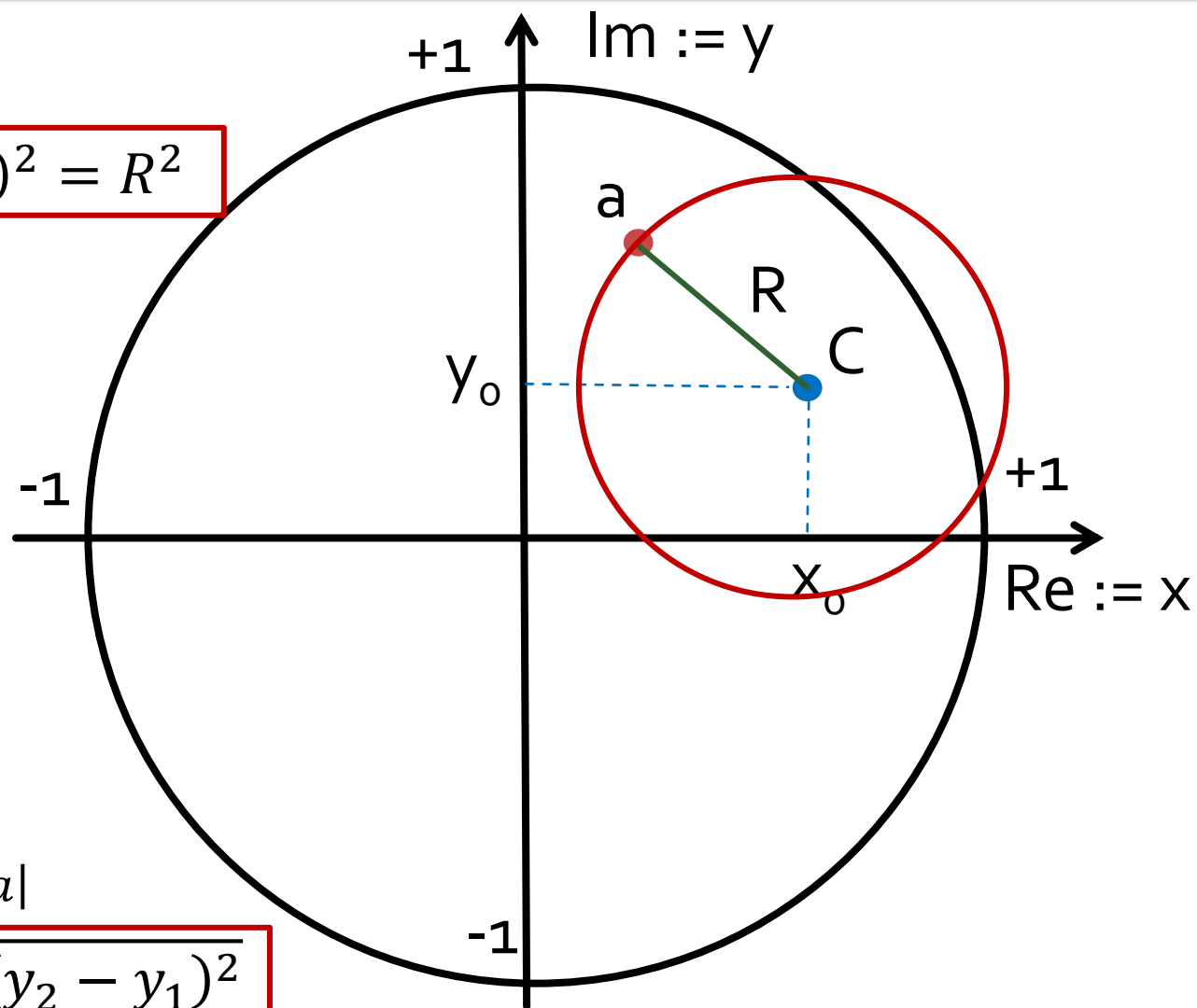
$$D = \sqrt{(x_2 - x_1)^2 + (y_2 - y_1)^2}$$



Stability

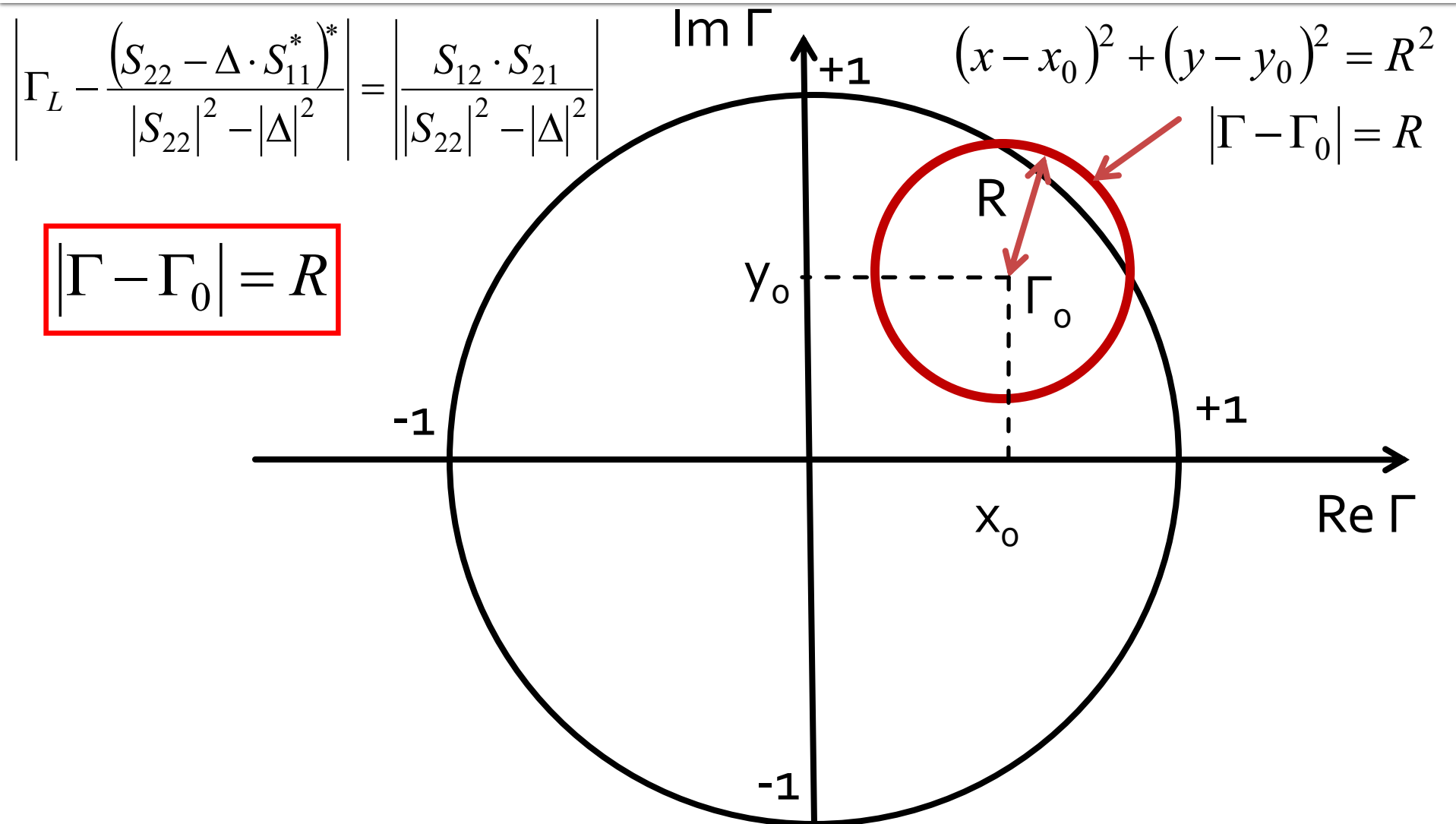

Output stability circle (CSOUT)

$$\left| \Gamma_L - \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12} \cdot S_{21}}{|S_{22}|^2 - |\Delta|^2} \right| \quad |\Gamma_L - C_L| = R_L$$

- We obtain the equation of a circle in the complex plane, which represents the locus of Γ_L for the **limit between stability and instability** ($|\Gamma_{in}| = 1$)
- This circle is the **output stability circle** (Γ_L)

$$C_L = \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \quad R_L = \frac{|S_{12} \cdot S_{21}|}{\left| |S_{22}|^2 - |\Delta|^2 \right|}$$

Input stability circle (CSIN)


- Similarly $|\Gamma_{out}|=1$ $\left| S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S} \right| = 1$
- We obtain the equation of a circle in the complex plane, which represents the locus of Γ_S for the **limit between stability and instability** ($|\Gamma_{out}| = 1$)
- This circle is the **input stability circle** (Γ_S)

$$C_S = \frac{(S_{11} - \Delta \cdot S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \quad R_S = \frac{|S_{12} \cdot S_{21}|}{\left| |S_{11}|^2 - |\Delta|^2 \right|}$$


Output stability circle (CSOUT)

- The **output stability circle** represents the locus of Γ_L for the **limit between stability and instability** ($|\Gamma_{in}| = 1$)
- The circle divides the complex planes in two areas, the **inside** and the **outside** of the circle
- The two areas will represent the locus of Γ_L for stability ($|\Gamma_{in}| < 1$) / instability ($|\Gamma_{in}| > 1$)

Output stability circle (CSOUT)

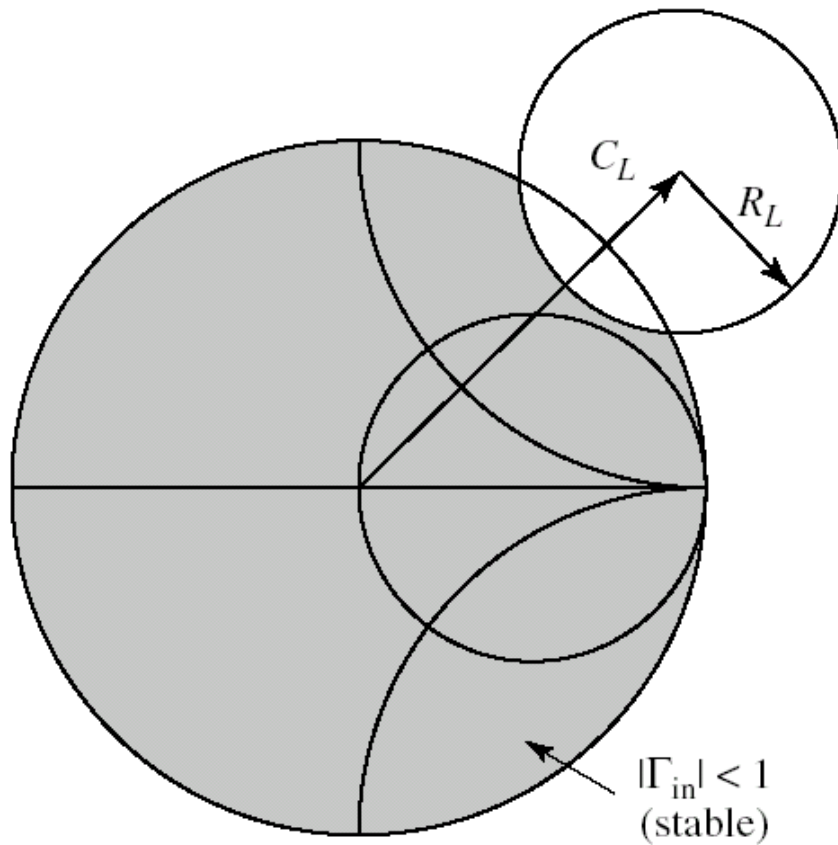

(a)

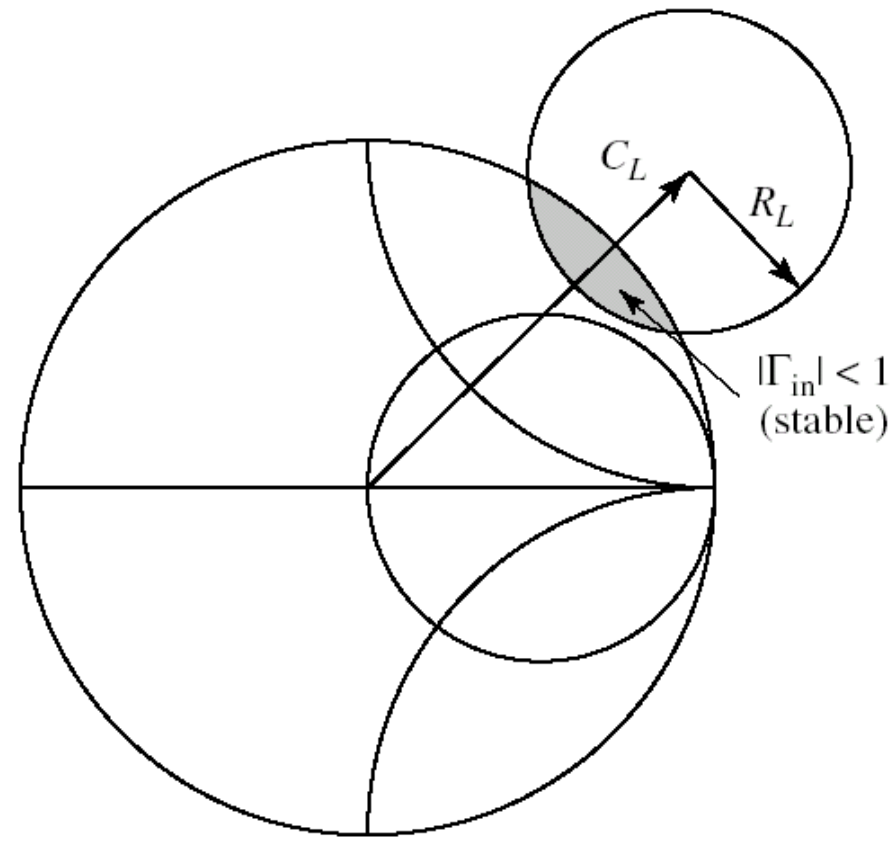

(b)

- Two cases possible: (a) stable outside/ (b) stable inside

Output stability circle (CSOUT)

- Identification of the stability / instability regions
 - The center of the Smith Chart in Γ_L complex plane corresponds to $\Gamma_L = 0$
 - Input reflection coefficient

$$\Gamma_{in} = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L} \quad \Gamma_{in}|_{\Gamma_L=0} = S_{11} \quad |\Gamma_{in}|_{\Gamma_L=0} = |S_{11}|$$

- A decision can be made based on $|S_{11}|$ value and on the position of the center of the Smith chart (origin of the complex plane) relative to the circle

Identification of the stability / instability regions

- Output stability circle
 - $|S_{11}| < 1 \rightarrow$ the center of the Smith chart on which Γ_L is represented is a **stable point**, so it's placed in the stability region (most often situation)
 - $|S_{11}| > 1 \rightarrow$ the center of the Smith chart on which Γ_L is represented is an **unstable point**, so it's placed in the instability region
- Input stability circle
 - $|S_{22}| < 1 \rightarrow$ the center of the Smith chart on which Γ_S is represented is a **stable point**, so it's placed in the stability region (most often situation)
 - $|S_{22}| > 1 \rightarrow$ the center of the Smith chart on which Γ_S is represented is a **unstable point**, so it's placed in the instability region

Example

- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @5GHz
 - $S_{11} = 0.64 \angle 139^\circ$
 - $S_{12} = 0.119 \angle -21^\circ$
 - $S_{21} = 3.165 \angle 16^\circ$
 - $S_{22} = 0.22 \angle 146^\circ$



```

!ATF-34143
!S-PARAMETERS at Vds=3V Id=20mA. LAST UPDATED 01-29-99

# ghz s ma r 50

2.0 0.75 -126 6.306 90 0.088 23 0.26 -120
2.5 0.72 -145 5.438 75 0.095 15 0.25 -140
3.0 0.69 -162 4.762 62 0.102 7 0.23 -156
4.0 0.65 166 3.806 38 0.111 -8 0.22 174
5.0 0.64 139 3.165 16 0.119 -21 0.22 146
6.0 0.65 114 2.706 -5 0.125 -35 0.23 118
7.0 0.66 89 2.326 -27 0.129 -49 0.25 91
8.0 0.69 67 2.017 -47 0.133 -62 0.29 67
9.0 0.72 48 1.758 -66 0.135 -75 0.34 46


!FREQ Fopt GAMMA OPT RN/Zo
!GHZ dB MAG ANG -

2.0 0.19 0.71 66 0.09
2.5 0.23 0.65 83 0.07
3.0 0.29 0.59 102 0.06
4.0 0.42 0.51 138 0.03
5.0 0.54 0.45 174 0.03
6.0 0.67 0.42 -151 0.05
7.0 0.79 0.42 -118 0.10
8.0 0.92 0.45 -88 0.18
9.0 1.04 0.51 -63 0.30
10.0 1.16 0.61 -43 0.46
  
```


$$\begin{cases}
 S_{11} = 0.64 \angle 139^\circ \\
 S_{11} = 0.64 \cdot \cos 139^\circ + j \cdot 0.64 \cdot \sin 139^\circ \\
 S_{11} = -0.4830 + j \cdot 0.4199
 \end{cases}$$

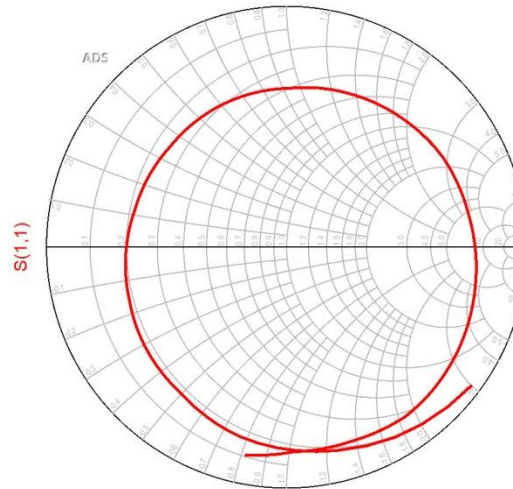Example


- ATF-34143
- at
 - $V_{ds}=3V$
 - $I_d=20mA$.




freq (500.0MHz to 18.00GHz)

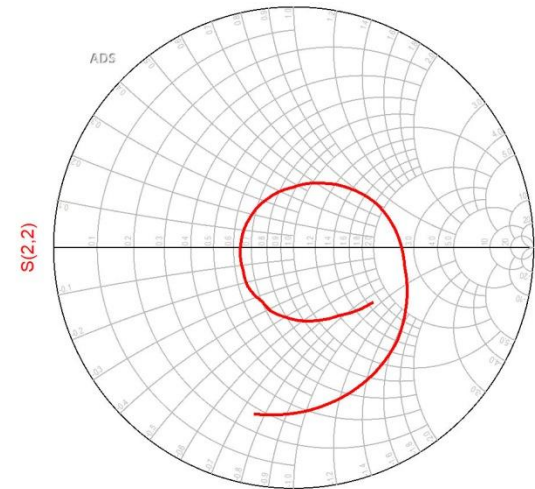

freq (500.0MHz to 18.00GHz)

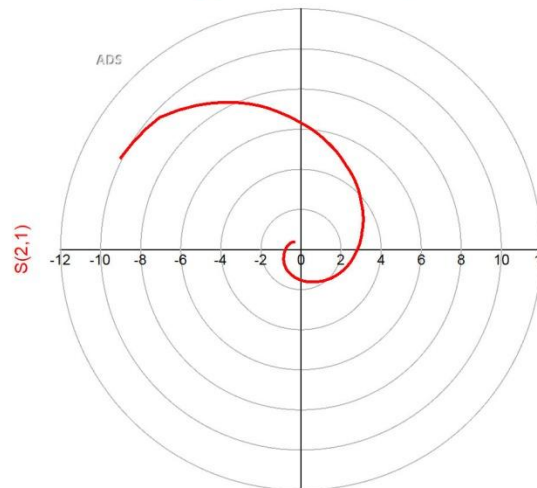

freq (500.0MHz to 18.00GHz)

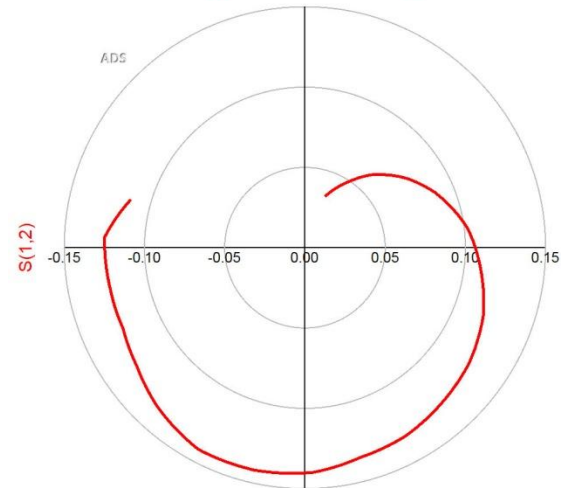

freq (500.0MHz to 18.00GHz)

Solution + region identification

- S parameters

- $S_{11} = -0.483 + 0.42 \cdot j$

- $S_{12} = 0.111 - 0.043 \cdot j$

- $S_{21} = 3.042 + 0.872 \cdot j$

- $S_{22} = -0.182 + 0.123 \cdot j$

- $|S_{11}| = 0.64 < 1$

- $|C_L| < R_L, o \in \text{CSOUT}$

- The center of the Smith chart is placed inside the output stability circle ($o \in \text{CSOUT}$) and is a stable point ($|S_{11}| < 1$)

- the inside of the output stability circle – stability region

- the outside of the output stability circle – instability region

$$C_L = \frac{(S_{22} - \Delta \cdot S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} = 3.931 - 0.897 \cdot j$$


$$|C_L| = 4.032$$

$$R_L = \frac{|S_{12} \cdot S_{21}|}{\left| |S_{22}|^2 - |\Delta|^2 \right|} = 4.891$$

Solution + region identification

- S parameters
 - $S_{11} = -0.483 + 0.42 \cdot j$
 - $S_{12} = 0.111 - 0.043 \cdot j$
 - $S_{21} = 3.042 + 0.872 \cdot j$
 - $S_{22} = -0.182 + 0.123 \cdot j$
 - $|S_{22}| = 0.22 < 1$
 - $|C_S| > R_S, 0 \notin \text{CSIN}$
 - The center of the Smith chart is placed outside the input stability circle ($0 \notin \text{CSIN}$) and is a stable point ($|S_{22}| < 1$)
 - the outside of the input stability circle – stability region
 - the inside of the input stability circle – instability region
- $$C_S = \frac{(S_{11} - \Delta \cdot S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} = -1.871 - 1.265 \cdot j$$
- $$|C_S| = 2.259$$
- $$R_S = \frac{|S_{12} \cdot S_{21}|}{\left| |S_{11}|^2 - |\Delta|^2 \right|} = 1.325$$

ADS


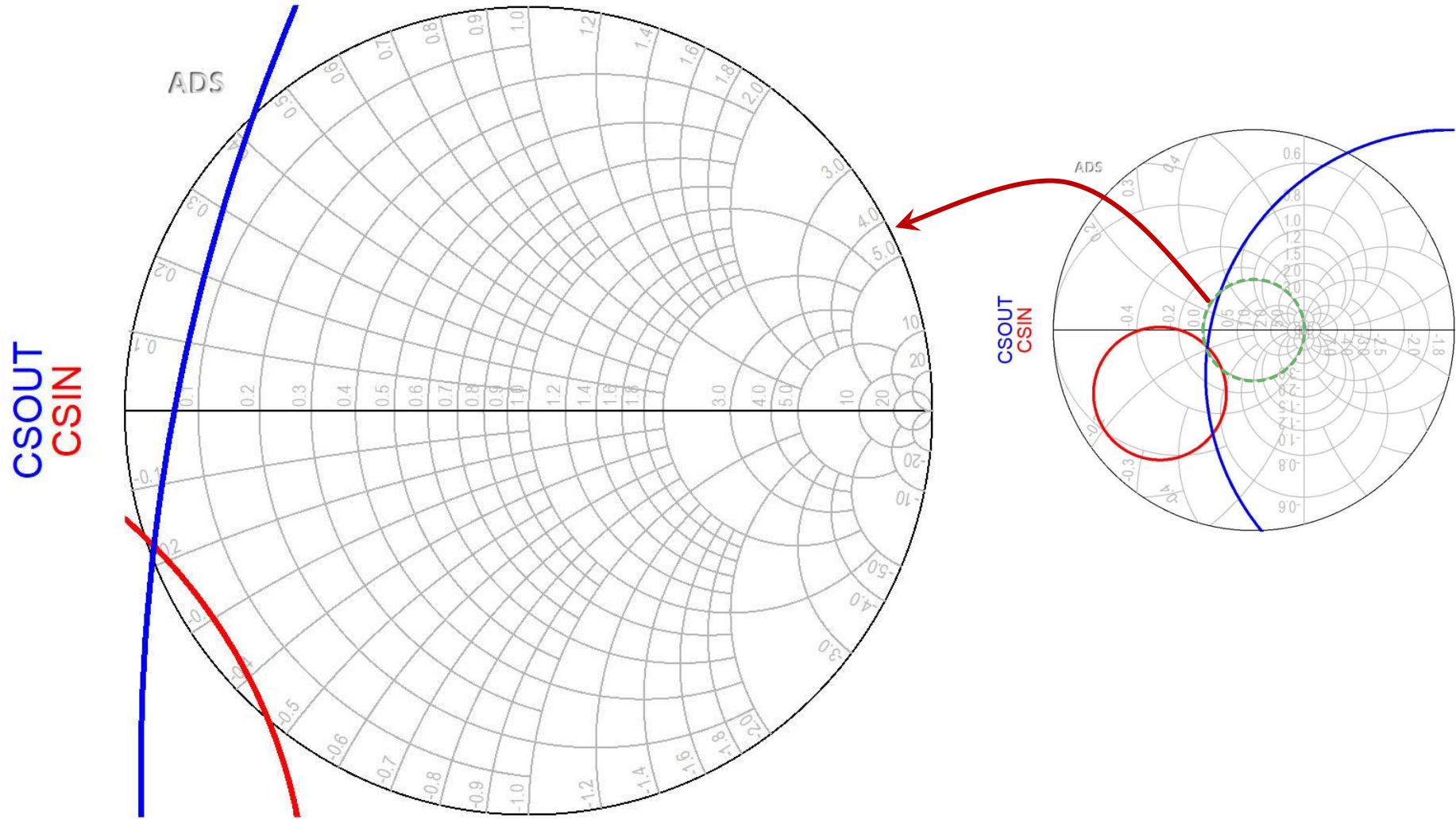


3D representation of $|\Gamma_{in}|$, $|\Gamma_{out}|$

- High variations -> we change to z logarithmic scale



scale $\Gamma_{in}(\Gamma_L) = S_{11} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_L}{1 - S_{22} \cdot \Gamma_L}$

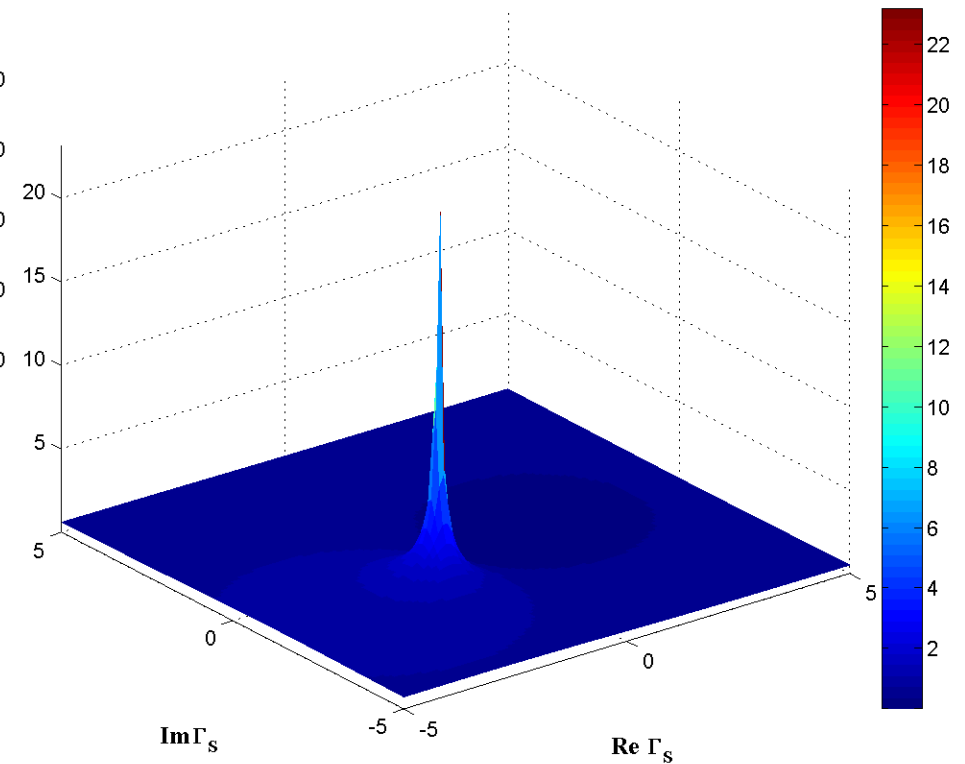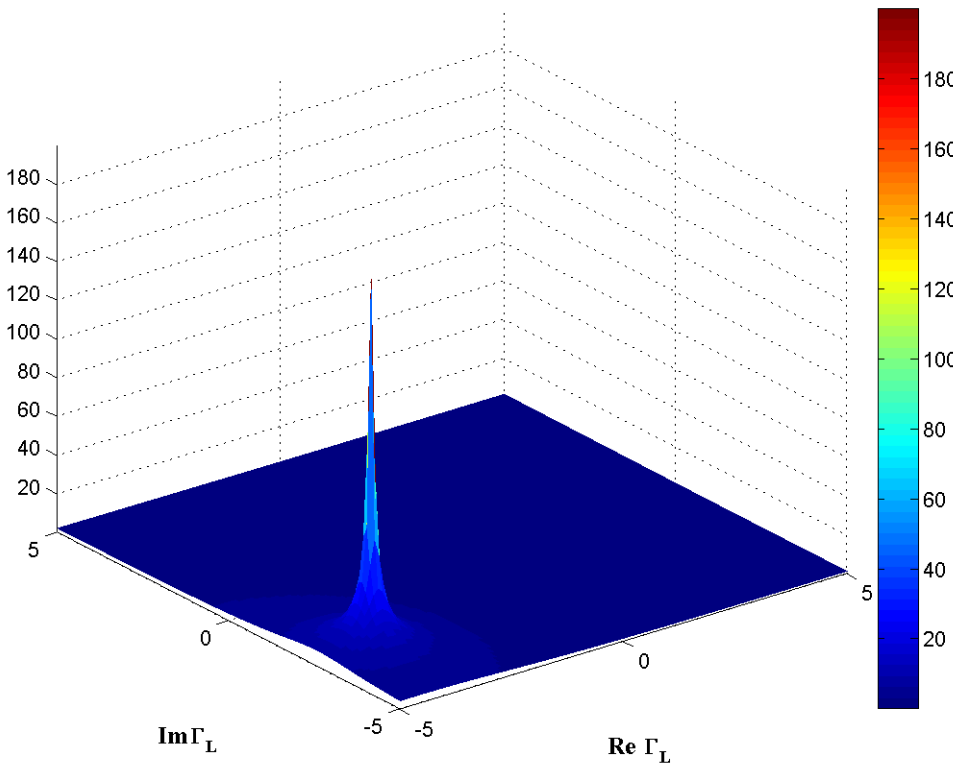$\Gamma_{out}(\Gamma_S) = S_{22} + \frac{S_{12} \cdot S_{21} \cdot \Gamma_S}{1 - S_{11} \cdot \Gamma_S}$



3D representation of $|\Gamma_{in}|$, $|\Gamma_{out}|$


- $\log_{10}|\Gamma_{in}|$, $\log_{10}|\Gamma_{out}|$

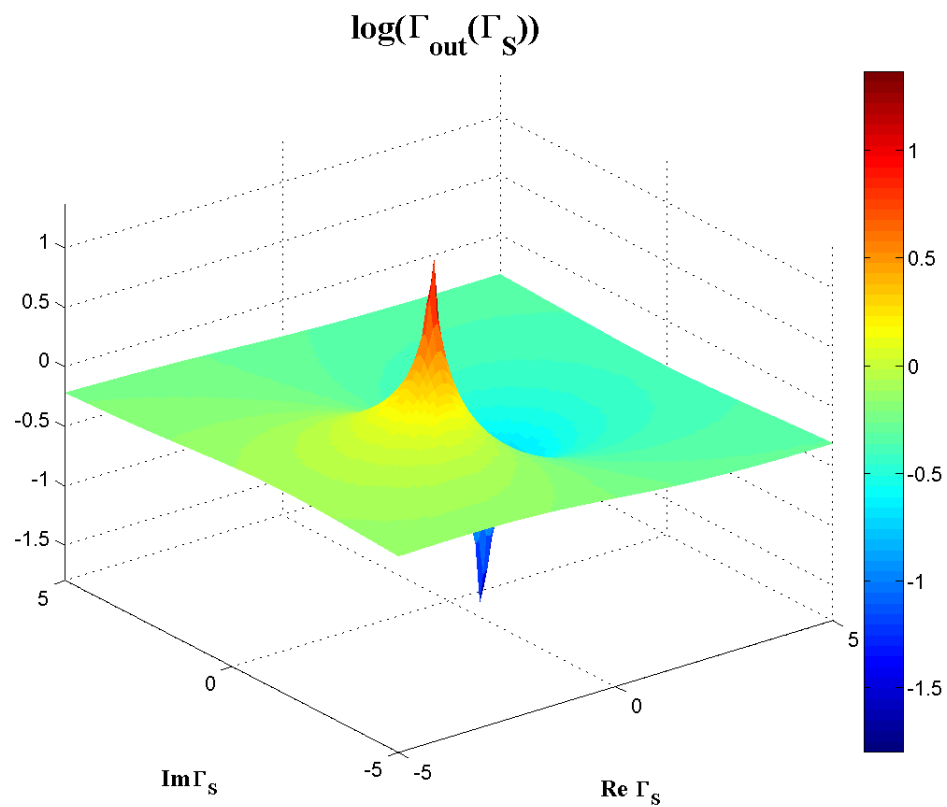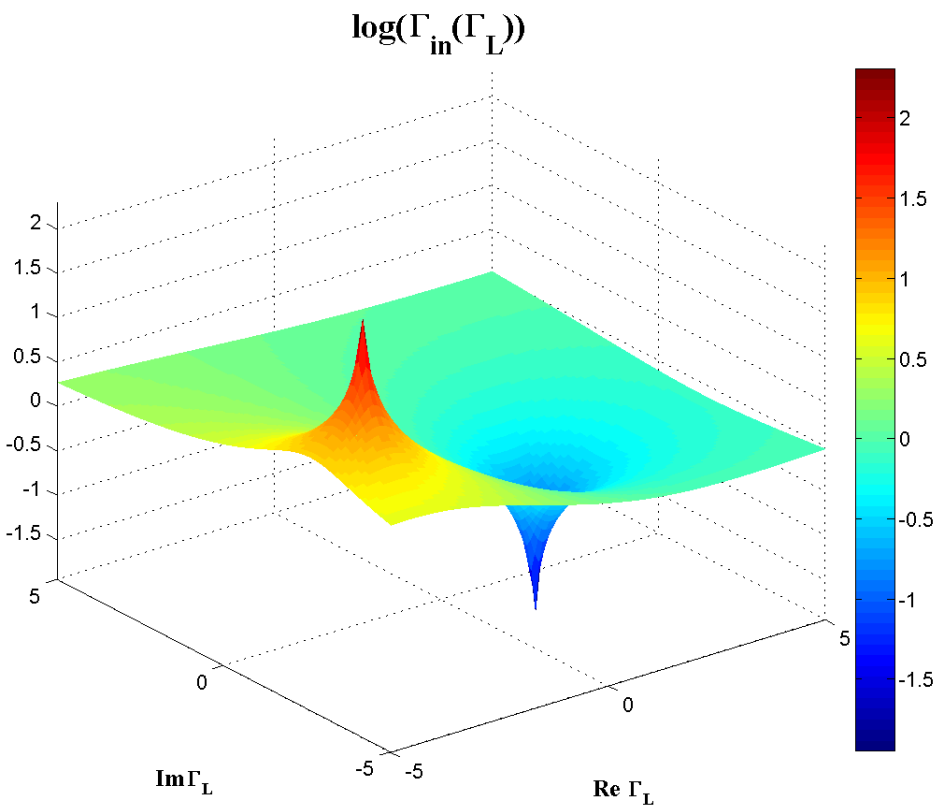


3D representation of $|\Gamma_{in}|$, $|\Gamma_{out}|$, $|\Gamma|=1$

- $|\Gamma| = 1 \rightarrow \log_{10}|\Gamma| = 0$, the intersection with the plane $z = 0$ is a circle


$\log(\Gamma_{in}(\Gamma_L))$

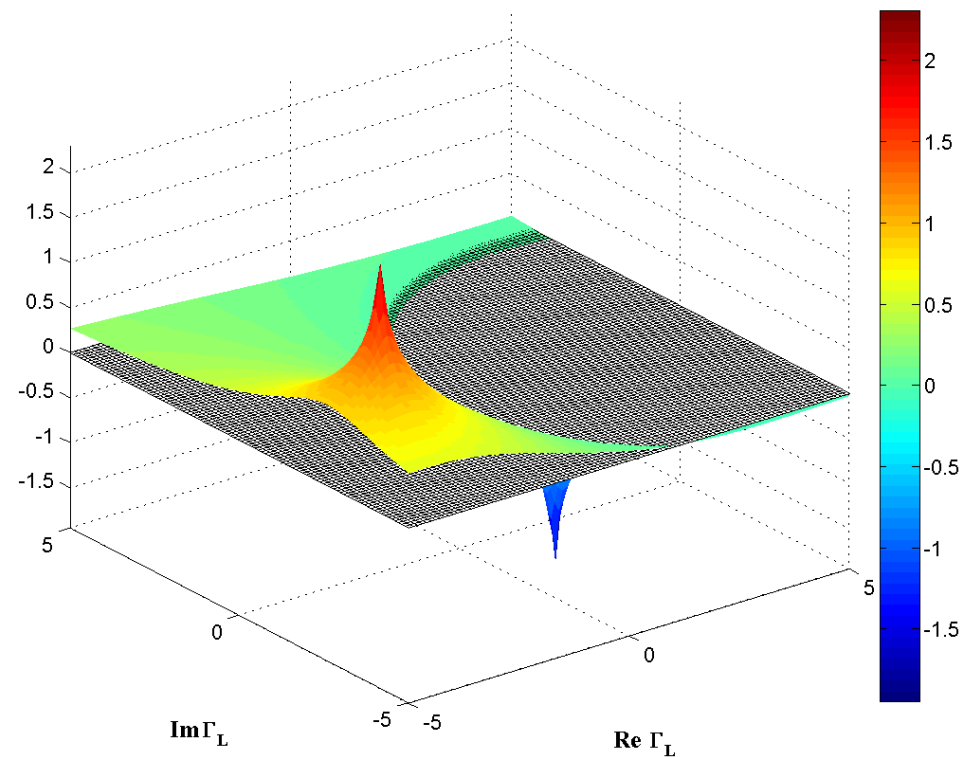


$\log(\Gamma_{out}(\Gamma_S))$

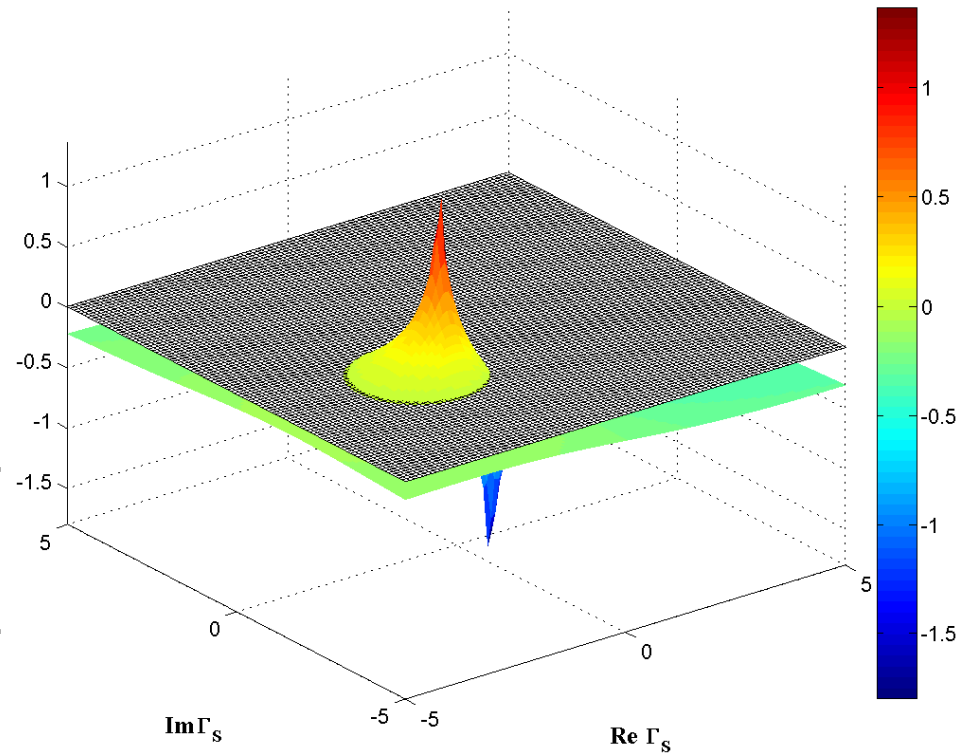

Contour map/lines

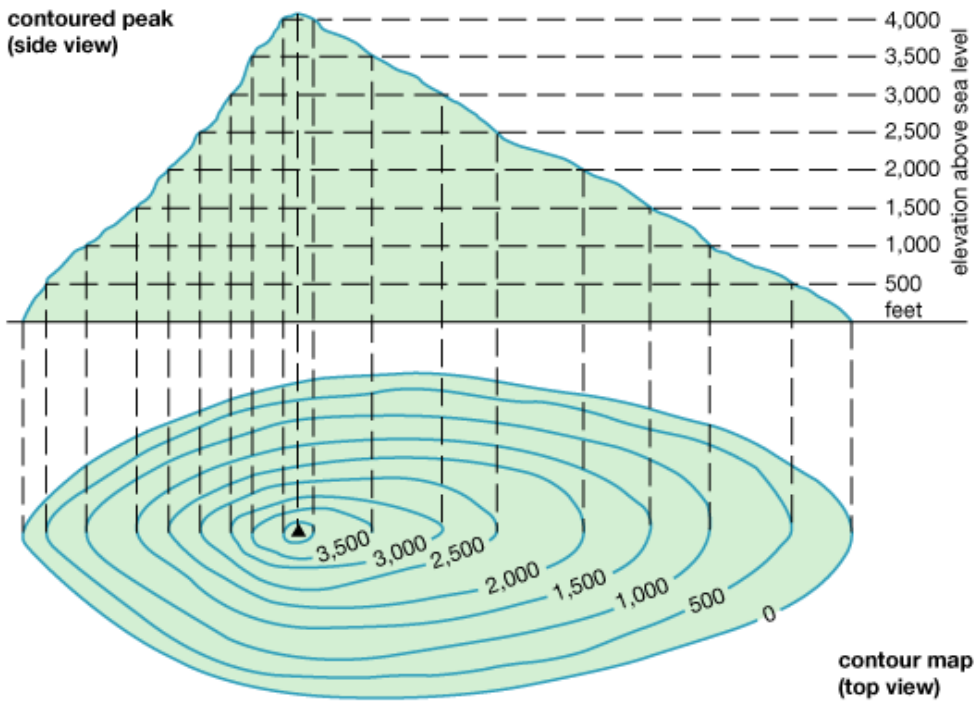


© 2011 Encyclopædia Britannica, Inc.

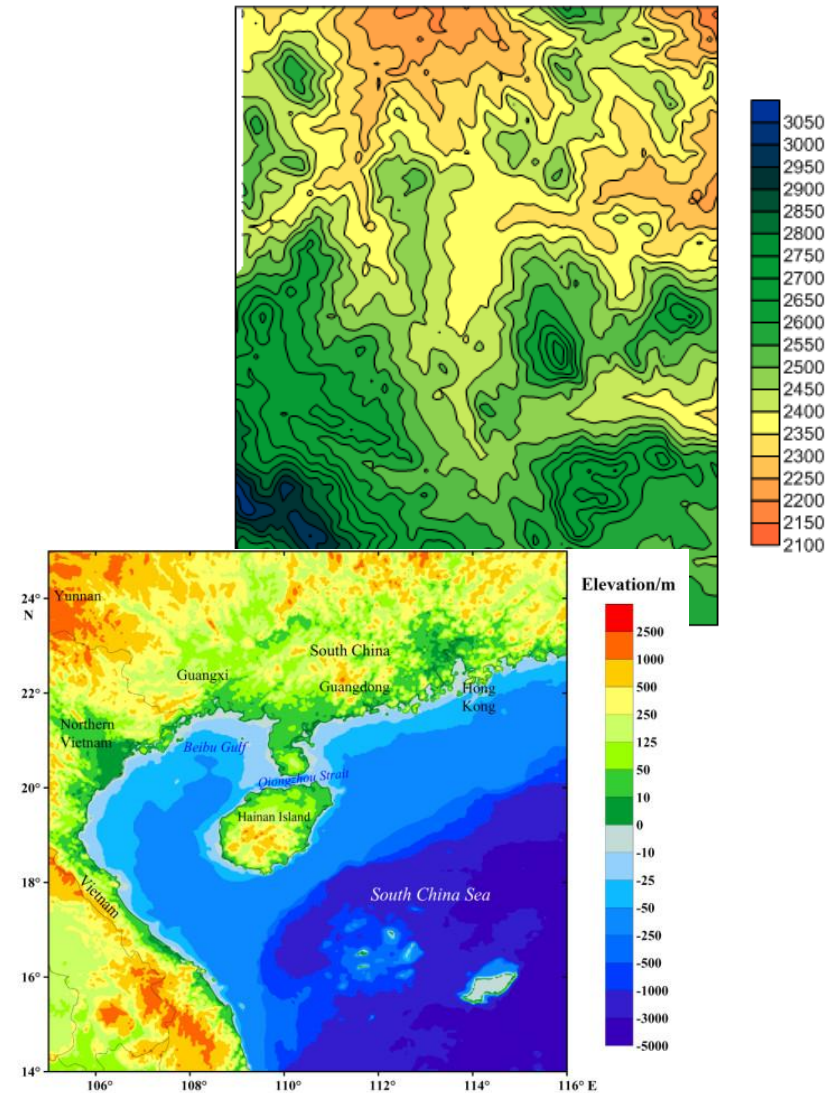

Contour lines of $\log_{10}|\Gamma_{in}|$


■ $\log_{10}|\Gamma_{in}| = 0, \Gamma_L, \text{CSOUT}$

$$\log_{10}|\Gamma_{in}| = 0, \\ |\Gamma_{in}| = 1$$

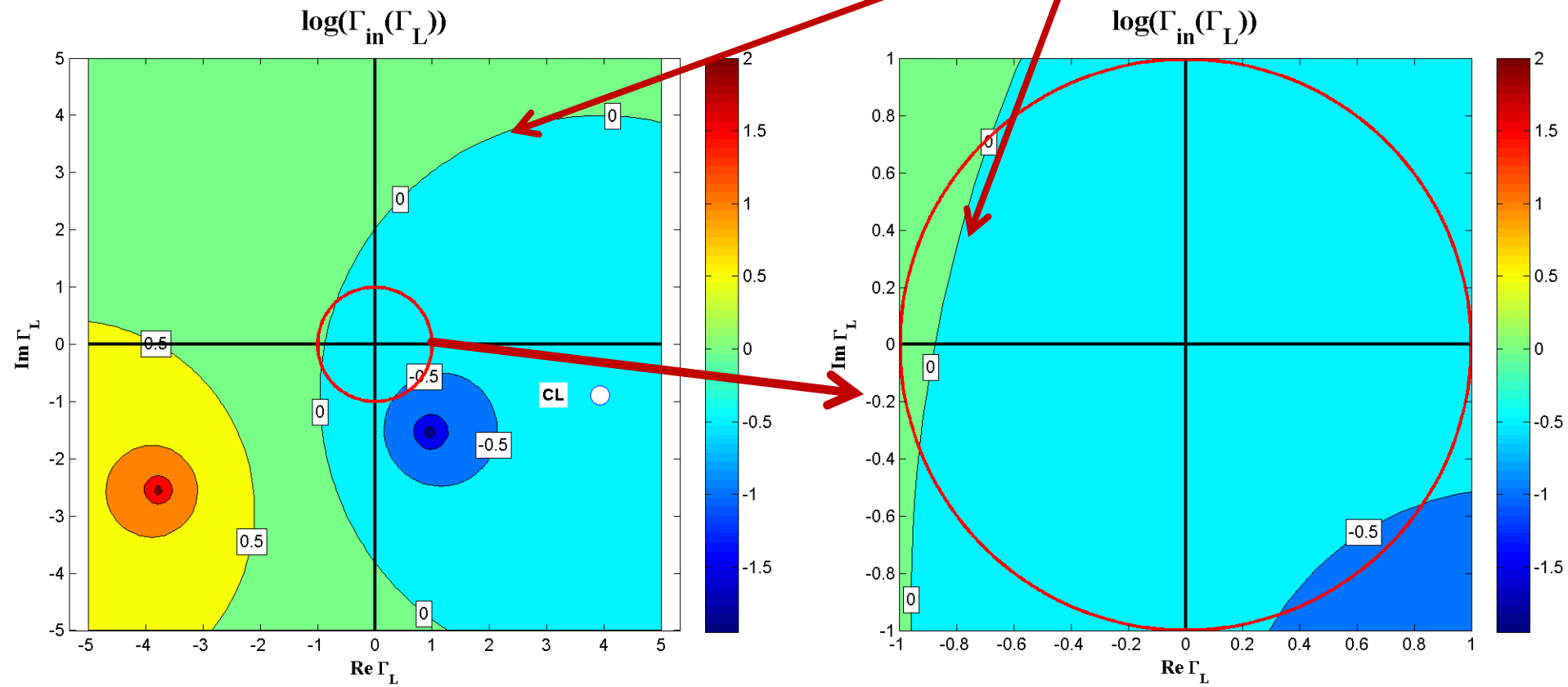




Contour lines of $\log_{10}|\Gamma_{out}|$

- $\log_{10}|\Gamma_{out}| = 0, \Gamma_S, \text{CSIN}$

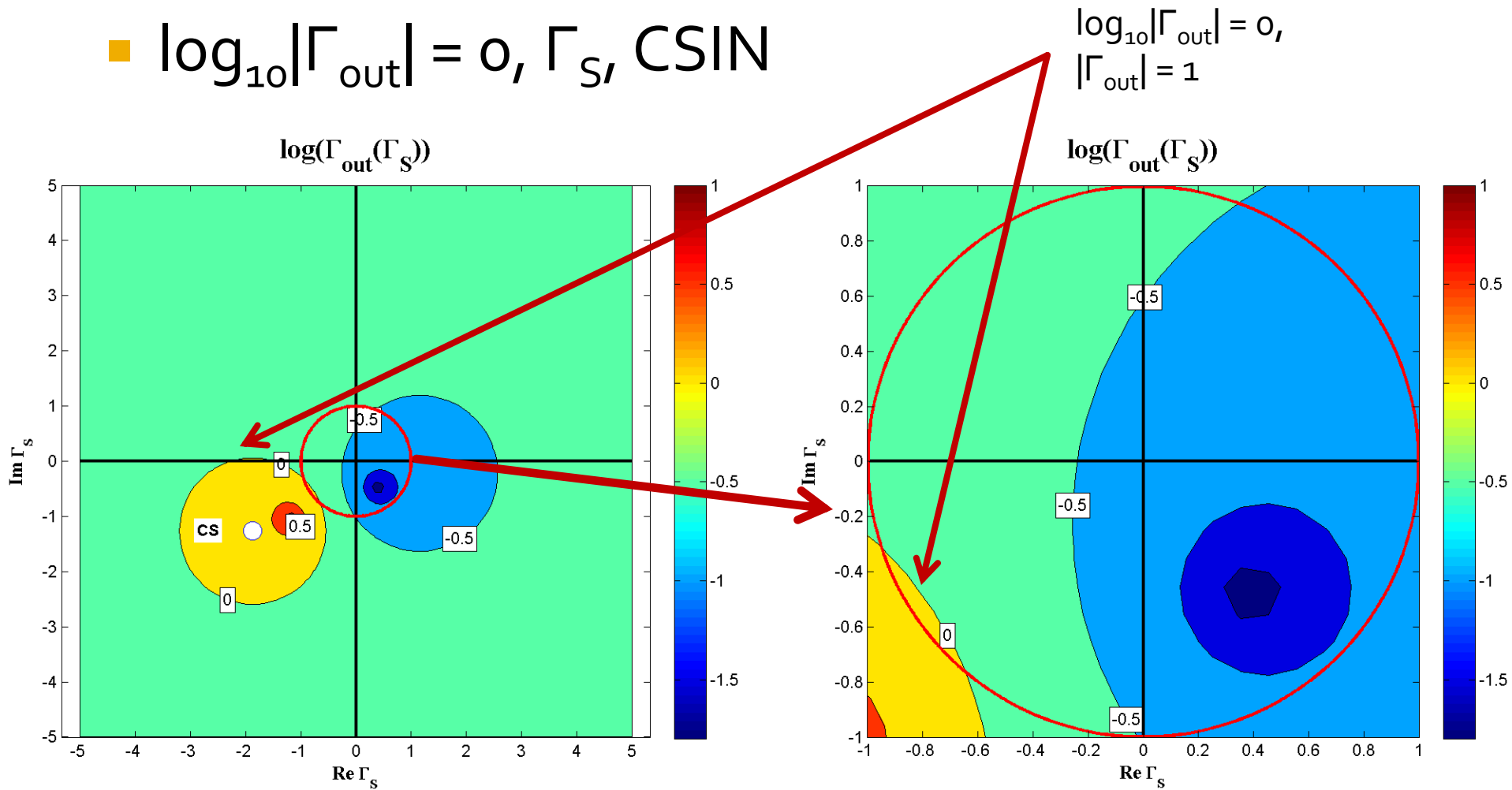


CSIN, CSOUT



CSOUT
CSIN

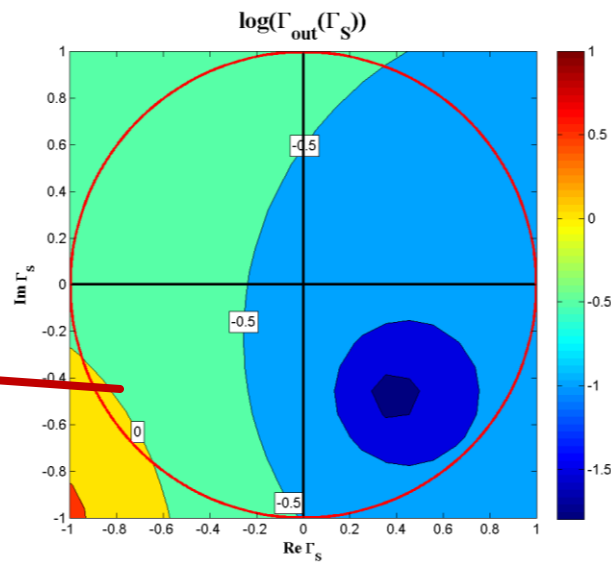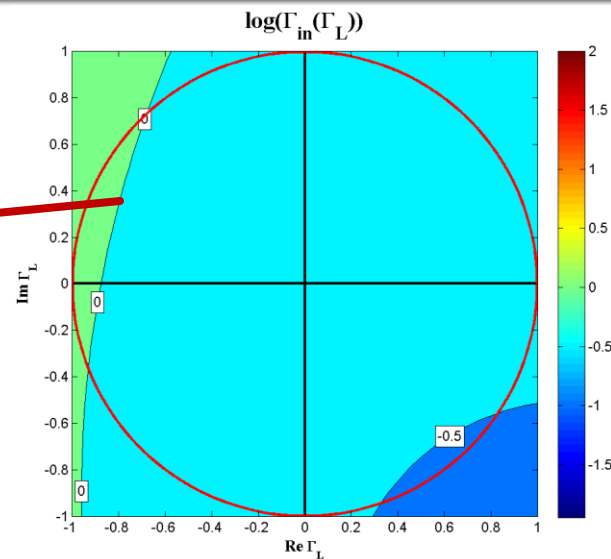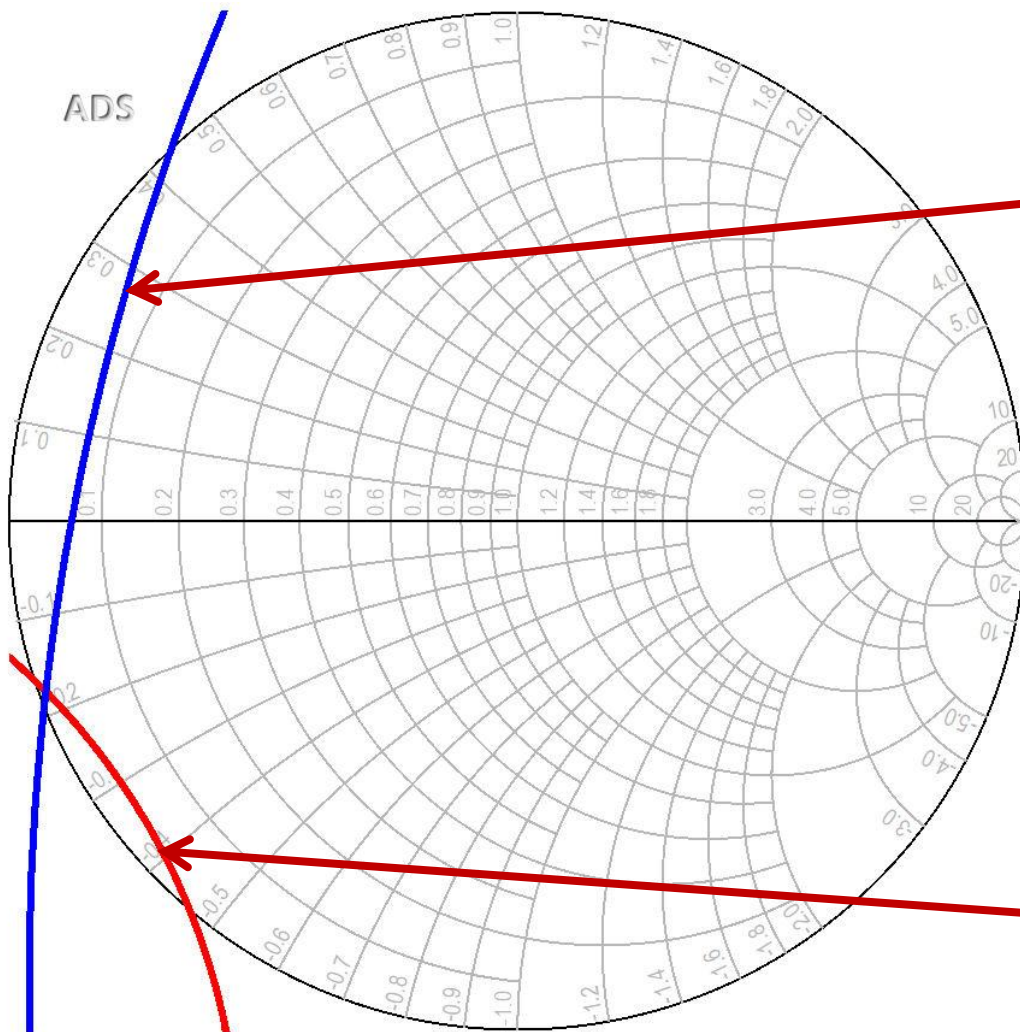



Several possible positioning

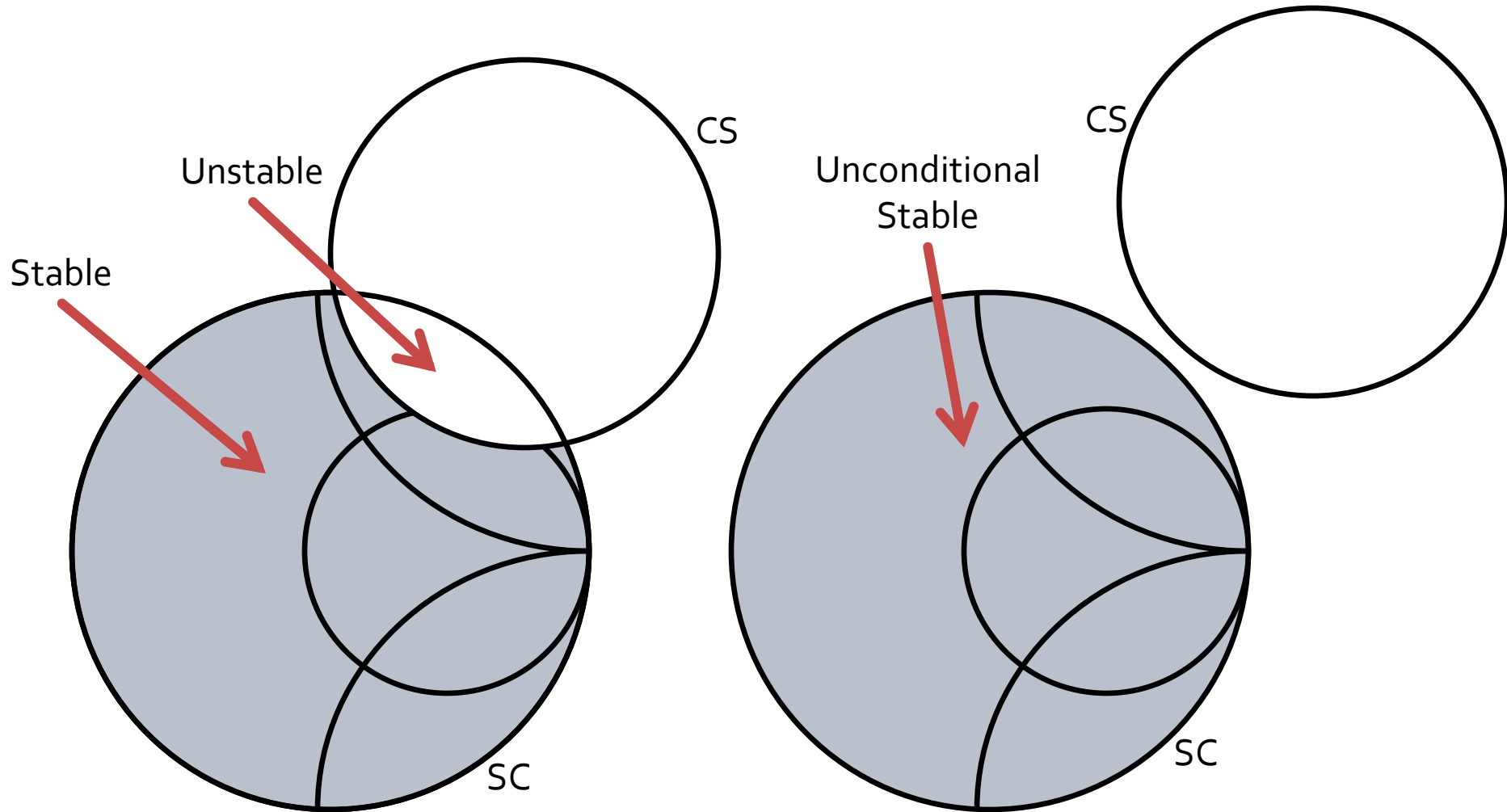

Several possible positioning

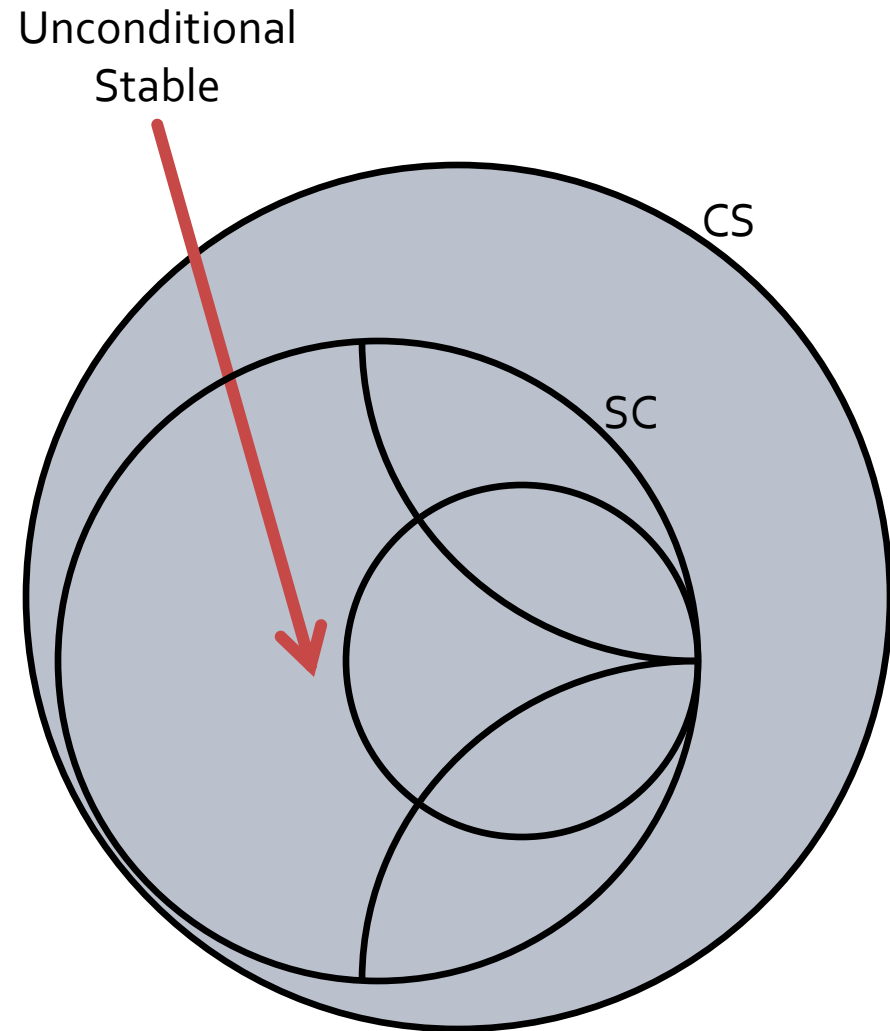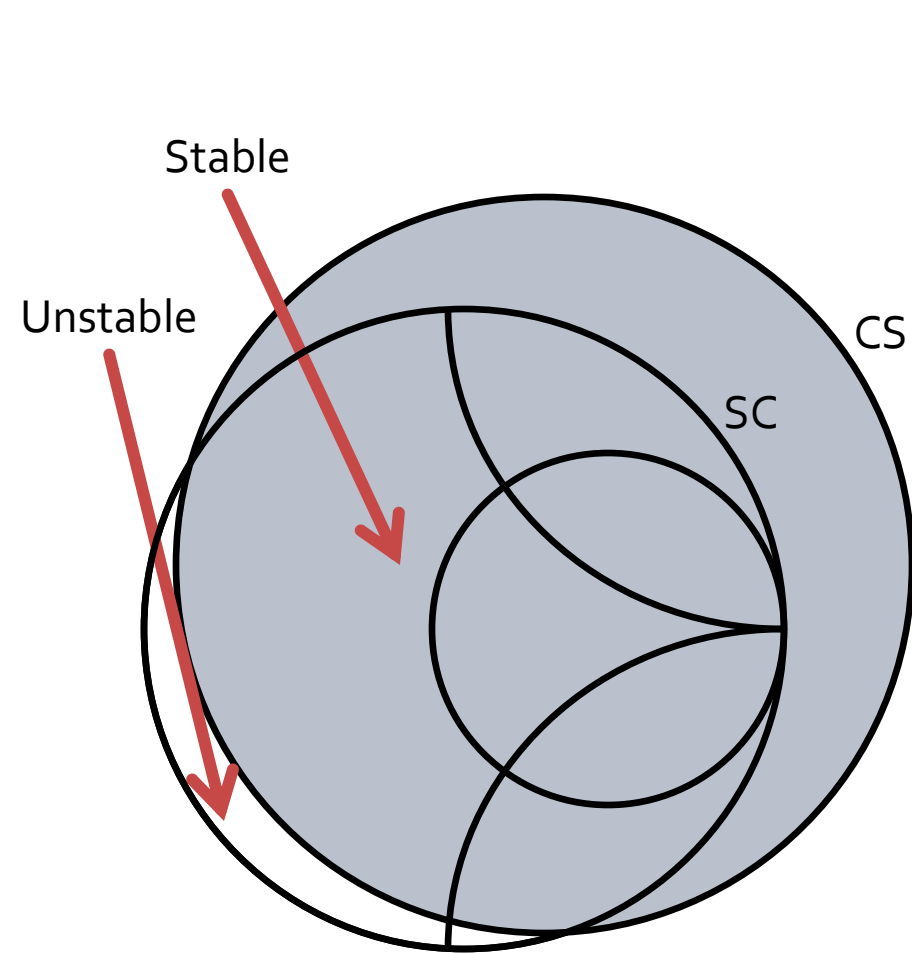

(Quite) Rare positioning

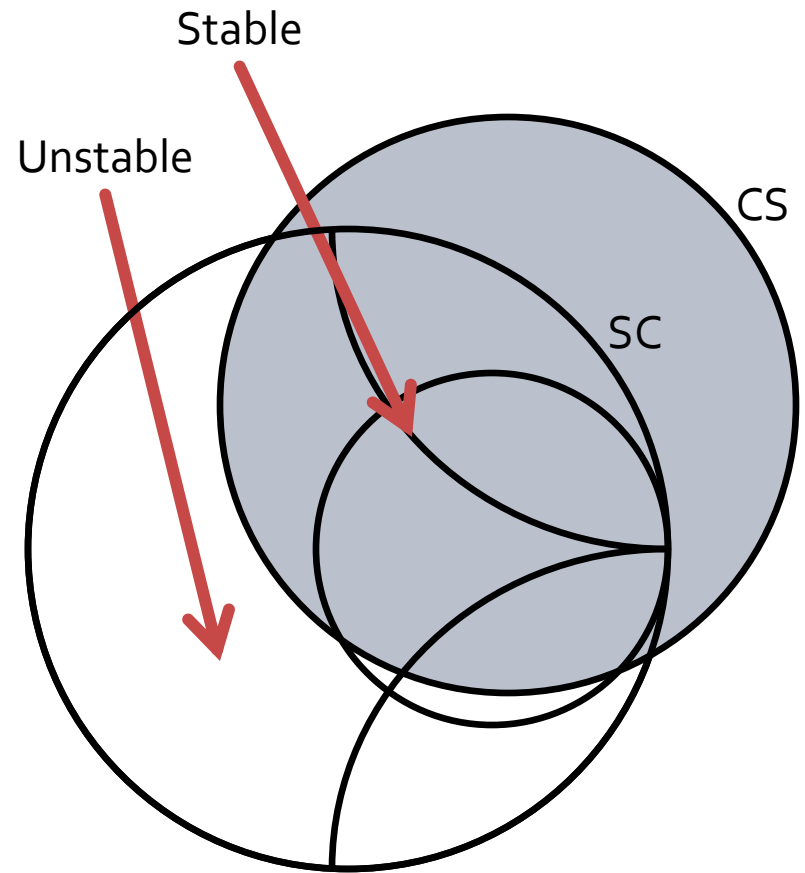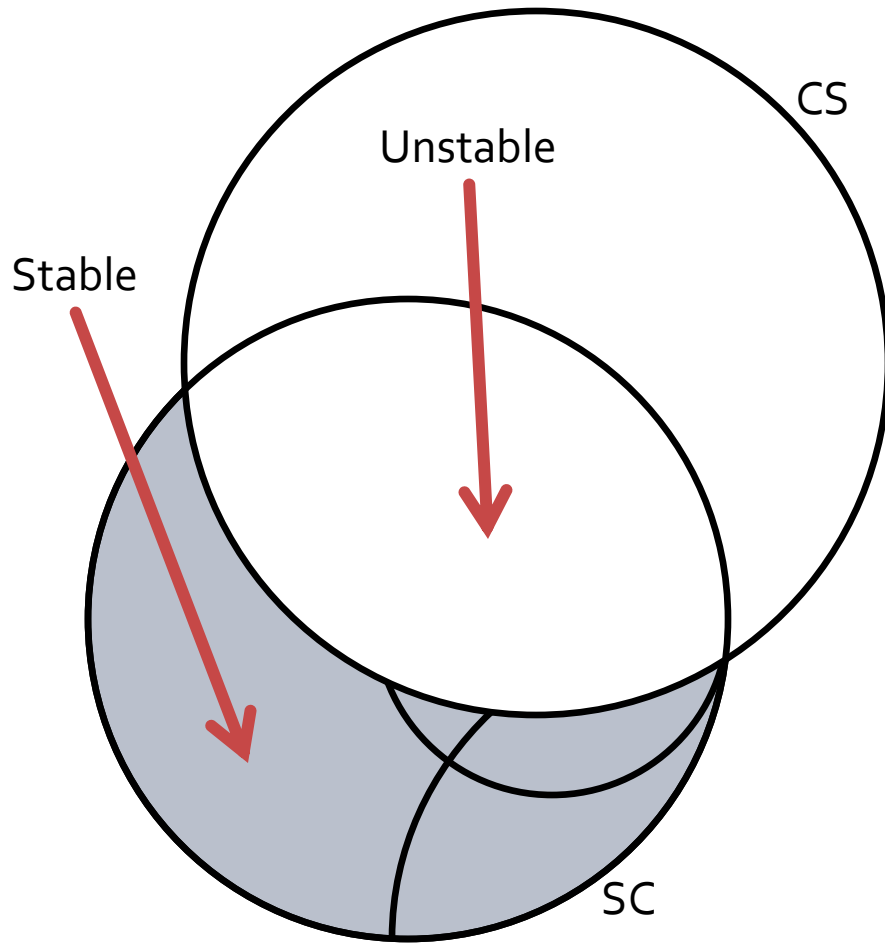

Stability

- **Unconditional stability:** the circuit is unconditionally stable if $|\Gamma_{in}| < 1$ and $|\Gamma_{out}| < 1$ for **any** passive impedance of the load/source
- **Conditional stability:** the circuit is conditionally stable if $|\Gamma_{in}| < 1$ and $|\Gamma_{out}| < 1$ only for **some** passive impedance of the load/source
 - passive impedance of the load/source \leftrightarrow interior of the Smith Chart (radius 1 circle in the complex plane)

Unconditional stability

- The two-port is unconditionally stable if either:
 - The stability circle is disjoint with the Smith Chart (exterior to the Chart) and the stable region is outside the circle
 - The stability circle encloses the entire Smith Chart and the stable region is inside the circle
- One mandatory condition for unconditional stability is $|S_{11}| < 1$ (CSOUT) or $|S_{22}| < 1$ (CSIN) – if in at least one point the two-port is not stable then it cannot be unconditionally stable

- Mathematically :


$$\left\{ \begin{array}{l} \left| |C_L| - R_L \right| > 1 \\ |S_{11}| < 1 \end{array} \right. \quad \left\{ \begin{array}{l} \left| |C_S| - R_S \right| > 1 \\ |S_{22}| < 1 \end{array} \right.$$

Tests for Unconditional Stability


- Useful for wide frequency range analysis
- It is not enough to check the stability only at the operating frequencies
 - we must obtain stable operation for chosen Γ_L and Γ_S at **any** frequency

Circles in wide frequency range

CSIN

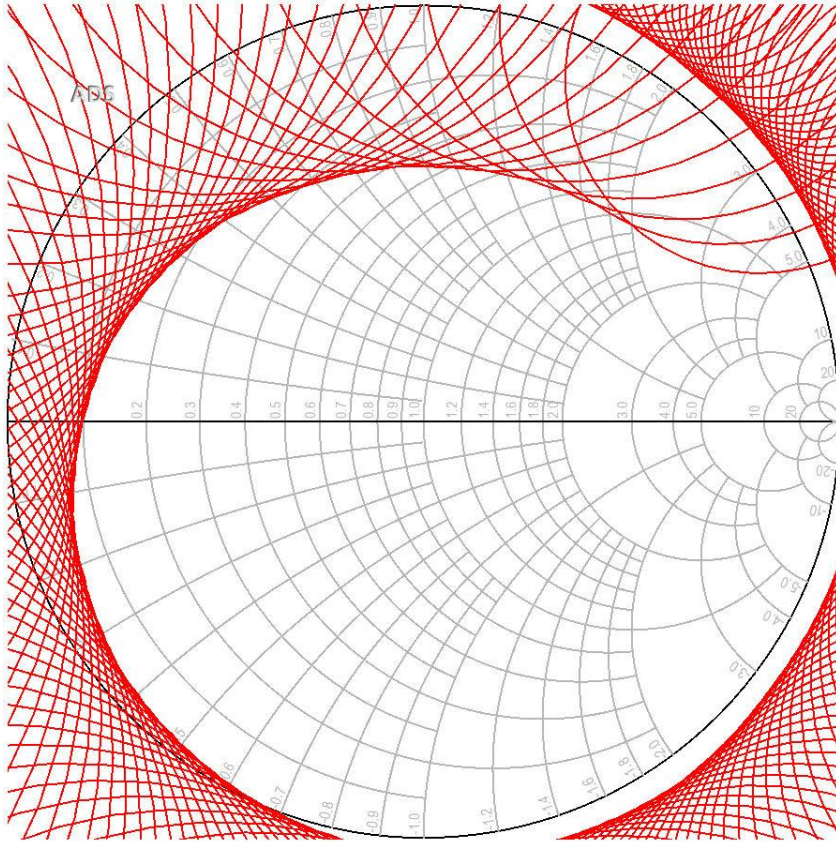

CSOUT

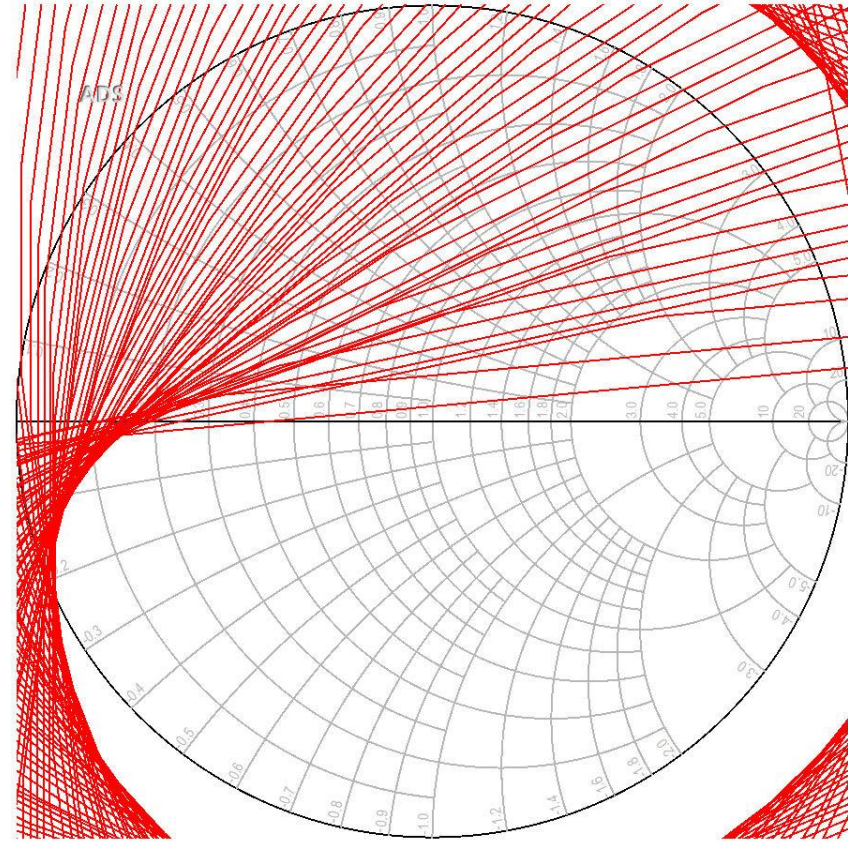

Rollet's condition

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 \cdot |S_{12} \cdot S_{21}|}$$

$$\Delta = S_{11} \cdot S_{22} - S_{12} \cdot S_{21}$$

- The two-port is **unconditionally stable** if:
- two conditions are simultaneously satisfied:
 - $K > 1$
 - $|\Delta| < 1$
- together with the implicit conditions:
 - $|S_{11}| < 1$
 - $|S_{22}| < 1$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 \cdot |S_{12} \cdot S_{21}|} > 1$$

$$|\Delta| = |S_{11} \cdot S_{22} - S_{12} \cdot S_{21}| < 1$$

μ Criterion

- Rollet's condition cannot be used to compare the relative stability of two or more devices because it involves constraints on two separate parameters, K and Δ

$$\mu = \frac{1 - |S_{11}|^2}{|S_{22} - \Delta \cdot S_{11}^*| + |S_{12} \cdot S_{21}|} > 1$$

- The two-port is **unconditionally stable** if:
 - $\mu > 1$
- together with the implicit conditions:
 - $|S_{11}| < 1$
 - $|S_{22}| < 1$
- In addition, it can be said that larger values of μ imply greater stability
 - μ is the distance from the center of the Smith Chart to the closest output stability circle

μ' Criterion


- Dual parameter to μ , determined in relation to the input stability circles

$$\mu' = \frac{1 - |S_{22}|^2}{|S_{11} - \Delta \cdot S_{22}^*| + |S_{12} \cdot S_{21}|} > 1$$

- The two-port is **unconditionally stable** if:
 - $\mu' > 1$
- together with the implicit conditions:
 - $|S_{11}| < 1$
 - $|S_{22}| < 1$
- In addition, it can be said that larger values of μ' imply greater stability
 - μ' is the distance from the center of the Smith Chart to the closest input stability circle


Rollet's condition

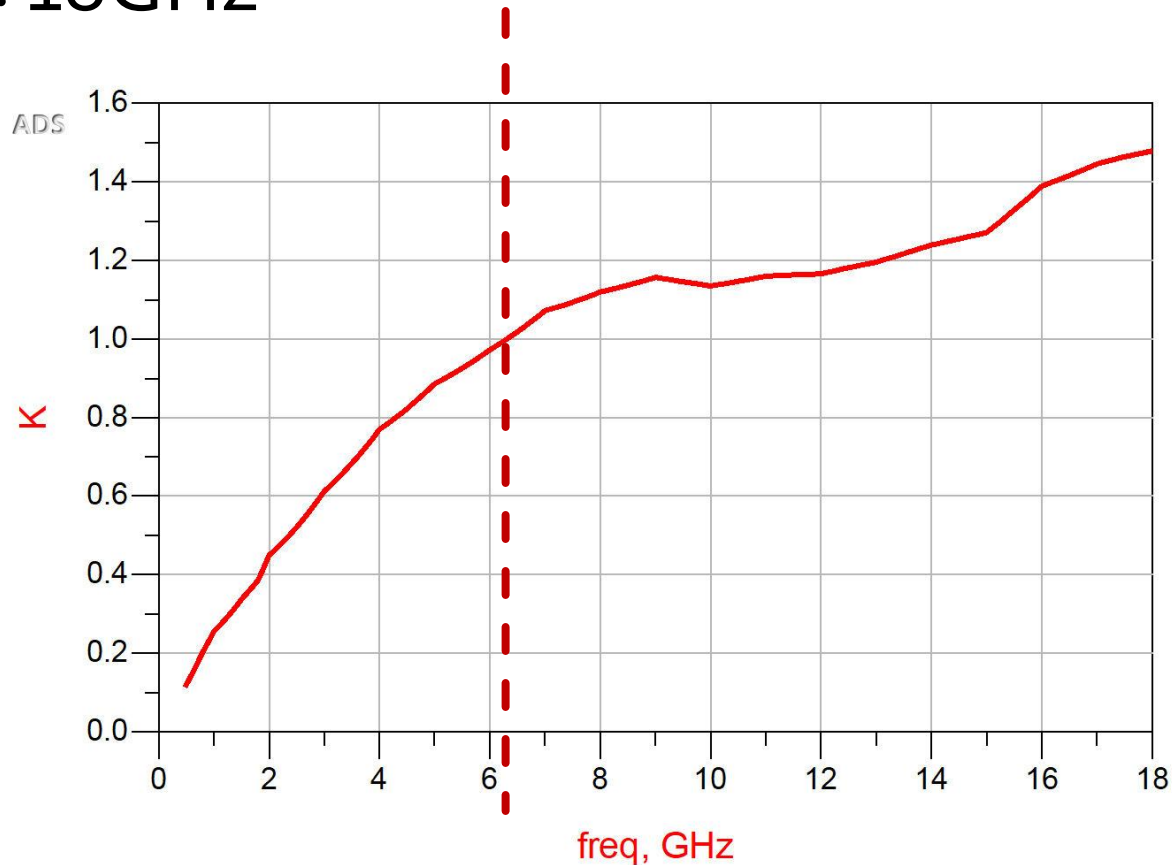- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz




μ Criterion

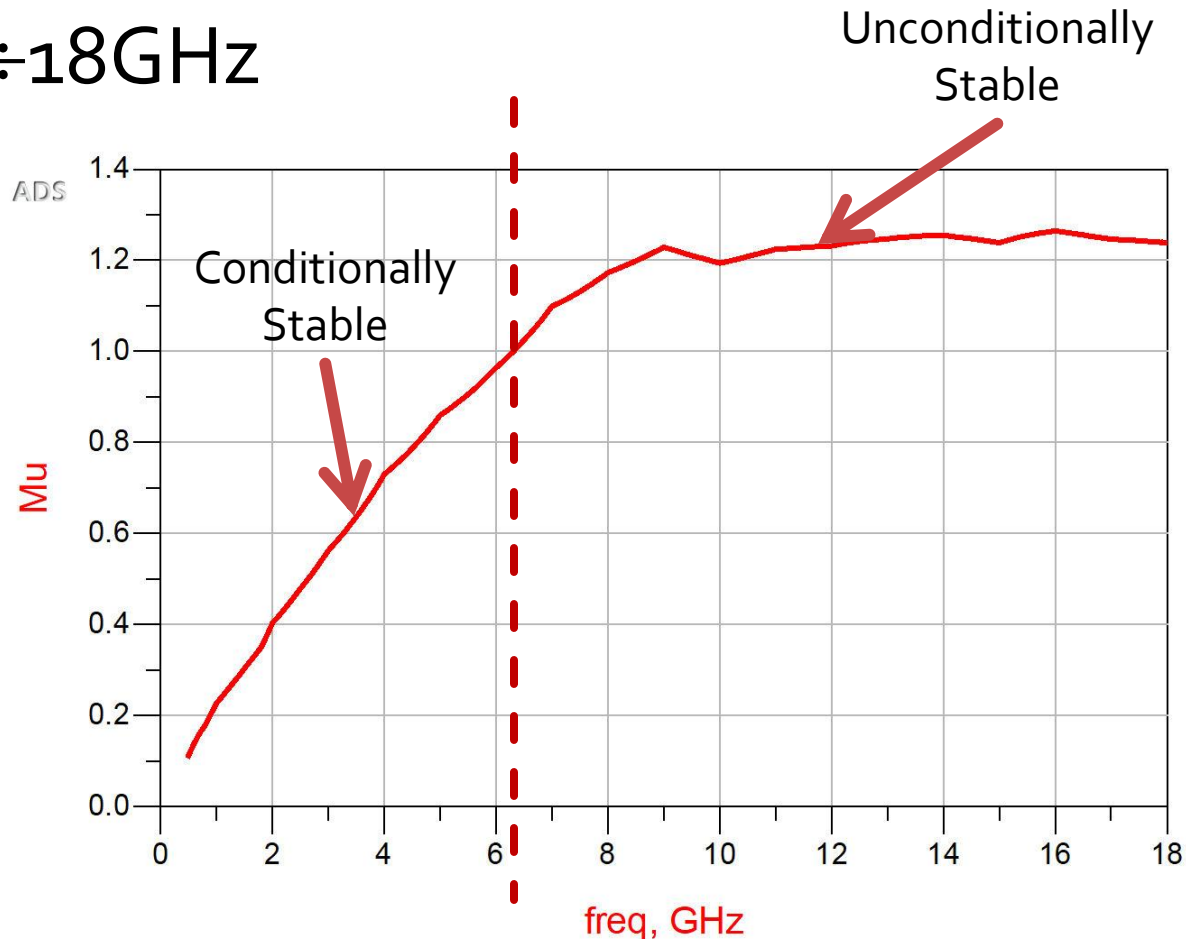- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz





μ' Criterion

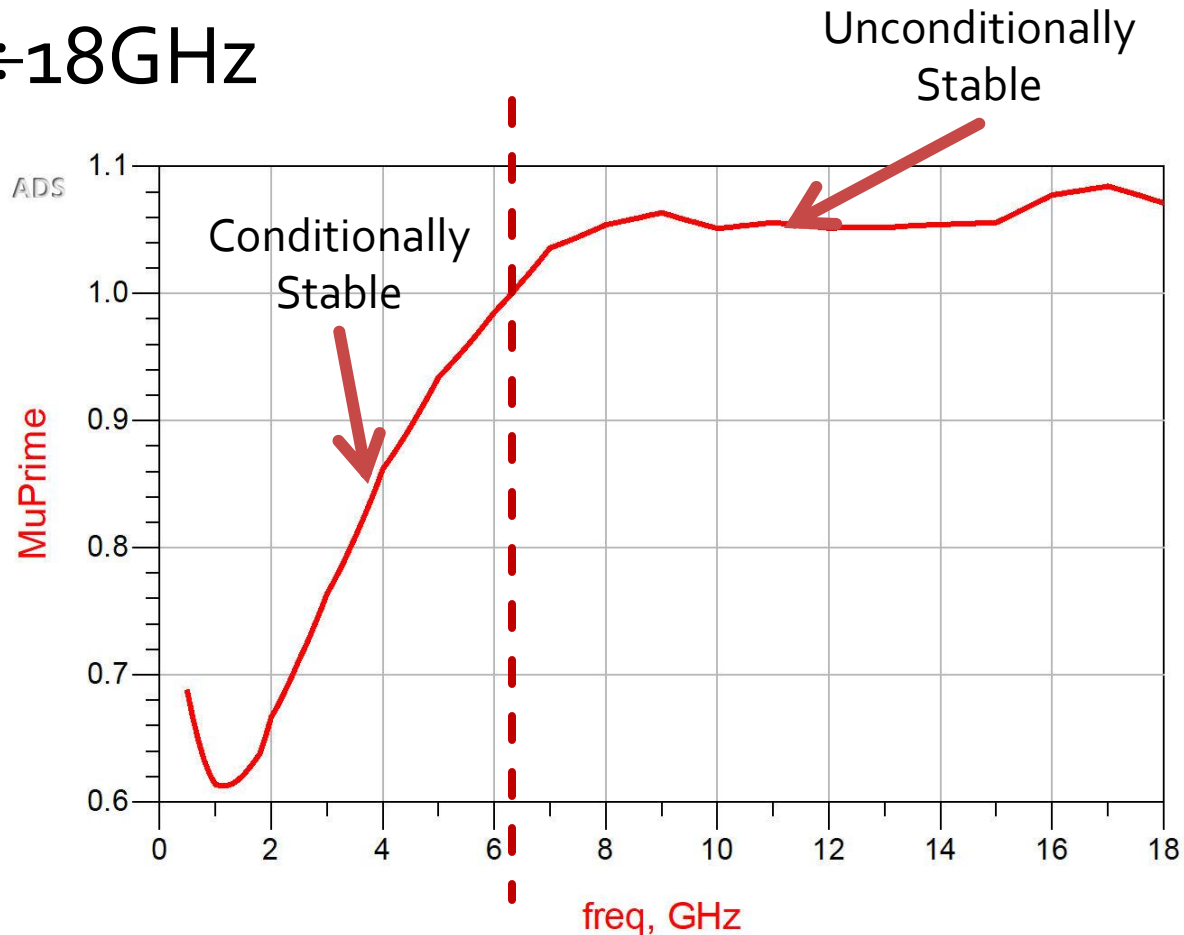- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz



Stability

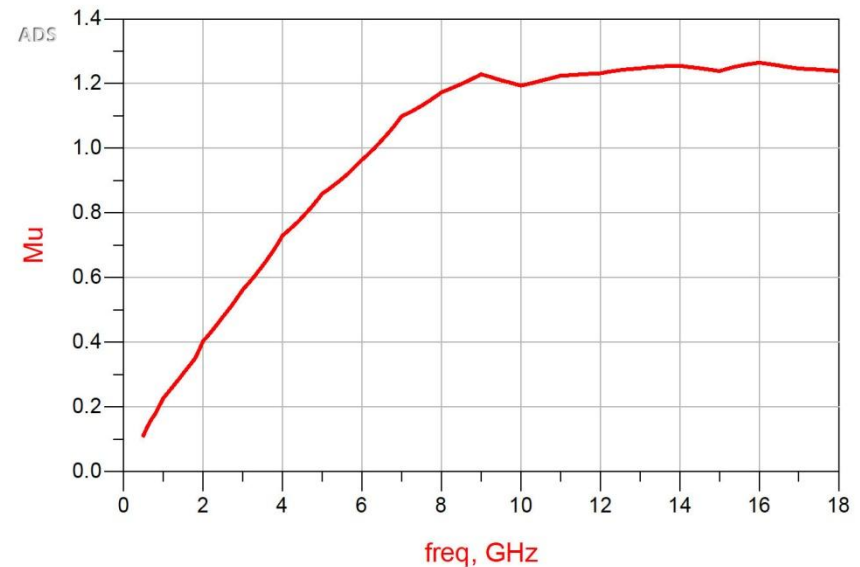
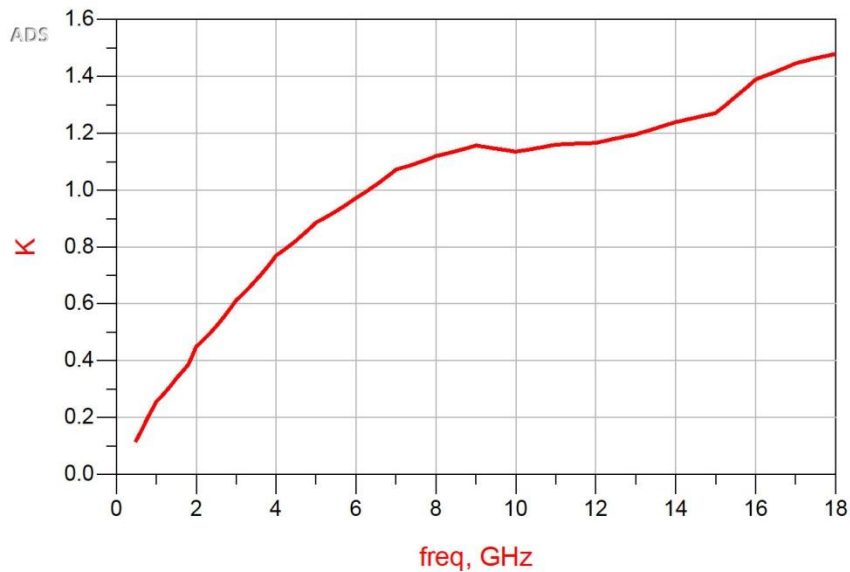
- ATF-34143 at $V_{ds}=3V$ $I_d=20mA$.
- @0.5÷18GHz
- unconditionally stable for $f > 6.31GHz$



Stabilization of two-port

- Unconditional stability in a wide frequency range has some important advantages
 - Ex: We can use ATF 34143 to design a (conditionally) stable amplifier at 5GHz, but this design is useless if the amplifier oscillates at 500MHz ($\mu \approx 0.1$)
- **The minimal requirement** when working with conditionally stable devices is to **check stability** at several frequencies over the operating bandwidth and outside the bandwidth
- Unconditional stability can be forced by inserting series/shunt resistors at two-port's input/output (with loss of gain!)


Input series resistor

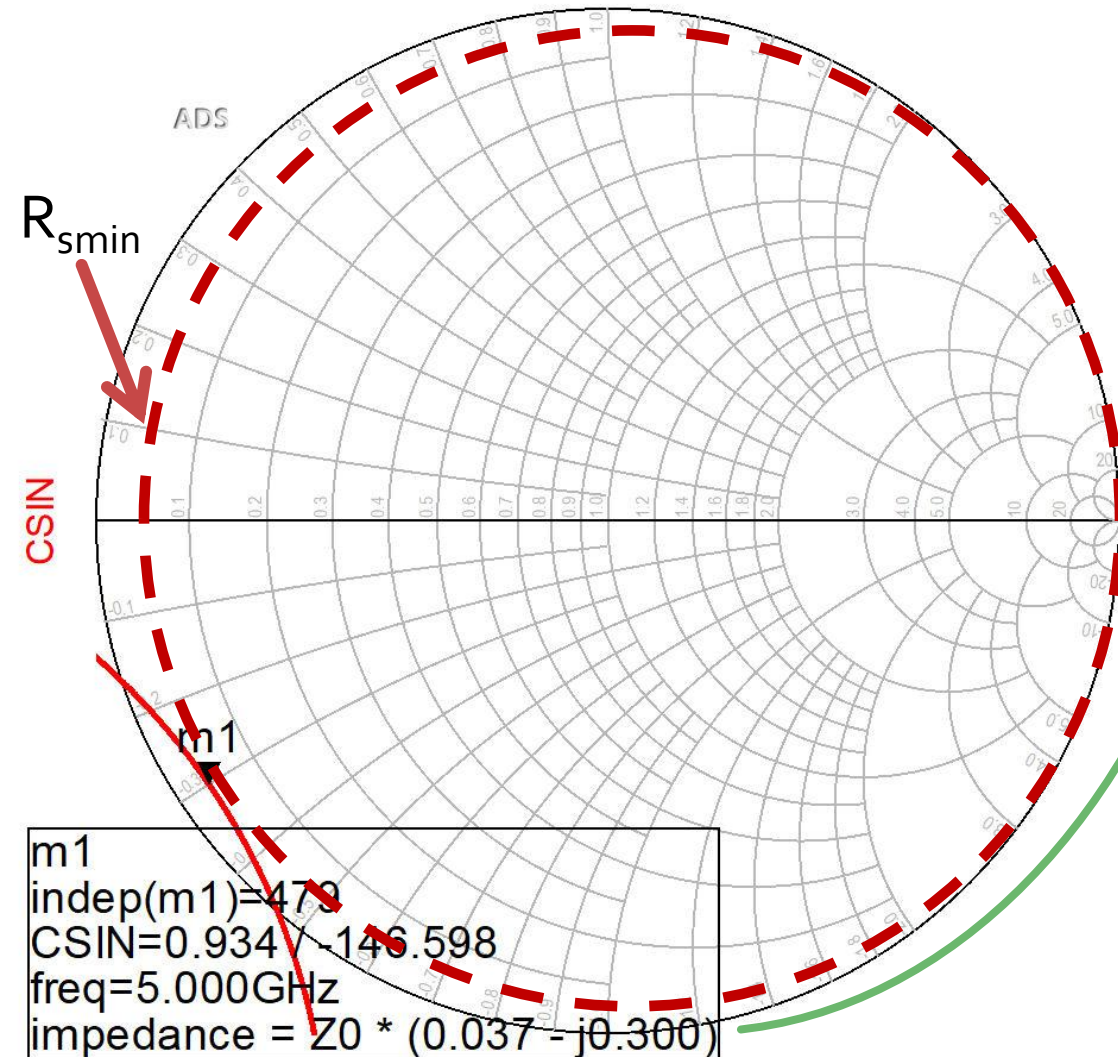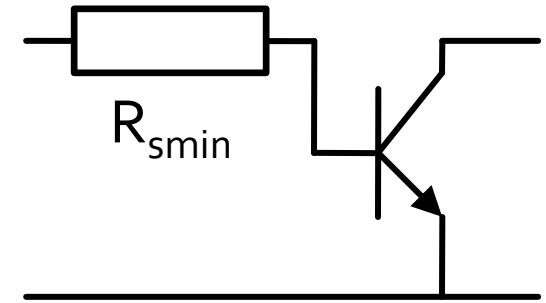

$$z = 0.037 - j \cdot 0.3$$



$$R_{smin} = 0.037 \cdot 50\Omega = 1.85\Omega$$

ADS, $R_s = 2\Omega$


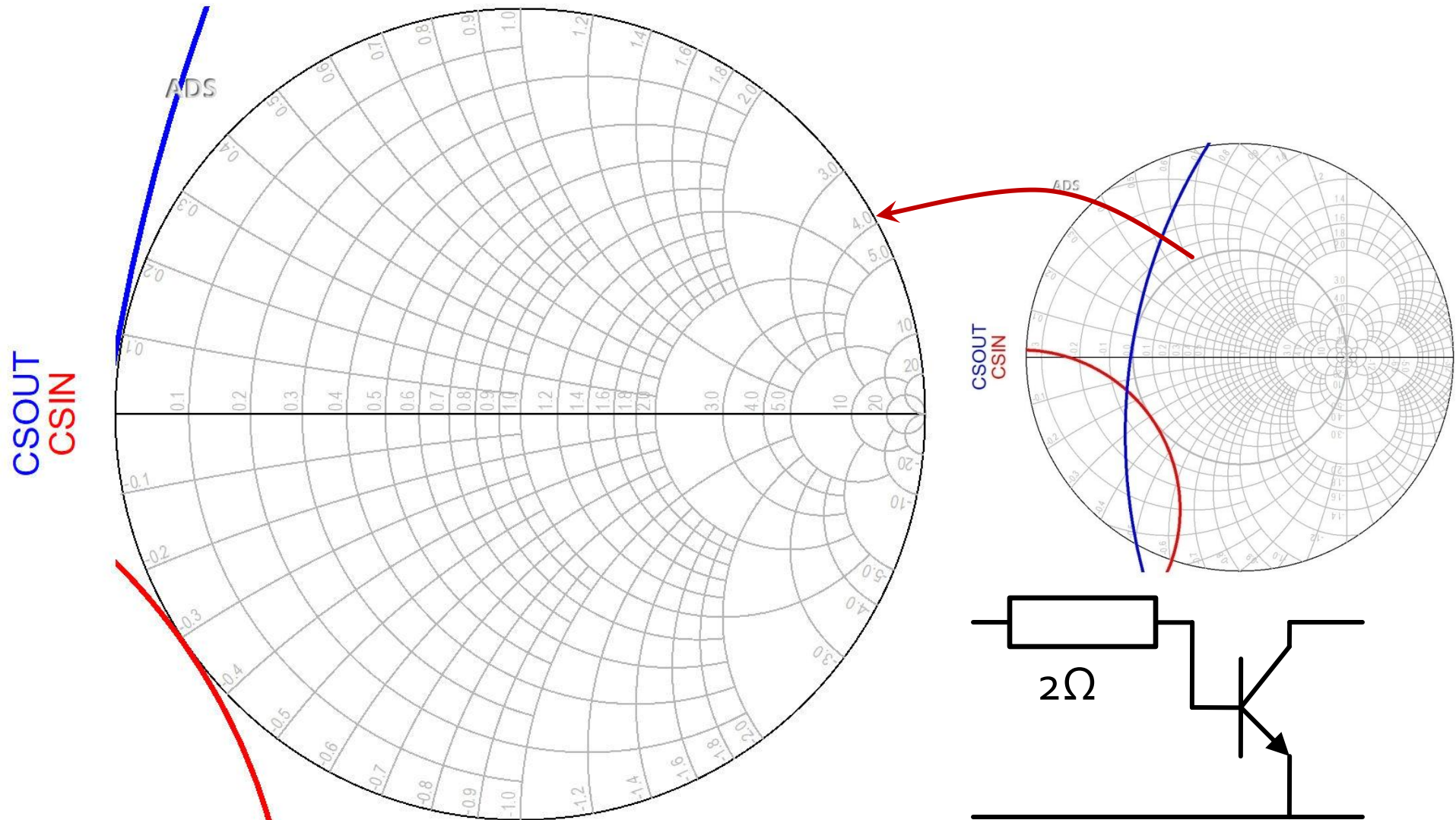


Input series resistor

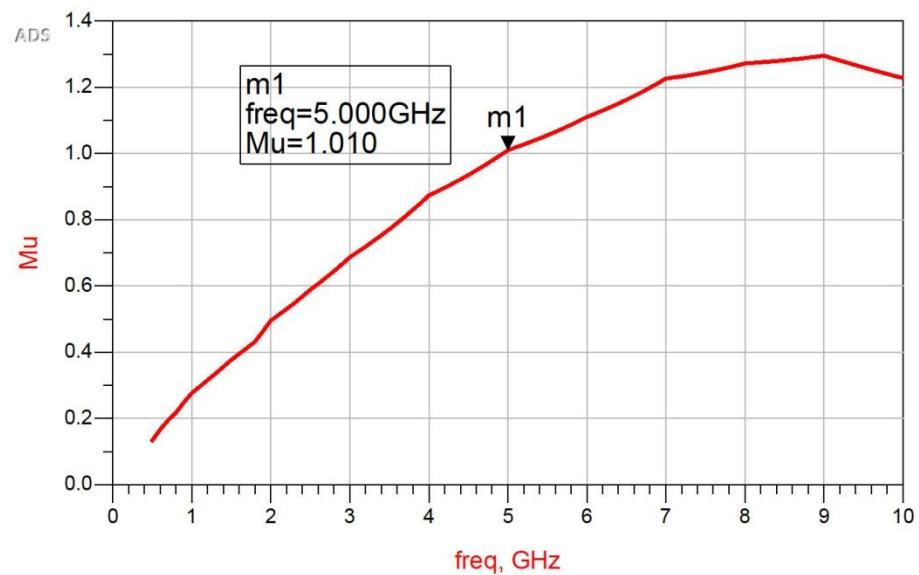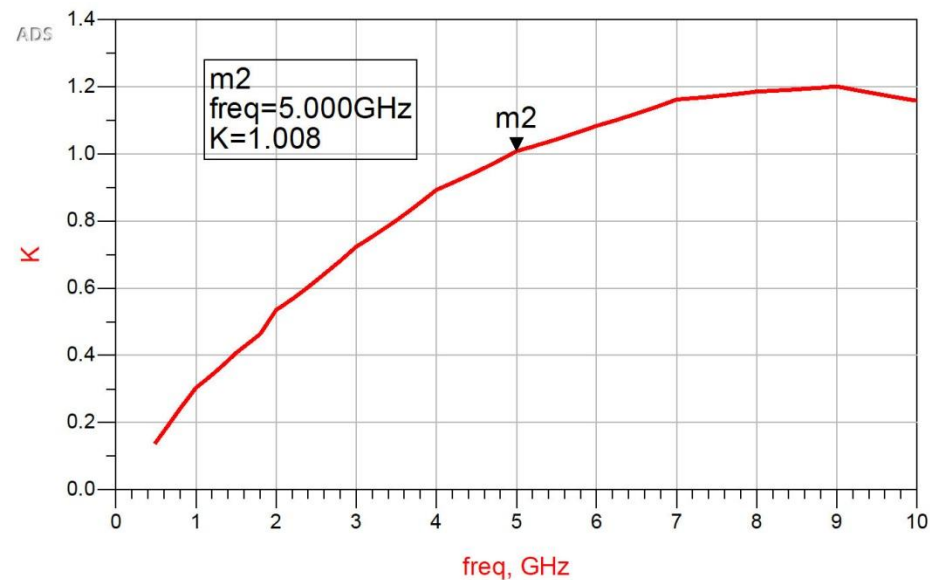- $R_s = 2\Omega$
- $K = 1.008$, $MAG = 13.694\text{dB}$ @ 5GHz
 - no stabilization, $K = 0.886$, $MAG = 14.248\text{dB}$ @ 5GHz



Input shunt resistor

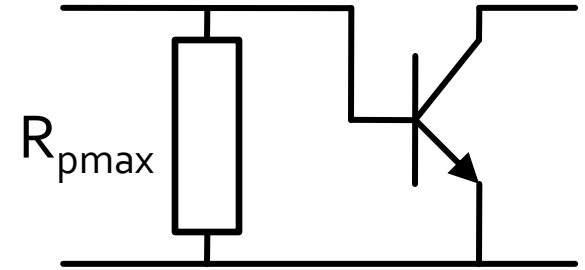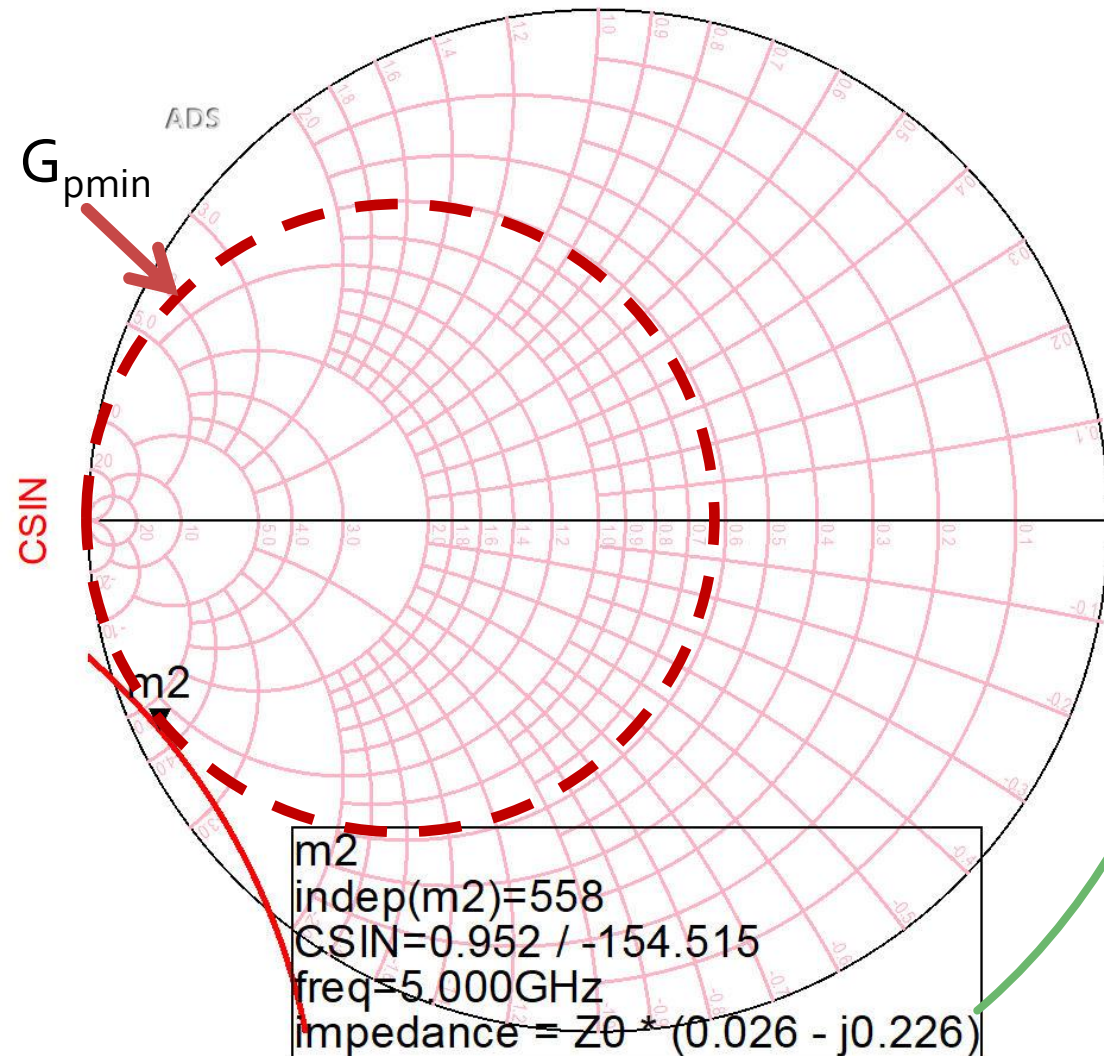

$$R_{pmax} = \frac{1}{G_{pmin}}$$


$$z = 0.026 - j \cdot 0.226$$

$$y = \frac{1}{z} = \frac{1}{0.026 - j \cdot 0.226}$$

$$y = 0.502 + j \cdot 4.367$$



$$R_{pmax} = \frac{50\Omega}{0.502} = 99.6\Omega$$

ADS, $R_p = 90\Omega$

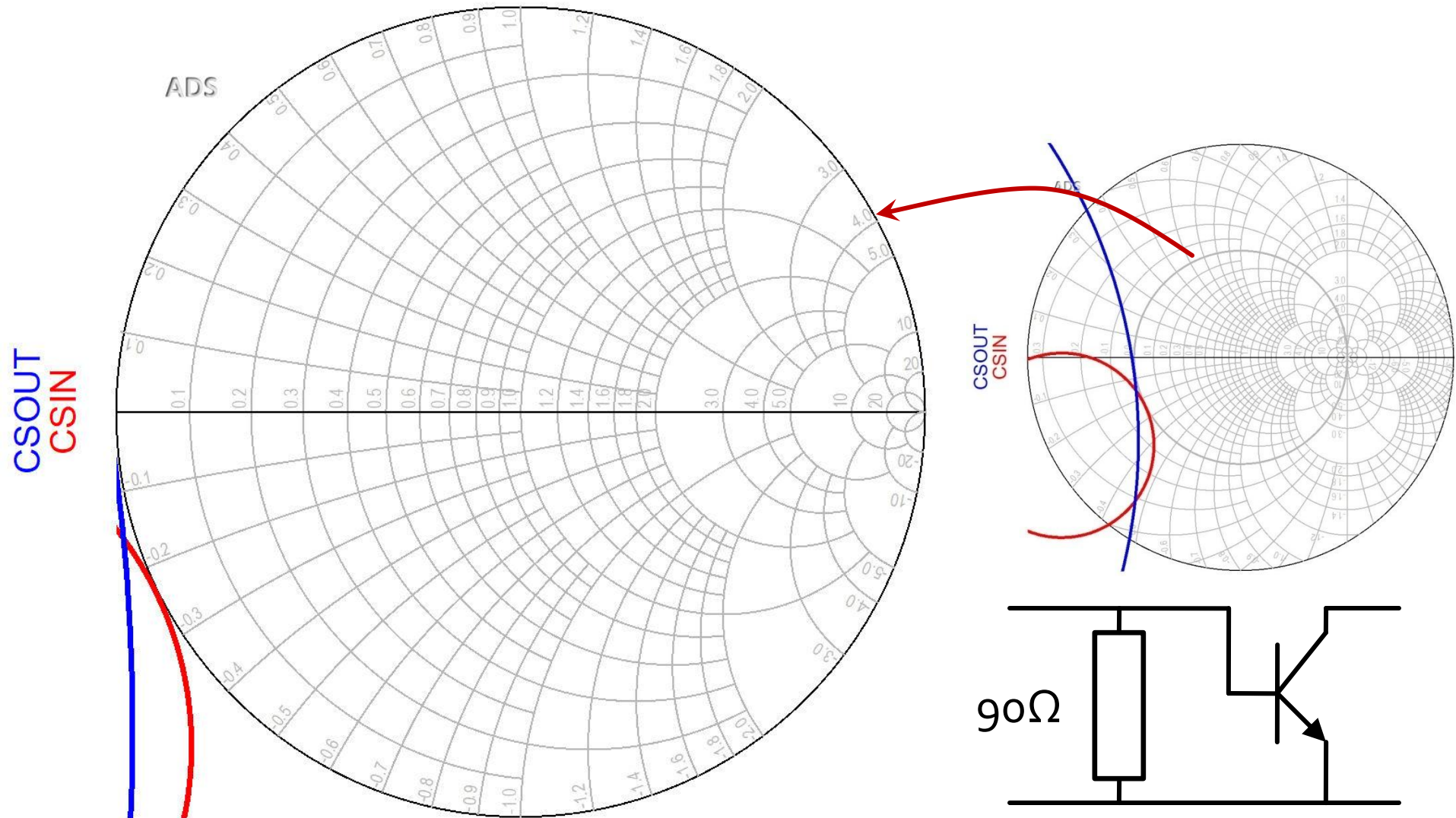



Input shunt resistor

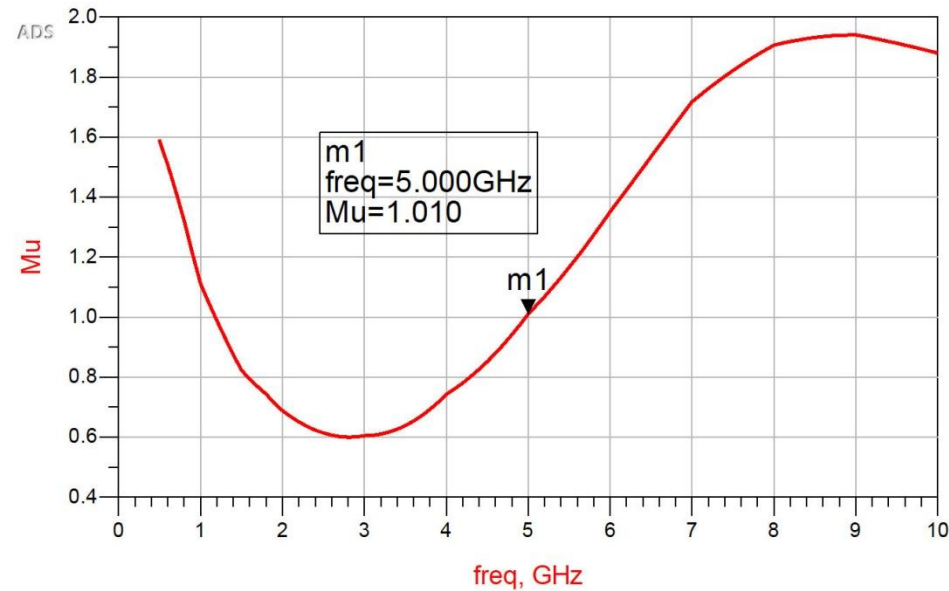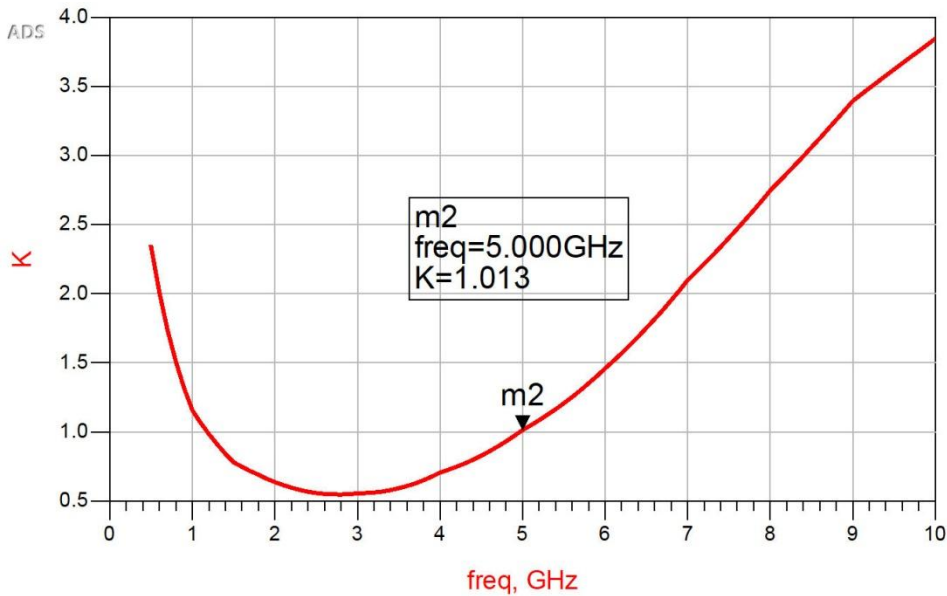- $R_p = 90\Omega$
- $K = 1.013$, $MAG = 13.561\text{dB}$ @ 5GHz
 - no stabilization, $K = 0.886$, $MAG = 14.248\text{dB}$ @ 5GHz



Output series/shunt resistor

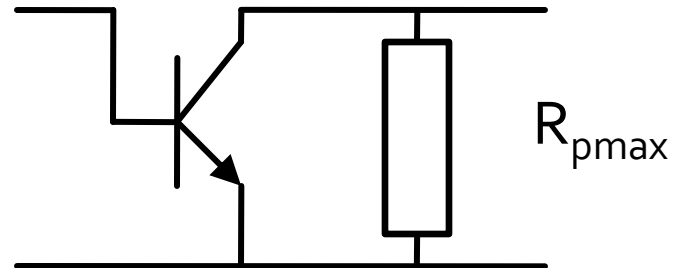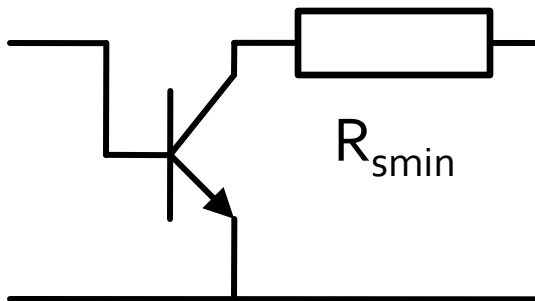
- The procedure can be applied similarly at the output (finding g/r circles tangent to CSOUT)
- From previous examples, resistive loading at the input has a positive effect over output stability and vice versa (resistive loading at the output, effect over input stability)



Stabilization of two-port

- Negative effect over the power gain
 - we must check MAG/MSG while designing resistive loading
- Negative effect over the noise (debated next)
- We can choose one of the 4 possibilities or a combination which offers better results (depending on transistor, application etc.)
- We can use frequency selective loading
 - Ex: RL, RC circuits which sacrifice performance only when needed to improve stability and have no effect at frequencies where the device is already stable
- It might be possible (and should be checked) that stability is improved as an effect of parasitic elements of biasing circuits (bypass capacitors and RF chokes)

Stabilization of two-port

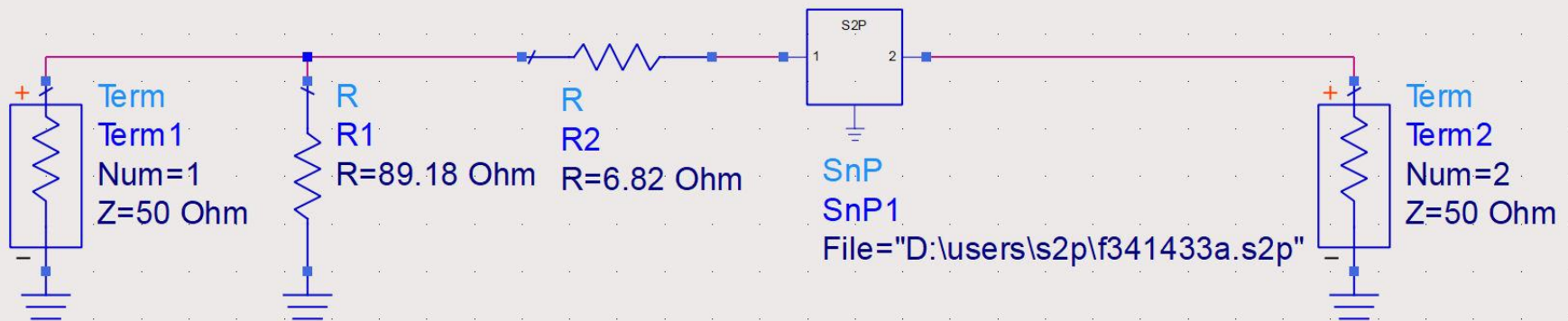

S-PARAMETERS


S_Param

SP1

Start=0.5 GHz

Stop=10.0 GHz

Step=0.1 GHz

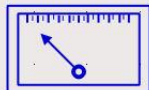


MaxGain

MaxGain

MAG

MAG=max_gain(S)

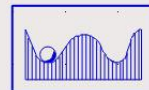


Mu

Mu

Mu1

Mu=mu(S)

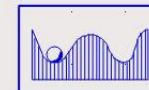



StabFact

StabFact


K

K=stab_fact(S)


Stabilization of two-port

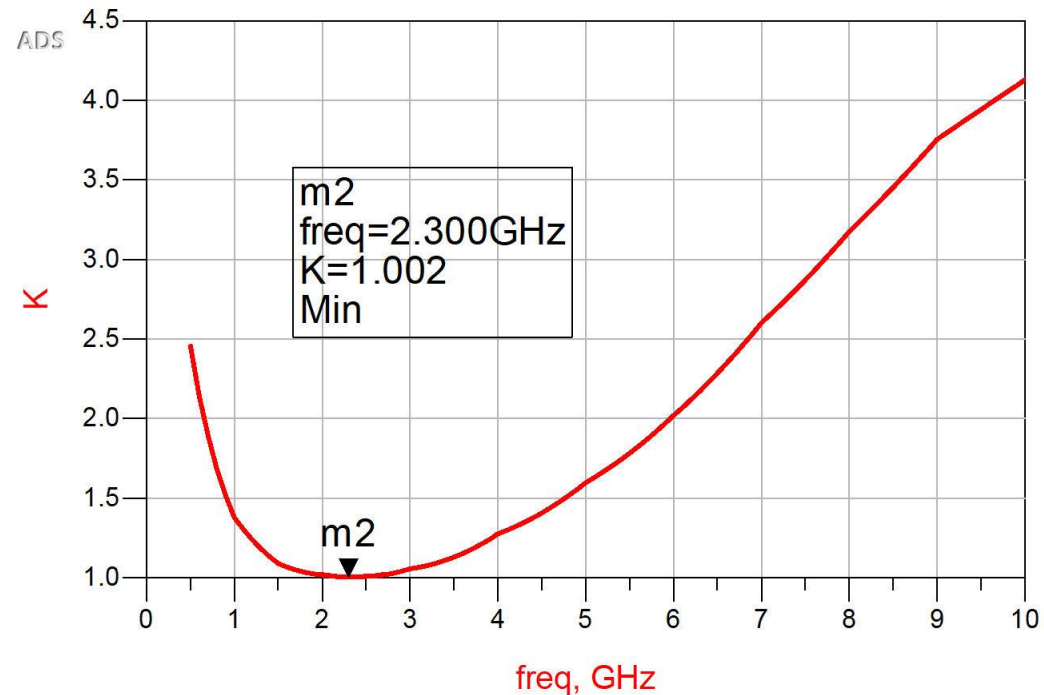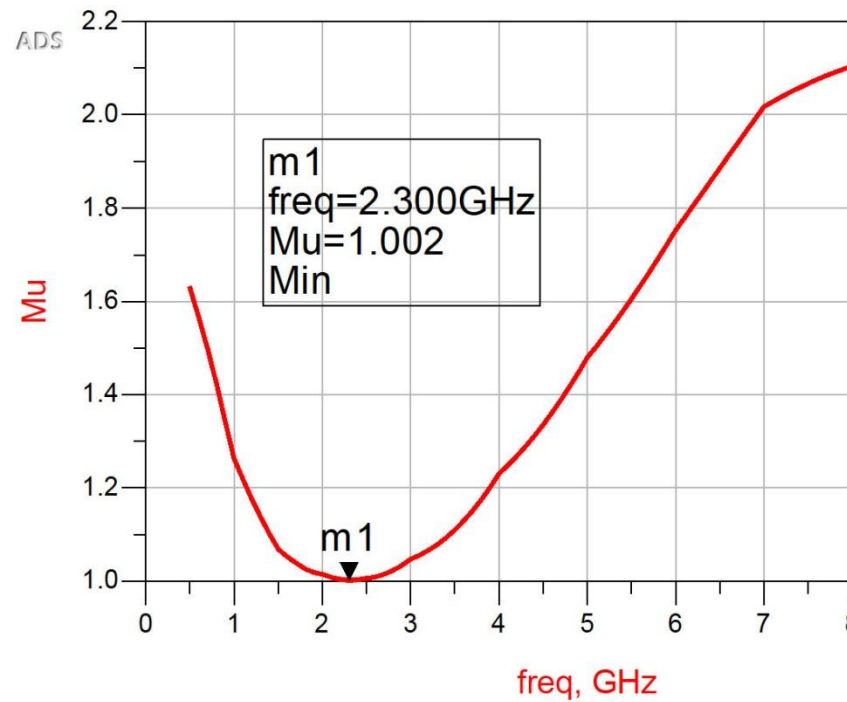

Stabilization of two-port

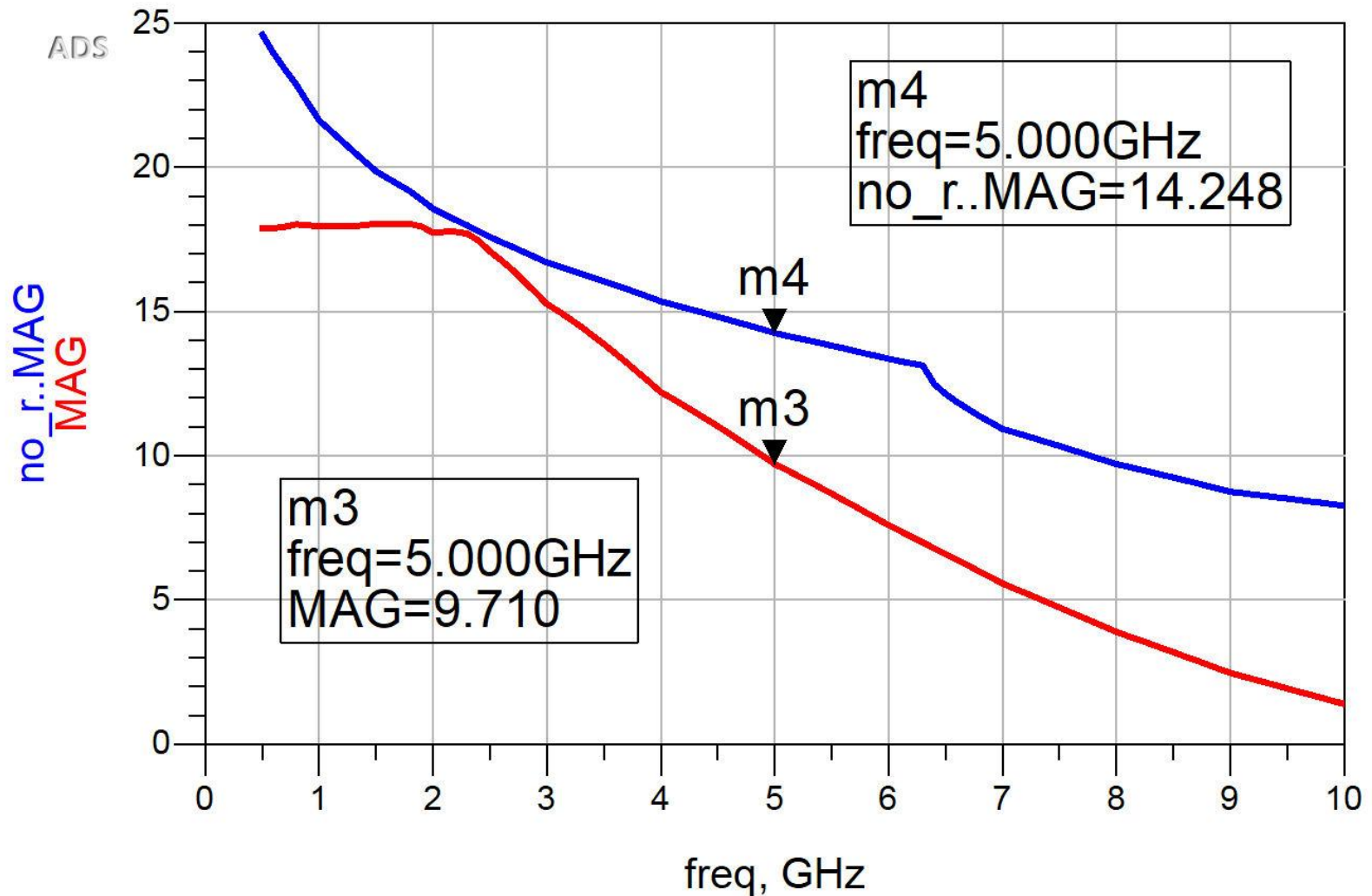


Stabilization of two-port

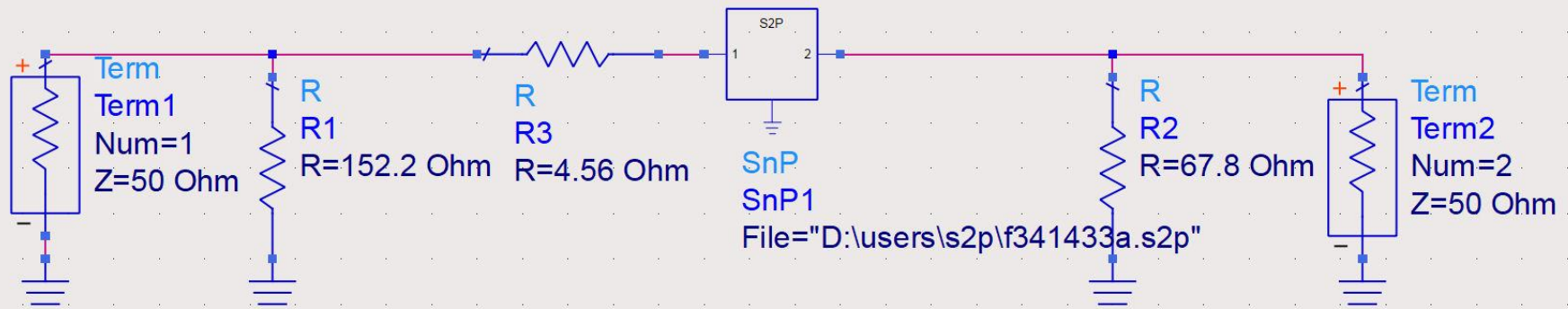


 S-PARAMETERS


S_Param
SP1
Start=0.5 GHz
Stop=10.0 GHz
Step=0.1 GHz

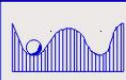 StabFact

StabFact
K
K=stab_fact(S)


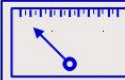
 MaxGain

MaxGain
MAG
MAG=max_gain(S)

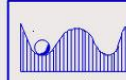
 Mu

Mu
Mu1
Mu=mu(S)

Stabilization of two-port

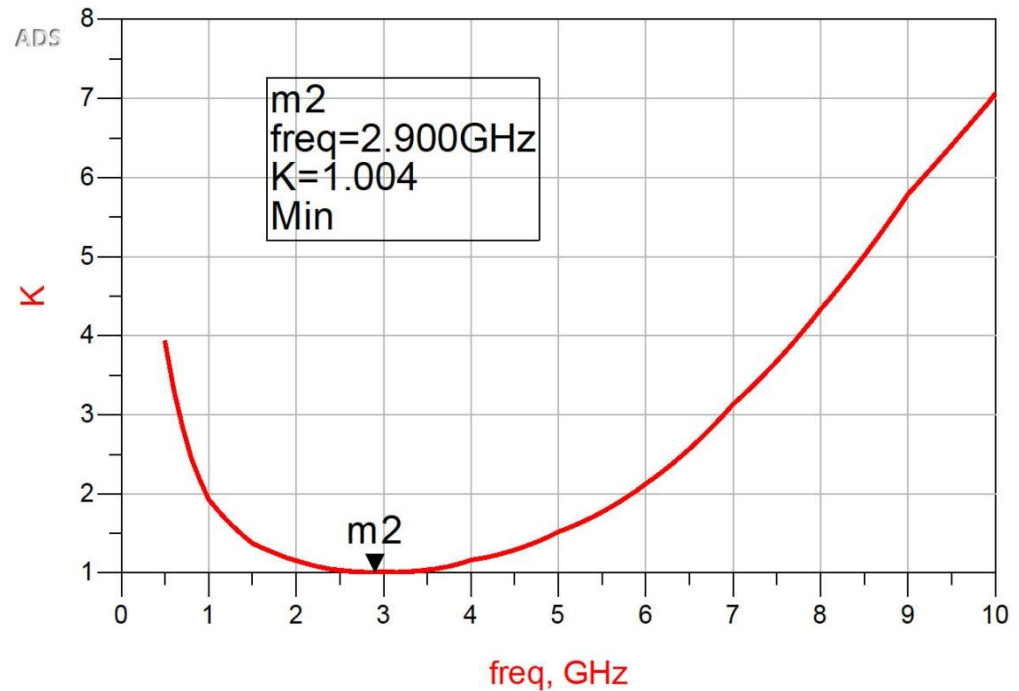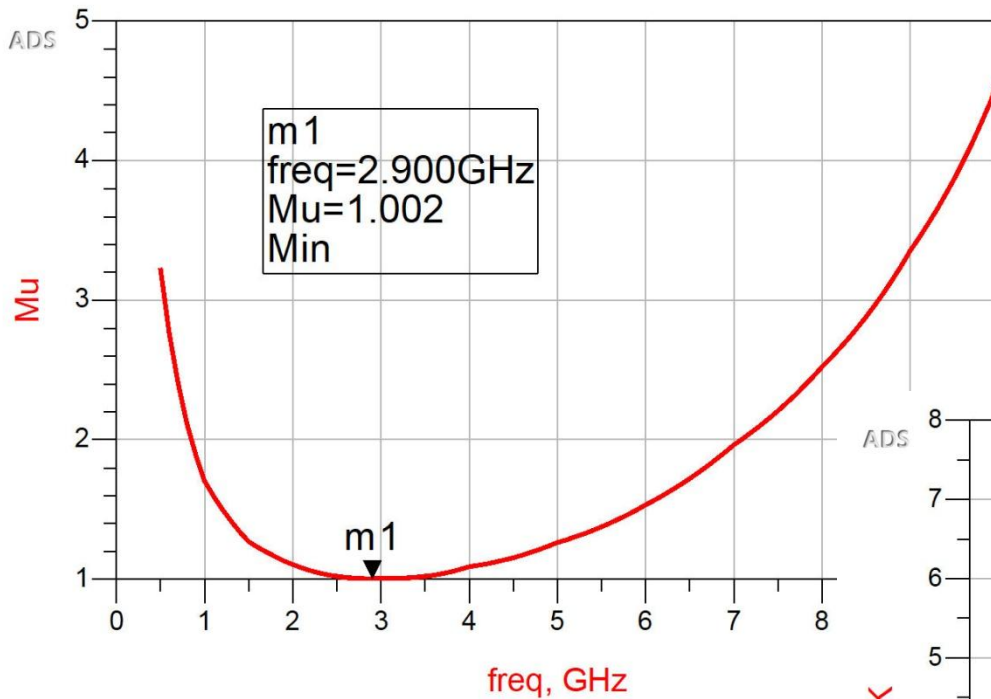

Stabilization of two-port

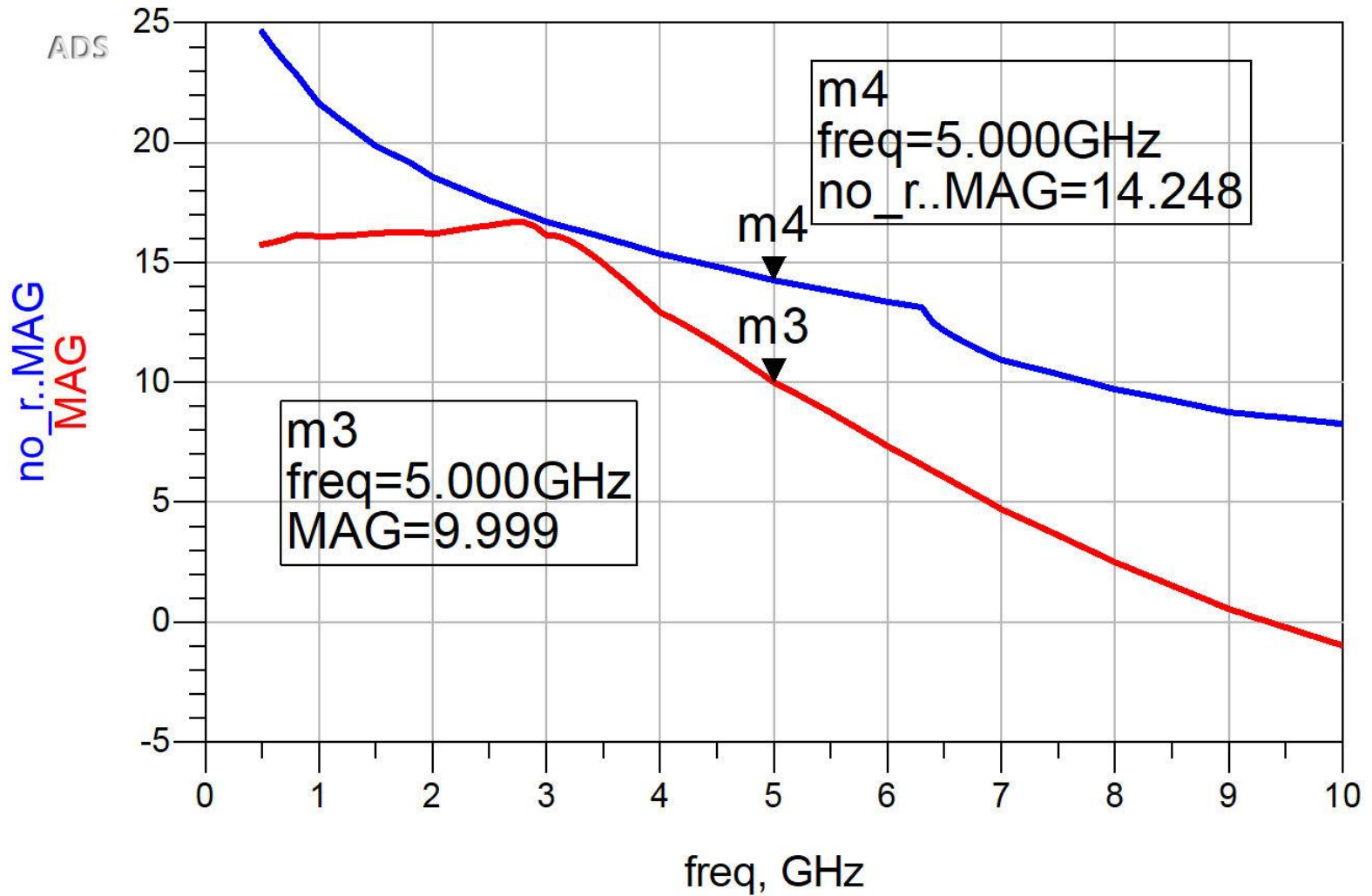

Contact

- Microwave and Optoelectronics Laboratory
- <https://rf-opto.etti.tuiasi.ro>
- rdamian@etti.tuiasi.ro